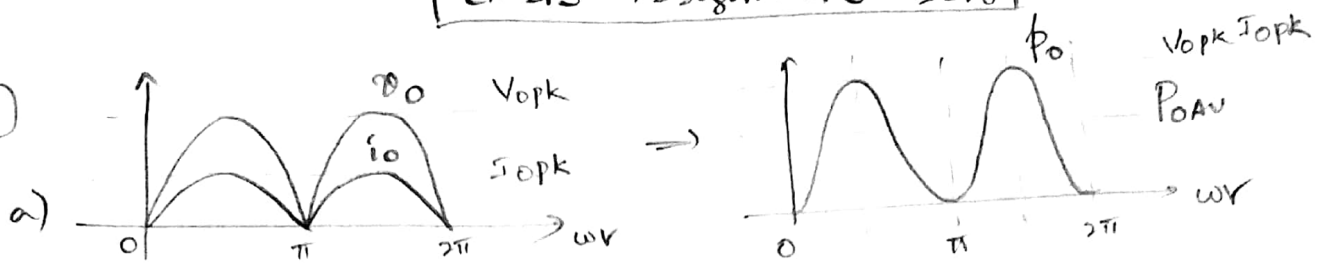


①




Average power dissipated in the resistor =  $\frac{V_{opk} I_{opk}}{2} = \frac{V_{opk}^2}{2R}$


$\Rightarrow \frac{V_{opk}^2}{2R} = 105.8 \text{ W} \Rightarrow V_{opk}^2 = 1058 \Rightarrow V_{opk} = 32.569 \text{ V}$

$\Rightarrow$  RMS voltage across each half of the secondary =  $\frac{V_{opk}}{\sqrt{2}} = 23 \text{ V}$

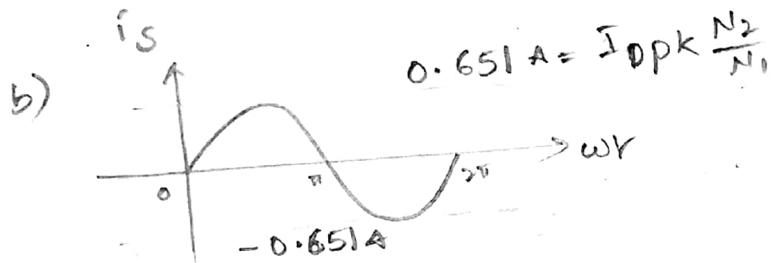$\Rightarrow \frac{N_1}{N_2} = \frac{230}{23} = 10 \text{ (8)} \quad \frac{N_2}{N_1} = \frac{1}{10} \text{ and } I_{opk} = \frac{32.569}{5} = 6.51 \text{ A}$



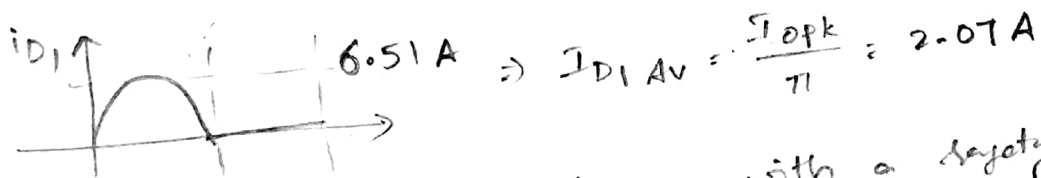
c) PIV =  $2 \times$  Peak voltage across secondary =  $2 \times 32.569 = 65.05 \text{ V}$



[150 V, 5 A] diode is chosen with a safety factor of 2

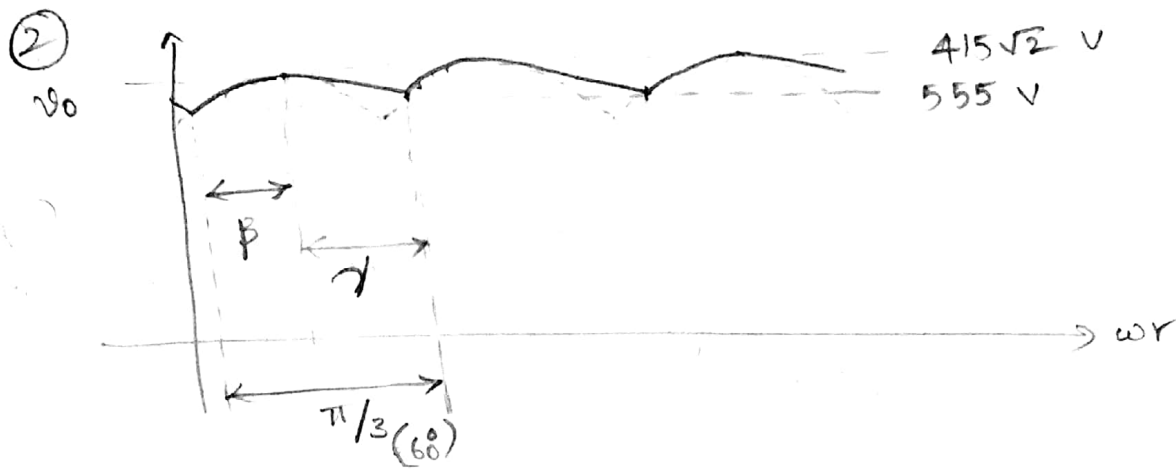d) Loss in each diode =  $I_{D1 AV} \times 0.8 = 1.656 \text{ W}$

Total loss =  $\frac{2 \text{ W}}{\text{Transformer}} + \frac{(2 \times 1.656)}{\text{Diodes}} = 5.312 \text{ W}$



$$\sin^{-1}\left(\frac{555}{415\sqrt{2}}\right) = \sin^{-1}(0.946) = 71.02^\circ$$

$$\Rightarrow \beta = 90^\circ - 71.02^\circ = 18.98^\circ$$

$$\Rightarrow \text{exponential fall time } \Delta t = \frac{(60 - 18.98)}{360} \times 20 \times 10^{-3}$$

$$= 2.28 \text{ ms}$$

Average power delivered to load (resistor)

$$P_{OAV} = \frac{V_{O_{RMS}}^2}{R}$$

For  $0 < \omega\tau < \beta$


$$v_o = V_1 \sin\left[\omega\tau + \left(\frac{\pi}{2} - \beta\right)\right]$$

for  $\beta < \omega\tau < \frac{\pi}{3}$

$$v_o = V_1 - \frac{\Delta V_o}{\Delta t} (t - t_1)$$

$$= V_1 - \frac{\Delta V_o}{\Delta \omega\tau} (\omega\tau - \omega\tau_1)$$
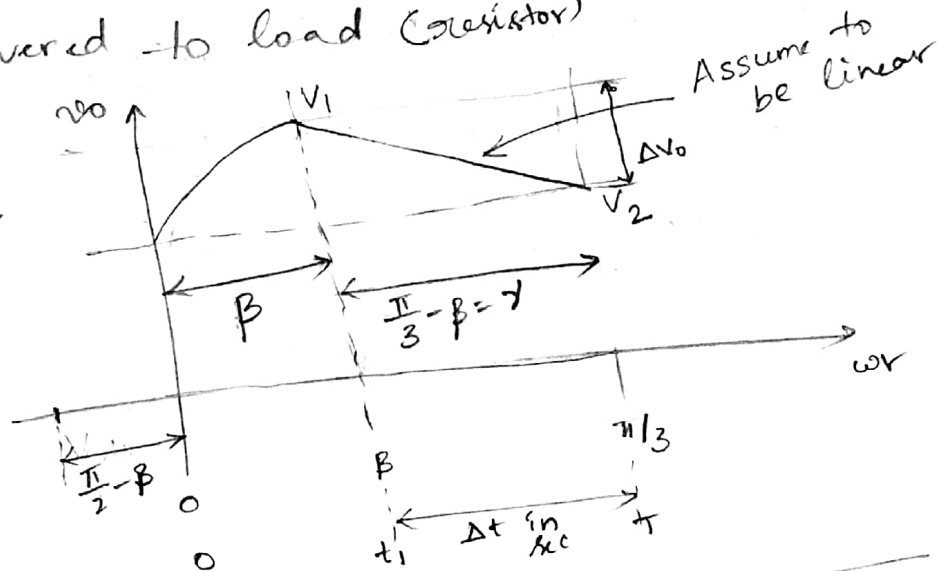
$$= V_1 - \frac{\Delta V_o}{\gamma} (\omega\tau - \beta)$$



$$V_{O_{RMS}} = \sqrt{\frac{1}{T} \int_0^T v_o^2(t) d\tau} = \sqrt{\frac{1}{\pi/3} \int_0^{\pi/3} v_o^2(\omega\tau) d\omega\tau}$$

$$\int_0^{\beta} v_o^2(\omega\tau) d\omega\tau = \int_0^{\beta} V_1^2 \cos^2(\omega\tau - \beta) d\omega\tau = V_1^2 \int_0^{\beta} \frac{1 + \cos(2\omega\tau - 2\beta)}{2} d\omega\tau$$

$$= \frac{V_1^2}{2} \left[ \beta + \left( \frac{\sin(2\omega\tau - 2\beta)}{2} \right) \Big|_0^{\beta} \right]$$

$$= \frac{V_1^2}{2} \left( \beta + \frac{\sin 2\beta}{2} \right) \rightarrow \text{A1}$$

$$\int_{\beta}^{\pi/3} v_0^2(\omega t) d\omega t = \frac{1}{3} \Delta \omega t (V_1^2 + V_2^2 + V_1 V_2)$$

$$\beta = \frac{1}{3} \left( \frac{\pi}{3} - \beta \right) (V_1^2 + V_2^2 + V_1 V_2) \rightarrow (A_2)$$

$$V_{RMS} = \sqrt{\frac{3}{\pi} \int_0^{\pi/3} v_0^2(\omega t) d\omega t} = \sqrt{\frac{3}{\pi} (A_1 + A_2)}$$

$$\begin{aligned} V_1 &= 415\sqrt{2} = 586.9 \text{ V} \\ V_2 &= 555 \text{ V} \\ \Delta V_0 &= 31.9 \text{ V} \\ \gamma &= \frac{41.02 \times \pi}{180} = 0.72 \\ \beta &= \frac{18.98 \times \pi}{180} = 0.33 \\ \sin 2\beta &= 0.3252 \\ \sin 2\beta &= 0.615 \\ \cos \beta &= 0.946 \end{aligned}$$

$$(A_1) = \frac{V_1^2}{2} \left( \beta + \frac{\sin 2\beta}{2} \right) = \frac{415^2 \times 2}{2} (0.33 + 0.31) = 110224$$

$$(A_2) = \frac{1}{3} \gamma (V_1^2 + V_2^2 + V_1 V_2) = \frac{1}{3} \times 0.72 ((415\sqrt{2})^2 + 555^2 + 415\sqrt{2} \times 555) = 234769$$

$$\Rightarrow V_{RMS} = 573.97 \text{ V}$$

$$P_{OAV} = \frac{V_{RMS}^2}{R} \Rightarrow 8000 = \frac{573.97^2}{R} \Rightarrow R = 41.18 \Omega$$

Calculation of the value of 'C' - by energy balance

change in energy stored in the capacitor ( $\Delta E_{cap}$ )

= energy consumed by the load resistor ( $E_{load}$ )

} During voltage fall


$$\frac{1}{2} C (V_1^2 - V_2^2) = \frac{1}{3} \Delta t \frac{(V_1^2 + V_2^2 + V_1 V_2)}{R}$$

$$\Rightarrow \frac{1}{2} C [(415\sqrt{2})^2 - 555^2] = \left[ \frac{1}{3R} \right] \times 2.28 \times 10^{-3} \times ((415\sqrt{2})^2 + 555^2 + 555 \times 415\sqrt{2})$$

$$\Rightarrow RC = 0.0408 \text{ sec}$$

$$R = 41.18 \Omega$$


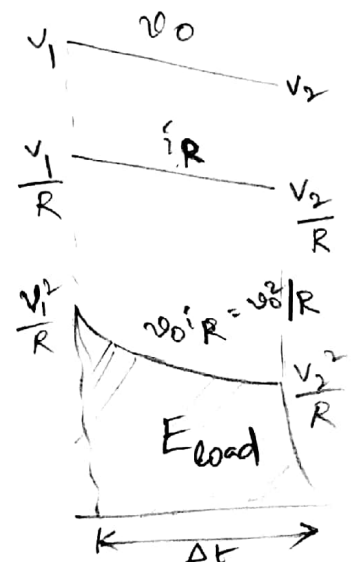
$$\Rightarrow C = 990.8 \mu\text{F} = 0.9908 \text{ mF}$$



$$= \frac{\gamma}{2\pi} \times 20 \text{ ms}$$

$$= \frac{41.02}{360} \times 20 \times 10^{-3} = 2.28 \text{ ms}$$

Peak input current

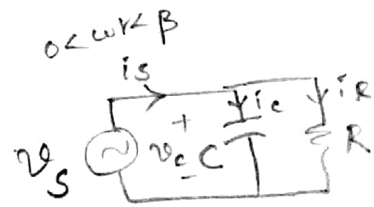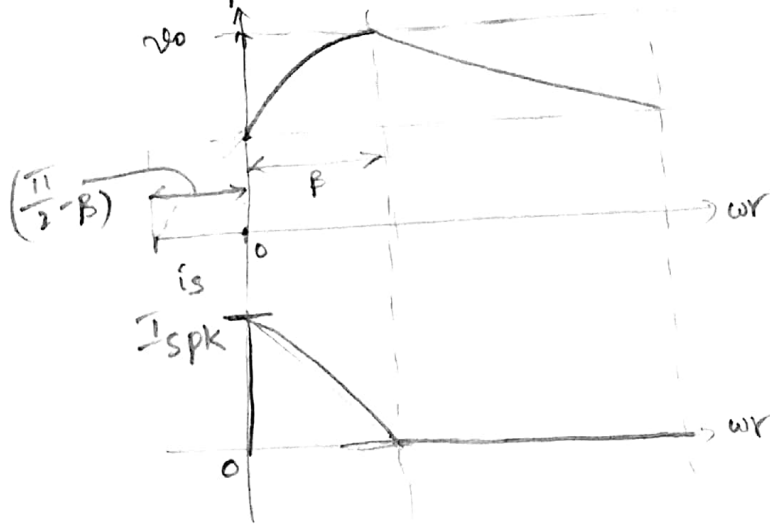

$$i_s = i_c + i_r$$

$$= C \frac{dv_s}{dt} + \frac{v_s}{R}$$


$$= \omega C V_1 \cos\left[\omega\tau + \left(\frac{\pi}{2} - \beta\right)\right] + \frac{V_1 \sin\left[\omega\tau + \left(\frac{\pi}{2} - \beta\right)\right]}{R}$$



At  $\omega\tau = 0$ ,  $i_s = I_{spk}$

$$\Rightarrow I_{spk} = \omega C V_1 \sin\beta + \frac{V_1 \cos\beta}{R}$$


$$I_{spk} = (2\pi \times 50 \times 990.8 \times 10^{-6} \times 415\sqrt{2} \times 0.8252) + \left( \frac{415\sqrt{2} \times 0.946}{41.18} \right) = 72.9 A$$

Simulated circuit:

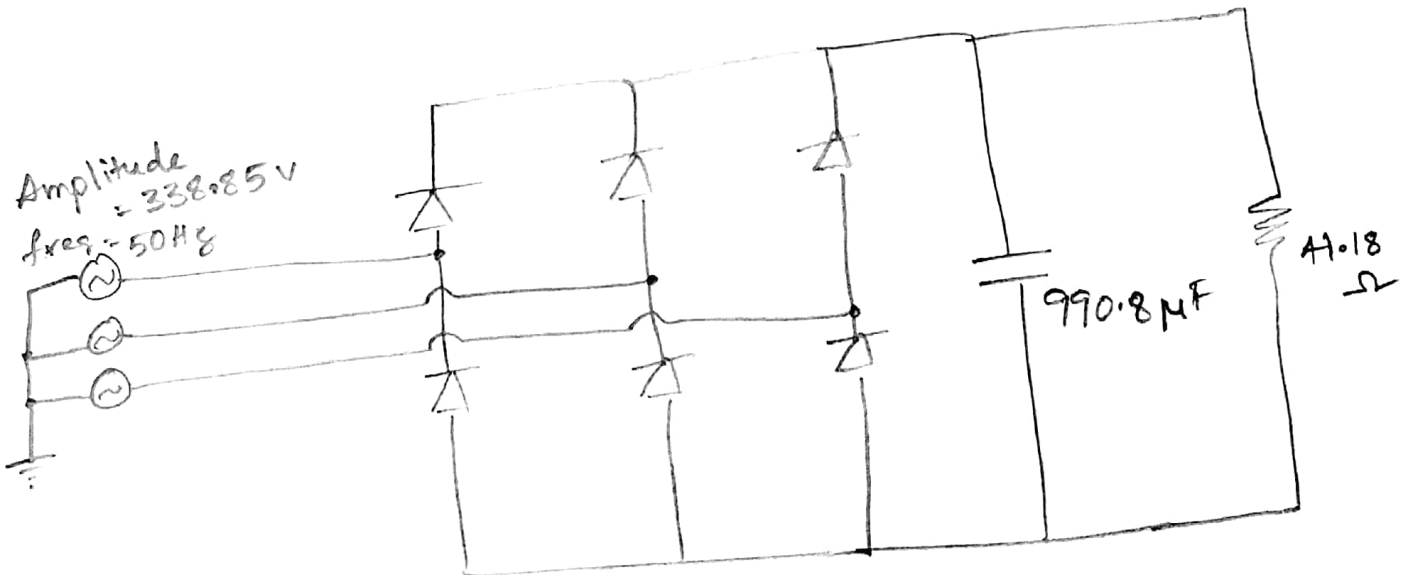

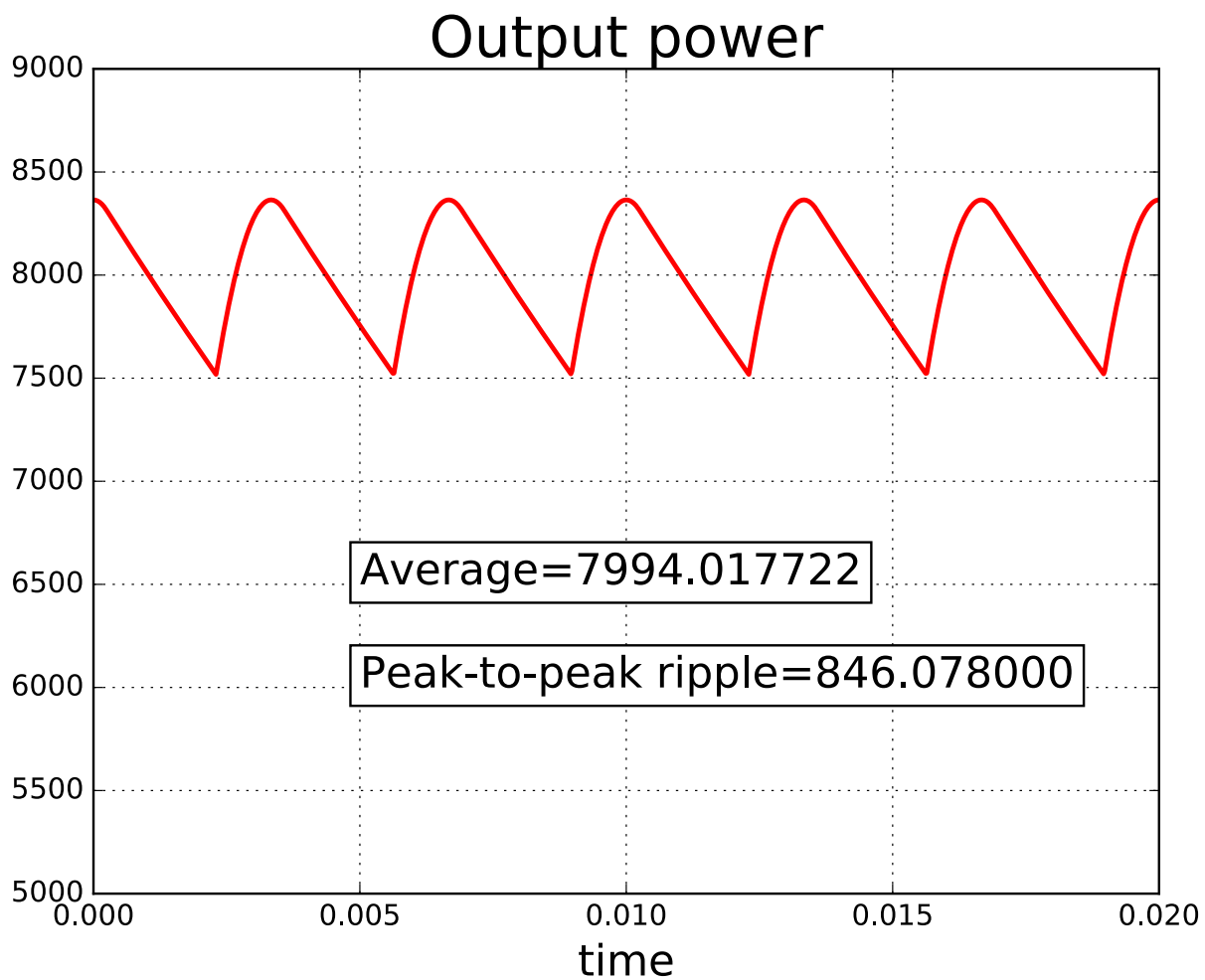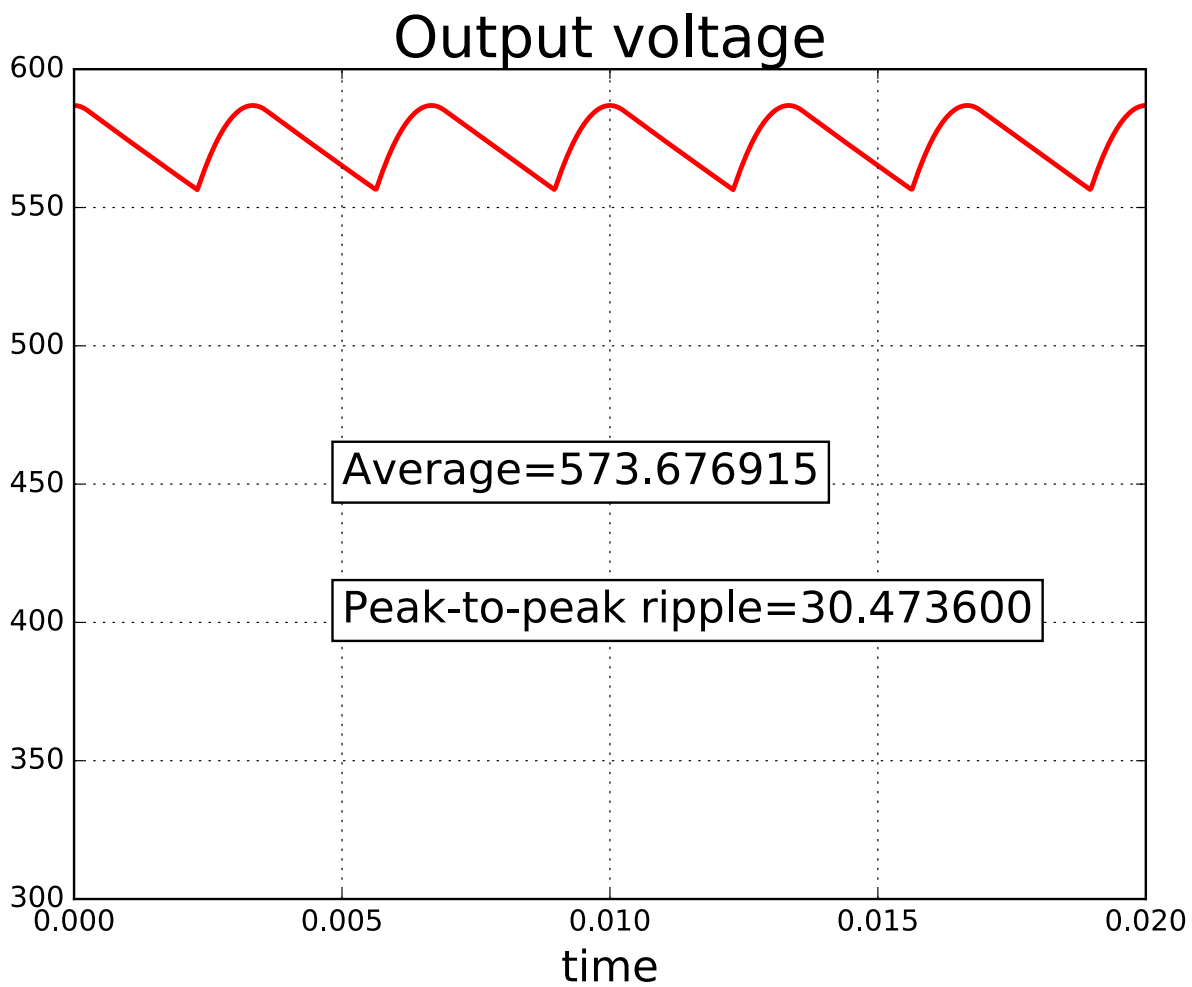

# Input voltage and current

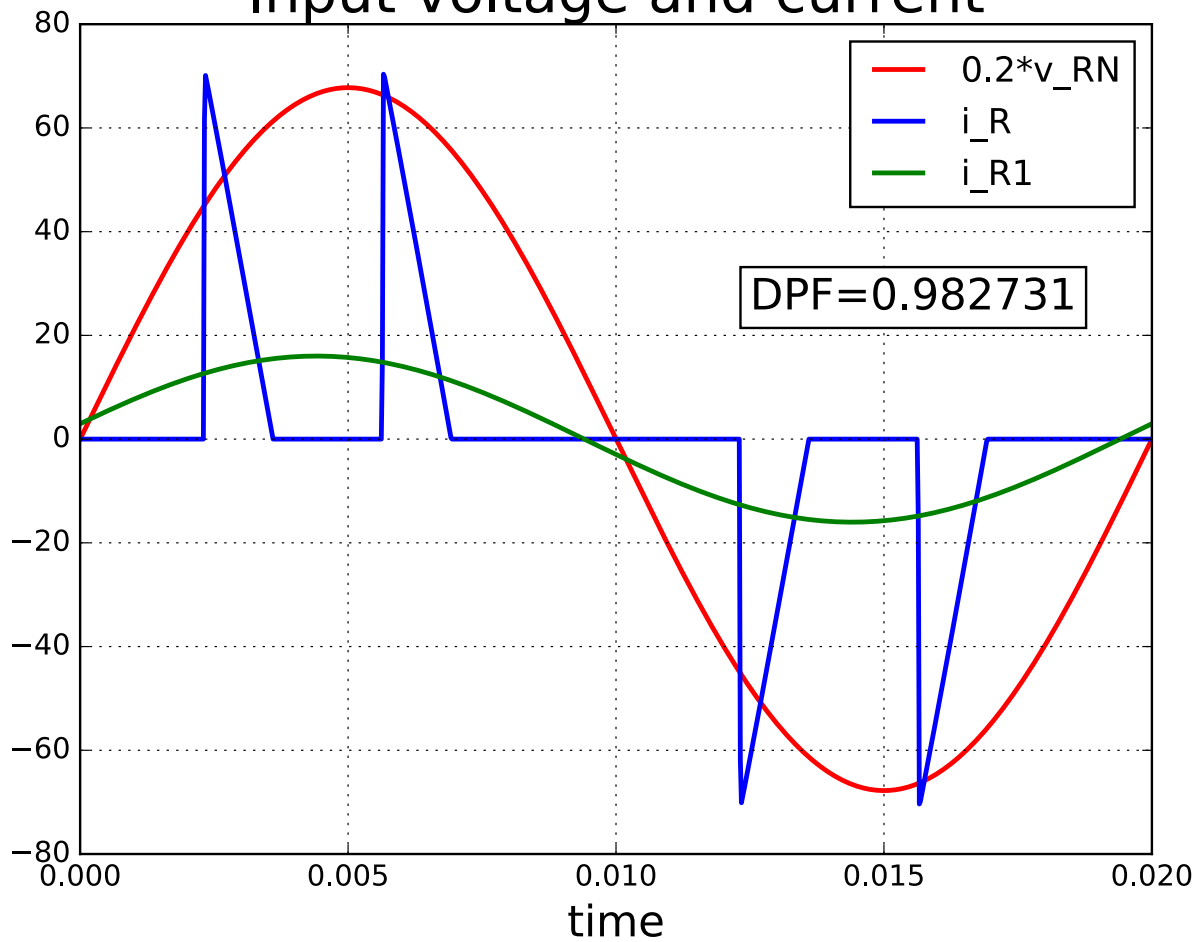

# Harmonic spectrum of input current

