
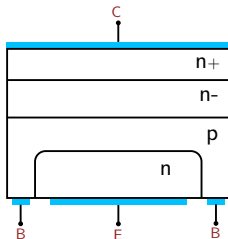




Fully-controlled power semiconductor switches

n-p-n Bipolar Junction Transistor (BJT)

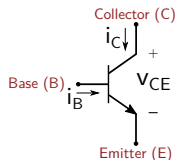



Minority carrier device
Conduction is due to
flow of electrons and holes

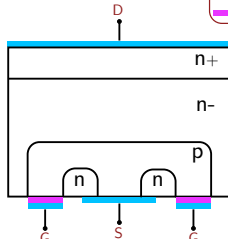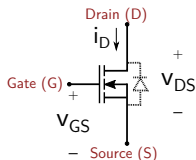n-channel enhancement-mode
Metal Oxide Semiconductor
Field Effect Transistor (MOSFET)



Majority carrier device
Conduction is primarily due to
flow of electrons

Insulated Gate Bipolar Transistor (IGBT)

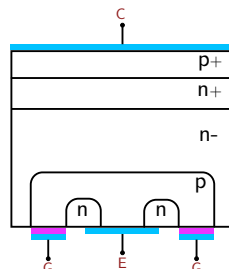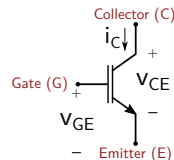


Minority carrier device
Conduction is due to
flow of electrons and holes




Fully-controlled power semiconductor switches




n-p-n Bipolar Junction Transistor (BJT)

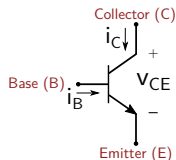

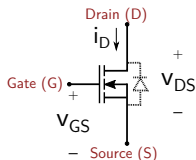n-channel enhancement-mode
Metal Oxide Semiconductor
Field Effect Transistor (MOSFET)




Insulated Gate Bipolar Transistor (IGBT)

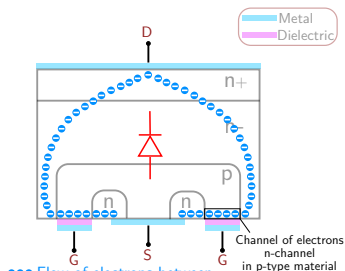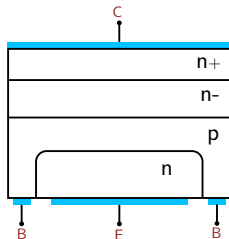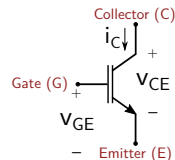

Flow of electrons between source and drain when V_{GS} is +ve

Body-diode of a MOSFET


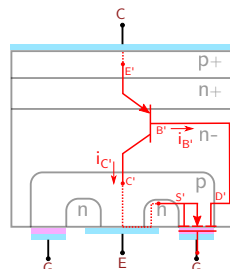


IGBT can be viewed as a MOSFET driving a p-n-p BJT





Fully-controlled power semiconductor switches

BJT

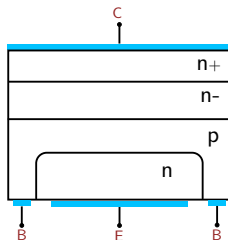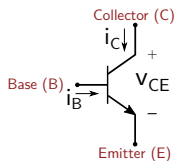



Can conduct only in one direction (C to E)
B-E junction should be forward-biased for conduction

MOSFET

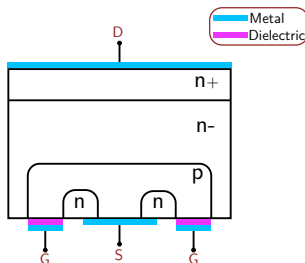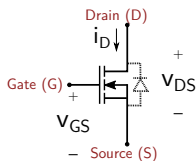

Can conduct in both directions
With positive v_{GS} , electrons can flow from D to S or S to D

IGBT

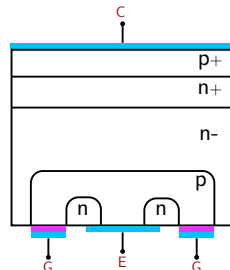
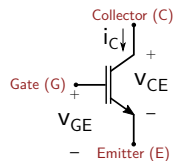


Can conduct only in one direction (C to E)
The p-n-p transistor can conduct only in one direction





Fully-controlled power semiconductor switches

BJT

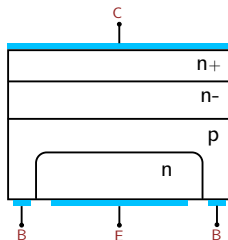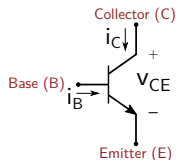

Can only block positive v_{CE}
 Base is thin and lightly doped
 Emitter is heavily doped
 B-E junction breaks down
 at very low negative voltages



MOSFET

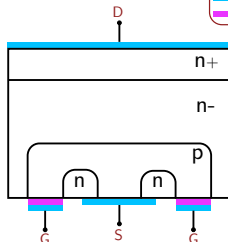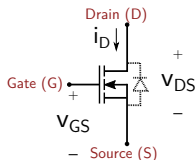

Can only block positive v_{DS}

Body diode conducts
 for negative v_{DS}

IGBT

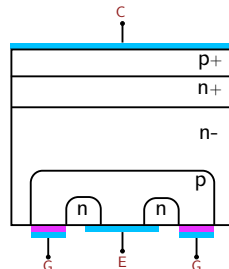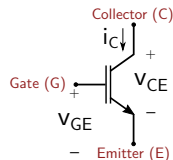



Can block v_{CE} in either direction

Reverse-blocking capability depends on
 the breakdown voltage of
 the p+ / n+ junction





Fully-controlled power semiconductor switches



BJT

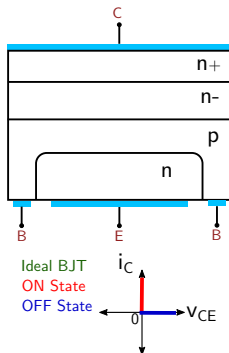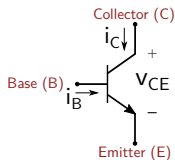



MOSFET

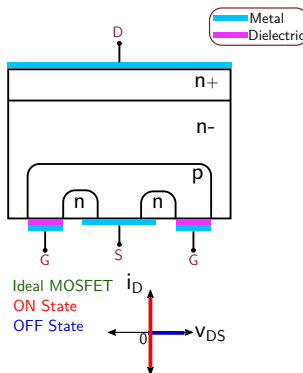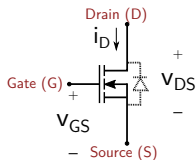

IGBT

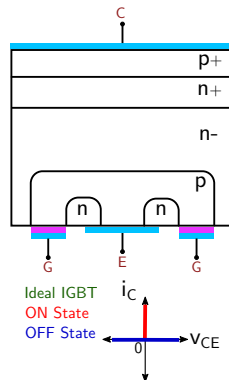
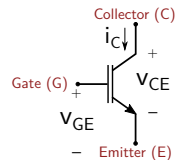


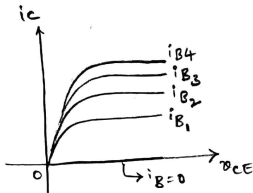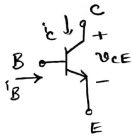Fully-controlled power semiconductor switches



$$i_{B4} > i_{B3} > i_{B2} > i_{B1}$$



current-controlled device

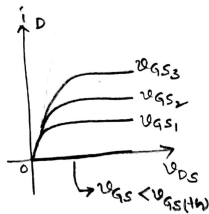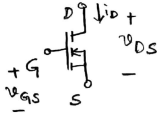

$$v_{GS3} > v_{GS2} > v_{GS1} > v_{GS(th)}$$

voltage-controlled device

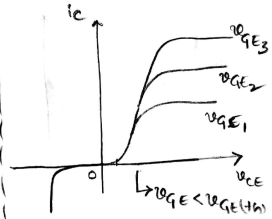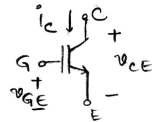MOSFET can be modeled as a resistor in the ON state $\Rightarrow R_{DS(on)}$




$$v_{GE3} > v_{GE2} > v_{GE1} > v_{GE(th)}$$

voltage-controlled device




Estimation of switching loss

Switching resistive load

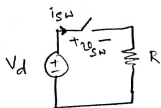

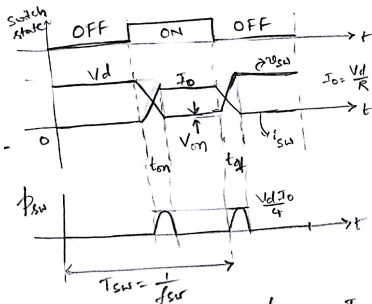
current-rise & voltage-fall occur simultaneously during turn-ON




$$P_{sw} = \text{Average of } p_{sw} \text{ over } T_{sw}$$

$$= \frac{1}{6} V_d I_o (t_{on} + t_{off}) f_{sw}$$

Switching inductive load (diode-clamped)

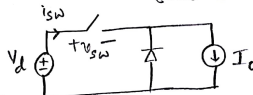


More losses

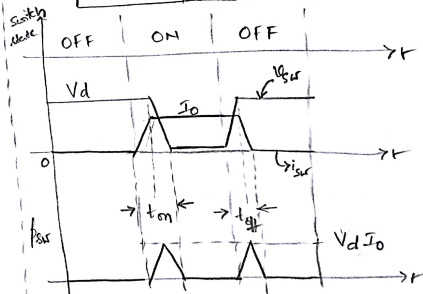

$$P_{sw} = \frac{1}{2} V_d I_o (t_{on} + t_{off}) f_{sw}$$

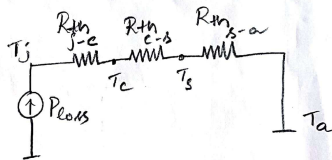current-rise is followed by voltage-fall during turn-on





$$T_j - T_a = P_{loss} \left[R_{thj-c} + R_{thc-s} + R_{ths-a} \right]$$

\downarrow \downarrow \swarrow

Thermal resistance of semiconductor Thermal resistance of the interface material between device & heat sink Thermal resistance of heat sink

R_{th-s-a} is lowered by using fan [forced-air cooling].

Module 3: Summary

- ▶ Fully-controlled switches: BJT, MOSFET and IGBT
- ▶ Estimation of switching loss in case of resistive load and diode-clamped inductive load
- ▶ Thermal model of a power semiconductor switch

