
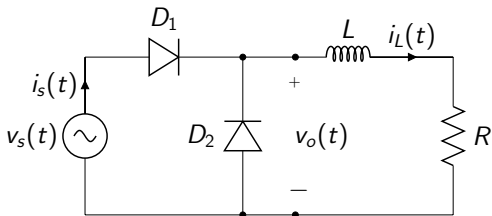
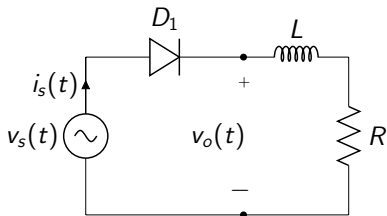
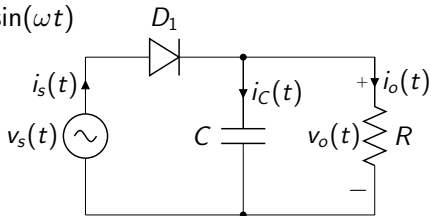




Single-phase half-wave (1-pulse) rectifiers

$$v_s(t) = V_m \sin(\omega t)$$

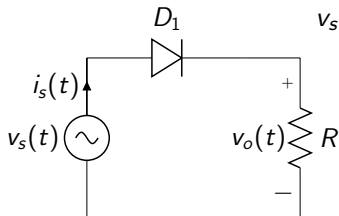

1-ph half-wave rectifier [(R-L load) / (L-filter and R-load)]

Waveforms in periodic steady state

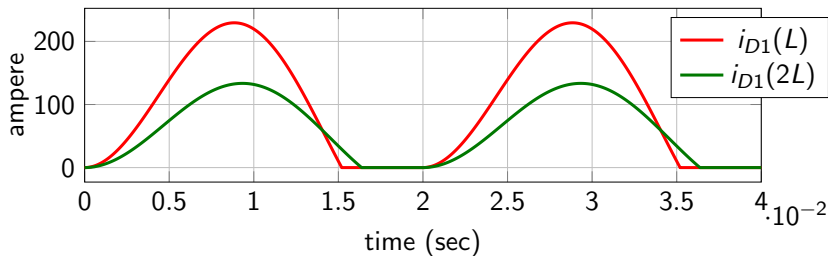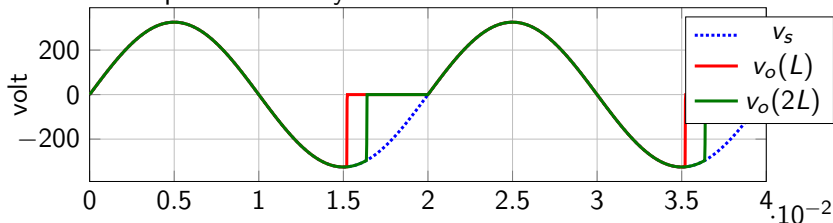


$$v_s = 230\sqrt{2} \sin(2\pi \cdot 50 \cdot t) \text{ V}, R=0.5\Omega, L=6.5\text{mH}, i_{D1} = i_s$$



1-ph half-wave rectifier (Free-wheeling diode, L-filter and R-load)

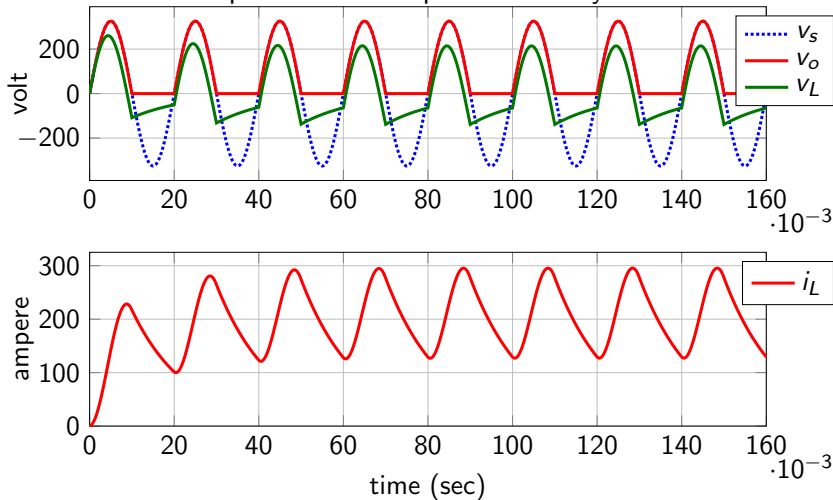Waveforms: Start-up transient and periodic steady state




$$v_s = 230\sqrt{2}\sin(2\pi \cdot 50 \cdot t)\text{V}, R=0.5\Omega, L=6.5\text{mH}, i_{D1} = i_s, v_L: \text{voltage across } L$$



1-ph half-wave rectifier (Free-wheeling diode, L-filter and R-load)

Waveforms in periodic steady state


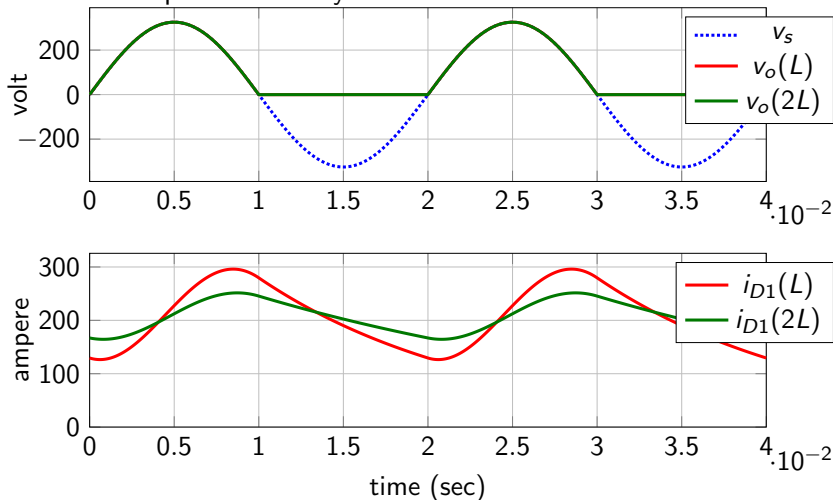


$$v_s = 230\sqrt{2}\sin(2\pi \cdot 50 \cdot t)\text{V}, R=0.5\Omega, L=6.5\text{mH}, i_{D1} = i_s \quad \text{Diode currents?}$$



1-ph half-wave rectifier (Capacitive filter and R load)

Waveforms in periodic steady state

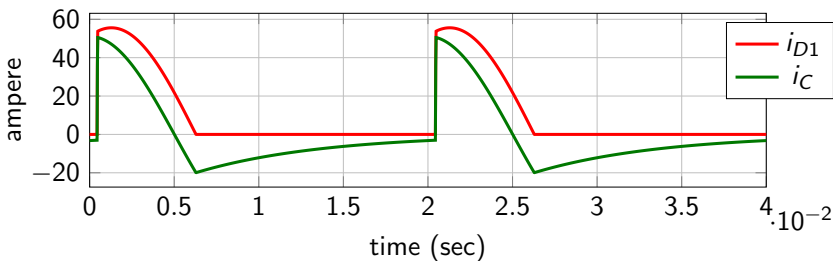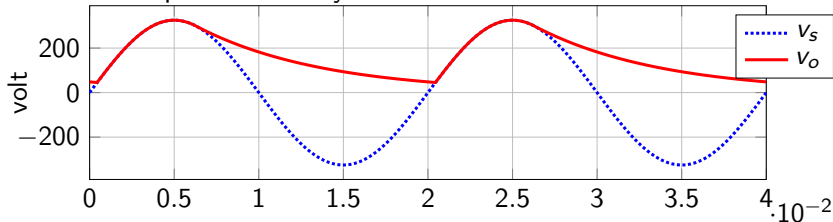


$$v_s = 230\sqrt{2}\sin(2\pi \cdot 50 \cdot t)\text{V}, R=15\Omega, C=0.5\text{mF}, i_{D1} = i_s$$



1-ph half-wave rectifier (Capacitive filter and R-load)


Waveforms in periodic steady state

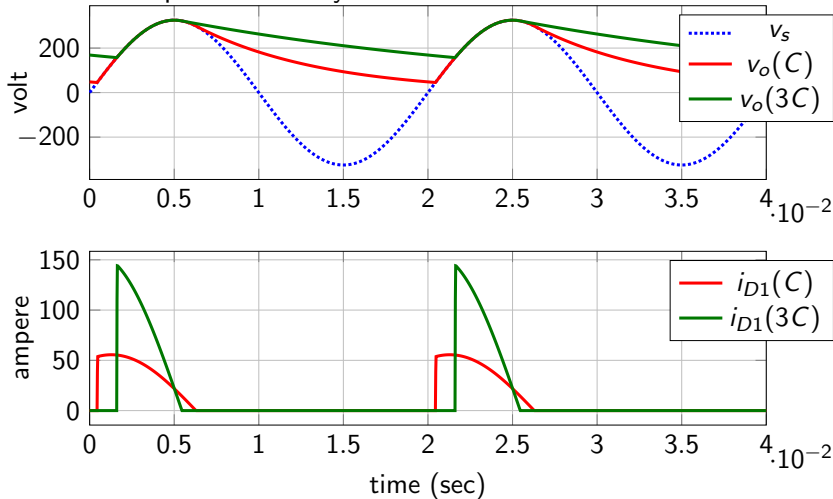


$$v_s = 230\sqrt{2} \sin(2\pi \cdot 50 \cdot t) \text{ V}, R=15\Omega, C=0.5\text{mF}, i_{D1} = i_s \quad \text{! } i_s \text{ vs } i_o!$$




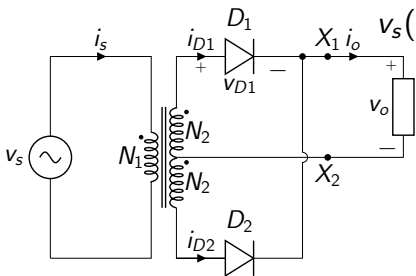
Single-phase full-wave (2-pulse) rectifiers



1-ph full-wave 2-diode rectifier


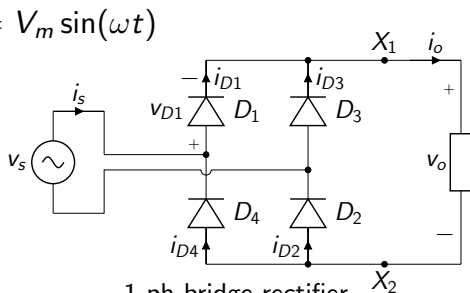


1-ph bridge rectifier



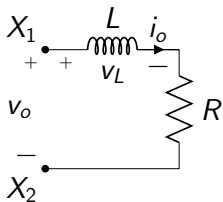
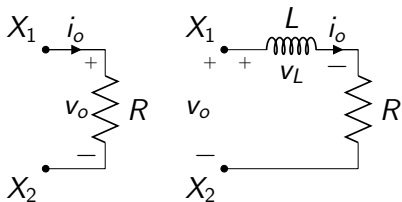


R with high L

$\omega L \gg R$

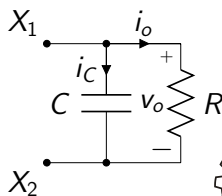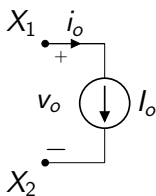

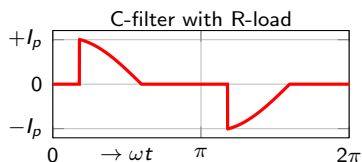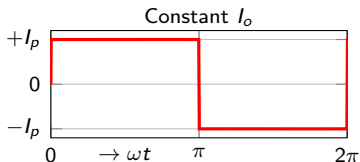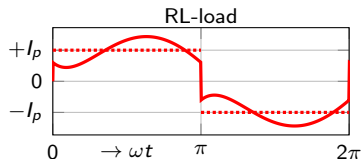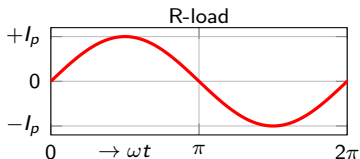1-ph full-wave rectifier: Waveforms of input current $i_s(t)$







Waveforms of $i_s(t)$ are the same for full-wave bridge rectifier and full-wave 2-diode rectifier (with $N_1 = N_2$ and ideal transformer)

Load type	I_p
R-load	$\frac{V_m}{R}$
RL-load	$\frac{2V_m}{\pi R}$
Const I_o	I_o
C-filter with R-load	$\frac{V_m}{R} \sin(\omega t_n) + \omega C V_m \cos(\omega t_n)$

ωt_n is the instant at which the diodes turn-ON



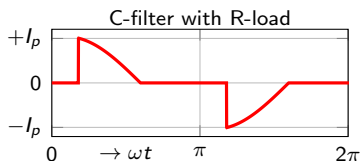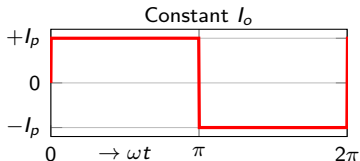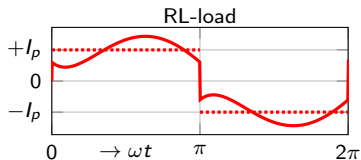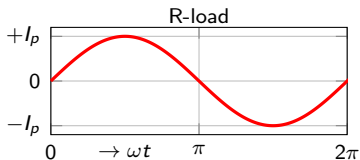1-ph full-wave rectifier: Waveforms of input current $i_s(t)$





In the case of constant current (I_o) load,

- ▶ $I_{sRMS} = I_o$; Fundamental $I_{s1RMS} = \frac{4I_o}{\pi\sqrt{2}} = 0.9I_o$; n^{th} harmonic $I_{snRMS} = \frac{I_{s1RMS}}{n}$
- ▶ $DPF = 1$ and $DF_1 = 0.9 \Rightarrow$ power factor $PF = 0.9$
- ▶ $i_s(t)$ doesn't contain even harmonics
- ▶ Total harmonic distortion $I_{sTHD} = 48.43\%$



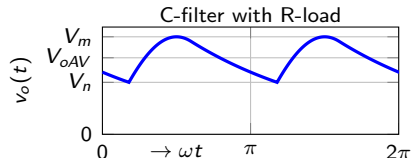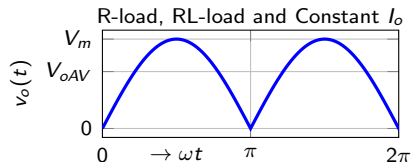1-ph full-wave rectifier: Waveforms of output voltage $v_o(t)$




$V_n = V_m \sin(\omega t_n)$ and ωt_n is the instant at which the diodes turn-ON

$$K = \omega RC$$

Load type	V_{oAV}
R-Load RL-Load Const I_o	$\frac{2V_m}{\pi}$
C-filter with R-load	$\frac{V_m}{\pi} \left[\cos(\omega t_n) + \sqrt{1 + K^2} - \frac{K^2}{\sqrt{1 + K^2}} e^{\frac{-\tan^{-1} K - \omega t_n}{K}} \right]$



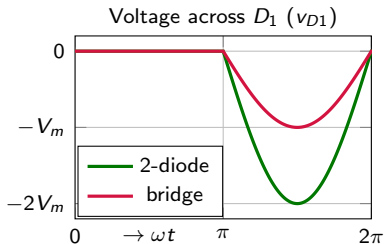
1-ph full-wave rectifier: Voltage across diode



- ▶ Peak inverse voltage (PIV) across each diode in a 2-diode rectifier (with $N_1 = N_2$) is twice that in a bridge rectifier
- ▶ In practical diodes, $v_{D1} \neq 0$ when D_1 is ON. Forward voltage drop across two diodes appears between source and load in bridge rectifier, while the center-tap (2-diode) rectifier has only one diode-voltage-drop between source and load



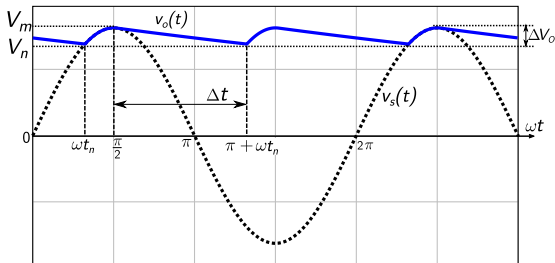1-ph full-wave rectifier: Design of C-filter



Specifications: (i) Input voltage and frequency (V_m and ω) (ii) average output power (P_o) (iii) peak-to-peak ripple in output voltage (ΔV_o)

Assumptions: (i) Diodes stop conducting at $\omega t = \pi/2$ and (ii) ripple in output power is negligible

$$\text{Peak-to-peak ripple } \Delta V_o = V_m - V_n = V_m - [V_m \sin(\omega t_n)] \Rightarrow \omega t_n = \sin^{-1} [1 - (\Delta V_o / V_m)]$$

Output power P_o is supplied only by the capacitor for the duration $\Delta t = \frac{(\pi/2) + \omega t_n}{\omega}$

$$\text{Change in energy of the capacitor } \frac{1}{2}C (V_m^2 - V_n^2) = P_o \Delta t$$



Connection of multiple diodes

Common cathode connection


Diode with its anode at the most positive voltage conducts

Common anode connection

Diode with its cathode at the most negative voltage conducts



3-ph half-wave (3-pulse) rectifier

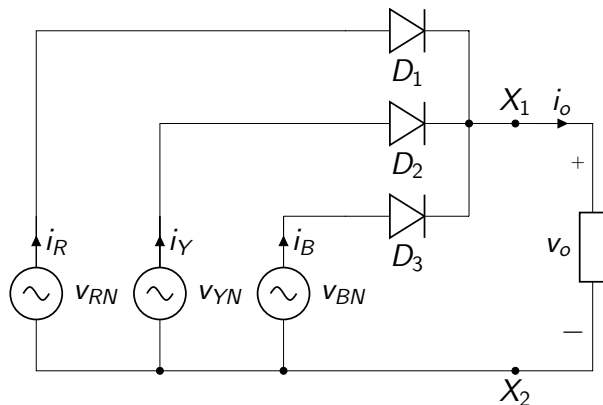


$$v_{RN} = V_m \sin(\omega t) \quad v_{YN} = V_m \sin\left(\omega t - \frac{2\pi}{3}\right) \quad v_{BN} = V_m \sin\left(\omega t + \frac{2\pi}{3}\right)$$

$i_R = i_{D1}$ and similar definitions for i_Y & i_B



3-ph half-wave (3-pulse) rectifier

Waveforms in periodic steady state

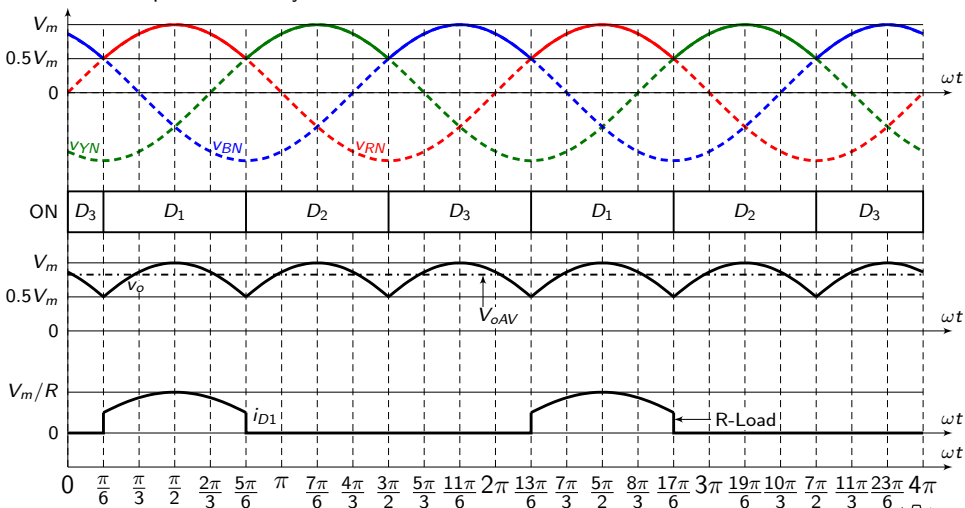

3-ph half-wave (3-pulse) rectifier

- Average output voltage

$$V_{oAV} = \frac{1}{(2\pi/3)} \int_{\pi/6}^{\frac{5\pi}{6}} V_m \sin(\omega t) d(\omega t) = \frac{3\sqrt{3}V_m}{2\pi}$$


- Peak-to-peak ripple in output voltage

$$V_{oPP} = 0.5V_m$$

- Each diode conducts for 120° (one-third of a line cycle)
- Input current $i_R(t)$ contains DC component (finite average value)



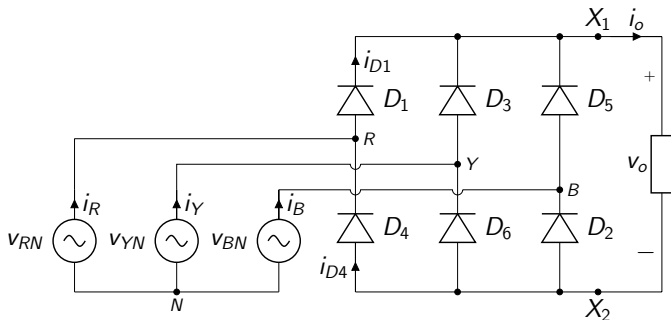3-ph full-wave/bridge (6-pulse) rectifier



$$v_{RN} = V_m \sin(\omega t) \quad v_{YN} = V_m \sin\left(\omega t - \frac{2\pi}{3}\right) \quad v_{BN} = V_m \sin\left(\omega t + \frac{2\pi}{3}\right)$$


$i_R = i_{D1} - i_{D4}$ and similar definitions for i_Y & i_B

PIV for each diode is $\sqrt{3}V_m$



3-ph full-wave/bridge (6-pulse) rectifier (R, RL and constant I_o)

Waveforms in periodic steady state

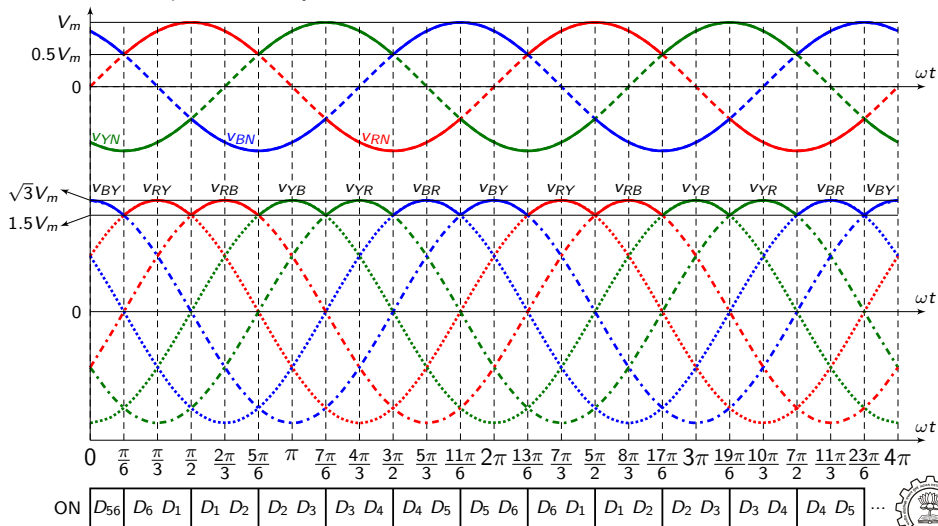

Waveforms in periodic steady state



Waveforms in periodic steady state



Waveforms in periodic steady state



3-ph full-wave/bridge (6-pulse) rectifier (R, RL and constant I_o)

- ▶ Average output voltage

$$\begin{aligned} V_{oAV} &= \frac{1}{(\pi/3)} \int_{\frac{\pi}{6}}^{\frac{\pi}{2}} v_{RY}(t) d(\omega t) \\ &= \frac{3}{\pi} \int_{\frac{\pi}{6}}^{\frac{\pi}{2}} \sqrt{3} V_m \sin \left(\omega t + \frac{\pi}{6} \right) d(\omega t) = \frac{3\sqrt{3} V_m}{\pi} \end{aligned}$$


- ▶ Maximum value of $v_o(t)$ is peak line-to-line voltage $\sqrt{3}V_m$
- ▶ Peak-to-peak ripple in output voltage

$$V_{oPP} = \sqrt{3}V_m - 1.5V_m = 0.232V_m$$
- ▶ Frequency of output voltage ripple is 300Hz (6 times the line frequency)
- ▶ Each diode conducts for 120° (one-third of a line cycle), two diodes conduct together
- ▶ Input current $i_R(t)$ doesn't contain even harmonics; doesn't contain triplen harmonics



3-ph full-wave/bridge (6-pulse) rectifier (constant I_o)

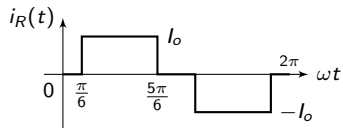In the case of constant current (I_o) load, $i_R(t)$ has the shape of a quasi-square wave



- ▶ $I_{RRMS} = I_o \sqrt{\frac{2}{3}}$; Fundamental $I_{R1RMS} = \frac{\sqrt{6}}{\pi} I_o$; n^{th} harmonic $I_{RnRMS} = \frac{I_{R1RMS}}{n}$
- ▶ $DPF = 1$ and $DF_1 = 0.955 \Rightarrow$ power factor $PF = 0.955$
- ▶ Order of harmonics in $i_R(t)$ is 5,7,11,13,17,19,... or $6m \pm 1$, $m = 1, 2, 3, \dots$
- ▶ Total harmonic distortion $I_{RTHD} = 31.08\%$







Effect of source inductance: Commutation (Constant load current I_o)

- ▶ Commutation: The process of current being transferred from one diode to the other
- ▶ Commutating inductance L_s is in series with v_s for 1-phase rectifiers
- ▶ For 3-phase rectifiers, L_s is in series with each of the sources, v_{RN} , v_{YN} and v_{BN}
- ▶ Commutation interval (in terms of angle) is denoted by μ
- ▶ Effects of commutation
 - ▶ Load regulation (Variation of output voltage with load)
 - ▶ Change in the shape of source (input) current waveform



Type of rectifier	$\cos \mu$	V_{oAV}
1-ph half-wave (free-wheeling diode)	$1 - \frac{\omega L_s I_o}{V_m}$	$\frac{V_m}{\pi} \left(1 - \frac{\omega L_s I_o}{2V_m} \right)$
1-ph bridge	$1 - \frac{2\omega L_s I_o}{V_m}$	$\frac{2V_m}{\pi} \left(1 - \frac{\omega L_s I_o}{V_m} \right)$
3-ph half-wave	$1 - \frac{2\omega L_s I_o}{\sqrt{3}V_m}$	$\frac{3\sqrt{3}V_m}{2\pi} \left(1 - \frac{\omega L_s I_o}{\sqrt{3}V_m} \right)$
3-ph bridge	$1 - \frac{2\omega L_s I_o}{\sqrt{3}V_m}$	$\frac{3\sqrt{3}V_m}{\pi} \left(1 - \frac{\omega L_s I_o}{\sqrt{3}V_m} \right)$



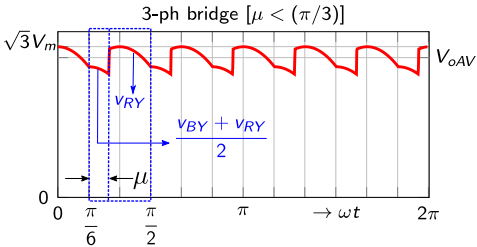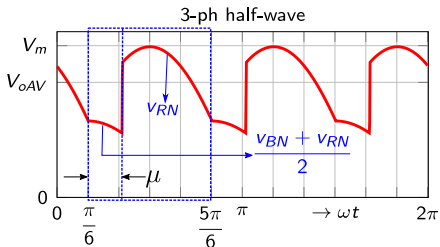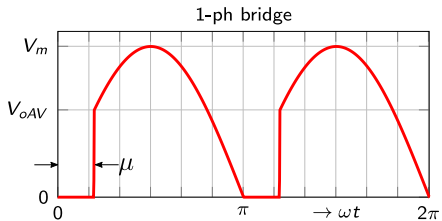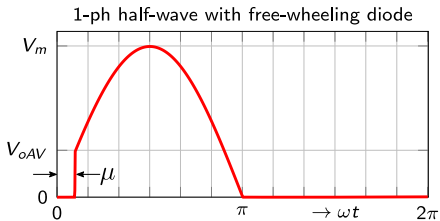Effect of source inductance: Waveforms of output voltage $v_o(t)$



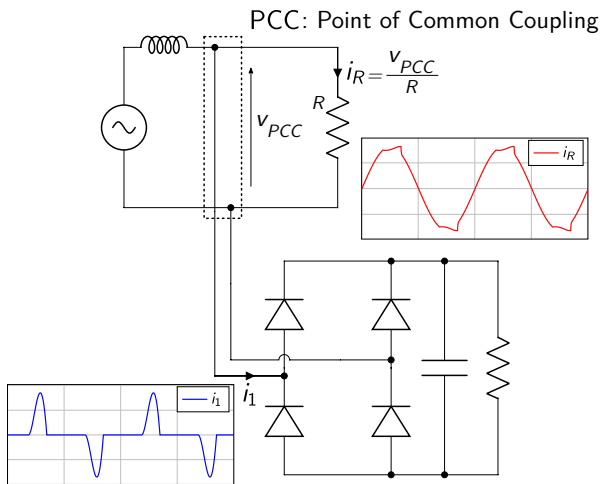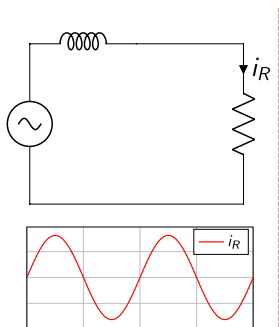
Input current of a rectifier: Effect on other loads



3-phase 12-pulse series-type diode rectifier


$$\frac{N_{s2}}{N_p} = \sqrt{3} \frac{N_{s1}}{N_p}$$

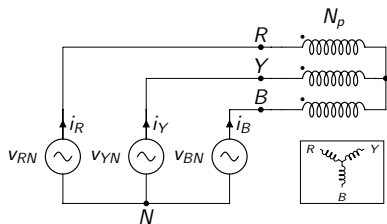V_{R2Y2} and V_{R1Y1} have equal magnitudes
 V_{R2Y2} leads V_{R1Y1} by 30°







$$i_R = \left(\frac{N_{s1}}{N_p} \right) i_{R1} + \left(\frac{N_{s2}}{N_p} \right) \left(\frac{i_{R2} - i_{B2}}{3} \right)$$

Ideal transformer

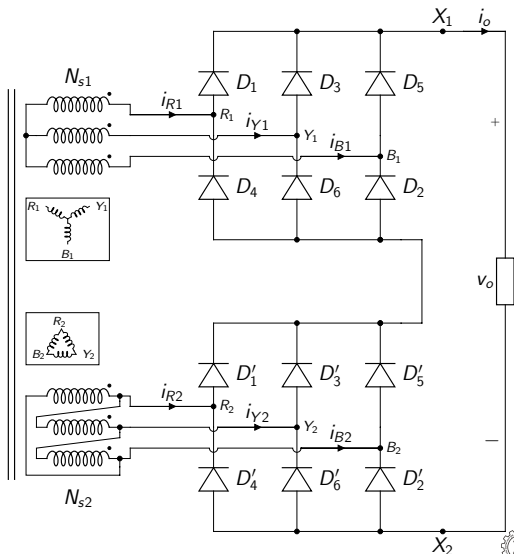

3-phase 12-pulse diode rectifier: R-load

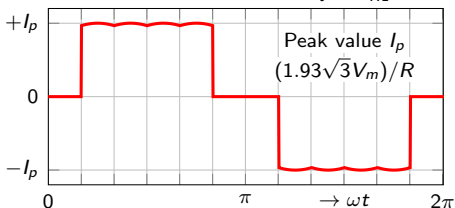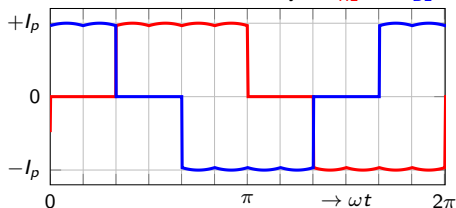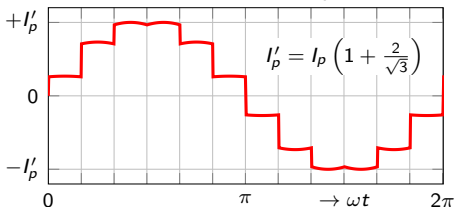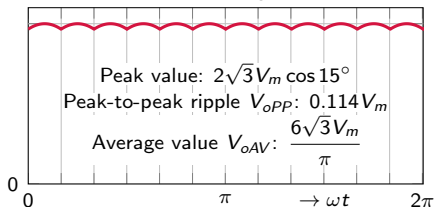Line current in secondary 1: i_{R1} Line currents in secondary 2: i_{R2} and i_{B2} Line current in primary: i_R Output voltage: v_o 


$$N_{s1} = N_p$$



3-phase 12-pulse diode rectifier (constant current I_o load)

$$N_{s1} = N_p$$

Input current: i_R

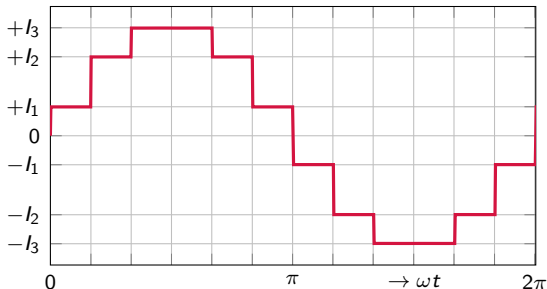

$$I_1 = \frac{I_o}{\sqrt{3}}$$

$$I_2 = I_o \left(1 + \frac{1}{\sqrt{3}} \right)$$

$$I_3 = I_o \left(1 + \frac{2}{\sqrt{3}} \right)$$

- ▶ $I_{RRMS} = I_o \sqrt{\frac{4}{3} + \frac{2}{\sqrt{3}}}$; Fundamental $I_{R1RMS} = \frac{2\sqrt{6}}{\pi} I_o$
- ▶ $DPF = 1$ and $DF_1 = 0.9886 \Rightarrow$ power factor $PF = 0.9886$
- ▶ Order of harmonics in $i_R(t)$ is 11,13,23,25,... or $12m \pm 1$, $m = 1, 2, 3, \dots$
- ▶ Total harmonic distortion $I_{RTHD} = 15.24\%$



Module 1: Summary

- ▶ Diode characteristics and loss calculations
- ▶ 1-pulse, 2-pulse, 3-pulse, 6-pulse and 12-pulse rectifiers
- ▶ R-load, constant current load (R with high L) and C-filter with R-load
- ▶ Effect of source inductance: commutation, load regulation
- ▶ Periodic steady-state and measures of periodic waveforms
- ▶ Fourier analysis and waveform symmetries
- ▶ Harmonic distortion at point of common coupling

