

# *Fundamentals of Power Electronics*

R. W. Erickson

## **Accompanying material for instructors**

The materials below are intended to be used by instructors of power electronics classes who have adopted *Fundamentals of Power Electronics* as a text. These instructors may download and use the files for educational purposes free of charge. Students and others who have purchased the text may also use the slides as an educational supplement to the text. Other uses of these materials is prohibited. All slides copyright R. W. Erickson 1997.

The slides for each chapter are contained in a .pdf file. These files can be read using the Adobe Acrobat viewer, available free from the [Adobe Acrobat web site](#). Slides and overhead transparencies covering the material of the entire book can be produced using these files.

[Back](#)

### **Introduction**

- [Chapter 1. Introduction](#) 98kB

### **Part 1: Converters in Equilibrium**

- [Chapter 2. Principles of steady-state converter analysis](#) 126kB
- [Chapter 3. Steady-state equivalent circuit modeling, losses, and efficiency](#) 98kB
- [Chapter 4. Switch realization](#) 201kB
- [Chapter 5. The discontinuous conduction mode](#) 96kB
- [Chapter 6. Converter circuits](#) 283kB

### **Part 2: Converter Dynamics and Control**

- [Chapter 7. Ac equivalent circuit modeling](#) 422kB
- [Chapter 8. Converter transfer functions](#)
- [Chapter 9. Controller design](#) 365kB
- [Chapter 10. Ac and dc equivalent circuit modeling of the discontinuous conduction mode](#) 218kB
- [Chapter 11. The current programmed mode](#) 236kB

### **Part 3: Magnetics**

- [Chapter 12. Basic magnetics theory](#) 196kB
- [Chapter 13. Filter inductor design](#) 67kB
- [Chapter 14. Transformer design](#) 175kB

## **Part 4: Modern Rectifiers and Power System Harmonics**

- [Chapter 15. Power and harmonics in nonsinusoidal systems](#) 91kB
- [Chapter 16. Line-commutated rectifiers](#) 130kB
- [Chapter 17. The ideal rectifier](#) 235kB
- [Chapter 18. Low harmonic rectifier modeling and control](#)

## **Part 5: Resonant Converters**

- [Chapter 19. Resonant conversion](#) 325kB
- [Chapter 20. Quasi-resonant converters](#) 177kB

## **Appendices**

- [Appendix 1. RMS values of commonly-observed converter waveforms](#) 26 kB
- [Appendix 2. Magnetics design tables](#) 26kB
- [Appendix 3. Averaged switch modeling of a CCM SEPIC](#) 41kB




Update 11/30/98 rwe

# ***Fundamentals of Power Electronics***

First Edition  
R. W. Erickson

[Power Electronics Group, University of Colorado at Boulder](#)

[About the second edition](#)

 

A new textbook on power electronics converters. This book is intended for use in introductory power electronics courses at the senior and first-year graduate level. It is also intended as a source for professionals working in power electronics, power conversion, and analog electronics. It emphasizes the fundamental concepts of power electronics, including averaged modeling of PWM converters and fundamentals of converter circuits and electronics, control systems, magnetics, low-harmonic rectifiers, and resonant converters.

## **Publisher and vitals**

New York: Chapman and Hall, May 1997.

Hardback

ISBN 0-412-08541-0

TK7881.15.E75 1997

7"x10", 791 pages, 929 line illustrations.

Note: Chapman and Hall has recently been acquired by Kluwer Academic Publishers

[Note to instructors: how to obtain a copy](#)

## **More information regarding contents of book**

- [Complete Table of Contents](#)
- [Abridged Table of Contents: Chapter titles only](#)
- [Preface](#)

- [Index](#) 101kB -searchable with Adobe Acrobat

[Errata, first printing](#)

## **Supplementary material for instructors**

- [Slides](#)
- [Solutions to selected problems](#)

## **Other supplementary material**

[Proximity effect: computer functions](#) 70kB

[Ferrite toroid data: Excel 5 spreadsheet](#)

[Derivation of  \$G\_{g0}\$ , Eqs. \(11.84\) and \(11.85\)](#)

---

Update 9/7/01 rwe

---

# CoPEC

## Colorado Power Electronics Center

University of Colorado, Boulder

---

[About CoPEC](#)

[Research](#)

[Publications](#)

[Students](#)

[Faculty](#)

[Courses](#)

[Textbook: Fundamentals of Power Electronics](#)

---

[Power Electronics in the CU Boulder Electrical and Computer Engineering Department](#)


[Links to Other Power Electronics Sites](#)

---

*Updated May 21, 2001.*

# Fundamentals of Power Electronics Second Edition

---

 

Authors: R. W. Erickson and D. Maksimovic  
University of Colorado, Boulder

Publisher: Kluwer Academic  
Publishers  
912 pages  
ISBN 0-7923-7270-0

- [First edition web site](#)
- [To order directly from the publisher](#)
- [Note to instructors: how to obtain desk copies](#)
- [Errata, second edition, first printing](#)
- [Errata, second edition, second printing](#)
- [New Certificate Program in Power Electronics](#)
- [PSPIICE circuit files and library](#)
- Courses at the University of Colorado that use the second edition
  - [ECEN 5797 Power](#)



[Electronics 1](#)

○ [ECEN 5807 Power](#)

[Electronics 2](#)

○ [ECEN 5817 Power](#)

[Electronics 3](#)

## Major Features of the Second Edition

- New material on converter simulation using averaged switch models
- Major revision of material on current mode control, including tables of transfer functions of basic converters
- Major revision of material on averaged switch modeling
- New material covering input filter design and Middlebrook's extra element theorem
- Improved explanations of the proximity effect and MMF diagrams
- New section on design of multiple-winding magnetics using the Kg method, including new examples
- New material on soft switching, including active clamp snubbers, the ZVT full bridge converter, and ARCP
- Major revision of material on low-harmonic rectifiers, to improve flow and readability. New material on critical conduction mode control
- Major revision and simplification of the chapter on ac modeling of the discontinuous conduction mode
- Revised problems, and a solutions manual

# Detailed description of revisions

- [Contents](#)
- [Preface to the Second Edition](#)
- Chapter 1 Introduction

## Part 1. Converters in Equilibrium

There are no substantial changes to the chapters of Part 1.

- Chapter 2 Principles of Steady-State Converter Analysis
- Chapter 3 Steady-State Equivalent Circuit Modeling, Losses, and Efficiency
- Chapter 4 Switch Realization
- Chapter 5 The Discontinuous Conduction Mode
- Chapter 6 Converter Circuits

---

## Part 2. Converter Dynamics and Control

- Chapter 7 AC Equivalent Circuit Modeling

Chapter 7 has been revised to improve the logical flow, including incorporation of the First Edition Appendix 3 into the chapter. The treatment of circuit averaging and averaged switch modeling (Section 7.4) has undergone major revision. Other changes include Fig. 7.4 and the related text, and Sections 7.2.2, 7.2.7.

- Chapter 8 Converter Transfer Functions

Major revisions to Chapter 8 include a new introduction, a new input filter example in Section 8.1.8, and substantial changes to the buck-boost converter example of Section 8.2.1 and the material of Sections 8.3 and 8.4.

- Chapter 9 Controller Design

Only minor changes to Chapter 9 were made.

- Chapter 10 Input Filter Design

This is an entirely new chapter that treats how input filters modify the transfer functions of a dc-dc



converter, and how to design an input filter that is adequately damped. The approach is based on Middlebrook's Extra Element Theorem (EET) of Appendix C, although it is possible to teach this chapter without use of the EET.

- Chapter 11 AC and DC Equivalent Circuit Modeling of the Discontinuous Conduction Mode

This chapter has been entirely revised and simplified.

- Chapter 12 Current Programmed Control

Treatment of the "more accurate model" in Section 12.3 has undergone a major revision. The explanation is more straightforward, and results are summarized for the basic buck, boost, and buck-boost converters. The results of simulation are used to illustrate how current programming changes the converter transfer function. The treatment of discontinuous conduction mode in Section 12.4 has been shortened.

---

## Part 3. Magnetics

- Chapter 13 Basic Magnetics Theory

The material on the skin and proximity effects has undergone a major revision, to better introduce the concepts of the proximity effect and MMF diagrams. The summary of operation of different magnetic devices has been moved from the filter inductor design chapter into this chapter.

- Chapter 14 Inductor Design

A new section on design of multiple-winding inductors using the Kg method has been added, including two new examples. The summary of different magnetic devices has been moved to the previous chapter, and the material on winding area optimization (previously in the transformer design chapter) has been moved into this chapter.

- Chapter 15 Transformer Design

Notation regarding maximum, peak, and saturation flux density has been made more clear. The section on winding area optimization has been moved to the previous chapter.

---

## Part 4. Modern Rectifiers, Inverters, and Power System Harmonics

- Chapter 16 Power and Harmonics in Nonsinusoidal Systems

Information on harmonic standards has been updated.

- Chapter 17 Line-Commutated Rectifiers

There is little change to this chapter.

- Chapter 18 Pulse-Width Modulated Rectifiers

Chapter 18 is a consolidation of Chapters 17 and 18 of the First Edition. The material has been completely reorganized, to improve its flow. A new section 18.2.2 has been added. Section 18.3.3 has been expanded, to better cover critical conduction mode control. The material on three-phase rectifier topologies has been streamlined.

---

## Part 5. Resonant Converters

- Chapter 19 Resonant Conversion

The order of the sections has been changed, to improve readability. Section 19.4 has been modified, to include better explanation of resonant inverter/electronic ballast design, and two examples have been added. The material on the ZVT converter has been moved to Chapter 20.

- Chapter 20 Soft Switching

A new Section 20.1 compares the turn-on and turn-off transitions of diode, MOSFET, and IGBT devices under the conditions of hard switching, zero-current switching, and zero-voltage switching. The material on quasi-resonant converters is unchanged. Coverage of multi-resonant and quasi-squarewave switches has been expanded, and includes plots of switch characteristics. A new Section 20.4 has been added, which covers soft-switching techniques. Included in Section 20.4 is an expanded explanation of the ZVT full-bridge converter, new material on active-clamp snubbers, and a short treatment of the auxiliary resonant commutated pole. The material on ac modeling of ZCS quasi-resonant converters has been dropped.

---

## Appendices

- Appendix A RMS Values of Commonly Observed Converter Waveforms

This appendix is unchanged.

- Appendix B Simulation of Converters

Appendix B is completely new. It covers SPICE simulation of converters using averaged switch models, including CCM, DCM, and current-programmed converters. This material complements the discussions of Chapters 7, 9, 11, 12, and 18. It has been placed in an appendix so that the chapter narratives are not interrupted by the details required to run a simulation program; nonetheless, the examples of this appendix are closely linked to the material covered in the chapters.

- [PSPICE circuit files and library used in Appendix B](#)

- Appendix C Middlebrook's Extra Element Theorem

This is a completely new appendix that explains the Extra Element Theorem and includes four tutorial examples. This material can be taught in conjunction with Chapter 10 and Section 19.4, if desired.

- Appendix D Magnetics Design Tables

This appendix is unchanged.

Update 12/8/00 rwe



# Fundamentals of Power Electronics Second Edition

[Up](#)

To instructors of Power Electronics courses: how to obtain an examination copy

Evaluation copies are available on a 60-day approval basis.

Please submit requests in writing on department letterhead and include the following course information:

- course name and number
- estimated enrollment
- semester date
- the text currently used
- your decision date

Please direct all requests to the Textbook Marketing Department at Kluwer Academic Publishers at the Norwell (Americas) or Dordrecht (all other countries) offices:

- In the Americas:  
101 Philip Drive  
Norwell, MA 02061  
USA  
Telephone: (781) 871-6600  
Fax: (781) 871-6528  
Attention: Ulysses Guasch  
E-mail: [ulysses.guasch@wkap.com](mailto:ulysses.guasch@wkap.com)
- All other countries:  
PO Box 989  
3300 AZ Dordrecht  
The Netherlands  
Telephone: (0) 31 78 6392 392  
Fax: (0) 31 78 6546 474  
E-mail: [services@wkap.nl](mailto:services@wkap.nl)

---

Update 12/15/00 rwe





# ***Fundamentals of Power Electronics***

**R. W. Erickson**

## **Table of Contents**

[Back](#)

### **1. Introduction**

- 1.1. Introduction to power processing
- 1.2. Several applications of power electronics
- 1.3. Elements of power electronics

## **Part I. Converters in Equilibrium**

### **2. Principles of steady state converter analysis**

- 2.1. Introduction
- 2.2. Inductor volt-second balance, capacitor charge balance, and the small-ripple approximation
- 2.3. Boost converter example
- 2.4. Cuk converter example
- 2.5. Estimating the output voltage ripple in converters containing two-pole low-pass filters
- 2.6. Summary of key points

### **3. Steady-state equivalent circuit modeling, losses, and efficiency**

- 3.1. The dc transformer model
- 3.2. Inclusion of inductor copper loss
- 3.3. Construction of equivalent circuit model
- 3.4. How to obtain the input port of the model
- 3.5. Example: Inclusion of semiconductor conduction losses in the boost converter model
- 3.6. Summary of key points

### **4. Switch realization**

- 4.1. Switch applications
  - 4.1.1. Single quadrant switches
  - 4.1.2. Current-bidirectional two-quadrant switches
  - 4.1.3. Voltage-bidirectional two-quadrant switch

4.1.4. Four-quadrant switches

4.1.5. Synchronous rectifiers

## 4.2. A brief survey of power semiconductor devices

4.2.1. Power diodes

4.2.2. Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET)

4.2.3. Bipolar Junction Transistor (BJT)

4.2.4. Insulated Gate Bipolar Transistor (IGBT)

4.2.5. Thyristors (SCR, GTO, MCT)

## 4.3. Switching loss

4.3.1. Transistor switching with clamped inductive load

4.3.2. Diode recovered charge

4.3.3. Device capacitances, and leakage, package, and stray inductances

4.3.4. Efficiency vs. switching frequency

## 4.4. Summary of key points

# 5. The discontinuous conduction mode

5.1. Origin of the discontinuous conduction mode, and mode boundary

5.2. Analysis of the conversion ratio  $M(D,K)$

5.3. Boost converter example

5.4. Summary of results and key points

# 6. Converter circuits

## 6.1. Circuit manipulations

6.1.1. Inversion of source and load

6.1.2. Cascade connection of converters

6.1.3. Rotation of three-terminal cell

6.1.4. Differential connection of the load

## 6.2. A short list of converters

## 6.3. Transformer isolation

6.3.1. Full-bridge and half-bridge isolated buck converters

6.3.2. Forward converter

6.3.3. Push-pull isolated buck converter

6.3.4. Flyback converter

6.3.5. Boost-derived isolated converters

6.3.6. Isolated versions of the SEPIC and the Cuk converter

## 6.4. Converter evaluation and design

- 6.4.1. Switch stress and utilization
- 6.4.2. Design using computer spreadsheet

## 6.5. Summary of key points

# Part II. Converter Dynamics and Control

## 7. AC modeling

### 7.1. Introduction

### 7.2. The basic ac modeling approach

- 7.2.1. Averaging the inductor waveforms
- 7.2.2. Discussion of the averaging approximation
- 7.2.3. Averaging the capacitor waveforms
- 7.2.4. The average input current
- 7.2.5. Perturbation and linearization
- 7.2.6. Construction of the small-signal equivalent circuit model
- 7.2.7. Results for several basic converters

### 7.3. Example: A nonideal flyback converter

### 7.4. State-space averaging

- 7.4.1. The state equations of a network
- 7.4.2. The basic state-space averaged model
- 7.4.3. Discussion of the state-space averaging result
- 7.4.4. Example: State-space averaging of a nonideal buck-boost converter

### 7.5. Circuit averaging and averaged switch modeling

- 7.5.1. Obtaining a time-invariant circuit
- 7.5.2. Circuit averaging
- 7.5.3. Perturbation and linearization
- 7.5.4. Averaged switch modeling

### 7.6. The canonical circuit model

- 7.6.1. Development of the canonical circuit model
- 7.6.2. Example: Manipulation of the buck-boost converter model into canonical form
- 7.6.3. Canonical circuit parameter values for some common converters

## 7.7. Modeling the pulse-width modulator

## 7.8. Summary of key points

# 8. Converter transfer functions

## 8.1. Review of Bode plots

8.1.1. Single pole response

8.1.2. Single zero response

8.1.3. Right half-plane zero

8.1.4. Frequency inversion

8.1.5. Combinations

8.1.6. Double pole response: resonance

8.1.7. The low-Q approximation

8.1.8. Approximate roots of an arbitrary-degree polynomial

## 8.2. Analysis of converter transfer functions

8.2.1. Example: Transfer functions of the boost converter

8.2.2. Transfer functions of some basic dc-dc converters

8.2.3. Physical origins of the RHP zero

## 8.3. Graphical construction of converter transfer functions

8.3.1. Series impedances: addition of asymptotes

8.3.2. Parallel impedances: inverse addition

8.3.3. Another example

8.3.4. Voltage divider transfer functions: division of asymptotes

## 8.4. Measurement of ac transfer functions and impedances

## 8.5. Summary of key points

# 9. Controller design

## 9.1. Introduction

## 9.2. Effect of negative feedback on the network transfer functions

9.2.1. Feedback reduces the transfer functions from disturbances to the output

9.2.2. Feedback causes the transfer function from the reference input to the output to be insensitive to variations in the gains in the forward path of the loop

## 9.3. Construction of the important quantities $1/(1+T)$ and $T/(1+T)$ and the closed-loop transfer

functions

## 9.4. Stability

9.4.1. The phase margin test

9.4.2. The relation between phase margin and closed-loop damping factor

9.4.3. Transient response vs. damping factor

## 9.5. Regulator design

9.5.1. Lead (PD) compensator

9.5.2. Lag (PI) compensator

9.5.3. Combined (PID) compensator

9.5.4. Design example

## 9.6. Measurement of loop gains

9.6.1. Voltage injection

9.6.2. Current injection

9.6.3. Measurement of unstable systems

## 9.7. Summary of key points

# **10. Ac and dc equivalent circuit modeling of the discontinuous conduction mode**

## 10.1. DCM averaged switch model

## 10.2. Small-signal ac modeling of the DCM switch network

## 10.3. Generalized switch averaging

10.3.1. DCM buck converter example

10.3.2. Proof of generalized averaged switch modeling

## 10.4. Summary of key points

# **11. Current programmed control**

## 11.1. Oscillation for $D > 0.5$

## 11.2. A simple first-order model

11.2.1. Simple model via algebraic approach: buck-boost example



11.2.2. Averaged switch modeling

11.3. A more accurate model

11.3.1. Current programmed controller model

11.3.2. Example: analysis of CPM buck converter

11.4. Discontinuous conduction mode

11.5. Summary of key points

## **Part III. Magnetics**

### **12. Basic magnetics theory**

12.1. Review of basic magnetics

12.1.1. Basic relations

12.1.2. Magnetic circuits

12.2. Transformer modeling

12.2.1. The ideal transformer

12.2.2. The magnetizing inductance

12.2.3. Leakage inductances

12.3. Loss mechanisms in magnetic devices

12.3.1. Core loss

12.3.2. Low-frequency copper loss

12.4. Eddy currents in winding conductors

12.4.1. The skin effect

12.4.2. The proximity effect

12.4.3. Magnetic fields in the vicinity of winding conductors: MMF diagrams

12.4.4. Power loss in a layer

12.4.5. Example: power loss in a transformer winding

12.4.6. PWM waveform harmonics

12.5. Summary of key points

### **13. Filter inductor design**

13.1. Several types of magnetic devices, their  $B$ - $H$  loops, and core vs. copper loss

13.2. Filter inductor design constraints

13.2.1. Maximum flux density

13.2.2. Inductance

13.2.3. Winding area

13.2.4. Winding resistance

13.3. The core geometrical constant  $K_g$

13.4. A step-by-step procedure

13.5. Summary of key points

## 14. Transformer design

14.1. Winding area optimization

14.2. Transformer design: basic constraints

14.2.1. Core loss

14.2.2. Flux density

14.2.3. Copper loss

14.2.4. Total power loss vs.  $B_{max}$

14.2.5. Optimum flux density

14.3. A step-by-step transformer design procedure

14.4. Examples

14.4.1. Example 1: single-output isolated Cuk converter

14.4.2. Example 2: multiple-output full-bridge buck converter

14.5. Ac inductor design

14.5.1. Outline of derivation

14.5.2. Step-by-step ac inductor design procedure

14.6. Summary

## Part IV. Modern Rectifiers, and Power System Harmonics

### 15. Power and harmonics in nonsinusoidal systems

### 15.1. Average power

### 15.2. Root-mean-square (rms) value of a waveform

### 15.3. Power factor

15.3.1. Linear resistive load, nonsinusoidal voltage

15.3.2. Nonlinear dynamic load, sinusoidal voltage

### 15.4. Power phasors in sinusoidal systems

### 15.5. Harmonic currents in three-phase systems

15.5.1. Harmonic currents in three-phase four-wire networks

15.5.2. Harmonic currents in three-phase three-wire networks

15.5.3. Harmonic current flow in power factor correction capacitors

### 15.6. AC line current harmonic standards

15.6.1. US MIL STD 461B

15.6.2. International Electrotechnical Commission standard 555

15.6.3. IEEE/ANSI standard 519

## **16. Line-commutated rectifiers**

### 16.1. The single-phase full wave rectifier

16.1.1. Continuous conduction mode

16.1.2. Discontinuous conduction mode

16.1.3. Behavior when  $C$  is large

16.1.4. Minimizing THD when  $C$  is small

### 16.2. The three-phase bridge rectifier

16.2.1. Continuous conduction mode

16.2.2. Discontinuous conduction mode

### 16.3. Phase control

16.3.1. Inverter mode

16.3.2. Harmonics and power factor

16.3.3. Commutation

## 16.4. Harmonic trap filters

## 16.5. Transformer connections

## 16.6. Summary

# 17. The ideal rectifier

## 17.1. Properties of the ideal rectifier

## 17.2. Realization of a near-ideal rectifier

## 17.3. Single-phase converter systems incorporating ideal rectifiers

## 17.4. RMS values of rectifier waveforms

### 17.4.1. Boost rectifier example

### 17.4.2. Comparison of single-phase rectifier topologies

## 17.5. Ideal three-phase rectifiers

### 17.5.1. Three-phase rectifiers operating in CCM

### 17.5.2. Some other approaches to three-phase rectification

## 17.6. Summary of key points

# 18. Low harmonic rectifier modeling and control

## 18.1. Modeling losses and efficiency in CCM high-quality rectifiers

### 18.1.1. Expression for controller duty cycle $d(t)$

### 18.1.2. Expression for the dc load current

### 18.1.3. Solution for converter efficiency

### 18.1.4. Design example

## 18.2. Controller schemes

### 18.2.1. Average current control

### 18.2.2. Feedforward

### 18.2.3. Current programmed control

### 18.2.4. Hysteretic control

### 18.2.5. Nonlinear carrier control

## 18.3. Control system modeling

- 18.3.1. Modeling the outer low-bandwidth control system
- 18.3.2. Modeling the inner wide-bandwidth average current controller

#### 18.4. Summary of key points

## Part V. Resonant converters

### 19. Resonant Conversion

#### 19.1. Sinusoidal analysis of resonant converters

- 19.1.1. Controlled switch network model
- 19.1.2. Modeling the rectifier and capacitive filter networks
- 19.1.3. Resonant tank network
- 19.1.4. Solution of converter voltage conversion ratio  $M = V/V_g$

#### 19.2. Examples

- 19.2.1. Series resonant dc-dc converter example
- 19.2.2. Subharmonic modes of the series resonant converter
- 19.2.3. Parallel resonant dc-dc converter example

#### 19.3. Exact characteristics of the series and parallel resonant converters

- 19.3.1. Series resonant converter
- 19.3.2. Parallel resonant converter

#### 19.4. Soft switching

- 19.4.1. Operation of the full bridge below resonance: zero-current switching
- 19.4.2. Operation of the full bridge above resonance: zero-voltage switching
- 19.4.3. The zero voltage transition converter

#### 19.5. Load-dependent properties of resonant converters

- 19.5.1. Inverter output characteristics
- 19.5.2. Dependence of transistor current on load
- 19.5.3. Dependence of the ZVS/ZCS boundary on load resistance

#### 19.6. Summary of key points

### 20. Quasi-resonant converters



- 20.1. The zero-current-switching quasi-resonant switch cell
  - 20.1.1. Waveforms of the half-wave ZCS quasi-resonant switch cell
  - 20.1.2. The average terminal waveforms
  - 20.1.3. The full-wave ZCS quasi-resonant switch cell
- 20.2. Resonant switch topologies
  - 20.2.1. The zero-voltage-switching quasi-resonant switch
  - 20.2.2. The zero-voltage-switching multi-resonant switch
  - 20.2.3. Quasi-square-wave resonant switches
- 20.3. Ac modeling of quasi-resonant converters
- 20.4. Summary of key points

## **Appendices**

### **Appendix 1. RMS values of commonly-observed converter waveforms**

- A1.1. Some common waveforms
- A1.2. General piecewise waveform

### **Appendix 2. Magnetics design tables**

- A2.1. Pot core data
- A2.2. EE core data
- A2.3. EC core data
- A2.4. ETD core data
- A2.5. PQ core data
- A2.6. American wire gauge data

### **Appendix 3. Averaged switch modeling of a CCM SEPIC**

## **Index**

# ***Fundamentals of Power Electronics***

**R. W. Erickson**

## **Table of Contents**

Chapter titles only

[Back](#)

1. Introduction

### **Part I. Converters in Equilibrium**

- 2. Principles of steady state converter analysis
- 3. Steady-state equivalent circuit modeling, losses, and efficiency
- 4. Switch realization
- 5. The discontinuous conduction mode
- 6. Converter circuits

### **Part II. Converter Dynamics and Control**

- 7. AC modeling
- 8. Converter transfer functions
- 9. Controller design
- 10. Ac and dc equivalent circuit modeling of the discontinuous conduction mode
- 11. Current programmed control

### **Part III. Magnetics**

- 12. Basic magnetics theory
- 13. Filter inductor design
- 14. Transformer design

### **Part IV. Modern Rectifiers, and Power System Harmonics**

- 15. Power and harmonics in nonsinusoidal systems
- 16. Line-commutated rectifiers

- 17. The ideal rectifier
- 18. Low harmonic rectifier modeling and control

## **Part V. Resonant Converters**

- 19. Resonant conversion
- 20. Quasi-resonant converters

## **Appendices**

- Appendix 1. RMS values of commonly-observed converter waveforms
- Appendix 2. Magnetics design tables
- Appendix 3. Averaged switch modeling of a CCM SEPIC

## **Index**

# Preface

## *Fundamentals of Power Electronics*

R. W. Erickson

[Back](#)

In many university curricula, the power electronics field has evolved beyond the status of comprising one or two special-topics courses. Often there are several courses dealing with the power electronics field, covering the topics of converters, motor drives, and power devices, with possibly additional advanced courses in these areas as well. There may also be more traditional power-area courses in energy conversion, machines, and power systems. In the breadth vs. depth tradeoff, it no longer makes sense for one textbook to attempt to cover all of these courses; indeed, each course should ideally employ a dedicated textbook. This text is intended for use in introductory power electronics courses on converters, taught at the senior or first-year graduate level. There is sufficient material for a one year course or, at a faster pace with some material omitted, for two quarters or one semester.

The first class on converters has been called a way of enticing control and electronics students into the power area via the "back door". The power electronics field is quite broad, and includes fundamentals in the areas of

- Converter circuits and electronics
- Control systems
- Magnetics
- Power applications
- Design-oriented analysis

This wide variety of areas is one of the things which makes the field so interesting and appealing to newcomers. This breadth also makes teaching the field a challenging undertaking, because one cannot assume that all students enrolled in the class have solid prerequisite knowledge in so many areas. Indeed, incoming students may have individual backgrounds in the power, control, or electronics areas, but rarely in all three. Yet it is usually desired to offer the class to upper-division undergraduate and entering graduate students. Hence, in teaching a class on converters (and in writing a textbook), there are two choices:

1. Avoid the problem of prerequisites, by either (a) assuming that the students have all of the prerequisites and discussing the material at a high level (suitable for an advanced graduate class), or (b) leaving out detailed discussions of the various contributing fields.
2. Attack the problem directly, by teaching or reviewing material from prerequisite areas as it is

needed. This material can then be directly applied to power electronics examples. This approach is suitable for a course in the fourth or fifth year, in which fundamentals are stressed.

Approach (2) is employed here. Thus, the book is not intended for survey courses, but rather, it treats fundamental concepts and design problems in sufficient depth that students can actually build converters. An attempt is made to deliver specific results. Completion of core circuits and electronics courses is the only prerequisite assumed; prior knowledge in the areas of magnetics, power, and control systems is helpful but not required.

In the power electronics literature, much has been made of the incorporation of other disciplines such as circuits, electronic devices, control systems, magnetics, and power applications, into the power electronics field. Yet the field has evolved, and now is more than a mere collection of circuits and applications linked to the fundamentals of other disciplines. There is a set of fundamentals that are unique to the field of power electronics. It is important to identify these fundamentals, and to explicitly organize our curricula, academic conferences, and other affairs around these fundamentals. This book is organized around the fundamental principles, while the applications and circuits are introduced along the way as examples.

A concerted effort is made to teach converter modeling. Fundamental topics covered include:

- Fundamentals of PWM converter analysis, including the principles of inductor volt-second balance and capacitor charge balance, and the small-ripple approximation (Chapter 2).
- Converter modeling, including the use of the dc transformer model, to predict efficiency and losses (Chapter 3).
- Realization of switching elements using semiconductor devices. One-, two-, and four-quadrant switches. A brief survey of power semiconductor devices (Chapter 4).
- An up-to-date treatment of switching losses and their origins. Diode stored charge, device capacitances, and ringing waveforms (Chapter 4).
- Origin and steady-state analysis of the discontinuous conduction mode (Chapter 5).
- Converter topologies (Chapter 6).
- The use of averaging to model converter small-signal ac behavior. Averaged switch modeling (Chapter 7).
- Converter small-signal ac transfer functions, including the origins of resonances and right half-plane zeroes. Control-to-output and line-to-output transfer functions, and output impedance (Chapter 8).
- A basic discussion of converter control systems, including objectives, the system block diagram, and the effect of feedback on converter behavior (Chapter 9).
- Ac modeling of the discontinuous conduction mode. Quantitative behavior of DCM small-signal transfer functions (Chapter 10).
- Current-programmed control. Oscillation for  $D > 0.5$ . Equivalent circuit modeling (Chapter 11).
- Basic magnetics, including inductor and transformer modeling, and loss mechanisms in high-frequency power magnetics (Chapter 12).
- An understanding of what determines the size of power inductors and transformers. Power inductor and transformer design issues (Chapters 13 and 14).
- Harmonics in power systems (Chapter 15).
- A modern viewpoint of rectifiers, including harmonics, power factor, and mitigation techniques in conventional rectifiers, and operation of sophisticated low-harmonic rectifiers (Chapters 16-18).
- Analysis and modeling of low-harmonic rectifiers (Chapters 17-18).
- Resonant inverters and dc-dc converters: approximate analysis techniques, characteristics of basic converters, and

load-dependent properties (Chapter 19).

- Zero voltage switching, zero current switching, and the zero-voltage-transition converter (Chapter 19).
- Resonant switch converters, including basic operation, efficiency and losses, and ac modeling (Chapter 20).

On teaching averaged converter modeling: I think that this is one of the important fundamentals of the field, and hence we should put serious effort into teaching it. Although we in the academic community may debate how to rigorously justify averaging, nonetheless it is easy to teach the students to average: Just average all of the waveforms over one switching period. In particular, for the continuous conduction mode, average the inductor voltages and capacitor currents over one switching period, ignoring the ripple. That's all that is required, and I have found that students quickly and easily learn to average waveforms. The results are completely general, they aren't limited to SPDT switches, and they can easily be used to refine the model by inclusion of losses, dynamics, and control variations. To model dynamics, it is also necessary to linearize the resulting equations. But derivation of small-signal models is nothing new to the students --they have already seen this in their core electronics classes, as well as in numerous math courses and perhaps also in energy conversion. It isn't necessary to teach full-blown state-space averaging, but I have included an optional (with asterisk) section on this for the graduate students. I personally prefer to initially skip Sections 7.4 and 7.5. After covering Chapters 8 and 9, I return to cover Sections 7.4 and 7.5 before teaching Chapters 10 and 11.

Averaging aside, it is also important to teach modeling in a pedagogically sound way. The object is to describe the important properties of the converter, in a simple and clear way. The dc transformer represents the basic function of a dc-dc converter, and so the modeling process should begin with a dc transformer having a turns ratio equal to the conversion ratio of the converter. For example, the model of the buck-boost converter ought to contain a buck transformer cascaded by a boost transformer, or perhaps the two transformers combined into a single  $D : D'$  transformer. This first-order model can later be refined if desired, by addition of loss elements, dynamic elements, etc.

The design-oriented analysis methods of R. D. Middlebrook have been well accepted by a significant portion of the power electronics community. While the objective of this text is the introduction of power electronics rather than design-oriented analysis, the converter analyses and examples are nonetheless done in a design-oriented way. Approximations are often encouraged, and several of the techniques of design-oriented analysis are explicitly taught in parts of Chapters 8 and 9. We need to teach our students how to apply our academic theory to real-world, and hence complicated, problems. Design-oriented analysis is the missing link.

Chapter 8 contains a "review" of Bode diagrams, including resonant responses and right half-plane zeroes. Also included is material on design-oriented analysis, in the context of converter transfer functions. The Bode diagram material is covered in more depth than in prerequisite classes. I have found that the material of Chapter 8 is especially popular with continuing education students who are practicing engineers. I recommend at least quickly covering this chapter in lecture. Those instructors who choose to skip some or all of Chapter 8 can assign it as reading, and hold students responsible for the material. In a similar manner, Chapter 9 contains a "review" of classical control systems, in the context of switching regulators. This chapter explicitly makes the connection between the small-signal converter models

derived in other chapters, and their intended application. Many power area students are unfamiliar with this material, and even control-area students comment that they learned something from the design-oriented approach.

Parts III, IV, and V can be covered in any order. Part III includes a review of basic magnetics, a discussion of proximity loss, and an introduction to the issues governing design of magnetic devices. The inclusion of step-by-step design procedures may be somewhat controversial; however, these procedures explicitly illustrate the issues inherent in magnetics design. Student tendencies towards cookbook mentality are mitigated by the inclusion of homework problems that cannot be solved using the given step-by-step procedures. Part IV, entitled "Modern rectifiers," covers the issues of power system harmonics, generation of harmonics by conventional rectifiers, and low-harmonic rectifiers. Chapters 17 and 18 cover low-harmonic rectifiers in depth, including converter analysis and modeling, and rectifier control systems. Resonant converters are treated in Part V. There have been a tremendous number of papers written on resonant converters, most of which are very detailed and complicated. Indeed, the complexity of resonant converter behavior makes it challenging to teach this subject in depth. Two somewhat introductory chapters are included here. State-plane analysis is omitted, and is left for an advanced graduate class. In Chapter 19, resonant inverters and dc-dc converters are introduced and are analyzed via the sinusoidal approximation. Soft switching is described, in the context of both resonant converters and the zero-voltage transition converter. Some resonant network theorems are also presented, which yield insight into the design of resonant inverters with reduced circulating currents, with zero-voltage switching over a wide range of load currents, and with desired output characteristics. Resonant switch converters are introduced and modeled in Chapter 20.

Most chapters include both short analysis problems, and longer analysis and/or design problems. References are given at the end of each chapter; these are not intended to be exhaustive bibliographies, but rather are a starting place for additional reading.

This text has evolved from course notes developed over thirteen years of teaching power electronics at the University of Colorado, Boulder. These notes, in turn, were heavily influenced by my previous experience as a graduate student at the California Institute of Technology, under the direction of Profs. Slobodan Cuk and R. D. Middlebrook, to whom I am grateful. In addition, I appreciate the numerous helpful technical discussions and suggestions of my colleague at the University of Colorado, Prof. Dragan Maksimovic. I would also like to thank the following individuals for their suggestions: Prof. Arthur Witulski (University of Arizona, Tucson), Prof. Sigmund Singer (Tel-Aviv University, Israel), Dr. Michael Madigan, and Carlos Oliveira.

Robert W. Erickson  
Boulder, Colorado



## INDEX

- Air gap
  - in coupled inductor, 502
  - in flyback transformer, 503
  - in inductor, 464-466, 498, 505, 509
  - in transformer, 469
- $A_L$  (mH/1000 turns), 509
- American wire gauge (AWG)
  - data, 755-756
  - design examples, 527, 531
- Amorphous alloys, 473
- Ampere's law, 457-458
- Amp-second balance (*see* Capacitor charge balance)
- Apparent power, 550
- Artificial ramp
  - circuit, 415
  - effect on CPM boost low-harmonic rectifier, 637-639
  - effect on line-to-output transfer function of CCM buck, 437-438
  - effect on small-signal CCM models, 428-438
  - effect on small-signal DCM models, 438-447
  - effect on stability of CPM controllers, 414-418
- Asymptotes (*see* Bode plots)
- Audiosusceptibility  $G_{vg}(s)$  (*see* Line-to-output transfer function)
- Average current control
  - feedforward, 635-636
  - in low-harmonic rectifier systems, 593-598, 634-636, 649, 650-652
  - modeling of, 649-652
- Averaged switch modeling, 239-245, 390-403
  - of current-programmed CCM converters, 423-428
  - of current-programmed DCM converters, 438-447
  - in discontinuous conduction mode, 370-390
  - equivalent circuit modeling of switching loss, 241-245
  - examples
    - nonideal buck converter, 241-245
    - DCM buck converter, 393-400
    - CCM SEPIC, 757-762
  - generalization of, 390-403
  - of ideal CCM switch networks, 242, 377, 757-762
  - of ideal DCM switch networks, 377
  - of quasi-resonant converters, 732-737
- Average power
  - and Fourier series, 542-543
  - modeled by power source element, 375-379, 423-428, 438-447
  - in nonsinusoidal systems, 542-555
  - predicted by averaged models, 57
  - power factor, 546-550
  - sinusoidal phasor diagram, 550-551
- Averaging
  - approximation, discussion of, 195-196, 200-202
  - averaged switch modeling, 239-245
  - basic approach, 198-209

- capacitor charge balance, 24
- circuit, 231-245
  - to find dc component, 6, 16
  - flyback ac model, 209-218
  - inductor volt-second balance, 22-23
  - introduction to, 193-198
  - modeling efficiency and loss via, 57
  - to model rectifier output, 645-647
  - to model 3 $\phi$  converters, 611-614
  - of quasi-resonant converters
    - ac modeling, 732-737
    - dc analysis, 712-728
  - state-space, 218-231
- Battery charger, 9, 70
- B-H* loop
  - in an ac inductor, 499-500
  - in a conventional transformer, 153, 500-501
  - in a coupled inductor, 501-502
  - in a filter inductor, 497-499
  - in a flyback transformer, 502-503
  - modeling of, 458-460
- Bidirectional dc-dc converters, 70
- Bipolar junction transistor (BJT)
  - breakdown mechanisms in, 86-87
  - construction and operation of, 82-87
  - current crowding, 85-86
  - Darlington-connected, 87
  - idealized switch characteristics, 65-66
  - on resistance, 53, 82
  - quasi-saturation, 82-83, 86
  - storage time, 84
  - stored minority charge in, 82-86
  - switching waveforms, 83-86
- Bode plots (*see also* Harmonic trap filters, sinusoidal approximation)
  - asymptote analytical equations, 275-276
  - CCM buck-boost example, 289-292
  - combinations, 272-276
  - complex poles, 276-282
  - frequency inversion, 271-272
  - graphical construction of, 296-309
    - addition, 296-301
    - closed-loop transfer functions, 329-332
    - division, 307-309
    - parallel combination, 301-307
    - parallel resonance, 301-303
    - series resonance, 298-303
  - impedance graph paper, 307
  - nonminimum phase zero, 269-271
  - reactance graph paper, 307
  - real pole, 263-268
  - real zero, 268-269
  - RHP zero, 269-271
  - transfer functions of buck, boost, buck-boost, 292-293
- Body diode (*see* MOSFET)

- Boost converter (*see also* Bridge configuration, Push-pull isolated converters)
  - active switch utilization in, 179, 608
  - averaged switch model, DCM, 380-381
  - circuit-averaged model, 233-239
  - current-programmed
    - averaged switch model, CCM, 424-425
    - averaged switch model, DCM, 443-444
    - small-signal ac model, CCM, 427-428, 430-431
    - small-signal ac model, DCM, 445-447
  - as inverted buck converter, 136-137
  - as low-harmonic rectifier, 594-597, 605-609, 617, 627-634
  - nonideal analysis of, 43-51, 53-57
  - quasi-resonant ZCS, 722-723
  - small-signal ac model
    - CCM, 208-210, 251
    - DCM, 385-390
  - steady-state analysis of,
    - CCM, 24-29
    - DCM, 121-125
  - transfer functions, CCM, 292-293
- Bridge configuration (dc-dc converters)
  - boost-derived full bridge, 171-172
  - buck-derived full bridge, 154-157
  - buck-derived half bridge, 157-159
  - full bridge transformer design example, 528-531
  - minimization of transformer copper loss in, 516-517
- Bridge configuration (inverters)
  - single phase, 7-8, 142-145, 148-150
  - three phase, 70, 143-148
- Buck-boost converter (*see also* Flyback converter)
  - 3 $\phi$ ac-dc rectifier, 615-616, 619
  - averaged switch model, DCM, 370-381
  - as cascaded buck and boost converters, 138-141
  - current-programmed
    - averaged switch model, DCM, 438-444
    - more accurate model, CCM, 430-432
    - simple model, CCM, 419-423
    - small-signal ac model, DCM, 445-447
  - dc-3 $\phi$ ac inverter, 71-72, 615-616
  - DCM characteristics, 115, 127-129, 381
  - as low-harmonic rectifier, 598-599
  - manipulation of ac model into canonical form, 248-251
  - nonideal, state-space averaged model of, 227-232
  - noninverting version, 139, 148-149
  - as rotated three-terminal cell, 141-142
  - small-signal ac model, CCM, 208-210, 251
  - small-signal ac model, DCM, 382-388
  - transfer functions, CCM, 289-293
  - transformer isolation in, 166-171
- Buck converter (*see also* Bridge configuration, Forward converter, Push-pull isolated converters), 6, 15-23, 34-35
  - active switch utilization in, 179
  - averaged switch model, 239-245
  - current-programmed

- averaged switch model, CCM, 423-427
- averaged switch model, DCM, 442-447
- small-signal ac model, CCM, 421-427, 431-438
- small-signal ac model, DCM, 442-447
- equivalent circuit modeling of,
  - small-signal ac, CCM, 208-210, 251
  - small-signal ac, DCM, 385-388, 393-400
  - steady-state, CCM, 51-53
  - steady-state, DCM, 380-381
- as high power factor rectifier
  - single phase, 599
  - three phase, 614-615
- multi-resonant realization, 729
- quasi-square-wave resonant realizations, 730-731
- quasi-resonant realizations
  - ac modeling of, 732-737
  - zero current switching, 662-663, 712-722, 723-724
  - zero voltage switching, 728
- small-signal ac model
  - CCM, 208-210, 251
  - DCM, 385-390
- steady-state analysis of,
  - CCM, 17-22, 23, 34-35, 51-53
  - DCM, 111-121, 380-381
- switching loss in, 94-101, 241-245
- employing synchronous rectifier, 73-74
- transfer functions, CCM, 292-293
- Buck<sup>2</sup> converter, 149, 151
- Buck 3 $\phi$  inverter (*see* Voltage source inverter)
- Canonical circuit model, 245-251
  - via generalized switch averaging, 402-403
  - manipulation into canonical form, 248-251
  - parameters for buck, boost, buck-boost, 251
  - physical development of, 245-248
  - transfer functions predicted by, 247-248, 292-293
- Capacitor amp-second balance (*see* Capacitor charge balance)
- Capacitor charge balance
  - boost converter example, 27
  - Cuk converter example, 31-32
  - definition, 24
  - in discontinuous conduction mode, 115
  - nonideal boost converter examples, 45, 55
- Capacitor voltage ripple
  - boost converter example, 28-29
  - buck converter example, 34-35
  - in converters containing two-pole filters, 34-35
  - Cuk converter example, 32-34
- Cascade connection of converters, 138-141
- Characteristic value  $\alpha$  (current programmed mode), 414, 417-418, 435-436
- Charge balance (*see* Capacitor charge balance)
- Circuit averaging (*see also* Averaged switch modeling), 231-245
  - averaging step, 235
  - boost converter example, 233-238

- linearization, 235-238
- obtaining a time-invariant network, 234-235
- summary of, 231-233
- Commutation
  - failure, 574
  - notching, 575
  - in 3 $\phi$  phase controlled rectifier, 573-575
- Compensators (*see also* Control system design)
  - design example, 346-354
  - lag, 343-345
  - lead, 340-340, 350-351
  - PD, 340-343, 350-351
  - PI, 343-345
  - PID, 345-346, 352-354
- Complex power, 550-551
- Computer power supply, 8-9
- Computer spreadsheet, design using, 180-183
- Conduction loss (*see* Copper loss, Semiconductor conduction loss)
- Conductivity modulation, 75, 79, 82, 87, 90
- Control system design (*see also* Compensators, Negative feedback), 323-368
  - compensation, 340-346
  - construction of closed-loop transfer functions, 326-332
  - design example, 346-354
  - for low-harmonic rectifiers
    - approaches, 634-652
    - modeling, 645-652
  - phase margin
    - test, 333-334
    - vs. closed-loop damping factor, 334-338
  - stability, 332-339
  - voltage regulator
    - block diagram, 324-325, 328, 347-349
    - design specifications, 339-340
- Control-to-output transfer function
  - as predicted by canonical model, 248
  - of CCM buck, boost, and buck-boost converters, 292-293
  - of current programmed converters, 422, 427-428, 434-437, 446
  - of DCM converters, 387-390, 396-399
  - of quasi-resonant converters, 733, 736
- Conversion ratio  $M$  (*see also* Switch conversion ratio  $\mu$ )
  - of boost, 18, 26, 127, 381
  - of buck, 18, 120, 381
  - of buck-boost, 18, 128, 381
  - of Cuk converter, 32, 381
  - of loss-free resistor networks, 376-381
  - in low-harmonic rectifiers, 593-595
  - modeling of, 40-43
  - of quasi-resonant converters, 711, 720-723
  - of parallel resonant converter, 676-678, 686-689
  - of SEPIC, 151, 381
  - of series resonant converter, 671-674, 679-686
  - via sinusoidal approximation, 670
- Copper loss

- allocation of window area to minimize, 513-517, 519
- high frequency effects
  - skin effect, 475-476
  - proximity effect, 476-490
- inductor design to meet specified, 503-509
- low frequency, 474
- modeling in converters, 43-53
- Core loss, 471-474, 518
- Coupled inductors
  - in Cuk converter, 494-495, 501
  - in multiple-output buck-derived converters, 501-502, 511
- Crossover frequency, 330-334
- Cuk converter
  - 3 $\phi$ ac-dc converter, 615-616
  - active switch utilization of, 179
  - as cascaded boost and buck converters, 141
  - conversion ratio  $M(D)$ , 32, 381
  - DCM averaged switch model of, 379-381
  - as low-harmonic rectifier, 597-599, 608
  - as rotated three-terminal cell, 141-142
  - steady-state analysis of, 29-34
  - transformer design example, 524-528
  - with transformer isolation, 176-177
- Current-fed bridge, 148, 150
- Current injection, 359-360
- Current programmed control, 408-451
  - ac modeling of
    - via averaged switch modeling, CCM, 423-428
    - via averaged switch modeling, DCM, 438-447
    - CCM more accurate model, 428-438
    - CCM simple approximation, 418-428
  - artificial ramp, 414-418
  - controller circuit, 409, 415
  - controller small-signal block diagram, 428-432
  - in half-bridge buck converters, 159, 410
  - in low harmonic rectifiers, 636-639
  - oscillation for  $D > 0.5$ , 411-418
  - in push-pull buck converters, 166, 410
- Current ripple (*see* inductor current ripple)
- Current sense circuit, isolated, 187-188
- Current source inverter (CSI), 146, 148
- Cycloconverter, 1, 72
- Damping factor  $\zeta$  (*see also*  $Q$ -factor), 277
- Dc conversion ratio (*see* Conversion ratio  $M$ )
- Dc link, 10
- Dc transformer model
  - in averaged switch models, 237-244, 760-762
  - in canonical model, 245-247, 250-251
  - in circuit averaged models, 237-238
  - comparison with DCM model, 377
  - derivation of, 40-43
  - equivalence with dependent sources, 41
  - manipulation of circuits containing, 41-42, 48-49

- in a nonideal boost converter, 48-49, 56
- in a nonideal buck converter, 52-53
- in small-signal ac CCM models, 208-210
- Decibel, 262
- Delta-wye transformer connection, 582-583
- Dependent power source (*see* Power source element)
- Derating factor, 180
- Design-oriented analysis, techniques of
  - analytical expressions for asymptotes, 275-276
  - approximate factorization, 285-288
  - doing algebra on the graph, 296-309
  - frequency inversion, 271-272
  - graphical construction
    - of Bode plots, 296-309
    - of closed-loop transfer functions, 329-332
  - low  $Q$  approximation, 282-284
  - philosophy of, 261, 306-307
- Differential connection of load
  - polyphase inverter, 143-148
  - single-phase inverter, 142-143
- Diode
  - antiparallel, 67
  - characteristics of, 78
  - fast recovery, 77
  - forward voltage drop (*see also* Semiconductor conduction losses), 53-57, 77
  - freewheeling, 67
  - parallel operation of, 77-78
  - recovered charge  $Q_r$ , 76, 97-100, 692, 729
  - recovery mechanisms, 76-77, 98-100
  - Schottky, 74, 77, 101
  - soft recovery, 98-99
  - snubbing of, 99
  - switching loss, 97-100, 101-103, 692
  - switching waveforms, 75-77, 98-100, 101-102
  - zero current switching of, 101-103, 690-692, 696, 725-726
  - zero voltage switching of, 692-696, 725-726, 729, 734
- Discontinuous conduction mode (DCM)
  - $B$ - $H$  loop, effect on, 503-504
  - boost converter example, 121-127
  - buck converter example, 111-121
  - buck-boost converter example, 370-381
  - in current programmed converters, 438-447
  - equivalent circuit modeling of, 369-381, 438-444
  - in forward converter, 159
  - in line-commutated rectifiers, 564-568, 569-570
  - in low-harmonic rectifiers
    - boost rectifier, single phase, 594-597
    - single-switch, three-phase, 615-619
  - mode boundary
    - in boost rectifier, 594-697
    - vs.  $K$ , 111-115, 121-122, 128
    - vs. load current and  $R_e$ , 381
    - origin of, 111-115
  - in parallel resonant converter, 687-689

- in PWM converters, 110-134, 369-407, 438-447
- in series resonant converter, 681-683
- small-signal ac modeling of, 382-403
- Displacement factor, 548, 550-551
- Distortion factor (*see also* Total harmonic distortion), 548-550
  - of single-phase rectifier, 548, 563-566
- Distributed power system, 9
- Doing algebra on the graph (*see* Graphical construction of Bode plots)
- Duty ratio
  - complement of, 16
  - definition of, 15-16
- EC core data, 754
- Eddy currents
  - in magnetic cores, 472
  - in winding conductors, 474-477
- EE core data, 753
- Effective resistance  $R_e$ 
  - in DCM averaged switch model, 374-381
  - in loss-free resistor model, 374-381
  - in resonant converter models
    - with capacitive filter network, 666-668
    - with inductive filter network, 674-676
- Emulated resistance  $R_e$ , 590-593
- Efficiency, 2
  - averaged switch modeling, predicted by, 245
  - of boost converter
    - as low-harmonic rectifier, 632-634
    - nonideal dc-dc, 49-51, 56
  - calculation via averaged model, 49-51, 56
  - vs. switching frequency, 103-104
- Equivalent circuit modeling
  - by canonical circuit model, 245-251
  - of CCM converters operating in steady-state, 40-61
  - of converters having pulsating input currents, 51-53
  - of current programmed switch networks
    - CCM, 423-428
    - DCM, 438-447
    - small-signal models, 421-422, 423-428, 445-447
  - of flyback converter, CCM, 168, 216-218
  - of ideal rectifiers, 590-593, 608-611
  - of ideal dc-dc converters, 40-42
  - of inductor copper loss, 43-51
  - small-signal models
    - CCM, 207-209, 230-232
    - DCM, 382-390
    - current programmed, 421-422, 424-428, 438-447
  - of switching loss, 241-245
  - of switch networks
    - CCM, 239-242
    - DCM, 370-381
  - of systems containing ideal rectifiers, 602
- Equilibrium (*see* Steady state)
- Equivalent series resistance (esr) of capacitor, 554-555
- ETD core data, 754



- Evaluation and design of converters, 177-183
- Experimental techniques
  - measurement of impedances, 312-314
  - measurement of loop gains
    - by current injection, 359-360
    - by voltage injection, 357-359
    - of an unstable system, 360-361
  - measurement of small-signal transfer functions, 309-311
- Factorization, approximate
  - approximate roots of arbitrary-degree polynomial, 282-288
  - graphical construction of Bode diagrams, 296-309
  - low- $Q$  approximation, 282-284
- Faraday's law, 456-457
- Feedback (*see* Control system design, Negative feedback)
- Ferrite
  - applications of, 499, 525, 528
  - core loss, 472, 473-474, 518
  - core tables, 751-755
  - saturation flux density, 459, 473
- Fill factor (*see*  $K_u$ )
- Filter inductor
  - $B$ - $H$  loop of, 497, 499
  - design of
    - derivation of procedure, 503-508
    - step-by-step procedure, 508-509
- Flux  $\Phi$ , 456
- Flux density  $B$ 
  - definition, 456
  - saturation value  $B_{sat}$ , 458-459
- Flux-linkage balance (*see* Inductor volt-second balance)
- Flyback converter (*see also* Buck-boost converter)
  - active switch utilization, 178-179
  - derivation of, 166-167
  - nonideal, ac modeling of, 209-218
  - single-switch rectifier, 3 $\phi$ ac-dc DCM, 623
  - spreadsheet design example, 180-183
  - steady-state analysis of, 166-170
  - two transistor version, 185-186
  - utilization of flyback transformer, 170-171
- Flyback transformer, 166-167, 170-173, 502-503, 619
- Forced commutation of SCRs, 90
- Forward converter (*see also* Buck converter), 159-164
  - active switch utilization, 179
  - spreadsheet design example, 180-183
  - steady-state analysis of, 159-164
  - transformer reset mechanisms, 162-163
  - transformer utilization in, 164
  - two transistor version, 163-164
- Four-quadrant switches (*see* Switch)
- Freewheeling diode, 67
- Frequency modulator, 732-733
- Gate turn-off thyristor (GTO), 92
- Generalized switch averaging, 390-403

- Geometrical constant (*see*  $K_g$ ,  $K_{gfe}$ )
- Graphical construction of Bode plots (*see also* Bode plots, Design-oriented analysis)
  - of converter transfer functions, 307-309
  - division, 307-309
  - of harmonic trap filters, 576-582
  - parallel combinations, 301-307
  - parallel resonance, 301-303
  - of parallel resonant converter, 677
  - series combinations, 296-301
  - series resonance, 298-301
  - of series resonant converter, 671-672
- Grounding problems, 312-314
- Gyrator, 682-683
- Harmonic correction, 621
- Harmonic loss factor  $F_H$ , 488-490
- Harmonics in power systems
  - average power vs. Fourier series, 542-543
  - distortion factor, 548
  - harmonic standards, 555-559
  - neutral currents, 552-553
  - power factor, 546-550
  - root-mean-square value of waveform, 543-546
  - rectifier harmonics, 548-550
  - in three-phase systems, 551-555
  - total harmonic distortion, 548
- Harmonic trap filters, 575-582
  - bypass resistor, 580-582
  - parallel resonance in, 577-579
  - reactive power in, 582
- H-bridge, 7-8, 142-145, 148-150
- Hold-up time, 601
- Hot spot formation, 77-78, 85-86
- Hysteresis loss  $P_H$ , 471-472
- Hysteretic control, 639-641
- Ideal rectifier (*see also* Low harmonic rectifiers), 590-626
  - in converter systems, 599-604
  - properties of, 590-593
  - realization of
    - single phase, 593-599
    - three phase, 608-622
  - rms values of waveforms in, 604-608
- IEC-555, 556-557
- IEEE/ANSI standard 519, 557-559
- Impedance graph paper, 307
- Inductor copper loss (*see* Copper loss)
- Inductor current ripple
  - in ac inductor, 499-500
  - boost example, 28
  - buck example, 21
  - calculation of, 21
  - in converters containing two-pole filters, 34-36
  - Cuk converter example, 32-33
  - in filter inductor, 497-499

- magnitude vs. DCM, 111-113
- Inductor design
  - ac inductor design
    - derivation, 531-533
    - step-by-step procedure, 533-534
  - filter inductor design
    - derivation, 503-508
    - step-by-step procedure, 508-509
- Inductor volt-second balance
  - boost example, 25-26
  - buck example, 22-23
  - Cuk converter example, 31-32
  - definition, 22
  - in discontinuous conduction mode, 115
- Input port, converter
  - ac modeling of, 203
  - boost static characteristics, 596-597, 639
  - modeling of, via state-space averaging, 200, 227, 231
  - steady-state modeling of, 51-53
- Inrush current, 601-602
- Insulated-gate bipolar transistor (IGBT)
  - construction and operation of, 87-90
  - current tailing in, 88-89, 96-97
  - equivalent circuit, 88
  - forward voltage drop, modeling of, 89
  - idealized switch characteristics, 65-66
  - parallel operation of, 89
  - switching loss in, 96-97
- Inversion of source and load, 136-137
- Inverters, 1
  - high frequency, 659-662, 697-705
  - line commutated, 572-573
  - single phase, 7-8, 68-69
  - sinusoidal analysis of resonant converters, 664-670, 697-705
  - three phase, 70, 143-148
- Iron laminations, 459, 473
- $K$ , dimensionless parameter
  - critical value  $K_{crit}(D)$ , 114-115, 121-122, 128
  - in current programmed mode analysis, 438
  - and DCM boundary, 114-115, 121-122, 128
  - in line-commutated rectifier analysis, 565-566
  - in steady-state DCM analysis, 120, 127-128
- $K_g$ , core geometrical constant
  - definition of, 507-507, 751
  - ferrite core tables of, 752-755
  - filter inductor design procedure using, 508-509
- $K_{ge}$ , ac core geometrical constant
  - ac inductor design procedure using, 531-534
  - definition of, 521, 751
  - ferrite core tables of, 752-755
  - transformer design using,
    - derivation, 517-521
    - examples, 524-531
    - step-by-step procedure, 521-524

- $K_L$ , rectifier dimensionless parameter, 565-566
- $K_u$ , window utilization factor, 507
- LCC resonant converter
  - dependence of transistor current on load, 701-702
  - introduction to, 659-661
  - ZVS/ZCS boundary, 703-705
- Lenz's law, 457, 472, 475
- Linear ripple approximation (*see* Small ripple approximation)
- Line-to-output transfer function  $G_{vg}(s)$ 
  - of the buck, boost, and buck-boost converters in CCM, 292-293
  - canonical model, as predicted by, 247-248
  - closed-loop, 326-327, 331-332
  - control system design of, 340, 353-354
  - of current-programmed converters, 422, 427-428, 437-438
  - of DCM converters, 387-388
  - of quasi-resonant converters, 736
- Litz wire, 487
- Loop gain (*see also* Control system design, Negative feedback)
  - definition, 327
  - measurement of, 355-361
- Loss-free resistor model
  - averaged switch model of discontinuous conduction mode, 374-381
  - ideal rectifier model
    - single phase, 590-593
    - three phase, 608-611
- Low harmonic rectifiers (*see also* Ideal rectifiers)
  - controller schemes
    - average current control, 634-636
    - current programmed control, 636-640
    - feedforward, 635-636
    - hysteretic control, 639-641
    - nonlinear carrier control, 641-645
  - modeling of
    - efficiency and losses, 627-634
    - low-bandwidth control loop, 645-650
    - wide-bandwidth average current control loop, 650-652
  - rms calculations in, 604-609
- Low  $Q$  approximation, 282-284
- Magnetic circuits, 463-466
- Magnetic field  $H$ , 455-456
- Magnetic path length  $l_m$ 
  - definition, 461
  - ferrite core tables, 752-755
- Magnetics, 453-538
  - ac inductor design, 531-534
  - basic relations, 455-462
  - copper loss, 474
  - core loss, 471-474
  - ferrite core tables, 752-755
  - filter inductor design, 503-509
  - magnetic circuits, 463-466
  - magnetic devices, types of, 497-503
  - optimizing  $B_{max}$  to minimize total loss, 520-521
  - optimizing window allocation to minimize copper loss, 513-517

- proximity effect, 476-490
- transformer basics, 152-154, 466-471
- transformer design, 517-531
- Magnetizing current, 152-153, 458-469
- Magnetomotive force (MMF)
  - definition, 455-456
  - MMF diagrams, 479-482
- Majority carrier devices (*see also* MOSFET, Schottky diode), 74-75
- Matrix converter, 72-73
- Mean length per turn (*MLT*)
  - definition, 507-508
  - ferrite core tables, 752-755
- Measurement of transfer functions and loop gains (*see* Experimental techniques)
- MIL-STD-461B, 556
- Minority carrier devices (*see also* Bipolar junction transistor, Diode, Gate turn-off thyristor, Insulated-gate bipolar transistor, MOS-controlled thyristor, Silicon controlled rectifier), 74-75
- Modulation index, 613-614
- MOS-controlled thyristor (MCT), 92-94
- MOSFET
  - body diode, 67-68, 79-80
  - conduction loss, modeling of, 53-57, 209-218
  - construction and operation of, 78-82
  - on resistance, 53-57, 79-82
  - switching loss owing to  $C_{ds}$ , 100-101
  - as synchronous rectifier, 73-74
  - terminal capacitances, 81
  - typical characteristics, 80-82
  - zero-voltage and zero-current switching of, 689-696
- Motor drive system, 9-10
- Multiplying controller (*see also* Average current control, Current programmed control), 596
- Multi-resonant switch
  - single-switch 3 $\phi$  buck rectifier, 620-621
  - zero-voltage switching dc-dc, 729
- Negative feedback (*see also* Control system design)
  - effects of, on network transfer functions, 326-329
  - objectives of, 193-194, 323-326
  - reduction of disturbances by, 327-329
  - reduction of sensitivity to variations in forward gain by, 329
- Nonlinear carrier control, 641-645
- Nonminimum-phase zero (*see* Right half-plane zero)
- Output characteristics
  - of the parallel resonant converter, 689
  - of resonant inverters, 699-700
  - of the series resonant converter, 685-686
- Overshoot, 338-340
- Parallel resonant converter
  - analysis via sinusoidal approximation, 664-670, 674-678
  - dependence of transistor current on load, 702
  - exact characteristics
    - continuous conduction mode, 686-687
    - control plane, 689
    - discontinuous conduction mode, 687-689
    - output plane, 689

- introduction to, 659-660
- as a low harmonic rectifier, 597
- Permeability  $\mu$ 
  - definition, 458-460
  - of free space,  $\mu_0$ , 458
  - relative,  $\mu_r$ , 458
- Phase asymptotes
  - of complex poles, 279-282
  - inverted forms, 272
  - of real pole, 266-268
  - of real zero, 269
  - of RHP zero, 270
- Phase control
  - of resonant converters, 659
  - of three-phase rectifiers, 570-575
  - of zero-voltage transition dc-dc converter, 696
- Phase margin
  - vs. closed-loop damping factor, 334-338
  - stability test, 333-334
- Poles
  - complex, Bode plots of, 276-282
  - the low  $Q$  approximation, 282-284
  - real, Bode plots of, 263-268
- Pot core data, 752
- Powdered iron, 459, 473
- Power factor (*see also* Total harmonic distortion, Displacement factor, Distortion factor)
  - definition of, 546-550
  - of bridge rectifier, single phase, 566
  - of peak detection rectifier, 548-550
  - of phase-controlled rectifier, three phase, 573
- Power sink element (*see* Power source element)
- Power source element
  - in averaged switch models
    - current programmed mode, CCM, 423-428
    - current programmed mode, DCM, 438-447
    - discontinuous conduction mode, 370-382
  - definition of, 375-377
  - in ideal rectifier model, 592, 599-603, 608-610
  - linearization of, 384-385, 425-426
  - in loss-free resistor model, 376-379
  - properties of, 375-377
- PQ core data, 755
- Proximity effect
  - conductor spacing factor  $\eta$ , 478
  - interleaving, effect on, 485-487
  - layer copper loss, 482-483
  - Litz wire, effect of, 487
  - MMF diagrams, 479-482
  - PWM waveform harmonics, 487-490
  - simple explanation, 476-478
  - transformer design procedure, accounting for, 519
  - winding loss, total, 483-487

- Pulse width modulation (PWM), 6-8, 17
  - modulator ac model, 253-254
  - operation of modulator, 252
  - spectrum of PWM waveform, 194-195
- Push-pull isolated converters
  - based on boost converter, 173
  - based on buck converter, 164-166, 410
  - Watkins-Johnson converter, 173
- $Q$  factor, 277-282
  - canonical model, predicted by, 309
  - closed-loop, vs. phase margin, 334-338
  - of the CCM buck, boost, and buck-boost converters, 293
  - the low  $Q$  approximation, 282-284
  - vs. overshoot, 338-339
  - of parallel resonant circuit, 303
  - of series resonant circuit, 300-301
- Quasi-resonant converters (*see also* Multi-resonant switch, Quasi-square-wave switch)
  - ac modeling of, 732-737
  - single-switch 3 $\phi$  buck rectifiers
    - multi-resonant, 620-621
    - zero current switching, 619-620
  - zero-current switching dc-dc
    - full wave, 723-724
    - half wave, 713-723
  - zero-voltage switching dc-dc, 726-728
- Quasi-square-wave converters, 730-731
- Quasi-static approximation, 661
- Quiescent operating point, 196-197, 204, 225
- Reactance graph paper (*see* Impedance graph paper)
- Reactive power
  - definition, 550-551
  - in harmonic trap filters, 582
  - in phase-controlled rectifiers, 573
- Rectifiers (*see also* Ideal rectifiers, Low harmonic rectifiers), 1
  - energy storage in single-phase, 599-604
  - high quality, 541
  - ideal, 590-626
  - line-commutated
    - phase control of, 570-575
    - single-phase, 548-550, 562-568
    - three-phase, 568-575
    - three-phase transformer connections in, 582-584
    - twelve pulse, 582-584
  - in resonant dc-dc converter, 666-668, 674-676
- Regulator system (*see also* Control system design), 192-193, 323-326, 634-645
- Reluctance, 463-466
- Resonance
  - Bode plots of complex poles, 276-282
  - graphical construction examples, 296-309
  - the low- $Q$  approximation, 282-284
  - parallel resonant network, 301-307
  - series resonant network, 301-307
- Resonant converters (*see also* Quasi-resonant converters, Multi-resonant converters, Quasi-square-wave converters, Zero voltage transition converter), 659-710

- analysis of, via sinusoidal approximation, 664-679
- LCC, 659-661, 701-705
- parallel, 597, 659-660, 674-678, 686-690, 702
- resonant link, 662
- series, 659-674, 679-686, 690-695, 702
- Resonant link converters, 662
- Resonant switches (*see* Quasi-resonant converters, Multi-resonant switch, Quasi-square-wave converters)
- Right half-plane zero
  - Bode plot of, 269-271
  - physical origins of, 294-295
- Ripple, switching, 17-19, 111-113, 194-196
- Root mean square value
  - of commonly-observed converter waveforms, 743-750
  - vs. Fourier series, 543-546
  - of near-ideal rectifier currents, table of, 609
  - of near-ideal rectifier waveforms, 604-609
- Rotation of three-terminal cell, 141-142
- Saturation
  - of inductors, 462, 465-466
  - of magnetic materials, 458-460
  - of transformers, 153-154, 469
- Schottky diode, 74, 77, 101
- Semiconductor conduction loss
  - boost converter example, 53-57
  - inclusion in ac model, 209-218
  - with synchronous rectifier, 73-74
- Semiconductor cost, 180
- Semiconductor power devices (*see also* Bipolar junction transistor, Diode, Gate turn-off thyristor, Insulated-gate bipolar transistor, MOS-controlled thyristor, Schottky diode, Silicon controlled rectifier), 62-109
  - charge control of, 75, 83-85, 94, 98, 101-103
  - conductivity modulation, 75
  - majority vs. minority carriers, 74-75
  - realization of switches using, 62-74
- SEPIC (*see* Single-ended primary inductance converter)
- Series pass regulator, 4-5
- Series resonant converter
  - analysis via sinusoidal approximation, 664-674
  - dependence of transistor current on load, 702
  - exact characteristics
    - continuous conduction mode, 679-681
    - control plane, 684
    - even discontinuous conduction mode, 682
    - odd discontinuous conduction mode, 681
    - output plane, 685-686
  - introduction to, 659-664
  - subharmonic modes in, 673-674
  - zero-current switching in, 690-692
  - zero-voltage switching in, 692-695
- Silicon area (*see* Switch stress)
- Silicon controlled rectifier (SCR)
  - construction and characteristics of, 89-92
  - equivalent circuit, 90



- inverter grade, 91
- Silicon steel, 459, 473
- Single-ended primary inductance converter (SEPIC), 38, 148
  - averaged switch model of
    - continuous conduction mode, 757-762
    - discontinuous conduction mode, 379-381
  - conversion ratio  $M(D)$ , 151, 381
  - inverse of, 151, 176
  - as low-harmonic rectifier, 597-599, 608-609
  - transformer isolation in, 174-176
- Single quadrant switch
  - definitions, 63-64
  - implementation, 64-67
  - origins of DCM, 110-113
- Sinusoidal approximation, 663, 664-679
- Sinusoidal PWM, 612-614
- Skin effect (*see also* Proximity effect), 472-476
- Slope compensation (*see* Artificial ramp)
- Small ripple approximation
  - in ac modeling approach, 198, 223-224
  - and average power loss, prediction of, 57
  - boost example, 25
  - buck example, 20
  - Cuk converter example, 30-31
  - definition, 19
  - in discontinuous conduction mode, 116
  - failure of, in two-pole filters, 34-36
- Small-signal ac modeling
  - via averaged switch modeling, 239-245
  - via circuit averaging, 231-245
  - of CCM converters, 193-260
  - of current programmed converters, 418-447
  - of DCM converters, 382-403
  - via generalized switch averaging, 390-403
  - of low harmonic rectifiers, 645-652
  - of quasi-resonant converters, 732-737
  - of resonant converters, 678
  - via state-space averaging, 218-231
- Snubber networks, 86, 94, 99, 696
- Soft switching (*see also* Zero current switching, Zero voltage switching), 689-696
- Spacecraft power system, 9
- Spreadsheet design of converters, 180-183
- State equations of a network, 218-221
- State-space averaging, 218-231
  - discussion, 223-226
  - example: nonideal buck-boost converter, 227-231
  - summary of result, 221-222
- Steady state
  - inductor current waveform, 22
  - operating point, 196-197, 204, 225
- Subharmonic
  - modes of series resonant converter, 673-674
  - number  $\xi$ , 679

## Switch

- averaged modeling of, 239-245, 377, 390-403
  - current-bidirectional two-quadrant, 67-70
  - four-quadrant, 71-73
  - ideal SPDT in converters, 4-6, 15-16, 24, 29
  - ideal SPST, 62-63
  - passive vs. active, 64-65, 91
  - power dissipated by ideal, 6, 17
  - quasi-resonant, 711-737
  - realization of, using semiconductor devices, 62-74
  - single-quadrant, 64-67
  - synchronous rectifier, 73-74
  - voltage-bidirectional two-quadrant, 70-71
- Switch conversion ratio  $\mu$
- definition, 392
  - DCM buck example, 395-401
  - in generalized canonical model, 405
  - of multi-resonant switch, 729
  - of quasi-resonant switches
    - full-wave ZCS, 723-724
    - full-wave ZVS, 727
    - half-wave ZCS, 713, 720-721
    - half-wave ZVS, 727
    - small-signal ac modeling using, 732-737
  - of quasi-square-wave switches, 731
- Switched mode, 3-4
- Switching frequency
- converter efficiency vs., 103-104
  - definition of, 16
  - transformer size vs., 527
- Switching harmonics (*see also* Ripple, switching), 6
- removal of via averaging, 194-196
- Switching loss (*see also* Soft switching, Zero current switching, Zero voltage switching)
- averaged switch modeling of, 241-245, 259-260
  - with clamped inductive load, 94-97
  - and current tailing, 96-97
  - and device capacitances, 100-101
  - and diode recovered charge, 97-100, 101-103
  - effect on converter efficiency, 103-104
  - and ringing waveforms, 101-103
  - and stray inductances, 100-101
- Switch stress  $S$ , 177-180
- Switch utilization  $U$ , 177-180
- Synchronous rectifier, 73-74
- Temperature rise
- in a converter, 2
  - in magnetics, 752
- Thyristor (*see* Gate turn-off thyristor, MOS-controlled thyristor, Silicon controlled rectifier)
- Topologies of converters (*see also* Boost, Bridge configuration, Buck, Buck-boost, Cuk converter, Forward converter, Transformer-isolated converters, etc.)
- Cascade connections, 138-141
  - Converter synthesis, 146-150

- Differential connection of load, 142-146
- Evaluation and comparison, 177-183, 608-609
- Inversion of source and load, 136-137
- Low-harmonic single-phase rectifiers, 593-599
- Low-harmonic three-phase rectifiers, 608-621
- Quasi-resonant converters, 724-731
- Resonant converters, 659-664
- Rotation of three-terminal cell, 141-142
- Transformer isolation, 150-177
- Total harmonic distortion (THD)
  - of current-programmed rectifiers, 639
  - definition, 550
  - vs. distortion factor, 550-551
  - IEEE-519 limits, 559-561
  - of peak detection rectifier, 551-552
  - of single-phase bridge rectifiers, 551-552, 566-570
  - of three-phase bridge rectifiers, 571-572, 575
- Transfer functions (*see also* Bode plots)
  - of the buck, boost, and buck-boost converters, 292-293
  - of current programmed converters, 422-423, 427, 436-438, 446-447
  - of DCM converters, 388-390
  - graphical construction of, 296-309
  - of low-harmonic rectifiers, 649-650, 651
  - measurement of, 309-311
  - predicted by canonical model, 247-248, 292-293
- Transformer connections in three-phase rectifiers, 582-584
- Transformer-isolated converters, 150-177
  - boost-derived topologies, 171-173
  - Cuk converter, 176-177
  - evaluation and comparison of, 177-183
  - flyback, 166-171
  - forward, 159-164
  - full bridge buck-derived, 154-157
  - half-bridge buck-derived, 157-159
  - multiple outputs and cross regulation, 151-152
  - push-pull buck-derived, 164-166
  - SEPIC, 174-176
  - transformer model, 152-154, 466-471
  - use of volt-second balance in, 153-154, 156-157
- Transformers
  - $B$ - $H$  loop in, 153, 500-501
  - design of,
    - derivation of procedure, 517-521
    - examples, 524-531
    - step-by-step procedure, 521-524
    - winding area optimization, 513-517
  - flyback transformer, 166-167
  - leakage inductance, 154, 469-471
  - magnetizing inductance, 152-154, 468-469
  - modeling of, 152-154, 466-471
  - SEPIC transformer, 174-175
  - volt-second balance in, 153-154, 156-157
- Triplen harmonics
  - in three-phase four-wire networks, 552-553

- in three-phase inverter modulation schemes, 614
- in three-phase rectifier circuits, 568-569
- in three-phase three-wire networks, 553-554
- Twelve-pulse rectifier, 582-584
- Two-quadrant switches (*see* Switch)
- Universal-input rectifiers, 602
- Variable-speed ac drive, 7-8
- Voltage conversion ratio (*see* Conversion ratio  $M$ )
- Voltage injection, 357-359
- Voltage-source inverter, 70, 146-147
- Volt-second balance (*see* Inductor volt-second balance)
- Watkins-Johnson converter, 148, 150, 173
  - inverse of, 148, 150
  - isolated push-pull, 173
- Window area  $W_A$ 
  - allocation of, to minimize total copper loss, 513-517
  - definition, 506-507
  - ferrite core tables, 752-755
- Window utilization factor  $K_u$ , 507
- Wire area  $A_w$ 
  - inductor design, 506-507, 509
  - American wire gauge (AWG) table, 755-756
- Zero-current switching (ZCS), 662
  - in quasi-resonant converters, 712-726
  - in quasi-square-wave converters, 730-731
  - in series resonant converter, 690-692
  - in single-switch three-phase low-harmonic rectifiers, 619-621
  - ZCS/ZVS boundary, 702-705
- Zero-voltage switching (ZVS), 662
  - in LCC resonant converter, 703-705
  - in multi-resonant converters, 729
  - in quasi-resonant converters, 726-728
  - in quasi-square-wave converters, 730-731
  - in series resonant converter, 692-695
  - in single-switch three-phase low-harmonic rectifiers, 619-621
  - in zero-voltage transition converter, 695-696
  - ZVS/ZCS boundary, 702-705
- Zero-voltage transition buck-derived converter, 695-696

# *Fundamentals of Power Electronics*

## Errata, first edition

### [Back](#)

Errors can be reported for inclusion on this list by sending email to [Bob Erickson](#). Please include page number and a short description.

- Page ii, small-print disclaimer near bottom of page contains two misspelled words
- Page 10, paragraph beginning "Design of the converter..."  
"line-to-transfer functions" should read "line-to-output transfer functions"
- Page 49, Eq. (3.19)  
RHS of equation should be divided by R
- Page 86, Fig. 4.35(a)  
Units of horizontal axis should be A
- Page 172, Fig. 6.36  
The bottom of the figure is cut off. Transistor  $Q_4$  conducts during the first subinterval of every switching period.
- Page 180, third line under heading 6.4.2  
typo "votlage" should read "voltage"
- Page 181, Table 6.2  
Values of  $L$  and  $C$  are missing. The values are:  $L = 25.96 \text{ uH}$ ,  $C = 25.0 \text{ uF}$ .
- Page 188, problem 6.8(d)  
Forward voltage drops of diodes  $D_1$  and  $D_2$  are equal to 0.7 V.
- Page 237, second line following Eq. (7.126)  
"small" should read "smaller"
- Page 241, third paragraph, first line  
reads "valiabies" -- should read "variables"
- Page 250, Equation (7.144)  
should read:  $e(s) = (V_g - V) - sLI/DD'$  (plus sign should be minus sign)
- Page 275, Figure 8.15  
Phase asymptote for frequencies between  $10 \cdot f_1$  and  $f_2/10$  should be +90 deg instead of -90 deg.
- Pages 289-293, Equation (8.112) and Table 8.2  
Missing factor of  $D'$  in Eq. (8.112). Mistake propagates to Eqs. (8.113), (8.121), (8.123), (8.124), (8.127), and Fig. 8.26. Buck-boost  $G_{d0}$  entry in Table 8.2 is also incorrect. Corrected Section 8.2.1 and Table 8.2 are in [attached pdf file](#).
- Page 300, line following Eq. (8.144)  
Should read: "Subsitution of Eq. (8.142) into Eq. (8.144) leads to"
- Page 311, last sentence

is missing a period

- Page 333, fourth line following Eq. (9.20)  
reads "simple" -- should be "simply"
- Page 347, first line of text  
Equation reference should read "Eq. (7.149)"
- Page 366, Problem 9.8, last sentence of paragraph (before (a))  
should read "The pulse-width modulator circuit obeys Eq. (7.149)." -- not "(7.132)"
- Page 385, Table 10.2  
 $g_2$  for the buck-boost converter is equal to  $2/MR_e$
- Page 419, Figure 11.12(a)  
 $i_g(t)$  is the current flowing out of the source  $v_g(t)$
- Page 427, Figure 11.20  
Value of ac resistance is inverted. The value should read:  $-R/D^2$
- Page 488, second paragraph, fourth sentence  
Change "greater" to "smaller", so that the sentence reads: "The skin depth  $d$  is smaller for high frequencies..."
- Page 516, Equations (14.14) and (14.15)  
Summation limits should be  $j = 1$  to  $k$
- Page 519, Equation (14.28)  
should contain a factor of 4 in denominator
- Page 534, Equation (14.84)  
should read:  $B_{pk} = B_{max} + LI_{dc}/nA_c$
- Page 546, Equation (15.14)  
Power loss should be  $(\text{rms voltage})^2 / R_{\text{shunt}}$
- Page 548, last sentence  
change "displacement factor" to "distortion factor"
- Page 576, end of first sentence after Eq. (16.12)  
 $i_s$  should read  $i_r$
- Page 637, Equation (18.27)  
Corrected version is in [attached pdf file](#).
- Page 654, Figure 18.20, and Problem 18.2  
Flyback transformer turns ratio is 1:1
- Appendix 3, page 760, Figure A3.3  
Polarity of dependent current source should be reversed.

---

update 10/25/99

# Fundamentals of Power Electronics

R. W. Erickson

## Solutions to Selected Problems

Solutions to selected problems at the end of chapters in the text *Fundamentals of Power Electronics* are listed below. These are intended as an educational supplement to the text, for the use of students who have purchased the book. All files copyright R. W. Erickson 1998.

These files can be read using the Adobe Acrobat viewer, available free from the [Adobe Acrobat web site](#).

[Up](#)

### Chapter 2

- [Problem 2.2](#) 144kB. Analysis of a SEPIC in a voltage regulator application.
- [Problem 2.3](#) 168kB. Inductor current and capacitor voltage ripples in the SEPIC.

### Chapter 3

- [Problem 3.3](#) 192kB. Modeling efficiency and losses in a buck converter with input filter.
- [Problem 3.6](#) 148kB. Comparison of boost and buck-boost converters in a voltage step-up application.

### Chapter 4

- [Problem 4.4](#) 196kB. Switch realization in a converter that is probably unfamiliar.

### Chapter 5

- [Problem 5.5](#) 81kB. CCM/DCM boundary for the Cuk converter.
- [Problem 5.6](#) 184kB. Solution of the Cuk converter in DCM.

### Chapter 6

- [Problem 6.1](#) 144kB. Analysis of a tapped-inductor boost converter.

## Chapter 8

- [Sample problem](#) 164kB. A solved problem on transfer function asymptotes, similar to problems 8.1 - 8.4.

## Chapter 12

- [Problem 12.1](#) 116kB. Magnetic circuit analysis.

---

Update 11/23/98 rwe



## Proximity Effect Functions

The functions below were used to generate Figs. 12.35, 12.36, and 12.38. The functions are written in Microsoft Visual Basic, and were called by an Excel spreadsheet. The functions can be easily modified for other programming languages.

Functions Gone and Gtwo implement Eq. (12.73). Function FR(phi, M) is identical to Eq. (12.84). Figure 12.32 is a plot of FR for various values of M and  $\phi$ . Figure 12.33 is a plot of FR(phi, M)/phi.

Function Pj(Phi1, M, j, D) is a normalized version of Eq. (12.89), the power loss in harmonic  $j$ . Function FH(phi1, M, D) coincides with Eq. (12.90) and (12.91). The series is summed numerically.

The copper loss in a winding is evaluated as follows. First, the dc and fundamental components of the current waveform are evaluated using Eq. (12.86). Then the functions FH and FR are evaluated. Finally, the results are plugged into Eq. (12.92).

Option Explicit

```
Function cosh(x)
    cosh = 0.5 * (Exp(x) + Exp(-x))
End Function
```

```
Function sinh(x)
    sinh = 0.5 * (Exp(x) - Exp(-x))
End Function
```

```
Function Gone(phi)
    Gone = (sinh(2 * phi) + Sin(2 * phi)) / (cosh(2 * phi) -
        Cos(2 * phi))
End Function
```

```
Function Gtwo(phi)
    Gtwo = (sinh(phi) * Cos(phi) + cosh(phi) * Sin(phi)) /
        (cosh(2 * phi) - Cos(2 * phi))
End Function
```

```
Function FR(phi, M)
    FR = phi * (Gone(phi) + 2 / 3 * (M * M - 1) * (Gone(phi) - 2
        * Gtwo(phi)))
End Function
```

```
Function pi()
    pi = 3.14159265
End Function
```


```
Function Pj(phi1, M, j, D)
    Dim sj, Ga
    sj = Sqr(j)
    Ga = Gone(phi1 * sj)
    Pj = (1 / (j * sj)) * (Sin(j * pi() * D)) ^ 2 * (Ga + 2 / 3 *
        (M * M - 1) * (Ga - 2 * Gtwo(phi1 * sj)))
End Function
```

```
Function FH(phil, M, D)
  Dim P1, Ptot, Pke, Pko, Peps, j, Pk
  P1 = Pj(phil, M, 1, D)
  Pko = P1
  Pke = Pj(phil, M, 2, D)
  Pk = Pko + Pke
  Ptot = P1
  Peps = P1 * 0.0002
  j = 3
  Do
    Pko = Pj(phil, M, j, D)
    j = j + 1
    Pke = Pj(phil, M, j, D)
    Pk = Pke + Pko
    Ptot = Ptot + Pk
    j = j + 1
  Loop Until Pk < Peps
  FH = Ptot / P1
End Function
```

Derivation of line-to-output transfer function, p. 437, Eqs. (11.84) and (11.85)


①  
Rw Erickson

Fig. 11.26

 


one method: manipulate  $\hat{v}_g$  so it appears as a disturbance (see section 9.2.1 and Fig 9.4(b))

 $\Rightarrow$  push  $\hat{v}_g$  blocks so the  $\hat{v}_g$  signal comes in near the output (at the pickoff point



②

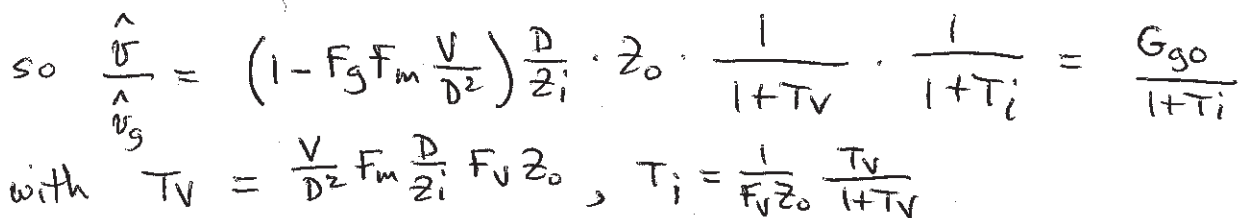

$$\text{so } \frac{\hat{v}}{\hat{v}_g} = \left(1 - F_g F_m \frac{V}{D^2}\right) \frac{D}{z_i} \cdot z_0 \cdot \frac{1}{1+T_V} \cdot \frac{1}{1+T_i} = \frac{G_{g0}}{1+T_i}$$

$$\text{with } T_V = \frac{V}{D^2} F_m \frac{D}{z_i} F_V z_0, \quad T_i = \frac{1}{F_V z_0} \frac{T_V}{1+T_V}$$

(3)

The disturbance  $\hat{v}_g$  enters at a summing node that is internal to both the  $T_V$  and  $T_i$  loops.

$$\text{Hence, } \frac{\hat{v}}{\hat{v}_g} = \underbrace{\left(1 - F_g F_m \frac{V}{D^2}\right) \frac{D}{z_i} z_o}_{\text{gain when } T_i \rightarrow 0 \text{ and } T_V \rightarrow 0} \cdot \frac{1}{1+T_V} \cdot \frac{1}{1+T_i}$$

In Eqs. (11.84) and (11.85), this transfer function is written as

$$\frac{G_{g0}}{1+T_i}$$

with  $G_{g0} = \frac{\left(1 - F_g F_m \frac{V}{D^2}\right) \frac{D}{z_i} z_o}{1+T_V}$

---

# Fundamentals of Power Electronics

Robert W. Erickson  
University of Colorado, Boulder


# Chapter 1: Introduction

---

- 1.1. Introduction to power processing
  - 1.2. Some applications of power electronics
  - 1.3. Elements of power electronics
- Summary of the course

# 1.1 Introduction to Power Processing

---

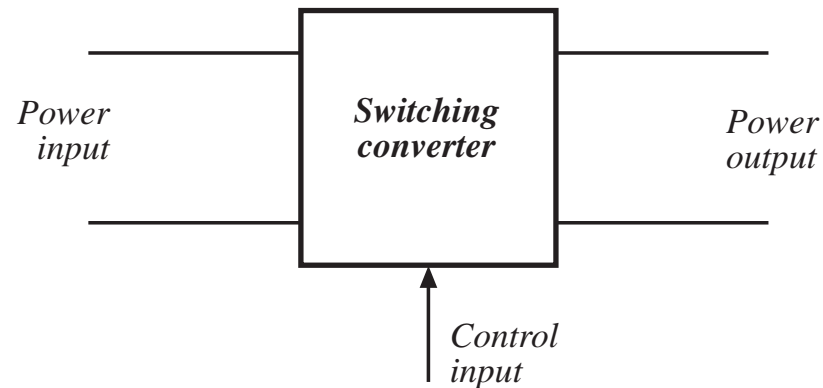


- |                               |   |
|-------------------------------|---|
| <i>Dc-dc conversion:</i>      | Change and control voltage magnitude                        |
| <i>Ac-dc rectification:</i>   | Possibly control dc voltage, ac current                     |
| <i>Dc-ac inversion:</i>       | Produce sinusoid of controllable<br>magnitude and frequency |
| <i>Ac-ac cycloconversion:</i> | Change and control voltage magnitude<br>and frequency       |



# Control is invariably required

---

 


# High efficiency is essential

---

$$\eta = \frac{P_{out}}{P_{in}}$$


$$P_{loss} = P_{in} - P_{out} = P_{out} \left( \frac{1}{\eta} - 1 \right)$$

 High efficiency leads to low  
power loss within converter  
Small size and reliable operation  
is then feasible  
Efficiency is a good measure of  
converter performance



# A high-efficiency converter


---

 

A goal of current converter technology is to construct converters of small size and weight, which process substantial power at high efficiency


# Devices available to the circuit designer

---

 

# Devices available to the circuit designer


---

 

Signal processing: avoid magnetics

# Devices available to the circuit designer

---

 

Power processing: avoid lossy elements

# Power loss in an ideal switch


---

Switch closed:  $v(t) = 0$

Switch open:  $i(t) = 0$


In either event:  $p(t) = v(t) i(t) = 0$

Ideal switch consumes zero power

 

# A simple dc-dc converter example

---

 

Input source: 100V


Output load: 50V, 10A, 500W

How can this converter be realized?




# Dissipative realization

## Resistive voltage divider


 

 
# Dissipative realization


Series pass regulator: transistor operates in active region



# Use of a SPDT switch

  
 
# The switch changes the dc voltage level



$D$  = switch duty cycle

$$0 \leq D \leq 1$$

$T_s$  = switching period


$$f_s = \text{switching frequency} \\ = 1 / T_s$$

DC component of  $v_s(t)$  = average value:

$$V_s = \frac{1}{T_s} \int_0^{T_s} v_s(t) dt = DV_g$$

 
# Addition of low pass filter

Addition of (ideally lossless)  $L$ - $C$  low-pass filter, for removal of switching harmonics:





- Choose filter cutoff frequency  $f_0$  much smaller than switching frequency  $f_s$
- This circuit is known as the “buck converter”


 
# Addition of control system for regulation of output voltage



# The boost converter

  

# A single-phase inverter

  

“H-bridge”

Modulate switch  
duty cycles to  
obtain sinusoidal  
low-frequency  
component



## 1.2 Several applications of power electronics


---

Power levels encountered in high-efficiency converters


- less than 1 W in battery-operated portable equipment
- tens, hundreds, or thousands of watts in power supplies for computers or office equipment
- kW to MW in variable-speed motor drives
- 1000 MW in rectifiers and inverters for utility dc transmission lines

# A computer power supply system

---

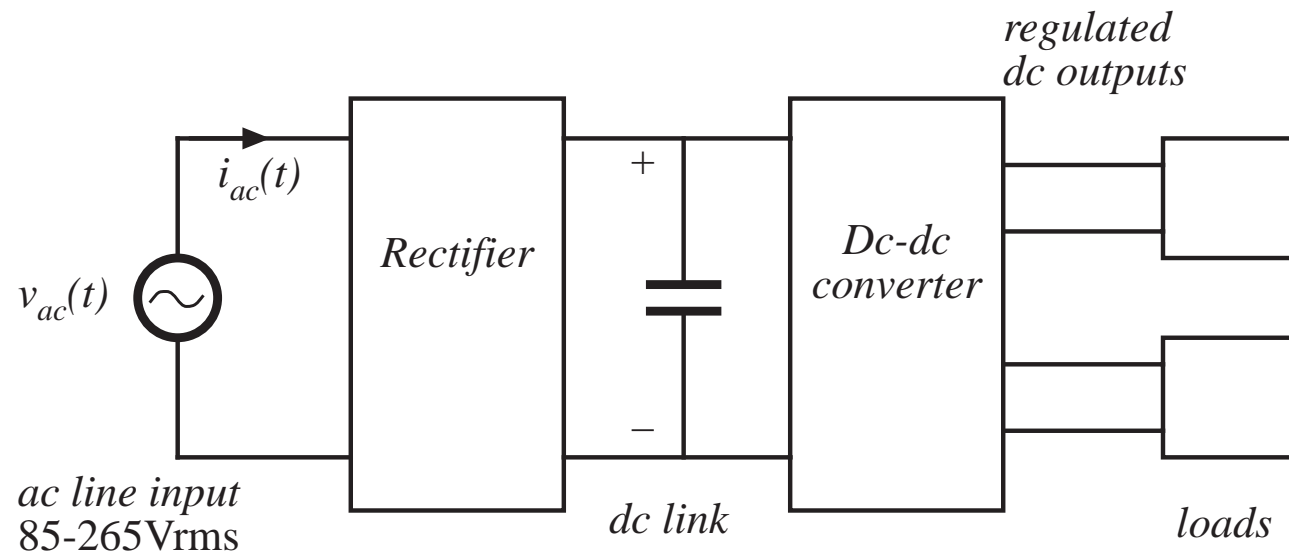


# A spacecraft power system

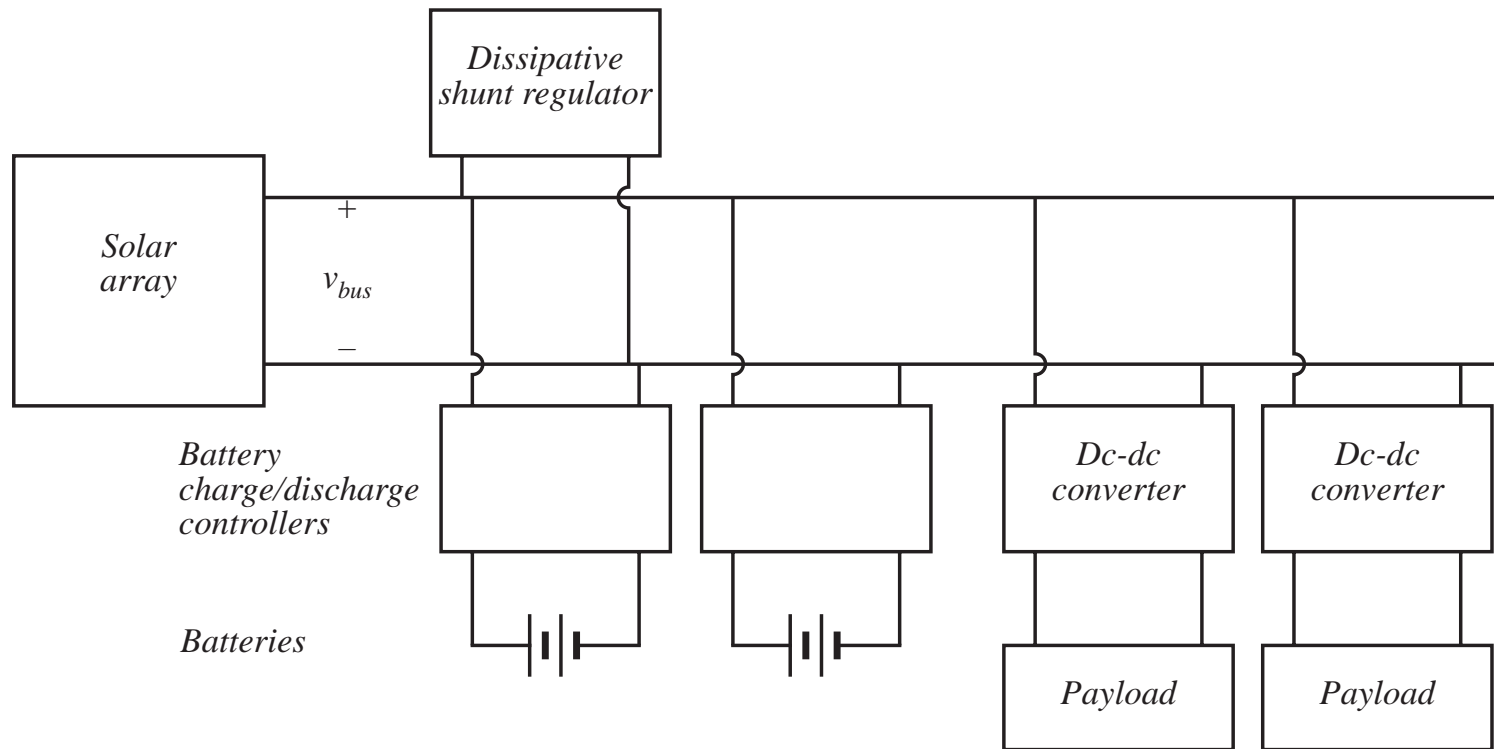

# A variable-speed ac motor drive system

---

 

## 1.3 Elements of power electronics

---

Power electronics incorporates concepts from the fields of

analog circuits

electronic devices

control systems

power systems


magnetics

electric machines


numerical simulation

# Part I. Converters in equilibrium


## Inductor waveforms

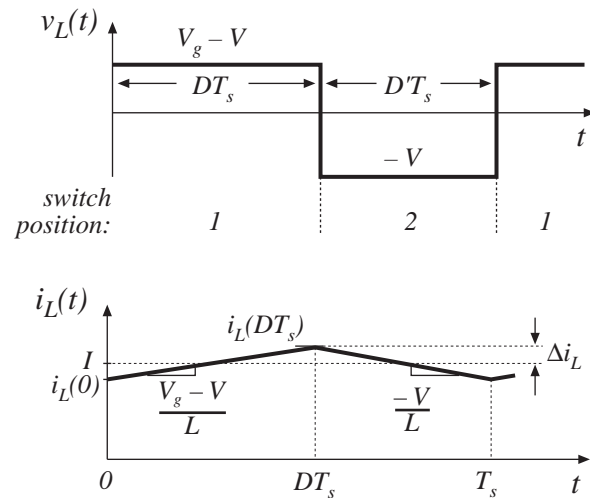

## Averaged equivalent circuit

 

## Predicted efficiency

 


*Discontinuous conduction mode*


*Transformer isolation*

# Switch realization: semiconductor devices

## The IGBT

 

## Switching loss

 

# Part I. Converters in equilibrium


---

2. Principles of steady state converter analysis
3. Steady-state equivalent circuit modeling, losses, and efficiency
4. Switch realization
5. The discontinuous conduction mode
6. Converter circuits




# Part II. Converter dynamics and control


## Closed-loop converter system

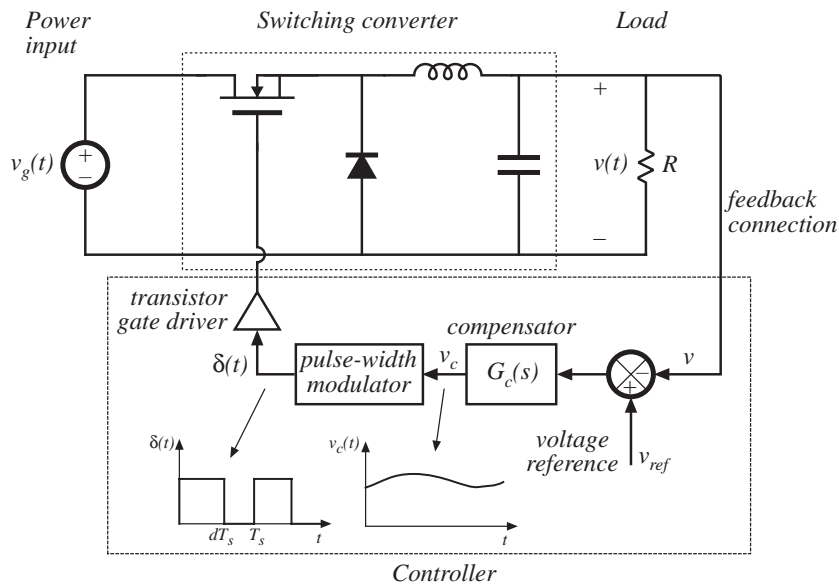

## Averaging the waveforms

 
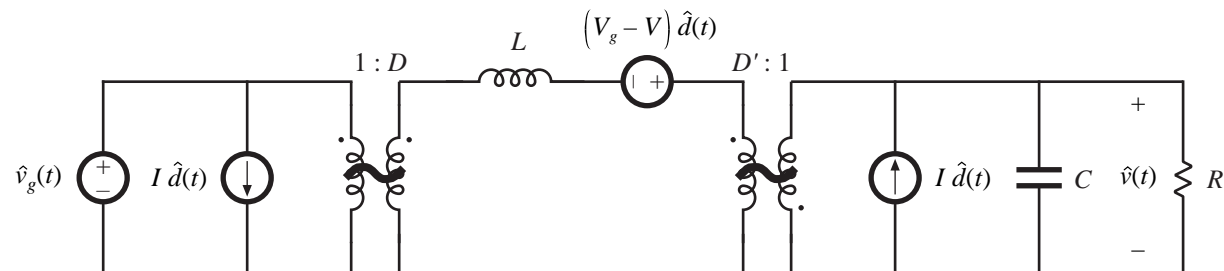
## Small-signal averaged equivalent circuit




# Part II. Converter dynamics and control

---


- 7. Ac modeling
- 8. Converter transfer functions
- 9. Controller design
- 10. Ac and dc equivalent circuit modeling of the discontinuous conduction mode
- 11. Current-programmed control

# Part III. Magnetics


*transformer design*

 

*the proximity effect*

 

 *transformer size vs. switching frequency*





# Part III. Magnetics

---


- 12. Basic magnetics theory
- 13. Filter inductor design
- 14. Transformer design

# Part IV. Modern rectifiers, and power system harmonics

  
## Pollution of power system by rectifier current harmonics



## A low-harmonic rectifier system

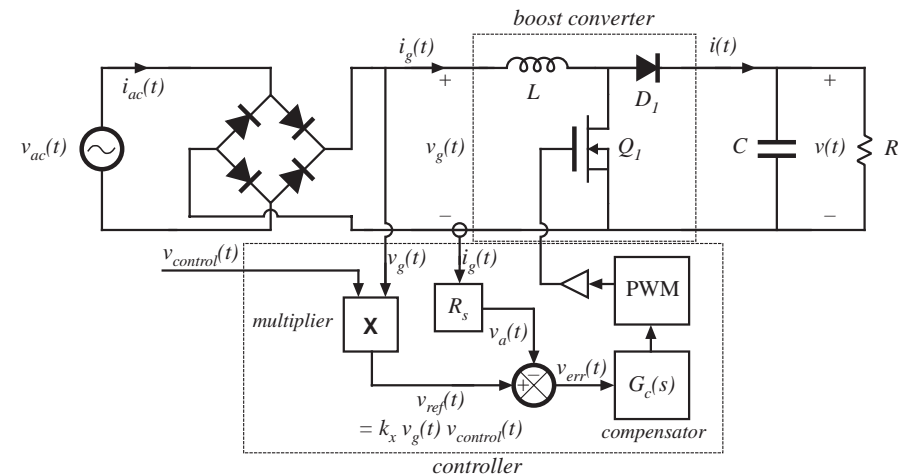

## Model of the ideal rectifier

 


# Part IV. Modern rectifiers, and power system harmonics

---


- 15. Power and harmonics in nonsinusoidal systems
- 16. Line-commutated rectifiers
- 17. The ideal rectifier
- 18. Low harmonic rectifier modeling and control

# Part V. Resonant converters


## The series resonant converter

 

*Zero voltage switching*

 

*Dc characteristics*

 

# Part V. Resonant converters

---

- 19. Resonant conversion
- 20. Quasi-resonant converters



# Chapter 2

## Principles of Steady-State Converter Analysis


---

- 2.1. Introduction
- 2.2. Inductor volt-second balance, capacitor charge balance, and the small ripple approximation
- 2.3. Boost converter example
- 2.4. Cuk converter example
- 2.5. Estimating the ripple in converters containing two-pole low-pass filters
- 2.6. Summary of key points

## 2.1 Introduction

### Buck converter


*SPDT switch changes dc component*

 

*Switch output voltage waveform*


Duty cycle  $D$ :  
 $0 \leq D \leq 1$

complement  $D'$ :  
 $D' = 1 - D$

 

# Dc component of switch output voltage

---

 


*Fourier analysis: Dc component = average value*


$$\langle v_s \rangle = \frac{1}{T_s} \int_0^{T_s} v_s(t) dt$$

$$\langle v_s \rangle = \frac{1}{T_s} (DT_s V_g) = DV_g$$
 
# Insertion of low-pass filter to remove switching harmonics and pass only dc component





$$v \approx \langle v_s \rangle = DV_g$$


 


# Three basic dc-dc converters



*Buck*

  

*Boost*

  

*Buck-boost*

  

# Objectives of this chapter


---

- Develop techniques for easily determining output voltage of an arbitrary converter circuit
- Derive the principles of *inductor volt-second balance* and *capacitor charge (amp-second) balance*
- Introduce the key *small ripple approximation*
- Develop simple methods for selecting filter element values
- Illustrate via examples
 
## 2.2. Inductor volt-second balance, capacitor charge balance, and the small ripple approximation


Actual output voltage waveform, buck converter

*Buck converter  
containing practical  
low-pass filter*




*Actual output voltage  
waveform*

$$v(t) = V + v_{\text{ripple}}(t)$$

 

# The small ripple approximation

$$v(t) = V + v_{\text{ripple}}(t)$$

 


In a well-designed converter, the output voltage ripple is small. Hence, the waveforms can be easily determined by ignoring the ripple:

$$\|v_{\text{ripple}}\| \ll V$$

$$v(t) \approx V$$


 
# Buck converter analysis: inductor current waveform



# Inductor voltage and current


## Subinterval 1: switch in position 1

*Inductor voltage*

$$v_L = V_g - v(t)$$

*Small ripple approximation:*

$$v_L \approx V_g - V$$

 

*Knowing the inductor voltage, we can now find the inductor current via*

$$v_L(t) = L \frac{di_L(t)}{dt}$$

*Solve for the slope:*

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} \approx \frac{V_g - V}{L}$$

$\Rightarrow$  *The inductor current changes with an essentially constant slope*

# Inductor voltage and current


## Subinterval 2: switch in position 2

*Inductor voltage*

$$v_L(t) = -v(t)$$

*Small ripple approximation:*

$$v_L(t) \approx -V$$

 

*Knowing the inductor voltage, we can again find the inductor current via*


$$v_L(t) = L \frac{di_L(t)}{dt}$$

*Solve for the slope:*

$$\frac{di_L(t)}{dt} \approx -\frac{V}{L}$$


$\Rightarrow$  *The inductor current changes with an essentially constant slope*

# Inductor voltage and current waveforms

 

$$v_L(t) = L \frac{di_L(t)}{dt}$$
 
# Determination of inductor current ripple magnitude




(change in  $i_L$ ) = (slope)(length of subinterval)

$$(2\Delta i_L) = \left( \frac{V_g - V}{L} \right) (DT_s)$$

$$\Rightarrow \Delta i_L = \frac{V_g - V}{2L} DT_s \qquad L = \frac{V_g - V}{2\Delta i_L} DT_s$$
 
# Inductor current waveform during turn-on transient



When the converter operates in equilibrium:

$$i_L((n+1)T_s) = i_L(nT_s)$$

# The principle of inductor volt-second balance: Derivation

---

Inductor defining relation:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Integrate over one complete switching period:

$$i_L(T_s) - i_L(0) = \frac{1}{L} \int_0^{T_s} v_L(t) dt$$

In periodic steady state, the net change in inductor current is zero:

$$0 = \int_0^{T_s} v_L(t) dt$$

*Hence, the total area (or volt-seconds) under the inductor voltage waveform is zero whenever the converter operates in steady state.*


An equivalent form:

$$0 = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \langle v_L \rangle$$

*The average inductor voltage is zero in steady state.*
 
# Inductor volt-second balance: Buck converter example

*Inductor voltage waveform,  
previously derived:*



Integral of voltage waveform is area of rectangles:

$$\lambda = \int_0^{T_s} v_L(t) dt = (V_g - V)(DT_s) + (-V)(D'T_s)$$

Average voltage is

$$\langle v_L \rangle = \frac{\lambda}{T_s} = D(V_g - V) + D'(-V)$$

Equate to zero and solve for  $V$ :

$$0 = DV_g - (D + D')V = DV_g - V \quad \Rightarrow \quad V = DV_g$$



# The principle of capacitor charge balance: Derivation

---

Capacitor defining relation:

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

Integrate over one complete switching period:

$$v_c(T_s) - v_c(0) = \frac{1}{C} \int_0^{T_s} i_c(t) dt$$


In periodic steady state, the net change in capacitor voltage is zero:

$$0 = \frac{1}{T_s} \int_0^{T_s} i_c(t) dt = \langle i_c \rangle$$


*Hence, the total area (or charge) under the capacitor current waveform is zero whenever the converter operates in steady state. The average capacitor current is then zero.*

## 2.3 Boost converter example

*Boost converter  
with ideal switch*

 


 *Realization using  
power MOSFET  
and diode*




# Boost converter analysis


*original  
converter*

 

*switch in position 1*

 

*switch in position 2*

 

# Subinterval 1: switch in position 1

---

*Inductor voltage and capacitor current*


$$v_L = V_g$$

$$i_C = -v / R$$

*Small ripple approximation:*

$$v_L = V_g$$

$$i_C = -V / R$$

 

## Subinterval 2: switch in position 2

*Inductor voltage and capacitor current*


$$v_L = V_g - v$$

$$i_C = i_L - v / R$$


*Small ripple approximation:*

$$v_L = V_g - V$$

$$i_C = I - V / R$$

 

 
# Inductor voltage and capacitor current waveforms


 
# Inductor volt-second balance

Net volt-seconds applied to inductor over one switching period:

$$\int_0^{T_s} v_L(t) dt = (V_g) DT_s + (V_g - V) D'T_s$$



Equate to zero and collect terms:

$$V_g (D + D') - V D' = 0$$

Solve for  $V$ :


$$V = \frac{V_g}{D'}$$

The voltage conversion ratio is therefore

$$M(D) = \frac{V}{V_g} = \frac{1}{D'} = \frac{1}{1 - D}$$

# Conversion ratio $M(D)$ of the boost converter

---

 



 
# Determination of inductor current dc component

Capacitor charge balance:

$$\int_0^{T_s} i_C(t) dt = \left(-\frac{V}{R}\right) DT_s + \left(I - \frac{V}{R}\right) D'T_s$$



Collect terms and equate to zero:


$$-\frac{V}{R} (D + D') + I D' = 0$$

Solve for  $I$ :

$$I = \frac{V}{D' R}$$

Eliminate  $V$  to express in terms of  $V_g$ :

$$I = \frac{V_g}{D'^2 R}$$

 

# Determination of inductor current ripple

Inductor current slope during subinterval 1:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g}{L}$$

Inductor current slope during subinterval 2:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g - V}{L}$$


Change in inductor current during subinterval 1 is (slope) (length of subinterval):

$$2\Delta i_L = \frac{V_g}{L} DT_s$$

Solve for peak ripple:

$$\Delta i_L = \frac{V_g}{2L} DT_s$$

 - Choose  $L$  such that desired ripple magnitude is obtained



# Determination of capacitor voltage ripple

Capacitor voltage slope during subinterval 1:

$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{-V}{RC}$$

Capacitor voltage slope during subinterval 2:

$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{I}{C} - \frac{V}{RC}$$


Change in capacitor voltage during subinterval 1 is (slope) (length of subinterval):

$$-2\Delta v = \frac{-V}{RC} DT_s$$

Solve for peak ripple:


$$\Delta v = \frac{V}{2RC} DT_s$$

 - Choose  $C$  such that desired voltage ripple magnitude is obtained
- In practice, capacitor *equivalent series resistance* (esr) leads to increased voltage ripple




## 2.4 Cuk converter example

*Cuk converter,  
with ideal switch*

 

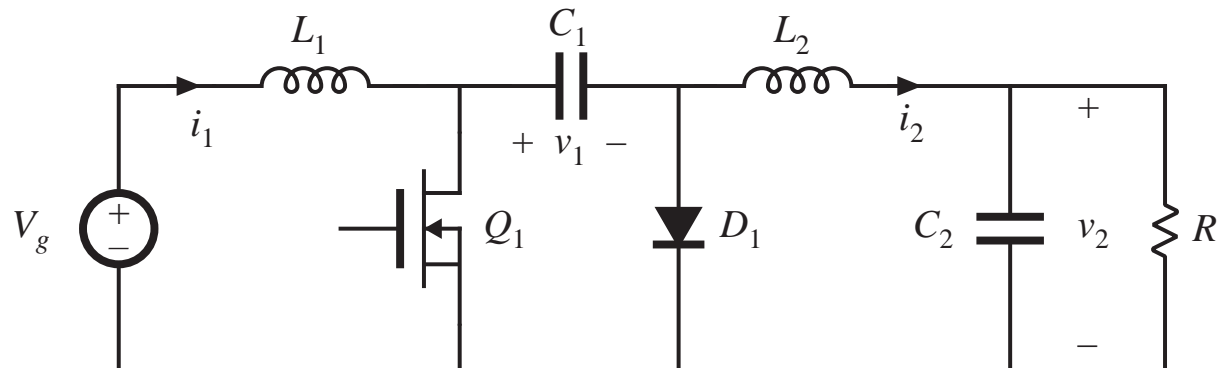
*Cuk converter:  
practical realization  
using MOSFET and  
diode*




# Cuk converter circuit
 
## with switch in positions 1 and 2

Switch in position 1:  
MOSFET conducts  
Capacitor  $C_1$  releases  
energy to output



 Switch in position 2:  
diode conducts  
Capacitor  $C_1$  is  
charged from input



# Waveforms during subinterval 1

## MOSFET conduction interval


Inductor voltages and capacitor currents:

$$v_{L1} = V_g$$

$$v_{L2} = -v_1 - v_2$$

$$i_{C1} = i_2$$

$$i_{C2} = i_2 - \frac{v_2}{R}$$

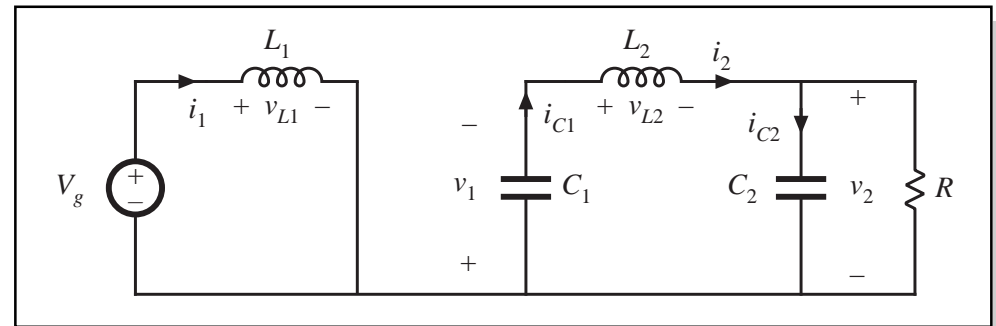

Small ripple approximation for subinterval 1:

$$v_{L1} = V_g$$

$$v_{L2} = -V_1 - V_2$$

$$i_{C1} = I_2$$

$$i_{C2} = I_2 - \frac{V_2}{R}$$

# Waveforms during subinterval 2

## Diode conduction interval


Inductor voltages and capacitor currents:

$$v_{L1} = V_g - v_1$$

$$v_{L2} = -v_2$$

$$i_{C1} = i_1$$

$$i_{C2} = i_2 - \frac{v_2}{R}$$

 

Small ripple approximation for subinterval 2:

$$v_{L1} = V_g - V_1$$

$$v_{L2} = -V_2$$

$$i_{C1} = I_1$$


$$i_{C2} = I_2 - \frac{V_2}{R}$$

# Equate average values to zero

The principles of inductor volt-second and capacitor charge balance state that the average values of the periodic inductor voltage and capacitor current waveforms are zero, when the converter operates in steady state. Hence, to determine the steady-state conditions in the converter, let us sketch the inductor voltage and capacitor current waveforms, and equate their average values to zero.

## **Waveforms:**

Inductor voltage  $v_{L1}(t)$

 


Volt-second balance on  $L_1$ :

$$\langle v_{L1} \rangle = DV_g + D'(V_g - V_1) = 0$$



# Equate average values to zero

*Inductor  $L_2$  voltage*

 


Average the waveforms:

$$\langle v_{L2} \rangle = D(-V_1 - V_2) + D'(-V_2) = 0$$


$$\langle i_{C1} \rangle = DI_2 + D'I_1 = 0$$

*Capacitor  $C_1$  current*

 

# Equate average values to zero

Capacitor current  $i_{C2}(t)$  waveform

 


$$\langle i_{C2} \rangle = I_2 - \frac{V_2}{R} = 0$$

Note: during both subintervals, the capacitor current  $i_{C2}$  is equal to the difference between the inductor current  $i_2$  and the load current  $V_2/R$ . When ripple is neglected,  $i_{C2}$  is constant and equal to zero.

# Cuk converter conversion ratio $M = V/V_g$

---

 

# Inductor current waveforms

Interval 1 slopes, using small ripple approximation:



$$\frac{di_1(t)}{dt} = \frac{v_{L1}(t)}{L_1} = \frac{V_g}{L_1}$$

$$\frac{di_2(t)}{dt} = \frac{v_{L2}(t)}{L_2} = \frac{-V_1 - V_2}{L_2}$$

Interval 2 slopes:

$$\frac{di_1(t)}{dt} = \frac{v_{L1}(t)}{L_1} = \frac{V_g - V_1}{L_1}$$
  
$$\frac{di_2(t)}{dt} = \frac{v_{L2}(t)}{L_2} = \frac{-V_2}{L_2}$$




# Capacitor $C_1$ waveform

Subinterval 1:

$$\frac{dv_1(t)}{dt} = \frac{i_{C1}(t)}{C_1} = \frac{I_2}{C_1}$$

Subinterval 2:
 
$$\frac{dv_1(t)}{dt} = \frac{i_{C1}(t)}{C_1} = \frac{I_1}{C_1}$$



# Ripple magnitudes

---

Analysis results

$$\Delta i_1 = \frac{V_g D T_s}{2L_1}$$

$$\Delta i_2 = \frac{V_1 + V_2}{2L_2} D T_s$$

$$\Delta v_1 = \frac{-I_2 D T_s}{2C_1}$$

Use dc converter solution to simplify:

$$\Delta i_1 = \frac{V_g D T_s}{2L_1}$$


$$\Delta i_2 = \frac{V_g D T_s}{2L_2}$$

$$\Delta v_1 = \frac{V_g D^2 T_s}{2D'RC_1}$$

**Q:** How large is the output voltage ripple?

 
## 2.5 Estimating ripple in converters containing two-pole low-pass filters

*Buck converter example: Determine output voltage ripple*



*Inductor current waveform.*


*What is the capacitor current?*

 
 
# Capacitor current and voltage, buck example


*Must not neglect inductor current ripple!*

*If the capacitor voltage ripple is small, then essentially all of the ac component of inductor current flows through the capacitor.*




 
# Estimating capacitor voltage ripple $\Delta v$




Current  $i_C(t)$  is positive for half of the switching period. This positive current causes the capacitor voltage  $v_C(t)$  to increase between its minimum and maximum extrema. During this time, the total charge  $q$  is deposited on the capacitor plates, where

$$q = C (2\Delta v)$$

$$\begin{aligned} (\text{change in charge}) &= \\ C (\text{change in voltage}) \end{aligned}$$
 
# Estimating capacitor voltage ripple $\Delta v$



The total charge  $q$  is the area of the triangle, as shown:

$$q = \frac{1}{2} \Delta i_L \frac{T_s}{2}$$



Eliminate  $q$  and solve for  $\Delta v$ :

$$\Delta v = \frac{\Delta i_L T_s}{8 C}$$

Note: in practice, capacitor equivalent series resistance (esr) further increases  $\Delta v$ .

# Inductor current ripple in two-pole filters

Example:  
problem 2.9

  

can use similar arguments, with

$$\lambda = L \Delta i$$

$\lambda$  = inductor flux linkages

= inductor volt-seconds

## 2.6 Summary of Key Points

---

1. The dc component of a converter waveform is given by its average value, or the integral over one switching period, divided by the switching period. Solution of a dc-dc converter to find its dc, or steady-state, voltages and currents therefore involves averaging the waveforms.
2. The linear ripple approximation greatly simplifies the analysis. In a well-designed converter, the switching ripples in the inductor currents and capacitor voltages are small compared to the respective dc components, and can be neglected.
3. The principle of inductor volt-second balance allows determination of the dc voltage components in any switching converter. In steady-state, the average voltage applied to an inductor must be zero.

# Summary of Chapter 2

---

4. The principle of capacitor charge balance allows determination of the dc components of the inductor currents in a switching converter. In steady-state, the average current applied to a capacitor must be zero.
5. By knowledge of the slopes of the inductor current and capacitor voltage waveforms, the ac switching ripple magnitudes may be computed. Inductance and capacitance values can then be chosen to obtain desired ripple magnitudes.
6. In converters containing multiple-pole filters, continuous (nonpulsating) voltages and currents are applied to one or more of the inductors or capacitors. Computation of the ac switching ripple in these elements can be done using capacitor charge and/or inductor flux-linkage arguments, without use of the small-ripple approximation.
7. Converters capable of increasing (boost), decreasing (buck), and inverting the voltage polarity (buck-boost and Cuk) have been described. Converter circuits are explored more fully in a later chapter.

# Chapter 3. Steady-State Equivalent Circuit Modeling, Losses, and Efficiency

---

- 3.1. The dc transformer model
- 3.2. Inclusion of inductor copper loss
- 3.3. Construction of equivalent circuit model
- 3.4. How to obtain the input port of the model
- 3.5. Example: inclusion of semiconductor conduction losses in the boost converter model
- 3.6. Summary of key points

## 3.1. The dc transformer model

Basic equations of an ideal dc-dc converter:

$$P_{in} = P_{out} \quad (\eta = 100\%)$$


$$V_g I_g = V I$$

$$V = M(D) V_g \quad (\text{ideal conversion ratio})$$

$$I_g = M(D) I$$


These equations are valid in steady-state. During transients, energy storage within filter elements may cause

$$P_{in} \neq P_{out}$$

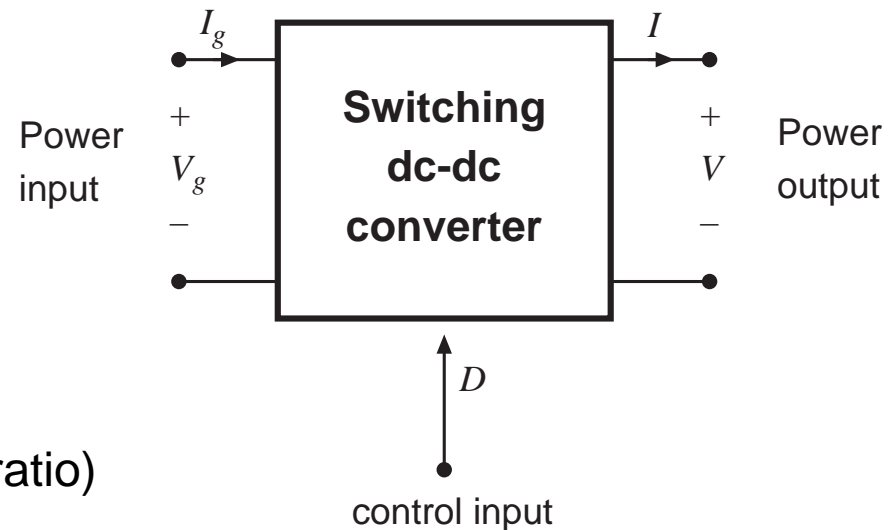

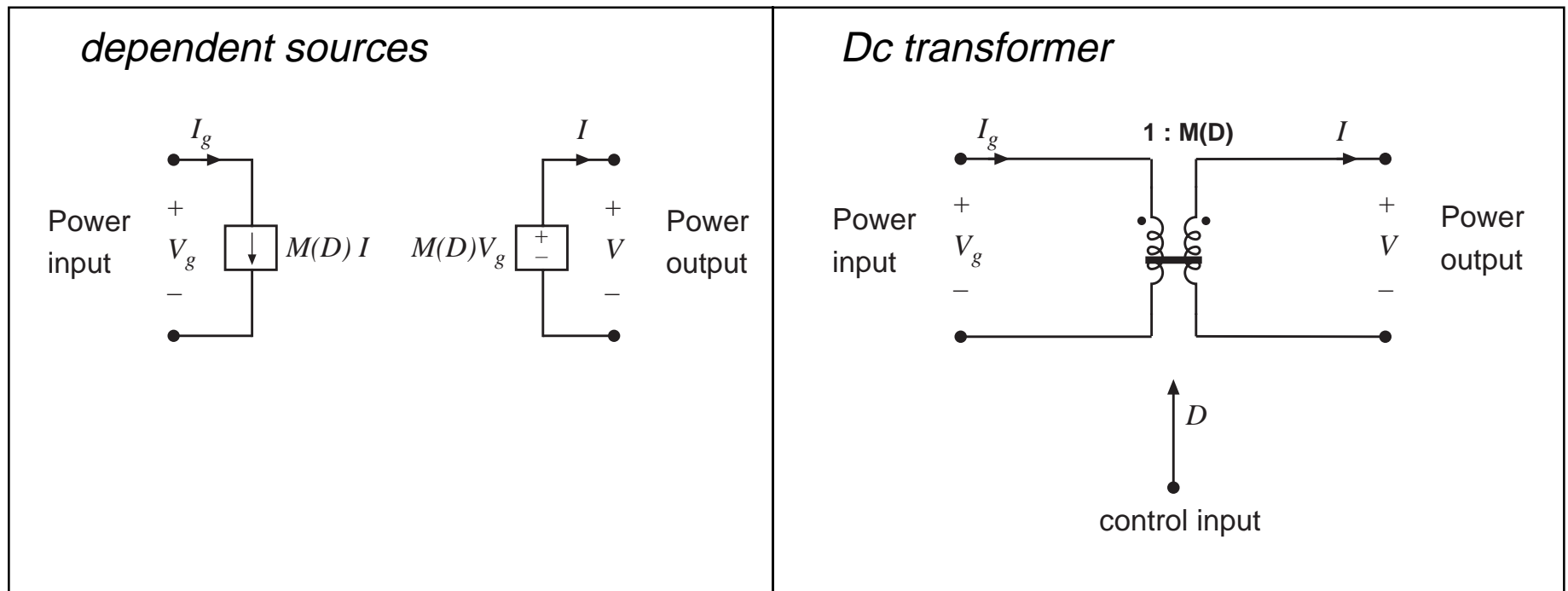
# Equivalent circuits corresponding to ideal dc-dc converter equations

$$P_{in} = P_{out} \quad V_g I_g = V I \quad V = M(D) V_g \quad I_g = M(D) I$$





# The dc transformer model

 


Models basic properties of ideal dc-dc converter:

- conversion of dc voltages and currents, ideally with 100% efficiency
- conversion ratio  $M$  controllable via duty cycle


- Solid line denotes ideal transformer model, capable of passing dc voltages and currents
- Time-invariant model (no switching) which can be solved to find dc components of converter waveforms

# Example: use of the dc transformer model


1. Original system

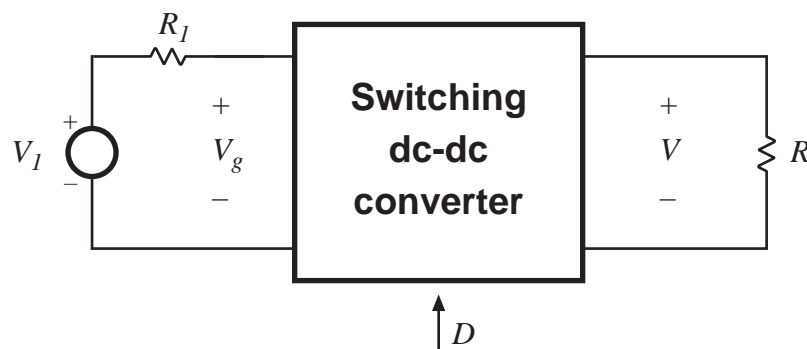

3. Push source through transformer

 

2. Insert dc transformer model

 

4. Solve circuit

$$V = M(D) V_I \frac{R}{R + M^2(D) R_I}$$


## 3.2. Inclusion of inductor copper loss

Dc transformer model can be extended, to include converter nonidealities.

 
Example: inductor copper loss (resistance of winding):



Insert this inductor model into boost converter circuit:



# Analysis of nonideal boost converter

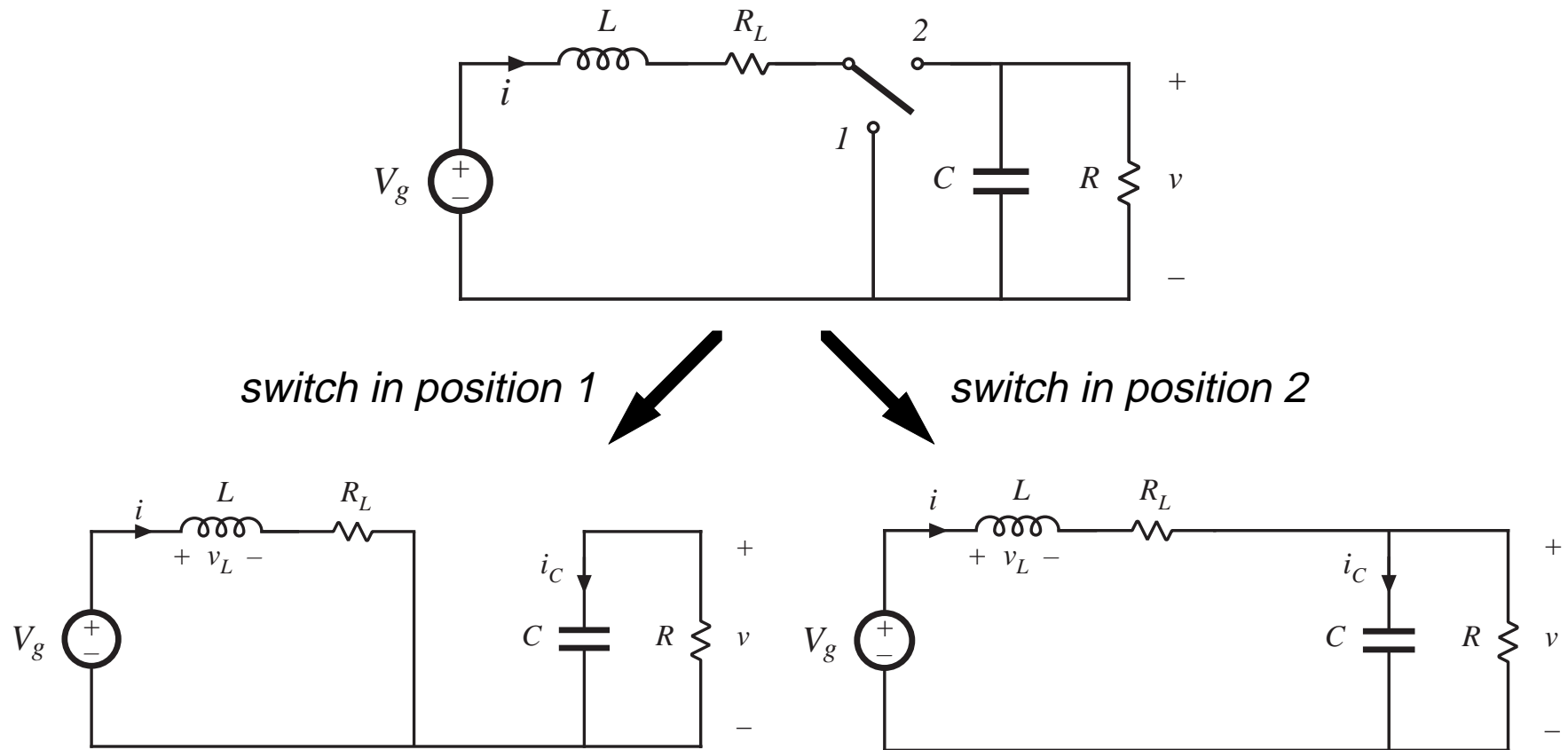


# Circuit equations, switch in position 1

Inductor current and capacitor voltage:

$$v_L(t) = V_g - i(t) R_L$$

$$i_C(t) = -v(t) / R$$

 


Small ripple approximation:

$$v_L(t) = V_g - I R_L$$

$$i_C(t) = -V / R$$

## Circuit equations, switch in position 2

---

 

$$v_L(t) = V_g - i(t) R_L - v(t) \approx V_g - I R_L - V$$

$$i_C(t) = i(t) - v(t) / R \approx I - V / R$$

# Inductor voltage and capacitor current waveforms

Average inductor voltage:

$$\begin{aligned}\langle v_L(t) \rangle &= \frac{1}{T_s} \int_0^{T_s} v_L(t) dt \\ &= D(V_g - I R_L) + D'(V_g - I R_L - V)\end{aligned}$$

Inductor volt-second balance:


$$0 = V_g - I R_L - D'V$$

Average capacitor current:

$$\langle i_C(t) \rangle = D(-V/R) + D'(I - V/R)$$

Capacitor charge balance:

$$0 = D'I - V/R$$

 

# Solution for output voltage


We now have two equations and two unknowns:

$$0 = V_g - I R_L - D'V$$

$$0 = D'I - V / R$$

Eliminate  $I$  and solve for  $V$ :
 
$$\frac{V}{V_g} = \frac{1}{D'} \frac{1}{(1 + R_L / D'^2 R)}$$





### 3.3. Construction of equivalent circuit model

---

Results of previous section (derived via inductor volt-sec balance and capacitor charge balance):


$$\begin{aligned}\langle v_L \rangle &= 0 = V_g - I R_L - D'V \\ \langle i_C \rangle &= 0 = D'I - V / R\end{aligned}$$

View these as loop and node equations of the equivalent circuit.  
Reconstruct an equivalent circuit satisfying these equations
 
# Inductor voltage equation

$$\langle v_L \rangle = 0 = V_g - I R_L - D'V$$

- Derived via Kirchoff's voltage law, to find the inductor voltage during each subinterval
- Average inductor voltage then set to zero
- This is a loop equation: the dc components of voltage around a loop containing the inductor sum to zero




- $IR_L$  term: voltage across resistor of value  $R_L$  having current  $I$
- $D'V$  term: for now, leave as dependent source
 
# Capacitor current equation

$$\langle i_c \rangle = 0 = D'I - V/R$$


- Derived via Kirchoff's current law, to find the capacitor current during each subinterval
- Average capacitor current then set to zero
- This is a node equation: the dc components of current flowing into a node connected to the capacitor sum to zero




- $V/R$  term: current through load resistor of value  $R$  having voltage  $V$
- $D'I$  term: for now, leave as dependent source

# Complete equivalent circuit



The two circuits, drawn together:

 

 The dependent sources are equivalent to a  $D' : I$  transformer:




*Dependent sources and transformers*

  


- *sources have same coefficient*
- *reciprocal voltage/current dependence*

# Solution of equivalent circuit

Converter equivalent circuit

 

 
Refer all elements to transformer secondary:



Solution for output voltage using voltage divider formula:

$$V = \frac{V_g}{D'} \frac{R}{R + \frac{R_L}{D'^2}} = \frac{V_g}{D'} \frac{1}{1 + \frac{R_L}{D'^2 R}}$$

## Solution for input (inductor) current

 

$$I = \frac{V_g}{D'^2 R + R_L} = \frac{V_g}{D'^2} \frac{1}{1 + \frac{R_L}{D'^2 R}}$$


# Solution for converter efficiency

$$P_{in} = (V_g) (I)$$

$$P_{out} = (V) (D'I)$$


$$\eta = \frac{P_{out}}{P_{in}} = \frac{(V) (D'I)}{(V_g) (I)} = \frac{V}{V_g} D'$$
 
$$\eta = \frac{1}{1 + \frac{R_L}{D'^2 R}}$$


 
# Efficiency, for various values of $R_L$


$$\eta = \frac{1}{1 + \frac{R_L}{D'^2 R}}$$




 
### 3.4. How to obtain the input port of the model

Buck converter example —use procedure of previous section to derive equivalent circuit




Average inductor voltage and capacitor current:

$$\langle v_L \rangle = 0 = DV_g - I_L R_L - V_C \qquad \langle i_C \rangle = 0 = I_L - V_C/R$$
 
## Construct equivalent circuit as usual

$$\langle v_L \rangle = 0 = DV_g - I_L R_L - V_C \quad \langle i_C \rangle = 0 = I_L - V_C/R$$




What happened to the transformer?

- Need another equation

# Modeling the converter input port

---

Input current waveform  $i_g(t)$ :

 


Dc component (average value) of  $i_g(t)$  is

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L$$
 
# Input port equivalent circuit


---

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L$$



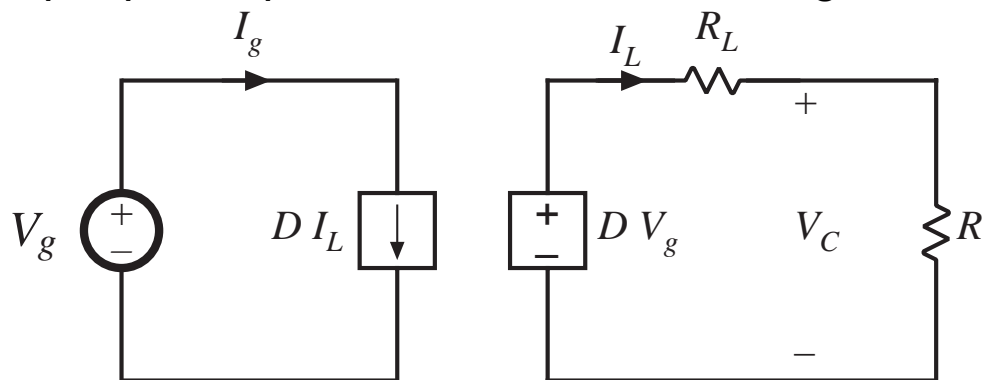
# Complete equivalent circuit, buck converter

Input and output port equivalent circuits, drawn together:



 
Replace dependent sources with equivalent dc transformer:



### 3.5. Example: inclusion of semiconductor conduction losses in the boost converter model

---

*Boost converter example*

 


Models of on-state semiconductor devices:

MOSFET: on-resistance  $R_{on}$

Diode: constant forward voltage  $V_D$  plus on-resistance  $R_D$



Insert these models into subinterval circuits
 
# Boost converter example: circuits during subintervals 1 and 2




*switch in position 1*

*switch in position 2*

  
 
# Average inductor voltage and capacitor current




$$\langle v_L \rangle = D(V_g - IR_L - IR_{on}) + D'(V_g - IR_L - V_D - IR_D - V) = 0$$

$$\langle i_C \rangle = D(-V/R) + D'(I - V/R) = 0$$



 
# Construction of equivalent circuits


$$V_g - IR_L - IDR_{on} - D'V_D - ID'R_D - D'V = 0$$




$$D'I - V/R = 0$$

 

# Complete equivalent circuit

 

# Solution for output voltage

 


$$V = \left( \frac{1}{D'} \right) \left( V_g - D' V_D \right) \left( \frac{D'^2 R}{D'^2 R + R_L + D R_{on} + D' R_D} \right)$$

$$\frac{V}{V_g} = \left( \frac{1}{D'} \right) \left( 1 - \frac{D' V_D}{V_g} \right) \left( \frac{1}{1 + \frac{R_L + D R_{on} + D' R_D}{D'^2 R}} \right)$$

# Solution for converter efficiency

$$P_{in} = (V_g) (I)$$

$$P_{out} = (V) (D'I)$$

 

$$\eta = D' \frac{V}{V_g} = \frac{\left(1 - \frac{D' V_D}{V_g}\right)}{\left(1 + \frac{R_L + D R_{on} + D' R_D}{D'^2 R}\right)}$$

*Conditions for high efficiency:*


$$V_g / D' \gg V_D$$

and  $D'^2 R \gg R_L + D R_{on} + D' R_D$
 
# Accuracy of the averaged equivalent circuit in prediction of losses

- Model uses average currents and voltages
- To correctly predict power loss in a resistor, use rms values
- Result is the same, provided ripple is small

*MOSFET current waveforms, for various ripple magnitudes:*



<i>Inductor current ripple</i>	<i>MOSFET rms current</i>	<i>Average power loss in <math>R_{on}</math></i>
(a) $\Delta i = 0$	$I \sqrt{D}$	$D I^2 R_{on}$
(b) $\Delta i = 0.1 I$	$(1.00167) I \sqrt{D}$	$(1.0033) D I^2 R_{on}$
(c) $\Delta i = I$	$(1.155) I \sqrt{D}$	$(1.3333) D I^2 R_{on}$

# Summary of chapter 3

---

1. The dc transformer model represents the primary functions of any dc-dc converter: transformation of dc voltage and current levels, ideally with 100% efficiency, and control of the conversion ratio  $M$  via the duty cycle  $D$ . This model can be easily manipulated and solved using familiar techniques of conventional circuit analysis.
2. The model can be refined to account for loss elements such as inductor winding resistance and semiconductor on-resistances and forward voltage drops. The refined model predicts the voltages, currents, and efficiency of practical nonideal converters.
3. In general, the dc equivalent circuit for a converter can be derived from the inductor volt-second balance and capacitor charge balance equations. Equivalent circuits are constructed whose loop and node equations coincide with the volt-second and charge balance equations. In converters having a pulsating input current, an additional equation is needed to model the converter input port; this equation may be obtained by averaging the converter input current.

# Chapter 4. Switch Realization

---

## 4.1. Switch applications

Single-, two-, and four-quadrant switches. Synchronous rectifiers

## 4.2. A brief survey of power semiconductor devices

Power diodes, MOSFETs, BJT, IGBT, and thyristors


## 4.3. Switching loss

Transistor switching with clamped inductive load. Diode recovered charge. Stray capacitances and inductances, and ringing. Efficiency vs. switching frequency.

## 4.4. Summary of key points
 
# SPST (single-pole single-throw) switches


*SPST switch, with voltage and current polarities defined*




*All power semiconductor devices function as SPST switches.*

## Buck converter

*with SPDT switch:*

 

*with two SPST switches:*

 





# Realization of SPDT switch using two SPST switches

---

- A nontrivial step: two SPST switches are not exactly equivalent to one SPDT switch
- It is possible for both SPST switches to be simultaneously ON or OFF
- Behavior of converter is then significantly modified  
—discontinuous conduction modes (ch. 5)
- Conducting state of SPST switch may depend on applied voltage or current —for example: diode

# Quadrants of SPST switch operation

  


A single-quadrant switch example:

*ON-state:*  $i > 0$


*OFF-state:*  $v > 0$

# Some basic switch applications


*Single-quadrant switch*

 

 
*Current-bidirectional two-quadrant switch*



 *Voltage-bidirectional two-quadrant switch*




*Four-quadrant switch*

 

## 4.1.1. Single-quadrant switches

---

 


**Active switch:** Switch state is controlled exclusively by a third terminal (control terminal).

**Passive switch:** Switch state is controlled by the applied current and/or voltage at terminals  $1$  and  $2$ .


**SCR:** A special case — turn-on transition is active, while turn-off transition is passive.

**Single-quadrant switch:** on-state  $i(t)$  and off-state  $v(t)$  are unipolar.

# The diode

 

Symbol

 


instantaneous  $i$ - $v$  characteristic



- *A passive switch*
- *Single-quadrant switch:*
- *can conduct positive on-state current*
- *can block negative off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the diode  $i$ - $v$  characteristic, then switch can be realized using a diode*

# The Bipolar Junction Transistor (BJT) and the Insulated Gate Bipolar Transistor (IGBT)

BJT

 


IGBT

  

instantaneous  $i$ - $v$  characteristic

- An active switch, controlled by terminal  $C$
- Single-quadrant switch:
- can conduct positive on-state current
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the transistor  $i$ - $v$  characteristic, then switch can be realized using a BJT or IGBT
 
# The Metal-Oxide Semiconductor Field Effect Transistor (MOSFET)




Symbol      instantaneous  $i$ - $v$  characteristic

- *An active switch, controlled by terminal  $C$*
- *Normally operated as single-quadrant switch:*
- *can conduct positive on-state current (can also conduct negative current in some circumstances)*
- *can block positive off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the MOSFET  $i$ - $v$  characteristic, then switch can be realized using a MOSFET*

# Realization of switch using transistors and diodes



*Buck converter example*

 

*Switch A: transistor*




*Switch B: diode*

*SPST switch  
operating points*

  




   
# Realization of buck converter using single-quadrant switches


 
## 4.1.2. Current-bidirectional two-quadrant switches



 
*BJT / anti-parallel  
diode realization*




*instantaneous  $i$ - $v$   
characteristic*

- *Usually an active switch, controlled by terminal C*
- *Normally operated as two-quadrant switch:*
- *can conduct positive or negative on-state current*
- *can block positive off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the composite  $i$ - $v$  characteristic, then switch can be realized as shown*


# Two quadrant switches

 


# MOSFET body diode

 

*Power MOSFET characteristics*

 


 *Power MOSFET, and its integral body diode*




*Use of external diodes to prevent conduction of body diode*

# A simple inverter

 

# Inverter: sinusoidal modulation of $D$

$$v_0(t) = (2D - 1) V_g$$

 

Sinusoidal modulation to produce ac output:


$$D(t) = 0.5 + D_m \sin(\omega t)$$

The resulting inductor current variation is also sinusoidal:

$$i_L(t) = \frac{v_0(t)}{R} = (2D - 1) \frac{V_g}{R}$$


Hence, current-bidirectional two-quadrant switches are required.
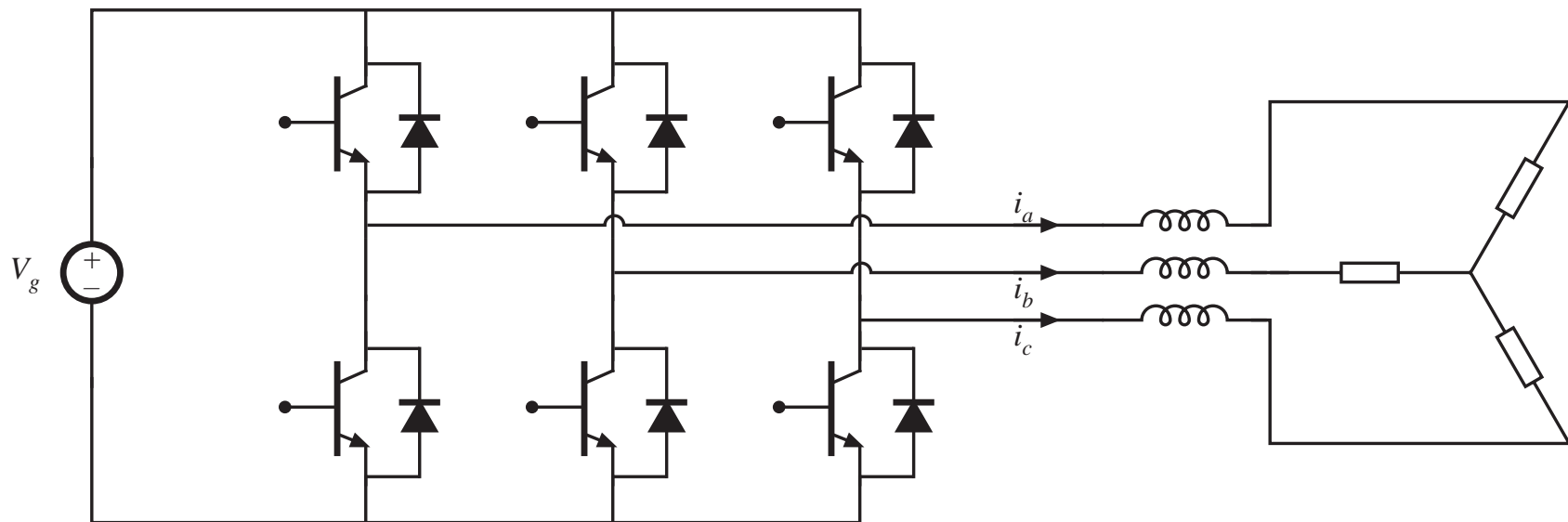
# The dc-3 $\phi$ ac voltage source inverter (VSI)



Switches must block dc input voltage, and conduct ac load current.

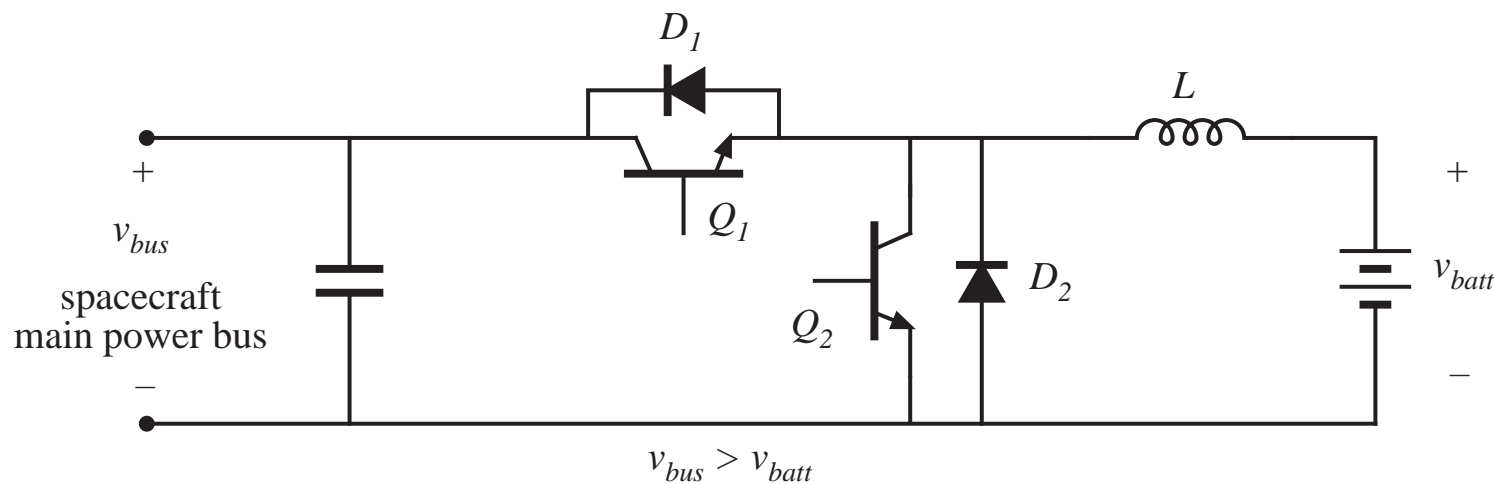
# Bidirectional battery charger/discharger




A dc-dc converter with bidirectional power flow.


 
### 4.1.3. Voltage-bidirectional two-quadrant switches




*BJT / series  
diode realization*

 


*instantaneous  $i$ - $v$   
characteristic*

- *Usually an active switch, controlled by terminal  $C$*
- *Normally operated as two-quadrant switch:*
- *can conduct positive on-state current*
- *can block positive or negative off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the composite  $i$ - $v$  characteristic, then switch can be realized as shown*
- *The SCR is such a device, without controlled turn-off*

# Two-quadrant switches

 

# A dc-3 $\phi$ ac buck-boost inverter

 


Requires voltage-bidirectional two-quadrant switches.

Another example: boost-type inverter, or current-source inverter (CSI).


## 4.1.4. Four-quadrant switches

---

 


- *Usually an active switch, controlled by terminal C*
- *can conduct positive or negative on-state current*
- *can block positive or negative off-state voltage*
 
# Three ways to realize a four-quadrant switch



 
# A 3 $\phi$ ac-3 $\phi$ ac matrix converter




- All voltages and currents are ac; hence, four-quadrant switches are required.
- Requires nine four-quadrant switches
 
## 4.1.5. Synchronous rectifiers


Replacement of diode with a backwards-connected MOSFET,  
to obtain reduced conduction loss




*ideal switch*

 

*conventional  
diode rectifier*

 


*MOSFET as  
synchronous  
rectifier*

 

*instantaneous  $i$ - $v$   
characteristic*
 
# Buck converter with synchronous rectifier



- MOSFET  $Q_2$  is controlled to turn on when diode would normally conduct
- Semiconductor conduction loss can be made arbitrarily small, by reduction of MOSFET on-resistances
- Useful in low-voltage high-current applications




## 4.2. A brief survey of power semiconductor devices

---


- Power diodes
  - Power MOSFETs
  - Bipolar Junction Transistors (BJTs)
  - Insulated Gate Bipolar Transistors (IGBTs)
  - Thyristors (SCR, GTO, MCT)
- 
- On resistance vs. breakdown voltage vs. switching times
  - Minority carrier and majority carrier devices
 
## 4.2.1. Power diodes


A power diode, under reverse-biased conditions:



# Forward-biased power diode

 

# Typical diode switching waveforms

 

# Types of power diodes

---

## *Standard recovery*

Reverse recovery time not specified, intended for 50/60Hz

## *Fast recovery and ultra-fast recovery*

Reverse recovery time and recovered charge specified

Intended for converter applications

## *Schottky diode*

A majority carrier device

Essentially no recovered charge

Model with equilibrium  $i$ - $v$  characteristic, in parallel with depletion region capacitance


Restricted to low voltage (few devices can block 100V or more)

# Characteristics of several commercial power rectifier diodes

<i>Part number</i>	<i>Rated max voltage</i>	<i>Rated avg current</i>	$V_F$ (typical)	$t_r$ (max)
<b><i>Fast recovery rectifiers</i></b>				
1N3913	400V	30A	1.1V	400ns
SD453N25S20PC	2500V	400A	2.2V	2 $\mu$ s
<b><i>Ultra-fast recovery rectifiers</i></b>				
MUR815	150V	8A	0.975V	35ns
MUR1560	600V	15A	1.2V	60ns
RHRU100120	1200V	100A	2.6V	60ns
<b><i>Schottky rectifiers</i></b>				
MBR6030L	30V	60A	0.48V	
444CNQ045	45V	440A	0.69V	
30CPQ150	150V	30A	1.19V	




# MOSFET: Off state

 

- $p$ - $n$  junction is reverse-biased
- off-state voltage appears across  $n$  region




# MOSFET: on state

 


- $p$ - $n$  junction is slightly reverse-biased
- positive gate voltage induces conducting channel
- drain current flows through  $n$  region and conducting channel
- on resistance = total resistances of  $n$  region, conducting channel, source and drain contacts, etc.

# MOSFET body diode

 


- $p$ - $n^-$  junction forms an effective diode, in parallel with the channel
- negative drain-to-source voltage can forward-bias the body diode
- diode can conduct the full MOSFET rated current
- diode switching speed not optimized —body diode is slow,  $Q_r$  is large

# Typical MOSFET characteristics

 

- Off state:  $V_{GS} < V_{th}$
- On state:  $V_{GS} \gg V_{th}$
- MOSFET can conduct peak currents well in excess of average current rating — characteristics are unchanged
- on-resistance has positive temperature coefficient, hence easy to parallel

# A simple MOSFET equivalent circuit

 

- $C_{gs}$  : large, essentially constant
- $C_{gd}$  : small, highly nonlinear
- $C_{ds}$  : intermediate in value, highly nonlinear
- switching times determined by rate at which gate driver charges/ discharges  $C_{gs}$  and  $C_{gd}$

$$C_{ds}(v_{ds}) = \frac{C_0}{\sqrt{1 + \frac{v_{ds}}{V_0}}}$$

$$C_{ds}(v_{ds}) \approx C_0 \sqrt{\frac{V_0}{v_{ds}}} = \frac{C'_0}{\sqrt{v_{ds}}}$$

# Characteristics of several commercial power MOSFETs

---

---

<i>Part number</i>	<i>Rated max voltage</i>	<i>Rated avg current</i>	$R_{on}$	$Q_g$ (typical)
IRFZ48	60V	50A	0.018 $\Omega$	110nC
IRF510	100V	5.6A	0.54 $\Omega$	8.3nC
IRF540	100V	28A	0.077 $\Omega$	72nC
APT10M25BNR	100V	75A	0.025 $\Omega$	171nC
IRF740	400V	10A	0.55 $\Omega$	63nC
MTM15N40E	400V	15A	0.3 $\Omega$	110nC
APT5025BN	500V	23A	0.25 $\Omega$	83nC
APT1001RBNR	1000V	11A	1.0 $\Omega$	150nC


---

# MOSFET: conclusions

---



- A majority-carrier device: fast switching speed
- Typical switching frequencies: tens and hundreds of kHz
- On-resistance increases rapidly with rated blocking voltage
- Easy to drive
- The device of choice for blocking voltages less than 500V
- 1000V devices are available, but are useful only at low power levels (100W)
- Part number is selected on the basis of on-resistance rather than current rating
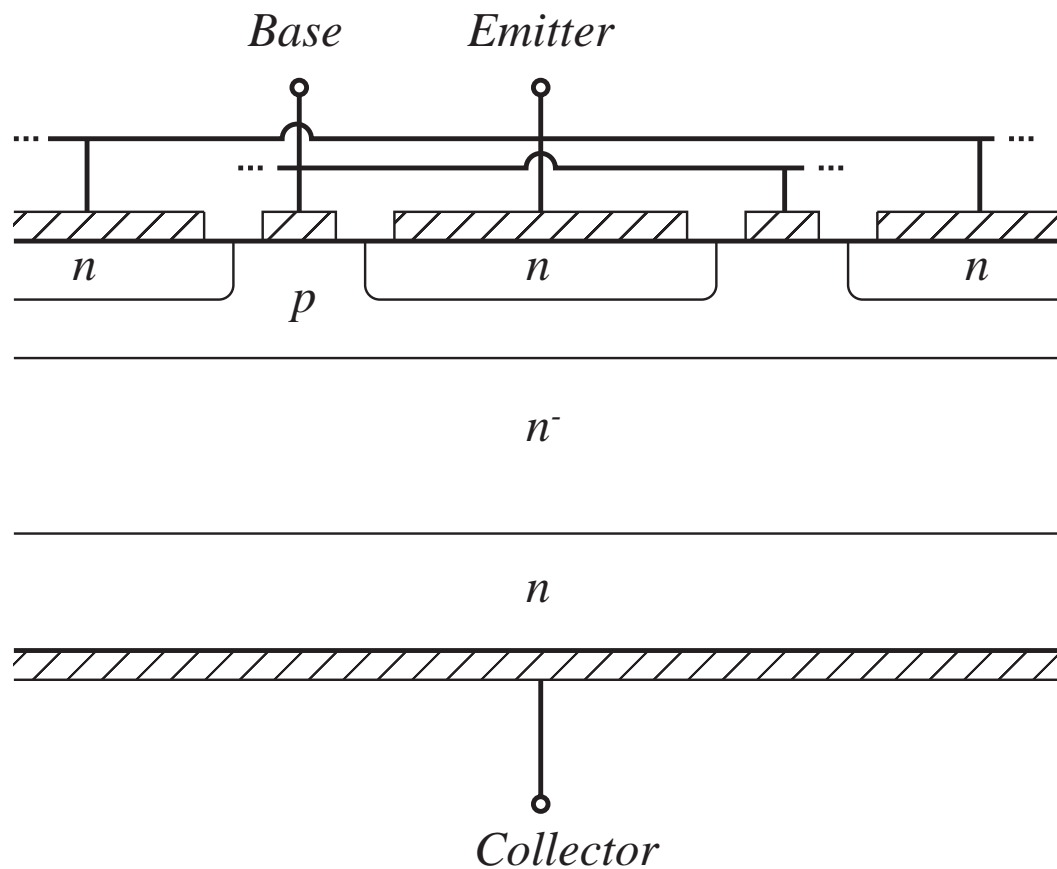
### 4.2.3. Bipolar Junction Transistor (BJT)



- Interdigitated base and emitter contacts
- Vertical current flow
- npn device is shown
- minority carrier device
- on-state: base-emitter and collector-base junctions are both forward-biased
- on-state: substantial minority charge in  $p$  and  $n^-$  regions, conductivity modulation


# BJT switching times

  




# Ideal base current waveform

---

 

 
# Current crowding due to excessive $I_{B2}$




can lead to  
formation of hot  
spots and device  
failure

# BJT characteristics

 

- Off state:  $I_B = 0$
- On state:  $I_B > I_C / \beta$
- Current gain  $\beta$  decreases rapidly at high current. Device should not be operated at instantaneous currents exceeding the rated value

# Breakdown voltages

 

$BV_{CBO}$ : avalanche breakdown voltage of base-collector junction, with the emitter open-circuited


$BV_{CEO}$ : collector-emitter breakdown voltage with zero base current

$BV_{sus}$ : breakdown voltage observed with positive base current

In most applications, the off-state transistor voltage must not exceed  $BV_{CEO}$ .

# Darlington-connected BJT

---

 


- Increased current gain, for high-voltage applications
- In a monolithic Darlington device, transistors  $Q_1$  and  $Q_2$  are integrated on the same silicon wafer
- Diode  $D_1$  speeds up the turn-off process, by allowing the base driver to actively remove the stored charge of both  $Q_1$  and  $Q_2$  during the turn-off transition

## Conclusions: BJT

---



- BJT has been replaced by MOSFET in low-voltage (<500V) applications
- BJT is being replaced by IGBT in applications at voltages above 500V
- A minority-carrier device: compared with MOSFET, the BJT exhibits slower switching, but lower on-resistance at high voltages
 
## 4.2.4. The Insulated Gate Bipolar Transistor (IGBT)




- A four-layer device
- Similar in construction to MOSFET, except extra  $p$  region
- On-state: minority carriers are injected into  $n^-$  region, leading to conductivity modulation
- compared with MOSFET: slower switching times, lower on-resistance, useful at higher voltages (up to 1700V)

# The IGBT

 
 


*Location of equivalent devices*

 



# Current tailing in IGBTs

  

# Characteristics of several commercial devices

<i>Part number</i>	<i>Rated max voltage</i>	<i>Rated avg current</i>	<i>V<sub>F</sub> (typical)</i>	<i>t<sub>f</sub> (typical)</i>
<b><i>Single-chip devices</i></b>				
HGTG32N60E2	600V	32A	2.4V	0.62μs
HGTG30N120D2	1200V	30A	3.2A	0.58μs
<b><i>Multiple-chip power modules</i></b>				
CM400HA-12E	600V	400A	2.7V	0.3μs
CM300HA-24E	1200V	300A	2.7V	0.3μs



# Conclusions: IGBT

---


- Becoming the device of choice in 500-1700V applications, at power levels of 1-1000kW
- Positive temperature coefficient at high current —easy to parallel and construct modules
- Forward voltage drop: diode in series with on-resistance. 2-4V typical
- Easy to drive —similar to MOSFET
- Slower than MOSFET, but faster than Darlington, GTO, SCR
- Typical switching frequencies: 3-30kHz
- IGBT technology is rapidly advancing —next generation: 2500V

## 4.2.5. Thyristors (SCR, GTO, MCT)

### The SCR

  


*construction*

 

 
# The Silicon Controlled Rectifier (SCR)

- Positive feedback —a latching device
- A minority carrier device
- Double injection leads to very low on-resistance, hence low forward voltage drops attainable in very high voltage devices
- Simple construction, with large feature size
- Cannot be actively turned off
- A voltage-bidirectional two-quadrant switch
- 5000-6000V, 1000-2000A devices


 
# Why the conventional SCR cannot be turned off via gate control

- Large feature size
- Negative gate current induces lateral voltage drop along gate-cathode junction
- Gate-cathode junction becomes reverse-biased only in vicinity of gate contact



# The Gate Turn-Off Thyristor (GTO)

---


- An SCR fabricated using modern techniques —small feature size
- Gate and cathode contacts are highly interdigitated
- Negative gate current is able to completely reverse-bias the gate-cathode junction

Turn-off transition:

- Turn-off current gain: typically 2-5
- Maximum controllable on-state current: maximum anode current that can be turned off via gate control. GTO can conduct peak currents well in excess of average current rating, but cannot switch off

 
# The MOS-Controlled Thyristor (MCT)

- Still an emerging device, but some devices are commercially available
- p-type device
- A latching SCR, with added built-in MOSFETs to assist the turn-on and turn-off processes
- Small feature size, highly interdigitated, modern fabrication





# The MCT: equivalent circuit

 

- Negative gate-anode voltage turns p-channel MOSFET  $Q_3$  on, causing  $Q_1$  and  $Q_2$  to latch ON
- Positive gate-anode voltage turns n-channel MOSFET  $Q_4$  on, reverse-biasing the base-emitter junction of  $Q_2$  and turning off the device
- Maximum current that can be interrupted is limited by the on-resistance of  $Q_4$

# Summary: Thyristors

---


- The thyristor family: double injection yields lowest forward voltage drop in high voltage devices. More difficult to parallel than MOSFETs and IGBTs
- The SCR: highest voltage and current ratings, low cost, passive turn-off transition
- The GTO: intermediate ratings (less than SCR, somewhat more than IGBT). Slower than IGBT. Slower than MCT. Difficult to drive.
- The MCT: So far, ratings lower than IGBT. Slower than IGBT. Easy to drive. Second breakdown problems? Still an emerging device.

## 4.3. Switching loss

---

- Energy is lost during the semiconductor switching transitions, via several mechanisms:
  - Transistor switching times
  - Diode stored charge
  - Energy stored in device capacitances and parasitic inductances
- Semiconductor devices are *charge controlled*
- Time required to insert or remove the controlling charge determines switching times
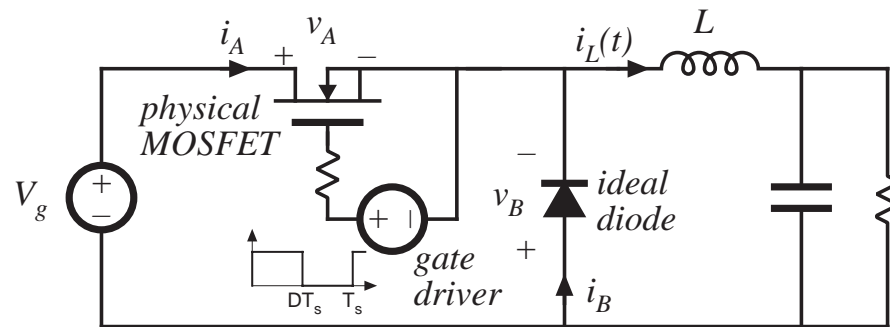
## 4.3.1. Transistor switching with clamped inductive load




*Buck converter example*

$$v_B(t) = v_A(t) - V_g$$

$$i_A(t) + i_B(t) = i_L$$

*transistor turn-off  
transition*
 
$$W_{off} = \frac{1}{2} V_g i_L (t_2 - t_0)$$



# Switching loss induced by transistor turn-off transition

---

Energy lost during transistor turn-off transition:


$$W_{off} = \frac{1}{2} V_g i_L (t_2 - t_0)$$

Similar result during transistor turn-on transition.

Average power loss:

$$P_{sw} = \frac{1}{T_s} \int_{\text{switching transitions}} p_A(t) dt = (W_{on} + W_{off}) f_s$$

 
# Switching loss due to current-tailing in IGBT



 
Example: buck converter with IGBT

transistor turn-off  
transition


$$P_{sw} = \frac{1}{T_s} \int_{\text{switching transitions}} p_A(t) dt = (W_{on} + W_{off}) f_s$$



## 4.3.2. Diode recovered charge

 

 - Diode recovered stored charge  $Q_r$  flows through transistor during transistor turn-on transition, inducing switching loss
- $Q_r$  depends on diode on-state forward current, and on the rate-of-change of diode current during diode turn-off transition



# Switching loss calculation

Energy lost in transistor:


$$W_D = \int_{\text{switching transition}} v_A(t) i_A(t) dt$$

With abrupt-recovery diode:

$$W_D \approx \int_{\text{switching transition}} V_g (i_L - i_B(t)) dt$$

$$= V_g i_L t_r + V_g Q_r$$

 - Often, this is the largest component of switching loss



Soft-recovery diode:

$$(t_2 - t_1) \gg (t_1 - t_0)$$

Abrupt-recovery diode:

$$(t_2 - t_1) \ll (t_1 - t_0)$$



### 4.3.3. Device capacitances, and leakage, package, and stray inductances

---

- Capacitances that appear effectively in parallel with switch elements are shorted when the switch turns on. Their stored energy is lost during the switch turn-on transition.
- Inductances that appear effectively in series with switch elements are open-circuited when the switch turns off. Their stored energy is lost during the switch turn-off transition.


Total energy stored in linear capacitive and inductive elements:

$$W_C = \sum_{\substack{\text{capacitive} \\ \text{elements}}} \frac{1}{2} C_i V_i^2$$

$$W_L = \sum_{\substack{\text{inductive} \\ \text{elements}}} \frac{1}{2} L_j I_j^2$$

# Example: semiconductor output capacitances

## *Buck converter example*

 

Energy lost during MOSFET turn-on transition  
(assuming linear capacitances):

$$W_C = \frac{1}{2} (C_{ds} + C_j) V_g^2$$

# MOSFET nonlinear $C_{ds}$

---

Approximate dependence of incremental  $C_{ds}$  on  $v_{ds}$  :

$$C_{ds}(v_{ds}) \approx C_0 \sqrt{\frac{V_0}{v_{ds}}} = \frac{C'_0}{\sqrt{v_{ds}}}$$

Energy stored in  $C_{ds}$  at  $v_{ds} = V_{DS}$  :

$$W_{Cds} = \int v_{ds} i_C dt = \int_0^{V_{DS}} v_{ds} C_{ds}(v_{ds}) dv_{ds}$$

$$W_{Cds} = \int_0^{V_{DS}} C'_0(v_{ds}) \sqrt{v_{ds}} dv_{ds} = \frac{2}{3} C_{ds}(V_{DS}) V_{DS}^2$$

— same energy loss as linear capacitor having value  $\frac{4}{3} C_{ds}(V_{DS})$

## Some other sources of this type of switching loss

---

### Schottky diode

- Essentially no stored charge
- Significant reverse-biased junction capacitance


### Transformer leakage inductance

- Effective inductances in series with windings
- A significant loss when windings are not tightly coupled


### Interconnection and package inductances

- Diodes
- Transistors
- A significant loss in high current applications

# Ringinduced by diode stored charge

 

 - Diode is forward-biased while  $i_L(t) > 0$
- Negative inductor current removes diode stored charge  $Q_r$
- When diode becomes reverse-biased, negative inductor current flows through capacitor  $C$ .
- Ringing of  $L$ - $C$  network is damped by parasitic losses. Ringing energy is lost.



# Energy associated with ringing

Recovered charge is  $Q_r = - \int_{t_2}^{t_3} i_L(t) dt$

Energy stored in inductor during interval  $t_2 \leq t \leq t_3$  :

$$W_L = \int_{t_2}^{t_3} v_L(t) i_L(t) dt$$


Applied inductor voltage during interval  $t_2 \leq t \leq t_3$  :

$$v_L(t) = L \frac{di_L(t)}{dt} = -V_2$$

Hence,

$$W_L = \int_{t_2}^{t_3} L \frac{di_L(t)}{dt} i_L(t) dt = \int_{t_2}^{t_3} (-V_2) i_L(t) dt$$
 
$$W_L = \frac{1}{2} L i_L^2(t_3) = V_2 Q_r$$



## 4.3.4. Efficiency vs. switching frequency

---

Add up all of the energies lost during the switching transitions of one switching period:

$$W_{tot} = W_{on} + W_{off} + W_D + W_C + W_L + \dots$$

Average switching power loss is

$$P_{sw} = W_{tot} f_{sw}$$

Total converter loss can be expressed as


$$P_{loss} = P_{cond} + P_{fixed} + W_{tot} f_{sw}$$

where

$P_{fixed}$  = fixed losses (independent of load and  $f_{sw}$ )

$P_{cond}$  = conduction losses

# Efficiency vs. switching frequency

 

Switching losses are equal to the other converter losses at the critical frequency

$$f_{crit} = \frac{P_{cond} + P_{fixed}}{W_{tot}}$$

This can be taken as a rough upper limit on the switching frequency of a practical converter. For  $f_{sw} > f_{crit}$ , the efficiency decreases rapidly with frequency.



# Summary of chapter 4

---

1. How an SPST ideal switch can be realized using semiconductor devices depends on the polarity of the voltage which the devices must block in the off-state, and on the polarity of the current which the devices must conduct in the on-state.
2. Single-quadrant SPST switches can be realized using a single transistor or a single diode, depending on the relative polarities of the off-state voltage and on-state current.
3. Two-quadrant SPST switches can be realized using a transistor and diode, connected in series (bidirectional-voltage) or in anti-parallel (bidirectional-current). Several four-quadrant schemes are also listed here.
4. A “synchronous rectifier” is a MOSFET connected to conduct reverse current, with gate drive control as necessary. This device can be used where a diode would otherwise be required. If a MOSFET with sufficiently low  $R_{on}$  is used, reduced conduction loss is obtained.

# Summary of chapter 4

---

5. Majority carrier devices, including the MOSFET and Schottky diode, exhibit very fast switching times, controlled essentially by the charging of the device capacitances. However, the forward voltage drops of these devices increases quickly with increasing breakdown voltage.
6. Minority carrier devices, including the BJT, IGBT, and thyristor family, can exhibit high breakdown voltages with relatively low forward voltage drop. However, the switching times of these devices are longer, and are controlled by the times needed to insert or remove stored minority charge.
7. Energy is lost during switching transitions, due to a variety of mechanisms. The resulting average power loss, or switching loss, is equal to this energy loss multiplied by the switching frequency. Switching loss imposes an upper limit on the switching frequencies of practical converters.

# Summary of chapter 4

---

8. The diode and inductor present a “clamped inductive load” to the transistor. When a transistor drives such a load, it experiences high instantaneous power loss during the switching transitions. An example where this leads to significant switching loss is the IGBT and the “current tail” observed during its turn-off transition.
9. Other significant sources of switching loss include diode stored charge and energy stored in certain parasitic capacitances and inductances. Parasitic ringing also indicates the presence of switching loss.

# Chapter 5. The Discontinuous Conduction Mode

---

- 5.1. Origin of the discontinuous conduction mode, and mode boundary
- 5.2. Analysis of the conversion ratio  $M(D,K)$
- 5.3. Boost converter example
- 5.4. Summary of results and key points


# Introduction to Discontinuous Conduction Mode (DCM)

---

- Occurs because switching ripple in inductor current or capacitor voltage causes polarity of applied switch current or voltage to reverse, such that the current- or voltage-unidirectional assumptions made in realizing the switch are violated.
- Commonly occurs in dc-dc converters and rectifiers, having single-quadrant switches. May also occur in converters having two-quadrant switches.
- Typical example: dc-dc converter operating at light load (small load current). Sometimes, dc-dc converters and rectifiers are purposely designed to operate in DCM at all loads.
- Properties of converters change radically when DCM is entered:
  - $M$  becomes load-dependent
  - Output impedance is increased
  - Dynamics are altered
  - Control of output voltage may be lost when load is removed
 
## 5.1. Origin of the discontinuous conduction mode, and mode boundary

Buck converter example, with single-quadrant switches



Minimum diode current is  $(I - \Delta i_L)$


Dc component  $I = V/R$

Current ripple is

$$\Delta i_L = \frac{(V_g - V)}{2L} DT_s = \frac{V_g DD'T_s}{2L}$$


Note that  $I$  depends on load, but  $\Delta i_L$  does not.

*continuous conduction mode (CCM)*

 

# Reduction of load current

Increase  $R$ , until  $I = \Delta i_L$

 

Minimum diode current is  $(I - \Delta i_L)$



Dc component  $I = V/R$

Current ripple is

$$\Delta i_L = \frac{(V_g - V)}{2L} DT_s = \frac{V_g DD'T_s}{2L}$$


Note that  $I$  depends on load, but  $\Delta i_L$  does not.

CCM-DCM boundary

  
 
# Further reduce load current

Increase  $R$  some more, such that  $I < \Delta i_L$



Minimum diode current is  $(I - \Delta i_L)$

Dc component  $I = V/R$



Current ripple is

$$\Delta i_L = \frac{(V_g - V)}{2L} DT_s = \frac{V_g DD'T_s}{2L}$$

Note that  $I$  depends on load, but  $\Delta i_L$  does not.

The load current continues to be positive and non-zero.

*Discontinuous conduction mode*

  



# Mode boundary

---

$$I > \Delta i_L \text{ for CCM}$$

$$I < \Delta i_L \text{ for DCM}$$

Insert buck converter expressions for  $I$  and  $\Delta i_L$  :

$$\frac{DV_g}{R} < \frac{DD'T_s V_g}{2L}$$

Simplify:

$$\frac{2L}{RT_s} < D'$$


This expression is of the form

$$K < K_{crit}(D) \text{ for DCM}$$


$$\text{where } K = \frac{2L}{RT_s} \text{ and } K_{crit}(D) = D'$$

# $K$ and $K_{crit}$ vs. $D$

for  $K < 1$ :

 

for  $K > 1$ :

 

# Critical load resistance $R_{crit}$

---

Solve  $K_{crit}$  equation for load resistance  $R$ :

$$R < R_{crit}(D) \quad \text{for CCM}$$

$$R > R_{crit}(D) \quad \text{for DCM}$$

where 
$$R_{crit}(D) = \frac{2L}{D'T_s}$$

# Summary: mode boundary

$$\begin{array}{llll}
 K > K_{crit}(D) & or & R < R_{crit}(D) & for\ CCM \\
 K < K_{crit}(D) & or & R > R_{crit}(D) & for\ DCM
 \end{array}$$

Table 5.1. CCM-DCM mode boundaries for the buck, boost, and buck-boost converters

Converter	$K_{crit}(D)$	$\max_{0 \leq D \leq 1} (K_{crit})$	$R_{crit}(D)$	$\min_{0 \leq D \leq 1} (R_{crit})$
Buck	$(1 - D)$	1	$\frac{2L}{(1 - D)T_s}$	$2 \frac{L}{T_s}$
Boost	$D (1 - D)^2$	$\frac{4}{27}$	$\frac{2L}{D (1 - D)^2 T_s}$	$\frac{27}{2} \frac{L}{T_s}$
Buck-boost	$(1 - D)^2$	1	$\frac{2L}{(1 - D)^2 T_s}$	$2 \frac{L}{T_s}$

## 5.2. Analysis of the conversion ratio $M(D,K)$

---

Analysis techniques for the discontinuous conduction mode:

Inductor volt-second balance

$$\langle v_L \rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = 0$$

Capacitor charge balance

$$\langle i_C \rangle = \frac{1}{T_s} \int_0^{T_s} i_C(t) dt = 0$$


Small ripple approximation sometimes applies:

$$v(t) \approx V \quad \text{because} \quad \Delta v \ll V$$

$$i(t) \approx I \quad \text{is a poor approximation when} \quad \Delta i > I$$

Converter steady-state equations obtained via charge balance on each capacitor and volt-second balance on each inductor. Use care in applying small ripple approximation.
 
# Example: Analysis of DCM buck converter $M(D,K)$



# Subinterval 1

---


$$v_L(t) = V_g - v(t)$$

$$i_C(t) = i_L(t) - v(t) / R$$

Small ripple approximation  
for  $v(t)$  (but not for  $i(t)$ !):

$$v_L(t) \approx V_g - V$$

$$i_C(t) \approx i_L(t) - V / R$$

 

## Subinterval 2

---


$$v_L(t) = -v(t)$$

$$i_C(t) = i_L(t) - v(t) / R$$

Small ripple approximation  
for  $v(t)$  but not for  $i(t)$ :

$$v_L(t) \approx -V$$

$$i_C(t) \approx i_L(t) - V / R$$

 




## Subinterval 3


$$v_L = 0, \quad i_L = 0$$
$$i_C(t) = i_L(t) - v(t) / R$$

Small ripple approximation:

$$v_L(t) = 0$$
$$i_C(t) = -V / R$$

 

# Inductor volt-second balance

 

Volt-second balance:

$$\langle v_L(t) \rangle = D_1(V_g - V) + D_2(-V) + D_3(0) = 0$$

Solve for  $V$ :

$$V = V_g \frac{D_1}{D_1 + D_2}$$

note that  $D_2$  is unknown

# Capacitor charge balance

node equation:

$$i_L(t) = i_C(t) + V / R$$



capacitor charge balance:

$$\langle i_C \rangle = 0$$

hence

$$\langle i_L \rangle = V / R$$

  must compute dc component of inductor current and equate to load current (for this buck converter example)



# Inductor current waveform

peak current:

$$i_L(D_1 T_s) = i_{pk} = \frac{V_g - V}{L} D_1 T_s$$


average current:

$$\langle i_L \rangle = \frac{1}{T_s} \int_0^{T_s} i_L(t) dt$$

triangle area formula:

$$\int_0^{T_s} i_L(t) dt = \frac{1}{2} i_{pk} (D_1 + D_2) T_s$$
 
$$\langle i_L \rangle = (V_g - V) \frac{D_1 T_s}{2L} (D_1 + D_2)$$



equate dc component to dc load current:

$$\frac{V}{R} = \frac{D_1 T_s}{2L} (D_1 + D_2) (V_g - V)$$

## Solution for $V$

---

Two equations and two unknowns ( $V$  and  $D_2$ ):

$$V = V_g \frac{D_1}{D_1 + D_2} \quad (\text{from inductor volt-second balance})$$

$$\frac{V}{R} = \frac{D_1 T_s}{2L} (D_1 + D_2) (V_g - V) \quad (\text{from capacitor charge balance})$$


Eliminate  $D_2$ , solve for  $V$ :

$$\frac{V}{V_g} = \frac{2}{1 + \sqrt{1 + 4K / D_1^2}}$$


where  $K = 2L / RT_s$

valid for  $K < K_{crit}$

# Buck converter $M(D,K)$

 

## 5.3. Boost converter example

 

Mode boundary:

$$I > \Delta i_L \text{ for CCM}$$

$$I < \Delta i_L \text{ for DCM}$$

Previous CCM soln:

$$I = \frac{V_g}{D'^2 R} \quad \Delta i_L = \frac{V_g}{2L} DT_s$$

# Mode boundary


$$\frac{V_g}{D'^2 R} > \frac{DT_s V_g}{2L} \quad \text{for CCM}$$

$$\frac{2L}{RT_s} > DD'^2 \quad \text{for CCM}$$

$$K > K_{crit}(D) \quad \text{for CCM}$$

$$K < K_{crit}(D) \quad \text{for DCM}$$

 
$$\text{where } K = \frac{2L}{RT_s} \quad \text{and} \quad K_{crit}(D) = DD'^2$$





 
# Mode boundary

$K > K_{crit}(D)$  for CCM  
 $K < K_{crit}(D)$  for DCM  
 where  $K = \frac{2L}{RT_s}$  and  $K_{crit}(D) = DD'^2$



# Conversion ratio: DCM boost

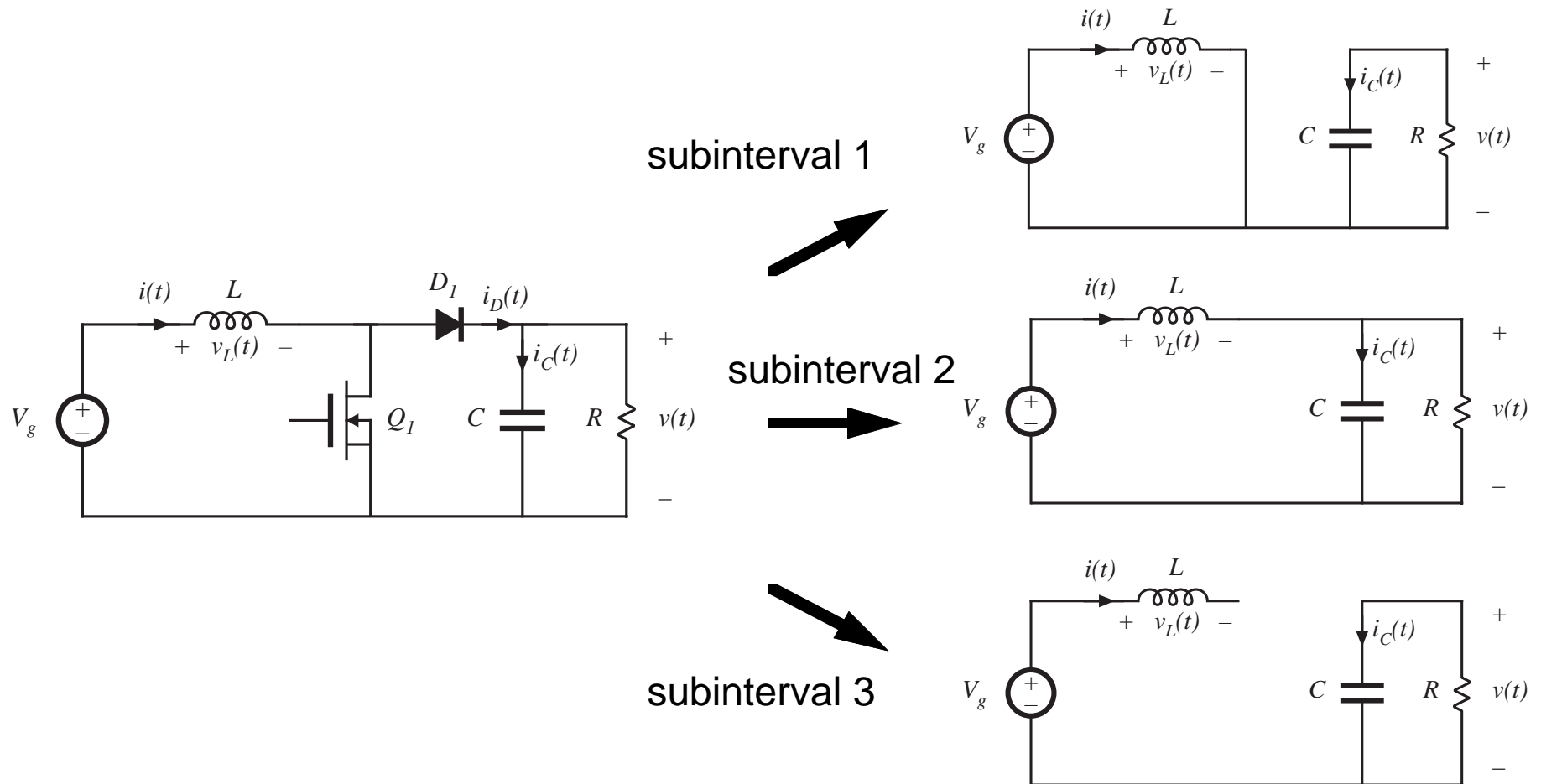

# Subinterval 1


$$v_L(t) = V_g$$

$$i_C(t) = -v(t) / R$$

Small ripple approximation  
for  $v(t)$  (but not for  $i(t)$ ):

$$v_L(t) \approx V_g$$

$$i_C(t) \approx -V / R$$

 

$$0 < t < D_I T_s$$

## Subinterval 2


$$v_L(t) = V_g - v(t)$$

$$i_C(t) = i(t) - v(t) / R$$

Small ripple approximation  
for  $v(t)$  but not for  $i(t)$ :

$$v_L(t) \approx V_g - V$$

$$i_C(t) \approx i(t) - V / R$$

 


$$D_1 T_s < t < (D_1 + D_2) T_s$$

## Subinterval 3

$$v_L = 0, \quad i = 0$$
$$i_C(t) = -v(t) / R$$


Small ripple approximation:

$$v_L(t) = 0$$
$$i_C(t) = -V / R$$

 

$$(D_1 + D_2)T_s < t < T_s$$

# Inductor volt-second balance

 

Volt-second balance:

$$D_1 V_g + D_2 (V_g - V) + D_3 (0) = 0$$

Solve for  $V$ :

$$V = \frac{D_1 + D_2}{D_2} V_g$$

note that  $D_2$  is unknown

# Capacitor charge balance

node equation:

$$i_D(t) = i_C(t) + v(t) / R$$


capacitor charge balance:

$$\langle i_C \rangle = 0$$

hence

$$\langle i_D \rangle = V / R$$

 must compute dc component of diode current and equate to load current (for this boost converter example)



# Inductor and diode current waveforms

peak current:


$$i_{pk} = \frac{V_g}{L} D_1 T_s$$

average diode current:

$$\langle i_D \rangle = \frac{1}{T_s} \int_0^{T_s} i_D(t) dt$$

triangle area formula:
 
$$\int_0^{T_s} i_D(t) dt = \frac{1}{2} i_{pk} D_2 T_s$$





## Equate diode current to load current

---

average diode current:

$$\langle i_D \rangle = \frac{1}{T_s} \left( \frac{1}{2} i_{pk} D_2 T_s \right) = \frac{V_g D_1 D_2 T_s}{2L}$$

equate to dc load current:

$$\frac{V_g D_1 D_2 T_s}{2L} = \frac{V}{R}$$

## Solution for $V$

---

Two equations and two unknowns ( $V$  and  $D_2$ ):

$$V = \frac{D_1 + D_2}{D_2} V_g \quad \text{(from inductor volt-second balance)}$$

$$\frac{V_g D_1 D_2 T_s}{2L} = \frac{V}{R} \quad \text{(from capacitor charge balance)}$$

Eliminate  $D_2$ , solve for  $V$ . From volt-sec balance eqn:

$$D_2 = D_1 \frac{V_g}{V - V_g}$$

Substitute into charge balance eqn, rearrange terms:

$$V^2 - V V_g - \frac{V_g^2 D_1^2}{K} = 0$$

## Solution for $V$

---

$$V^2 - VV_g - \frac{V_g^2 D_1^2}{K} = 0$$

Use quadratic formula:

$$\frac{V}{V_g} = \frac{1 \pm \sqrt{1 + 4D_1^2 / K}}{2}$$


Note that one root leads to positive  $V$ , while other leads to negative  $V$ . Select positive root:

$$\frac{V}{V_g} = M(D_1, K) = \frac{1 + \sqrt{1 + 4D_1^2 / K}}{2}$$

where  $K = 2L / RT_s$   
valid for  $K < K_{crit}(D)$

Transistor duty cycle  $D$  = interval 1 duty cycle  $D_1$

# Boost converter characteristics

 

$$M = \begin{cases} \frac{1}{1-D} & \text{for } K > K_{crit} \\ \frac{1 + \sqrt{1 + 4D^2 / K}}{2} & \text{for } K < K_{crit} \end{cases}$$

Approximate  $M$  in DCM:

$$M \approx \frac{1}{2} + \frac{D}{\sqrt{K}}$$


# Summary of DCM characteristics

*Table 5.2. Summary of CCM-DCM characteristics for the buck, boost, and buck-boost converters*

<i>Converter</i>	$K_{crit}(D)$	<i>DCM</i> $M(D, K)$	<i>DCM</i> $D_2(D, K)$	<i>CCM</i> $M(D)$
Buck	$(1 - D)$	$\frac{2}{1 + \sqrt{1 + 4K / D^2}}$	$\frac{K}{D} M(D, K)$	$D$
Boost	$D (1 - D)^2$	$\frac{2}{1 + \sqrt{1 + 4D^2 / K}}$	$\frac{K}{D} M(D, K)$	$\frac{1}{1 - D}$
Buck-boost	$(1 - D)^2$	$-\frac{D}{\sqrt{K}}$	$\sqrt{K}$	$-\frac{D}{1 - D}$

*with*  $K = 2L / RT_s$ . *DCM occurs for*  $K < K_{crit}$ .

# Summary of DCM characteristics

 

- DCM buck and boost characteristics are asymptotic to  $M = 1$  and to the DCM buck-boost characteristic
- DCM buck-boost characteristic is linear
- CCM and DCM characteristics intersect at mode boundary. Actual  $M$  follows characteristic having larger magnitude
- DCM boost characteristic is nearly linear

# Summary of key points

---

1. The discontinuous conduction mode occurs in converters containing current- or voltage-unidirectional switches, when the inductor current or capacitor voltage ripple is large enough to cause the switch current or voltage to reverse polarity.
2. Conditions for operation in the discontinuous conduction mode can be found by determining when the inductor current or capacitor voltage ripples and dc components cause the switch on-state current or off-state voltage to reverse polarity.
3. The dc conversion ratio  $M$  of converters operating in the discontinuous conduction mode can be found by application of the principles of inductor volt-second and capacitor charge balance.

# Summary of key points

---

4. Extra care is required when applying the small-ripple approximation. Some waveforms, such as the output voltage, should have small ripple which can be neglected. Other waveforms, such as one or more inductor currents, may have large ripple that cannot be ignored.
5. The characteristics of a converter changes significantly when the converter enters DCM. The output voltage becomes load-dependent, resulting in an increase in the converter output impedance.



# Chapter 6. Converter Circuits

---

6.1. Circuit manipulations

6.2. A short list of  
converters

6.3. Transformer isolation


6.4. Converter evaluation  
and design

6.5. Summary of key  
points

- Where do the boost, buck-boost, and other converters originate?
- How can we obtain a converter having given desired properties?
- What converters are possible?
- How can we obtain transformer isolation in a converter?
- For a given application, which converter is best?

## 6.1. Circuit manipulations

---

 

Begin with buck converter: derived in chapter 1 from first principles


- Switch changes dc component, low-pass filter removes switching harmonics
- Conversion ratio is  $M = D$

## 6.1.1. Inversion of source and load

Interchange power input and output ports of a converter


Buck converter example

$$V_2 = DV_1$$

 

# Inversion of source and load

Interchange power source and load:

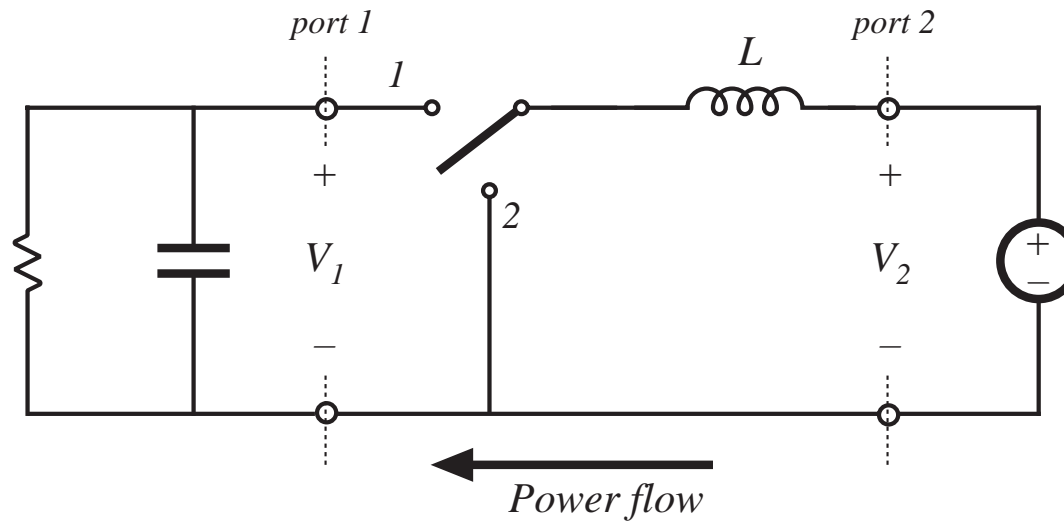


$$V_2 = DV_1 \qquad V_1 = \frac{1}{D} V_2$$

# Realization of switches as in chapter 4


- Reversal of power flow requires new realization of switches
- Transistor conducts when switch is in position 2
- Interchange of  $D$  and  $D'$

$$V_1 = \frac{1}{D'} V_2$$

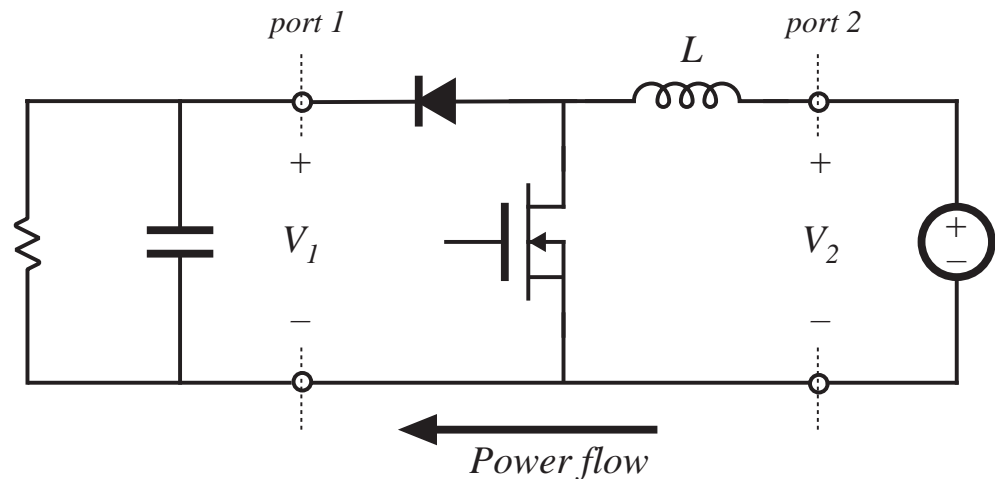


Inversion of buck converter yields boost converter
 
## 6.1.2. Cascade connection of converters



$$\begin{aligned} V_1 &= M_1(D) V_g \\ V &= M_2(D) V_1 \end{aligned} \quad \longrightarrow \quad \frac{V}{V_g} = M(D) = M_1(D) M_2(D)$$


## Example: buck cascaded by boost

 


$$\begin{aligned} \frac{V_1}{V_g} &= D \\ \frac{V}{V_1} &= \frac{1}{1-D} \end{aligned} \quad \longrightarrow \quad \frac{V}{V_g} = \frac{D}{1-D}$$

# Buck cascaded by boost: simplification of internal filter

remove capacitor  $C_1$

 


combine inductors  $L_1$  and  $L_2$

 

*Noninverting  
buck-boost  
converter*





# Noninverting buck-boost converter

 


*subinterval 1*

*subinterval 2*

  


# Reversal of output voltage polarity

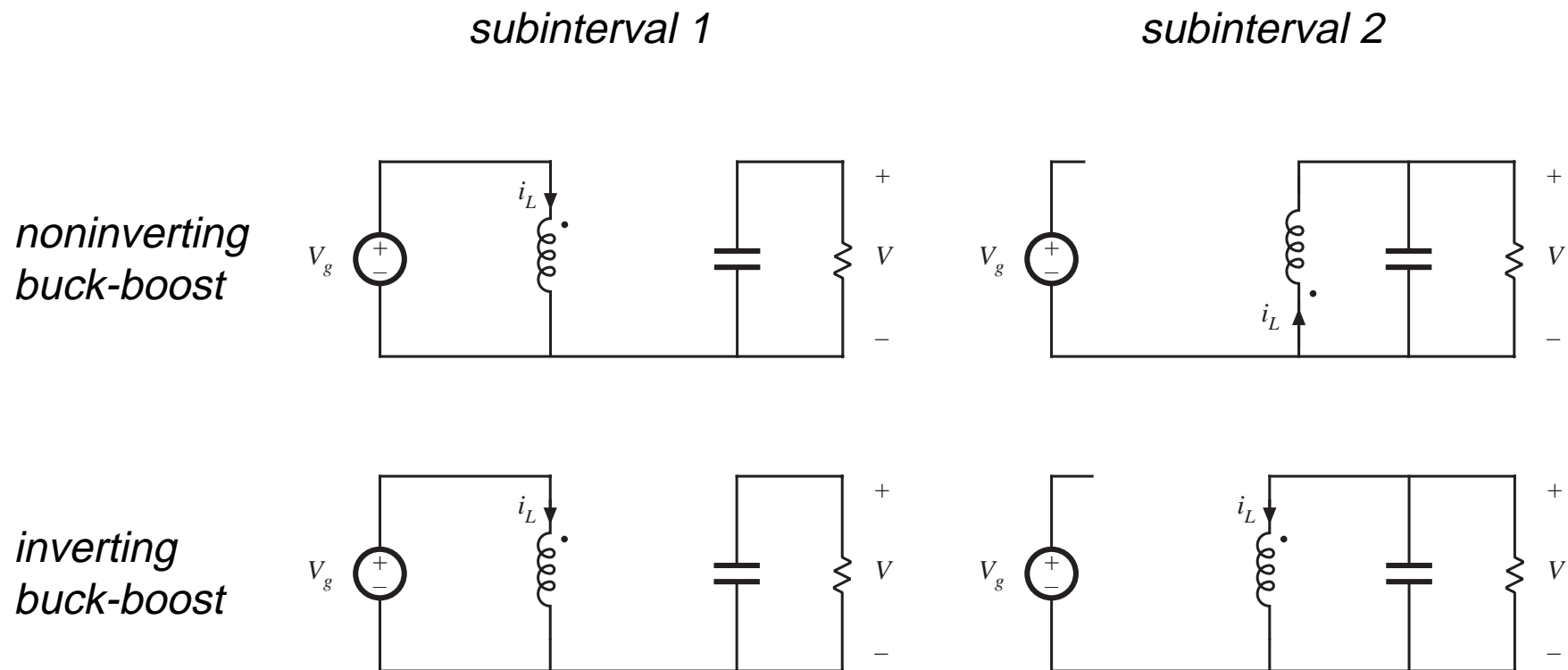


# Reduction of number of switches: inverting buck-boost


*subinterval 1*

 

*subinterval 2*

 

 One side of inductor always connected to ground  
— hence, only one SPDT switch needed:



$$\frac{V}{V_g} = -\frac{D}{1-D}$$

# Discussion: cascade connections

---

- Properties of buck-boost converter follow from its derivation as buck cascaded by boost

Equivalent circuit model: buck  $1:D$  transformer cascaded by boost  $D':1$  transformer

Pulsating input current of buck converter


Pulsating output current of boost converter

- Other cascade connections are possible

Cuk converter: boost cascaded by buck
 
## 6.1.3. Rotation of three-terminal cell

Treat inductor and SPDT switch as three-terminal cell:




Three-terminal cell can be connected between source and load in three nontrivial distinct ways:

a-A b-B c-C	buck converter
a-C b-A c-B	boost converter
a-A b-C c-B	buck-boost converter
 
# Rotation of a dual three-terminal network

A capacitor and SPDT switch as a three-terminal cell:



Three-terminal cell can be connected between source and load in three nontrivial distinct ways:

a-A b-B c-C

buck converter with L-C input filter


a-C b-A c-B

boost converter with L-C output filter

a-A b-C c-B

Cuk converter
 
## 6.1.4. Differential connection of load to obtain bipolar output voltage




Differential load voltage is

$$V = V_1 - V_2$$

The outputs  $V_1$  and  $V_2$  may both be positive, but the differential output voltage  $V$  can be positive or negative.
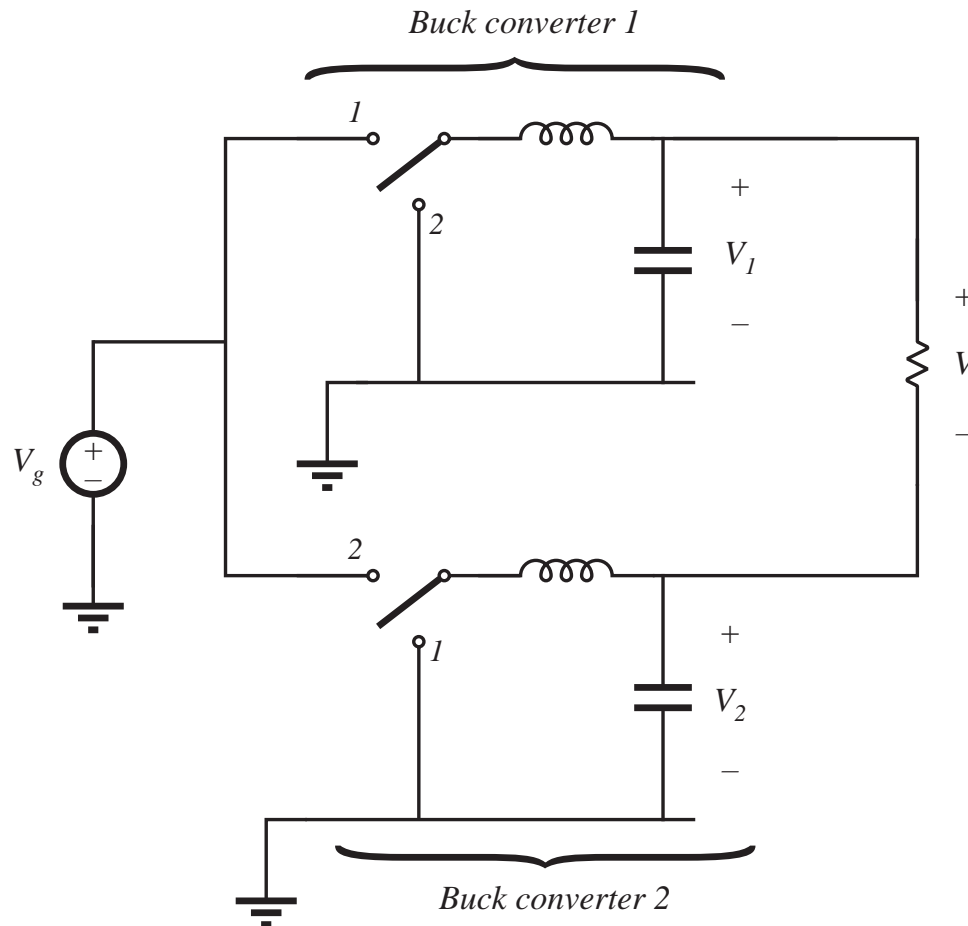
# Differential connection using two buck converters



Converter #1 transistor driven with duty cycle  $D$

Converter #2 transistor driven with duty cycle complement  $D'$

Differential load voltage is

$$V = DV_g - D'V_g$$

Simplify:


$$V = (2D - 1) V_g$$



# Conversion ratio $M(D)$ , differentially-connected buck converters


---

$$V = (2D - 1) V_g$$

 


# Simplification of filter circuit, differentially-connected buck converters

Original circuit

 


Bypass load directly with capacitor

 


# Simplification of filter circuit, differentially-connected buck converters

Combine series-connected  
inductors

 


Re-draw for clarity

 

H-bridge, or bridge inverter

Commonly used in single-phase  
inverter applications and in servo  
amplifier applications
 
# Differential connection to obtain 3Ø inverter



With balanced 3Ø load, neutral voltage is

$$V_n = \frac{1}{3} (V_1 + V_2 + V_3)$$

Phase voltages are


$$V_{an} = V_1 - V_n$$

$$V_{bn} = V_2 - V_n$$

$$V_{cn} = V_3 - V_n$$


Control converters such that their output voltages contain the same dc biases. This dc bias will appear at the neutral point  $V_n$ . It then cancels out, so phase voltages contain no dc bias.
 
## 3 $\phi$ differential connection of three buck converters



## 3 $\phi$ differential connection of three buck converters

Re-draw for clarity:

 

“Voltage-source inverter” or buck-derived three-phase inverter

## 6.2. A short list of converters

---

An infinite number of converters are possible, which contain switches embedded in a network of inductors and capacitors

Two simple classes of converters are listed here:

- Single-input single-output converters containing a single inductor. The switching period is divided into two subintervals. This class contains eight converters.
- Single-input single-output converters containing two inductors. The switching period is divided into two subintervals. Several of the more interesting members of this class are listed.

# Single-input single-output converters containing one inductor

---

- Use switches to connect inductor between source and load, in one manner during first subinterval and in another during second subinterval
- There are a limited number of ways to do this, so all possible combinations can be found
- After elimination of degenerate and redundant cases, eight converters are found:

## *dc-dc converters*

buck    boost    buck-boost    noninverting buck-boost

## *dc-ac converters*

bridge    Watkins-Johnson

## *ac-dc converters*



current-fed bridge    inverse of Watkins-Johnson



# Converters producing a unipolar output voltage



## 1. Buck

$$M(D) = D$$

  

## 2. Boost



$$M(D) = \frac{1}{1-D}$$

  

# Converters producing a unipolar output voltage



3. Buck-boost

$$M(D) = -\frac{D}{1-D}$$

  

4. Noninverting buck-boost



$$M(D) = \frac{D}{1-D}$$

  

# Converters producing a bipolar output voltage suitable as dc-ac inverters


5. Bridge

$$M(D) = 2D - 1$$

 
 


6. Watkins-Johnson

$$M(D) = \frac{2D - 1}{D}$$

 



or

  

# Converters producing a bipolar output voltage suitable as ac-dc rectifiers




7. Current-fed bridge

$$M(D) = \frac{1}{2D-1}$$



 
 


8. Inverse of Watkins-Johnson

$$M(D) = \frac{D}{2D-1}$$

   

   
 
# Several members of the class of two-inductor converters



# Several members of the class of two-inductor converters



3. Inverse of SEPIC

$$M(D) = \frac{D}{1-D}$$

  

4. Buck<sup>2</sup>

$$M(D) = D^2$$

  

## 6.3. Transformer isolation


---

### Objectives:


- Isolation of input and output ground connections, to meet safety requirements
- Reduction of transformer size by incorporating high frequency isolation transformer inside converter
- Minimization of current and voltage stresses when a large step-up or step-down conversion ratio is needed — use transformer turns ratio
- Obtain multiple output voltages via multiple transformer secondary windings and multiple converter secondary circuits

# A simple transformer model

*Multiple winding transformer*

 

*Equivalent circuit model*

 




# The magnetizing inductance $L_M$

- Models magnetization of transformer core material
- Appears effectively in parallel with windings
- If all secondary windings are disconnected, then primary winding behaves as an inductor, equal to the magnetizing inductance
- At dc: magnetizing inductance tends to short-circuit. Transformers cannot pass dc voltages
- Transformer saturates when magnetizing current  $i_M$  is too large

*Transformer core B-H characteristic*

 

# Volt-second balance in $L_M$

The magnetizing inductance is a real inductor, obeying


$$v_1(t) = L_M \frac{di_M(t)}{dt}$$

integrate:

$$i_M(t) - i_M(0) = \frac{1}{L_M} \int_0^t v_1(\tau) d\tau$$

Magnetizing current is determined by integral of the applied winding voltage. The magnetizing current and the winding currents are independent quantities. Volt-second balance applies: in steady-state,  $i_M(T_s) = i_M(0)$ , and hence
 
$$0 = \frac{1}{T_s} \int_0^{T_s} v_1(t) dt$$




# Transformer reset

---


- “Transformer reset” is the mechanism by which magnetizing inductance volt-second balance is obtained
- The need to reset the transformer volt-seconds to zero by the end of each switching period adds considerable complexity to converters
- To understand operation of transformer-isolated converters:
  - replace transformer by equivalent circuit model containing magnetizing inductance
  - analyze converter as usual, treating magnetizing inductance as any other inductor
  - apply volt-second balance to all converter inductors, including magnetizing inductance

## 6.3.1. Full-bridge and half-bridge isolated buck converters


*Full-bridge isolated buck converter*

 
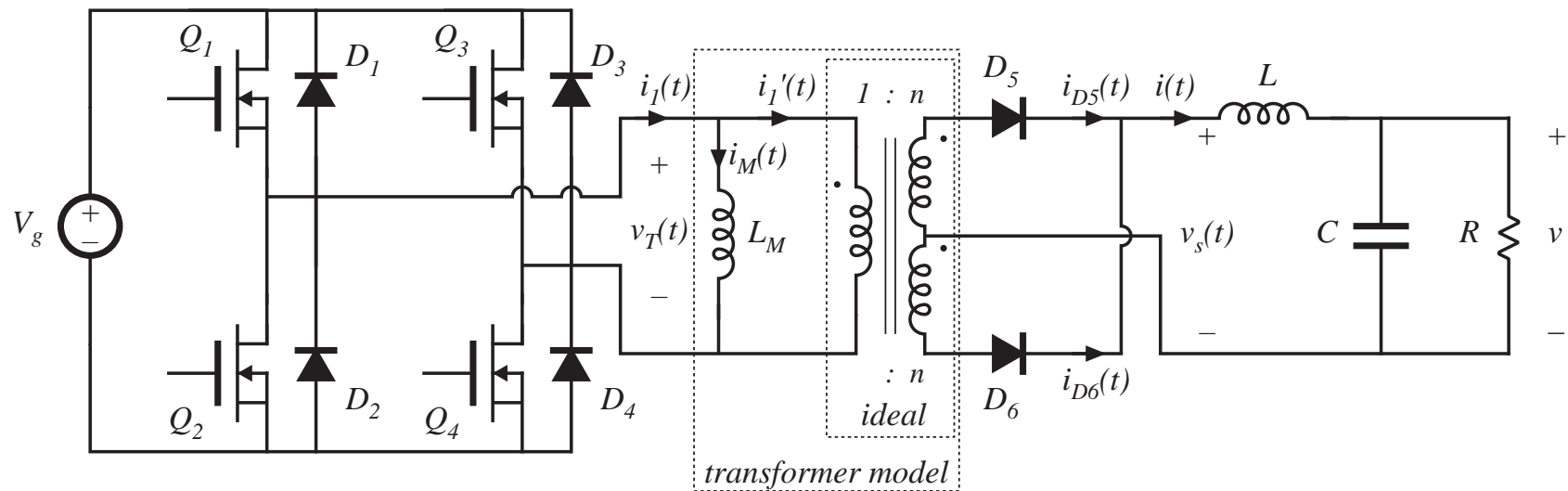
# Full-bridge, with transformer equivalent circuit



# Full-bridge: waveforms

 

- During first switching period: transistors  $Q_1$  and  $Q_4$  conduct for time  $DT_s$ , applying volt-seconds  $V_g DT_s$  to primary winding
- During next switching period: transistors  $Q_2$  and  $Q_3$  conduct for time  $DT_s$ , applying volt-seconds  $-V_g DT_s$  to primary winding
- Transformer volt-second balance is obtained over two switching periods
- Effect of nonidealities?

## Effect of nonidealities on transformer volt-second balance

---

Volt-seconds applied to primary winding during first switching period:

$$(V_g - (Q_1 \text{ and } Q_4 \text{ forward voltage drops}))(Q_1 \text{ and } Q_4 \text{ conduction time})$$

Volt-seconds applied to primary winding during next switching period:

$$- (V_g - (Q_2 \text{ and } Q_3 \text{ forward voltage drops}))(Q_2 \text{ and } Q_3 \text{ conduction time})$$



These volt-seconds never add to *exactly* zero.

Net volt-seconds are applied to primary winding

Magnetizing current slowly increases in magnitude

Saturation can be prevented by placing a capacitor in series with primary, or by use of current programmed mode (chapter 11)


# Operation of secondary-side diodes

 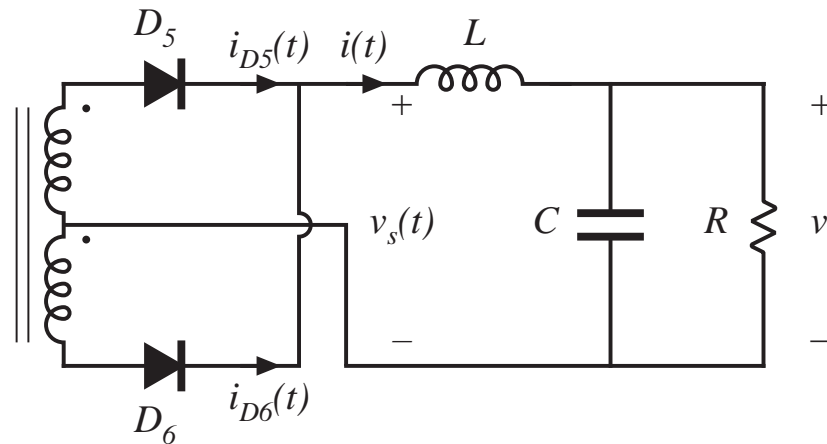

- During second ( $D'$ ) subinterval, both secondary-side diodes conduct
- Output filter inductor current divides approximately equally between diodes
- Secondary amp-turns add to approximately zero
- Essentially no net magnetization of transformer core by secondary winding currents


 
# Volt-second balance on output filter inductor




$$V = \langle v_s \rangle$$


$$V = nDV_g$$

$$M(D) = nD$$

buck converter with turns ratio

 


# Half-bridge isolated buck converter

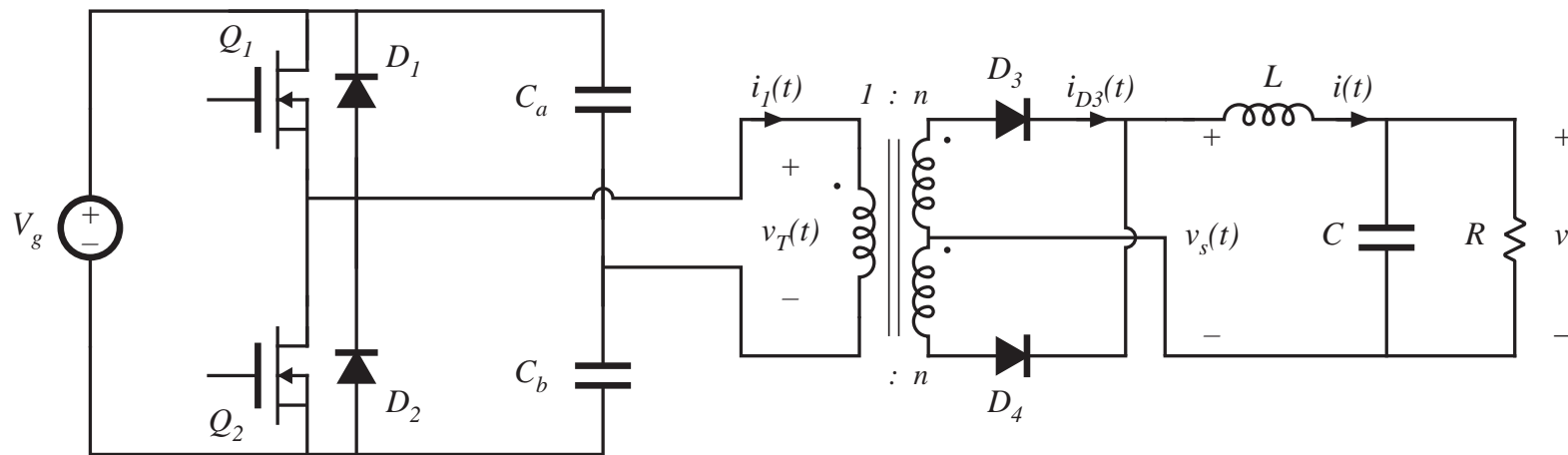


- Replace transistors  $Q_3$  and  $Q_4$  with large capacitors
- Voltage at capacitor centerpoint is  $0.5V_g$
- $v_s(t)$  is reduced by a factor of two
- $M = 0.5 nD$

## 6.3.2. Forward converter

 


- Buck-derived transformer-isolated converter
- Single-transistor and two-transistor versions
- Maximum duty cycle is limited
- Transformer is reset while transistor is off
 
# Forward converter with transformer equivalent circuit




# Forward converter: waveforms

 


- Magnetizing current, in conjunction with diode  $D_1$ , operates in discontinuous conduction mode
- Output filter inductor, in conjunction with diode  $D_3$ , may operate in either CCM or DCM


# Subinterval 1: transistor conducts

 

## Subinterval 2: transformer reset

 


## Subinterval 3

 


 
# Magnetizing inductance volt-second balance



$$\langle v_l \rangle = D (V_g) + D_2 (-V_g n_1 / n_2) + D_3 (0) = 0$$

# Transformer reset

---

From magnetizing current volt-second balance:

$$\langle v_1 \rangle = D (V_g) + D_2 (-V_g n_1 / n_2) + D_3 (0) = 0$$

Solve for  $D_2$ :

$$D_2 = \frac{n_2}{n_1} D$$

$D_3$  cannot be negative. But  $D_3 = 1 - D - D_2$ . Hence

$$D_3 = 1 - D - D_2 \geq 0$$

$$D_3 = 1 - D \left( 1 + \frac{n_2}{n_1} \right) \geq 0$$


Solve for  $D$

$$D \leq \frac{1}{1 + \frac{n_2}{n_1}}$$



$$\text{for } n_1 = n_2: \quad D \leq \frac{1}{2}$$
 
# What happens when $D > 0.5$

magnetizing current  
waveforms,  
for  $n_1 = n_2$



# Conversion ratio $M(D)$

  

$$\langle v_{D3} \rangle = V = \frac{n_3}{n_1} D V_g$$

## Maximum duty cycle vs. transistor voltage stress

---

Maximum duty cycle limited to

$$D \leq \frac{1}{1 + \frac{n_2}{n_1}}$$


which can be increased by increasing the turns ratio  $n_2 / n_1$ . But this increases the peak transistor voltage:

$$\max v_{Q1} = V_g \left( 1 + \frac{n_1}{n_2} \right)$$

For  $n_1 = n_2$

$$D \leq \frac{1}{2} \quad \text{and} \quad \max v_{Q1} = 2V_g$$

# The two-transistor forward converter

 


$$V = nDV_g$$

$$D \leq \frac{1}{2}$$

$$\max v_{Q1} = \max v_{Q2} = V_g$$

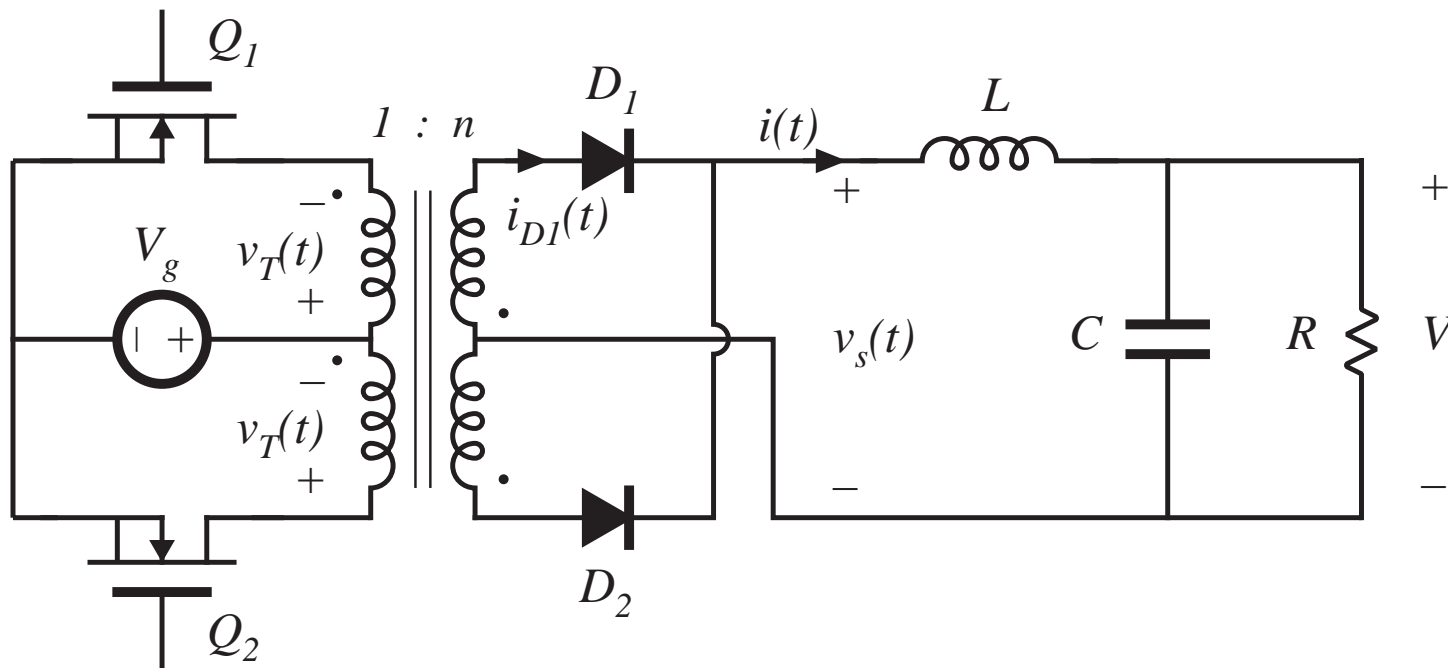
### 6.3.3. Push-pull isolated buck converter



$$V = nDV_g$$

$$0 \leq D \leq 1$$

# Waveforms: push-pull

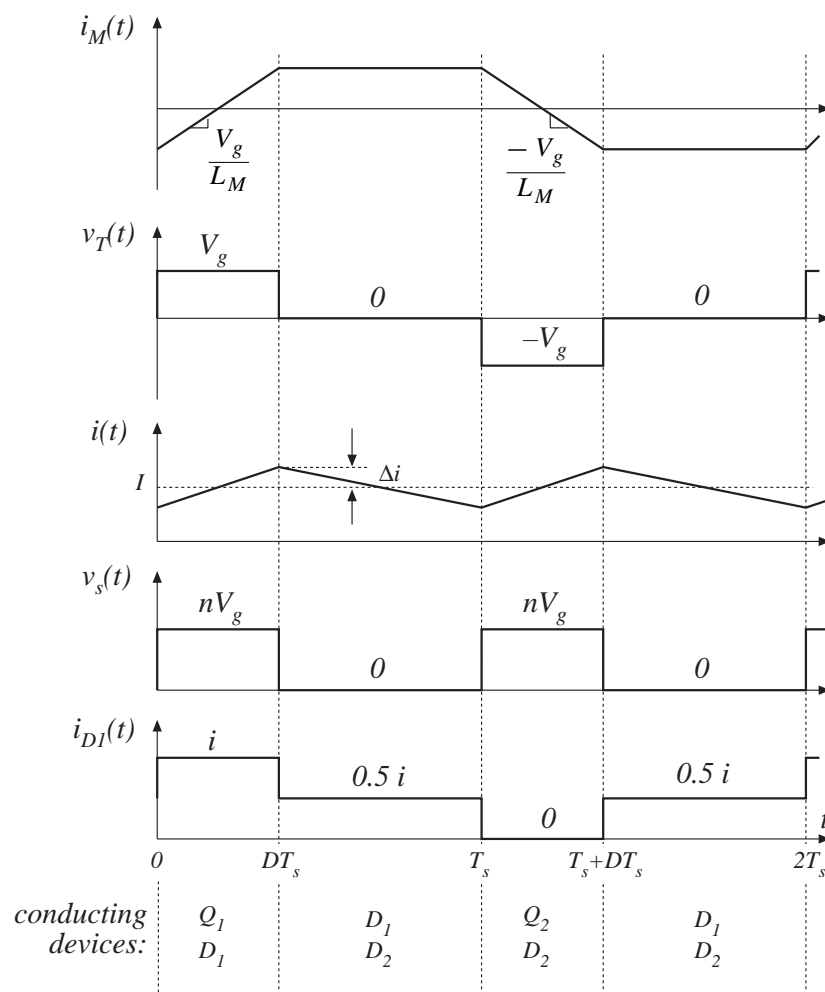


- Used with low-voltage inputs
- Secondary-side circuit identical to full bridge
- As in full bridge, transformer volt-second balance is obtained over two switching periods
- Effect of nonidealities on transformer volt-second balance?
- Current programmed control can be used to mitigate transformer saturation problems. Duty cycle control not recommended.




## 6.3.4. Flyback converter

*buck-boost converter:*

 


 *construct inductor winding using two parallel wires:*



 
## Derivation of flyback converter, cont.


*Isolate inductor windings: the flyback converter*



 *Flyback converter having a  $1:n$  turns ratio and positive output:*




# The “flyback transformer”

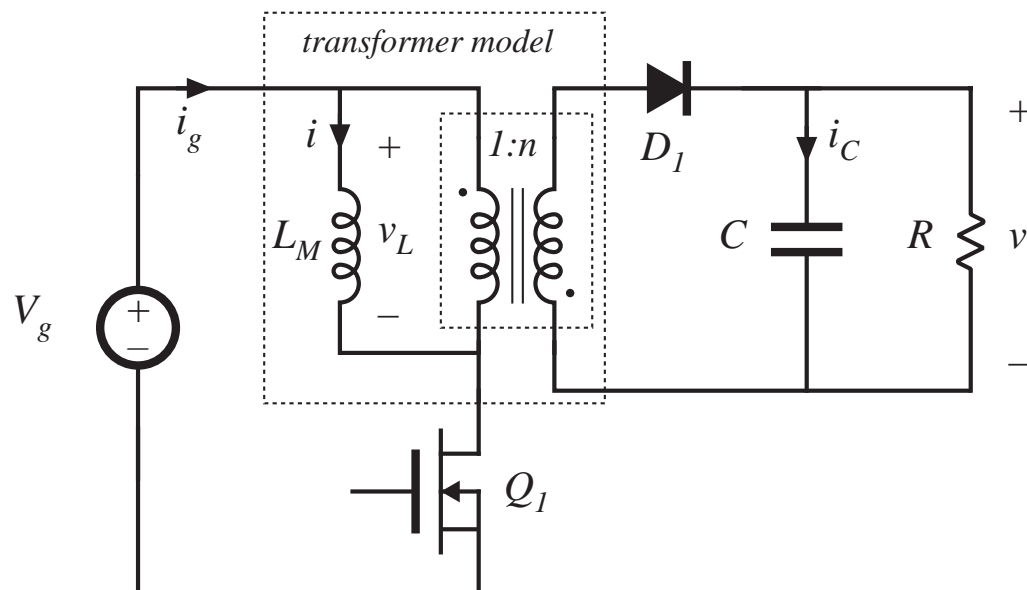

- A two-winding inductor
- Symbol is same as transformer, but function differs significantly from ideal transformer
- Energy is stored in magnetizing inductance
- Magnetizing inductance is relatively small

- Current does not simultaneously flow in primary and secondary windings
- Instantaneous winding voltages follow turns ratio
- Instantaneous (and rms) winding currents do not follow turns ratio
- Model as (small) magnetizing inductance in parallel with ideal transformer

# Subinterval 1

 


$$\begin{aligned} v_L &= V_g \\ i_C &= -\frac{v}{R} \\ i_g &= i \end{aligned}$$

CCM: small ripple approximation leads to

$$\begin{aligned} v_L &= V_g \\ i_C &= -\frac{V}{R} \\ i_g &= I \end{aligned}$$

## Subinterval 2

 


$$\begin{aligned} v_L &= -\frac{v}{n} \\ i_C &= \frac{i}{n} - \frac{v}{R} \\ i_g &= 0 \end{aligned}$$

CCM: small ripple approximation leads to

$$\begin{aligned} v_L &= -\frac{V}{n} \\ i_C &= \frac{I}{n} - \frac{V}{R} \\ i_g &= 0 \end{aligned}$$

# CCM Flyback waveforms and solution

 

Volt-second balance:

$$\langle v_L \rangle = D (V_g) + D' \left(-\frac{V}{n}\right) = 0$$

Conversion ratio is

$$M(D) = \frac{V}{V_g} = n \frac{D}{D'}$$

Charge balance:

$$\langle i_C \rangle = D \left(-\frac{V}{R}\right) + D' \left(\frac{I}{n} - \frac{V}{R}\right) = 0$$

Dc component of magnetizing current is

$$I = \frac{nV}{D'R}$$

Dc component of source current is



$$I_g = \langle i_g \rangle = D (I) + D' (0)$$

# Equivalent circuit model: CCM Flyback

$$\langle v_L \rangle = D(V_g) + D'(-\frac{V}{n}) = 0$$

$$\langle i_C \rangle = D(-\frac{V}{R}) + D'(\frac{I}{n} - \frac{V}{R}) = 0$$
 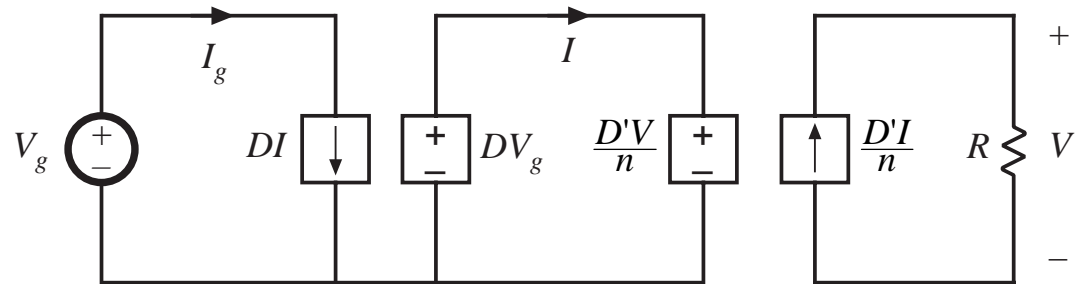
$$I_g = \langle i_g \rangle = D(I) + D'(0)$$



# Discussion: Flyback converter

---

- Widely used in low power and/or high voltage applications
- Low parts count
- Multiple outputs are easily obtained, with minimum additional parts
- Cross regulation is inferior to buck-derived isolated converters
- Often operated in discontinuous conduction mode
- DCM analysis: DCM buck-boost with turns ratio




## 6.3.5. Boost-derived isolated converters

---

- A wide variety of boost-derived isolated dc-dc converters can be derived, by inversion of source and load of buck-derived isolated converters:
  - full-bridge and half-bridge isolated boost converters
  - inverse of forward converter: the “reverse” converter
  - push-pull boost-derived converter


Of these, the full-bridge and push-pull boost-derived isolated converters are the most popular, and are briefly discussed here.
 
# Full-bridge transformer-isolated boost-derived converter




- Circuit topologies are equivalent to those of nonisolated boost converter
- With 1:1 turns ratio, inductor current  $i(t)$  and output current  $i_o(t)$  waveforms are identical to nonisolated boost converter

# Transformer reset mechanism

 

- As in full-bridge buck topology, transformer volt-second balance is obtained over two switching periods.
- During first switching period: transistors  $Q_1$  and  $Q_4$  conduct for time  $DT_s$ , applying volt-seconds  $VDT_s$  to secondary winding.
- During next switching period: transistors  $Q_2$  and  $Q_3$  conduct for time  $DT_s$ , applying volt-seconds  $-VDT_s$  to secondary winding.

# Conversion ratio $M(D)$

 

Application of volt-second balance to inductor voltage waveform:


$$\langle v_L \rangle = D (V_g) + D' (V_g - V/n) = 0$$

Solve for  $M(D)$ :

$$M(D) = \frac{V}{V_g} = \frac{n}{D'}$$


—boost with turns ratio  $n$

# Push-pull boost-derived converter

 


$$M(D) = \frac{V}{V_g} = \frac{n}{D'}$$
 
## Push-pull converter based on Watkins-Johnson converter




### 6.3.6. Isolated versions of the SEPIC and Cuk converter


*Basic nonisolated SEPIC*

 


*Isolated SEPIC*

 

# Isolated SEPIC

 

 
$$M(D) = \frac{V}{V_g} = \frac{n D}{D'}$$






# Inverse SEPIC

*Nonisolated inverse SEPIC*

 


*Isolated inverse SEPIC*

 


# Obtaining isolation in the Cuk converter

*Nonisolated Cuk converter*

 

 
*Split capacitor  $C_1$  into series capacitors  $C_{1a}$  and  $C_{1b}$*


 
# Isolated Cuk converter

Insert transformer  
between capacitors  
 $C_{1a}$  and  $C_{1b}$

$$M(D) = \frac{V}{V_g} = \frac{n D}{D'}$$



## Discussion

- Capacitors  $C_{1a}$  and  $C_{1b}$  ensure that no dc voltage is applied to transformer primary or secondary windings
- Transformer functions in conventional manner, with small magnetizing current and negligible energy storage within the magnetizing inductance

## 6.4. Converter evaluation and design

---

For a given application, which converter topology is best?

There is no ultimate converter, perfectly suited for all possible applications

Trade studies

- Rough designs of several converter topologies to meet the given specifications
- An unbiased quantitative comparison of worst-case transistor currents and voltages, transformer size, etc.

Comparison via switch stress, switch utilization, and semiconductor cost

Spreadsheet design

## 6.4.1. Switch stress and switch utilization

---

- Largest single cost in a converter is usually the cost of the active semiconductor devices
- Conduction and switching losses associated with the active semiconductor devices often dominate the other sources of loss

This suggests evaluating candidate converter approaches by comparing the voltage and current stresses imposed on the active semiconductor devices.

Minimization of total switch stresses leads to reduced loss, and to minimization of the total silicon area required to realize the power devices of the converter.

# Total active switch stress $S$

---

In a converter having  $k$  active semiconductor devices, the total active switch stress  $S$  is defined as

$$S = \sum_{j=1}^k V_j I_j$$

where

$V_j$  is the peak voltage applied to switch  $j$ ,

$I_j$  is the rms current applied to switch  $j$  (peak current is also sometimes used).

In a good design, the total active switch stress is minimized.

# Active switch utilization $U$

---

It is desired to minimize the total active switch stress, while maximizing the output power  $P_{load}$ .

The active switch utilization  $U$  is defined as

$$U = \frac{P_{load}}{S}$$

The active switch utilization is the converter output power obtained per unit of active switch stress. It is a converter figure-of-merit, which measures how well a converter utilizes its semiconductor devices.

Active switch utilization is less than 1 in transformer-isolated converters, and is a quantity to be maximized.

Converters having low switch utilizations require extra active silicon area, and operate with relatively low efficiency.

Active switch utilization is a function of converter operating point.

# CCM flyback example: Determination of $S$

During subinterval 2, the transistor blocks voltage  $V_{Q1,pk}$  equal to  $V_g$  plus the reflected load voltage:



$$V_{Q1,pk} = V_g + V / n = \frac{V_g}{D'}$$

Transistor current coincides with  $i_g(t)$ . RMS value is

$$I_{Q1,rms} = I \sqrt{D} = \frac{P_{load}}{V_g \sqrt{D}}$$

Switch stress  $S$  is
  
$$S = V_{Q1,pk} I_{Q1,rms} = (V_g + V / n) (I \sqrt{D})$$





# CCM flyback example: Determination of $U$

Express load power  $P_{load}$  in terms of  $V$  and  $I$ :


$$P_{load} = D' V \frac{I}{n}$$

Previously-derived expression for  $S$ :

$$S = V_{Q1,pk} I_{Q1,rms} = (V_g + V / n) (I \sqrt{D})$$

Hence switch utilization  $U$  is

$$U = \frac{P_{load}}{S} = D' \sqrt{D}$$

 

## Flyback example: switch utilization $U(D)$


For given  $V$ ,  $V_g$ ,  $P_{load}$ , the designer can arbitrarily choose  $D$ . The turns ratio  $n$  must then be chosen according to

$$n = \frac{V}{V_g} \frac{D'}{D}$$

Single operating point design: choose  $D = 1/3$ .

small  $D$  leads to large transistor current

 large  $D$  leads to large transistor voltage



# Comparison of switch utilizations of some common converters

*Table 6.1. Active switch utilizations of some common dc-dc converters, single operating point.*

<i>Converter</i>	$U(D)$	$\max U(D)$	$\max U(D)$ <i>occurs at</i> $D =$
Buck	$\sqrt{D}$	1	1
Boost	$\frac{D'}{\sqrt{D}}$	$\infty$	0
Buck-boost, flyback, nonisolated SEPIC, isolated SEPIC, nonisolated Cuk, isolated Cuk	$D'\sqrt{D}$	$\frac{2}{3\sqrt{3}} = 0.385$	$\frac{1}{3}$
Forward, $n_1 = n_2$	$\frac{1}{2}\sqrt{D}$	$\frac{1}{2\sqrt{2}} = 0.353$	$\frac{1}{2}$
Other isolated buck-derived converters (full-bridge, half-bridge, push-pull)	$\frac{\sqrt{D}}{2\sqrt{2}}$	$\frac{1}{2\sqrt{2}} = 0.353$	1
Isolated boost-derived converters (full bridge, push-pull)	$\frac{D'}{2\sqrt{1+D}}$	$\frac{1}{2}$	0

# Switch utilization : Discussion

---

- Increasing the range of operating points leads to reduced switch utilization
- Buck converter
  - can operate with high switch utilization ( $U$  approaching 1) when  $D$  is close to 1
- Boost converter
  - can operate with high switch utilization ( $U$  approaching  $\infty$ ) when  $D$  is close to 1
- Transformer isolation leads to reduced switch utilization
- Buck-derived transformer-isolated converters
  - $U \leq 0.353$
  - should be designed to operate with  $D$  as large as other considerations allow
  - transformer turns ratio can be chosen to optimize design

# Switch utilization: Discussion

---

- Nonisolated and isolated versions of buck-boost, SEPIC, and Cuk converters

$$U \leq 0.385$$

Single-operating-point optimum occurs at  $D = 1/3$

Nonisolated converters have lower switch utilizations than buck or boost

Isolation can be obtained without penalizing switch utilization

# Active semiconductor cost vs. switch utilization

---

$$\left( \begin{array}{c} \text{semiconductor cost} \\ \text{per kW output power} \end{array} \right) = \frac{\left( \begin{array}{c} \text{semiconductor device cost} \\ \text{per rated kVA} \end{array} \right)}{\left( \begin{array}{c} \text{voltage} \\ \text{derating} \\ \text{factor} \end{array} \right) \left( \begin{array}{c} \text{current} \\ \text{derating} \\ \text{factor} \end{array} \right) \left( \begin{array}{c} \text{converter} \\ \text{switch} \\ \text{utilization} \end{array} \right)}$$

(semiconductor device cost per rated kVA) = cost of device, divided by product of rated blocking voltage and rms current, in \$/kVA. Typical values are less than \$1/kVA

(voltage derating factor) and (current derating factor) are required to obtain reliable operation. Typical derating factors are 0.5 - 0.75

Typical cost of active semiconductor devices in an isolated dc-dc converter: \$1 - \$10 per kW of output power.

## 6.4.2. Converter design using computer spreadsheet

---

Given ranges of  $V_g$  and  $P_{load}$ , as well as desired value of  $V$  and other quantities such as switching frequency, ripple, etc., there are two basic engineering design tasks:

- Compare converter topologies and select the best for the given specifications
- Optimize the design of a given converter

A computer spreadsheet is a very useful tool for this job. The results of the steady-state converter analyses of chapters 1-6 can be entered, and detailed design investigations can be quickly performed:

- Evaluation of worst-case stresses over a range of operating points
- Evaluation of design tradeoffs

# Spreadsheet design example

---

---

## *Specifications*

maximum input voltage $V_g$	390V
minimum input voltage $V_g$	260V
output voltage $V$	15V
maximum load power $P_{load}$	200W
minimum load power $P_{load}$	20W
switching frequency $f_s$	100kHz
maximum output ripple $\Delta v$	0.1V

---


- Input voltage: rectified 230Vrms  $\pm 20\%$
- Regulated output of 15V
- Rated load power 200W
- Must operate at 10% load
- Select switching frequency of 100kHz
- Output voltage ripple  $\leq 0.1V$

Compare single-transistor forward and flyback converters in this application

Specifications are entered at top of spreadsheet



# Forward converter design, CCM

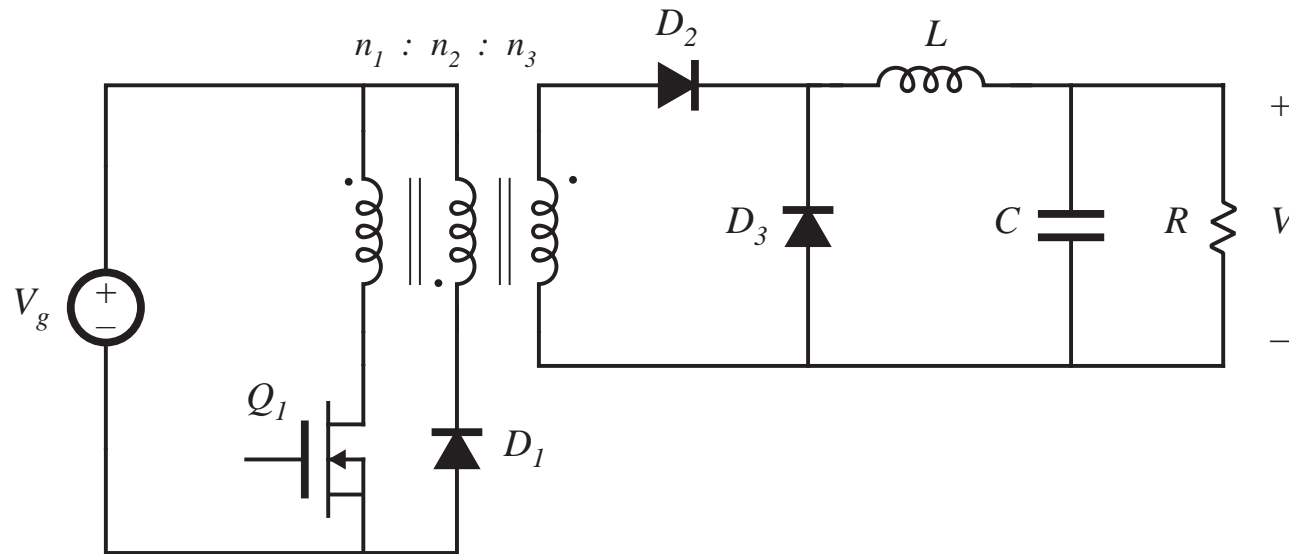


## Design variables

reset winding turns ratio $n_2 / n_1$	1
turns ratio $n_3 / n_1$	0.125
inductor current ripple $\Delta i$	2A ref to sec

- Design for CCM at full load; may operate in DCM at light load

# Flyback converter design, CCM

 

## *Design variables*

turns ratio  $n_2 / n_1$

0.125

inductor current ripple  $\Delta i$

3A ref to sec

- Design for CCM at full load; may operate in DCM at light load

## Enter results of converter analysis into spreadsheet (Forward converter example)

---

Maximum duty cycle occurs at minimum  $V_g$  and maximum  $P_{load}$ .  
Converter then operates in CCM, with

$$D = \frac{n_1}{n_3} \frac{V}{V_g}$$

Inductor current ripple is

$$\Delta i = \frac{D' V T_s}{2 L}$$

Solve for  $L$ :

$$L = \frac{D' V T_s}{2 \Delta i}$$

$\Delta i$  is a design variable. For a given  $\Delta i$ , the equation above can be used to determine  $L$ . To ensure CCM operation at full load,  $\Delta i$  should be less than the full-load output current.  $C$  can be found in a similar manner.

## Forward converter example, continued

---

Check for DCM at light load. The solution of the buck converter operating in DCM is

$$V = \frac{n_3}{n_1} V_g \frac{2}{\sqrt{1 + 4K / D^2}}$$

$$\text{with } K = 2 L / R T_s, \text{ and } R = V^2 / P_{load}$$

These equations apply equally well to the forward converter, provided that all quantities are referred to the transformer secondary side.

Solve for  $D$ :

$$D = \frac{2\sqrt{K}}{\sqrt{\left(\frac{2n_3 V_g}{n_1 V} - 1\right)^2 - 1}} \quad \text{in DCM} \qquad D = \frac{n_1}{n_3} \frac{V}{V_g} \quad \text{in CCM}$$

at a given operating point, the actual duty cycle is the small of the values calculated by the CCM and DCM equations above. Minimum  $D$  occurs at minimum  $P_{load}$  and maximum  $V_g$ .

## More regarding forward converter example

---

Worst-case component stresses can now be evaluated.

Peak transistor voltage is

$$\max v_{Q1} = V_g \left( 1 + \frac{n_1}{n_2} \right)$$

Rms transistor current is

$$I_{Q1, rms} = \frac{n_3}{n_1} \sqrt{D} \sqrt{I^2 + (\Delta i)^2 / 3} \approx \frac{n_3}{n_1} \sqrt{D} I$$

(this neglects transformer magnetizing current)

Other component stresses can be found in a similar manner.  
Magnetics design is left for a later chapter.

# Results: forward and flyback converter spreadsheets

## *Forward converter design, CCM*

### *Design variables*

reset winding turns ratio $n_2 / n_1$	1
turns ratio $n_3 / n_1$	0.125
inductor current ripple $\Delta i$	2A ref to sec

### *Results*

maximum duty cycle $D$	0.462
minimum $D$ , at full load	0.308
minimum $D$ , at minimum load	0.251

### *Worst-case stresses*

peak transistor voltage $v_{Q1}$	780V
rms transistor current $i_{Q1}$	1.13A
transistor utilization $U$	0.226
peak diode voltage $v_{D1}$	49V
rms diode current $i_{D1}$	9.1A
peak diode voltage $v_{D2}$	49V
rms diode current $i_{D2}$	11.1A
rms output capacitor current $i_C$	1.15A

## *Flyback converter design, CCM*

### *Design variables*

turns ratio $n_2 / n_1$	0.125
inductor current ripple $\Delta i$	3A ref to sec

### *Results*

maximum duty cycle $D$	0.316
minimum $D$ , at full load	0.235
minimum $D$ , at minimum load	0.179

### *Worst-case stresses*

peak transistor voltage $v_{Q1}$	510V
rms transistor current $i_{Q1}$	1.38A
transistor utilization $U$	0.284
peak diode voltage $v_{D1}$	64V
rms diode current $i_{D1}$	16.3A
peak diode current $i_{D1}$	22.2A
rms output capacitor current $i_C$	9.1A

# Discussion: transistor voltage

---

## *Flyback converter*

Ideal peak transistor voltage: 510V

Actual peak voltage will be higher, due to ringing caused by transformer leakage inductance

An 800V or 1000V MOSFET would have an adequate design margin

## *Forward converter*

Ideal peak transistor voltage: 780V, 53% greater than flyback

MOSFETs having voltage rating greater than 1000V are not available (in 1995) —when ringing due to transformer leakage inductance is accounted for, this design will have an inadequate design margin

Fix: use two-transistor forward converter, or change reset winding turns ratio

A conclusion: reset mechanism of flyback is superior to forward

# Discussion: rms transistor current

---

## *Forward*

1.13A worst-case

transistor utilization 0.226

## *Flyback*

1.38A worst case, 22% higher than forward

transistor utilization 0.284

CCM flyback exhibits higher peak and rms currents. Currents in DCM flyback are even higher



## Discussion: secondary-side diode and capacitor stresses

---

### *Forward*

peak diode voltage 49V

rms diode current 9.1A / 11.1A

rms capacitor current 1.15A

### *Flyback*

peak diode voltage 64V

rms diode current 16.3A

peak diode current 22.2A

rms capacitor current 9.1A

Secondary-side currents, especially capacitor currents, limit the practical application of the flyback converter to situations where the load current is not too great.

# Summary of key points

---

1. The boost converter can be viewed as an inverse buck converter, while the buck-boost and Cuk converters arise from cascade connections of buck and boost converters. The properties of these converters are consistent with their origins. Ac outputs can be obtained by differential connection of the load. An infinite number of converters are possible, and several are listed in this chapter.
2. For understanding the operation of most converters containing transformers, the transformer can be modeled as a magnetizing inductance in parallel with an ideal transformer. The magnetizing inductance must obey all of the usual rules for inductors, including the principle of volt-second balance.

# Summary of key points

---

3. The steady-state behavior of transformer-isolated converters may be understood by first replacing the transformer with the magnetizing-inductance-plus-ideal-transformer equivalent circuit. The techniques developed in the previous chapters can then be applied, including use of inductor volt-second balance and capacitor charge balance to find dc currents and voltages, use of equivalent circuits to model losses and efficiency, and analysis of the discontinuous conduction mode.
4. In the full-bridge, half-bridge, and push-pull isolated versions of the buck and/or boost converters, the transformer frequency is twice the output ripple frequency. The transformer is reset while it transfers energy: the applied voltage polarity alternates on successive switching periods.

# Summary of key points

---

5. In the conventional forward converter, the transformer is reset while the transistor is off. The transformer magnetizing inductance operates in the discontinuous conduction mode, and the maximum duty cycle is limited.
6. The flyback converter is based on the buck-boost converter. The flyback transformer is actually a two-winding inductor, which stores and transfers energy.
7. The transformer turns ratio is an extra degree-of-freedom which the designer can choose to optimize the converter design. Use of a computer spreadsheet is an effective way to determine how the choice of turns ratio affects the component voltage and current stresses.
8. Total active switch stress, and active switch utilization, are two simplified figures-of-merit which can be used to compare the various converter circuits.

# Part II

## Converter Dynamics and Control

---

7. AC equivalent circuit modeling
8. Converter transfer functions
9. Controller design
10. Ac and dc equivalent circuit modeling of the discontinuous conduction mode
11. Current programmed control

# Chapter 7. AC Equivalent Circuit Modeling

---

- 7.1. Introduction
- 7.2. The basic ac modeling approach
- 7.3. Example: A nonideal flyback converter
- 7.4. State-space averaging
- 7.5. Circuit averaging and averaged switch modeling
- 7.6. The canonical circuit model
- 7.7. Modeling the pulse-width modulator
- 7.8. Summary of key points

## 7.1. Introduction

Objective: maintain  $v(t)$  equal to an accurate, constant value  $V$ .


There are disturbances:

- in  $v_g(t)$
- in  $R$

There are uncertainties:

- in element values
- in  $V_g$
- in  $R$

 *A simple dc-dc regulator system, employing a buck converter*



# Applications of control in power electronics

---

## *Dc-dc converters*

Regulate dc output voltage.

Control the duty cycle  $d(t)$  such that  $v(t)$  accurately follows a reference signal  $v_{ref}$ .

## *Dc-ac inverters*

Regulate an ac output voltage.

Control the duty cycle  $d(t)$  such that  $v(t)$  accurately follows a reference signal  $v_{ref}(t)$ .

## *Ac-dc rectifiers*

Regulate the dc output voltage.

Regulate the ac input current waveform.

Control the duty cycle  $d(t)$  such that  $i_g(t)$  accurately follows a reference signal  $i_{ref}(t)$ , and  $v(t)$  accurately follows a reference signal  $v_{ref}$ .



# Objective of Part II

---

Develop tools for modeling, analysis, and design of converter control systems

Need dynamic models of converters:

How do ac variations in  $v_g(t)$ ,  $R$ , or  $d(t)$  affect the output voltage  $v(t)$ ?

What are the small-signal transfer functions of the converter?

- Extend the steady-state converter models of Chapters 2 and 3, to include CCM converter dynamics (Chapter 7)
- Construct converter small-signal transfer functions (Chapter 8)
- Design converter control systems (Chapter 9)
- Model converters operating in DCM (Chapter 10)
- Current-programmed control of converters (Chapter 11)

# Modeling

---

- Representation of physical behavior by mathematical means
- Model dominant behavior of system, ignore other insignificant phenomena
- Simplified model yields physical insight, allowing engineer to design system to operate in specified manner
- Approximations neglect small but complicating phenomena
- After basic insight has been gained, model can be refined (if it is judged worthwhile to expend the engineering effort to do so), to account for some of the previously neglected phenomena


# Neglecting the switching ripple

Suppose the duty cycle is modulated sinusoidally:


$$d(t) = D + D_m \cos \omega_m t$$

where  $D$  and  $D_m$  are constants,  $|D_m| \ll D$ , and the modulation frequency  $\omega_m$  is much smaller than the converter switching frequency  $\omega_s = 2\pi f_s$ .

 The resulting variations in transistor gate drive signal and converter output voltage:


 
# Output voltage spectrum with sinusoidal modulation of duty cycle



Contains frequency components at:

- Modulation frequency and its harmonics
- Switching frequency and its harmonics
- Sidebands of switching frequency

With small switching ripple, high-frequency components (switching harmonics and sidebands) are small.

If ripple is neglected, then only low-frequency components (modulation frequency and harmonics) remain.

# Objective of ac converter modeling

---

- Predict how low-frequency variations in duty cycle induce low-frequency variations in the converter voltages and currents
- Ignore the switching ripple
- Ignore complicated switching harmonics and sidebands

Approach:

- Remove switching harmonics by averaging all waveforms over one switching period

# Averaging to remove switching ripple

---

Average over one switching period to remove switching ripple:

$$L \frac{d\langle i_L(t) \rangle_{T_s}}{dt} = \langle v_L(t) \rangle_{T_s}$$

$$C \frac{d\langle v_C(t) \rangle_{T_s}}{dt} = \langle i_C(t) \rangle_{T_s}$$

where

$$\langle x_L(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} x(\tau) d\tau$$

Note that, in steady-state,

$$\langle v_L(t) \rangle_{T_s} = 0$$

$$\langle i_C(t) \rangle_{T_s} = 0$$

by inductor volt-second balance and capacitor charge balance.

# Nonlinear averaged equations

---

The averaged voltages and currents are, in general, nonlinear functions of the converter duty cycle, voltages, and currents. Hence, the averaged equations


$$L \frac{d\langle i_L(t) \rangle_{T_s}}{dt} = \langle v_L(t) \rangle_{T_s}$$
$$C \frac{d\langle v_C(t) \rangle_{T_s}}{dt} = \langle i_C(t) \rangle_{T_s}$$

constitute a system of nonlinear differential equations.


Hence, must linearize by constructing a small-signal converter model.

# Small-signal modeling of the BJT

Nonlinear Ebers-Moll model

 


 Linearized small-signal model, active region




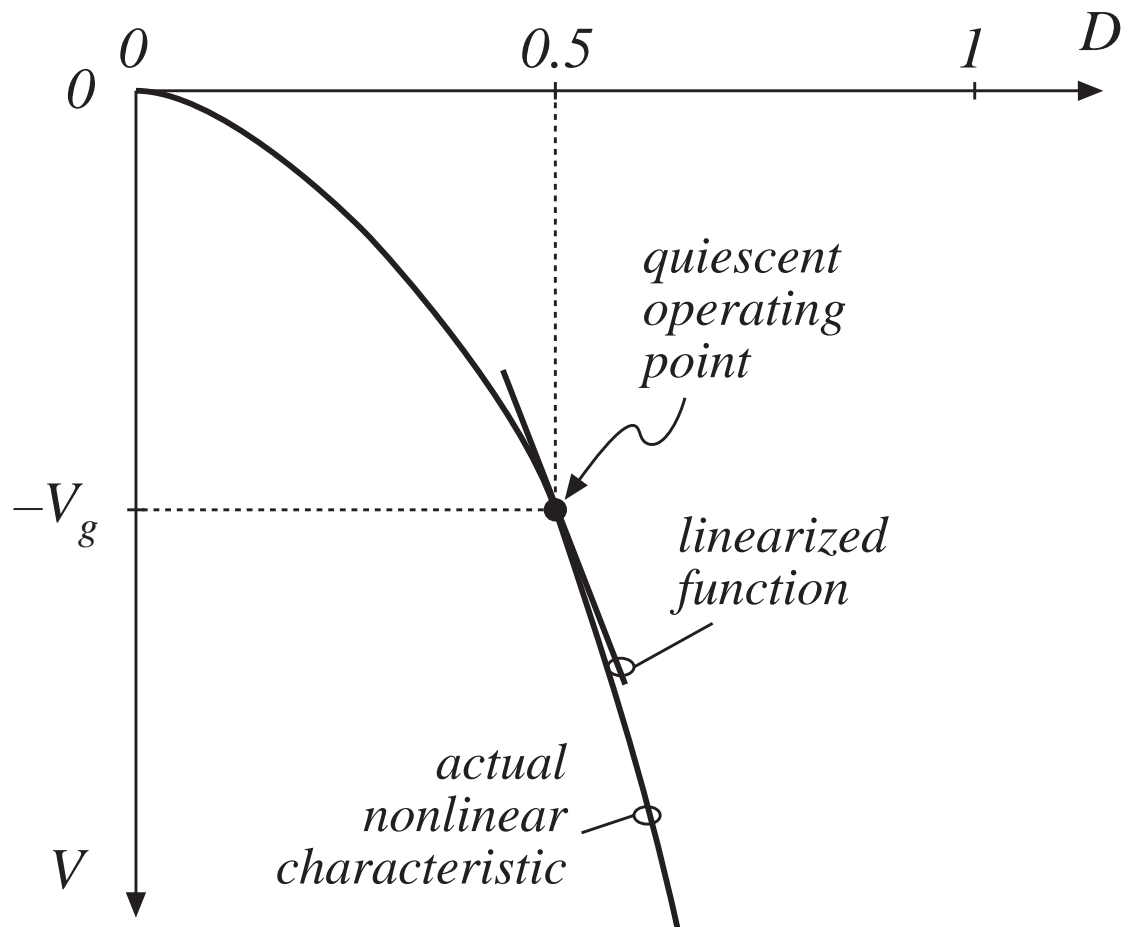
# Buck-boost converter: nonlinear static control-to-output characteristic




Example: linearization  
at the quiescent  
operating point

$$D = 0.5$$

# Result of averaged small-signal ac modeling

Small-signal ac equivalent circuit model

 


*buck-boost example*

## 7.2. The basic ac modeling approach

---

*Buck-boost converter example*

 


# Switch in position 1

Inductor voltage and capacitor current are:

$$v_L(t) = L \frac{di(t)}{dt} = v_g(t)$$
 
$$i_C(t) = C \frac{dv(t)}{dt} = -\frac{v(t)}{R}$$



Small ripple approximation: replace waveforms with their low-frequency averaged values:

$$v_L(t) = L \frac{di(t)}{dt} \approx \left\langle v_g(t) \right\rangle_{T_s}$$


$$i_C(t) = C \frac{dv(t)}{dt} \approx -\frac{\left\langle v(t) \right\rangle_{T_s}}{R}$$

## Switch in position 2

Inductor voltage and capacitor current are:

$$v_L(t) = L \frac{di(t)}{dt} = v(t)$$
 
$$i_C(t) = C \frac{dv(t)}{dt} = -i(t) - \frac{v(t)}{R}$$



Small ripple approximation: replace waveforms with their low-frequency averaged values:

$$v_L(t) = L \frac{di(t)}{dt} \approx \langle v(t) \rangle_{T_s}$$

$$i_C(t) = C \frac{dv(t)}{dt} \approx -\langle i(t) \rangle_{T_s} - \frac{\langle v(t) \rangle_{T_s}}{R}$$

## 7.2.1 Averaging the inductor waveforms

### Inductor voltage waveform

Low-frequency average is found by evaluation of


$$\langle x_L(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} x(\tau) d\tau$$

Average the inductor voltage in this manner:

$$\langle v_L(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} v_L(\tau) d\tau \approx d(t) \langle v_g(t) \rangle_{T_s} + d'(t) \langle v(t) \rangle_{T_s}$$

Insert into Eq. (7.2):
 
$$L \frac{d\langle i(t) \rangle_{T_s}}{dt} = d(t) \langle v_g(t) \rangle_{T_s} + d'(t) \langle v(t) \rangle_{T_s}$$




*This equation describes how the low-frequency components of the inductor waveforms evolve in time.*

## 7.2.2 Discussion of the averaging approximation

Use of the average inductor voltage allows us to determine the net change in inductor current over one switching period, while neglecting the switching ripple.

In steady-state, the average inductor voltage is zero (volt-second balance), and hence the inductor current waveform is periodic:  $i(t + T_s) = i(t)$ . There is no net change in inductor current over one switching period.

 During transients or ac variations, the average inductor voltage is not zero in general, and this leads to net variations in inductor current.



# Net change in inductor current is correctly predicted by the average inductor voltage

---

Inductor equation:

$$L \frac{di(t)}{dt} = v_L(t)$$

Divide by  $L$  and integrate over one switching period:

$$\int_t^{t+T_s} di = \frac{1}{L} \int_t^{t+T_s} v_L(\tau) d\tau$$


Left-hand side is the change in inductor current. Right-hand side can be related to average inductor voltage by multiplying and dividing by  $T_s$  as follows:

$$i(t + T_s) - i(t) = \frac{1}{L} T_s \langle v_L(t) \rangle_{T_s}$$

So the net change in inductor current over one switching period is exactly equal to the period  $T_s$  multiplied by the average slope  $\langle v_L \rangle_{T_s} / L$ .


 
# Average inductor voltage correctly predicts average slope of $i_L(t)$



The net change in inductor current over one switching period is exactly equal to the period  $T_s$  multiplied by the average slope  $\langle v_L \rangle_{T_s} / L$ .

$$\frac{d\langle i(t) \rangle_{T_s}}{dt}$$


---

We have

$$i(t + T_s) - i(t) = \frac{1}{L} T_s \langle v_L(t) \rangle_{T_s}$$

Rearrange:

$$L \frac{i(t + T_s) - i(t)}{T_s} = \langle v_L(t) \rangle_{T_s}$$

Define the derivative of  $\langle i \rangle_{T_s}$  as (Euler formula):


$$\frac{d\langle i(t) \rangle_{T_s}}{dt} = \frac{i(t + T_s) - i(t)}{T_s}$$

Hence,

$$L \frac{d\langle i(t) \rangle_{T_s}}{dt} = \langle v_L(t) \rangle_{T_s}$$
 
# Computing how the inductor current changes over one switching period

Let's compute the actual inductor current waveform, using the linear ripple approximation.



With switch in position 1:

$$\underbrace{i(dT_s)}_{\text{(final value)}} = \underbrace{i(0)}_{\text{(initial value)}} + \underbrace{(dT_s)}_{\text{(length of interval)}} \underbrace{\left( \frac{\langle v_g(t) \rangle_{T_s}}{L} \right)}_{\text{(average slope)}}$$

With switch in position 2:

$$\underbrace{i(T_s)}_{\text{(final value)}} = \underbrace{i(dT_s)}_{\text{(initial value)}} + \underbrace{(dT_s)}_{\text{(length of interval)}} \underbrace{\left( \frac{\langle v(t) \rangle_{T_s}}{L} \right)}_{\text{(average slope)}}$$


# Net change in inductor current over one switching period

Eliminate  $i(dT_s)$ , to express  $i(T_s)$  directly as a function of  $i(0)$ :

$$i(T_s) = i(0) + \underbrace{\frac{T_s}{L} \left( d(t) \langle v_g(t) \rangle_{T_s} + d'(t) \langle v(t) \rangle_{T_s} \right)}_{\langle v_L(t) \rangle_{T_s}}$$

The intermediate step of computing  $i(dT_s)$  is eliminated.

 The final value  $i(T_s)$  is equal to the initial value  $i(0)$ , plus the switching period  $T_s$  multiplied by the average slope  $\langle v_L \rangle_{T_s} / L$ .




## 7.2.3 Averaging the capacitor waveforms

Average capacitor current:

$$\langle i_C(t) \rangle_{T_s} = d(t) \left( -\frac{\langle v(t) \rangle_{T_s}}{R} \right) + d'(t) \left( -\langle i(t) \rangle_{T_s} - \frac{\langle v(t) \rangle_{T_s}}{R} \right)$$

Collect terms, and equate to  $C d\langle v \rangle_{T_s} / dt$ :
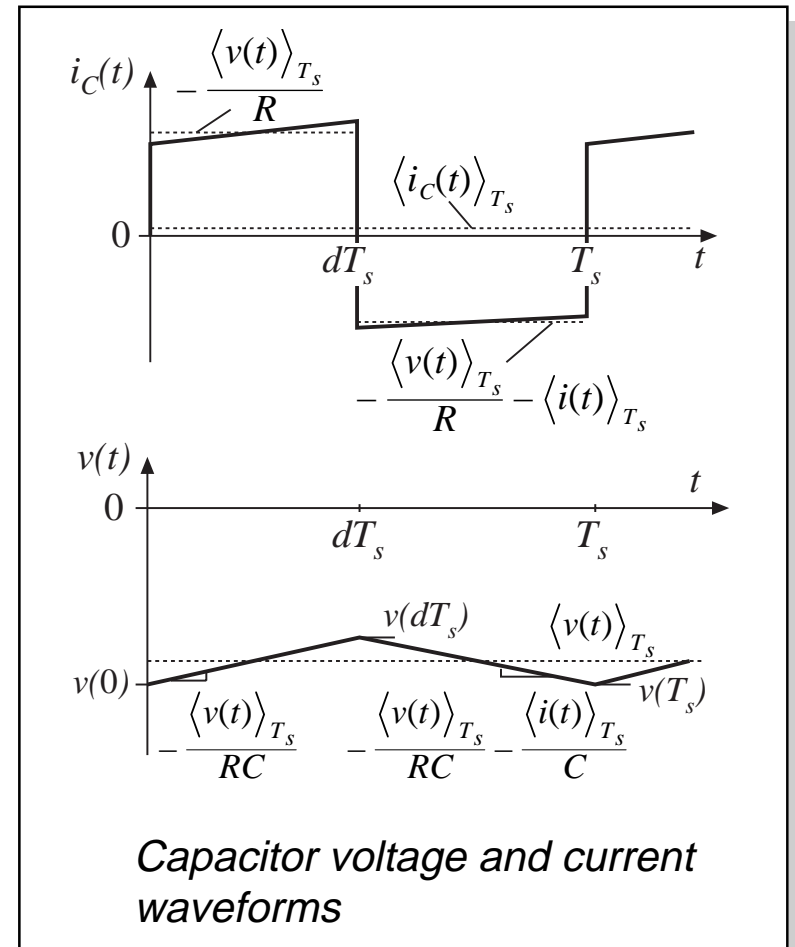
$$C \frac{d\langle v(t) \rangle_{T_s}}{dt} = -d'(t) \langle i(t) \rangle_{T_s} - \frac{\langle v(t) \rangle_{T_s}}{R}$$



## 7.2.4 The average input current


We found in Chapter 3 that it was sometimes necessary to write an equation for the average converter input current, to derive a complete dc equivalent circuit model. It is likewise necessary to do this for the ac model.

Buck-boost input current waveform is

$$i_g(t) = \begin{cases} \langle i(t) \rangle_{T_s} & \text{during subinterval 1} \\ 0 & \text{during subinterval 2} \end{cases}$$

Average value:
 
$$\langle i_g(t) \rangle_{T_s} = d(t) \langle i(t) \rangle_{T_s}$$



## 7.2.5. Perturbation and linearization

---

Converter averaged equations:

$$\begin{aligned}L \frac{d\langle i(t) \rangle_{T_s}}{dt} &= d(t) \langle v_g(t) \rangle_{T_s} + d'(t) \langle v(t) \rangle_{T_s} \\C \frac{d\langle v(t) \rangle_{T_s}}{dt} &= -d'(t) \langle i(t) \rangle_{T_s} - \frac{\langle v(t) \rangle_{T_s}}{R} \\ \langle i_g(t) \rangle_{T_s} &= d(t) \langle i(t) \rangle_{T_s}\end{aligned}$$

—nonlinear because of multiplication of the time-varying quantity  $d(t)$  with other time-varying quantities such as  $i(t)$  and  $v(t)$ .

## Construct small-signal model: Linearize about quiescent operating point

---

If the converter is driven with some steady-state, or quiescent, inputs

$$d(t) = D$$
$$\langle v_g(t) \rangle_{T_s} = V_g$$

then, from the analysis of Chapter 2, after transients have subsided the inductor current, capacitor voltage, and input current

$$\langle i(t) \rangle_{T_s}, \langle v(t) \rangle_{T_s}, \langle i_g(t) \rangle_{T_s}$$

reach the quiescent values  $I$ ,  $V$ , and  $I_g$ , given by the steady-state analysis as

$$V = -\frac{D}{D'} V_g$$
$$I = -\frac{V}{D' R}$$
$$I_g = D I$$



# Perturbation

---

So let us assume that the input voltage and duty cycle are equal to some given (dc) quiescent values, plus superimposed small ac variations:

$$\begin{aligned}\langle v_g(t) \rangle_{T_s} &= V_g + \hat{v}_g(t) \\ d(t) &= D + \hat{d}(t)\end{aligned}$$

In response, and after any transients have subsided, the converter dependent voltages and currents will be equal to the corresponding quiescent values, plus small ac variations:

$$\begin{aligned}\langle i(t) \rangle_{T_s} &= I + \hat{i}(t) \\ \langle v(t) \rangle_{T_s} &= V + \hat{v}(t) \\ \langle i_g(t) \rangle_{T_s} &= I_g + \hat{i}_g(t)\end{aligned}$$

# The small-signal assumption

---

If the ac variations are much smaller in magnitude than the respective quiescent values,

$$|\hat{v}_g(t)| \ll |V_g|$$

$$|\hat{d}(t)| \ll |D|$$

$$|\hat{i}(t)| \ll |I|$$

$$|\hat{v}(t)| \ll |V|$$

$$|\hat{i}_g(t)| \ll |I_g|$$

then the nonlinear converter equations can be linearized.

# Perturbation of inductor equation

Insert the perturbed expressions into the inductor differential equation:

$$L \frac{d(I + \hat{i}(t))}{dt} = (D + \hat{d}(t)) (V_g + \hat{v}_g(t)) + (D' - \hat{d}(t)) (V + \hat{v}(t))$$

note that  $d'(t)$  is given by

$$d'(t) = (1 - d(t)) = 1 - (D + \hat{d}(t)) = D' - \hat{d}(t) \quad \text{with } D' = 1 - D$$

Multiply out and collect terms:

$$L \left( \frac{dI}{dt} + \frac{d\hat{i}(t)}{dt} \right) = \underbrace{(DV_g + D'V)}_{\text{Dc terms}} + \underbrace{\left( D\hat{v}_g(t) + D'\hat{v}(t) + (V_g - V)\hat{d}(t) \right)}_{\substack{1^{st} \text{ order ac terms} \\ \text{(linear)}}} + \underbrace{\hat{d}(t)(\hat{v}_g(t) - \hat{v}(t))}_{\substack{2^{nd} \text{ order ac terms} \\ \text{(nonlinear)}}$$

# The perturbed inductor equation

$$L \left( \frac{dI}{dt} + \frac{d\hat{i}(t)}{dt} \right) = \underbrace{(DV_g + D'V)}_{\text{Dc terms}} + \underbrace{\left( D\hat{v}_g(t) + D'\hat{v}(t) + (V_g - V) \hat{d}(t) \right)}_{\substack{1^{st} \text{ order ac terms} \\ \text{(linear)}}} + \underbrace{\hat{d}(t) (\hat{v}_g(t) - \hat{v}(t))}_{\substack{2^{nd} \text{ order ac terms} \\ \text{(nonlinear)}}}$$

Since  $I$  is a constant (dc) term, its derivative is zero

The right-hand side contains three types of terms:

- Dc terms, containing only dc quantities
- First-order ac terms, containing a single ac quantity, usually multiplied by a constant coefficient such as a dc term. These are linear functions of the ac variations
- Second-order ac terms, containing products of ac quantities. These are nonlinear, because they involve multiplication of ac quantities

# Neglect of second-order terms

$$L \left( \frac{d\hat{i}(t)}{dt} + \frac{d\hat{i}(t)}{dt} \right) = \underbrace{(DV_g + D'V)}_{\text{Dc terms}} + \underbrace{\left( D\hat{v}_g(t) + D'\hat{v}(t) + (V_g - V) \hat{d}(t) \right)}_{\substack{1^{st} \text{ order ac terms} \\ \text{(linear)}}} + \underbrace{\hat{d}(t) (\hat{v}_g(t) - \hat{v}(t))}_{\substack{2^{nd} \text{ order ac terms} \\ \text{(nonlinear)}}}$$

Provided

$$\begin{aligned} |\hat{v}_g(t)| &\ll |V_g| \\ |\hat{d}(t)| &\ll |D| \\ |\hat{i}(t)| &\ll |I| \\ |\hat{v}(t)| &\ll |V| \\ |\hat{i}_g(t)| &\ll |I_g| \end{aligned}$$

then the second-order ac terms are much smaller than the first-order terms. For example,

$$|\hat{d}(t) \hat{v}_g(t)| \ll |D \hat{v}_g(t)| \quad \text{when} \quad |\hat{d}(t)| \ll D$$

So neglect second-order terms.

Also, dc terms on each side of equation are equal.

# Linearized inductor equation

---

Upon discarding second-order terms, and removing dc terms (which add to zero), we are left with

$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) + D'\hat{v}(t) + (V_g - V)\hat{d}(t)$$

This is the desired result: a linearized equation which describes small-signal ac variations.

Note that the quiescent values  $D$ ,  $D'$ ,  $V$ ,  $V_g$ , are treated as given constants in the equation.

# Capacitor equation

Perturbation leads to

$$C \frac{d(V + \hat{v}(t))}{dt} = - (D' - \hat{d}(t)) (I + \hat{i}(t)) - \frac{(V + \hat{v}(t))}{R}$$

Collect terms:

$$C \left( \frac{dV^0}{dt} + \frac{d\hat{v}(t)}{dt} \right) = \underbrace{\left( -D'I - \frac{V}{R} \right)}_{\text{Dc terms}} + \underbrace{\left( -D'\hat{i}(t) - \frac{\hat{v}(t)}{R} + I\hat{d}(t) \right)}_{\substack{1^{st} \text{ order ac terms} \\ \text{(linear)}}} + \underbrace{\hat{d}(t)\hat{i}(t)}_{\substack{2^{nd} \text{ order ac term} \\ \text{(nonlinear)}}$$

Neglect second-order terms. Dc terms on both sides of equation are equal. The following terms remain:

$$C \frac{d\hat{v}(t)}{dt} = -D'\hat{i}(t) - \frac{\hat{v}(t)}{R} + I\hat{d}(t)$$

This is the desired small-signal linearized capacitor equation.

# Average input current

---

Perturbation leads to

$$I_g + \hat{i}_g(t) = (D + \hat{d}(t)) (I + \hat{i}(t))$$

Collect terms:

$$\underbrace{I_g}_{Dc\ term} + \underbrace{\hat{i}_g(t)}_{1^{st}\ order\ ac\ term} = \underbrace{(DI)}_{Dc\ term} + \underbrace{(D\hat{i}(t) + I\hat{d}(t))}_{1^{st}\ order\ ac\ terms\ (linear)} + \underbrace{\hat{d}(t)\hat{i}(t)}_{2^{nd}\ order\ ac\ term\ (nonlinear)}$$

Neglect second-order terms. Dc terms on both sides of equation are equal. The following first-order terms remain:

$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$

This is the linearized small-signal equation which describes the converter input port.



## 7.2.6. Construction of small-signal equivalent circuit model

---

The linearized small-signal converter equations:

$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) + D'\hat{v}(t) + (V_g - V)\hat{d}(t)$$

$$C \frac{d\hat{v}(t)}{dt} = -D'\hat{i}(t) - \frac{\hat{v}(t)}{R} + I\hat{d}(t)$$


$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$

Reconstruct equivalent circuit corresponding to these equations, in manner similar to the process used in Chapter 3.
 
# Inductor loop equation

---


$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) + D'\hat{v}(t) + (V_g - V) \hat{d}(t)$$


 
# Capacitor node equation

---


$$C \frac{d\hat{v}(t)}{dt} = -D' \hat{i}(t) - \frac{\hat{v}(t)}{R} + I \hat{d}(t)$$


 
# Input port node equation


---

$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$




# Complete equivalent circuit

Collect the three circuits:

 

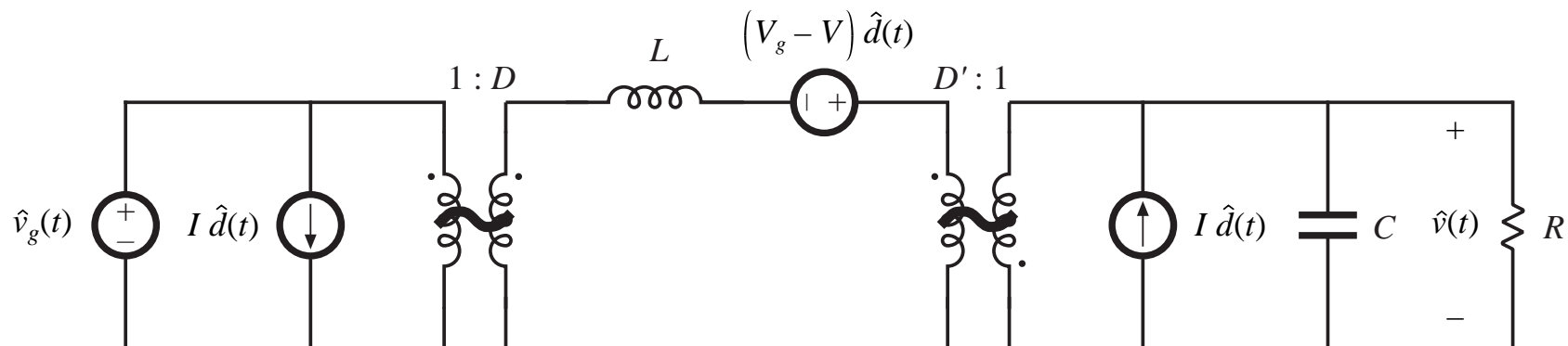
Replace dependent sources with ideal dc transformers:




Small-signal ac equivalent circuit model of the buck-boost converter

## 7.2.7. Results for several basic converters

*buck*

 


*boost*

 


# Results for several basic converters

*buck-boost*

 

## 7.3. Example: a nonideal flyback converter

*Flyback converter example*

 


- MOSFET has on-resistance  $R_{on}$
- Flyback transformer has magnetizing inductance  $L$ , referred to primary




# Circuits during subintervals 1 and 2


*Flyback converter, with transformer equivalent circuit*

 

*Subinterval 1*

 

*Subinterval 2*

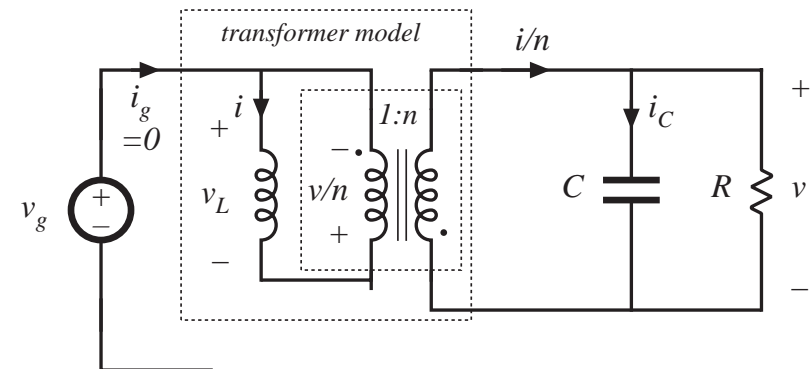

# Subinterval 1

Circuit equations:

$$v_L(t) = v_g(t) - i(t) R_{on}$$

$$i_C(t) = -\frac{v(t)}{R}$$


$$i_g(t) = i(t)$$

Small ripple approximation:

$$v_L(t) = \langle v_g(t) \rangle_{T_s} - \langle i(t) \rangle_{T_s} R_{on}$$

$$i_C(t) = -\frac{\langle v(t) \rangle_{T_s}}{R}$$

$$i_g(t) = \langle i(t) \rangle_{T_s}$$

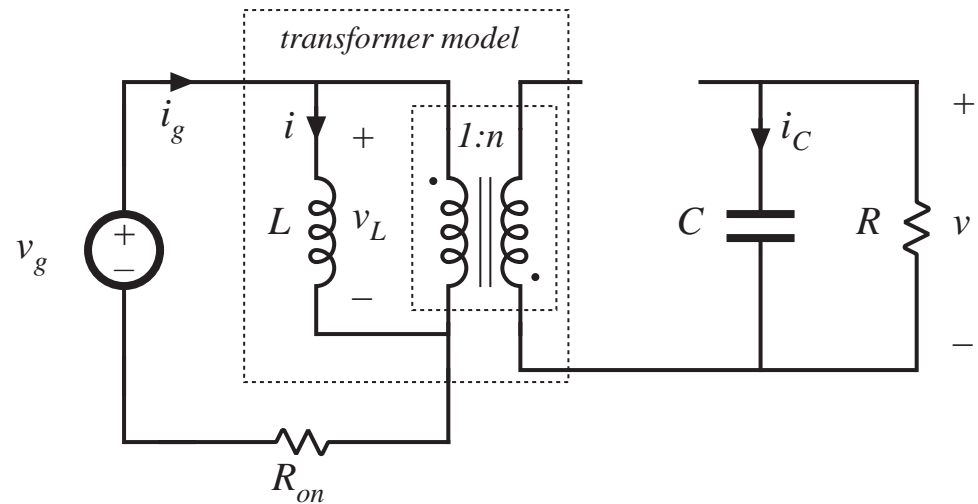

MOSFET conducts, diode is reverse-biased


## Subinterval 2

Circuit equations:

$$\begin{aligned}v_L(t) &= -\frac{v(t)}{n} \\ i_C(t) &= -\frac{i(t)}{n} - \frac{v(t)}{R} \\ i_g(t) &= 0\end{aligned}$$


Small ripple approximation:
 
$$\begin{aligned}v_L(t) &= -\frac{\langle v(t) \rangle_{T_s}}{n} \\ i_C(t) &= -\frac{\langle i(t) \rangle_{T_s}}{n} - \frac{\langle v(t) \rangle_{T_s}}{R} \\ i_g(t) &= 0\end{aligned}$$



MOSFET is off, diode conducts

# Inductor waveforms

 


Average inductor voltage:

$$\langle v_L(t) \rangle_{T_s} = d(t) \left( \langle v_g(t) \rangle_{T_s} - \langle i(t) \rangle_{T_s} R_{on} \right) + d'(t) \left( \frac{-\langle v(t) \rangle_{T_s}}{n} \right)$$

Hence, we can write:

$$L \frac{d\langle i(t) \rangle_{T_s}}{dt} = d(t) \langle v_g(t) \rangle_{T_s} - d(t) \langle i(t) \rangle_{T_s} R_{on} - d'(t) \frac{\langle v(t) \rangle_{T_s}}{n}$$

# Capacitor waveforms

 


Average capacitor current:

$$\langle i_C(t) \rangle_{T_s} = d(t) \left( -\frac{\langle v(t) \rangle_{T_s}}{R} \right) + d'(t) \left( \frac{\langle i(t) \rangle_{T_s}}{n} - \frac{\langle v(t) \rangle_{T_s}}{R} \right)$$

Hence, we can write:

$$C \frac{d\langle v(t) \rangle_{T_s}}{dt} = d'(t) \frac{\langle i(t) \rangle_{T_s}}{n} - \frac{\langle v(t) \rangle_{T_s}}{R}$$

# Input current waveform

 

Average input current:

$$\langle i_g(t) \rangle_{T_s} = d(t) \langle i(t) \rangle_{T_s}$$

# The averaged converter equations

---

$$\begin{aligned}
 L \frac{d\langle i(t) \rangle_{T_s}}{dt} &= d(t) \langle v_g(t) \rangle_{T_s} - d(t) \langle i(t) \rangle_{T_s} R_{on} - d'(t) \frac{\langle v(t) \rangle_{T_s}}{n} \\
 C \frac{d\langle v(t) \rangle_{T_s}}{dt} &= d'(t) \frac{\langle i(t) \rangle_{T_s}}{n} - \frac{\langle v(t) \rangle_{T_s}}{R} \\
 \langle i_g(t) \rangle_{T_s} &= d(t) \langle i(t) \rangle_{T_s}
 \end{aligned}$$

— a system of nonlinear differential equations

Next step: perturbation and linearization. Let

$$\begin{aligned}
 \langle v_g(t) \rangle_{T_s} &= V_g + \hat{v}_g(t) & \langle i(t) \rangle_{T_s} &= I + \hat{i}(t) \\
 d(t) &= D + \hat{d}(t) & \langle v(t) \rangle_{T_s} &= V + \hat{v}(t) \\
 & & \langle i_g(t) \rangle_{T_s} &= I_g + \hat{i}_g(t)
 \end{aligned}$$

# Perturbation of the averaged inductor equation

$$L \frac{d\langle i(t) \rangle_{T_s}}{dt} = d(t) \langle v_g(t) \rangle_{T_s} - d(t) \langle i(t) \rangle_{T_s} R_{on} - d'(t) \frac{\langle v(t) \rangle_{T_s}}{n}$$

$$L \frac{d(I + \hat{i}(t))}{dt} = (D + \hat{d}(t)) (V_g + \hat{v}_g(t)) - (D' - \hat{d}(t)) \frac{(V + \hat{v}(t))}{n} - (D + \hat{d}(t)) (I + \hat{i}(t)) R_{on}$$

$$L \left( \frac{dI}{dt} + \frac{d\hat{i}(t)}{dt} \right) = \underbrace{\left( DV_g - D' \frac{V}{n} - DR_{on}I \right)}_{Dc \text{ terms}} + \underbrace{\left( D\hat{v}_g(t) - D' \frac{\hat{v}(t)}{n} + \left( V_g + \frac{V}{n} - IR_{on} \right) \hat{d}(t) - DR_{on}\hat{i}(t) \right)}_{1^{st} \text{ order ac terms (linear)}} + \underbrace{\left( \hat{d}(t)\hat{v}_g(t) + \hat{d}(t)\frac{\hat{v}(t)}{n} - \hat{d}(t)\hat{i}(t)R_{on} \right)}_{2^{nd} \text{ order ac terms (nonlinear)}}$$



# Linearization of averaged inductor equation

---

Dc terms:

$$0 = DV_g - D'\frac{V}{n} - DR_{on}I$$

Second-order terms are small when the small-signal assumption is satisfied. The remaining first-order terms are:

$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) - D'\frac{\hat{v}(t)}{n} + \left( V_g + \frac{V}{n} - IR_{on} \right) \hat{d}(t) - DR_{on}\hat{i}(t)$$

This is the desired linearized inductor equation.

# Perturbation of averaged capacitor equation

---

Original averaged equation:

$$C \frac{d\langle v(t) \rangle_{T_s}}{dt} = d'(t) \frac{\langle i(t) \rangle_{T_s}}{n} - \frac{\langle v(t) \rangle_{T_s}}{R}$$

Perturb about quiescent operating point:

$$C \frac{d(V + \hat{v}(t))}{dt} = (D' - \hat{d}(t)) \frac{(I + \hat{i}(t))}{n} - \frac{(V + \hat{v}(t))}{R}$$

Collect terms:

$$C \left( \frac{dV}{dt} + \frac{d\hat{v}(t)}{dt} \right) = \underbrace{\left( \frac{D'I}{n} - \frac{V}{R} \right)}_{\text{Dc terms}} + \underbrace{\left( \frac{D'\hat{i}(t)}{n} - \frac{\hat{v}(t)}{R} - \frac{I\hat{d}(t)}{n} \right)}_{\substack{1^{st} \text{ order ac terms} \\ \text{(linear)}}} - \underbrace{\frac{\hat{d}(t)\hat{i}(t)}{n}}_{\substack{2^{nd} \text{ order ac term} \\ \text{(nonlinear)}}$$

# Linearization of averaged capacitor equation

---

Dc terms:

$$0 = \left( \frac{D'I}{n} - \frac{V}{R} \right)$$

Second-order terms are small when the small-signal assumption is satisfied. The remaining first-order terms are:

$$C \frac{d\hat{v}(t)}{dt} = \frac{D'\hat{i}(t)}{n} - \frac{\hat{v}(t)}{R} - \frac{I\hat{d}(t)}{n}$$

This is the desired linearized capacitor equation.

# Perturbation of averaged input current equation

---

Original averaged equation:

$$\langle i_g(t) \rangle_{T_s} = d(t) \langle i(t) \rangle_{T_s}$$

Perturb about quiescent operating point:

$$I_g + \hat{i}_g(t) = (D + \hat{d}(t)) (I + \hat{i}(t))$$

Collect terms:

$$\underbrace{I_g}_{Dc\ term} + \underbrace{\hat{i}_g(t)}_{1^{st}\ order\ ac\ term} = \underbrace{(DI)}_{Dc\ term} + \underbrace{(D\hat{i}(t) + I\hat{d}(t))}_{1^{st}\ order\ ac\ terms\ (linear)} + \underbrace{\hat{d}(t)\hat{i}(t)}_{2^{nd}\ order\ ac\ term\ (nonlinear)}$$

# Linearization of averaged input current equation

---

Dc terms:

$$I_g = DI$$

Second-order terms are small when the small-signal assumption is satisfied. The remaining first-order terms are:

$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$

This is the desired linearized input current equation.

# Summary: dc and small-signal ac converter equations

---

Dc equations:

$$0 = DV_g - D'\frac{V}{n} - DR_{on}I$$

$$0 = \left( \frac{D'I}{n} - \frac{V}{R} \right)$$

$$I_g = DI$$

Small-signal ac equations:

$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) - D'\frac{\hat{v}(t)}{n} + \left( V_g + \frac{V}{n} - IR_{on} \right) \hat{d}(t) - DR_{on}\hat{i}(t)$$


$$C \frac{d\hat{v}(t)}{dt} = \frac{D'\hat{i}(t)}{n} - \frac{\hat{v}(t)}{R} - \frac{I\hat{d}(t)}{n}$$

$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$

Next step: construct equivalent circuit models.
 
# Small-signal ac equivalent circuit: inductor loop


$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) - D'\frac{\hat{v}(t)}{n} + \left( V_g + \frac{V}{n} - IR_{on} \right) \hat{d}(t) - DR_{on}\hat{i}(t)$$


 
## Small-signal ac equivalent circuit: capacitor node

---

$$C \frac{d\hat{v}(t)}{dt} = \frac{D'\hat{i}(t)}{n} - \frac{\hat{v}(t)}{R} - \frac{I\hat{d}(t)}{n}$$





 
# Small-signal ac equivalent circuit: converter input node


---

$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$




# Small-signal ac model, nonideal flyback converter example

Combine circuits:

 

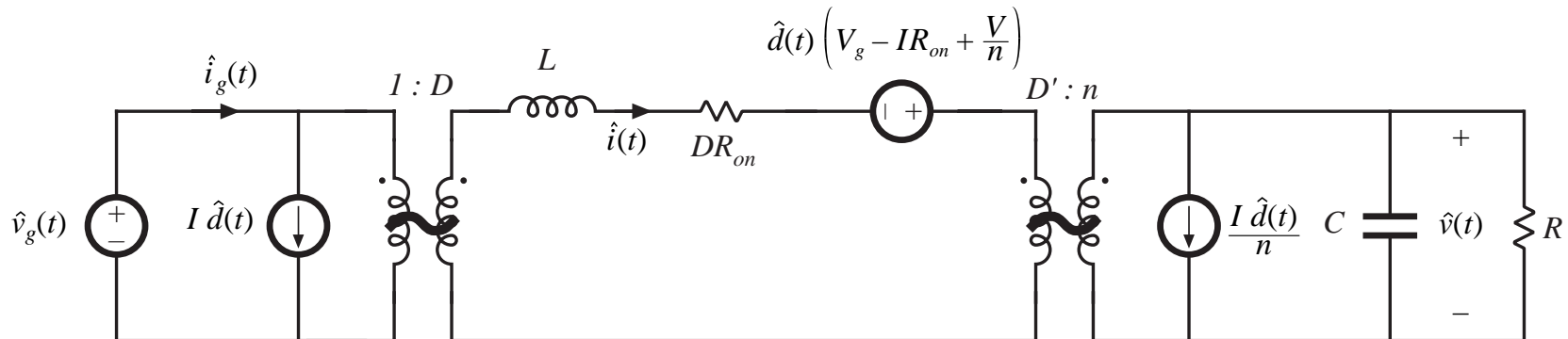Replace dependent sources with ideal transformers:



## 7.4. State Space Averaging

---

- A formal method for deriving the small-signal ac equations of a switching converter
- Equivalent to the modeling method of the previous sections
- Uses the state-space matrix description of linear circuits
- Often cited in the literature
- A general approach: if the state equations of the converter can be written for each subinterval, then the small-signal averaged model can always be derived
- Computer programs exist which utilize the state-space averaging method

## 7.4.1. The state equations of a network

---

- A canonical form for writing the differential equations of a system
- If the system is linear, then the derivatives of the *state variables* are expressed as linear combinations of the system independent inputs and state variables themselves
- The physical state variables of a system are usually associated with the storage of energy
- For a typical converter circuit, the physical state variables are the inductor currents and capacitor voltages
- Other typical physical state variables: position and velocity of a motor shaft
- At a given point in time, the values of the state variables depend on the previous history of the system, rather than the present values of the system inputs
- To solve the differential equations of a system, the initial values of the state variables must be specified

## State equations of a linear system, in matrix form

---

A canonical matrix form:  $\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A} \mathbf{x}(t) + \mathbf{B} \mathbf{u}(t)$

$$\mathbf{y}(t) = \mathbf{C} \mathbf{x}(t) + \mathbf{E} \mathbf{u}(t)$$

State vector  $\mathbf{x}(t)$  contains inductor currents, capacitor voltages, etc.:

$$\mathbf{x}(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \\ \vdots \end{bmatrix}, \quad \frac{d\mathbf{x}(t)}{dt} = \begin{bmatrix} \frac{dx_1(t)}{dt} \\ \frac{dx_2(t)}{dt} \\ \vdots \end{bmatrix}$$

Input vector  $\mathbf{u}(t)$  contains independent sources such as  $v_g(t)$


Output vector  $\mathbf{y}(t)$  contains other dependent quantities to be computed, such as  $i_g(t)$

Matrix  $\mathbf{K}$  contains values of capacitance, inductance, and mutual inductance, so that  $\mathbf{K} d\mathbf{x}/dt$  is a vector containing capacitor currents and inductor winding voltages. These quantities are expressed as linear combinations of the independent inputs and state variables. The matrices  $\mathbf{A}$ ,  $\mathbf{B}$ ,  $\mathbf{C}$ , and  $\mathbf{E}$  contain the constants of proportionality.
 
# Example

State vector

$$\mathbf{x}(t) = \begin{bmatrix} v_1(t) \\ v_2(t) \\ i(t) \end{bmatrix}$$



Matrix **K**

$$\mathbf{K} = \begin{bmatrix} C_1 & 0 & 0 \\ 0 & C_2 & 0 \\ 0 & 0 & L \end{bmatrix}$$

Input vector


$$\mathbf{u}(t) = \begin{bmatrix} i_{in}(t) \end{bmatrix}$$

Choose output vector as

$$\mathbf{y}(t) = \begin{bmatrix} v_{out}(t) \\ i_{R1}(t) \end{bmatrix}$$

To write the state equations of this circuit, we must express the inductor voltages and capacitor currents as linear combinations of the elements of the  $\mathbf{x}(t)$  and  $\mathbf{u}(t)$  vectors.

# Circuit equations

 

Find  $i_{C1}$  via node equation: 
$$i_{C1}(t) = C_1 \frac{dv_1(t)}{dt} = i_{in}(t) - \frac{v_1(t)}{R} - i(t)$$

Find  $i_{C2}$  via node equation: 
$$i_{C2}(t) = C_2 \frac{dv_2(t)}{dt} = i(t) - \frac{v_2(t)}{R_2 + R_3}$$

Find  $v_L$  via loop equation: 
$$v_L(t) = L \frac{di(t)}{dt} = v_1(t) - v_2(t)$$

# Equations in matrix form

The same equations:

$$i_{c1}(t) = C_1 \frac{dv_1(t)}{dt} = i_{in}(t) - \frac{v_1(t)}{R} - i(t)$$

$$i_{c2}(t) = C_2 \frac{dv_2(t)}{dt} = i(t) - \frac{v_2(t)}{R_2 + R_3}$$


$$v_L(t) = L \frac{di(t)}{dt} = v_1(t) - v_2(t)$$

Express in matrix form:

$$\underbrace{\begin{bmatrix} C_1 & 0 & 0 \\ 0 & C_2 & 0 \\ 0 & 0 & L \end{bmatrix}}_{\mathbf{K}} \underbrace{\begin{bmatrix} \frac{dv_1(t)}{dt} \\ \frac{dv_2(t)}{dt} \\ \frac{di(t)}{dt} \end{bmatrix}}_{\frac{d\mathbf{x}(t)}{dt}} = \underbrace{\begin{bmatrix} -\frac{1}{R_1} & 0 & -1 \\ 0 & -\frac{1}{R_2 + R_3} & 1 \\ 1 & -1 & 0 \end{bmatrix}}_{\mathbf{A}} \underbrace{\begin{bmatrix} v_1(t) \\ v_2(t) \\ i(t) \end{bmatrix}}_{\mathbf{x}(t)} + \underbrace{\begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix}}_{\mathbf{B}} \underbrace{[i_{in}(t)]}_{\mathbf{u}(t)}$$



# Output (dependent signal) equations

 

Express elements of the vector  $\mathbf{y}$  as linear combinations of elements of  $\mathbf{x}$  and  $\mathbf{u}$ :

$$v_{out}(t) = v_2(t) \frac{R_3}{R_2 + R_3}$$

$$i_{R1}(t) = \frac{v_1(t)}{R_1}$$

## Express in matrix form

---

The same equations:

$$v_{out}(t) = v_2(t) \frac{R_3}{R_2 + R_3}$$

$$i_{R1}(t) = \frac{v_1(t)}{R_1}$$

Express in matrix form:

$$\underbrace{\begin{bmatrix} v_{out}(t) \\ i_{R1}(t) \end{bmatrix}}_{\mathbf{y}(t)} = \underbrace{\begin{bmatrix} 0 & \frac{R_3}{R_2 + R_3} & 0 \\ \frac{1}{R_1} & 0 & 0 \end{bmatrix}}_{\mathbf{C}} \underbrace{\begin{bmatrix} v_1(t) \\ v_2(t) \\ i(t) \end{bmatrix}}_{\mathbf{x}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{E}} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{u}(t)}$$

## 7.4.2. The basic state-space averaged model

---

*Given:* a PWM converter, operating in continuous conduction mode, with two subintervals during each switching period.

*During subinterval 1*, when the switches are in position 1, the converter reduces to a linear circuit that can be described by the following state equations:

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_1 \mathbf{x}(t) + \mathbf{B}_1 \mathbf{u}(t)$$
$$\mathbf{y}(t) = \mathbf{C}_1 \mathbf{x}(t) + \mathbf{E}_1 \mathbf{u}(t)$$

*During subinterval 2*, when the switches are in position 2, the converter reduces to another linear circuit, that can be described by the following state equations:

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_2 \mathbf{x}(t) + \mathbf{B}_2 \mathbf{u}(t)$$
$$\mathbf{y}(t) = \mathbf{C}_2 \mathbf{x}(t) + \mathbf{E}_2 \mathbf{u}(t)$$

# Equilibrium (dc) state-space averaged model

---

Provided that the natural frequencies of the converter, as well as the frequencies of variations of the converter inputs, are much slower than the switching frequency, then the state-space averaged model that describes the converter in equilibrium is

$$\mathbf{0} = \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U}$$

$$\mathbf{Y} = \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U}$$

where the averaged matrices are

$$\mathbf{A} = D \mathbf{A}_1 + D' \mathbf{A}_2$$

$$\mathbf{B} = D \mathbf{B}_1 + D' \mathbf{B}_2$$

$$\mathbf{C} = D \mathbf{C}_1 + D' \mathbf{C}_2$$

$$\mathbf{E} = D \mathbf{E}_1 + D' \mathbf{E}_2$$

and the equilibrium dc components are

$\mathbf{X}$  = *equilibrium (dc) state vector*

$\mathbf{U}$  = *equilibrium (dc) input vector*

$\mathbf{Y}$  = *equilibrium (dc) output vector*

$D$  = *equilibrium (dc) duty cycle*

# Solution of equilibrium averaged model

---

Equilibrium state-space averaged model:

$$\mathbf{0} = \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U}$$

$$\mathbf{Y} = \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U}$$

Solution for  $\mathbf{X}$  and  $\mathbf{Y}$ :

$$\mathbf{X} = -\mathbf{A}^{-1} \mathbf{B} \mathbf{U}$$

$$\mathbf{Y} = \left( -\mathbf{C} \mathbf{A}^{-1} \mathbf{B} + \mathbf{E} \right) \mathbf{U}$$

# Small-signal ac state-space averaged model

---

$$\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{dt} = \mathbf{A} \hat{\mathbf{x}}(t) + \mathbf{B} \hat{\mathbf{u}}(t) + \left\{ (\mathbf{A}_1 - \mathbf{A}_2) \mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2) \mathbf{U} \right\} \hat{d}(t)$$
$$\hat{\mathbf{y}}(t) = \mathbf{C} \hat{\mathbf{x}}(t) + \mathbf{E} \hat{\mathbf{u}}(t) + \left\{ (\mathbf{C}_1 - \mathbf{C}_2) \mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2) \mathbf{U} \right\} \hat{d}(t)$$

where

$\hat{\mathbf{x}}(t)$  = small – signal (ac) perturbation in state vector

$\hat{\mathbf{u}}(t)$  = small – signal (ac) perturbation in input vector

$\hat{\mathbf{y}}(t)$  = small – signal (ac) perturbation in output vector

$\hat{d}(t)$  = small – signal (ac) perturbation in duty cycle

So if we can write the converter state equations during subintervals 1 and 2, then we can always find the averaged dc and small-signal ac models

## 7.4.3. Discussion of the state-space averaging result

---

As in Sections 7.1 and 7.2, the low-frequency components of the inductor currents and capacitor voltages are modeled by averaging over an interval of length  $T_s$ . Hence, we define the average of the state vector as:

$$\langle \mathbf{x}(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} \mathbf{x}(\tau) d\tau$$

The low-frequency components of the input and output vectors are modeled in a similar manner.

By averaging the inductor voltages and capacitor currents, one obtains:

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left( d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left( d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$

## Change in state vector during first subinterval

---

During subinterval 1, we have

$$\begin{aligned}\mathbf{K} \frac{d\mathbf{x}(t)}{dt} &= \mathbf{A}_1 \mathbf{x}(t) + \mathbf{B}_1 \mathbf{u}(t) \\ \mathbf{y}(t) &= \mathbf{C}_1 \mathbf{x}(t) + \mathbf{E}_1 \mathbf{u}(t)\end{aligned}$$

So the elements of  $\mathbf{x}(t)$  change with the slope

$$\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1} \left( \mathbf{A}_1 \mathbf{x}(t) + \mathbf{B}_1 \mathbf{u}(t) \right)$$


Small ripple assumption: the elements of  $\mathbf{x}(t)$  and  $\mathbf{u}(t)$  do not change significantly during the subinterval. Hence the slopes are essentially constant and are equal to

$$\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1} \left( \mathbf{A}_1 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_1 \langle \mathbf{u}(t) \rangle_{T_s} \right)$$


 
## Change in state vector during first subinterval

$$\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1} \left( \mathbf{A}_1 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_1 \langle \mathbf{u}(t) \rangle_{T_s} \right)$$



Net change in state vector over first subinterval:

$$\underbrace{\mathbf{x}(dT_s)}_{\text{final value}} = \underbrace{\mathbf{x}(0)}_{\text{initial value}} + \underbrace{(dT_s)}_{\text{interval length}} \underbrace{\mathbf{K}^{-1} \left( \mathbf{A}_1 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_1 \langle \mathbf{u}(t) \rangle_{T_s} \right)}_{\text{slope}}$$

## Change in state vector during second subinterval

---

Use similar arguments.

State vector now changes with the essentially constant slope

$$\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1} \left( \mathbf{A}_2 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_2 \langle \mathbf{u}(t) \rangle_{T_s} \right)$$

The value of the state vector at the end of the second subinterval is therefore

$$\underbrace{\mathbf{x}(T_s)}_{\text{final value}} = \underbrace{\mathbf{x}(dT_s)}_{\text{initial value}} + \underbrace{(dT_s)}_{\text{interval length}} \underbrace{\mathbf{K}^{-1} \left( \mathbf{A}_2 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_2 \langle \mathbf{u}(t) \rangle_{T_s} \right)}_{\text{slope}}$$

## Net change in state vector over one switching period

---

We have:

$$\mathbf{x}(dT_s) = \mathbf{x}(0) + (dT_s) \mathbf{K}^{-1} \left( \mathbf{A}_1 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_1 \langle \mathbf{u}(t) \rangle_{T_s} \right)$$

$$\mathbf{x}(T_s) = \mathbf{x}(dT_s) + (d'T_s) \mathbf{K}^{-1} \left( \mathbf{A}_2 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_2 \langle \mathbf{u}(t) \rangle_{T_s} \right)$$


Eliminate  $\mathbf{x}(dT_s)$ , to express  $\mathbf{x}(T_s)$  directly in terms of  $\mathbf{x}(0)$  :

$$\mathbf{x}(T_s) = \mathbf{x}(0) + dT_s \mathbf{K}^{-1} \left( \mathbf{A}_1 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_1 \langle \mathbf{u}(t) \rangle_{T_s} \right) + d'T_s \mathbf{K}^{-1} \left( \mathbf{A}_2 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_2 \langle \mathbf{u}(t) \rangle_{T_s} \right)$$

Collect terms:

$$\mathbf{x}(T_s) = \mathbf{x}(0) + T_s \mathbf{K}^{-1} \left( d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + T_s \mathbf{K}^{-1} \left( d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$
 
## Approximate derivative of state vector




Use Euler approximation:

$$\frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} \approx \frac{\mathbf{x}(T_s) - \mathbf{x}(0)}{T_s}$$

We obtain:

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left( d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left( d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$
 
# Low-frequency components of output vector



Remove switching harmonics by averaging over one switching period:

$$\langle \mathbf{y}(t) \rangle_{T_s} = d(t) \left( \mathbf{C}_1 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{E}_1 \langle \mathbf{u}(t) \rangle_{T_s} \right) + d'(t) \left( \mathbf{C}_2 \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{E}_2 \langle \mathbf{u}(t) \rangle_{T_s} \right)$$

Collect terms:

$$\langle \mathbf{y}(t) \rangle_{T_s} = \left( d(t) \mathbf{C}_1 + d'(t) \mathbf{C}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left( d(t) \mathbf{E}_1 + d'(t) \mathbf{E}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$

## Averaged state equations: quiescent operating point

---

The averaged (nonlinear) state equations:

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left( d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left( d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$
$$\langle \mathbf{y}(t) \rangle_{T_s} = \left( d(t) \mathbf{C}_1 + d'(t) \mathbf{C}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left( d(t) \mathbf{E}_1 + d'(t) \mathbf{E}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$

The converter operates in equilibrium when the derivatives of all elements of  $\langle \mathbf{x}(t) \rangle_{T_s}$  are zero. Hence, the converter quiescent operating point is the solution of

$$\mathbf{0} = \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U}$$

$$\mathbf{Y} = \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U}$$

where	$\mathbf{A} = D \mathbf{A}_1 + D' \mathbf{A}_2$	and	$\mathbf{X} = \text{equilibrium (dc) state vector}$
	$\mathbf{B} = D \mathbf{B}_1 + D' \mathbf{B}_2$		$\mathbf{U} = \text{equilibrium (dc) input vector}$
	$\mathbf{C} = D \mathbf{C}_1 + D' \mathbf{C}_2$		$\mathbf{Y} = \text{equilibrium (dc) output vector}$
	$\mathbf{E} = D \mathbf{E}_1 + D' \mathbf{E}_2$		$D = \text{equilibrium (dc) duty cycle}$

## Averaged state equations: perturbation and linearization

$$\begin{array}{ll}
 \text{Let } \langle \mathbf{x}(t) \rangle_{T_s} = \mathbf{X} + \hat{\mathbf{x}}(t) & \text{with } \|\mathbf{U}\| \gg \|\hat{\mathbf{u}}(t)\| \\
 \langle \mathbf{u}(t) \rangle_{T_s} = \mathbf{U} + \hat{\mathbf{u}}(t) & D \gg |\hat{d}(t)| \\
 \langle \mathbf{y}(t) \rangle_{T_s} = \mathbf{Y} + \hat{\mathbf{y}}(t) & \|\mathbf{X}\| \gg \|\hat{\mathbf{x}}(t)\| \\
 d(t) = D + \hat{d}(t) \Rightarrow d'(t) = D' - \hat{d}(t) & \|\mathbf{Y}\| \gg \|\hat{\mathbf{y}}(t)\|
 \end{array}$$

Substitute into averaged state equations:

$$\begin{aligned}
 \mathbf{K} \frac{d(\mathbf{X} + \hat{\mathbf{x}}(t))}{dt} = & \left( (D + \hat{d}(t)) \mathbf{A}_1 + (D' - \hat{d}(t)) \mathbf{A}_2 \right) (\mathbf{X} + \hat{\mathbf{x}}(t)) \\
 & + \left( (D + \hat{d}(t)) \mathbf{B}_1 + (D' - \hat{d}(t)) \mathbf{B}_2 \right) (\mathbf{U} + \hat{\mathbf{u}}(t))
 \end{aligned}$$

$$\begin{aligned}
 (\mathbf{Y} + \hat{\mathbf{y}}(t)) = & \left( (D + \hat{d}(t)) \mathbf{C}_1 + (D' - \hat{d}(t)) \mathbf{C}_2 \right) (\mathbf{X} + \hat{\mathbf{x}}(t)) \\
 & + \left( (D + \hat{d}(t)) \mathbf{E}_1 + (D' - \hat{d}(t)) \mathbf{E}_2 \right) (\mathbf{U} + \hat{\mathbf{u}}(t))
 \end{aligned}$$

## Averaged state equations: perturbation and linearization

$$\begin{aligned}
 \underbrace{\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{dt}}_{\text{first-order ac}} &= \underbrace{(\mathbf{A}\mathbf{X} + \mathbf{B}\mathbf{U})}_{\text{dc terms}} + \underbrace{\mathbf{A}\hat{\mathbf{x}}(t) + \mathbf{B}\hat{\mathbf{u}}(t) + \left\{ (\mathbf{A}_1 - \mathbf{A}_2)\mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2)\mathbf{U} \right\} \hat{d}(t)}_{\text{first-order ac terms}} \\
 &+ \underbrace{(\mathbf{A}_1 - \mathbf{A}_2)\hat{\mathbf{x}}(t)\hat{d}(t) + (\mathbf{B}_1 - \mathbf{B}_2)\hat{\mathbf{u}}(t)\hat{d}(t)}_{\text{second-order nonlinear terms}}
 \end{aligned}$$
  

$$\begin{aligned}
 \underbrace{(\mathbf{Y} + \hat{\mathbf{y}}(t))}_{\text{dc} + 1\text{st order ac}} &= \underbrace{(\mathbf{C}\mathbf{X} + \mathbf{E}\mathbf{U})}_{\text{dc terms}} + \underbrace{\mathbf{C}\hat{\mathbf{x}}(t) + \mathbf{E}\hat{\mathbf{u}}(t) + \left\{ (\mathbf{C}_1 - \mathbf{C}_2)\mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2)\mathbf{U} \right\} \hat{d}(t)}_{\text{first-order ac terms}} \\
 &+ \underbrace{(\mathbf{C}_1 - \mathbf{C}_2)\hat{\mathbf{x}}(t)\hat{d}(t) + (\mathbf{E}_1 - \mathbf{E}_2)\hat{\mathbf{u}}(t)\hat{d}(t)}_{\text{second-order nonlinear terms}}
 \end{aligned}$$



# Linearized small-signal state equations


---

Dc terms drop out of equations. Second-order (nonlinear) terms are small when the small-signal assumption is satisfied. We are left with:

$$\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{dt} = \mathbf{A} \hat{\mathbf{x}}(t) + \mathbf{B} \hat{\mathbf{u}}(t) + \left\{ (\mathbf{A}_1 - \mathbf{A}_2) \mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2) \mathbf{U} \right\} \hat{d}(t)$$
$$\hat{\mathbf{y}}(t) = \mathbf{C} \hat{\mathbf{x}}(t) + \mathbf{E} \hat{\mathbf{u}}(t) + \left\{ (\mathbf{C}_1 - \mathbf{C}_2) \mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2) \mathbf{U} \right\} \hat{d}(t)$$

This is the desired result.
 
## 7.4.4. Example: State-space averaging of a nonideal buck-boost converter



Model nonidealities:

- MOSFET on-resistance  $R_{on}$
- Diode forward voltage drop  $V_D$

state vector

$$\mathbf{x}(t) = \begin{bmatrix} i(t) \\ v(t) \end{bmatrix}$$

input vector


$$\mathbf{u}(t) = \begin{bmatrix} v_g(t) \\ V_D \end{bmatrix}$$

output vector

$$\mathbf{y}(t) = \begin{bmatrix} i_g(t) \end{bmatrix}$$
 
# Subinterval 1

$$\begin{aligned} L \frac{di(t)}{dt} &= v_g(t) - i(t) R_{on} \\ C \frac{dv(t)}{dt} &= -\frac{v(t)}{R} \\ i_g(t) &= i(t) \end{aligned}$$




$$\underbrace{\begin{bmatrix} L & 0 \\ 0 & C \end{bmatrix}}_{\mathbf{K}} \underbrace{\frac{d}{dt} \begin{bmatrix} i(t) \\ v(t) \end{bmatrix}}_{\frac{d\mathbf{x}(t)}{dt}} = \underbrace{\begin{bmatrix} -R_{on} & 0 \\ 0 & -\frac{1}{R} \end{bmatrix}}_{\mathbf{A}_1} \underbrace{\begin{bmatrix} i(t) \\ v(t) \end{bmatrix}}_{\mathbf{x}(t)} + \underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix}}_{\mathbf{B}_1} \underbrace{\begin{bmatrix} v_g(t) \\ V_D \end{bmatrix}}_{\mathbf{u}(t)}$$

$$\underbrace{\begin{bmatrix} i_g(t) \end{bmatrix}}_{\mathbf{y}(t)} = \underbrace{\begin{bmatrix} 1 & 0 \end{bmatrix}}_{\mathbf{C}_1} \underbrace{\begin{bmatrix} i(t) \\ v(t) \end{bmatrix}}_{\mathbf{x}(t)} + \underbrace{\begin{bmatrix} 0 & 0 \end{bmatrix}}_{\mathbf{E}_1} \underbrace{\begin{bmatrix} v_g(t) \\ V_D \end{bmatrix}}_{\mathbf{u}(t)}$$
 
## Subinterval 2

$$\begin{aligned} L \frac{di(t)}{dt} &= v(t) - V_D \\ C \frac{dv(t)}{dt} &= -\frac{v(t)}{R} - i(t) \\ i_g(t) &= 0 \end{aligned}$$



$$\underbrace{\begin{bmatrix} L & 0 \\ 0 & C \end{bmatrix}}_{\mathbf{K}} \underbrace{\frac{d}{dt} \begin{bmatrix} i(t) \\ v(t) \end{bmatrix}}_{\frac{d\mathbf{x}(t)}{dt}} = \underbrace{\begin{bmatrix} 0 & 1 \\ -1 & -\frac{1}{R} \end{bmatrix}}_{\mathbf{A}_2} \underbrace{\begin{bmatrix} i(t) \\ v(t) \end{bmatrix}}_{\mathbf{x}(t)} + \underbrace{\begin{bmatrix} 0 & -1 \\ 0 & 0 \end{bmatrix}}_{\mathbf{B}_2} \underbrace{\begin{bmatrix} v_g(t) \\ V_D \end{bmatrix}}_{\mathbf{u}(t)}$$
  

$$\underbrace{\begin{bmatrix} i_g(t) \end{bmatrix}}_{\mathbf{y}(t)} = \underbrace{\begin{bmatrix} 0 & 0 \end{bmatrix}}_{\mathbf{C}_2} \underbrace{\begin{bmatrix} i(t) \\ v(t) \end{bmatrix}}_{\mathbf{x}(t)} + \underbrace{\begin{bmatrix} 0 & 0 \end{bmatrix}}_{\mathbf{E}_2} \underbrace{\begin{bmatrix} v_g(t) \\ V_D \end{bmatrix}}_{\mathbf{u}(t)}$$

## Evaluate averaged matrices

---

$$\mathbf{A} = D\mathbf{A}_1 + D'\mathbf{A}_2 = D \begin{bmatrix} -R_{on} & 0 \\ 0 & -\frac{1}{R} \end{bmatrix} + D' \begin{bmatrix} 0 & 1 \\ -1 & -\frac{1}{R} \end{bmatrix} = \begin{bmatrix} -DR_{on} & D' \\ -D' & -\frac{1}{R} \end{bmatrix}$$

In a similar manner,

$$\mathbf{B} = D\mathbf{B}_1 + D'\mathbf{B}_2 = \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix}$$

$$\mathbf{C} = D\mathbf{C}_1 + D'\mathbf{C}_2 = \begin{bmatrix} D & 0 \end{bmatrix}$$

$$\mathbf{E} = D\mathbf{E}_1 + D'\mathbf{E}_2 = \begin{bmatrix} 0 & 0 \end{bmatrix}$$

# DC state equations

---

$$\begin{aligned}
 \mathbf{0} &= \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U} \\
 \mathbf{Y} &= \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U}
 \end{aligned}
 \quad \text{or,} \quad
 \begin{aligned}
 \begin{bmatrix} 0 \\ 0 \end{bmatrix} &= \begin{bmatrix} -DR_{on} & D' \\ -D' & -\frac{1}{R} \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix} + \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix} \\
 I_g &= \begin{bmatrix} D & 0 \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix} + \begin{bmatrix} 0 & 0 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix}
 \end{aligned}$$


---

DC solution:

$$\begin{aligned}
 \begin{bmatrix} I \\ V \end{bmatrix} &= \left( \frac{1}{1 + \frac{D}{D'^2} \frac{R_{on}}{R}} \right) \begin{bmatrix} \frac{D}{D'^2 R} & \frac{1}{D' R} \\ -\frac{D}{D'} & 1 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix} \\
 I_g &= \left( \frac{1}{1 + \frac{D}{D'^2} \frac{R_{on}}{R}} \right) \begin{bmatrix} \frac{D^2}{D'^2 R} & \frac{D}{D' R} \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix}
 \end{aligned}$$


# Steady-state equivalent circuit

DC state equations:

$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -DR_{on} & D' \\ -D' & -\frac{1}{R} \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix} + \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix}$$

$$\begin{bmatrix} I_g \end{bmatrix} = \begin{bmatrix} D & 0 \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix} + \begin{bmatrix} 0 & 0 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix}$$

Corresponding equivalent circuit:

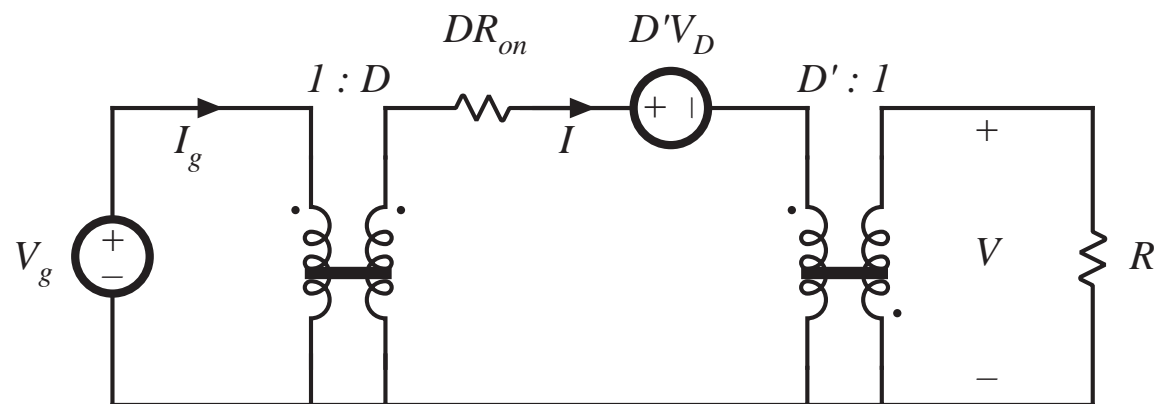

# Small-signal ac model

Evaluate matrices in small-signal model:

$$(\mathbf{A}_1 - \mathbf{A}_2) \mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2) \mathbf{U} = \begin{bmatrix} -V \\ I \end{bmatrix} + \begin{bmatrix} V_g - IR_{on} + V_D \\ 0 \end{bmatrix} = \begin{bmatrix} V_g - V - IR_{on} + V_D \\ I \end{bmatrix}$$

$$(\mathbf{C}_1 - \mathbf{C}_2) \mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2) \mathbf{U} = [I]$$

Small-signal ac state equations:

$$\begin{bmatrix} L & 0 \\ 0 & C \end{bmatrix} \frac{d}{dt} \begin{bmatrix} \hat{i}(t) \\ \hat{v}(t) \end{bmatrix} = \begin{bmatrix} -DR_{on} & D' \\ -D' & -\frac{1}{R} \end{bmatrix} \begin{bmatrix} \hat{i}(t) \\ \hat{v}(t) \end{bmatrix} + \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \hat{v}_g(t) \\ \hat{v}_D(t) \end{bmatrix} + \begin{bmatrix} V_g - V - IR_{on} + V_D \\ I \end{bmatrix} \hat{d}(t)$$

$$\begin{bmatrix} \hat{i}_g(t) \end{bmatrix} = \begin{bmatrix} D & 0 \end{bmatrix} \begin{bmatrix} \hat{i}(t) \\ \hat{v}(t) \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \hat{v}_g(t) \\ \hat{v}_D(t) \end{bmatrix} + \begin{bmatrix} 0 \\ I \end{bmatrix} \hat{d}(t)$$



# Construction of ac equivalent circuit

Small-signal ac equations, in scalar form:


$$L \frac{d\hat{i}(t)}{dt} = D' \hat{v}(t) - DR_{on} \hat{i}(t) + D \hat{v}_g(t) + \left( V_g - V - IR_{on} + V_D \right) \hat{d}(t)$$

$$C \frac{d\hat{v}(t)}{dt} = -D' \hat{i}(t) - \frac{\hat{v}(t)}{R} + I \hat{d}(t)$$


$$\hat{i}_g(t) = D \hat{i}(t) + I \hat{d}(t)$$

Corresponding equivalent circuits:


*inductor equation*

 

*input eqn*

 


*capacitor eqn*

 

# Complete small-signal ac equivalent circuit

Combine individual circuits to obtain

 


## 7.5. Circuit Averaging and Averaged Switch Modeling

---


- Historically, circuit averaging was the first method known for modeling the small-signal ac behavior of CCM PWM converters
- It was originally thought to be difficult to apply in some cases
- There has been renewed interest in circuit averaging and its corrolary, averaged switch modeling, in the last decade
- Can be applied to a wide variety of converters
  - We will use it to model DCM, CPM, and resonant converters
  - Also useful for incorporating switching loss into ac model of CCM converters
  - Applicable to 3 $\phi$  PWM inverters and rectifiers
  - Can be applied to phase-controlled rectifiers
- Rather than averaging and linearizing the converter state equations, the averaging and linearization operations are performed directly on the converter circuit
 
# Separate switch network from remainder of converter





# Boost converter example

*Ideal boost converter example*

 

*Two ways to define the switch network*

  

# Discussion

---

- The number of ports in the switch network is less than or equal to the number of SPST switches
- Simple dc-dc case, in which converter contains two SPST switches: switch network contains two ports



The switch network terminal waveforms are then the port voltages and currents:  $v_1(t)$ ,  $i_1(t)$ ,  $v_2(t)$ , and  $i_2(t)$ .

Two of these waveforms can be taken as independent inputs to the switch network; the remaining two waveforms are then viewed as dependent outputs of the switch network.

- Definition of the switch network terminal quantities is not unique. Different definitions lead equivalent results having different forms

# Boost converter example


Let's use definition (a):

  

Since  $i_1(t)$  and  $v_2(t)$  coincide with the converter inductor current and output voltage, it is convenient to define these waveforms as the independent inputs to the switch network. The switch network dependent outputs are then  $v_1(t)$  and  $i_2(t)$ .
 
# Obtaining a time-invariant network: Modeling the terminal behavior of the switch network



Replace the switch network with dependent sources, which correctly represent the dependent output waveforms of the switch network



*Boost converter example*


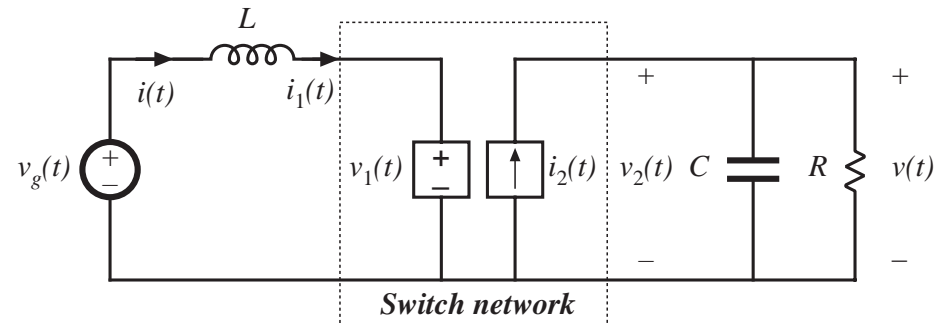 
# Definition of dependent generator waveforms




The waveforms of the dependent generators are defined to be identical to the actual terminal waveforms of the switch network.

The circuit is therefore electrical identical to the original converter.

So far, no approximations have been made.
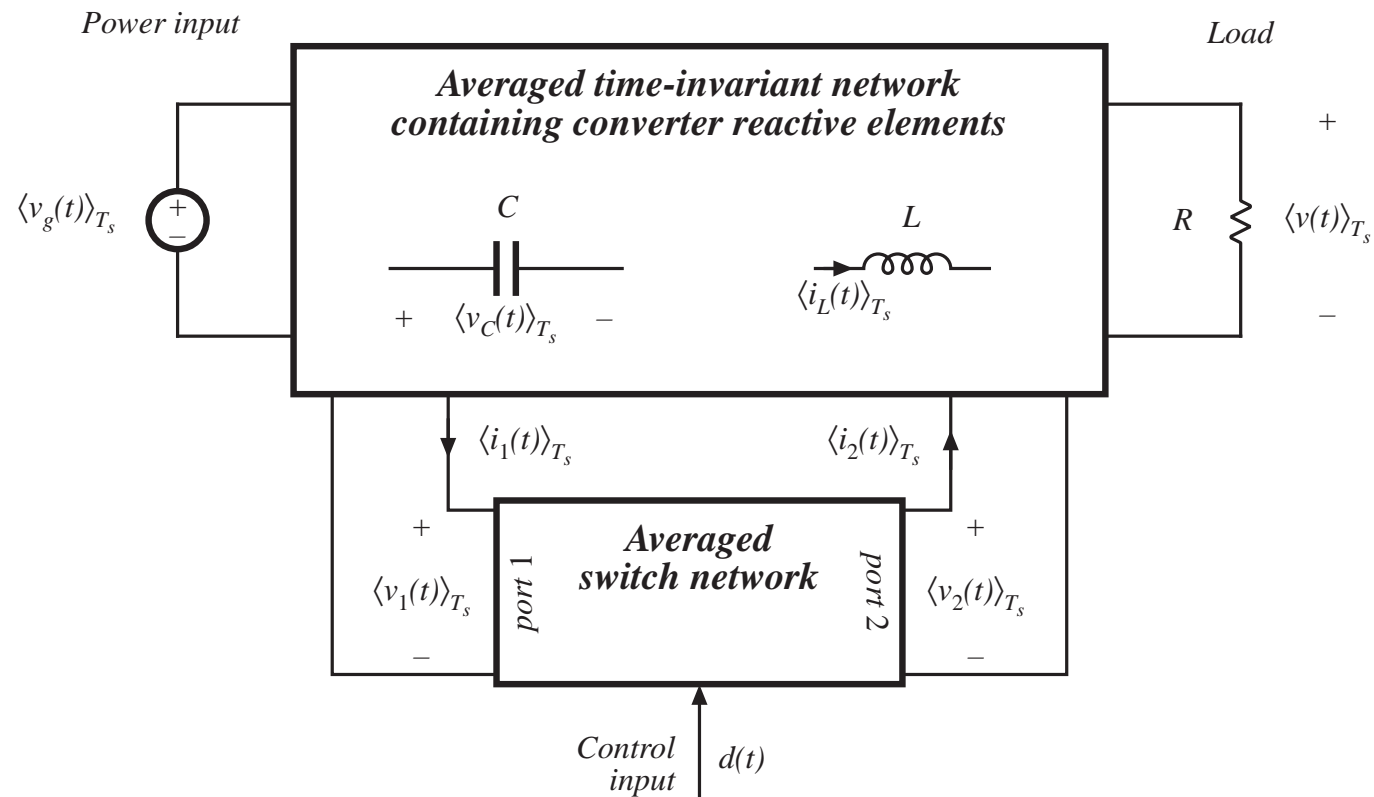
# The circuit averaging step

Now average all waveforms over one switching period:




# The averaging step

---



The basic assumption is made that the natural time constants of the converter are much longer than the switching period, so that the converter contains low-pass filtering of the switching harmonics. One may average the waveforms over an interval that is short compared to the system natural time constants, without significantly altering the system response. In particular, averaging over the switching period  $T_s$  removes the switching harmonics, while preserving the low-frequency components of the waveforms.

In practice, the only work needed for this step is to average the switch dependent waveforms.
 
# Averaging step: boost converter example



  
# Compute average values of dependent sources



Average the waveforms of the dependent sources:

$$\langle v_1(t) \rangle_{T_s} = d'(t) \langle v_2(t) \rangle_{T_s}$$
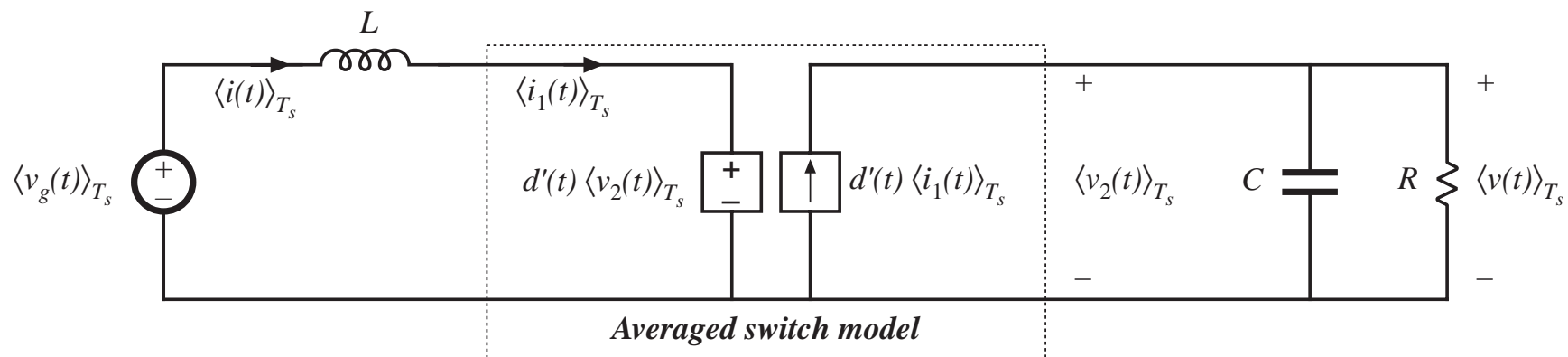
$$\langle i_2(t) \rangle_{T_s} = d'(t) \langle i_1(t) \rangle_{T_s}$$



# Perturb and linearize

As usual, let:

$$\langle v_g(t) \rangle_{T_s} = V_g + \hat{v}_g(t)$$

$$d(t) = D + \hat{d}(t) \Rightarrow d'(t) = D' - \hat{d}(t)$$


$$\langle i(t) \rangle_{T_s} = \langle i_1(t) \rangle_{T_s} = I + \hat{i}(t)$$

$$\langle v(t) \rangle_{T_s} = \langle v_2(t) \rangle_{T_s} = V + \hat{v}(t)$$

$$\langle v_1(t) \rangle_{T_s} = V_1 + \hat{v}_1(t)$$

$$\langle i_2(t) \rangle_{T_s} = I_2 + \hat{i}_2(t)$$


The circuit becomes:

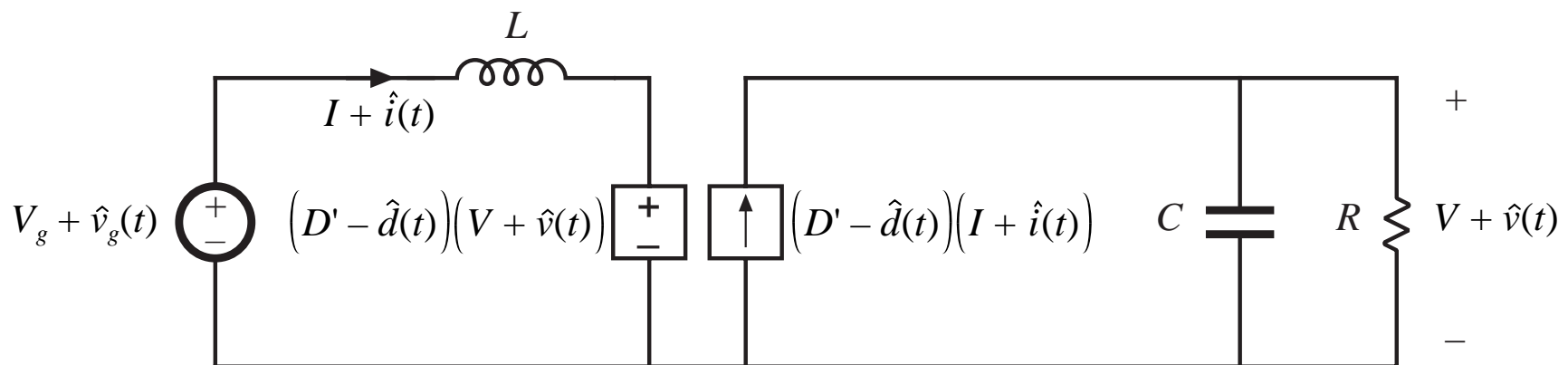

# Dependent voltage source

$$\left( D' - \hat{d}(t) \right) \left( V + \hat{v}(t) \right) = D' \left( V + \hat{v}(t) \right) - V \hat{d}(t) - \hat{v}(t) \hat{d}(t)$$


*nonlinear,  
2nd order*

 

# Dependent current source


$$\left(D' - \hat{d}(t)\right) \left(I + \hat{i}(t)\right) = D' \left(I + \hat{i}(t)\right) - I \hat{d}(t) - \hat{i}(t) \hat{d}(t)$$

*nonlinear,  
2nd order*

 



# Linearized circuit-averaged model

 

# Summary: Circuit averaging method

---


Model the switch network with equivalent voltage and current sources, such that an equivalent time-invariant network is obtained

Average converter waveforms over one switching period, to remove the switching harmonics


Perturb and linearize the resulting low-frequency model, to obtain a small-signal equivalent circuit
 
# Averaged switch modeling: CCM

*Circuit averaging of the boost converter: in essence, the switch network was replaced with an effective ideal transformer and generators:*


 
# Basic functions performed by switch network




For the boost example, we can conclude that the switch network performs two basic functions:

- Transformation of dc and small-signal ac voltage and current levels, according to the  $D':1$  conversion ratio
- Introduction of ac voltage and current variations, drive by the control input duty cycle variations

Circuit averaging modifies only the switch network. Hence, to obtain a small-signal converter model, we need only replace the switch network with its averaged model. Such a procedure is called *averaged switch modeling*.




# Averaged switch modeling: Procedure

 1. Define a switch network and its terminal waveforms. For a simple transistor-diode switch network as in the buck, boost, etc., there are two ports and four terminal quantities:  $v_1$ ,  $i_1$ ,  $v_2$ ,  $i_2$ . The switch network also contains a control input  $d$ . Buck example:



2. To derive an averaged switch model, express the average values of two of the terminal quantities, for example  $\langle v_2 \rangle_{T_s}$  and  $\langle i_1 \rangle_{T_s}$ , as functions of the other average terminal quantities  $\langle v_1 \rangle_{T_s}$  and  $\langle i_1 \rangle_{T_s}$ .  $\langle v_2 \rangle_{T_s}$  and  $\langle i_1 \rangle_{T_s}$  may also be functions of the control input  $d$ , but they should not be expressed in terms of other converter signals.


# The basic buck-type CCM switch cell

   

$$\begin{aligned}\langle i_1(t) \rangle_{T_s} &= d(t) \langle i_2(t) \rangle_{T_s} \\ \langle v_2(t) \rangle_{T_s} &= d(t) \langle v_1(t) \rangle_{T_s}\end{aligned}$$

# Replacement of switch network by dependent sources, CCM buck example


*Circuit-averaged model*

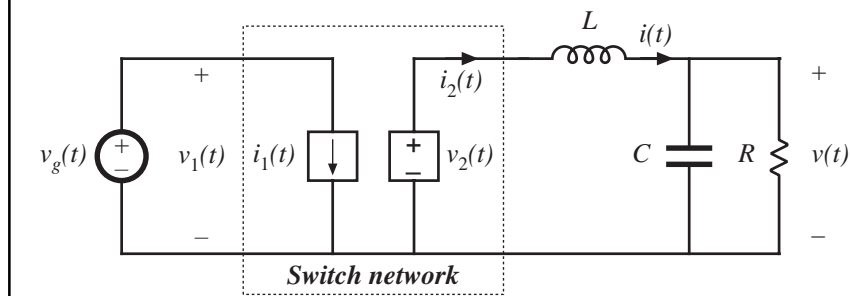


*Perturbation and linearization of switch network:*

$$I_1 + \hat{i}_1(t) = D(I_2 + \hat{i}_2(t)) + I_2 \hat{d}(t)$$






 
$$V_2 + \hat{v}_2(t) = D(V_1 + \hat{v}_1(t)) + V_1 \hat{d}(t)$$



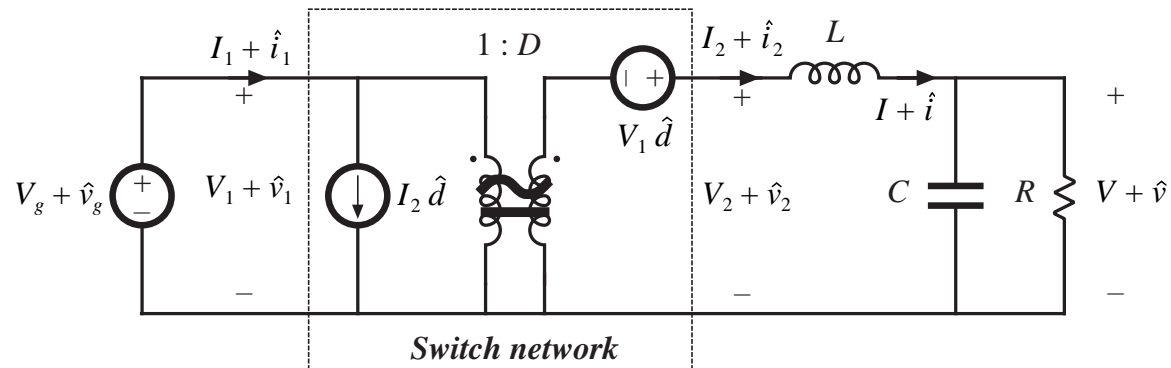*Resulting  
averaged switch  
model: CCM  
buck converter*


      
# Three basic switch networks, and their CCM dc and small-signal ac averaged switch models




*see also*

Appendix 3  
Averaged switch  
modeling of a  
CCM SEPIC



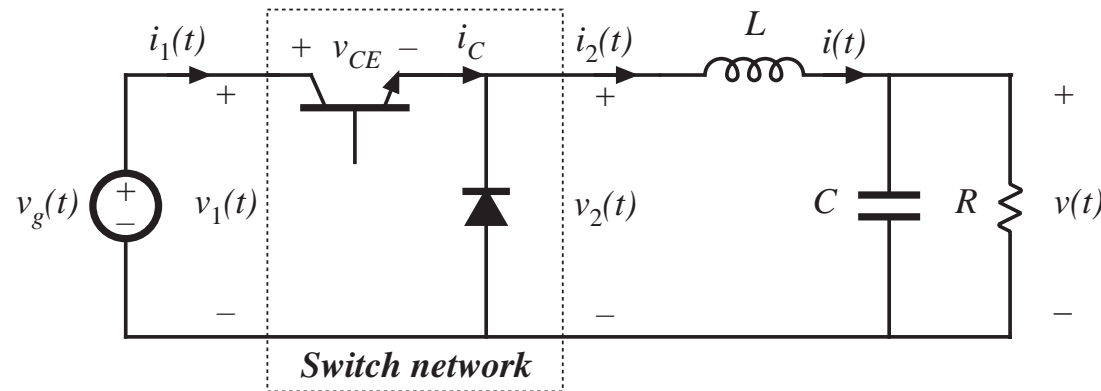
## Example: Averaged switch modeling of CCM buck converter, including switching loss




$$i_1(t) = i_C(t)$$

$$v_2(t) = v_1(t) - v_{CE}(t)$$

 

Switch network terminal waveforms:  $v_1$ ,  $i_1$ ,  $v_2$ ,  $i_2$ . To derive averaged switch model, express  $\langle v_2 \rangle_{T_s}$  and  $\langle i_1 \rangle_{T_s}$  as functions of  $\langle v_1 \rangle_{T_s}$  and  $\langle i_1 \rangle_{T_s}$ .  $\langle v_2 \rangle_{T_s}$  and  $\langle i_1 \rangle_{T_s}$  may also be functions of the control input  $d$ , but they should not be expressed in terms of other converter signals.

# Averaging $i_1(t)$

 

$$\begin{aligned} \langle i_1(t) \rangle_{T_s} &= \frac{1}{T_s} \int_0^{T_s} i_1(t) dt \\ &= \langle i_2(t) \rangle_{T_s} \left( \frac{t_1 + t_{vf} + t_{vr} + \frac{1}{2} t_{ir} + \frac{1}{2} t_{if}}{T_s} \right) \end{aligned}$$

## Expression for $\langle i_1(t) \rangle$

*Given*

$$\begin{aligned}\langle i_1(t) \rangle_{T_s} &= \frac{1}{T_s} \int_0^{T_s} i_1(t) dt \\ &= \langle i_2(t) \rangle_{T_s} \left( \frac{t_1 + t_{vf} + t_{vr} + \frac{1}{2} t_{ir} + \frac{1}{2} t_{if}}{T_s} \right)\end{aligned}$$


*Let*

$$\begin{aligned}d &= \left( \frac{t_1 + \frac{1}{2} t_{vf} + \frac{1}{2} t_{vr} + \frac{1}{2} t_{ir} + \frac{1}{2} t_{if}}{T_s} \right) \\ d_v &= \left( \frac{t_{vf} + t_{vr}}{T_s} \right) \\ d_i &= \left( \frac{t_{ir} + t_{if}}{T_s} \right)\end{aligned}$$

*Then we can write*

$$\langle i_1(t) \rangle_{T_s} = \langle i_2(t) \rangle_{T_s} \left( d + \frac{1}{2} d_v \right)$$
 
## Averaging the switch network output voltage $v_2(t)$




$$\langle v_2(t) \rangle_{T_s} = \langle v_1(t) - v_{CE}(t) \rangle_{T_s} = \frac{1}{T_s} \int_0^{T_s} (-v_{CE}(t)) dt + \langle v_1(t) \rangle_{T_s}$$

$$\langle v_2(t) \rangle_{T_s} = \langle v_1(t) \rangle_{T_s} \left( \frac{t_1 + \frac{1}{2} t_{vf} + \frac{1}{2} t_{vr}}{T_s} \right)$$


$$\langle v_2(t) \rangle_{T_s} = \langle v_1(t) \rangle_{T_s} \left( d - \frac{1}{2} d_i \right)$$
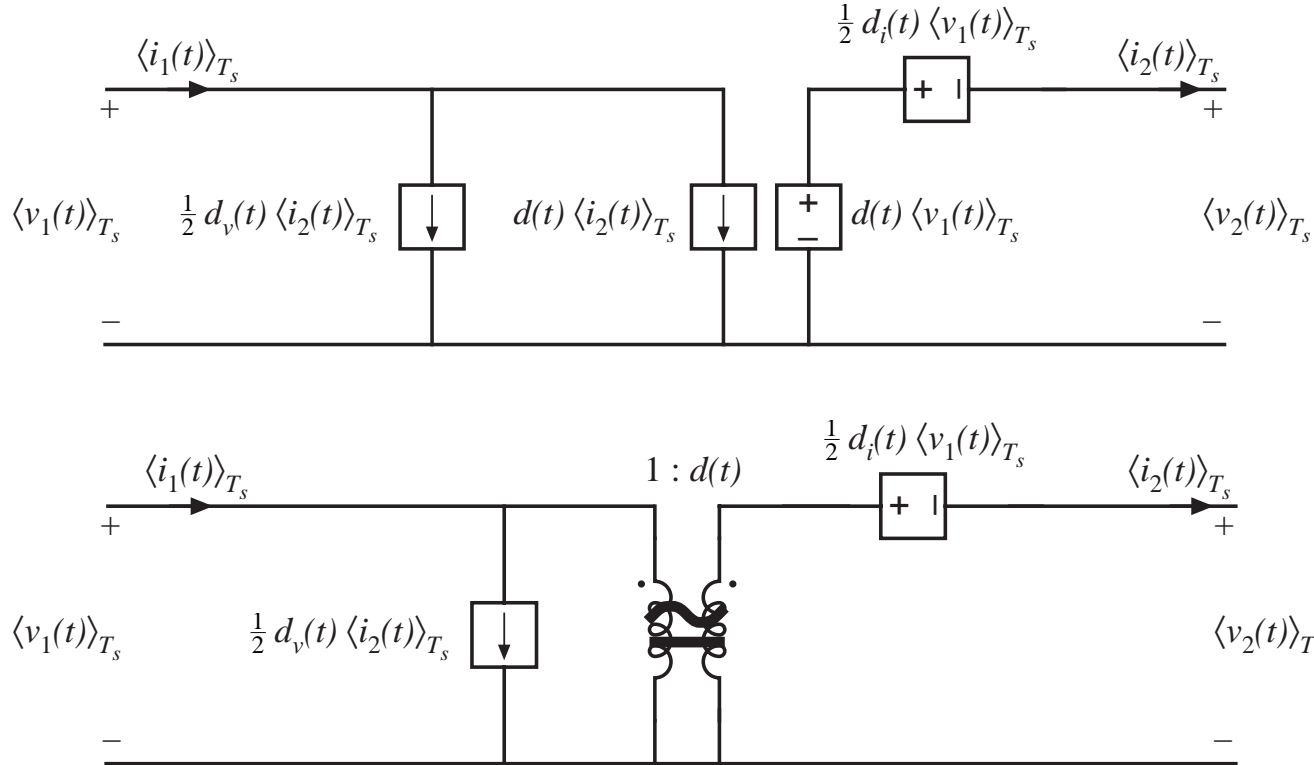
# Construction of large-signal averaged-switch model

$$\langle i_1(t) \rangle_{T_s} = \langle i_2(t) \rangle_{T_s} \left( d + \frac{1}{2} d_v \right) \quad \langle v_2(t) \rangle_{T_s} = \langle v_1(t) \rangle_{T_s} \left( d - \frac{1}{2} d_i \right)$$



 
# Switching loss predicted by averaged switch model



$$P_{sw} = \frac{1}{2} (d_v + d_i) \langle i_2(t) \rangle_{T_s} \langle v_1(t) \rangle_{T_s}$$
 
## Solution of averaged converter model in steady state



*Output voltage:*

$$V = \left( D - \frac{1}{2} D_i \right) V_g = D V_g \left( 1 - \frac{D_i}{2D} \right)$$

*Efficiency calculation:*

$$P_{in} = V_g I_1 = V_1 I_2 \left( D + \frac{1}{2} D_v \right)$$

$$P_{out} = V I_2 = V_1 I_2 \left( D - \frac{1}{2} D_i \right)$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{\left( D - \frac{1}{2} D_i \right)}{\left( D + \frac{1}{2} D_v \right)} = \frac{\left( 1 - \frac{D_i}{2D} \right)}{\left( 1 + \frac{D_v}{2D} \right)}$$

## 7.6. The canonical circuit model

---

All PWM CCM dc-dc converters perform the same basic functions:

- Transformation of voltage and current levels, ideally with 100% efficiency
- Low-pass filtering of waveforms
- Control of waveforms by variation of duty cycle

Hence, we expect their equivalent circuit models to be qualitatively similar.

Canonical model:


- A standard form of equivalent circuit model, which represents the above physical properties
- Plug in parameter values for a given specific converter



## 7.6.1. Development of the canonical circuit model

 
### 1. Transformation of dc voltage and current levels

- modeled as in Chapter 3 with ideal dc transformer
- effective turns ratio  $M(D)$
- can refine dc model by addition of effective loss elements, as in Chapter 3



# Steps in the development of the canonical circuit model

 
2. *Ac variations in  $v_g(t)$  induce ac variations in  $v(t)$*
- *these variations are also transformed by the conversion ratio  $M(D)$*




# Steps in the development of the canonical circuit model
 
## 3. Converter must contain an effective low-pass filter characteristic

- necessary to filter switching ripple
- also filters ac variations
- effective filter elements may not coincide with actual element values, but can also depend on operating point



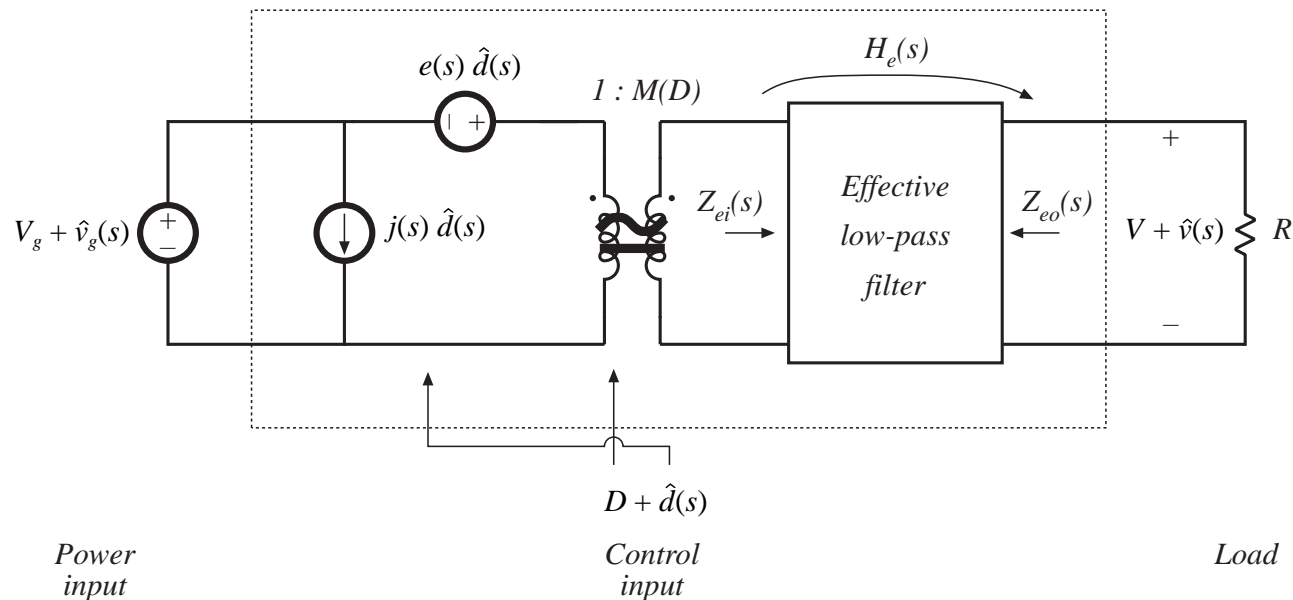
# Steps in the development of the canonical circuit model



4. *Control input variations also induce ac variations in converter waveforms*
  - *Independent sources represent effects of variations in duty cycle*
  - *Can push all sources to input side as shown. Sources may then become frequency-dependent*
 
# Transfer functions predicted by canonical model



Line-to-output transfer function:


$$G_{vg}(s) = \frac{\hat{v}(s)}{\hat{v}_g(s)} = M(D) H_e(s)$$

Control-to-output transfer function:

$$G_{vd}(s) = \frac{\hat{v}(s)}{\hat{d}(s)} = e(s) M(D) H_e(s)$$
 
## 7.6.2. Example: manipulation of the buck-boost converter model into canonical form


*Small-signal ac model of the buck-boost converter*



- Push independent sources to input side of transformers
- Push inductor to output side of transformers
- Combine transformers
 
# Step 1

*Push voltage source through 1:D transformer  
Move current source through D':1 transformer*




## Step 2

*How to move the current source past the inductor:*

*Break ground connection of current source, and connect to node A instead.*

 
*Connect an identical current source from node A to ground, so that the node equations are unchanged.*




 
## Step 3

*The parallel-connected current source and inductor can now be replaced by a Thevenin-equivalent network:*



## Step 4


*Now push current source through 1:D transformer.*

*Push current source past voltage source, again by:*

*Breaking ground connection of current source, and connecting to node B instead.*

*Connecting an identical current source from node B to ground, so that the node equations are unchanged.*

 
*Note that the resulting parallel-connected voltage and current sources are equivalent to a single voltage source.*



## Step 5: final result

*Push voltage source through 1:D transformer, and combine with existing input-side transformer.*

*Combine series-connected transformers.*

 

# Coefficient of control-input voltage generator

---

Voltage source coefficient is:

$$e(s) = \frac{V_g + V}{D} - \frac{s LI}{D D'}$$

Simplification, using dc relations, leads to

$$e(s) = -\frac{V}{D^2} \left( 1 - \frac{s DL}{D'^2 R} \right)$$

Pushing the sources past the inductor causes the generator to become frequency-dependent.

## 7.6.3. Canonical circuit parameters for some common converters

 



Table 7.1. Canonical model parameters for the ideal buck, boost, and buck-boost converters

Converter	$M(D)$	$L_e$	$e(s)$	$j(s)$
Buck	$D$	$L$	$\frac{V}{D^2}$	$\frac{V}{R}$
Boost	$\frac{1}{D'}$	$\frac{L}{D'^2}$	$V \left( 1 - \frac{sL}{D'^2 R} \right)$	$\frac{V}{D'^2 R}$
Buck-boost	$-\frac{D}{D'}$	$\frac{L}{D'^2}$	$-\frac{V}{D^2} \left( 1 - \frac{sDL}{D'^2 R} \right)$	$-\frac{V}{D'^2 R}$

 
## 7.7. Modeling the pulse-width modulator

Pulse-width modulator converts voltage signal  $v_c(t)$  into duty cycle signal  $d(t)$ .

What is the relation between  $v_c(t)$  and  $d(t)$ ?



# A simple pulse-width modulator

 


# Equation of pulse-width modulator

For a linear sawtooth waveform:

$$d(t) = \frac{v_c(t)}{V_M} \quad \text{for } 0 \leq v_c(t) \leq V_M$$

 So  $d(t)$  is a linear function of  $v_c(t)$ .





# Perturbed equation of pulse-width modulator

PWM equation:

$$d(t) = \frac{v_c(t)}{V_M} \quad \text{for } 0 \leq v_c(t) \leq V_M$$

Perturb:


$$v_c(t) = V_c + \hat{v}_c(t)$$

$$d(t) = D + \hat{d}(t)$$

Result:

$$D + \hat{d}(t) = \frac{V_c + \hat{v}_c(t)}{V_M}$$

Block diagram:

 

Dc and ac relations:

$$D = \frac{V_c}{V_M}$$


$$\hat{d}(t) = \frac{\hat{v}_c(t)}{V_M}$$

# Sampling in the pulse-width modulator

The input voltage is a continuous function of time, but there can be only one discrete value of the duty cycle for each switching period.

Therefore, the pulse-width modulator samples the control waveform, with sampling rate equal to the switching frequency.

 In practice, this limits the useful frequencies of ac variations to values much less than the switching frequency. Control system bandwidth must be sufficiently less than the Nyquist rate  $f_s/2$ . Models that do not account for sampling are accurate only at frequencies much less than  $f_s/2$ .



## 7.8. Summary of key points

---

1. The CCM converter analytical techniques of Chapters 2 and 3 can be extended to predict converter ac behavior. The key step is to average the converter waveforms over one switching period. This removes the switching harmonics, thereby exposing directly the desired dc and low-frequency ac components of the waveforms. In particular, expressions for the averaged inductor voltages, capacitor currents, and converter input current are usually found.
2. Since switching converters are nonlinear systems, it is desirable to construct small-signal linearized models. This is accomplished by perturbing and linearizing the averaged model about a quiescent operating point.
3. Ac equivalent circuits can be constructed, in the same manner used in Chapter 3 to construct dc equivalent circuits. If desired, the ac equivalent circuits may be refined to account for the effects of converter losses and other nonidealities.

## Summary of key points

---

4. The state-space averaging method of section 7.4 is essentially the same as the basic approach of section 7.2, except that the formality of the state-space network description is used. The general results are listed in section 7.4.2.
5. The circuit averaging technique also yields equivalent results, but the derivation involves manipulation of circuits rather than equations. Switching elements are replaced by dependent voltage and current sources, whose waveforms are defined to be identical to the switch waveforms of the actual circuit. This leads to a circuit having a time-invariant topology. The waveforms are then averaged to remove the switching ripple, and perturbed and linearized about a quiescent operating point to obtain a small-signal model.

## Summary of key points

---

6. When the switches are the only time-varying elements in the converter, then circuit averaging affects only the switch network. The converter model can then be derived by simply replacing the switch network with its averaged model. Dc and small-signal ac models of several common CCM switch networks are listed in section 7.5.4. Switching losses can also be modeled using this approach.

7. The canonical circuit describes the basic properties shared by all dc-dc PWM converters operating in the continuous conduction mode. At the heart of the model is the ideal  $1:M(D)$  transformer, introduced in Chapter 3 to represent the basic dc-dc conversion function, and generalized here to include ac variations. The converter reactive elements introduce an effective low-pass filter into the network. The model also includes independent sources which represent the effect of duty cycle variations. The parameter values in the canonical models of several basic converters are tabulated for easy reference.

# Summary of key points

---

8. The conventional pulse-width modulator circuit has linear gain, dependent on the slope of the sawtooth waveform, or equivalently on its peak-to-peak magnitude.

# Chapter 8. Converter Transfer Functions

---

## 8.1. Review of Bode plots

- 8.1.1. Single pole response
- 8.1.2. Single zero response
- 8.1.3. Right half-plane zero
- 8.1.4. Frequency inversion
- 8.1.5. Combinations
- 8.1.6. Double pole response: resonance
- 8.1.7. The low-Q approximation
- 8.1.8. Approximate roots of an arbitrary-degree polynomial

## 8.2. Analysis of converter transfer functions

- 8.2.1. Example: transfer functions of the buck-boost converter
- 8.2.2. Transfer functions of some basic CCM converters
- 8.2.3. Physical origins of the right half-plane zero in converters

# Converter Transfer Functions

---

## 8.3. Graphical construction of converter transfer functions

8.3.1. Series impedances: addition of asymptotes

8.3.2. Parallel impedances: inverse addition of asymptotes

8.3.3. Another example

8.3.4. Voltage divider transfer functions: division of asymptotes

## 8.4. Measurement of ac transfer functions and impedances

## 8.5. Summary of key points



# Design-oriented analysis

---

How to approach a real (and hence, complicated) system

Problems:

- Complicated derivations

- Long equations

- Algebra mistakes

Design objectives:

- Obtain physical insight which leads engineer to synthesis of a good design

- Obtain simple equations that can be inverted, so that element values can be chosen to obtain desired behavior. Equations that cannot be inverted are useless for design!

*Design-oriented analysis* is a structured approach to analysis, which attempts to avoid the above problems

# Some elements of design-oriented analysis, discussed in this chapter

---

- Writing transfer functions in normalized form, to directly expose salient features
- Obtaining simple analytical expressions for asymptotes, corner frequencies, and other salient features, allows element values to be selected such that a given desired behavior is obtained
- Use of inverted poles and zeroes, to refer transfer function gains to the most important asymptote
- Analytical approximation of roots of high-order polynomials
- Graphical construction of Bode plots of transfer functions and polynomials, to
  - avoid algebra mistakes
  - approximate transfer functions
  - obtain insight into origins of salient features

## 8.1. Review of Bode plots

### *Decibels*

$$\|G\|_{\text{dB}} = 20 \log_{10}(\|G\|)$$

*Decibels of quantities having units (impedance example): normalize before taking log*

$$\|Z\|_{\text{dB}} = 20 \log_{10}\left(\frac{\|Z\|}{R_{\text{base}}}\right)$$

*Table 8.1. Expressing magnitudes in decibels*

<i>Actual magnitude</i>	<i>Magnitude in dB</i>
1/2	– 6dB
1	0 dB
2	6 dB
5 = 10/2	20 dB – 6 dB = 14 dB
10	20dB
1000 = 10 <sup>3</sup>	3 · 20dB = 60 dB

5Ω is equivalent to 14dB with respect to a base impedance of  $R_{\text{base}} = 1\Omega$ , also known as 14dBΩ.

60dBμA is a current 60dB greater than a base current of 1μA, or 1mA.

# Bode plot of $f^n$


Bode plots are effectively log-log plots, which cause functions which vary as  $f^n$  to become linear plots. Given:

$$\|G\| = \left(\frac{f}{f_0}\right)^n$$

Magnitude in dB is


$$\|G\|_{\text{dB}} = 20 \log_{10} \left(\frac{f}{f_0}\right)^n = 20n \log_{10} \left(\frac{f}{f_0}\right)$$

 - Slope is  $20n$  dB/decade
- Magnitude is 1, or 0dB, at frequency  $f = f_0$



## 8.1.1. Single pole response

*Simple R-C example*

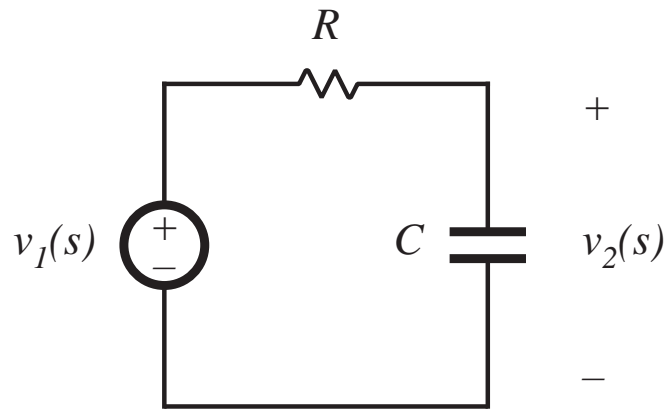

Transfer function is

$$G(s) = \frac{v_2(s)}{v_1(s)} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R}$$

Express as rational fraction:

$$G(s) = \frac{1}{1 + sRC}$$

This coincides with the normalized form

$$G(s) = \frac{1}{\left(1 + \frac{s}{\omega_0}\right)}$$

with  $\omega_0 = \frac{1}{RC}$

## $G(j\omega)$ and $\| G(j\omega) \|$

Let  $s = j\omega$ :


$$G(j\omega) = \frac{1}{\left(1 + j \frac{\omega}{\omega_0}\right)} = \frac{1 - j \frac{\omega}{\omega_0}}{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

Magnitude is

$$\begin{aligned} \| G(j\omega) \| &= \sqrt{\left[ \operatorname{Re} (G(j\omega)) \right]^2 + \left[ \operatorname{Im} (G(j\omega)) \right]^2} \\ &= \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} \end{aligned}$$

Magnitude in dB:

$$\| G(j\omega) \|_{\text{dB}} = -20 \log_{10} \left( \sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2} \right) \text{ dB}$$

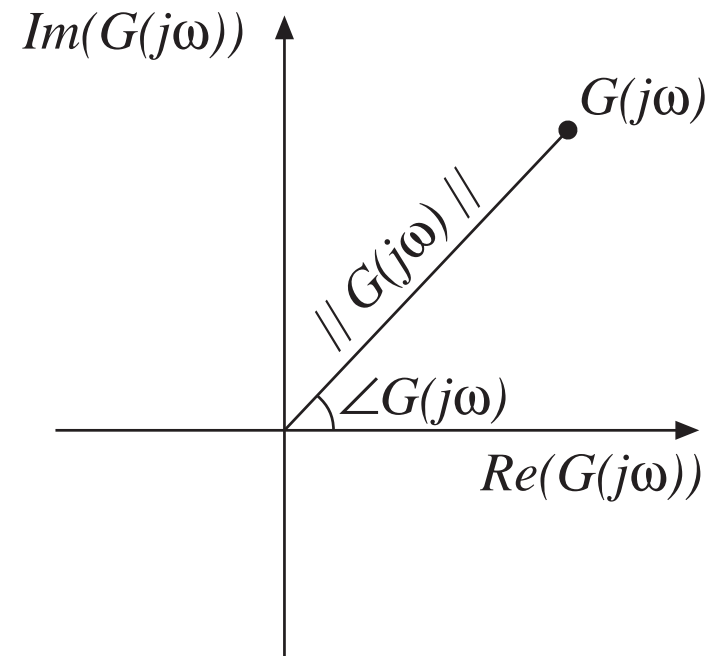

# Asymptotic behavior: low frequency

For small frequency,  
 $\omega \ll \omega_0$  and  $f \ll f_0$  :

$$\left(\frac{\omega}{\omega_0}\right) \ll 1$$

Then  $\|G(j\omega)\|$   
becomes


$$\|G(j\omega)\| \approx \frac{1}{\sqrt{1}} = 1$$

Or, in dB,

$$\|G(j\omega)\|_{\text{dB}} \approx 0\text{dB}$$

This is the low-frequency  
asymptote of  $\|G(j\omega)\|$

$$\|G(j\omega)\| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

 

# Asymptotic behavior: high frequency

For high frequency,  
 $\omega \gg \omega_0$  and  $f \gg f_0$  :


$$\left(\frac{\omega}{\omega_0}\right) \gg 1$$

$$1 + \left(\frac{\omega}{\omega_0}\right)^2 \approx \left(\frac{\omega}{\omega_0}\right)^2$$

Then  $\|G(j\omega)\|$   
becomes

$$\|G(j\omega)\| \approx \frac{1}{\sqrt{\left(\frac{\omega}{\omega_0}\right)^2}} = \left(\frac{f}{f_0}\right)^{-1}$$

$$\|G(j\omega)\| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

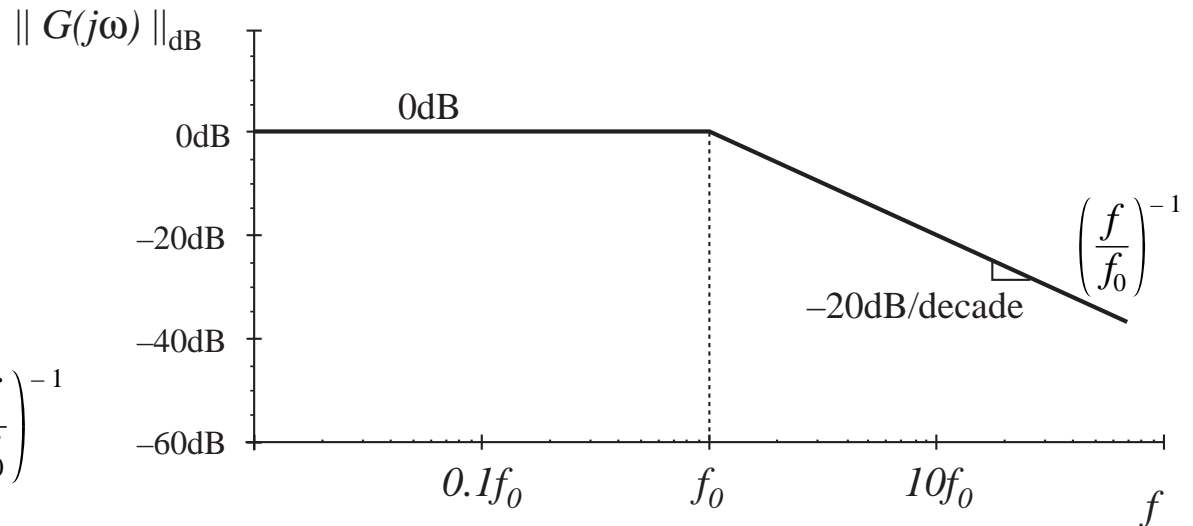

The high-frequency asymptote of  $\|G(j\omega)\|$  varies as  $f^{-1}$ .  
Hence,  $n = -1$ , and a straight-line asymptote having a  
slope of  $-20\text{dB/decade}$  is obtained. The asymptote has  
a value of 1 at  $f = f_0$  .



## Deviation of exact curve near $f = f_0$

---

Evaluate exact magnitude:

*at  $f = f_0$ :*


$$\|G(j\omega_0)\| = \frac{1}{\sqrt{1 + \left(\frac{\omega_0}{\omega_0}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\|G(j\omega_0)\|_{\text{dB}} = -20 \log_{10} \left( \sqrt{1 + \left(\frac{\omega_0}{\omega_0}\right)^2} \right) \approx -3 \text{ dB}$$


*at  $f = 0.5f_0$  and  $2f_0$ :*

Similar arguments show that the exact curve lies 1dB below the asymptotes.

# Summary: magnitude

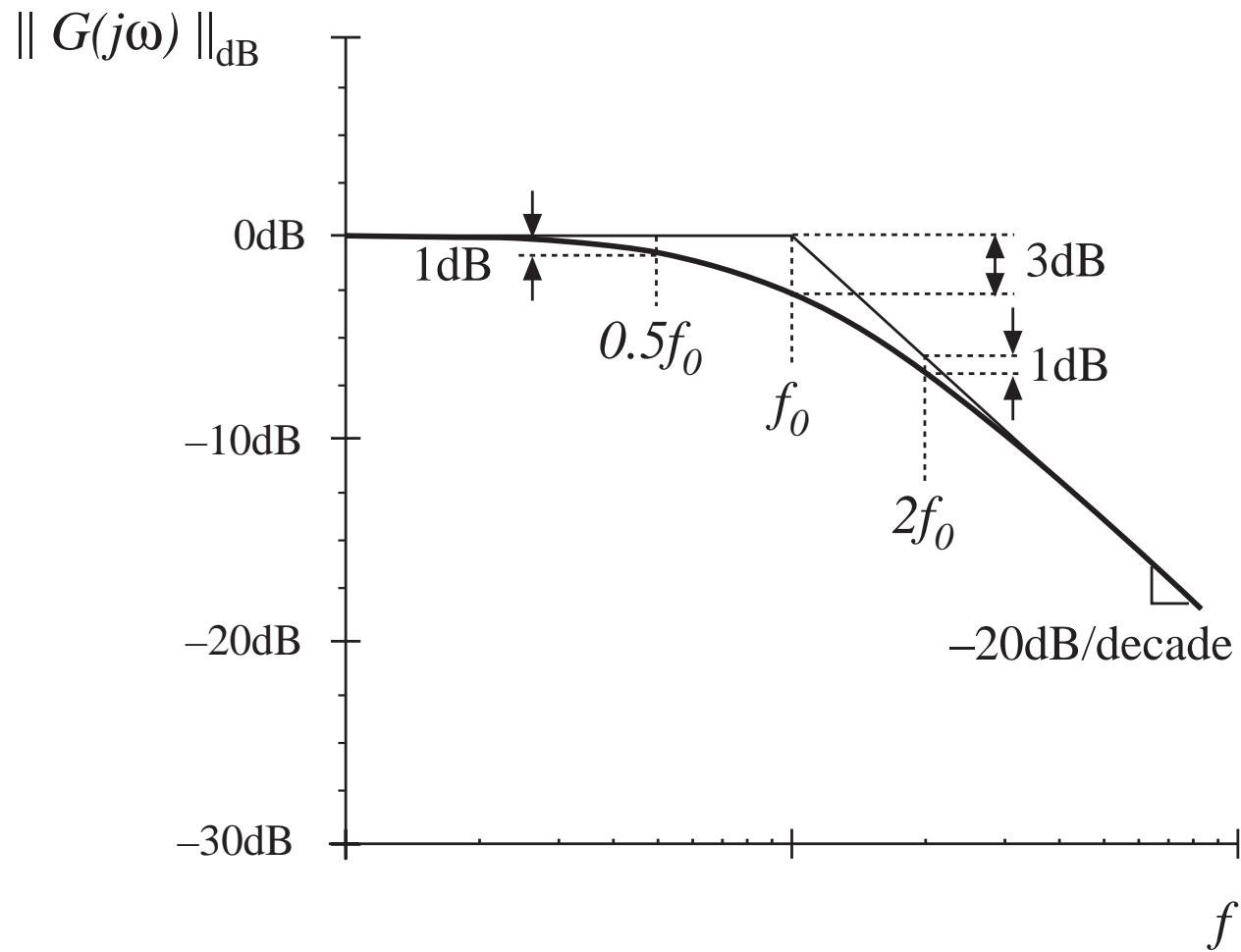


# Phase of $G(j\omega)$

 

$$G(j\omega) = \frac{1}{\left(1 + j \frac{\omega}{\omega_0}\right)} = \frac{1 - j \frac{\omega}{\omega_0}}{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

$$\angle G(j\omega) = -\tan^{-1} \left( \frac{\omega}{\omega_0} \right)$$

# Phase of $G(j\omega)$

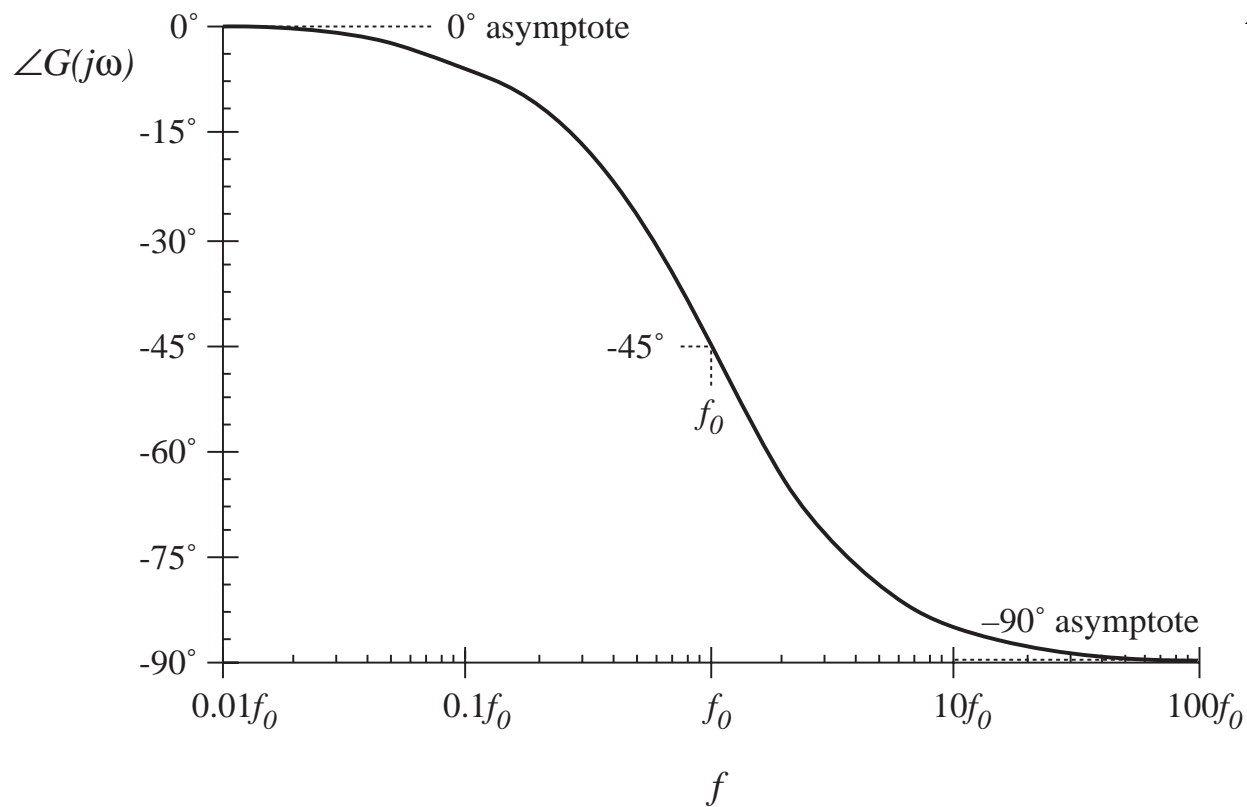

$$\angle G(j\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$\omega$	$\angle G(j\omega)$
0	$0^\circ$
$\omega_0$	$-45^\circ$
$\infty$	$-90^\circ$

# Phase asymptotes

---

Low frequency:  $0^\circ$

High frequency:  $-90^\circ$

Low- and high-frequency asymptotes do not intersect

Hence, need a midfrequency asymptote


Try a midfrequency asymptote having slope identical to actual slope at the corner frequency  $f_0$ . One can show that the asymptotes then intersect at the break frequencies

$$f_a = f_0 e^{-\pi/2} \approx f_0 / 4.81$$


$$f_b = f_0 e^{\pi/2} \approx 4.81 f_0$$
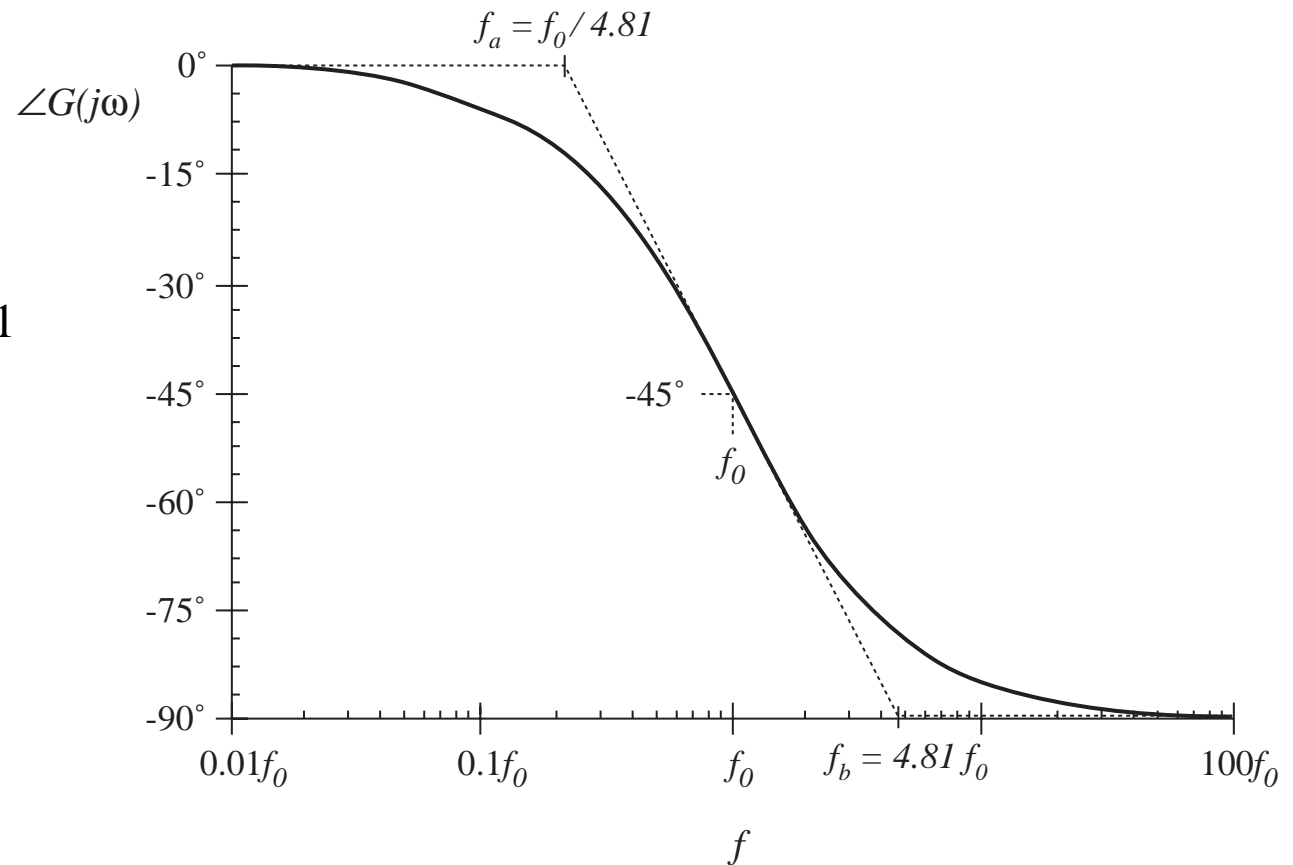
# Phase asymptotes


$$f_a = f_0 e^{-\pi/2} \approx f_0 / 4.81$$
$$f_b = f_0 e^{\pi/2} \approx 4.81 f_0$$



# Phase asymptotes: a simpler choice

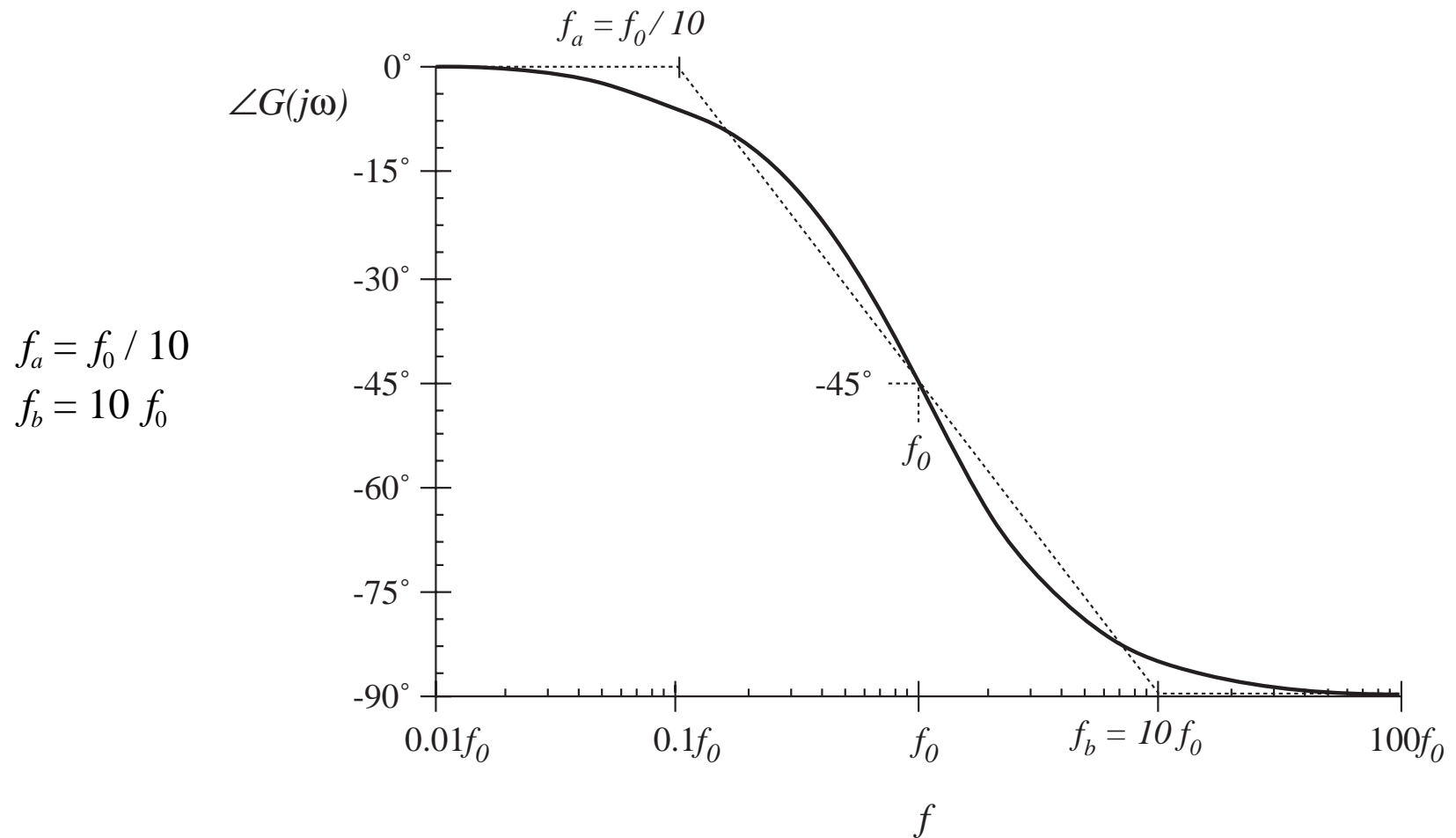

# Summary: Bode plot of real pole

 



## 8.1.2. Single zero response

---

Normalized form:

$$G(s) = \left(1 + \frac{s}{\omega_0}\right)$$

Magnitude:

$$\|G(j\omega)\| = \sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

Use arguments similar to those used for the simple pole, to derive asymptotes:

0dB at low frequency,  $\omega \ll \omega_0$

+20dB/decade slope at high frequency,  $\omega \gg \omega_0$


Phase:

$$\angle G(j\omega) = \tan^{-1} \left( \frac{\omega}{\omega_0} \right)$$

—with the exception of a missing minus sign, same as simple pole
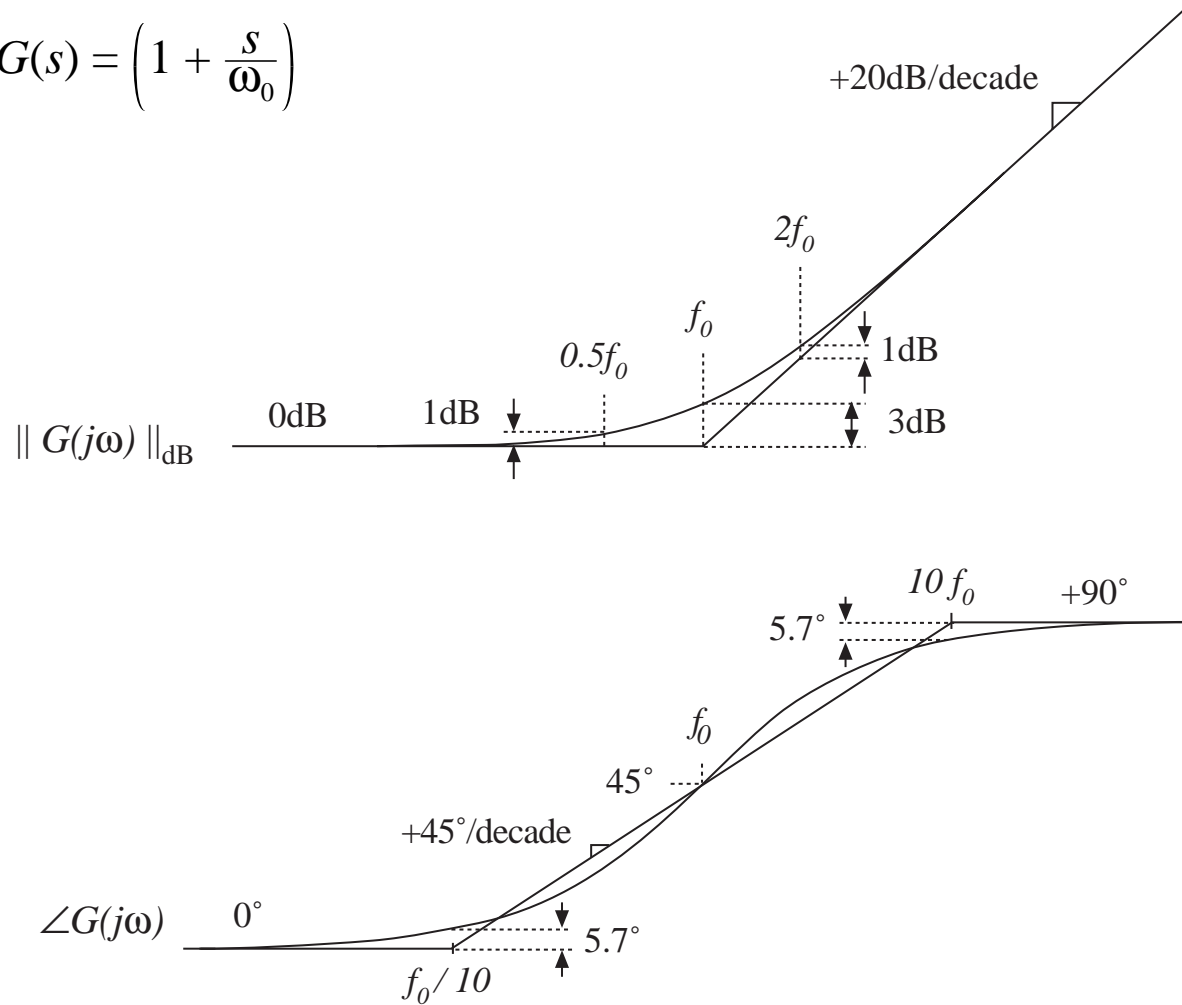
# Summary: Bode plot, real zero

$$G(s) = \left(1 + \frac{s}{\omega_0}\right)$$



### 8.1.3. Right half-plane zero

---

Normalized form:

$$G(s) = \left(1 - \frac{s}{\omega_0}\right)$$

Magnitude:

$$\|G(j\omega)\| = \sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

—same as conventional (left half-plane) zero. Hence, magnitude asymptotes are identical to those of LHP zero.

Phase:


$$\angle G(j\omega) = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

—same as real pole.

The RHP zero exhibits the magnitude asymptotes of the LHP zero, and the phase asymptotes of the pole
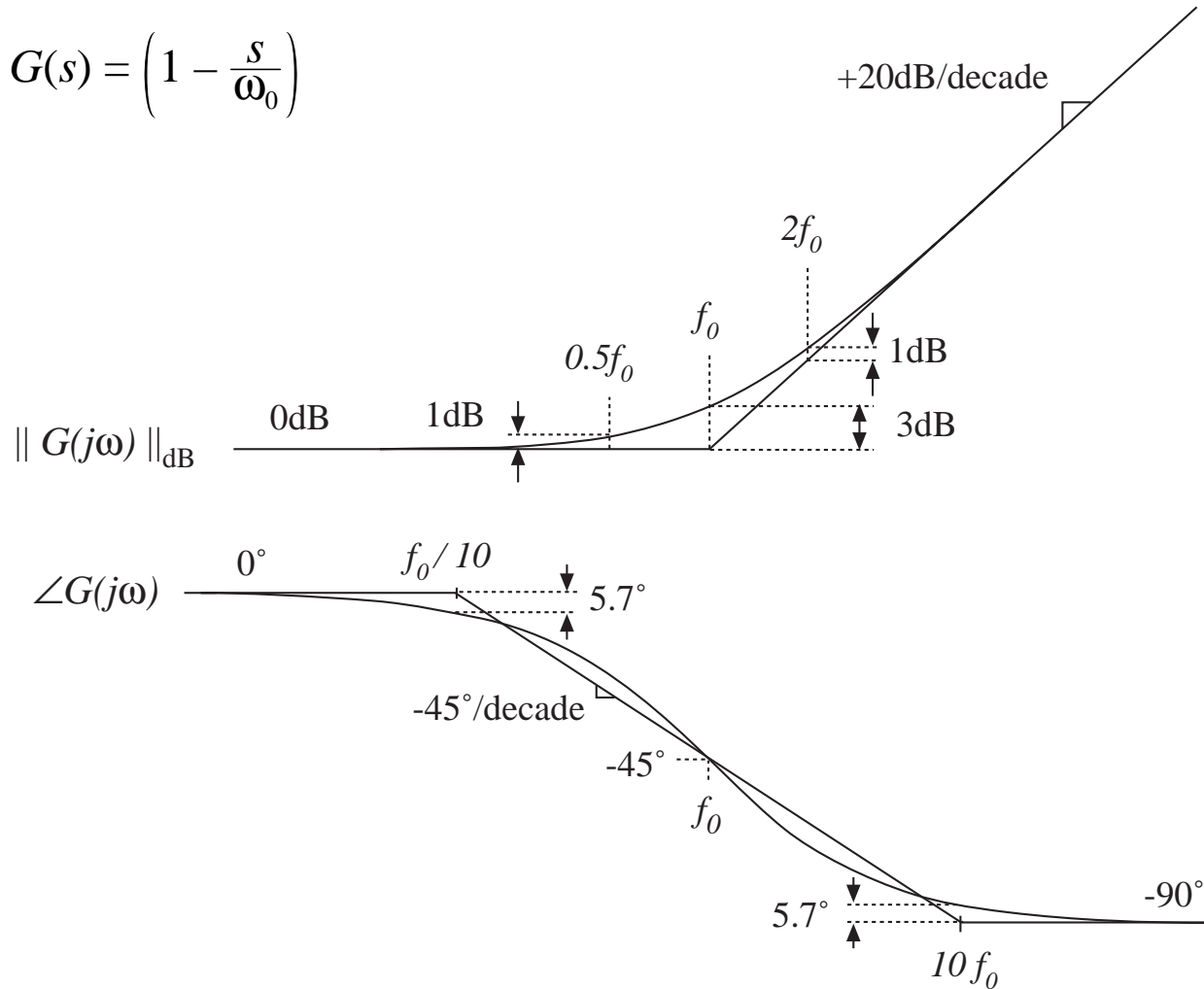
# Summary: Bode plot, RHP zero

$$G(s) = \left(1 - \frac{s}{\omega_0}\right)$$



## 8.1.4. Frequency inversion

---

Reversal of frequency axis. A useful form when describing mid- or high-frequency flat asymptotes. Normalized form, inverted pole:

$$G(s) = \frac{1}{\left(1 + \frac{\omega_0}{s}\right)}$$


An algebraically equivalent form:

$$G(s) = \frac{\left(\frac{s}{\omega_0}\right)}{\left(1 + \frac{s}{\omega_0}\right)}$$

The inverted-pole format emphasizes the high-frequency gain.
 
# Asymptotes, inverted pole

$$G(s) = \frac{1}{\left(1 + \frac{\omega_0}{s}\right)}$$



# Inverted zero

---

Normalized form, inverted zero:


$$G(s) = \left( 1 + \frac{\omega_0}{s} \right)$$

An algebraically equivalent form:

$$G(s) = \frac{\left( 1 + \frac{s}{\omega_0} \right)}{\left( \frac{s}{\omega_0} \right)}$$

Again, the inverted-zero format emphasizes the high-frequency gain.

# Asymptotes, inverted zero

 



## 8.1.5. Combinations

---

Suppose that we have constructed the Bode diagrams of two complex-valued functions of frequency,  $G_1(\omega)$  and  $G_2(\omega)$ . It is desired to construct the Bode diagram of the product,  $G_3(\omega) = G_1(\omega) G_2(\omega)$ .

Express the complex-valued functions in polar form:

$$G_1(\omega) = R_1(\omega) e^{j\theta_1(\omega)}$$

$$G_2(\omega) = R_2(\omega) e^{j\theta_2(\omega)}$$

$$G_3(\omega) = R_3(\omega) e^{j\theta_3(\omega)}$$

The product  $G_3(\omega)$  can then be written

$$G_3(\omega) = G_1(\omega) G_2(\omega) = R_1(\omega) e^{j\theta_1(\omega)} R_2(\omega) e^{j\theta_2(\omega)}$$

$$G_3(\omega) = \left( R_1(\omega) R_2(\omega) \right) e^{j(\theta_1(\omega) + \theta_2(\omega))}$$

# Combinations

---

$$G_3(\omega) = \left( R_1(\omega) R_2(\omega) \right) e^{j(\theta_1(\omega) + \theta_2(\omega))}$$

The composite phase is

$$\theta_3(\omega) = \theta_1(\omega) + \theta_2(\omega)$$

The composite magnitude is

$$R_3(\omega) = R_1(\omega) R_2(\omega)$$


$$\left| R_3(\omega) \right|_{\text{dB}} = \left| R_1(\omega) \right|_{\text{dB}} + \left| R_2(\omega) \right|_{\text{dB}}$$

Composite phase is sum of individual phases.

Composite magnitude, when expressed in dB, is sum of individual magnitudes.

 
# Example 1: $$G(s) = \frac{G_0}{\left(1 + \frac{s}{\omega_1}\right) \left(1 + \frac{s}{\omega_2}\right)}$$

with  $G_0 = 40 \Rightarrow 32 \text{ dB}$ ,  $f_1 = \omega_1/2\pi = 100 \text{ Hz}$ ,  $f_2 = \omega_2/2\pi = 2 \text{ kHz}$


 
## Example 2

Determine the transfer function  $A(s)$  corresponding to the following asymptotes:



## Example 2, continued

One solution:

$$A(s) = A_0 \frac{\left(1 + \frac{s}{\omega_1}\right)}{\left(1 + \frac{s}{\omega_2}\right)}$$

Analytical expressions for asymptotes:

$$\text{For } f < f_1 \quad \left\| A_0 \frac{\left(1 + \frac{s}{\omega_1}\right)}{\left(1 + \frac{s}{\omega_2}\right)} \right\|_{s=j\omega} = A_0 \frac{1}{1} = A_0$$

$$\text{For } f_1 < f < f_2 \quad \left\| A_0 \frac{\left(\frac{s}{\omega_1} + 1\right)}{\left(1 + \frac{s}{\omega_2}\right)} \right\|_{s=j\omega} = A_0 \frac{\left\| \frac{s}{\omega_1} \right\|_{s=j\omega}}{1} = A_0 \frac{\omega}{\omega_1} = A_0 \frac{f}{f_1}$$

## Example 2, continued

---

For  $f > f_2$

$$\left\| A_0 \frac{\left( \cancel{s} + \frac{s}{\omega_1} \right)}{\left( \cancel{s} + \frac{s}{\omega_2} \right)} \right\|_{s=j\omega} = A_0 \frac{\left\| \frac{s}{\omega_1} \right\|_{s=j\omega}}{\left\| \frac{s}{\omega_2} \right\|_{s=j\omega}} = A_0 \frac{\omega_2}{\omega_1} = A_0 \frac{f_2}{f_1}$$

So the high-frequency asymptote is

$$A_\infty = A_0 \frac{f_2}{f_1}$$

Another way to express  $A(s)$ : use inverted poles and zeroes, and express  $A(s)$  directly in terms of  $A_\infty$

$$A(s) = A_\infty \frac{\left( 1 + \frac{\omega_1}{s} \right)}{\left( 1 + \frac{\omega_2}{s} \right)}$$

## 8.1.6 Quadratic pole response: resonance

Example


$$G(s) = \frac{v_2(s)}{v_1(s)} = \frac{1}{1 + s\frac{L}{R} + s^2LC}$$

Second-order denominator, of the form

$$G(s) = \frac{1}{1 + a_1s + a_2s^2}$$

with  $a_1 = L/R$  and  $a_2 = LC$

 How should we construct the Bode diagram?



## Approach 1: factor denominator

---

$$G(s) = \frac{1}{1 + a_1 s + a_2 s^2}$$

We might factor the denominator using the quadratic formula, then construct Bode diagram as the combination of two real poles:

$$G(s) = \frac{1}{\left(1 - \frac{s}{s_1}\right) \left(1 - \frac{s}{s_2}\right)} \quad \text{with} \quad s_1 = -\frac{a_1}{2a_2} \left[ 1 - \sqrt{1 - \frac{4a_2}{a_1^2}} \right]$$
$$s_2 = -\frac{a_1}{2a_2} \left[ 1 + \sqrt{1 - \frac{4a_2}{a_1^2}} \right]$$

- If  $4a_2 \leq a_1^2$ , then the roots  $s_1$  and  $s_2$  are real. We can construct Bode diagram as the combination of two real poles.
- If  $4a_2 > a_1^2$ , then the roots are complex. In Section 8.1.1, the assumption was made that  $\omega_0$  is real; hence, the results of that section cannot be applied and we need to do some additional work.



## Approach 2: Define a standard normalized form for the quadratic case

---

$$G(s) = \frac{1}{1 + 2\zeta \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2} \quad \text{or} \quad G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

- When the coefficients of  $s$  are real and positive, then the parameters  $\zeta$ ,  $\omega_0$ , and  $Q$  are also real and positive
- The parameters  $\zeta$ ,  $\omega_0$ , and  $Q$  are found by equating the coefficients of  $s$
- The parameter  $\omega_0$  is the angular corner frequency, and we can define  $f_0 = \omega_0/2\pi$
- The parameter  $\zeta$  is called the *damping factor*.  $\zeta$  controls the shape of the exact curve in the vicinity of  $f = f_0$ . The roots are complex when  $\zeta < 1$ .
- In the alternative form, the parameter  $Q$  is called the *quality factor*.  $Q$  also controls the shape of the exact curve in the vicinity of  $f = f_0$ . The roots are complex when  $Q > 0.5$ .

# The $Q$ -factor

---

In a second-order system,  $\zeta$  and  $Q$  are related according to

$$Q = \frac{1}{2\zeta}$$

$Q$  is a measure of the dissipation in the system. A more general definition of  $Q$ , for sinusoidal excitation of a passive element or system is

$$Q = 2\pi \frac{(\text{peak stored energy})}{(\text{energy dissipated per cycle})}$$

For a second-order passive system, the two equations above are equivalent. We will see that  $Q$  has a simple interpretation in the Bode diagrams of second-order transfer functions.

## Analytical expressions for $f_0$ and $Q$

---

Two-pole low-pass filter  
example: we found that

$$G(s) = \frac{v_2(s)}{v_1(s)} = \frac{1}{1 + s\frac{L}{R} + s^2LC}$$

Equate coefficients of like  
powers of  $s$  with the  
standard form

$$G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Result:

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$
$$Q = R\sqrt{\frac{C}{L}}$$

# Magnitude asymptotes, quadratic form


In the form  $G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$

let  $s = j\omega$  and find magnitude:  $\|G(j\omega)\| = \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \frac{1}{Q^2} \left(\frac{\omega}{\omega_0}\right)^2}}$

Asymptotes are

$$\|G\| \rightarrow 1 \quad \text{for } \omega \ll \omega_0$$

$$\|G\| \rightarrow \left(\frac{f}{f_0}\right)^{-2} \quad \text{for } \omega \gg \omega_0$$

 


## Deviation of exact curve from magnitude asymptotes

$$\|G(j\omega)\| = \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \frac{1}{Q^2} \left(\frac{\omega}{\omega_0}\right)^2}}$$



At  $\omega = \omega_0$ , the exact magnitude is

$$\|G(j\omega_0)\| = Q \quad \text{or, in dB:} \quad \|G(j\omega_0)\|_{\text{dB}} = |Q|_{\text{dB}}$$

The exact curve has magnitude  $Q$  at  $f = f_0$ . The deviation of the exact curve from the asymptotes is  $|Q|_{\text{dB}}$

 

# Two-pole response: exact curves

  

## 8.1.7. The low- $Q$ approximation

---

Given a second-order denominator polynomial, of the form

$$G(s) = \frac{1}{1 + a_1 s + a_2 s^2} \quad \text{or} \quad G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

When the roots are real, i.e., when  $Q < 0.5$ , then we can factor the denominator, and construct the Bode diagram using the asymptotes for real poles. We would then use the following normalized form:

$$G(s) = \frac{1}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)}$$


This is a particularly desirable approach when  $Q \ll 0.5$ , i.e., when the corner frequencies  $\omega_1$  and  $\omega_2$  are well separated.

# An example

A problem with this procedure is the complexity of the quadratic formula used to find the corner frequencies.

R-L-C network example:
 
$$G(s) = \frac{v_2(s)}{v_1(s)} = \frac{1}{1 + s\frac{L}{R} + s^2LC}$$



Use quadratic formula to factor denominator. Corner frequencies are:

$$\omega_1, \omega_2 = \frac{L/R \pm \sqrt{(L/R)^2 - 4LC}}{2LC}$$



# Factoring the denominator

---

$$\omega_1, \omega_2 = \frac{L/R \pm \sqrt{(L/R)^2 - 4LC}}{2LC}$$

This complicated expression yields little insight into how the corner frequencies  $\omega_1$  and  $\omega_2$  depend on  $R$ ,  $L$ , and  $C$ .

When the corner frequencies are well separated in value, it can be shown that they are given by the much simpler (approximate) expressions

$$\omega_1 \approx \frac{R}{L}, \quad \omega_2 \approx \frac{1}{RC}$$

$\omega_1$  is then independent of  $C$ , and  $\omega_2$  is independent of  $L$ .

These simpler expressions can be derived via the Low- $Q$  Approximation.

# Derivation of the Low- $Q$ Approximation

---

Given

$$G(s) = \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Use quadratic formula to express corner frequencies  $\omega_1$  and  $\omega_2$  in terms of  $Q$  and  $\omega_0$  as:

$$\omega_1 = \frac{\omega_0}{Q} \frac{1 - \sqrt{1 - 4Q^2}}{2}$$

$$\omega_2 = \frac{\omega_0}{Q} \frac{1 + \sqrt{1 - 4Q^2}}{2}$$

## Corner frequency $\omega_2$

$$\omega_2 = \frac{\omega_0}{Q} \frac{1 + \sqrt{1 - 4Q^2}}{2}$$

can be written in the form

$$\omega_2 = \frac{\omega_0}{Q} F(Q)$$


where

$$F(Q) = \frac{1}{2} \left( 1 + \sqrt{1 - 4Q^2} \right)$$

For small  $Q$ ,  $F(Q)$  tends to 1.

We then obtain
 
$$\omega_2 \approx \frac{\omega_0}{Q} \quad \text{for } Q \ll \frac{1}{2}$$



For  $Q < 0.3$ , the approximation  $F(Q) = 1$  is within 10% of the exact value.

## Corner frequency $\omega_1$

$$\omega_1 = \frac{\omega_0}{Q} \frac{1 - \sqrt{1 - 4Q^2}}{2}$$

can be written in the form

$$\omega_1 = \frac{Q \omega_0}{F(Q)}$$


where

$$F(Q) = \frac{1}{2} \left( 1 + \sqrt{1 - 4Q^2} \right)$$

For small  $Q$ ,  $F(Q)$  tends to 1.


We then obtain
 
$$\omega_1 \approx Q \omega_0 \quad \text{for } Q \ll \frac{1}{2}$$



For  $Q < 0.3$ , the approximation  $F(Q) = 1$  is within 10% of the exact value.

# The Low-Q Approximation

 

## *R-L-C Example*

---

For the previous example:

$$G(s) = \frac{v_2(s)}{v_1(s)} = \frac{1}{1 + s\frac{L}{R} + s^2LC}$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$
$$Q = R\sqrt{\frac{C}{L}}$$

Use of the Low- $Q$  Approximation leads to

$$\omega_1 \approx Q \omega_0 = R \sqrt{\frac{C}{L}} \frac{1}{\sqrt{LC}} = \frac{R}{L}$$
$$\omega_2 \approx \frac{\omega_0}{Q} = \frac{1}{\sqrt{LC}} \frac{1}{R\sqrt{\frac{C}{L}}} = \frac{1}{RC}$$

## 8.2. Analysis of converter transfer functions

---

- 8.2.1. Example: transfer functions of the buck-boost converter
- 8.2.2. Transfer functions of some basic CCM converters
- 8.2.3. Physical origins of the right half-plane zero in converters

## 8.2.1. Example: transfer functions of the buck-boost converter

---

Small-signal ac equations of the buck-boost converter, derived in section 7.2:

$$L \frac{d\hat{i}(t)}{dt} = D\hat{v}_g(t) + D'\hat{v}(t) + (V_g - V)\hat{d}(t)$$

$$C \frac{d\hat{v}(t)}{dt} = -D'\hat{i}(t) - \frac{\hat{v}(t)}{R} + I\hat{d}(t)$$

$$\hat{i}_g(t) = D\hat{i}(t) + I\hat{d}(t)$$



# Definition of transfer functions

---

The converter contains two inputs,  $\hat{d}(s)$  and  $\hat{v}_g(s)$  and one output,  $\hat{v}(s)$

Hence, the ac output voltage variations can be expressed as the superposition of terms arising from the two inputs:

$$\hat{v}(s) = G_{vd}(s) \hat{d}(s) + G_{vg}(s) \hat{v}_g(s)$$

The control-to-output and line-to-output transfer functions can be defined as

$$G_{vd}(s) = \left. \frac{\hat{v}(s)}{\hat{d}(s)} \right|_{\hat{v}_g(s)=0} \quad \text{and} \quad G_{vg}(s) = \left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\hat{d}(s)=0}$$

# Derivation of transfer functions

---

## *Algebraic approach*

Take Laplace transform of converter equations, letting initial conditions be zero:

$$sL\hat{i}(s) = D\hat{v}_g(s) + D'\hat{v}(s) + (V_g - V)\hat{d}(s)$$

$$sC\hat{v}(s) = -D'\hat{i}(s) - \frac{\hat{v}(s)}{R} + I\hat{d}(s)$$

Eliminate  $\hat{i}(s)$ , and solve for  $\hat{v}(s)$

$$\hat{i}(s) = \frac{D\hat{v}_g(s) + D'\hat{v}(s) + (V_g - V)\hat{d}(s)}{sL}$$

# Derivation of transfer functions

---

$$sC\hat{v}(s) = -\frac{D'}{sL} \left( D\hat{v}_g(s) + D'\hat{v}(s) + (V_g - V) \hat{d}(s) \right) - \frac{\hat{v}(s)}{R} + I\hat{d}(s)$$

$$\hat{v}(s) = \frac{-DD'}{D'^2 + s\frac{L}{R} + s^2 LC} \hat{v}_g(s) - \frac{V_g - V - sLI}{D'^2 + s\frac{L}{R} + s^2 LC} \hat{d}(s)$$

write in normalized form:

$$\hat{v}(s) = \left( -\frac{D}{D'} \right) \frac{1}{1 + s\frac{L}{D'^2 R} + s^2 \frac{LC}{D'^2}} \hat{v}_g(s) - \left( \frac{V_g - V}{D'^2} \right) \frac{\left( 1 - s\frac{LI}{V_g - V} \right)}{1 + s\frac{L}{D'^2 R} + s^2 \frac{LC}{D'^2}} \hat{d}(s)$$

# Derivation of transfer functions

---

Hence, the line-to-output transfer function is

$$G_{vg}(s) = \left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\hat{d}(s)=0} = \left( -\frac{D}{D'} \right) \frac{1}{1 + s \frac{L}{D'^2 R} + s^2 \frac{LC}{D'^2}}$$

which is of the following standard form:

$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{s}{Q\omega_0} + \left( \frac{s}{\omega_0} \right)^2}$$

## Salient features of the line-to-output transfer function

---

Equate standard form to derived transfer function, to determine expressions for the salient features:

$$G_{s0} = -\frac{D}{D'}$$

$$\frac{1}{\omega_0^2} = \frac{LC}{D'^2}$$

$$\omega_0 = \frac{D'}{\sqrt{LC}}$$

$$\frac{1}{Q\omega_0} = \frac{L}{D'^2 R}$$

$$Q = D'R \sqrt{\frac{C}{L}}$$

# Control-to-output transfer function

---

$$G_{vd}(s) = \left. \frac{\hat{v}(s)}{\hat{d}(s)} \right|_{\hat{v}_g(s)=0} = \left( -\frac{V_g - V}{D'^2} \right) \frac{\left( 1 - s \frac{LI}{V_g - V} \right)}{\left( 1 + s \frac{L}{D'^2 R} + s^2 \frac{LC}{D'^2} \right)}$$

Standard form:

$$G_{vd}(s) = G_{d0} \frac{\left( 1 - \frac{s}{\omega_z} \right)}{\left( 1 + \frac{s}{Q\omega_0} + \left( \frac{s}{\omega_0} \right)^2 \right)}$$

## Salient features of control-to-output transfer function

---

$$G_{d0} = -\frac{V_g - V}{D'^2} = -\frac{V_g}{D'^3} = \frac{V}{D D'^2}$$

$$\omega_z = \frac{V_g - V}{L I} = \frac{D' R}{D L} \quad (\text{RHP})$$

$$\omega_0 = \frac{D'}{\sqrt{LC}}$$

$$Q = D' R \sqrt{\frac{C}{L}}$$

— Simplified using the dc relations:

$$V = -\frac{D}{D'} V_g$$
$$I = -\frac{V}{D' R}$$

## Plug in numerical values

---

Suppose we are given the following numerical values:

$$D = 0.6$$

$$R = 10\Omega$$

$$V_g = 30V$$

$$L = 160\mu H$$

$$C = 160\mu F$$

Then the salient features have the following numerical values:

$$|G_{g0}| = \frac{D}{D'} = 1.5 \Rightarrow 3.5\text{dB}$$

$$|G_{d0}| = \frac{|V|}{D D'^2} = 469V \Rightarrow 53.4\text{dBV}$$


$$f_0 = \frac{\omega_0}{2\pi} = \frac{D'}{2\pi\sqrt{LC}} = 400\text{Hz}$$

$$Q = D'R\sqrt{\frac{C}{L}} = 4 \Rightarrow 12\text{dB}$$


$$f_z = \frac{\omega_z}{2\pi} = \frac{D'R}{2\pi DL} = 6.6\text{kHz}$$


 
# Bode plot: control-to-output transfer function


 
# Bode plot: line-to-output transfer function



## 8.2.2. Transfer functions of some basic CCM converters

Table 8.2. Salient features of the small-signal CCM transfer functions of some basic dc-dc converters

Converter	$G_{g0}$	$G_{d0}$	$\omega_0$	$Q$	$\omega_z$
buck	$D$	$\frac{V}{D}$	$\frac{1}{\sqrt{LC}}$	$R \sqrt{\frac{C}{L}}$	$\infty$
boost	$\frac{1}{D'}$	$\frac{V}{D'}$	$\frac{D'}{\sqrt{LC}}$	$D'R \sqrt{\frac{C}{L}}$	$\frac{D'^2 R}{L}$
buck-boost	$-\frac{D}{D'}$	$\frac{V}{D D'^2}$	$\frac{D'}{\sqrt{LC}}$	$D'R \sqrt{\frac{C}{L}}$	$\frac{D'^2 R}{D L}$

where the transfer functions are written in the standard forms


$$G_{vd}(s) = G_{d0} \frac{\left(1 - \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2\right)}$$

$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$
 
### 8.2.3. Physical origins of the right half-plane zero

---

$$G(s) = \left(1 - \frac{s}{\omega_0}\right)$$




- *phase reversal at high frequency*
- *transient response: output initially tends in wrong direction*


# Two converters whose CCM control-to-output transfer functions exhibit RHP zeroes

$$\langle i_D \rangle_{T_s} = d' \langle i_L \rangle_{T_s}$$

*Boost*

 


*Buck-boost*

 

 
# Waveforms, step increase in duty cycle

$$\langle i_D \rangle_{T_s} = d' \langle i_L \rangle_{T_s}$$


- Increasing  $d(t)$  causes the average diode current to initially decrease
- As inductor current increases to its new equilibrium value, average diode current eventually increases



# Impedance graph paper

 

 
# Transfer functions predicted by canonical model






# Output impedance $Z_{out}$ : set sources to zero

---

 


$$Z_{out} = Z_1 \parallel Z_2$$

 
# Graphical construction of output impedance



 
# Graphical construction of filter effective transfer function


 
## Boost and buck-boost converters: $L_e = L / D'^2$


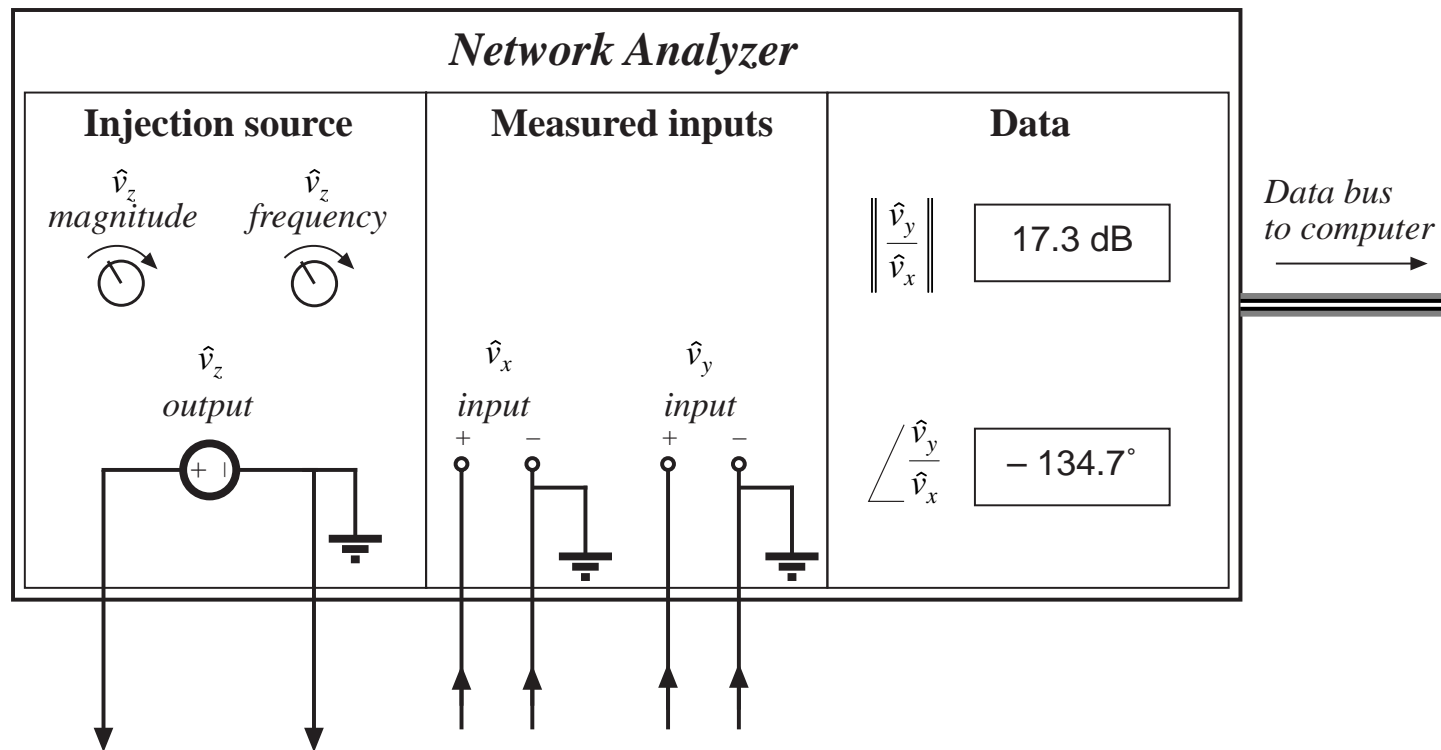
## 8.4. Measurement of ac transfer functions and impedances



# Swept sinusoidal measurements

---

- Injection source produces sinusoid  $\hat{v}_z$  of controllable amplitude and frequency
- Signal inputs  $\hat{v}_x$  and  $\hat{v}_y$  perform function of narrowband tracking voltmeter:


Component of input at injection source frequency is measured

Narrowband function is essential: switching harmonics and other noise components are removed

- Network analyzer measures


$$\left\| \frac{\hat{v}_y}{\hat{v}_x} \right\| \quad \text{and} \quad \angle \frac{\hat{v}_y}{\hat{v}_x}$$

# Measurement of an ac transfer function

 

- Potentiometer establishes correct quiescent operating point
- Injection sinusoid coupled to device input via dc blocking capacitor
- Actual device input and output voltages are measured as  $\hat{v}_x$  and  $\hat{v}_y$
- Dynamics of blocking capacitor are irrelevant

# Measurement of an output impedance

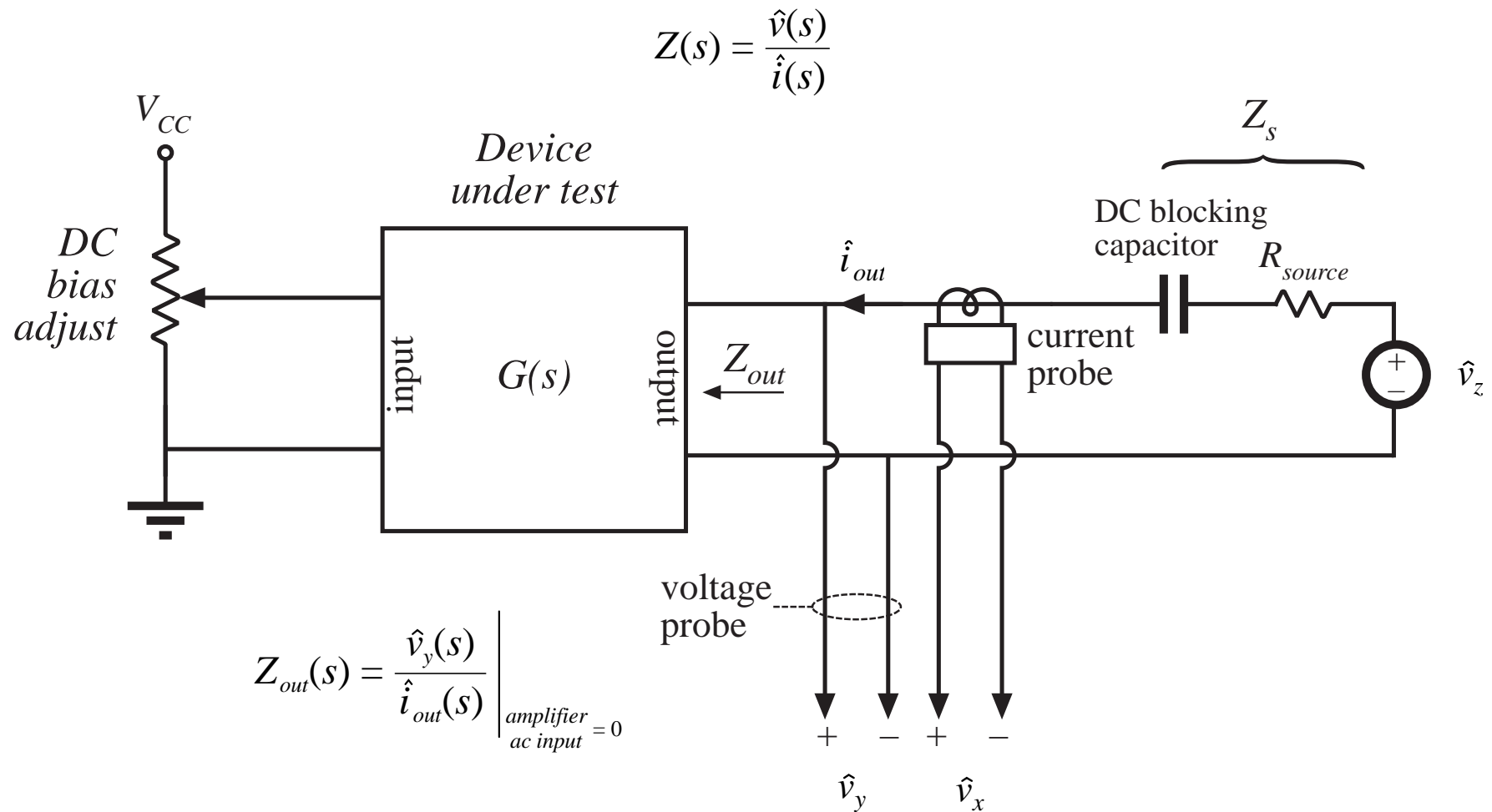



# Measurement of output impedance

---

- Treat output impedance as transfer function from output current to output voltage:

$$Z(s) = \frac{\hat{v}(s)}{\hat{i}(s)} \qquad Z_{out}(s) = \frac{\hat{v}_y(s)}{\hat{i}_{out}(s)} \bigg|_{\substack{\text{amplifier} \\ \text{ac input} = 0}}$$

- Potentiometer at device input port establishes correct quiescent operating point
- Current probe produces voltage proportional to current; this voltage is connected to network analyzer channel  $\hat{v}_x$
- Network analyzer result must be multiplied by appropriate factor, to account for scale factors of current and voltage probes

# Measurement of small impedances


Grounding problems cause measurement to fail:

Injection current can return to analyzer via two paths. Injection current which returns via voltage probe ground induces voltage drop in voltage probe, corrupting the measurement. Network analyzer measures

$$Z + (1 - k) Z_{probe} = Z + Z_{probe} \parallel Z_{rz}$$


For an accurate measurement, require

$$\|Z\| \gg \|(Z_{probe} \parallel Z_{rz})\|$$

 
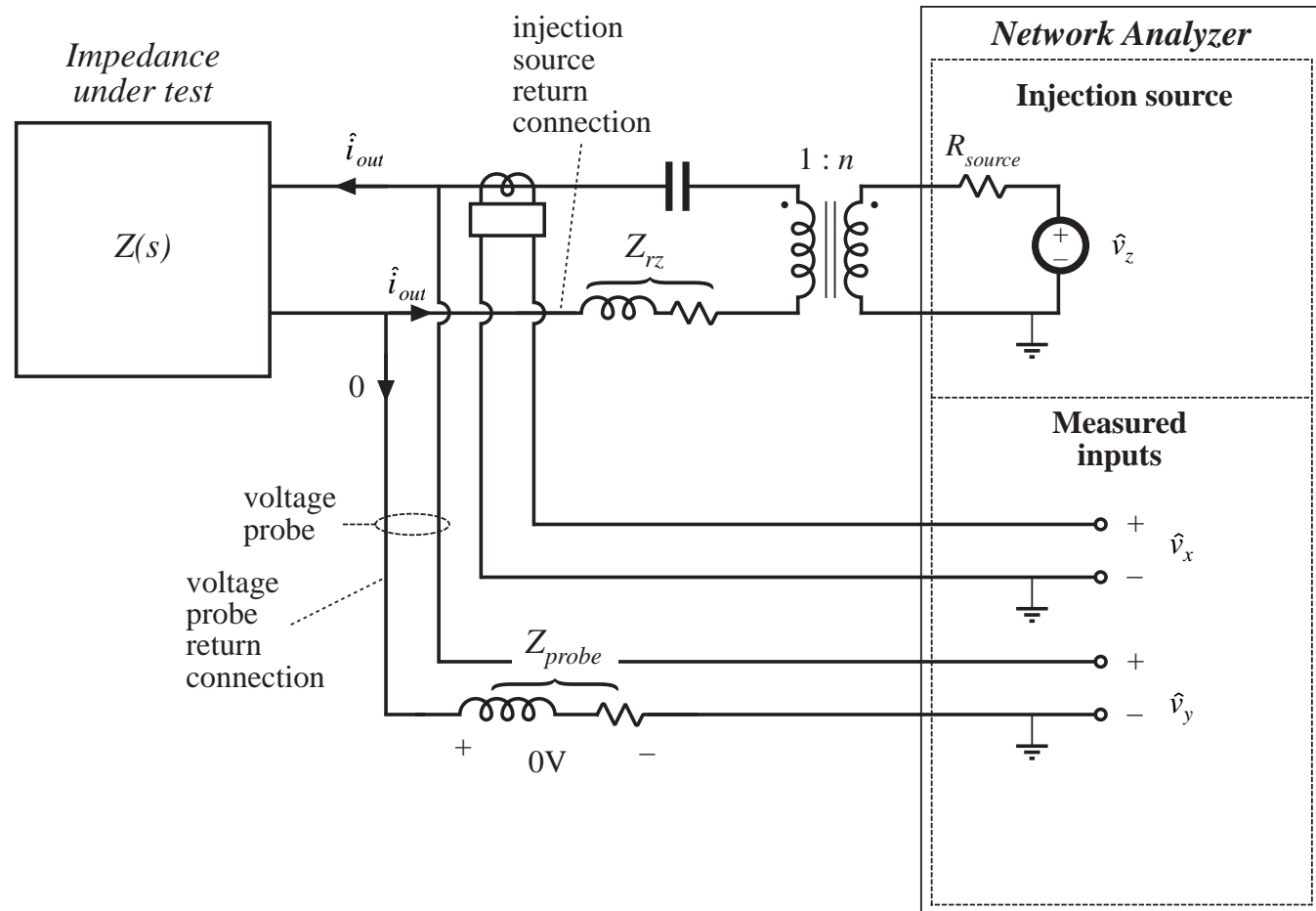
# Improved measurement: add isolation transformer

Injection current must now return entirely through transformer. No additional voltage is induced in voltage probe ground connection



## 8.5. Summary of key points

---

1. The magnitude Bode diagrams of functions which vary as  $(f/f_0)^n$  have slopes equal to  $20n$  dB per decade, and pass through 0dB at  $f = f_0$ .
2. It is good practice to express transfer functions in normalized pole-zero form; this form directly exposes expressions for the salient features of the response, i.e., the corner frequencies, reference gain, etc.
3. The right half-plane zero exhibits the magnitude response of the left half-plane zero, but the phase response of the pole.
4. Poles and zeroes can be expressed in frequency-inverted form, when it is desirable to refer the gain to a high-frequency asymptote.

## Summary of key points

---

5. A two-pole response can be written in the standard normalized form of Eq. (8-53). When  $Q > 0.5$ , the poles are complex conjugates. The magnitude response then exhibits peaking in the vicinity of the corner frequency, with an exact value of  $Q$  at  $f = f_0$ . High  $Q$  also causes the phase to change sharply near the corner frequency.
6. When the  $Q$  is less than 0.5, the two pole response can be plotted as two real poles. The low-  $Q$  approximation predicts that the two poles occur at frequencies  $f_0 / Q$  and  $Qf_0$ . These frequencies are within 10% of the exact values for  $Q \leq 0.3$ .
7. The low-  $Q$  approximation can be extended to find approximate roots of an arbitrary degree polynomial. Approximate analytical expressions for the salient features can be derived. Numerical values are used to justify the approximations.

## Summary of key points

---

8. Salient features of the transfer functions of the buck, boost, and buck-boost converters are tabulated in section 8.2.2. The line-to-output transfer functions of these converters contain two poles. Their control-to-output transfer functions contain two poles, and may additionally contain a right half-plane zero.
9. Approximate magnitude asymptotes of impedances and transfer functions can be easily derived by graphical construction. This approach is a useful supplement to conventional analysis, because it yields physical insight into the circuit behavior, and because it exposes suitable approximations. Several examples, including the impedances of basic series and parallel resonant circuits and the transfer function  $H_e(s)$  of the boost and buck-boost converters, are worked in section 8.3.
10. Measurement of transfer functions and impedances using a network analyzer is discussed in section 8.4. Careful attention to ground connections is important when measuring small impedances.

# Chapter 9. Controller Design

---

## 9.1. Introduction

## 9.2. Effect of negative feedback on the network transfer functions

9.2.1. Feedback reduces the transfer function from disturbances to the output

9.2.2. Feedback causes the transfer function from the reference input to the output to be insensitive to variations in the gains in the forward path of the loop

## 9.3. Construction of the important quantities $1/(1+T)$ and $T/(1+T)$ and the closed-loop transfer functions

# Controller design

---

## 9.4. Stability

- 9.4.1. The phase margin test
- 9.4.2. The relation between phase margin and closed-loop damping factor
- 9.4.3. Transient response vs. damping factor

## 9.5. Regulator design

- 9.5.1. Lead (PD) compensator
- 9.5.2. Lag (PI) compensator
- 9.5.3. Combined (PID) compensator
- 9.5.4. Design example



# Controller design

---

## 9.6. Measurement of loop gains


9.6.1. Voltage injection

9.6.2. Current injection

9.6.3. Measurement of unstable systems

## 9.7. Summary of key points

## 9.1. Introduction

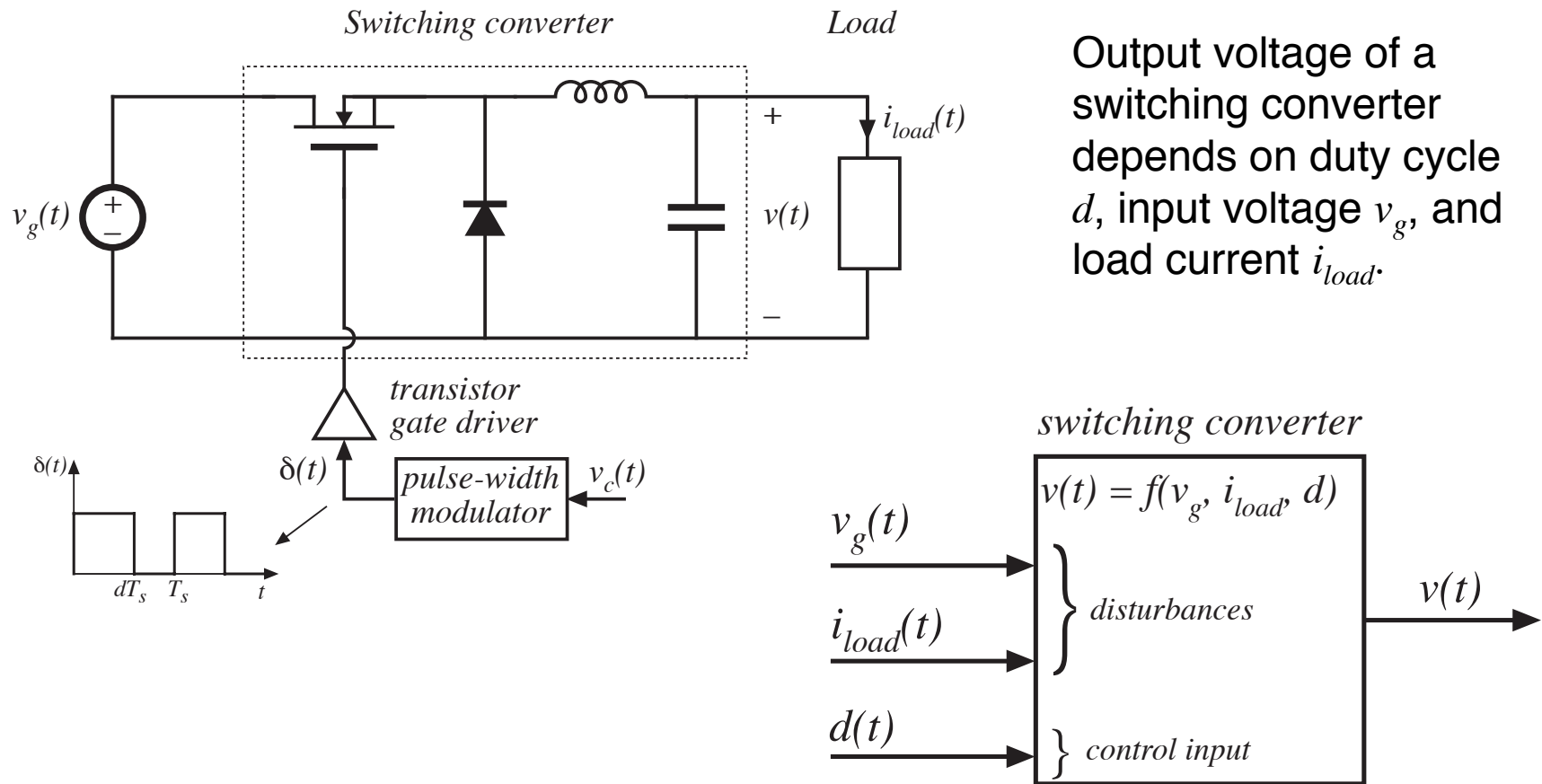


# The dc regulator application

---

Objective: maintain constant output voltage  $v(t) = V$ , in spite of disturbances in  $v_g(t)$  and  $i_{load}(t)$ .

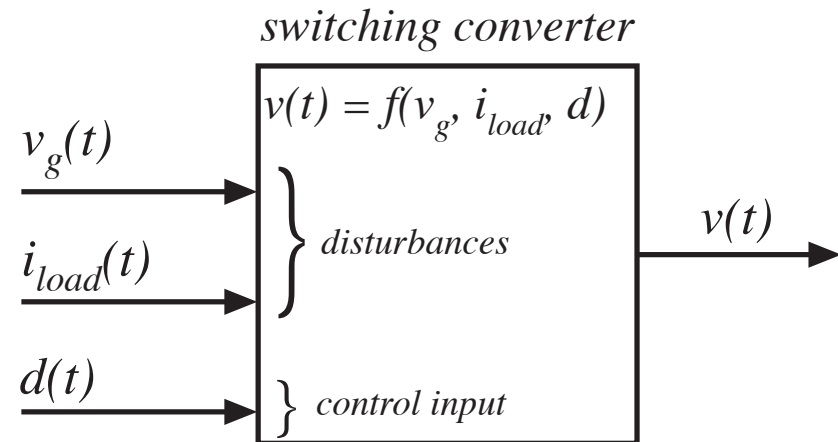Typical variation in  $v_g(t)$ : 100Hz or 120Hz ripple, produced by rectifier circuit.



Load current variations: a significant step-change in load current, such as from 50% to 100% of rated value, may be applied.

A typical output voltage regulation specification:  $5V \pm 0.1V$ .

Circuit elements are constructed to some specified tolerance. In high volume manufacturing of converters, all output voltages must meet specifications.


# The dc regulator application

---


So we cannot expect to set the duty cycle to a single value, and obtain a given constant output voltage under all conditions.

Negative feedback: build a circuit that automatically adjusts the duty cycle as necessary, to obtain the specified output voltage with high accuracy, regardless of disturbances or component tolerances.
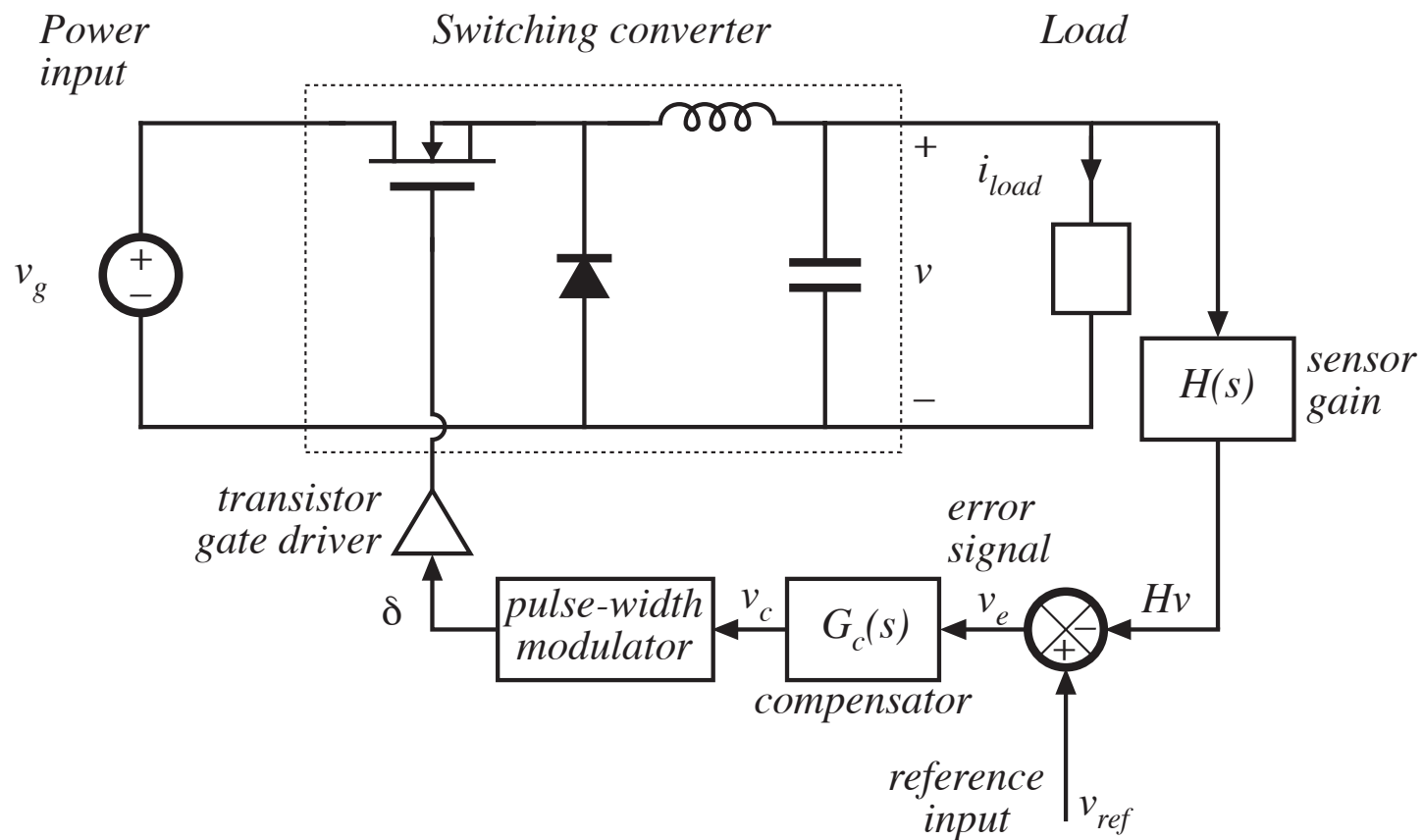
# Negative feedback: a switching regulator system




# Negative feedback

 

## 9.2. Effect of negative feedback on the network transfer functions

Small signal model: open-loop converter

 

Output voltage can be expressed as

$$\hat{v}(s) = G_{vd}(s) \hat{d}(s) + G_{vg}(s) \hat{v}_g(s) \pm Z_{out}(s) \hat{i}_{load}(s)$$

where

$$G_{vd}(s) = \left. \frac{\hat{v}(s)}{\hat{d}(s)} \right|_{\substack{\hat{v}_g = 0 \\ \hat{i}_{load} = 0}} \quad G_{vg}(s) = \left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\substack{\hat{d} = 0 \\ \hat{i}_{load} = 0}} \quad Z_{out}(s) = \pm \left. \frac{\hat{v}(s)}{\hat{i}_{load}(s)} \right|_{\substack{\hat{d} = 0 \\ \hat{v}_g = 0}}$$


# Voltage regulator system small-signal model

- Use small-signal converter model
- Perturb and linearize remainder of feedback loop:

$$v_{ref}(t) = V_{ref} + \hat{v}_{ref}(t)$$


$$v_e(t) = V_e + \hat{v}_e(t)$$

*etc.*

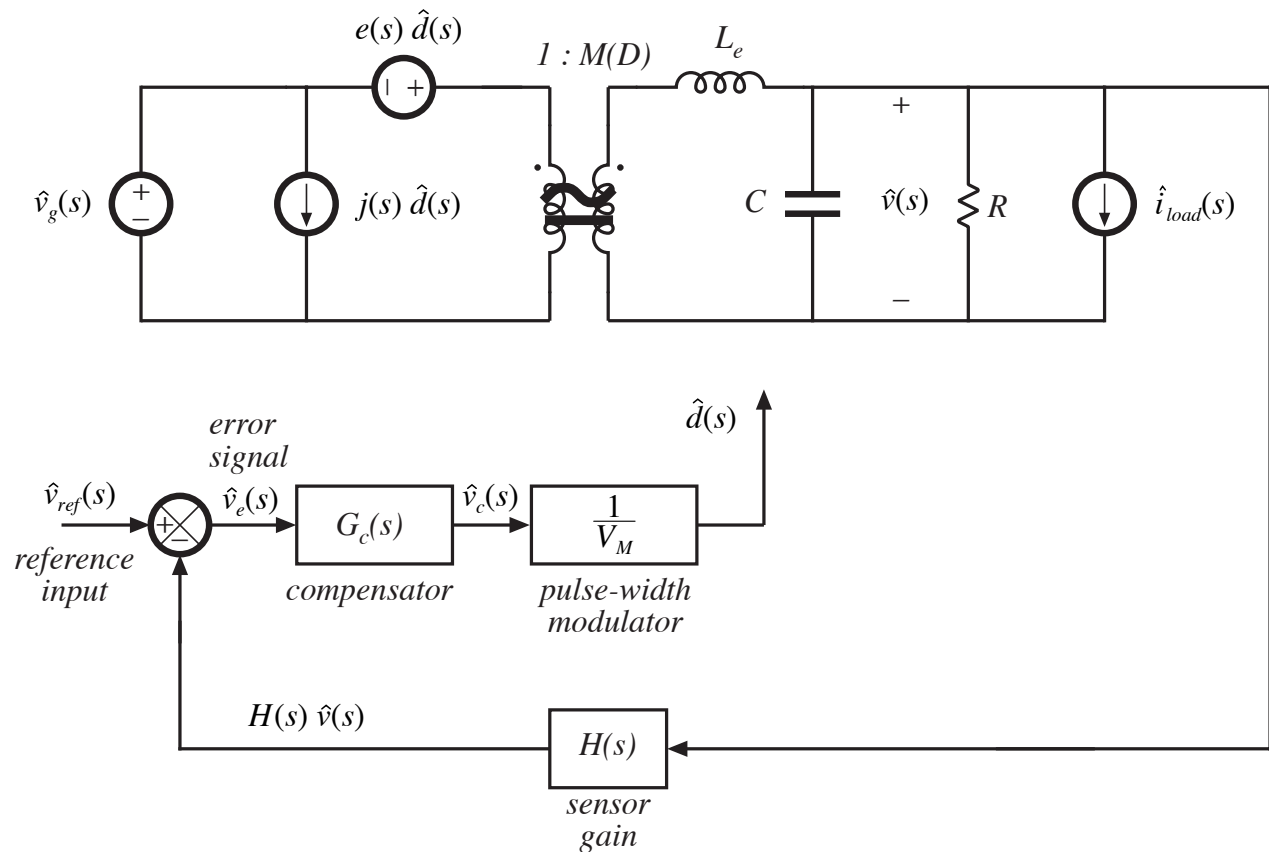


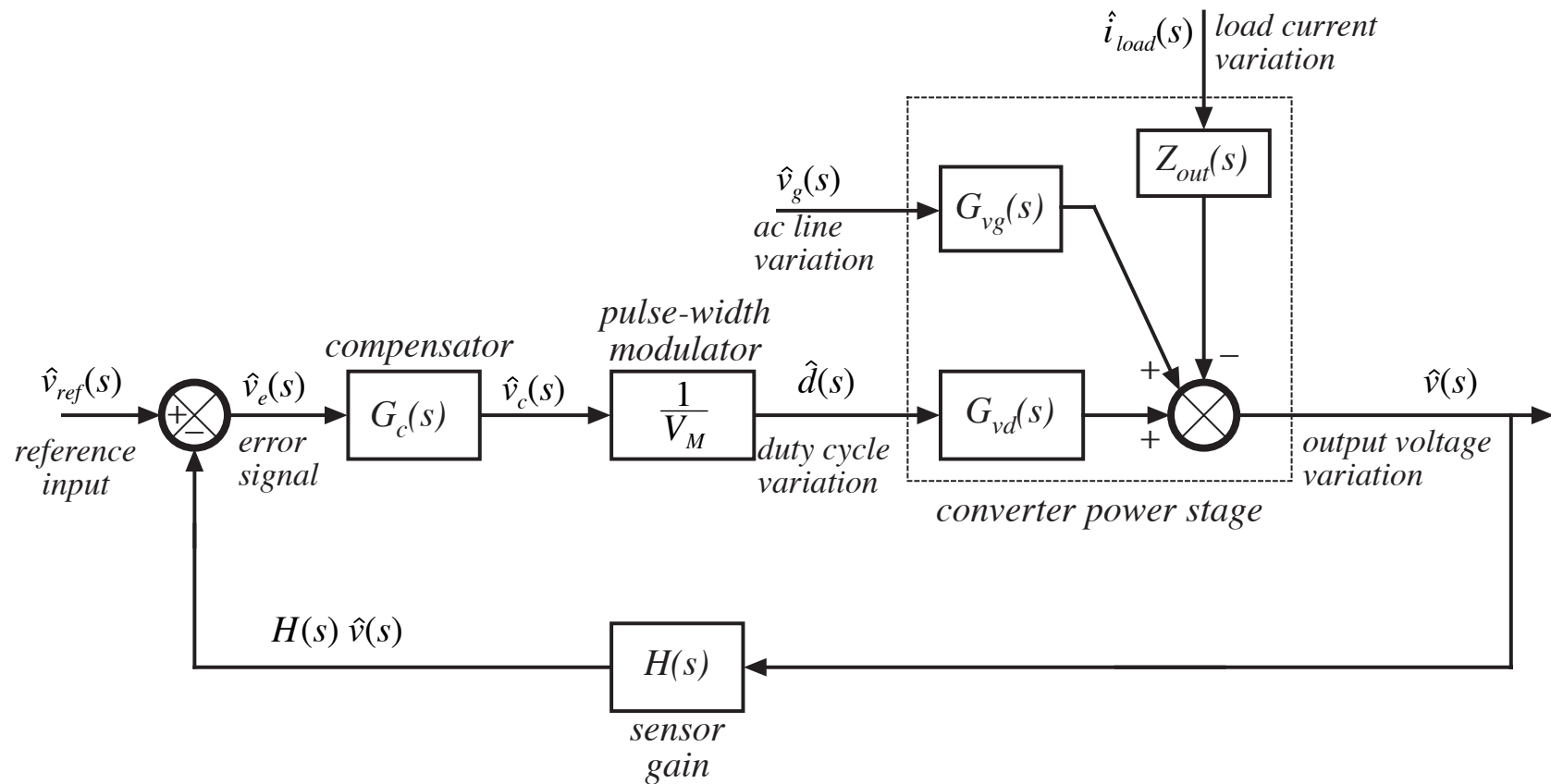
# Regulator system small-signal block diagram



# Solution of block diagram

---

Manipulate block diagram to solve for  $\hat{v}(s)$ . Result is

$$\hat{v} = \hat{v}_{ref} \frac{G_c G_{vd} / V_M}{1 + H G_c G_{vd} / V_M} + \hat{v}_g \frac{G_{vg}}{1 + H G_c G_{vd} / V_M} \pm \hat{i}_{load} \frac{Z_{out}}{1 + H G_c G_{vd} / V_M}$$

which is of the form

$$\hat{v} = \hat{v}_{ref} \frac{1}{H} \frac{T}{1 + T} + \hat{v}_g \frac{G_{vg}}{1 + T} \pm \hat{i}_{load} \frac{Z_{out}}{1 + T}$$

with  $T(s) = H(s) G_c(s) G_{vd}(s) / V_M = \text{"loop gain"}$

Loop gain  $T(s)$  = products of the gains around the negative feedback loop.

## 9.2.1. Feedback reduces the transfer functions from disturbances to the output

---

Original (open-loop) line-to-output transfer function:

$$G_{vg}(s) = \left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\substack{\hat{d}=0 \\ \hat{i}_{load}=0}}$$

With addition of negative feedback, the line-to-output transfer function becomes:

$$\left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\substack{\hat{v}_{ref}=0 \\ \hat{i}_{load}=0}} = \frac{G_{vg}(s)}{1 + T(s)}$$

Feedback reduces the line-to-output transfer function by a factor of

$$\frac{1}{1 + T(s)}$$

If  $T(s)$  is large in magnitude, then the line-to-output transfer function becomes small.

# Closed-loop output impedance

---

Original (open-loop) output impedance:

$$Z_{out}(s) = \pm \left. \frac{\hat{v}(s)}{\hat{i}_{load}(s)} \right|_{\substack{\hat{d}=0 \\ \hat{v}_g=0}}$$

With addition of negative feedback, the output impedance becomes:

$$\left. \frac{\hat{v}(s)}{\pm \hat{i}_{load}(s)} \right|_{\substack{\hat{v}_{ref}=0 \\ \hat{v}_g=0}} = \frac{Z_{out}(s)}{1 + T(s)}$$

Feedback reduces the output impedance by a factor of

$$\frac{1}{1 + T(s)}$$

If  $T(s)$  is large in magnitude, then the output impedance is greatly reduced in magnitude.

## 9.2.2. Feedback causes the transfer function from the reference input to the output to be insensitive to variations in the gains in the forward path of the loop

---

Closed-loop transfer function from  $\hat{v}_{ref}$  to  $\hat{v}(s)$  is:

$$\left. \frac{\hat{v}(s)}{\hat{v}_{ref}(s)} \right|_{\substack{\hat{v}_g = 0 \\ \hat{i}_{load} = 0}} = \frac{1}{H(s)} \frac{T(s)}{1 + T(s)}$$

If the loop gain is large in magnitude, i.e.,  $\|T\| \gg 1$ , then  $(1+T) \approx T$  and  $T/(1+T) \approx T/T = 1$ . The transfer function then becomes

$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} \approx \frac{1}{H(s)}$$


which is independent of the gains in the forward path of the loop.

This result applies equally well to dc values:

$$\frac{V}{V_{ref}} = \frac{1}{H(0)} \frac{T(0)}{1 + T(0)} \approx \frac{1}{H(0)}$$

## 9.3. Construction of the important quantities $1/(1+T)$ and $T/(1+T)$

Example

 

At the crossover frequency  $f_c$ ,  $\|T\| = 1$


## Approximating $1/(1+T)$ and $T/(1+T)$

---

$$\frac{T}{1+T} \approx \begin{cases} 1 & \text{for } \|T\| \gg 1 \\ T & \text{for } \|T\| \ll 1 \end{cases}$$

$$\frac{1}{1+T(s)} \approx \begin{cases} \frac{1}{T(s)} & \text{for } \|T\| \gg 1 \\ 1 & \text{for } \|T\| \ll 1 \end{cases}$$

# Example: construction of $T/(1+T)$

 



## Example: analytical expressions for approximate reference to output transfer function

---

At frequencies sufficiently less than the crossover frequency, the loop gain  $T(s)$  has large magnitude. The transfer function from the reference to the output becomes

$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} = \frac{1}{H(s)} \frac{T(s)}{1 + T(s)} \approx \frac{1}{H(s)}$$


This is the desired behavior: the output follows the reference according to the ideal gain  $1/H(s)$ . The feedback loop works well at frequencies where the loop gain  $T(s)$  has large magnitude.

At frequencies above the crossover frequency,  $\|T\| < 1$ . The quantity  $T/(1+T)$  then has magnitude approximately equal to 1, and we obtain

$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} = \frac{1}{H(s)} \frac{T(s)}{1 + T(s)} \approx \frac{T(s)}{H(s)} = \frac{G_c(s)G_{vd}(s)}{V_M}$$

This coincides with the open-loop transfer function from the reference to the output. At frequencies where  $\|T\| < 1$ , the loop has essentially no effect on the transfer function from the reference to the output.
 
# Same example: construction of $1 / (1+T)$



## Interpretation: how the loop rejects disturbances

---

Below the crossover frequency:  $f < f_c$   
and  $\|T\| > 1$

Then  $1/(1+T) \approx 1/T$ , and  
disturbances are reduced in  
magnitude by  $1/\|T\|$

Above the crossover frequency:  $f > f_c$   
and  $\|T\| < 1$

Then  $1/(1+T) \approx 1$ , and the  
feedback loop has essentially  
no effect on disturbances

$$\frac{1}{1+T(s)} \approx \begin{cases} \frac{1}{T(s)} & \text{for } \|T\| \gg 1 \\ 1 & \text{for } \|T\| \ll 1 \end{cases}$$

# Terminology: open-loop vs. closed-loop

---

Original transfer functions, before introduction of feedback (“open-loop transfer functions”):

$$G_{vd}(s) \quad G_{vg}(s) \quad Z_{out}(s)$$

Upon introduction of feedback, these transfer functions become (“closed-loop transfer functions”):

$$\frac{1}{H(s)} \quad \frac{T(s)}{1 + T(s)} \quad \frac{G_{vg}(s)}{1 + T(s)} \quad \frac{Z_{out}(s)}{1 + T(s)}$$

The loop gain:

$$T(s)$$

## 9.4. Stability

---

Even though the original open-loop system is stable, the closed-loop transfer functions can be unstable and contain right half-plane poles. Even when the closed-loop system is stable, the transient response can exhibit undesirable ringing and overshoot, due to the high  $Q$ -factor of the closed-loop poles in the vicinity of the crossover frequency.

When feedback destabilizes the system, the denominator  $(1+T(s))$  terms in the closed-loop transfer functions contain roots in the right half-plane (i.e., with positive real parts). If  $T(s)$  is a rational fraction of the form  $N(s) / D(s)$ , where  $N(s)$  and  $D(s)$  are polynomials, then we can write

$$\frac{T(s)}{1 + T(s)} = \frac{\frac{N(s)}{D(s)}}{1 + \frac{N(s)}{D(s)}} = \frac{N(s)}{N(s) + D(s)}$$
$$\frac{1}{1 + T(s)} = \frac{1}{1 + \frac{N(s)}{D(s)}} = \frac{D(s)}{N(s) + D(s)}$$

- Could evaluate stability by evaluating  $N(s) + D(s)$ , then factoring to evaluate roots. This is a lot of work, and is not very illuminating.

# Determination of stability directly from $T(s)$

---

- Nyquist stability theorem: general result.
- A special case of the Nyquist stability theorem: the phase margin test  
Allows determination of closed-loop stability (i.e., whether  $1/(1+T(s))$  contains RHP poles) directly from the magnitude and phase of  $T(s)$ .  
A good design tool: yields insight into how  $T(s)$  should be shaped, to obtain good performance in transfer functions containing  $1/(1+T(s))$  terms.

## 9.4.1. The phase margin test

---

A test on  $T(s)$ , to determine whether  $1/(1+T(s))$  contains RHP poles.

The crossover frequency  $f_c$  is defined as the frequency where

$$\|T(j2\pi f_c)\| = 1 \Rightarrow 0\text{dB}$$


The phase margin  $\varphi_m$  is determined from the phase of  $T(s)$  at  $f_c$ , as follows:

$$\varphi_m = 180^\circ + \angle T(j2\pi f_c)$$

If there is exactly one crossover frequency, and if  $T(s)$  contains no RHP poles, then

the quantities  $T(s)/(1+T(s))$  and  $1/(1+T(s))$  contain no RHP poles whenever the phase margin  $\varphi_m$  is positive.
 
# Example: a loop gain leading to a stable closed-loop system




$$\angle T(j2\pi f_c) = -112^\circ$$

$$\varphi_m = 180^\circ - 112^\circ = +68^\circ$$


 
# Example: a loop gain leading to an unstable closed-loop system



$$\angle T(j2\pi f_c) = -230^\circ$$

$$\varphi_m = 180^\circ - 230^\circ = -50^\circ$$

## 9.4.2. The relation between phase margin and closed-loop damping factor

---

How much phase margin is required?

A small positive phase margin leads to a stable closed-loop system having complex poles near the crossover frequency with high  $Q$ . The transient response exhibits overshoot and ringing.


Increasing the phase margin reduces the  $Q$ . Obtaining real poles, with no overshoot and ringing, requires a large phase margin.

The relation between phase margin and closed-loop  $Q$  is quantified in this section.
 
# A simple second-order system

Consider the case where  $T(s)$  can be well-approximated in the vicinity of the crossover frequency as

$$T(s) = \frac{1}{\left(\frac{s}{\omega_0}\right) \left(1 + \frac{s}{\omega_2}\right)}$$



# Closed-loop response

---

If

$$T(s) = \frac{1}{\left(\frac{s}{\omega_0}\right)\left(1 + \frac{s}{\omega_2}\right)}$$

Then

$$\frac{T(s)}{1 + T(s)} = \frac{1}{1 + \frac{1}{T(s)}} = \frac{1}{1 + \frac{s}{\omega_0} + \frac{s^2}{\omega_0\omega_2}}$$

or,


$$\frac{T(s)}{1 + T(s)} = \frac{1}{1 + \frac{s}{Q\omega_c} + \left(\frac{s}{\omega_c}\right)^2}$$

where

$$\omega_c = \sqrt{\omega_0\omega_2} = 2\pi f_c \qquad Q = \frac{\omega_0}{\omega_c} = \sqrt{\frac{\omega_0}{\omega_2}}$$
 
# Low- $Q$ case


$$Q = \frac{\omega_0}{\omega_c} = \sqrt{\frac{\omega_0}{\omega_2}} \quad \text{low-}Q \text{ approximation:} \quad Q \omega_c = \omega_0 \quad \frac{\omega_c}{Q} = \omega_2$$


 
# High-Q case

$$\omega_c = \sqrt{\omega_0 \omega_2} = 2\pi f_c$$

$$Q = \frac{\omega_0}{\omega_c} = \sqrt{\frac{\omega_0}{\omega_2}}$$



## $Q$ vs. $\varphi_m$


---

Solve for exact crossover frequency, evaluate phase margin, express as function of  $\varphi_m$ . Result is:

$$Q = \frac{\sqrt{\cos \varphi_m}}{\sin \varphi_m}$$

$$\varphi_m = \tan^{-1} \sqrt{\frac{1 + \sqrt{1 + 4Q^4}}{2Q^4}}$$

## $Q$ vs. $\varphi_m$

 



## 9.4.3. Transient response vs. damping factor

---

Unit-step response of second-order system  $T(s)/(1+T(s))$

$$\hat{v}(t) = 1 + \frac{2Q e^{-\omega_c t/2Q}}{\sqrt{4Q^2 \pm 1}} \sin \left[ \frac{\sqrt{4Q^2 \pm 1}}{2Q} \omega_c t + \tan^{-1}(\sqrt{4Q^2 \pm 1}) \right] \quad Q > 0.5$$


$$\hat{v}(t) = 1 \pm \frac{\omega_2}{\omega_2 \pm \omega_1} e^{\pm \omega_1 t} \pm \frac{\omega_1}{\omega_1 \pm \omega_2} e^{\pm \omega_2 t} \quad Q < 0.5$$

$$\omega_1, \omega_2 = \frac{\omega_c}{2Q} \left( 1 \pm \sqrt{1 \pm 4Q^2} \right)$$

For  $Q > 0.5$ , the peak value is

$$\text{peak } \hat{v}(t) = 1 + e^{\pm \pi / \sqrt{4Q^2 \pm 1}}$$

# Transient response vs. damping factor

 

## 9.5. Regulator design

---

Typical specifications:


- Effect of load current variations on output voltage regulation  
This is a limit on the maximum allowable output impedance
- Effect of input voltage variations on the output voltage regulation  
This limits the maximum allowable line-to-output transfer function
- Transient response time  
This requires a sufficiently high crossover frequency
- Overshoot and ringing  
An adequate phase margin must be obtained

The regulator design problem: add compensator network  $G_c(s)$  to modify  $T(s)$  such that all specifications are met.


## 9.5.1. Lead (PD) compensator

$$G_c(s) = G_{c0} \frac{\left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_p}\right)}$$

Improves phase margin

 

# Lead compensator: maximum phase lead

 

$$f_{\varphi_{\max}} = \sqrt{f_z f_p}$$

$$\angle G_c(f_{\varphi_{\max}}) = \tan^{-1} \left( \frac{\sqrt{\frac{f_p}{f_z}} \pm \sqrt{\frac{f_z}{f_p}}}{2} \right)$$

$$\frac{f_p}{f_z} = \frac{1 + \sin(\theta)}{1 \pm \sin(\theta)}$$

# Lead compensator design


To optimally obtain a compensator phase lead of  $\theta$  at frequency  $f_c$ , the pole and zero frequencies should be chosen as follows:

$$f_z = f_c \sqrt{\frac{1 \pm \sin(\theta)}{1 + \sin(\theta)}}$$


$$f_p = f_c \sqrt{\frac{1 + \sin(\theta)}{1 \pm \sin(\theta)}}$$

If it is desired that the magnitude of the compensator gain at  $f_c$  be unity, then  $G_{c0}$  should be chosen as

$$G_{c0} = \sqrt{\frac{f_z}{f_p}}$$

 


# Example: lead compensation

 
 
## 9.5.2. Lag (PI) compensation

$$G_c(s) = G_{c\infty} \left( 1 + \frac{\omega_L}{s} \right)$$

Improves low-frequency loop gain and regulation





# Example: lag compensation

original  
(uncompensated)  
loop gain is

$$T_u(s) = \frac{T_{u0}}{\left(1 + \frac{s}{\omega_0}\right)}$$


compensator:

$$G_c(s) = G_{c\infty} \left(1 + \frac{\omega_L}{s}\right)$$

Design strategy:  
choose


$G_{c\infty}$  to obtain desired  
crossover frequency

 $\omega_L$  sufficiently low to  
maintain adequate  
phase margin



 
## Example, continued

Construction of  $1/(1+T)$ , lag compensator example:



 
### 9.5.3. Combined (PID) compensator

$$G_c(s) = G_{cm} \frac{\left(1 + \frac{\omega_L}{s}\right) \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$



## 9.5.4. Design example

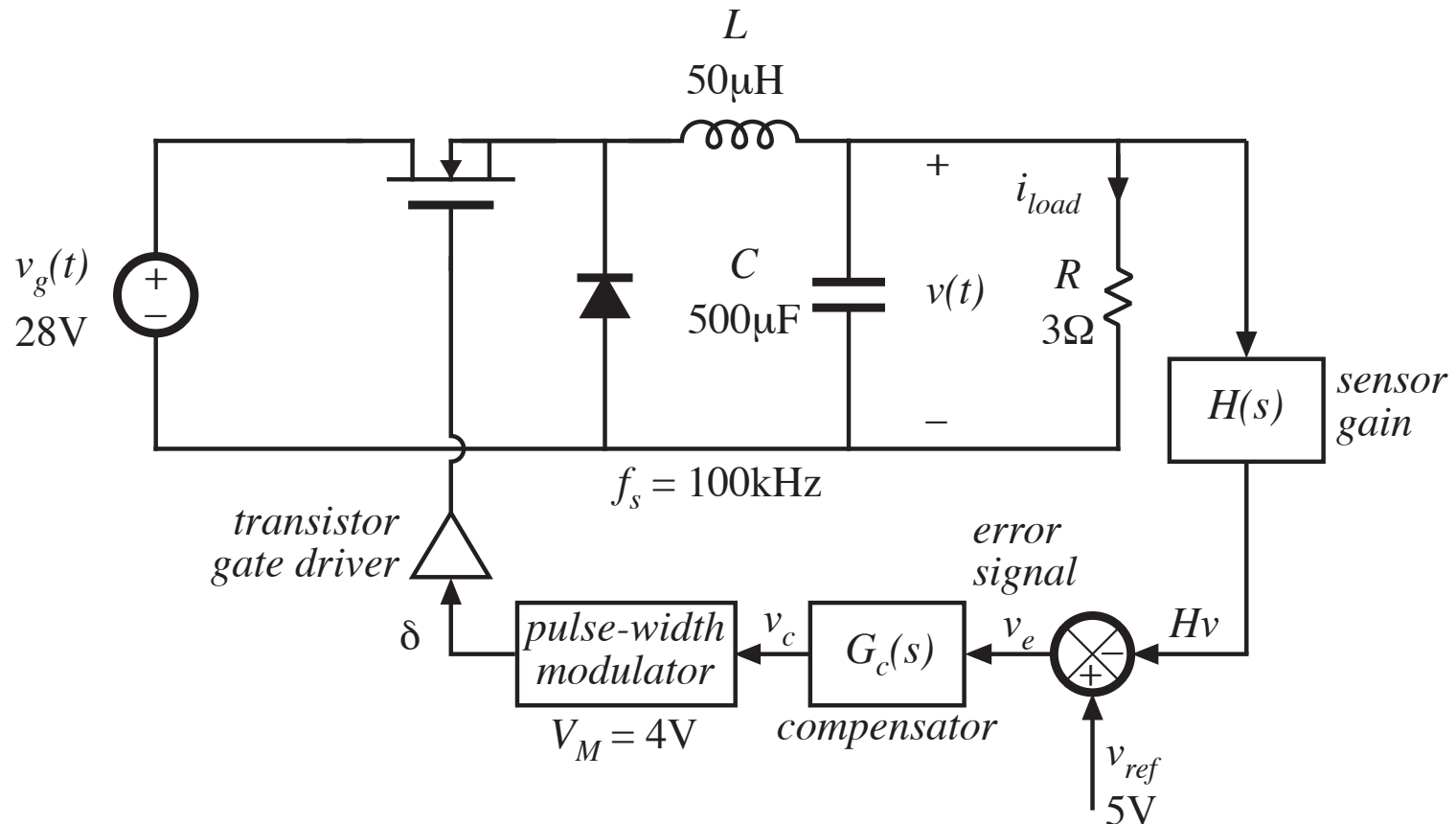


# Quiescent operating point

---

Input voltage	$V_g = 28\text{V}$
Output	$V = 15\text{V}, I_{load} = 5\text{A}, R = 3\Omega$
Quiescent duty cycle	$D = 15/28 = 0.536$
Reference voltage	$V_{ref} = 5\text{V}$
Quiescent value of control voltage	$V_c = DV_M = 2.14\text{V}$
Gain $H(s)$	$H = V_{ref}/V = 5/15 = 1/3$

# Small-signal model

 

# Open-loop control-to-output transfer function $G_{vd}(s)$

$$G_{vd}(s) = \frac{V}{D} \frac{1}{1 + s\frac{L}{R} + s^2LC}$$

standard form:


$$G_{vd}(s) = G_{d0} \frac{1}{1 + \frac{s}{Q_0\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

salient features:

$$G_{d0} = \frac{V}{D} = 28V$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = 1\text{kHz}$$
 
$$Q_0 = R\sqrt{\frac{C}{L}} = 9.5 \Rightarrow 19.5\text{dB}$$



# Open-loop line-to-output transfer function and output impedance

---

$$G_{vg}(s) = D \frac{1}{1 + s\frac{L}{R} + s^2LC}$$

—same poles as control-to-output transfer function  
standard form:

$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{s}{Q_0\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Output impedance:


$$Z_{out}(s) = R \parallel \frac{1}{sC} \parallel sL = \frac{sL}{1 + s\frac{L}{R} + s^2LC}$$


 
# System block diagram

$$T(s) = G_c(s) \left( \frac{1}{V_M} \right) G_{vd}(s) H(s)$$

$$T(s) = \frac{G_c(s) H(s)}{V_M} \frac{V}{D} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left( \frac{s}{\omega_0} \right)^2}$$




# Uncompensated loop gain (with $G_c = 1$ )

With  $G_c = 1$ , the loop gain is

$$T_u(s) = T_{u0} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$
 
$$T_{u0} = \frac{H V}{D V_M} = 2.33 \Rightarrow 7.4\text{dB}$$



$$f_c = 1.8\text{kHz}, \varphi_m = 5^\circ$$

# Lead compensator design

---


- Obtain a crossover frequency of 5kHz, with phase margin of  $52^\circ$
- $T_u$  has phase of approximately  $-180^\circ$  at 5kHz, hence lead (PD) compensator is needed to increase phase margin.
- Lead compensator should have phase of  $+52^\circ$  at 5kHz
- $T_u$  has magnitude of -20.6dB at 5kHz
- Lead compensator gain should have magnitude of +20.6dB at 5kHz
- Lead compensator pole and zero frequencies should be

$$f_z = (5\text{kHz}) \sqrt{\frac{1 \pm \sin(52^\circ)}{1 + \sin(52^\circ)}} = 1.7\text{kHz}$$


$$f_p = (5\text{kHz}) \sqrt{\frac{1 + \sin(52^\circ)}{1 \pm \sin(52^\circ)}} = 14.5\text{kHz}$$

- Compensator dc gain should be  $G_{c0} = \left(\frac{f_c}{f_0}\right)^2 \frac{1}{T_{u0}} \sqrt{\frac{f_z}{f_p}} = 3.7 \Rightarrow 11.3\text{dB}$


# Lead compensator Bode plot

 

# Loop gain, with lead compensator

 


# $1/(1+T)$ , with lead compensator

 


- need more low-frequency loop gain
- hence, add inverted zero (PID controller)

# Improved compensator (PID)

 


- add inverted zero to PD compensator, without changing dc gain or corner frequencies
- choose  $f_L$  to be  $f_c/10$ , so that phase margin is unchanged
 
## $T(s)$ and $1/(1+T(s))$ , with PID compensator






# Line-to-output transfer function

 

## 9.6. Measurement of loop gains

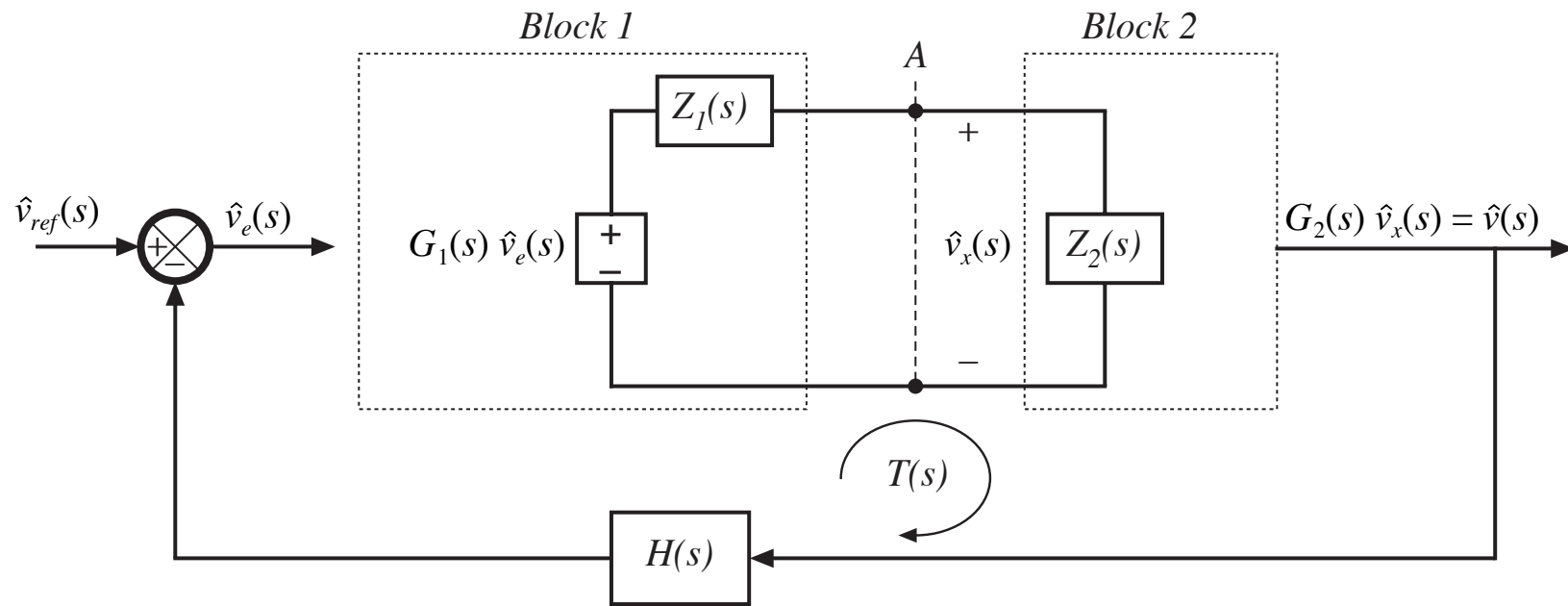


Objective: experimentally determine loop gain  $T(s)$ , by making measurements at point A

Correct result is

$$T(s) = G_1(s) \left( \frac{Z_2(s)}{Z_1(s) + Z_2(s)} \right) G_2(s) H(s)$$
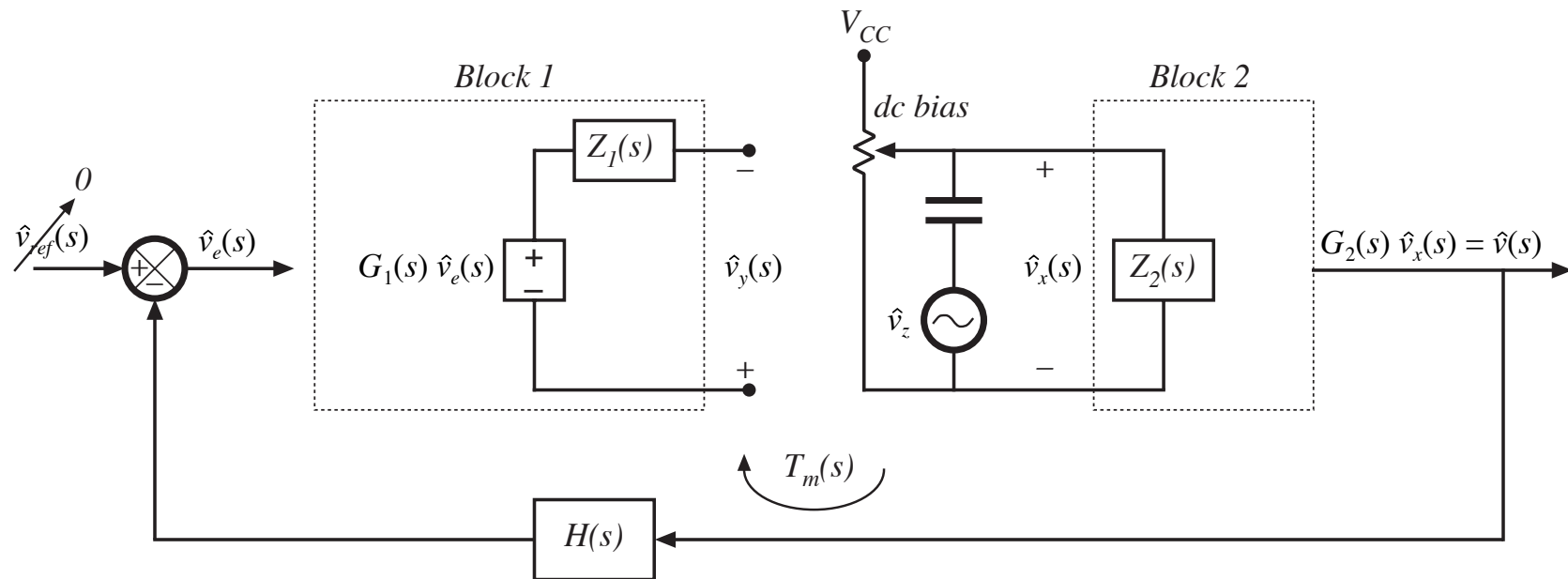
# Conventional approach: break loop, measure $T(s)$ as conventional transfer function



measured gain is

$$T_m(s) = \left. \frac{\hat{v}_y(s)}{\hat{v}_x(s)} \right|_{\substack{\hat{v}_{ref}=0 \\ \hat{v}_g=0}}$$

$$T_m(s) = G_1(s) G_2(s) H(s)$$

# Measured vs. actual loop gain

---

Actual loop gain:

$$T(s) = G_1(s) \left( \frac{Z_2(s)}{Z_1(s) + Z_2(s)} \right) G_2(s) H(s)$$

Measured loop gain:

$$T_m(s) = G_1(s) G_2(s) H(s)$$

Express  $T_m$  as function of  $T$ :

$$T_m(s) = T(s) \left( 1 + \frac{Z_1(s)}{Z_2(s)} \right)$$


$$T_m(s) \approx T(s) \quad \text{provided that} \quad \|Z_2\| \gg \|Z_1\|$$

# Discussion

---

- Breaking the loop disrupts the loading of block 2 on block 1.  
A suitable injection point must be found, where loading is not significant.
- Breaking the loop disrupts the dc biasing and quiescent operating point.  
A potentiometer must be used, to correctly bias the input to block 2.  
In the common case where the dc loop gain is large, it is very difficult to correctly set the dc bias.
- It would be desirable to avoid breaking the loop, such that the biasing circuits of the system itself set the quiescent operating point.

## 9.6.1. Voltage injection

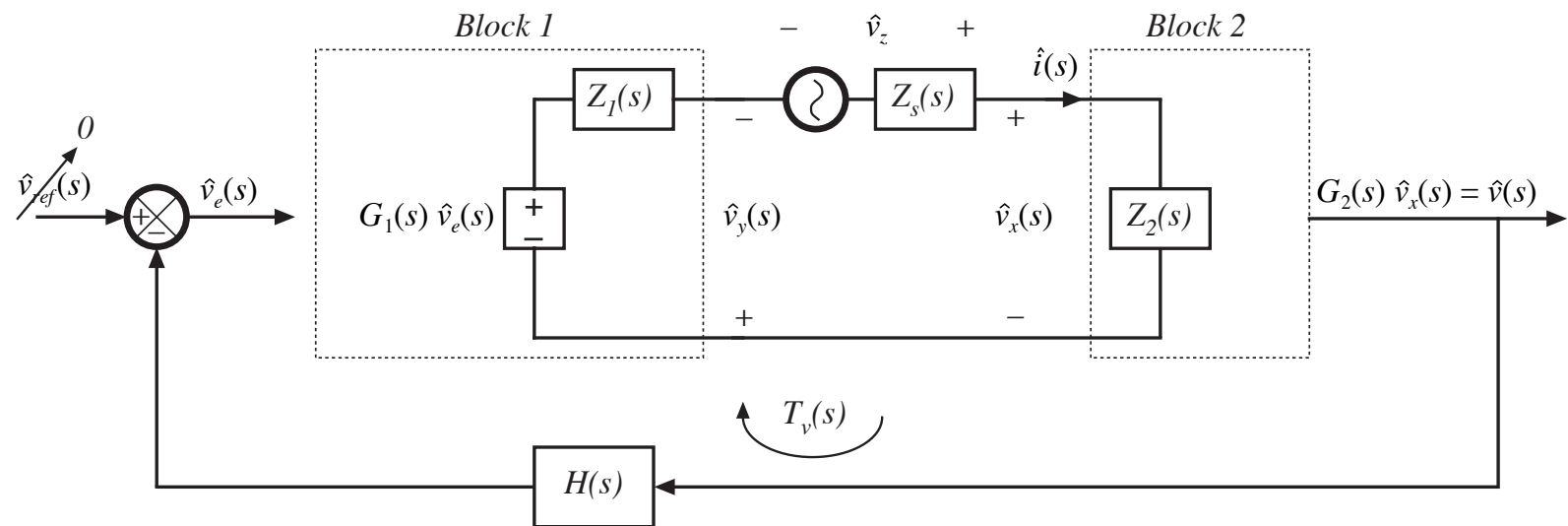

- Ac injection source  $v_z$  is connected between blocks 1 and 2
- Dc bias is determined by biasing circuits of the system itself
- Injection source does modify loading of block 2 on block 1

# Voltage injection: measured transfer function $T_v(s)$

Network analyzer measures

$$T_v(s) = \left. \frac{\hat{v}_y(s)}{\hat{v}_x(s)} \right|_{\substack{\hat{v}_{ref}=0 \\ \hat{v}_g=0}}$$

Solve block diagram:

$$\hat{v}_e(s) = \pm H(s) G_2(s) \hat{v}_x(s)$$


$$\pm \hat{v}_y(s) = G_1(s) \hat{v}_e(s) \pm \hat{i}(s) Z_1(s)$$

Hence

$$\pm \hat{v}_y(s) = \pm \hat{v}_x(s) G_2(s) H(s) G_1(s) \pm \hat{i}(s) Z_1(s)$$

with
 
$$\hat{i}(s) = \frac{\hat{v}_x(s)}{Z_2(s)}$$



Substitute:

$$\hat{v}_y(s) = \hat{v}_x(s) \left( G_1(s) G_2(s) H(s) + \frac{Z_1(s)}{Z_2(s)} \right)$$

which leads to the measured gain

$$T_v(s) = G_1(s) G_2(s) H(s) + \frac{Z_1(s)}{Z_2(s)}$$

## Comparison of $T_v(s)$ with $T(s)$

---

Actual loop gain is

$$T(s) = G_1(s) \left( \frac{Z_2(s)}{Z_1(s) + Z_2(s)} \right) G_2(s) H(s)$$

Gain measured via voltage injection:

$$T_v(s) = G_1(s) G_2(s) H(s) + \frac{Z_1(s)}{Z_2(s)}$$

Express  $T_v(s)$  in terms of  $T(s)$ :

$$T_v(s) = T(s) \left( 1 + \frac{Z_1(s)}{Z_2(s)} \right) + \frac{Z_1(s)}{Z_2(s)}$$


Condition for accurate measurement:

$$T_v(s) \approx T(s) \quad \text{provided} \quad (i) \quad \|Z_1(s)\| \ll \|Z_2(s)\|, \quad \text{and}$$

$$(ii) \quad \|T(s)\| \gg \left\| \frac{Z_1(s)}{Z_2(s)} \right\|$$



# Example: voltage injection

 

$$Z_1(s) = 50\Omega$$


$$Z_2(s) = 500\Omega$$

$$\frac{Z_1(s)}{Z_2(s)} = 0.1 \Rightarrow \pm 20\text{dB}$$

$$\left(1 + \frac{Z_1(s)}{Z_2(s)}\right) = 1.1 \Rightarrow 0.83\text{dB}$$


suppose actual  $T(s) = \frac{10^4}{\left(1 + \frac{s}{2\pi \cdot 10\text{Hz}}\right) \left(1 + \frac{s}{2\pi \cdot 100\text{kHz}}\right)}$
 
## Example: measured $T_v(s)$ and actual $T(s)$



## 9.6.2. Current injection

$$T_i(s) = \left. \frac{\hat{i}_y(s)}{\hat{i}_x(s)} \right|_{\substack{\hat{v}_{ref} = 0 \\ \hat{v}_g = 0}}$$

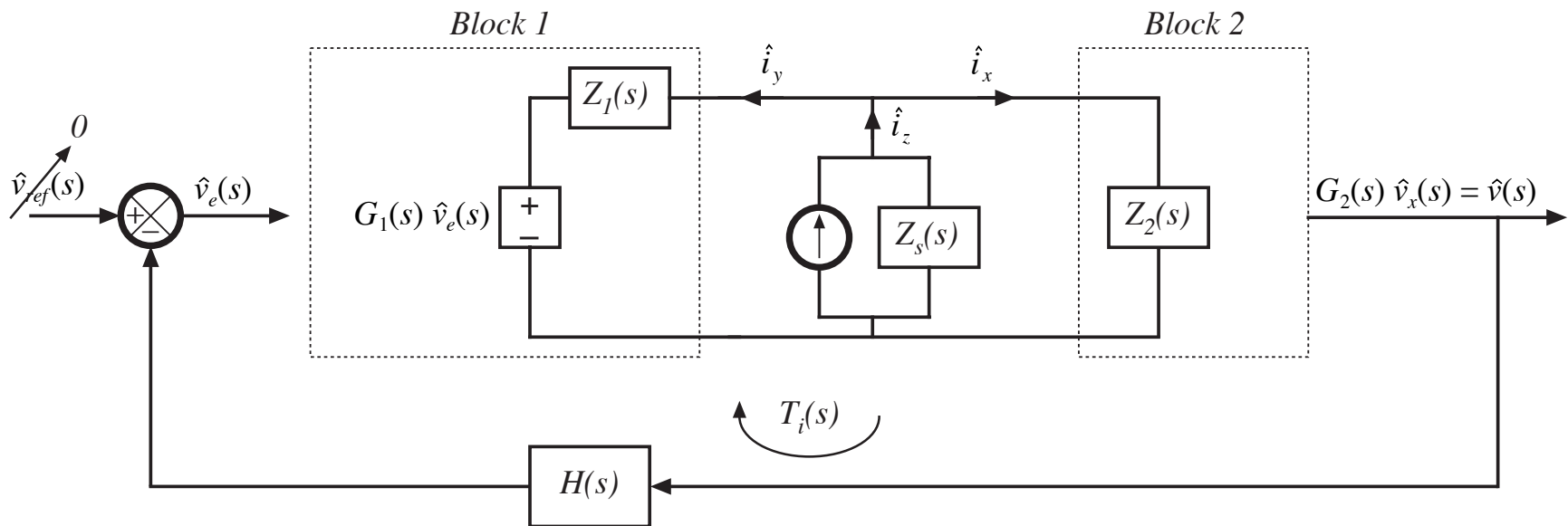

# Current injection

It can be shown that


$$T_i(s) = T(s) \left( 1 + \frac{Z_2(s)}{Z_1(s)} \right) + \frac{Z_2(s)}{Z_1(s)}$$

Conditions for obtaining accurate measurement:

(i)  $\|Z_2(s)\| \ll \|Z_1(s)\|$ , and


(ii)  $\|T(s)\| \gg \left\| \frac{Z_2(s)}{Z_1(s)} \right\|$

 Injection source impedance  $Z_s$  is irrelevant. We could inject using a Thevenin-equivalent voltage source:


 
## 9.6.3. Measurement of unstable systems

- Injection source impedance  $Z_s$  does not affect measurement
- Increasing  $Z_s$  reduces loop gain of circuit, tending to stabilize system
- Original (unstable) loop gain is measured (not including  $Z_s$ ), while circuit operates stably



## 9.7. Summary of key points

---

1. Negative feedback causes the system output to closely follow the reference input, according to the gain  $1 / H(s)$ . The influence on the output of disturbances and variation of gains in the forward path is reduced.
2. The loop gain  $T(s)$  is equal to the products of the gains in the forward and feedback paths. The loop gain is a measure of how well the feedback system works: a large loop gain leads to better regulation of the output. The crossover frequency  $f_c$  is the frequency at which the loop gain  $T$  has unity magnitude, and is a measure of the bandwidth of the control system.

## Summary of key points

---

3. The introduction of feedback causes the transfer functions from disturbances to the output to be multiplied by the factor  $1/(1+T(s))$ . At frequencies where  $T$  is large in magnitude (i.e., below the crossover frequency), this factor is approximately equal to  $1/T(s)$ . Hence, the influence of low-frequency disturbances on the output is reduced by a factor of  $1/T(s)$ . At frequencies where  $T$  is small in magnitude (i.e., above the crossover frequency), the factor is approximately equal to 1. The feedback loop then has no effect. Closed-loop disturbance-to-output transfer functions, such as the line-to-output transfer function or the output impedance, can easily be constructed using the algebra-on-the-graph method.
4. Stability can be assessed using the phase margin test. The phase of  $T$  is evaluated at the crossover frequency, and the stability of the important closed-loop quantities  $T/(1+T)$  and  $1/(1+T)$  is then deduced. Inadequate phase margin leads to ringing and overshoot in the system transient response, and peaking in the closed-loop transfer functions.

## Summary of key points

---

5. Compensators are added in the forward paths of feedback loops to shape the loop gain, such that desired performance is obtained. Lead compensators, or PD controllers, are added to improve the phase margin and extend the control system bandwidth. PI controllers are used to increase the low-frequency loop gain, to improve the rejection of low-frequency disturbances and reduce the steady-state error.
6. Loop gains can be experimentally measured by use of voltage or current injection. This approach avoids the problem of establishing the correct quiescent operating conditions in the system, a common difficulty in systems having a large dc loop gain. An injection point must be found where interstage loading is not significant. Unstable loop gains can also be measured.



# Chapter 10


## Ac and Dc Equivalent Circuit Modeling of the Discontinuous Conduction Mode

---

### Introduction

 - 10.1. DCM Averaged Switch Model
- 10.2. Small-Signal AC Modeling of the DCM Switch Network
- 10.3. Generalized Averaged Switch Modeling
- 10.4. Summary of Key Points

We are missing ac and dc equivalent circuit models  
for the discontinuous conduction mode



# Change in characteristics at the CCM/DCM boundary

---


- Steady-state output voltage becomes strongly load-dependent
- Simpler dynamics: one pole and the RHP zero are moved to very high frequency, and can normally be ignored
- Traditionally, boost and buck-boost converters are designed to operate in DCM at full load
- All converters may operate in DCM at light load

So we need equivalent circuits that model the steady-state and small-signal ac models of converters operating in DCM



The averaged switch approach will be employed
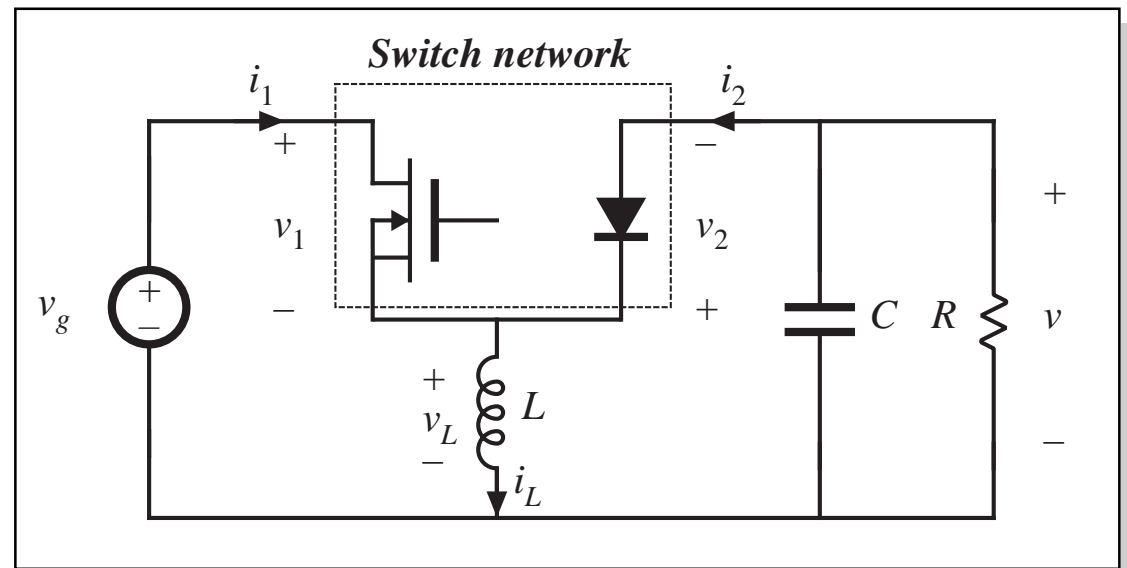
## 10.1 Derivation of DCM averaged switch model: buck-boost example

- Define switch terminal quantities  $v_1$ ,  $i_1$ ,  $v_2$ ,  $i_2$ , as shown
- Let us find the averaged quantities  $\langle v_1 \rangle$ ,  $\langle i_1 \rangle$ ,  $\langle v_2 \rangle$ ,  $\langle i_2 \rangle$ , for operation in DCM, and determine the relations between them



# DCM waveforms

  

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

# Basic DCM equations

Peak inductor current:

$$i_{pk} = \frac{v_g}{L} d_1 T_s$$

Average inductor voltage:


$$\langle v_L(t) \rangle_{T_s} = d_1 \langle v_g(t) \rangle_{T_s} + d_2 \langle v(t) \rangle_{T_s} + d_3 \cdot 0$$

In DCM, the diode switches off when the inductor current reaches zero. Hence,  $i(0) = i(T_s) = 0$ , and the average inductor voltage is zero. This is true even during transients.

$$\langle v_L(t) \rangle_{T_s} = d_1(t) \langle v_g(t) \rangle_{T_s} + d_2(t) \langle v(t) \rangle_{T_s} = 0$$

Solve for  $d_2$ :

$$d_2(t) = -d_1(t) \frac{\langle v_g(t) \rangle_{T_s}}{\langle v(t) \rangle_{T_s}}$$

 

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode

# Average switch network terminal voltages

Average the  $v_1(t)$  waveform:


$$\langle v_1(t) \rangle_{T_s} = d_1(t) \cdot 0 + d_2(t) \left( \langle v_g(t) \rangle_{T_s} - \langle v(t) \rangle_{T_s} \right) + d_3(t) \langle v_g(t) \rangle_{T_s}$$

Eliminate  $d_2$  and  $d_3$ :

$$\langle v_1(t) \rangle_{T_s} = \langle v_g(t) \rangle_{T_s}$$

Similar analysis for  $v_2(t)$  waveform leads to
 
$$\begin{aligned} \langle v_2(t) \rangle_{T_s} &= d_1(t) \left( \langle v_g(t) \rangle_{T_s} - \langle v(t) \rangle_{T_s} \right) + d_2(t) \cdot 0 + d_3(t) \left( -\langle v(t) \rangle_{T_s} \right) \\ &= -\langle v(t) \rangle_{T_s} \end{aligned}$$



# Average switch network terminal currents

Average the  $i_1(t)$  waveform:

$$\langle i_1(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} i_1(t) dt = \frac{q_1}{T_s}$$

The integral  $q_1$  is the area under the  $i_1(t)$  waveform during first subinterval. Use triangle area formula:

$$q_1 = \int_t^{t+T_s} i_1(t) dt = \frac{1}{2} (d_1 T_s) (i_{pk})$$


Eliminate  $i_{pk}$ :

$$\langle i_1(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \langle v_1(t) \rangle_{T_s}$$

Note  $\langle i_1(t) \rangle_{T_s}$  is not equal to  $d \langle i_L(t) \rangle_{T_s}$  !

Similar analysis for  $i_2(t)$  waveform leads to

$$\langle i_2(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \frac{\langle v_1(t) \rangle_{T_s}^2}{\langle v_2(t) \rangle_{T_s}}$$

 

Chapter 10: Ac and dc equivalent circuit modeling of the discontinuous conduction mode




# Input port: Averaged equivalent circuit

---

$$\langle i_1(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \langle v_1(t) \rangle_{T_s}$$

$$\langle i_1(t) \rangle_{T_s} = \frac{\langle v_1(t) \rangle_{T_s}}{R_e(d_1)}$$


$$R_e(d_1) = \frac{2L}{d_1^2 T_s}$$

 

 
# Output port: Averaged equivalent circuit

$$\langle i_2(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \frac{\langle v_1(t) \rangle_{T_s}^2}{\langle v_2(t) \rangle_{T_s}}$$


$$\langle i_2(t) \rangle_{T_s} \langle v_2(t) \rangle_{T_s} = \frac{\langle v_1(t) \rangle_{T_s}^2}{R_e(d_1)} = \langle p(t) \rangle_{T_s}$$



# The dependent power source

 

 - *Must avoid open- and short-circuit connections of power sources*
- *Power sink: negative  $p(t)$*



# How the power source arises in lossless two-port networks

---

In a lossless two-port network without internal energy storage:  
instantaneous input power is equal to instantaneous output power


In all but a small number of special cases, the instantaneous power  
throughput is dependent on the applied external source and load

If the instantaneous power depends only on the external elements  
connected to one port, then the power is not dependent on the  
characteristics of the elements connected to the other port. The other  
port becomes a source of power, equal to the power flowing through  
the first port


A power source (or power sink) element is obtained
 
# Properties of power sources


*Series and parallel connection of power sources*



 *Reflection of power source through a transformer*



# The loss-free resistor (LFR)

 


*A two-port lossless network*

*Input port obeys Ohm's Law*


*Power entering input port is transferred to output port*
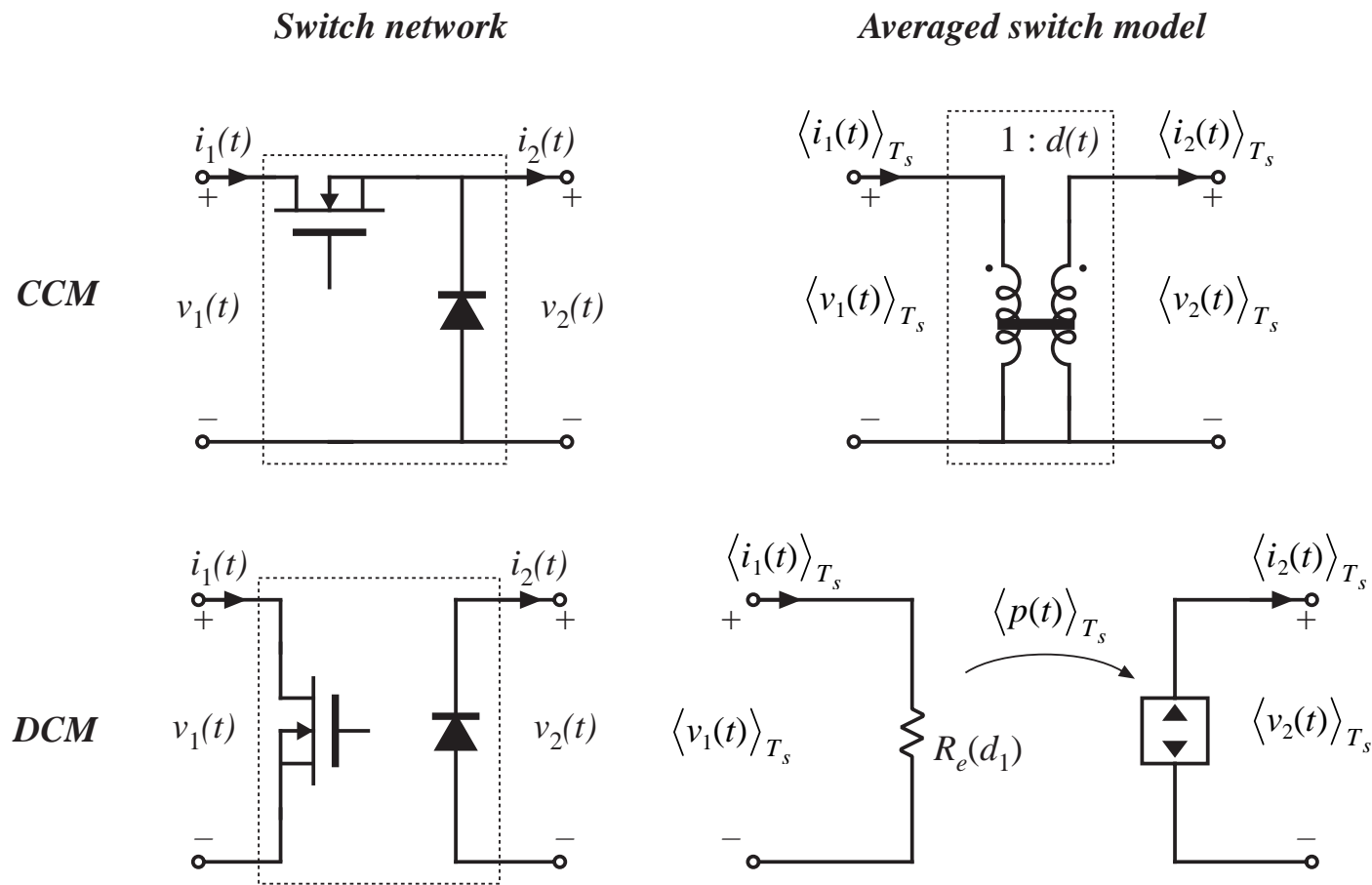
# Averaged modeling of CCM and DCM switch networks




# Averaged switch model: buck-boost example

*Original circuit*

 

*Averaged model*

 




## Solution of averaged model: steady state

Let

$L \rightarrow$  short circuit

$C \rightarrow$  open circuit

 

Converter input power:

$$P = \frac{V_g^2}{R_e}$$

Converter output power:

$$P = \frac{V^2}{R}$$

Equate and solve:

$$P = \frac{V_g^2}{R_e} = \frac{V^2}{R}$$

$$\frac{V}{V_g} = \pm \sqrt{\frac{R}{R_e}}$$

## Steady-state LFR solution

---

$$\frac{V}{V_g} = \pm \sqrt{\frac{R}{R_e}} \quad \text{is a general result, for any system that can be modeled as an LFR.}$$

For the buck-boost converter, we have


$$R_e(D) = \frac{2L}{D^2 T_s}$$

Eliminate  $R_e$ :

$$\frac{V}{V_g} = - \sqrt{\frac{D^2 T_s R}{2L}} = - \frac{D}{\sqrt{K}}$$

which agrees with the previous steady-state solution of Chapter 5.
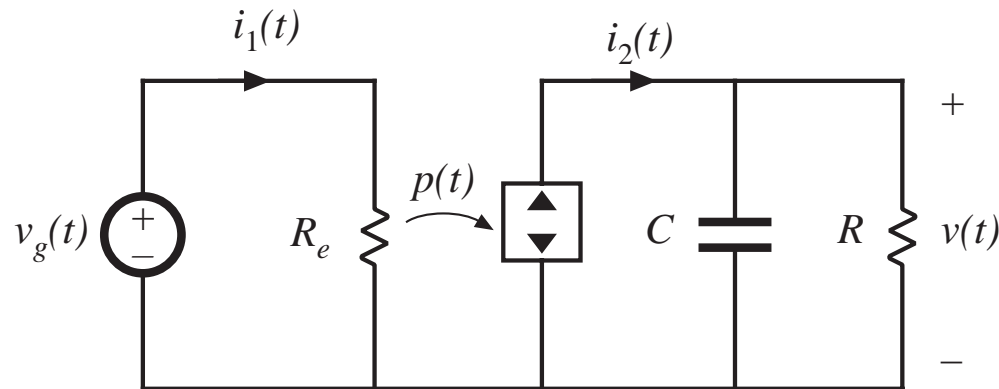
# Steady-state LFR solution with ac terminal waveforms



Converter average input  
power:

$$P_{av} = \frac{V_{g,rms}^2}{R_e}$$

Converter average output  
power:

$$P_{av} = \frac{V_{rms}^2}{R}$$


Note that no average power  
flows into capacitor

Equate and solve:

$$\frac{V_{rms}}{V_{g,rms}} = \sqrt{\frac{R}{R_e}}$$

 
# Averaged models of other DCM converters

- Determine averaged terminal waveforms of switch network
- In each case, averaged transistor waveforms obey Ohm's law, while averaged diode waveforms behave as dependent power source
- Can simply replace transistor and diode with the averaged model as follows:




# DCM buck, boost

*Buck*

 


$$R_e = \frac{2L}{d^2 T_s}$$

*Boost*

 


# DCM Cuk, SEPIC

*Cuk*

 

*SEPIC*

 


# Steady-state solution: DCM buck, boost


Let  $L \rightarrow$  short circuit

$C \rightarrow$  open circuit

*Buck*

 

*Boost*

 

# Steady-state solution of DCM/LFR models

Table 10.1. CCM and DCM conversion ratios of basic converters

Converter	$M$ , CCM	$M$ , DCM
Buck	$D$	$\frac{2}{1 + \sqrt{1 + 4R_e/R}}$
Boost	$\frac{1}{1 - D}$	$\frac{1 + \sqrt{1 + 4R/R_e}}{2}$
Buck-boost, Cuk	$\frac{-D}{1 - D}$	$-\sqrt{\frac{R}{R_e}}$
SEPIC	$\frac{D}{1 - D}$	$\sqrt{\frac{R}{R_e}}$


$$\begin{aligned}
 I &> I_{crit} && \text{for CCM} \\
 I &< I_{crit} && \text{for DCM}
 \end{aligned}$$

$$I_{crit} = \frac{1 - D}{D} \frac{V_g}{R_e(D)}$$



## 10.2 Small-signal ac modeling of the DCM switch network

*Large-signal averaged model*

 

$$\langle i_1(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \langle v_1(t) \rangle_{T_s}$$

$$\langle i_2(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \frac{\langle v_1(t) \rangle_{T_s}^2}{\langle v_2(t) \rangle_{T_s}}$$

*Perturb and linearize: let*

$$d(t) = D + \hat{d}(t)$$

$$\langle v_1(t) \rangle_{T_s} = V_1 + \hat{v}_1(t)$$

$$\langle i_1(t) \rangle_{T_s} = I_1 + \hat{i}_1(t)$$

$$\langle v_2(t) \rangle_{T_s} = V_2 + \hat{v}_2(t)$$

$$\langle i_2(t) \rangle_{T_s} = I_2 + \hat{i}_2(t)$$

$$\hat{i}_1 = \frac{\hat{v}_1}{r_1} + j_1 \hat{d} + g_1 \hat{v}_2$$

$$\hat{i}_2 = -\frac{\hat{v}_2}{r_2} + j_2 \hat{d} + g_2 \hat{v}_1$$

# Linearization via Taylor series

*Given the nonlinear equation*

$$\langle i_1(t) \rangle_{T_s} = \frac{\langle v_1(t) \rangle_{T_s}}{R_e(d(t))} = f_1\left(\langle v_1(t) \rangle_{T_s}, \langle v_2(t) \rangle_{T_s}, d(t)\right)$$

*Expand in three-dimensional Taylor series about the quiescent operating point:*

$$I_1 + \hat{i}_1(t) = f_1(V_1, V_2, D) + \hat{v}_1(t) \left. \frac{df_1(v_1, V_2, D)}{dv_1} \right|_{v_1 = V_1} \quad \text{(for simple notation, drop angle brackets)}$$

$$+ \hat{v}_2(t) \left. \frac{df_1(V_1, v_2, D)}{dv_2} \right|_{v_2 = V_2} + \hat{d}(t) \left. \frac{df_1(V_1, V_2, d)}{dd} \right|_{d = D}$$

+ higher-order nonlinear terms

## Equate dc and first-order ac terms

AC

$$\hat{i}_1(t) = \hat{v}_1(t) \frac{1}{r_1} + \hat{v}_2(t) g_1 + \hat{d}(t) j_1$$

$$\frac{1}{r_1} = \left. \frac{df_1(v_1, V_2, D)}{dv_1} \right|_{v_1 = V_1} = \frac{1}{R_e(D)}$$

$$g_1 = \left. \frac{df_1(V_1, v_2, D)}{dv_2} \right|_{v_2 = V_2} = 0$$

$$\begin{aligned} j_1 &= \left. \frac{df_1(V_1, V_2, d)}{dd} \right|_{d=D} = -\frac{V_1}{R_e^2(D)} \left. \frac{dR_e(d)}{dd} \right|_{d=D} \\ &= \frac{2V_1}{DR_e(D)} \end{aligned}$$

DC

$$I_1 = f_1(V_1, V_2, D) = \frac{V_1}{R_e(D)}$$

## Output port same approach

---


$$\langle i_2(t) \rangle_{T_s} = \frac{\langle v_1(t) \rangle_{T_s}^2}{R_e(d(t)) \langle v_2(t) \rangle_{T_s}} = f_2\left(\langle v_1(t) \rangle_{T_s}, \langle v_2(t) \rangle_{T_s}, d(t)\right)$$

$$I_2 = f_2(V_1, V_2, D) = \frac{V_1^2}{R_e(D) V_2} \quad \text{DC terms}$$


$$\hat{i}_2(t) = \hat{v}_2(t) \left(-\frac{1}{r_2}\right) + \hat{v}_1(t)g_2 + \hat{d}(t)j_2 \quad \text{Small-signal ac linearization}$$

# Output resistance parameter $r_2$

$$\frac{1}{r_2} = - \left. \frac{df_2(V_1, v_2, D)}{dv_2} \right|_{v_2 = V_2} = \frac{1}{R} = \frac{1}{M^2 R_e(D)}$$

 


# Small-signal DCM switch model parameters

 



**Table 10.2.** Small-signal DCM switch model parameters

Switch type	$g_1$	$j_1 \hat{d}$	$r_1$	$g_2$	$j_2$	$r_2$
Buck, Fig. 10.16(a)	$\frac{1}{R_e}$	$\frac{2(1-M)V_1}{DR_e}$	$R_e$	$\frac{2-M}{MR_e}$	$\frac{2(1-M)V_1}{DMR_e}$	$M^2 R_e$
Boost, Fig. 10.16(b)	$\frac{1}{(M-1)^2 R_e}$	$\frac{2MV_1}{D(M-1)R_e}$	$\frac{(M-1)^2}{M} R_e$	$\frac{2M-1}{(M-1)^2 R_e}$	$\frac{2V_1}{D(M-1)R_e}$	$(M-1)^2 R_e$
Buck-boost, Fig. 10.7(b)	0	$\frac{2V_1}{DR_e}$	$R_e$	$\frac{2M}{R_e}$	$\frac{2V_1}{DMR_e}$	$M^2 R_e$

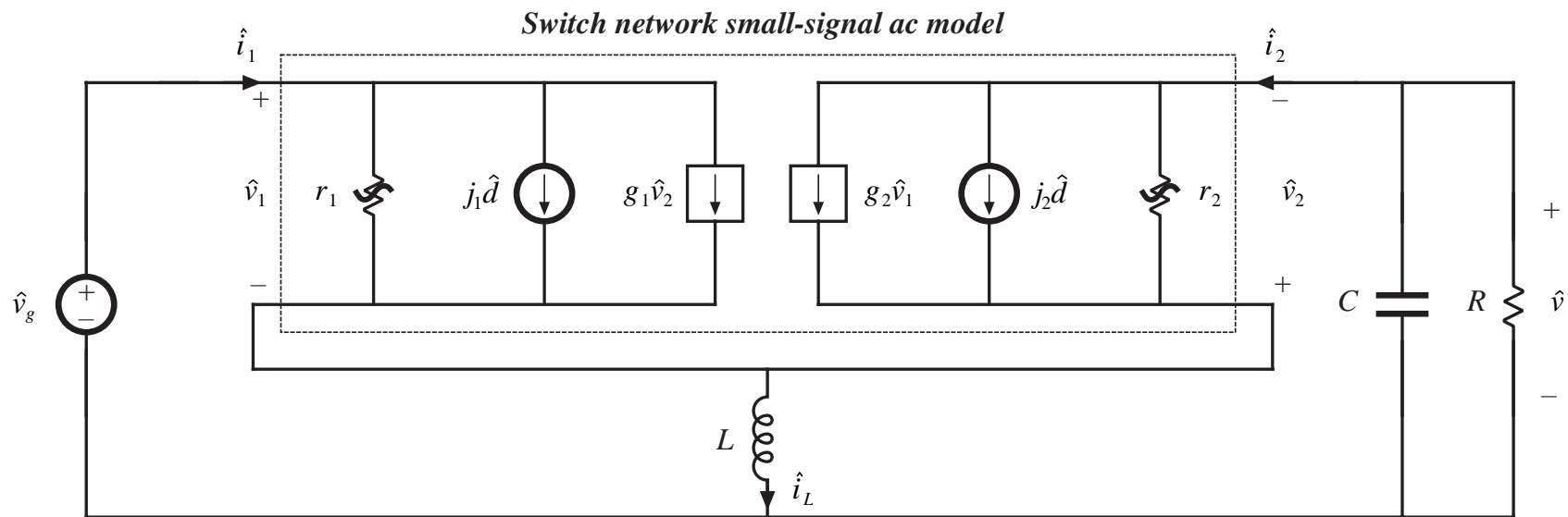
# Small-signal ac model, DCM buck-boost example


  
# A more convenient way to model the buck and boost small-signal DCM switch networks




 In any event, a small-signal two-port model is used, of the form




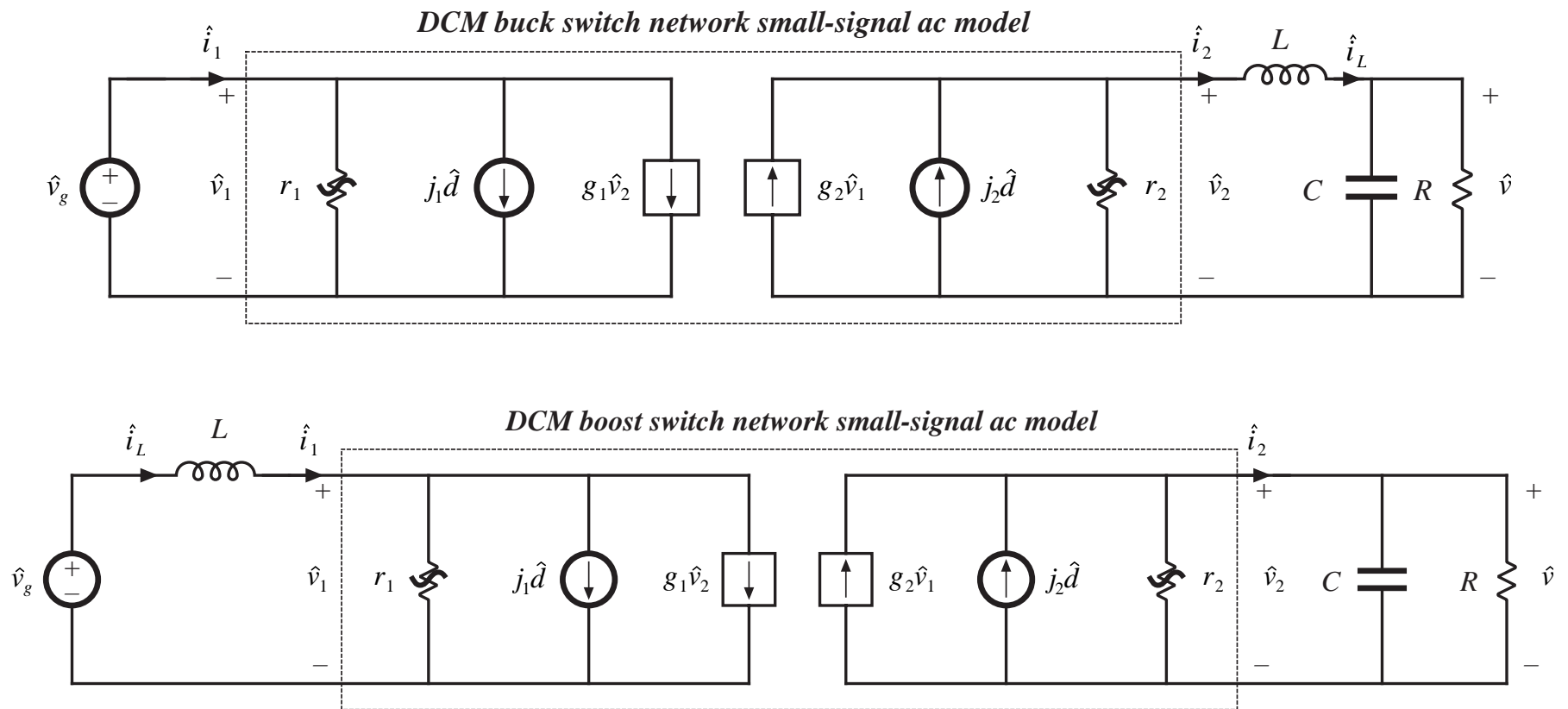
# Small-signal ac models of the DCM buck and boost converters (more convenient forms)



# DCM small-signal transfer functions


---

- When expressed in terms of  $R$ ,  $L$ ,  $C$ , and  $M$  (not  $D$ ), the small-signal transfer functions are the same in DCM as in CCM
- Hence, DCM boost and buck-boost converters exhibit two poles and one RHP zero in control-to-output transfer functions
- **But**, value of  $L$  is small in DCM. Hence
  - RHP zero appears at high frequency, usually greater than switching frequency
  - Pole due to inductor dynamics appears at high frequency, near to or greater than switching frequency
  - So DCM buck, boost, and buck-boost converters exhibit essentially a single-pole response
- A simple approximation: let  $L \rightarrow 0$
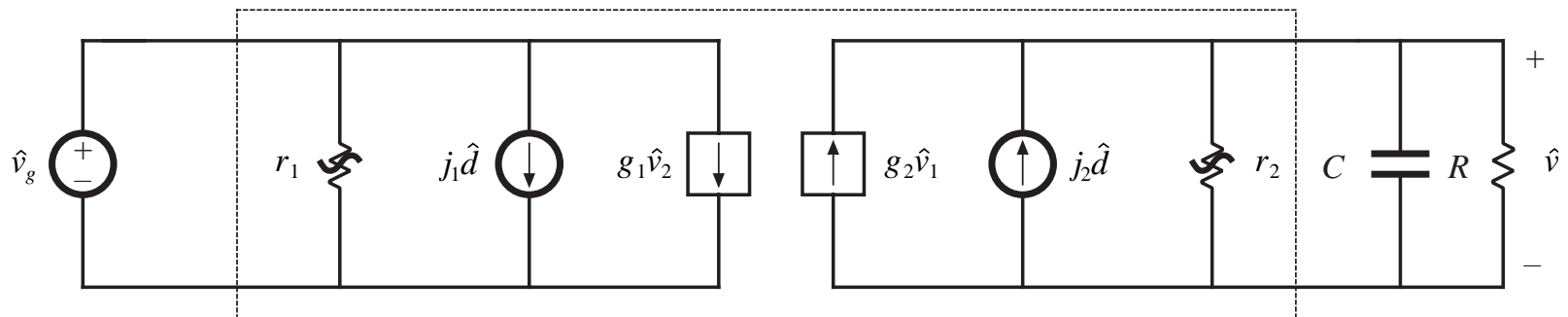
# The simple approximation $L \rightarrow 0$

Buck, boost, and buck-boost converter models all reduce to

*DCM switch network small-signal ac model*



Transfer functions

$$\begin{aligned}
 \text{control-to-output} \quad G_{vd}(s) &= \left. \frac{\hat{v}}{\hat{d}} \right|_{\hat{v}_g=0} = \frac{G_{d0}}{1 + \frac{s}{\omega_p}} & \text{with} \quad G_{d0} &= j_2 (R \parallel r_2) \\
 & & \omega_p &= \frac{1}{(R \parallel r_2) C} \\
 \text{line-to-output} \quad G_{vg}(s) &= \left. \frac{\hat{v}}{\hat{v}_g} \right|_{\hat{d}=0} = \frac{G_{g0}}{1 + \frac{s}{\omega_p}} & G_{g0} &= g_2 (R \parallel r_2) = M
 \end{aligned}$$

# Transfer function salient features

**Table 10.3.** Salient features of DCM converter small-signal transfer functions

Converter	$G_{d0}$	$G_{g0}$	$\omega_p$
Buck	$\frac{2V}{D} \frac{1-M}{2-M}$	$M$	$\frac{2-M}{(1-M)RC}$
Boost	$\frac{2V}{D} \frac{M-1}{2M-1}$	$M$	$\frac{2M-1}{(M-1)RC}$
Buck-boost	$\frac{V}{D}$	$M$	$\frac{2}{RC}$

# DCM boost example

---

$$R = 12 \, \Omega$$

$$L = 5 \, \mu\text{H}$$

$$C = 470 \, \mu\text{F}$$

$$f_s = 100 \, \text{kHz}$$

The output voltage is regulated to be  $V = 36 \, \text{V}$ . It is desired to determine  $G_{vd}(s)$  at the operating point where the load current is  $I = 3 \, \text{A}$  and the dc input voltage is  $V_g = 24 \, \text{V}$ .

## Evaluate simple model parameters

$$P = I(V - V_g) = (3 \text{ A})(36 \text{ V} - 24 \text{ V}) = 36 \text{ W}$$


$$R_e = \frac{V_g^2}{P} = \frac{(24 \text{ V})^2}{36 \text{ W}} = 16 \Omega$$

$$D = \sqrt{\frac{2L}{R_e T_s}} = \sqrt{\frac{2(5 \mu\text{H})}{(16 \Omega)(10 \mu\text{s})}} = 0.25$$

$$G_{d0} = \frac{2V}{D} \frac{M-1}{2M-1} = \frac{2(36 \text{ V})}{(0.25)} \frac{\left(\frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)}{\left(2 \frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)} = 72 \text{ V} \Rightarrow 37 \text{ dBV}$$

$$f_p = \frac{\omega_p}{2\pi} = \frac{2M-1}{2\pi (M-1)RC} = \frac{\left(2 \frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)}{2\pi \left(\frac{(36 \text{ V})}{(24 \text{ V})} - 1\right)(12 \Omega)(470 \mu\text{F})} = 112 \text{ Hz}$$
 
# Control-to-output transfer function, boost example



## 10.3 Generalized Switch Averaging

---

An approach that directly relates the transfer functions of converters

- operating in DCM, and/or

- with current programmed control, and/or

- with resonant switches, and/or


- with other control schemes or switch implementations,

to the transfer functions of the parent CCM converter, derived in Chapter 7.


The models for these other modes, control schemes, and switch implementations are shown to be equivalent to the CCM models of Chapter 7, plus additional effective feedback loops that describe the switch behavior


 
# Converter and switch network state equations



# Averaged system equations

 

## Averaging the switch network dependent quantities

---

Place switch network dependent outputs in vector  $y_s(t)$ , then average over one switching period, to obtain an equation of the form

$$\langle \mathbf{y}_s(t) \rangle_{T_s} = \mathbf{f} \left( \langle \mathbf{u}_s(t) \rangle_{T_s}, \langle \mathbf{u}_c(t) \rangle_{T_s} \right)$$

Now attempt to write the converter state equations in the same form used for CCM state-space averaging in Chapter 7. This can be done provided that the above equation can be manipulated into the form

$$\langle \mathbf{y}_s(t) \rangle_{T_s} = \mu(t) \mathbf{y}_{s1}(t) + \mu'(t) \mathbf{y}_{s2}(t)$$

where  $y_{s1}(t)$  is the value of  $y_s(t)$  in the CCM converter during subinterval 1

$y_{s2}(t)$  is the value of  $y_s(t)$  in the CCM converter during subinterval 2

$\mu$  is called the switch conversion ratio

$$\mu' = 1 - \mu$$

# Switch conversion ratio $\mu$

---

If it is true that

$$\langle \mathbf{y}_s(t) \rangle_{T_s} = \mu(t) \mathbf{y}_{s1}(t) + \mu'(t) \mathbf{y}_{s2}(t)$$

then CCM equations can be used directly, simply by replacing the duty cycle  $d(t)$  with the switch conversion ratio  $\mu(t)$ :

Steady-state relations are found by replacing  $D$  with  $\mu_0$


Small-signal transfer functions are found by replacing  $\hat{d}(t)$  with  $\hat{\mu}(t)$

The switch conversion ratio  $\mu$  is a generalization of the CCM duty cycle  $d$ . In general,  $\mu$  may depend on the switch independent inputs, that is, converter voltages and currents. So feedback may be built into the switch network.


A proof follows later.

## 10.3.1 Buck converter example

Original  
converter

 

DCM  
large-signal  
averaged  
model

 

# Defining the switch network inputs and outputs

Switch input vector


$$\mathbf{u}_s(t) = \begin{bmatrix} v_1(t) \\ i_2(t) \end{bmatrix}$$

Switch control input


$$\mathbf{u}_c(t) = [d(t)]$$

Switch output vector
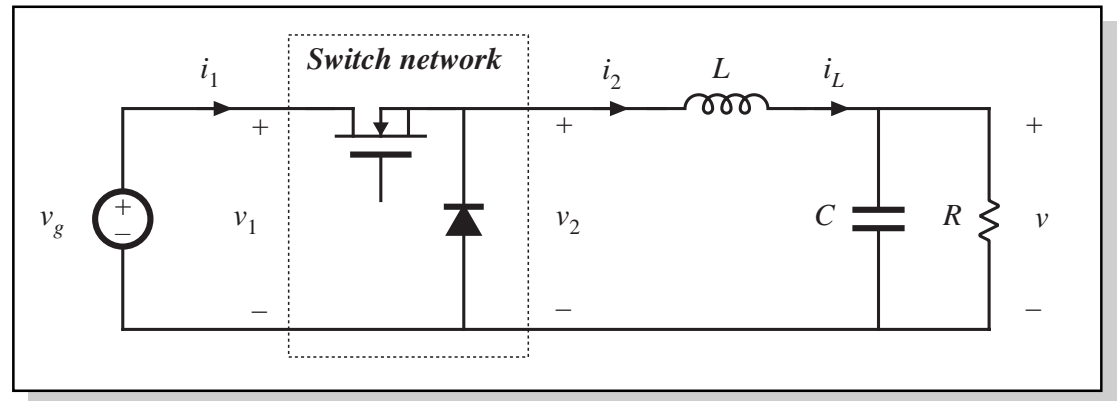
$$\mathbf{y}_s(t) = \begin{bmatrix} v_2(t) \\ i_1(t) \end{bmatrix}$$



# Switch output waveforms, CCM operation

 

CCM switch outputs during subintervals 1 and 2 are:

$$\mathbf{y}_{s1}(t) = \begin{bmatrix} \langle v_1(t) \rangle_{T_s} \\ \langle i_2(t) \rangle_{T_s} \end{bmatrix}, \quad \mathbf{y}_{s2}(t) = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

Hence, we should define the switch conversion ratio  $\mu$  to satisfy

$$\begin{bmatrix} \langle v_2(t) \rangle_{T_s} \\ \langle i_1(t) \rangle_{T_s} \end{bmatrix} = \mu(t) \begin{bmatrix} \langle v_1(t) \rangle_{T_s} \\ \langle i_2(t) \rangle_{T_s} \end{bmatrix} + (1 - \mu(t)) \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

For CCM operation, this equation is satisfied with  $\mu = d$ .

## Solve for $\mu$ , in general

---

$$\langle \mathbf{y}_s(t) \rangle_{T_s} = \mu(t) \mathbf{y}_{s1}(t) + \mu'(t) \mathbf{y}_{s2}(t) \quad \Rightarrow$$

$$\begin{bmatrix} \langle v_2(t) \rangle_{T_s} \\ \langle i_1(t) \rangle_{T_s} \end{bmatrix} = \mu(t) \begin{bmatrix} \langle v_1(t) \rangle_{T_s} \\ \langle i_2(t) \rangle_{T_s} \end{bmatrix} + (1 - \mu(t)) \begin{bmatrix} 0 \\ 0 \end{bmatrix} \quad \Rightarrow$$


$$\mu(t) = \frac{\langle v_2(t) \rangle_{T_s}}{\langle v_1(t) \rangle_{T_s}} = \frac{\langle i_1(t) \rangle_{T_s}}{\langle i_2(t) \rangle_{T_s}}$$

This is a general definition of  $\mu$ , for the switch network as defined previously for the buck converter. It is valid not only in CCM, but also in DCM and ...



# Evaluation of $\mu$

Solve  
averaged  
model for  $\mu$

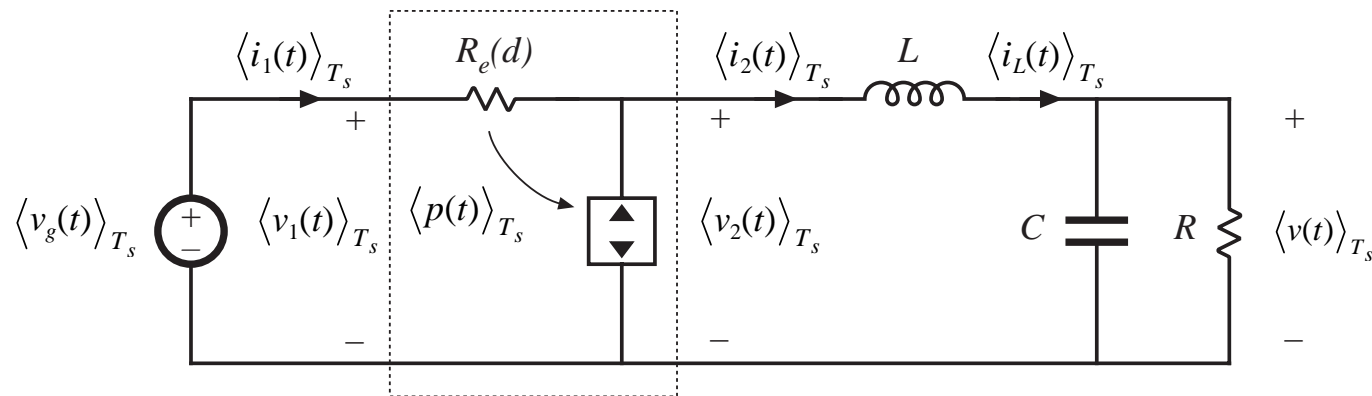

$$\mu(t) = \frac{\langle v_2(t) \rangle_{T_s}}{\langle v_1(t) \rangle_{T_s}} = \frac{\langle i_1(t) \rangle_{T_s}}{\langle i_2(t) \rangle_{T_s}}$$

$$\langle v_2(t) \rangle_{T_s} = \langle v_1(t) \rangle_{T_s} - \langle i_1(t) \rangle_{T_s} R_e(d)$$

$$1 = \frac{\langle v_1(t) \rangle_{T_s}}{\langle v_2(t) \rangle_{T_s}} - \frac{\langle i_1(t) \rangle_{T_s} R_e(d)}{\langle v_2(t) \rangle_{T_s}} = \frac{1}{\mu} - \frac{\langle i_1(t) \rangle_{T_s} R_e(d)}{\langle v_2(t) \rangle_{T_s}}$$

$$\Rightarrow \mu = \frac{1}{1 + R_e(d) \frac{\langle i_1(t) \rangle_{T_s}}{\langle v_2(t) \rangle_{T_s}}}$$

for DCM

# Elimination of dependent quantities

---

we found that

$$\mu = \frac{1}{1 + R_e(d) \frac{\langle i_1(t) \rangle_{T_s}}{\langle v_2(t) \rangle_{T_s}}}$$

Lossless switch network:

$$\langle i_1(t) \rangle_{T_s} \langle v_1(t) \rangle_{T_s} = \langle i_2(t) \rangle_{T_s} \langle v_2(t) \rangle_{T_s} \quad \Rightarrow \quad \frac{\langle i_1(t) \rangle_{T_s}}{\langle v_2(t) \rangle_{T_s}} = \frac{\langle i_2(t) \rangle_{T_s}}{\langle v_1(t) \rangle_{T_s}}$$

Hence

$$\mu \left( \langle v_1(t) \rangle_{T_s}, \langle i_2(t) \rangle_{T_s}, d \right) = \frac{1}{1 + R_e(d) \frac{\langle i_2(t) \rangle_{T_s}}{\langle v_1(t) \rangle_{T_s}}}$$

## DCM switch conversion ratio $\mu$

---

$$\mu\left(\langle v_1(t) \rangle_{T_s}, \langle i_2(t) \rangle_{T_s}, d\right) = \frac{1}{1 + R_e(d) \frac{\langle i_2(t) \rangle_{T_s}}{\langle v_1(t) \rangle_{T_s}}}$$

- A general result for DCM
- Replace  $d$  of CCM expression with  $\mu$  to obtain a valid DCM expression
- In DCM, switch conversion ratio is a function of not only the transistor duty cycle  $d$ , but also the switch independent terminal waveforms  $i_2$  and  $v_1$ . The switch network contains built-in feedback.

# Perturbation and linearization

---

$$\begin{aligned}\mu(t) &= \mu_0 + \hat{\mu}(t) \\ \langle \mathbf{u}_s(t) \rangle_{T_s} &= \mathbf{U}_s + \hat{\mathbf{u}}_s(t) \\ \mathbf{u}_c(t) &= \mathbf{U}_c + \hat{\mathbf{u}}_c(t)\end{aligned}$$

Steady-state components:

$$\mu_0 = \mu(\mathbf{U}_s, \mathbf{U}_c, D)$$

Buck example:

$$\mu_0 = \frac{1}{1 + R_e(D) \frac{I_2}{V_1}}$$

# Buck example: steady-state solution

---

In CCM, we know that

$$\frac{V}{V_g} = M(D) = D$$
$$I_L = \frac{V}{R}$$

DCM: replace  $D$  with  $\mu_0$ :

$$\frac{V}{V_g} = M(\mu_0) = \mu_0$$
$$I_2 = \frac{V}{R}$$

Can now solve for  $V$  to obtain the usual DCM expression for  $V/V_g$ .

with 
$$\mu_0 = \frac{1}{1 + R_e(D) \frac{I_2}{V_1}}$$

# DCM buck example: small-signal equations

---

Express linearized conversion ratio as a function of switch control input and independent terminal inputs:

$$\hat{\mu}(t) = \frac{\hat{v}_1(t)}{V_s} - \frac{\hat{i}_2(t)}{I_s} + k_s \hat{d}(t)$$


The gains are found by evaluation of derivatives at the quiescent operating point

$$\frac{1}{V_s} = \left. \frac{d\mu(v_1, I_2, D)}{dv_1} \right|_{v_1 = V_1} = \frac{\mu_0^2 I_2 R_e(D)}{V_1^2}$$

$$\frac{1}{I_s} = - \left. \frac{d\mu(V_1, i_2, D)}{di_2} \right|_{i_2 = I_2} = \frac{\mu_0^2 R_e(D)}{V_1}$$

$$k_s = \left. \frac{d\mu(V_1, I_2, d)}{dd} \right|_{d = D} = \frac{2\mu_0^2 I_2 R_e(D)}{DV_1}$$

# Result: small-signal model of DCM buck

 


# Control-to-output transfer function

$$G_{vd}(s) = \left. \frac{\hat{v}(s)}{\hat{d}(s)} \right|_{\hat{v}_g(s)=0}$$

$$G_{vd}(s) = G_{vd\infty}(s) \frac{T_i(s)}{1 + T_i(s)}$$


$$T_i(s) = \frac{V_g}{I_s Z_{ei}(s)}$$
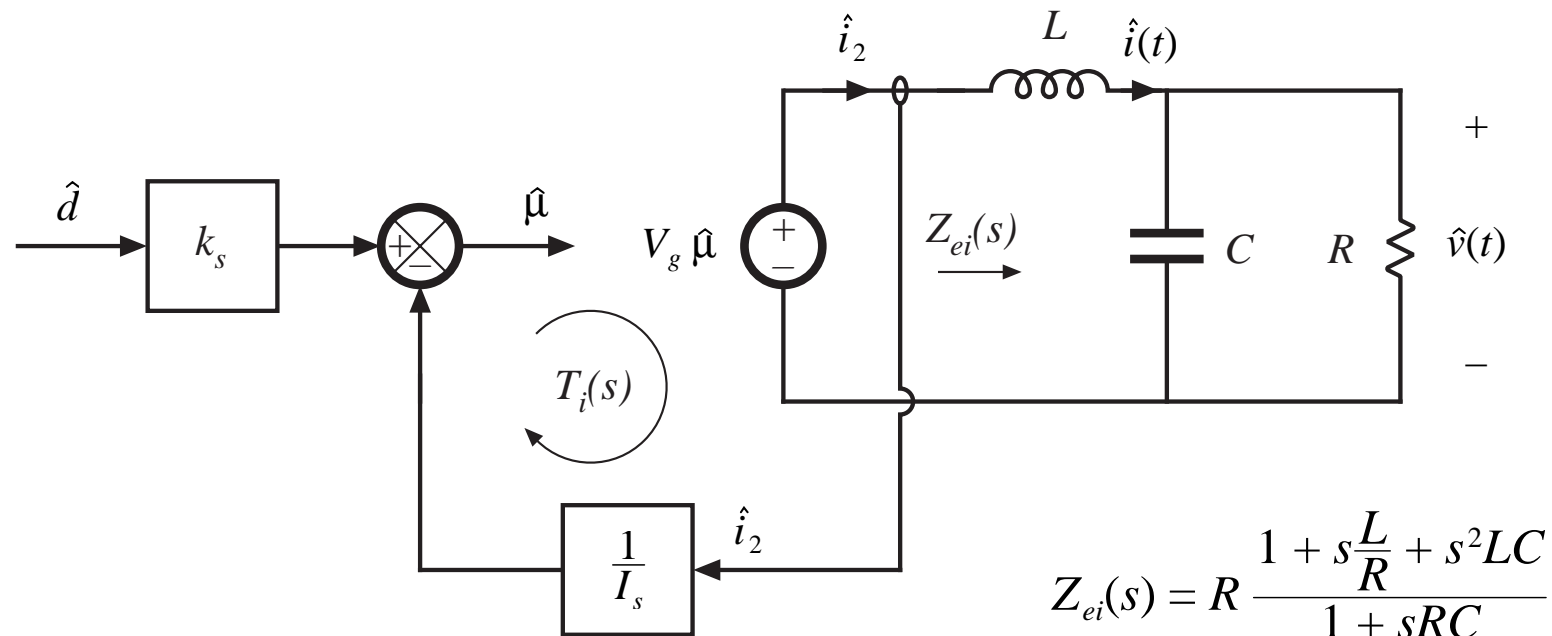
$$G_{vd\infty}(s) = k_s I_s \left( R \parallel \frac{1}{sC} \right)$$






# Magnitude of the loop gain $T_i(s)$

 
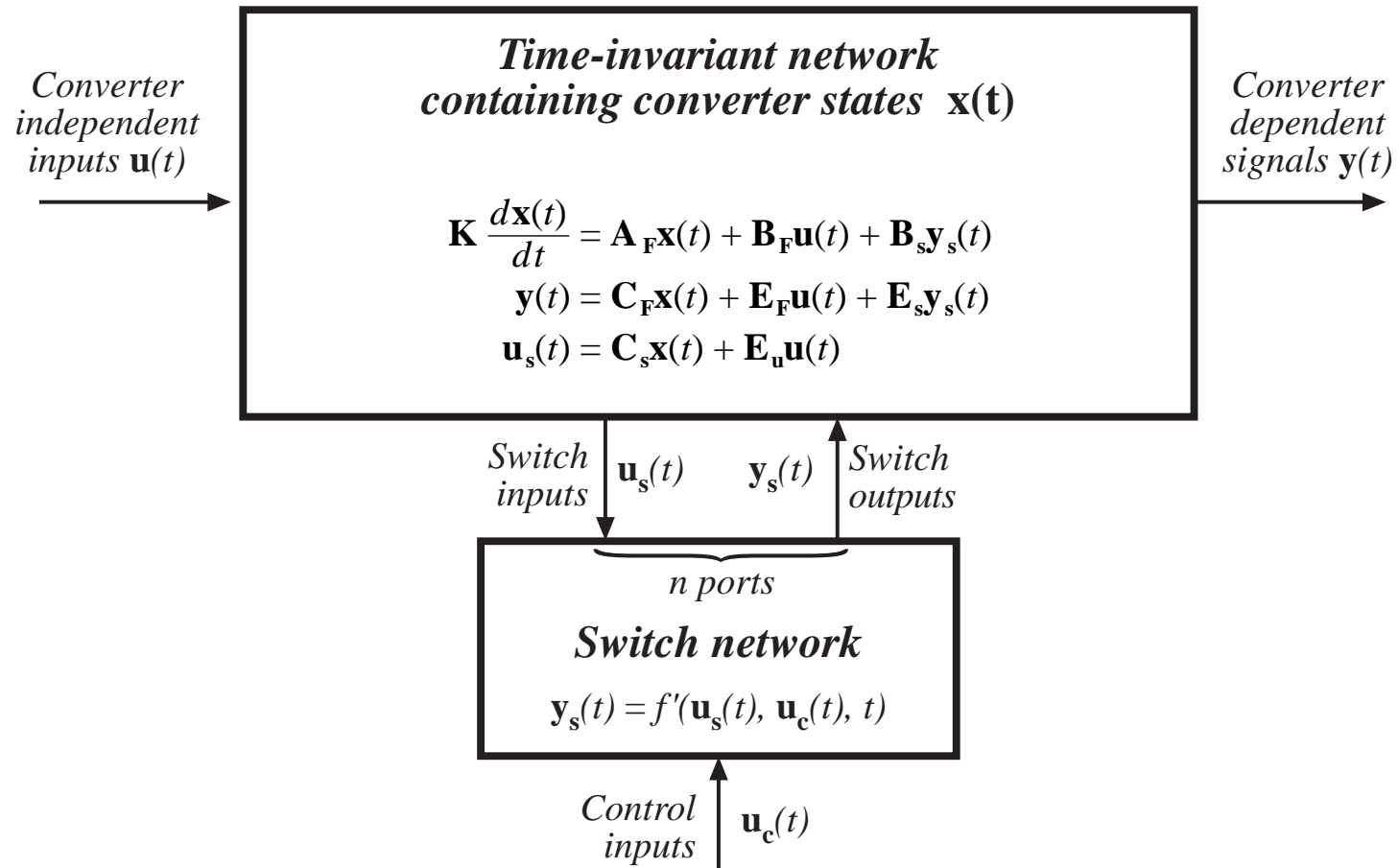
## 10.3.2 Proof of Generalized Averaged Switch Modeling



# System state equations

$$\begin{aligned}\mathbf{K} \frac{d\mathbf{x}(t)}{dt} &= \mathbf{A}_F \mathbf{x}(t) + \mathbf{B}_F \mathbf{u}(t) + \mathbf{B}_s \mathbf{y}_s(t) \\ \mathbf{y}(t) &= \mathbf{C}_F \mathbf{x}(t) + \mathbf{E}_F \mathbf{u}(t) + \mathbf{E}_s \mathbf{y}_s(t) \\ \mathbf{u}_s(t) &= \mathbf{C}_s \mathbf{x}(t) + \mathbf{E}_u \mathbf{u}(t) \\ \mathbf{y}_s(t) &= \mathbf{f}'(\mathbf{u}_s(t), \mathbf{u}_c(t), t)\end{aligned}$$

Average:

$$\begin{aligned}\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} &= \mathbf{A}_F \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_F \langle \mathbf{u}(t) \rangle_{T_s} + \mathbf{B}_s \langle \mathbf{y}_s(t) \rangle_{T_s} \\ \langle \mathbf{y}(t) \rangle_{T_s} &= \mathbf{C}_F \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{E}_F \langle \mathbf{u}(t) \rangle_{T_s} + \mathbf{E}_s \langle \mathbf{y}_s(t) \rangle_{T_s} \\ \langle \mathbf{u}_s(t) \rangle_{T_s} &= \mathbf{C}_s \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{E}_u \langle \mathbf{u}(t) \rangle_{T_s} \\ \langle \mathbf{y}_s(t) \rangle_{T_s} &= \mathbf{f}\left(\langle \mathbf{u}_s(t) \rangle_{T_s}, \langle \mathbf{u}_c(t) \rangle_{T_s}\right)\end{aligned}$$

Also suppose that we can write

$$\langle \mathbf{y}_s(t) \rangle_{T_s} = \mu(t) \mathbf{y}_{s1}(t) + \mu'(t) \mathbf{y}_{s2}(t)$$

*Values of  $\mathbf{y}_s(t)$  during subintervals 1 and 2 are defined as  $\mathbf{y}_{s1}(t)$  and  $\mathbf{y}_{s2}(t)$*

# System averaged state equations

---

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \mathbf{A}_F \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_F \langle \mathbf{u}(t) \rangle_{T_s} + \mu \mathbf{B}_s \mathbf{y}_{s1}(t) + \mu' \mathbf{B}_s \mathbf{y}_{s2}(t)$$

$$\langle \mathbf{y}(t) \rangle_{T_s} = \mathbf{C}_F \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{E}_F \langle \mathbf{u}(t) \rangle_{T_s} + \mu \mathbf{E}_s \mathbf{y}_{s1}(t) + \mu' \mathbf{E}_s \mathbf{y}_{s2}(t)$$

It is desired to relate this to the result of the state-space averaging method, in which the converter state equations for subinterval 1 are written as

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_1 \mathbf{x}(t) + \mathbf{B}_1 \mathbf{u}(t)$$

$$\mathbf{y}(t) = \mathbf{C}_1 \mathbf{x}(t) + \mathbf{E}_1 \mathbf{u}(t)$$

with similar expressions for subinterval 2

But the time-invariant network equations predict that the converter state equations for the first subinterval are

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_F \mathbf{x}(t) + \mathbf{B}_F \mathbf{u}(t) + \mathbf{B}_s \mathbf{y}_{s1}(t)$$

$$\mathbf{y}(t) = \mathbf{C}_F \mathbf{x}(t) + \mathbf{E}_F \mathbf{u}(t) + \mathbf{E}_s \mathbf{y}_{s1}(t)$$

Now equate the two expressions

## Equate the state equation expressions derived via the two methods

---

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_1\mathbf{x}(t) + \mathbf{B}_1\mathbf{u}(t) = \mathbf{A}_F\mathbf{x}(t) + \mathbf{B}_F\mathbf{u}(t) + \mathbf{B}_s\mathbf{y}_{s1}(t)$$
$$\mathbf{y}(t) = \mathbf{C}_1\mathbf{x}(t) + \mathbf{E}_1\mathbf{u}(t) = \mathbf{C}_F\mathbf{x}(t) + \mathbf{E}_F\mathbf{u}(t) + \mathbf{E}_s\mathbf{y}_{s1}(t)$$

Solve for  $\mathbf{B}_s\mathbf{y}_{s1}$  and  $\mathbf{E}_s\mathbf{y}_{s1}$  :

$$\mathbf{B}_s\mathbf{y}_{s1}(t) = (\mathbf{A}_1 - \mathbf{A}_F)\mathbf{x}(t) + (\mathbf{B}_1 - \mathbf{B}_F)\mathbf{u}(t)$$
$$\mathbf{E}_s\mathbf{y}_{s1}(t) = (\mathbf{C}_1 - \mathbf{C}_F)\mathbf{x}(t) + (\mathbf{E}_1 - \mathbf{E}_F)\mathbf{u}(t)$$

Result for subinterval 2:

$$\mathbf{B}_s\mathbf{y}_{s2}(t) = (\mathbf{A}_2 - \mathbf{A}_F)\mathbf{x}(t) + (\mathbf{B}_2 - \mathbf{B}_F)\mathbf{u}(t)$$
$$\mathbf{E}_s\mathbf{y}_{s2}(t) = (\mathbf{C}_2 - \mathbf{C}_F)\mathbf{x}(t) + (\mathbf{E}_2 - \mathbf{E}_F)\mathbf{u}(t)$$

Now plug these results back into averaged state equations

# Averaged state equations

---

$$\begin{aligned}\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} &= \mathbf{A}_F \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{B}_F \langle \mathbf{u}(t) \rangle_{T_s} \\ &+ \mu \left( (\mathbf{A}_1 - \mathbf{A}_F) \langle \mathbf{x}(t) \rangle_{T_s} + (\mathbf{B}_1 - \mathbf{B}_F) \langle \mathbf{u}(t) \rangle_{T_s} \right) \\ &+ \mu' \left( (\mathbf{A}_2 - \mathbf{A}_F) \langle \mathbf{x}(t) \rangle_{T_s} + (\mathbf{B}_2 - \mathbf{B}_F) \langle \mathbf{u}(t) \rangle_{T_s} \right) \\ \langle \mathbf{y}(t) \rangle_{T_s} &= \mathbf{C}_F \langle \mathbf{x}(t) \rangle_{T_s} + \mathbf{E}_F \langle \mathbf{u}(t) \rangle_{T_s} \\ &+ \mu \left( (\mathbf{C}_1 - \mathbf{C}_F) \langle \mathbf{x}(t) \rangle_{T_s} + (\mathbf{E}_1 - \mathbf{E}_F) \langle \mathbf{u}(t) \rangle_{T_s} \right) \\ &+ \mu' \left( (\mathbf{C}_2 - \mathbf{C}_F) \langle \mathbf{x}(t) \rangle_{T_s} + (\mathbf{E}_2 - \mathbf{E}_F) \langle \mathbf{u}(t) \rangle_{T_s} \right)\end{aligned}$$

## Collect terms

---

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left( \mu \mathbf{A}_1 + \mu' \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left( \mu \mathbf{B}_1 + \mu' \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$
$$\langle \mathbf{y}(t) \rangle_{T_s} = \left( \mu \mathbf{C}_1 + \mu' \mathbf{C}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left( \mu \mathbf{E}_1 + \mu' \mathbf{E}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}$$

- This is the desired result. It is identical to the large-signal result of the state-space averaging method, except that the duty cycle  $d$  has been replaced with the conversion ratio  $\mu$ .
- Hence, we can use any result derived via state-space averaging, by simply replacing  $d$  with  $\mu$ .

# Perturb and linearize

---

$$\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = (\mu \mathbf{A}_1 + \mu' \mathbf{A}_2) \langle \mathbf{x}(t) \rangle_{T_s} + (\mu \mathbf{B}_1 + \mu' \mathbf{B}_2) \langle \mathbf{u}(t) \rangle_{T_s}$$
$$\langle \mathbf{y}(t) \rangle_{T_s} = (\mu \mathbf{C}_1 + \mu' \mathbf{C}_2) \langle \mathbf{x}(t) \rangle_{T_s} + (\mu \mathbf{E}_1 + \mu' \mathbf{E}_2) \langle \mathbf{u}(t) \rangle_{T_s}$$

Let

$$\begin{aligned}\langle \mathbf{x}(t) \rangle_{T_s} &= \mathbf{X} + \hat{\mathbf{x}}(t) \\ \langle \mathbf{u}(t) \rangle_{T_s} &= \mathbf{U} + \hat{\mathbf{u}}(t) \\ \langle \mathbf{y}(t) \rangle_{T_s} &= \mathbf{Y} + \hat{\mathbf{y}}(t) \\ \mu(t) &= \mu_0 + \hat{\mu}(t) \\ \langle \mathbf{u}_s(t) \rangle_{T_s} &= \mathbf{U}_s + \hat{\mathbf{u}}_s(t) \\ \langle \mathbf{u}_c(t) \rangle_{T_s} &= \mathbf{U}_c + \hat{\mathbf{u}}_c(t)\end{aligned}$$



# Result

DC model

$$\mathbf{0} = \mathbf{A}\mathbf{X} + \mathbf{B}\mathbf{U}$$

$$\mathbf{Y} = \mathbf{C}\mathbf{X} + \mathbf{E}\mathbf{U}$$

Small-signal  
ac model

$$\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{dt} = \mathbf{A}\hat{\mathbf{x}}(t) + \mathbf{B}\hat{\mathbf{u}}(t) + \left( (\mathbf{A}_1 - \mathbf{A}_2)\mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2)\mathbf{U} \right) \hat{\mu}(t)$$

$$\hat{\mathbf{y}}(t) = \mathbf{C}\hat{\mathbf{x}}(t) + \mathbf{E}\hat{\mathbf{u}}(t) + \left( (\mathbf{C}_1 - \mathbf{C}_2)\mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2)\mathbf{U} \right) \hat{\mu}(t)$$

with the linearized  
switch gains

$$\hat{\mu}(t) = \mathbf{k}_s^T \hat{\mathbf{u}}_s(t) + \mathbf{k}_c^T \hat{\mathbf{u}}_c(t)$$

where

$$\mathbf{A} = (\mu_0 \mathbf{A}_1 + \mu_0' \mathbf{A}_2)$$

$$\mathbf{B} = (\mu_0 \mathbf{B}_1 + \mu_0' \mathbf{B}_2)$$


$$\mathbf{C} = (\mu_0 \mathbf{C}_1 + \mu_0' \mathbf{C}_2)$$

$$\mathbf{E} = (\mu_0 \mathbf{E}_1 + \mu_0' \mathbf{E}_2)$$

$$\mathbf{k}_s^T = \frac{d\mu \left( \langle \mathbf{u}_s(t) \rangle_{T_s}, \langle \mathbf{u}_c(t) \rangle_{T_s} \right)}{d \langle \mathbf{u}_s(t) \rangle_{T_s}} \bigg|_{\substack{\langle \mathbf{u}_s(t) \rangle_{T_s} = \mathbf{U}_s \\ \langle \mathbf{u}_c(t) \rangle_{T_s} = \mathbf{U}_c}}$$

$$\mathbf{k}_c^T = \frac{d\mu \left( \langle \mathbf{u}_s(t) \rangle_{T_s}, \langle \mathbf{u}_c(t) \rangle_{T_s} \right)}{d \langle \mathbf{u}_c(t) \rangle_{T_s}} \bigg|_{\substack{\langle \mathbf{u}_s(t) \rangle_{T_s} = \mathbf{U}_s \\ \langle \mathbf{u}_c(t) \rangle_{T_s} = \mathbf{U}_c}}$$

# A generalized canonical model

 

## 10.4 Summary of Key Points

---

1. In the discontinuous conduction mode, the average transistor voltage and current are proportional, and hence obey Ohm's law. An averaged equivalent circuit can be obtained by replacing the transistor with an effective resistor  $R_e(d)$ . The average diode voltage and current obey a power source characteristic, with power equal to the power effectively dissipated by  $R_e$ . In the averaged equivalent circuit, the diode is replaced with a dependent power source.
2. The two-port lossless network consisting of an effective resistor and power source, which results from averaging the transistor and diode waveforms of DCM converters, is called a loss-free resistor. This network models the basic power-processing functions of DCM converters, much in the same way that the ideal dc transformer models the basic functions of CCM converters.
3. The large-signal averaged model can be solved under equilibrium conditions to determine the quiescent values of the converter currents and voltages. Average power arguments can often be used.

## Key points

---

4. A small-signal ac model for the DCM switch network can be derived by perturbing and linearizing the loss-free resistor network. The result has the form of a two-port  $y$ -parameter model. The model describes the small-signal variations in the transistor and diode currents, as functions of variations in the duty cycle and in the transistor and diode ac voltage variations. This model is most convenient for ac analysis of the buck-boost converter.
5. To simplify the ac analysis of the DCM buck and boost converters, it is convenient to define two other forms of the small-signal switch model, corresponding to the switch networks of Figs. 10.16(a) and 10.16(b). These models are also  $y$ -parameter two-port models, but have different parameter values.

## Key points

---

6. Since the inductor value is small when the converter operates in the discontinuous conduction mode, the inductor dynamics of the DCM buck, boost, and buck-boost converters occur at high frequency, above or just below the switching frequency. Hence, in most cases the inductor dynamics can be ignored. In the small-signal ac model, the inductance  $L$  is set to zero, and the remaining model is solved relatively easily for the low-frequency converter dynamics. The DCM buck, boost, and buck-boost converters exhibit transfer functions containing a single low-frequency dominant pole.
7. It is also possible to adapt the CCM models developed in Chapter 7 to treat converters with switches that operate in DCM, as well as other switches discussed in later chapters. The switch conversion ratio  $\mu$  is a generalization of the duty cycle  $d$  of CCM switch networks; this quantity can be substituted in place of  $d$  in any CCM model. The result is a model that is valid for DCM operation. Hence, existing CCM models can be adapted directly.


## Key points

---


8. The conversion ratio  $\mu$  of DCM switch networks is a function of the applied voltage and current. As a result, the switch network contains effective feedback. So the small-signal model of a DCM converter can be expressed as the CCM converter model, plus effective feedback representing the behavior of the DCM switch network. Two effects of this feedback are increase of the converter output impedance via current feedback, and decrease of the  $Q$ -factor of the transfer function poles. The pole arising from the inductor dynamics occurs at the crossover frequency of the effective current feedback loop.

# Chapter 11

## Current Programmed Control

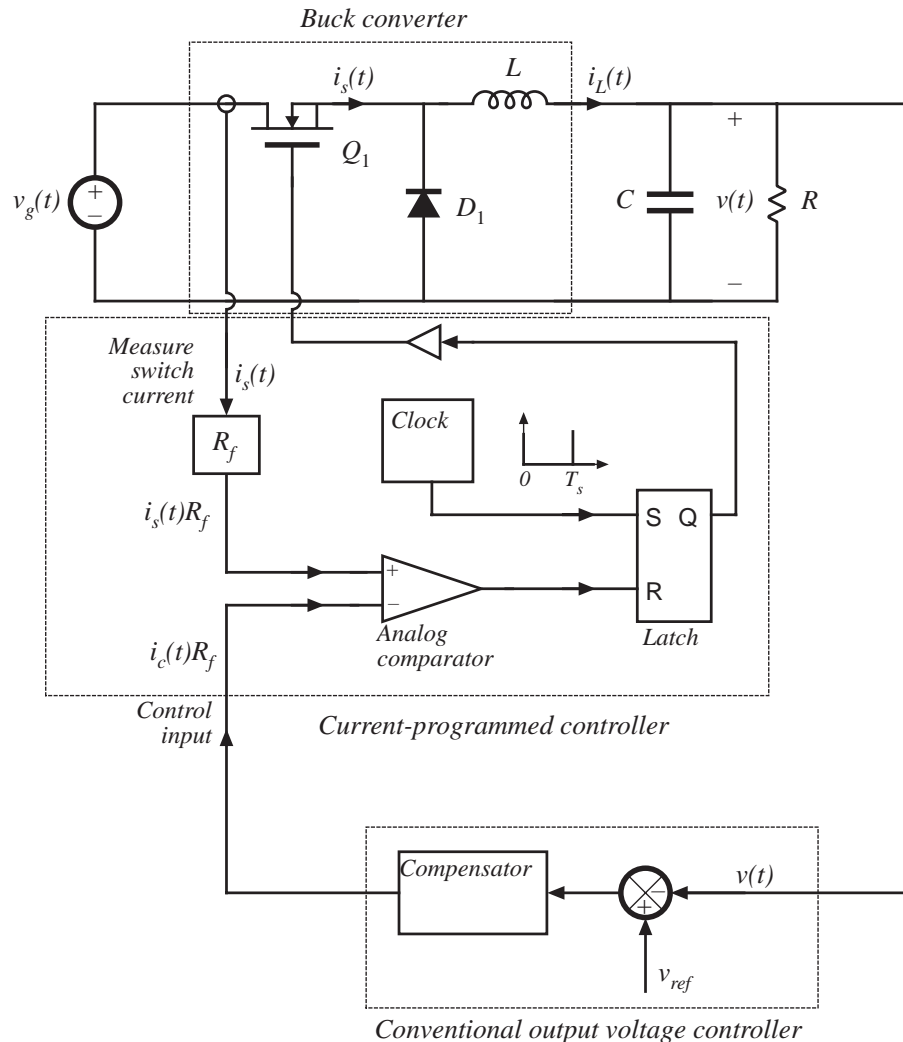

 The peak transistor current replaces the duty cycle as the converter control input.



# Current programmed control vs. duty cycle control

---

Advantages of current programmed control:

- Simpler dynamics —inductor pole is moved to high frequency
- Simple robust output voltage control, with large phase margin, can be obtained without use of compensator lead networks
- It is always necessary to sense the transistor current, to protect against overcurrent failures. We may as well use the information during normal operation, to obtain better control
- Transistor failures due to excessive current can be prevented simply by limiting  $i_c(t)$
- Transformer saturation problems in bridge or push-pull converters can be mitigated

A disadvantage: susceptibility to noise



# Chapter 11: Outline

---

- 11.1 Oscillation for  $D > 0.5$
- 11.2 A simple first-order model
  - Simple model via algebraic approach
  - Averaged switch modeling
- 11.3 A more accurate model
  - Current programmed controller model: block diagram
  - CPM buck converter example
- 11.4 Discontinuous conduction mode
- 11.5 Summary

## 11.1 Oscillation for $D > 0.5$


---

- The current programmed controller is inherently unstable for  $D > 0.5$ , regardless of the converter topology
- Controller can be stabilized by addition of an artificial ramp

Objectives of this section:

- Stability analysis
- Describe artificial ramp scheme

# Inductor current waveform, CCM

 

*Inductor current slopes  $m_1$  and  $-m_2$*

buck converter

$$m_1 = \frac{v_g - v}{L} \quad -m_2 = -\frac{v}{L}$$

boost converter

$$m_1 = \frac{v_g}{L} \quad -m_2 = \frac{v_g - v}{L}$$

buck–boost converter

$$m_1 = \frac{v_g}{L} \quad -m_2 = \frac{v}{L}$$

# Steady-state inductor current waveform, CPM

First interval:

$$i_L(dT_s) = i_c = i_L(0) + m_1 dT_s$$

Solve for  $d$ :

$$d = \frac{i_c - i_L(0)}{m_1 T_s}$$


Second interval:

$$\begin{aligned} i_L(T_s) &= i_L(dT_s) - m_2 d' T_s \\ &= i_L(0) + m_1 dT_s - m_2 d' T_s \end{aligned}$$


In steady state:

$$0 = M_1 D T_s - M_2 D' T_s$$


$$\frac{M_2}{M_1} = \frac{D}{D'}$$

 

# Perturbed inductor current waveform

 
 
# Change in inductor current perturbation over one switching period



$$\hat{i}_L(0) = -m_1 \hat{d}T_s$$

$$\hat{i}_L(T_s) = m_2 \hat{d}T_s$$

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left( -\frac{D}{D'} \right)$$

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left( -\frac{m_2}{m_1} \right)$$

# Change in inductor current perturbation over many switching periods

---

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left( -\frac{D}{D'} \right)$$

$$\hat{i}_L(2T_s) = \hat{i}_L(T_s) \left( -\frac{D}{D'} \right) = \hat{i}_L(0) \left( -\frac{D}{D'} \right)^2$$


$$\hat{i}_L(nT_s) = \hat{i}_L((n-1)T_s) \left( -\frac{D}{D'} \right) = \hat{i}_L(0) \left( -\frac{D}{D'} \right)^n$$

$$|\hat{i}_L(nT_s)| \rightarrow \begin{cases} 0 & \text{when } \left| -\frac{D}{D'} \right| < 1 \\ \infty & \text{when } \left| -\frac{D}{D'} \right| > 1 \end{cases}$$

For stability:  $D < 0.5$
 
## Example: unstable operation for $D = 0.6$


$$\alpha = -\frac{D}{D'} = \left(-\frac{0.6}{0.4}\right) = -1.5$$






 
## Example: stable operation for $D = 1/3$

$$\alpha = -\frac{D}{D'} = \left(-\frac{1/3}{2/3}\right) = -0.5$$


  
# Stabilization via addition of an artificial ramp to the measured switch current waveform



Now, transistor switches off when


$$i_a(dT_s) + i_L(dT_s) = i_c$$

or,


$$i_L(dT_s) = i_c - i_a(dT_s)$$

# Steady state waveforms with artificial ramp

$$i_L(dT_s) = i_c - i_a(dT_s)$$

 

# Stability analysis: perturbed waveform

 

# Stability analysis: change in perturbation over complete switching periods

---

First subinterval:

$$\hat{i}_L(0) = -\hat{d}T_s (m_1 + m_a)$$

Second subinterval:

$$\hat{i}_L(T_s) = -\hat{d}T_s (m_a - m_2)$$

Net change over one switching period:

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left( -\frac{m_2 - m_a}{m_1 + m_a} \right)$$

After  $n$  switching periods:

$$\hat{i}_L(nT_s) = \hat{i}_L((n-1)T_s) \left( -\frac{m_2 - m_a}{m_1 + m_a} \right) = \hat{i}_L(0) \left( -\frac{m_2 - m_a}{m_1 + m_a} \right)^n = \hat{i}_L(0) \alpha^n$$

Characteristic value:

$$\alpha = -\frac{m_2 - m_a}{m_1 + m_a} \quad \left| \hat{i}_L(nT_s) \right| \rightarrow \begin{cases} 0 & \text{when } |\alpha| < 1 \\ \infty & \text{when } |\alpha| > 1 \end{cases}$$


# The characteristic value $\alpha$

---

$$\alpha = - \frac{1 - \frac{m_a}{m_2}}{\frac{D'}{D} + \frac{m_a}{m_2}}$$

- For stability, require  $|\alpha| < 1$
- Buck and buck-boost converters:  $m_2 = -v/L$   
So if  $v$  is well-regulated, then  $m_2$  is also well-regulated
- A common choice:  $m_a = 0.5 m_2$   
This leads to  $\alpha = -1$  at  $D = 1$ , and  $|\alpha| < 1$  for  $0 \leq D < 1$ .  
The minimum  $\alpha$  that leads to stability for all  $D$ .
- Another common choice:  $m_a = m_2$   
This leads to  $\alpha = 0$  for  $0 \leq D < 1$ .  
Deadbeat control, finite settling time

## 11.2 A Simple First-Order Model

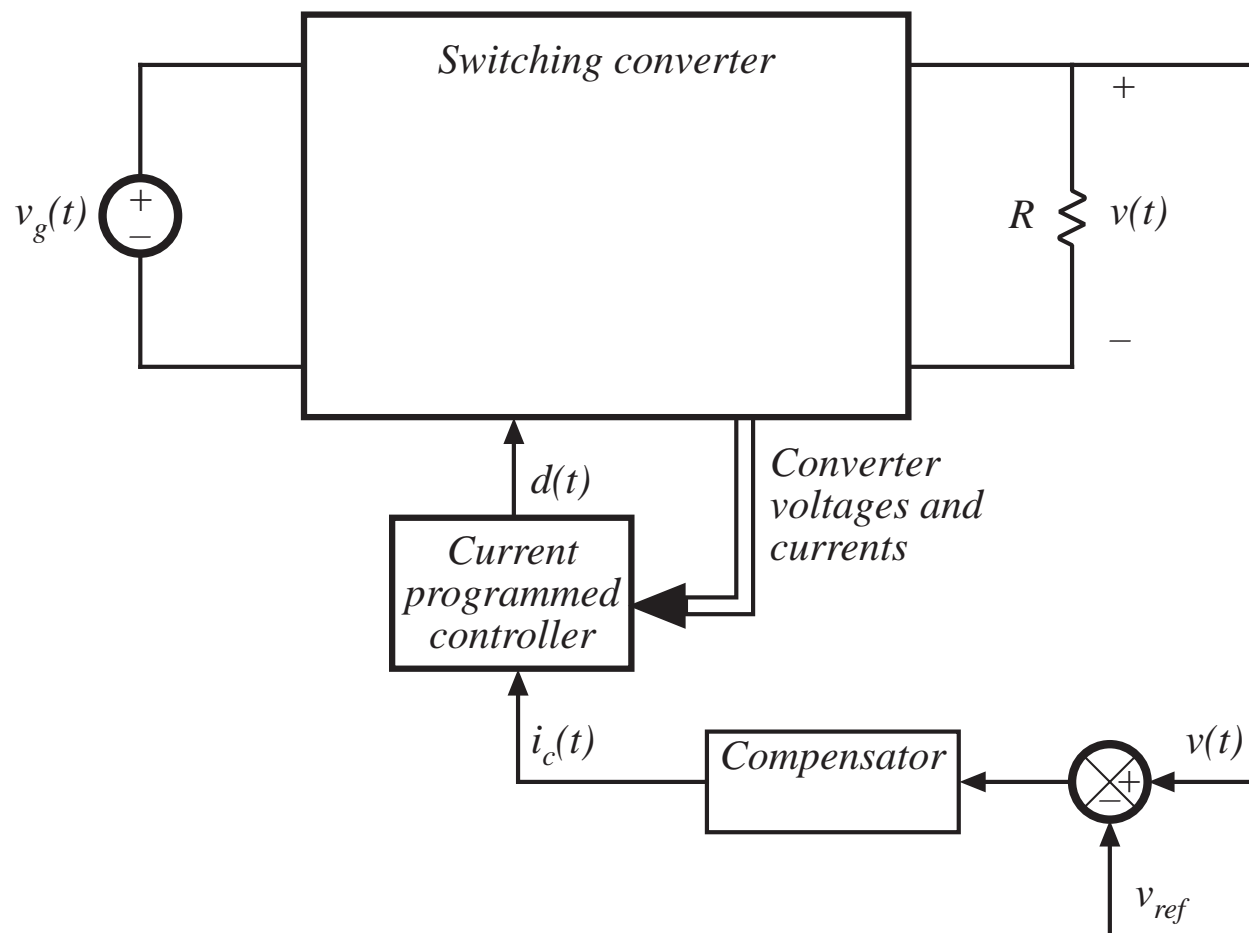

# The first-order approximation

---



$$\langle i_L(t) \rangle_{T_s} = i_c(t)$$

- Neglects switching ripple and artificial ramp
- Yields physical insight and simple first-order model
- Accurate when converter operates well into CCM (so that switching ripple is small) and when the magnitude of the artificial ramp is not too large
- Resulting small-signal relation:

$$\hat{i}_L(s) \approx \hat{i}_c(s)$$


  
## 11.2.1 Simple model via algebraic approach: CCM buck-boost example



## Small-signal equations of CCM buck–boost, duty cycle control

---

$$L \frac{d\hat{i}_L(t)}{dt} = D\hat{v}_g(t) + D'\hat{v}(t) + (V_g - V)\hat{d}(t)$$

$$C \frac{d\hat{v}(t)}{dt} = -D'\hat{i}_L - \frac{\hat{v}(t)}{R} + I_L\hat{d}(t)$$

$$\hat{i}_g(t) = D\hat{i}_L + I_L\hat{d}(t)$$

Derived in Chapter 7

## Transformed equations

---

Take Laplace transform, letting initial conditions be zero:

$$sL\hat{i}_L(s) = D\hat{v}_g(s) + D'\hat{v}(s) + (V_g - V)\hat{d}(s)$$

$$sC\hat{v}(s) = -D'\hat{i}_L(s) - \frac{\hat{v}(s)}{R} + I_L\hat{d}(s)$$

$$\hat{i}_g(s) = D\hat{i}_L(s) + I_L\hat{d}(s)$$

## The simple approximation

---

Now let

$$\hat{i}_L(s) \approx \hat{i}_c(s)$$

Eliminate the duty cycle (now an intermediate variable), to express the equations using the new control input  $i_L$ . The inductor equation becomes:

$$sL\hat{i}_c(s) \approx D\hat{v}_g(s) + D'\hat{v}(s) + (V_g - V)\hat{d}(s)$$

Solve for the duty cycle variations:

$$\hat{d}(s) = \frac{sL\hat{i}_c(s) - D\hat{v}_g(s) - D'\hat{v}(s)}{(V_g - V)}$$

## The simple approximation, continued

---

Substitute this expression to eliminate the duty cycle from the remaining equations:

$$sC\hat{v}(s) = -D'\hat{i}_c(s) - \frac{\hat{v}(s)}{R} + I_L \frac{sL\hat{i}_c(s) - D\hat{v}_g(s) - D'\hat{v}(s)}{(V_g - V)}$$

$$\hat{i}_g(s) = D\hat{i}_c(s) + I_L \frac{sL\hat{i}_c(s) - D\hat{v}_g(s) - D'\hat{v}(s)}{(V_g - V)}$$


Collect terms, simplify using steady-state relations:

$$sC\hat{v}(s) = \left( \frac{sLD}{D'R} - D' \right) \hat{i}_c(s) - \left( \frac{D}{R} + \frac{1}{R} \right) \hat{v}(s) - \left( \frac{D^2}{D'R} \right) \hat{v}_g(s)$$

$$\hat{i}_g(s) = \left( \frac{sLD}{D'R} + D \right) \hat{i}_c(s) - \left( \frac{D}{R} \right) \hat{v}(s) - \left( \frac{D^2}{D'R} \right) \hat{v}_g(s)$$

 
## Construct equivalent circuit: input port

$$\hat{i}_g(s) = \left( \frac{sLD}{D'R} + D \right) \hat{i}_c(s) - \left( \frac{D}{R} \right) \hat{v}(s) - \left( \frac{D^2}{D'R} \right) \hat{v}_g(s)$$



 
## Construct equivalent circuit: output port

$$sC\hat{v}(s) = \left( \frac{sLD}{D'R} - D' \right) \hat{i}_c(s) - \left( \frac{D}{R} + \frac{1}{R} \right) \hat{v}(s) - \left( \frac{D^2}{D'R} \right) \hat{v}_g(s)$$


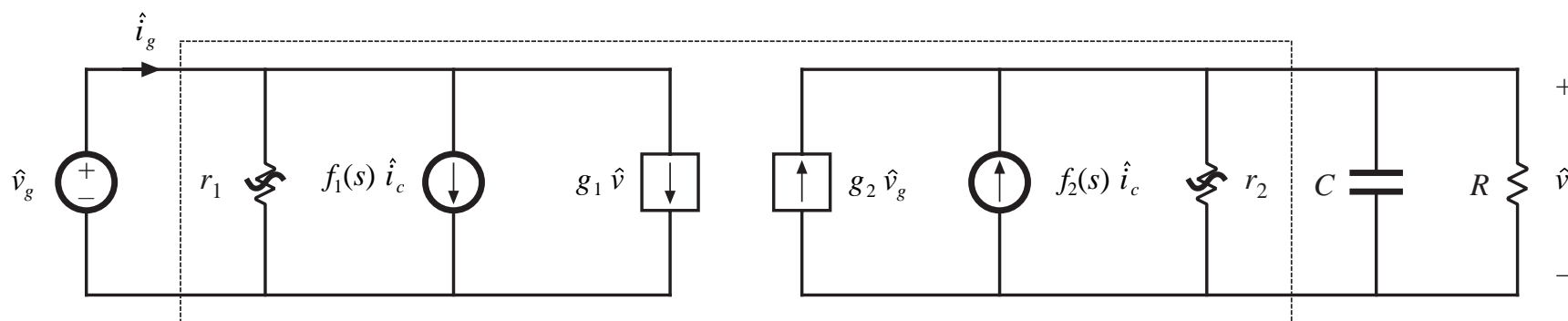
# CPM Canonical Model, Simple Approximation






# Table of results for basic converters

**Table 11.1** Current programmed mode small-signal equivalent circuit parameters, simple model

Converter	$g_1$	$f_1$	$r_1$	$g_2$	$f_2$	$r_2$
Buck	$\frac{D}{R}$	$D \left( 1 + \frac{sL}{R} \right)$	$-\frac{R}{D^2}$	0	1	$\infty$
Boost	0	1	$\infty$	$\frac{1}{D'R}$	$D' \left( 1 - \frac{sL}{D'^2 R} \right)$	$R$
Buck-boost	$-\frac{D}{R}$	$D \left( 1 + \frac{sL}{D'R} \right)$	$-\frac{D'R}{D^2}$	$-\frac{D^2}{D'R}$	$-D' \left( 1 - \frac{sDL}{D'^2 R} \right)$	$\frac{R}{D}$
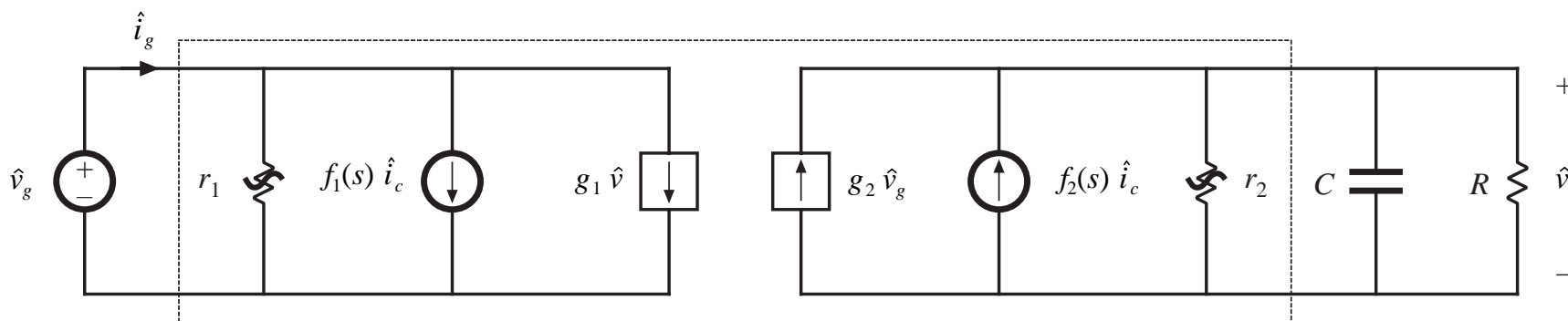
# Transfer functions predicted by simple model




*Control-to-output transfer function*

$$G_{vc}(s) = \left. \frac{\hat{v}(s)}{\hat{i}_c(s)} \right|_{\hat{v}_g=0} = f_2 \left( r_2 \parallel R \parallel \frac{1}{sC} \right)$$

*Result for buck-boost example*

$$G_{vc}(s) = -R \frac{D'}{1+D} \frac{\left( 1 - s \frac{DL}{D'^2 R} \right)}{\left( 1 + s \frac{RC}{1+D} \right)}$$
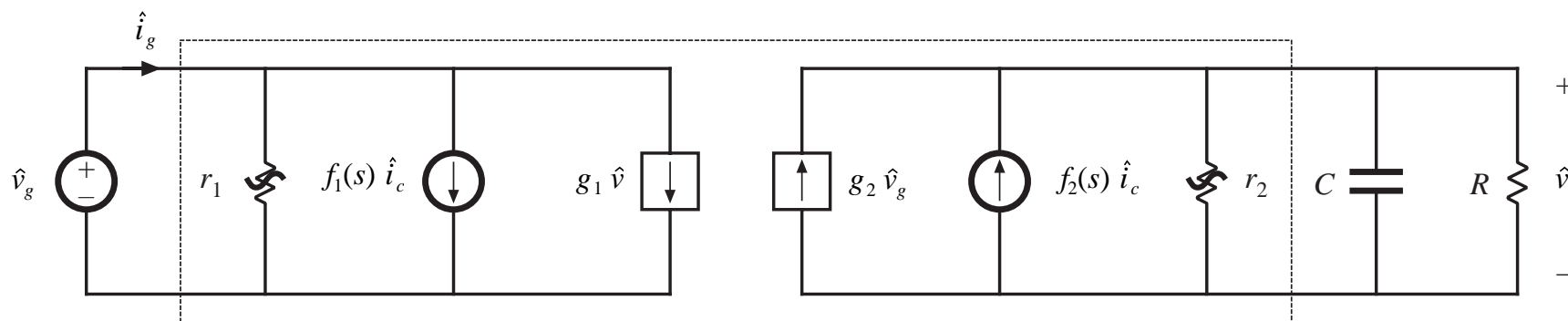
# Transfer functions predicted by simple model




*Line-to-output transfer function*

$$G_{vg}(s) = \left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\hat{i}_c=0} = g_2 \left( r_2 \parallel R \parallel \frac{1}{sC} \right)$$

*Result for buck-boost example*

$$G_{vg}(s) = -\frac{D^2}{1-D^2} \frac{1}{\left( 1 + s \frac{RC}{1+D} \right)}$$
 
# Transfer functions predicted by simple model




*Output impedance*

$$Z_{out}(s) = r_2 \parallel R \parallel \frac{1}{sC}$$

*Result for buck-boost example*

$$Z_{out}(s) = \frac{R}{1 + D} \frac{1}{\left(1 + s \frac{RC}{1 + D}\right)}$$
 
## 11.2.2 Averaged switch modeling with the simple approximation



*Averaged terminal waveforms,*

*CCM:*

$$\begin{aligned}\langle v_2(t) \rangle_{T_s} &= d(t) \langle v_1(t) \rangle_{T_s} \\ \langle i_1(t) \rangle_{T_s} &= d(t) \langle i_2(t) \rangle_{T_s}\end{aligned}$$

*The simple approximation:*

$$\langle i_2(t) \rangle_{T_s} \approx \langle i_c(t) \rangle_{T_s}$$

## CPM averaged switch equations

---

$$\begin{aligned}\langle v_2(t) \rangle_{T_s} &= d(t) \langle v_1(t) \rangle_{T_s} & \langle i_2(t) \rangle_{T_s} &\approx \langle i_c(t) \rangle_{T_s} \\ \langle i_1(t) \rangle_{T_s} &= d(t) \langle i_2(t) \rangle_{T_s}\end{aligned}$$


Eliminate duty cycle:

$$\begin{aligned}\langle i_1(t) \rangle_{T_s} &= d(t) \langle i_c(t) \rangle_{T_s} = \frac{\langle v_2(t) \rangle_{T_s}}{\langle v_1(t) \rangle_{T_s}} \langle i_c(t) \rangle_{T_s} \\ \langle i_1(t) \rangle_{T_s} \langle v_1(t) \rangle_{T_s} &= \langle i_c(t) \rangle_{T_s} \langle v_2(t) \rangle_{T_s} = \langle p(t) \rangle_{T_s}\end{aligned}$$

So:


- Output port is a current source
- Input port is a dependent current sink

# CPM averaged switch model

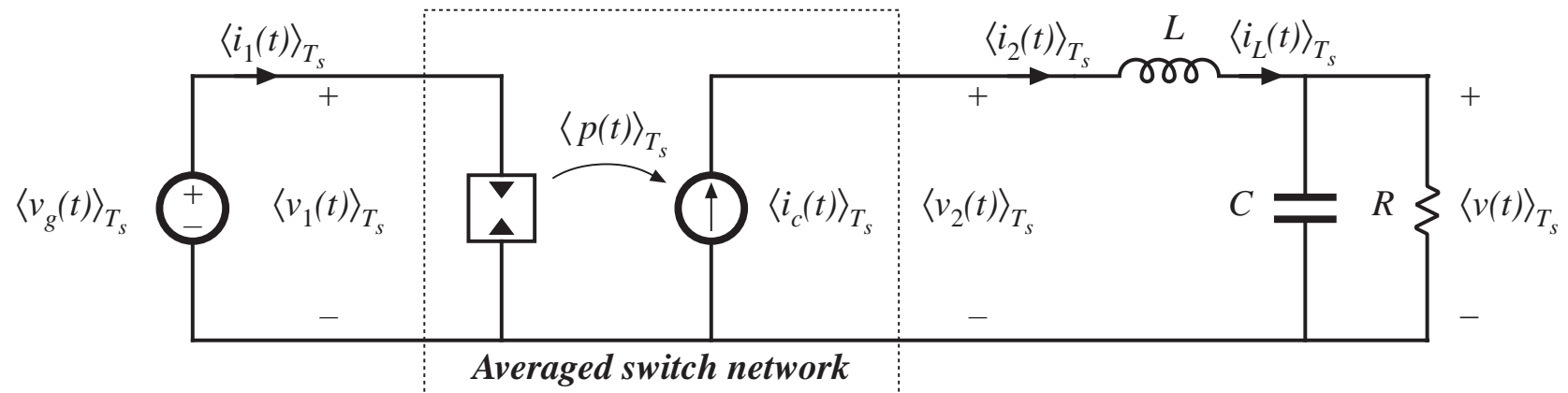


# Results for other converters

*Boost*

 

*Buck-boost*

 



## Perturbation and linearization to construct small-signal model

---

Let

$$\langle v_1(t) \rangle_{T_s} = V_1 + \hat{v}_1(t)$$

$$\langle i_1(t) \rangle_{T_s} = I_1 + \hat{i}_1(t)$$

$$\langle v_2(t) \rangle_{T_s} = V_2 + \hat{v}_2(t)$$

$$\langle i_2(t) \rangle_{T_s} = I_2 + \hat{i}_2(t)$$

$$\langle i_c(t) \rangle_{T_s} = I_c + \hat{i}_c(t)$$

Resulting input port equation:

$$(V_1 + \hat{v}_1(t)) (I_1 + \hat{i}_1(t)) = (I_c + \hat{i}_c(t)) (V_2 + \hat{v}_2(t))$$

Small-signal result:


$$\hat{i}_1(t) = \hat{i}_c(t) \frac{V_2}{V_1} + \hat{v}_2(t) \frac{I_c}{V_1} - \hat{v}_1(t) \frac{I_1}{V_1}$$

Output port equation:

$$\hat{i}_2 = \hat{i}_c$$


# Resulting small-signal model

## Buck example

 


$$\hat{i}_1(t) = \hat{i}_c(t) \frac{V_2}{V_1} + \hat{v}_2(t) \frac{I_c}{V_1} - \hat{v}_1(t) \frac{I_1}{V_1}$$
 
# Origin of input port negative incremental resistance



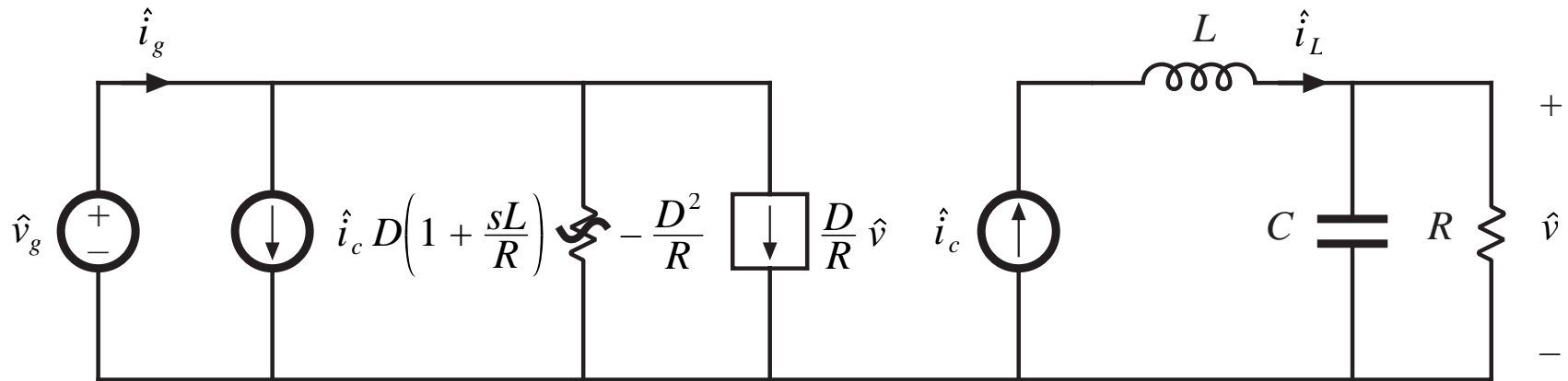
## Expressing the equivalent circuit in terms of the converter input and output voltages



$$\hat{i}_1(s) = D \left( 1 + s \frac{L}{R} \right) \hat{i}_c(s) + \frac{D}{R} \hat{v}(s) - \frac{D^2}{R} \hat{v}_g(s)$$
 
## Predicted transfer functions of the CPM buck converter



$$G_{vc}(s) = \left. \frac{\hat{v}(s)}{\hat{i}_c(s)} \right|_{\hat{v}_g=0} = \left( R \parallel \frac{1}{sC} \right)$$

$$G_{vg}(s) = \left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\hat{i}_c=0} = 0$$

## 11.3 A More Accurate Model

---


- The simple models of the previous section yield insight into the low-frequency behavior of CPM converters
- Unfortunately, they do not always predict everything that we need to know:

Line-to-output transfer function of the buck converter

Dynamics at frequencies approaching  $f_s$

- More accurate model accounts for nonideal operation of current mode controller built-in feedback loop
- Converter duty-cycle-controlled model, plus block diagram that accurately models equations of current mode controller
 
## 11.3.1 Current programmed controller model



$$\begin{aligned} \langle i_L(t) \rangle_{T_s} &= \langle i_c(t) \rangle_{T_s} - m_a dT_s - d \frac{m_1 dT_s}{2} - d' \frac{m_2 d'T_s}{2} \\ &= \langle i_c(t) \rangle_{T_s} - m_a dT_s - m_1 \frac{d^2 T_s}{2} - m_2 \frac{d'^2 T_s}{2} \end{aligned}$$

# Perturb

Let

$$\langle i_L(t) \rangle_{T_s} = I_L + \hat{i}_L(t)$$

$$\langle i_c(t) \rangle_{T_s} = I_c + \hat{i}_c(t)$$

$$d(t) = D + \hat{d}(t)$$

$$m_1(t) = M_1 + \hat{m}_1(t)$$

$$m_2(t) = M_2 + \hat{m}_2(t)$$

It is assumed that the artificial ramp slope does not vary.

*Note that it is necessary to perturb the slopes, since these depend on the applied inductor voltage. For basic converters,*

buck converter

$$\hat{m}_1 = \frac{\hat{v}_g - \hat{v}}{L} \quad \hat{m}_2 = \frac{\hat{v}}{L}$$

boost converter

$$\hat{m}_1 = \frac{\hat{v}_g}{L} \quad \hat{m}_2 = \frac{\hat{v} - \hat{v}_g}{L}$$

buck-boost converter

$$\hat{m}_1 = \frac{\hat{v}_g}{L} \quad \hat{m}_2 = -\frac{\hat{v}}{L}$$



# Linearize

$$\begin{aligned} (I_L + \hat{i}_L(t)) = & (I_c + \hat{i}_c(t)) - M_a T_s (D + \hat{d}(t)) - (M_1 + \hat{m}_1(t)) (D + \hat{d}(t))^2 \frac{T_s}{2} \\ & - (M_2 + \hat{m}_2(t)) (D' - \hat{d}(t))^2 \frac{T_s}{2} \end{aligned}$$

The first-order ac terms are

$$\hat{i}_L(t) = \hat{i}_c(t) - \left( M_a T_s + D M_1 T_s - D' M_2 T_s \right) \hat{d}(t) - \frac{D^2 T_s}{2} \hat{m}_1(t) - \frac{D'^2 T_s}{2} \hat{m}_2(t)$$

Simplify using dc relationships:

$$\hat{i}_L(t) = \hat{i}_c(t) - M_a T_s \hat{d}(t) - \frac{D^2 T_s}{2} \hat{m}_1(t) - \frac{D'^2 T_s}{2} \hat{m}_2(t)$$

Solve for duty cycle variations:

$$\hat{d}(t) = \frac{1}{M_a T_s} \left[ \hat{i}_c(t) - \hat{i}_L(t) - \frac{D^2 T_s}{2} \hat{m}_1(t) - \frac{D'^2 T_s}{2} \hat{m}_2(t) \right]$$

# Equation of the current programmed controller

The expression for the duty cycle is of the general form

$$\hat{d}(t) = F_m \left[ \hat{i}_c(t) - \hat{i}_L(t) - F_g \hat{v}_g(t) - F_v \hat{v}(t) \right]$$


$$F_m = 1/M_a T_s$$

Table 11.2. Current programmed controller gains for basic converters

Converter	$F_g$	$F_v$
Buck	$\frac{D^2 T_s}{2L}$	$\frac{(1 - 2D) T_s}{2L}$
Boost	$\frac{(2D - 1) T_s}{2L}$	$\frac{D'^2 T_s}{2L}$
Buck-boost	$\frac{D^2 T_s}{2L}$	$-\frac{D'^2 T_s}{2L}$

 
## Block diagram of the current programmed controller

$$\hat{d}(t) = F_m \left[ \hat{i}_c(t) - \hat{i}_L(t) - F_g \hat{v}_g(t) - F_v \hat{v}(t) \right]$$




- Describes the duty cycle chosen by the CPM controller
- Append this block diagram to the duty cycle controlled converter model, to obtain a complete CPM system model


# CPM buck converter model

 


# CPM boost converter model

 


# CPM buck-boost converter model

 
 
## 11.3.2 Example: analysis of CPM buck converter


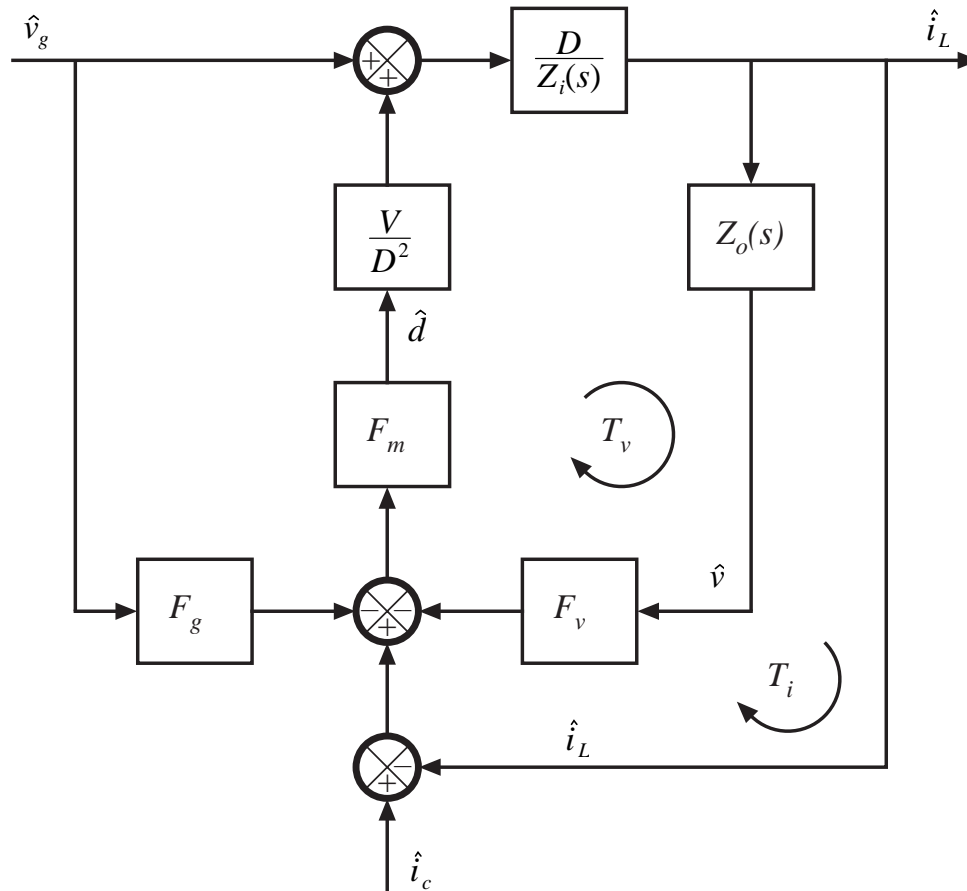
## Block diagram of entire CPM buck converter



Voltage loop gain:

$$T_v(s) = F_m \frac{V}{D^2} \frac{D}{Z_i(s)} Z_o(s) F_v$$

Current loop gain:

$$T_i(s) = \frac{1}{Z_o(s) F_v} \frac{T_v(s)}{1 + T_v(s)}$$

$$T_i(s) = \frac{F_m \frac{V}{D^2} \frac{D}{Z_i(s)}}{1 + F_m \frac{V}{D^2} \frac{D}{Z_i(s)} Z_o(s) F_v}$$

Transfer function from  $\hat{i}_c$  to  $\hat{i}_L$ :

$$\frac{\hat{i}_L(s)}{\hat{i}_c(s)} = \frac{T_i(s)}{1 + T_i(s)}$$



## Discussion: Transfer function from $\hat{i}_c$ to $\hat{i}_L$

---

- When the loop gain  $T_i(s)$  is large in magnitude, then  $\hat{i}_L$  is approximately equal to  $\hat{i}_c$ . The results then coincide with the simple approximation. 
$$\frac{\hat{i}_L(s)}{\hat{i}_c(s)} = \frac{T_i(s)}{1 + T_i(s)}$$
- The control-to-output transfer function can be written as

$$G_{vc}(s) = \frac{\hat{v}(s)}{\hat{i}_c(s)} = Z_o(s) \frac{T_i(s)}{1 + T_i(s)}$$

which is the simple approximation result, multiplied by the factor  $T_i/(1 + T_i)$ .

# Loop gain $T_i(s)$

---

Result for the buck converter:


$$T_i(s) = \left( K \frac{1 - \alpha}{1 + \alpha} \right) \frac{(1 + sRC)}{1 + s \left( \frac{L}{R} \frac{2DM_a}{M_2} \frac{1 - \alpha}{1 + \alpha} \right) + s^2 \left( LC \frac{2DM_a}{M_2} \frac{1 - \alpha}{1 + \alpha} \right)}$$

Characteristic value  $\alpha = - \frac{1 - \frac{m_a}{m_2}}{\frac{D'}{D} + \frac{m_a}{m_2}}$  Controller stable for  $|\alpha| < 1$

$$K = 2L/RT_s$$

CCM for  $K > D'$

# Loop gain

 

$$T_i(s) = T_{i0} \frac{\left(1 + \frac{s}{\omega_z}\right)}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

$$T_{i0} = K \frac{1 - \alpha}{1 + \alpha}$$

$$\omega_z = \frac{1}{RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC \frac{2DM_a}{M_2} \frac{1 - \alpha}{1 + \alpha}}}$$

$$Q = R \sqrt{\frac{C}{L}} \sqrt{\frac{M_2}{2DM_a} \frac{1 + \alpha}{1 - \alpha}}$$

# Crossover frequency $f_c$

---

High frequency asymptote of  $T_i$  is

$$T_i(s) \approx T_{i0} \frac{\left(\frac{s}{\omega_z}\right)}{\left(\frac{s}{\omega_0}\right)^2} = T_{i0} \frac{\omega_0^2}{s\omega_z}$$

Equate magnitude to one at crossover frequency:

$$\|T_i(j2\pi f_c)\| \approx T_{i0} \frac{f_0^2}{2\pi f_c f_z} = 1$$

Solve for crossover frequency:

$$f_c = \frac{M_2}{M_a} \frac{f_s}{2\pi D}$$

# Construction of transfer functions

---

$$\frac{\hat{i}_L(s)}{\hat{i}_c(s)} = \frac{T_i(s)}{1 + T_i(s)} \approx \frac{1}{\left(1 + \frac{s}{\omega_c}\right)}$$

$$G_{vc}(s) = Z_o(s) \frac{T_i(s)}{1 + T_i(s)} \approx R \frac{1}{\left(1 + sRC\right) \left(1 + \frac{s}{\omega_c}\right)}$$

—the result of the simple first-order model, with an added pole at the loop crossover frequency

## Exact analysis

---

$$G_{vc}(s) = R \left( \frac{T_{i0}}{1 + T_{i0}} \right) \frac{1}{1 + s \left( \frac{T_{i0}}{1 + T_{i0}} \frac{1}{\omega_z} + \frac{1}{(1 + T_{i0}) Q \omega_0} \right) + \frac{1}{1 + T_{i0}} \left( \frac{s}{\omega_0} \right)^2}$$

for  $|T_{i0}| \gg 1$ ,

$$G_{vc}(s) \approx R \frac{1}{1 + \frac{s}{\omega_z} + \frac{s^2}{T_{i0} \omega_0^2}}$$

Low  $Q$  approximation:

$$G_{vc}(s) \approx R \frac{1}{\left( 1 + \frac{s}{\omega_z} \right) \left( 1 + \frac{s \omega_z}{T_{i0} \omega_0^2} \right)}$$

which agrees with the previous slide

# Line-to-output transfer function

---

Solution of complete block diagram leads to

$$\hat{v}(s) = \hat{i}_c(s) Z_o(s) \frac{T_i(s)}{1 + T_i(s)} + \hat{v}_g(s) \frac{G_{g0}(s)}{1 + T_i(s)}$$

with

$$G_{g0}(s) = Z_o(s) \frac{D}{Z_i(s)} \frac{\left(1 - \frac{V}{D^2} F_m F_g\right)}{\left(1 + \frac{V}{D^2} F_m F_v Z_o(s) \frac{D}{Z_i(s)}\right)}$$

# Line-to-output transfer function

---

$$G_{vg}(s) = \left. \frac{\hat{v}(s)}{\hat{v}_g(s)} \right|_{\hat{i}_c(s)=0} = \frac{G_{g0}(s)}{1 + T_i(s)}$$

$$G_{vg}(s) = \frac{\left( \frac{1}{1 + T_{i0}} \right) \frac{(1 - \alpha)}{(1 + \alpha)} 2D^2 \left( \frac{M_a}{M_2} - \frac{1}{2} \right)}{1 + s \left( \frac{T_{i0}}{1 + T_{i0}} \frac{1}{\omega_z} + \frac{1}{(1 + T_{i0}) Q \omega_0} \right) + \frac{1}{1 + T_{i0}} \left( \frac{s}{\omega_0} \right)^2}$$

Poles are identical to control-to-output transfer function, and can be factored the same way:

$$G_{vg}(s) \approx \frac{G_{vg}(0)}{\left( 1 + \frac{s}{\omega_z} \right) \left( 1 + \frac{s}{\omega_c} \right)}$$



## Line-to-output transfer function: dc gain

---

$$G_{vg}(0) \approx \frac{2D^2}{K} \left( \frac{M_a}{M_2} - \frac{1}{2} \right) \quad \text{for large } T_{i0}$$

For any  $T_{i0}$ , the dc gain goes to zero when  $M_a/M_2 = 0.5$



Effective feedforward of input voltage variations in CPM controller then effectively cancels out the  $v_g$  variations in the direct forward path of the converter.

## 11.4 Discontinuous conduction mode

---

- Again, use averaged switch modeling approach
- Result: simply replace
  - Transistor by power sink
  - Diode by power source
- Inductor dynamics appear at high frequency, near to or greater than the switching frequency
- Small-signal transfer functions contain a single low frequency pole
- DCM CPM boost and buck-boost are stable without artificial ramp
- DCM CPM buck without artificial ramp is stable for  $D < 2/3$ . A small artificial ramp  $m_a \geq 0.086m_2$  leads to stability for all  $D$ .

# DCM CPM buck-boost example

  


# Analysis

$$i_{pk} = m_1 d_1 T_s$$

$$m_1 = \frac{\langle v_1(t) \rangle_{T_s}}{L}$$

$$\begin{aligned} i_c &= i_{pk} + m_a d_1 T_s \\ &= (m_1 + m_a) d_1 T_s \end{aligned}$$
 
$$d_1(t) = \frac{i_c(t)}{(m_1 + m_a) T_s}$$



# Averaged switch input port equation


$$\langle i_1(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} i_1(\tau) d\tau = \frac{q_1}{T_s}$$

$$\langle i_1(t) \rangle_{T_s} = \frac{1}{2} i_{pk}(t) d_1(t)$$

$$\langle i_1(t) \rangle_{T_s} = \frac{1}{2} m_1 d_1^2(t) T_s$$

$$\langle i_1(t) \rangle_{T_s} = \frac{\frac{1}{2} L i_c^2 f_s}{\langle v_1(t) \rangle_{T_s} \left( 1 + \frac{m_a}{m_1} \right)^2}$$
 
$$\langle i_1(t) \rangle_{T_s} \langle v_1(t) \rangle_{T_s} = \frac{\frac{1}{2} L i_c^2 f_s}{\left( 1 + \frac{m_a}{m_1} \right)^2} = \langle p(t) \rangle_{T_s}$$



## Discussion: switch network input port

---

- Averaged transistor waveforms obey a power sink characteristic
- During first subinterval, energy is transferred from input voltage source, through transistor, to inductor, equal to

$$W = \frac{1}{2} L i_{pk}^2$$

This energy transfer process accounts for power flow equal to

$$\langle p(t) \rangle_{T_s} = W f_s = \frac{1}{2} L i_{pk}^2 f_s$$

which is equal to the power sink expression of the previous slide.

# Averaged switch output port equation


$$\langle i_2(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} i_2(\tau) d\tau = \frac{q_2}{T_s}$$

$$q_2 = \frac{1}{2} i_{pk} d_2 T_s$$

$$d_2(t) = d_1(t) \frac{\langle v_1(t) \rangle_{T_s}}{\langle v_2(t) \rangle_{T_s}}$$

$$\langle i_2(t) \rangle_{T_s} = \frac{\langle p(t) \rangle_{T_s}}{\langle v_2(t) \rangle_{T_s}}$$
 
$$\langle i_2(t) \rangle_{T_s} \langle v_2(t) \rangle_{T_s} = \frac{\frac{1}{2} L i_c^2(t) f_s}{\left(1 + \frac{m_a}{m_1}\right)^2} = \langle p(t) \rangle_{T_s}$$




## Discussion: switch network output port

---


- Averaged diode waveforms obey a power sink characteristic
- During second subinterval, all stored energy in inductor is transferred, through diode, to load
- Hence, in averaged model, diode becomes a power source, having value equal to the power consumed by the transistor power sink element



# Averaged equivalent circuit

 

# Steady state model: DCM CPM buck-boost

 

*Solution*

$$\frac{V^2}{R} = P$$


$$P = \frac{\frac{1}{2} L I_c^2(t) f_s}{\left(1 + \frac{M_a}{M_1}\right)^2}$$

$$V = \sqrt{PR} = I_c \sqrt{\frac{RLf_s}{2 \left(1 + \frac{M_a}{M_1}\right)^2}}$$


for a resistive load

# Models of buck and boost

*Buck*

 

*Boost*

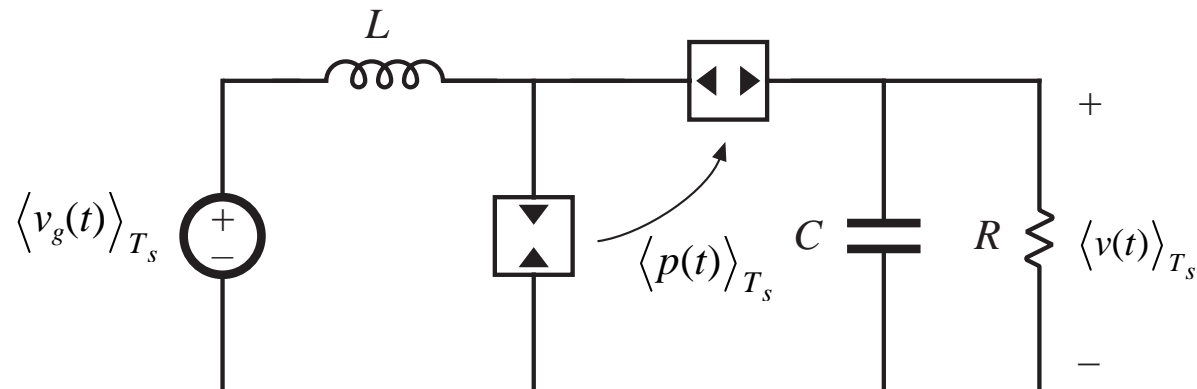

# Summary of steady-state DCM CPM characteristics


Table 11.3. Steady-state DCM CPM characteristics of basic converters

Converter	$M$	$I_{crit}$	Stability range when $m_a = 0$
Buck	$\frac{P_{load} - P}{P_{load}}$	$\frac{1}{2} \left( I_c - M m_a T_s \right)$	$0 \leq M < \frac{2}{3}$
Boost	$\frac{P_{load}}{P_{load} - P}$	$\frac{\left( I_c - \frac{M-1}{M} m_a T_s \right)}{2 M}$	$0 \leq D \leq 1$
Buck-boost	Depends on load characteristic: $P_{load} = P$	$\frac{\left( I_c - \frac{M}{M-1} m_a T_s \right)}{2 (M-1)}$	$0 \leq D \leq 1$

$$\begin{aligned} |I| &> |I_{crit}| && \text{for CCM} \\ |I| &< |I_{crit}| && \text{for DCM} \end{aligned}$$

 
## Buck converter: output characteristic with $m_a = 0$

$$I = \frac{P}{V_g - V} + \frac{P}{V} = \frac{P}{V \left( 1 - \frac{V_g}{V} \right)}$$




- with a resistive load, there can be two operating points
- the operating point having  $V > 0.67 V_g$  can be shown to be unstable


# Linearized small-signal models: Buck

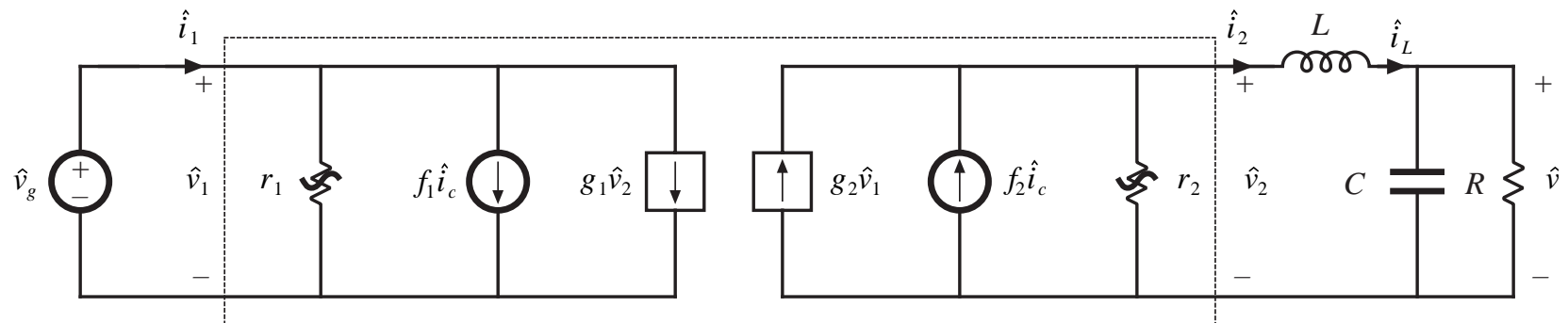

# Linearized small-signal models: Boost

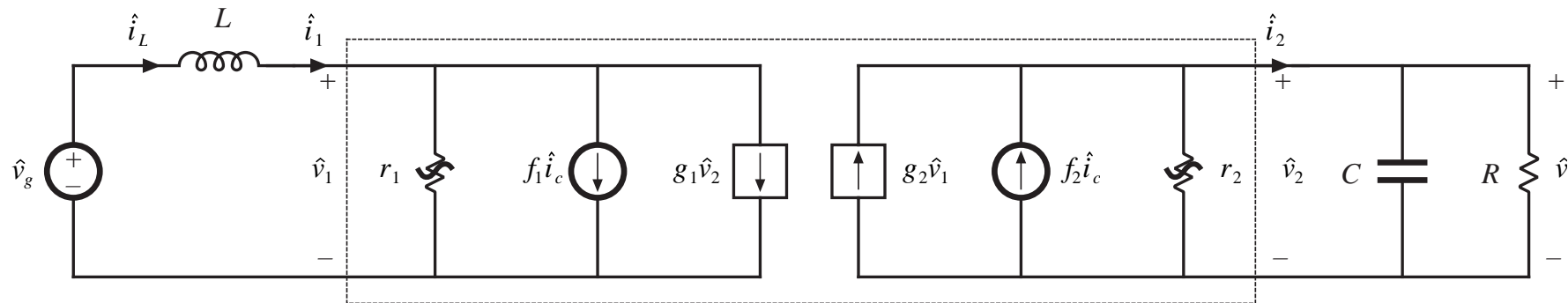
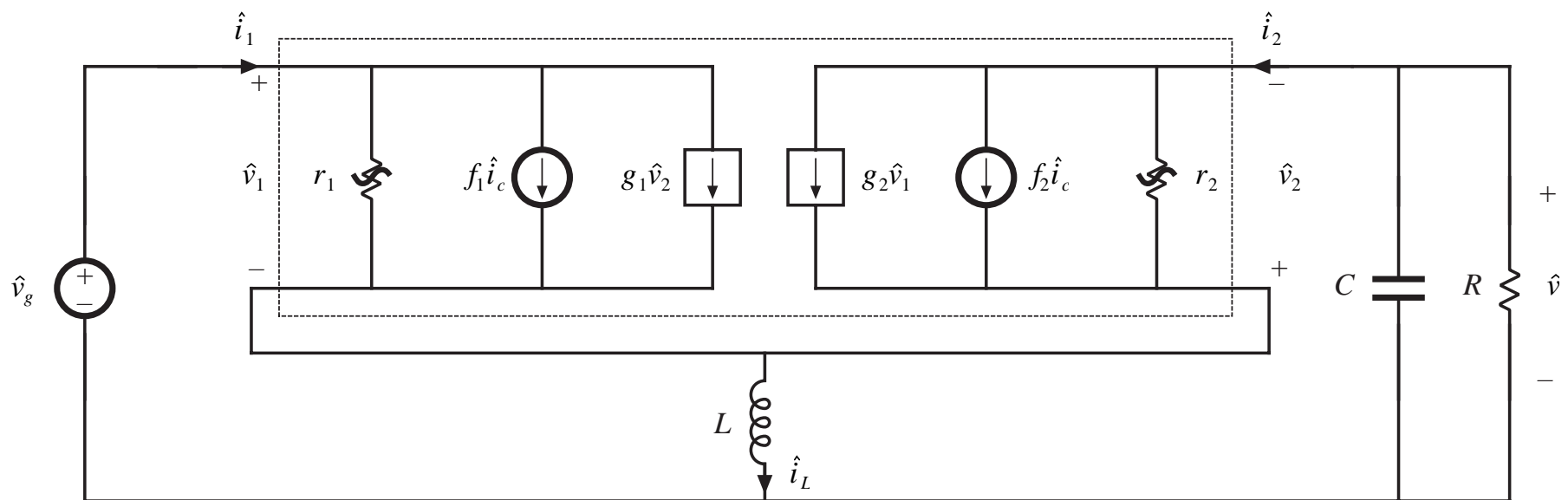
# Linearized small-signal models: Buck-boost





# DCM CPM small-signal parameters: input port

Table 11.4. Current programmed DCM small-signal equivalent circuit parameters: input port

Converter	$g_1$	$f_1$	$r_1$
Buck	$\frac{1}{R} \left( \frac{M^2}{1-M} \right) \frac{\left( 1 - \frac{m_a}{m_1} \right)}{\left( 1 + \frac{m_a}{m_1} \right)}$	$2 \frac{I_1}{I_c}$	$-R \left( \frac{1-M}{M^2} \right) \frac{\left( 1 + \frac{m_a}{m_1} \right)}{\left( 1 - \frac{m_a}{m_1} \right)}$
Boost	$-\frac{1}{R} \left( \frac{M}{M-1} \right)$	$2 \frac{I}{I_c}$	$\frac{R}{M^2 \left( \frac{2-M}{M-1} + \frac{2 \frac{m_a}{m_1}}{1 + \frac{m_a}{m_1}} \right)}$
Buck-boost	0	$2 \frac{I_1}{I_c}$	$\frac{-R}{M^2} \frac{\left( 1 + \frac{m_a}{m_1} \right)}{\left( 1 - \frac{m_a}{m_1} \right)}$


# DCM CPM small-signal parameters: output port

Table 11.5. Current programmed DCM small-signal equivalent circuit parameters: output port

Converter	$g_2$	$f_2$	$r_2$
Buck	$\frac{1}{R} \left( \frac{M}{1-M} \right) \frac{\left( \frac{m_a}{m_1} (2-M) - M \right)}{\left( 1 + \frac{m_a}{m_1} \right)}$	$2 \frac{I}{I_c}$	$R \frac{(1-M) \left( 1 + \frac{m_a}{m_1} \right)}{\left( 1 - 2M + \frac{m_a}{m_1} \right)}$
Boost	$\frac{1}{R} \left( \frac{M}{M-1} \right)$	$2 \frac{I_2}{I_c}$	$R \left( \frac{M-1}{M} \right)$
Buck-boost	$\frac{2M}{R} \frac{\left( \frac{m_a}{m_1} \right)}{\left( 1 + \frac{m_a}{m_1} \right)}$	$2 \frac{I_2}{I_c}$	$R$

# Simplified DCM CPM model, with $L = 0$

*Buck, boost, buck-boost all become*

 

$$G_{vc}(s) = \left. \frac{\hat{v}}{\hat{i}_c} \right|_{\hat{v}_g=0} = \frac{G_{c0}}{1 + \frac{s}{\omega_p}}$$

$$G_{c0} = f_2 (R \parallel r_2)$$

$$\omega_p = \frac{1}{(R \parallel r_2) C}$$

$$G_{vg}(s) = \left. \frac{\hat{v}}{\hat{v}_g} \right|_{\hat{i}_c=0} = \frac{G_{g0}}{1 + \frac{s}{\omega_p}}$$

$$G_{g0} = g_2 (R \parallel r_2)$$

## Buck $\omega_p$

---

Plug in parameters:

$$\omega_p = \frac{1}{RC} \frac{(2 - 3M)(1 - M) + \frac{m_a}{m_2} M(2 - M)}{(1 - M)\left(1 - M + M \frac{m_a}{m_2}\right)}$$

- For  $m_a = 0$ , numerator is negative when  $M > 2/3$ .
- $\omega_p$  then constitutes a RHP pole. Converter is unstable.
- Addition of small artificial ramp stabilizes system.
- $m_a > 0.086$  leads to stability for all  $M \leq 1$ .
- Output voltage feedback can also stabilize system, without an artificial ramp

## 11.5 Summary of key points

---

1. In current-programmed control, the peak switch current  $i_s(t)$  follows the control input  $i_c(t)$ . This widely used control scheme has the advantage of a simpler control-to-output transfer function. The line-to-output transfer functions of current-programmed buck converters are also reduced.
2. The basic current-programmed controller is unstable when  $D > 0.5$ , regardless of the converter topology. The controller can be stabilized by addition of an artificial ramp having slope  $m_a$ . When  $m_a \geq 0.5 m_2$ , then the controller is stable for all duty cycle.
3. The behavior of current-programmed converters can be modeled in a simple and intuitive manner by the first-order approximation  $\langle i_L(t) \rangle_{T_s} \approx i_c(t)$ . The averaged terminal waveforms of the switch network can then be modeled simply by a current source of value  $i_c$ , in conjunction with a power sink or power source element. Perturbation and linearization of these elements leads to the small-signal model. Alternatively, the small-signal converter equations derived in Chapter 7 can be adapted to cover the current programmed mode, using the simple approximation  $i_L(t) \approx i_c(t)$ .

## Summary of key points

---

4. The simple model predicts that one pole is eliminated from the converter line-to-output and control-to-output transfer functions. Current programming does not alter the transfer function zeroes. The dc gains become load-dependent.
5. The more accurate model of Section 11.3 correctly accounts for the difference between the average inductor current  $\langle i_L(t) \rangle_{T_s}$  and the control input  $i_c(t)$ . This model predicts the nonzero line-to-output transfer function  $G_{vg}(s)$  of the buck converter. The current-programmed controller behavior is modeled by a block diagram, which is appended to the small-signal converter models derived in Chapter 7. Analysis of the resulting multiloop feedback system then leads to the relevant transfer functions.
6. The more accurate model predicts that the inductor pole occurs at the crossover frequency  $f_c$  of the effective current feedback loop gain  $T_i(s)$ . The frequency  $f_c$  typically occurs in the vicinity of the converter switching frequency  $f_s$ . The more accurate model also predicts that the line-to-output transfer function  $G_{vg}(s)$  of the buck converter is nulled when  $m_a = 0.5 m_2$ .

## Summary of key points

---

7. Current programmed converters operating in the discontinuous conduction mode are modeled in Section 11.4. The averaged transistor waveforms can be modeled by a power sink, while the averaged diode waveforms are modeled by a power source. The power is controlled by  $i_c(t)$ . Perturbation and linearization of these averaged models, as usual, leads to small-signal equivalent circuits.

---

## Part III. Magnetics

- 12. Basic Magnetics Theory
- 13. Filter Inductor Design
- 14. Transformer Design



# Chapter 12. Basic Magnetism Theory

---

## 12.1. Review of basic magnetism

12.1.1. Basic relations

12.1.2. Magnetic circuits

## 12.2. Transformer modeling

12.2.1. The ideal transformer

12.2.3. Leakage inductances

12.2.2. The magnetizing inductance

## 12.3. Loss mechanisms in magnetic devices

12.3.1. Core loss

12.3.2. Low-frequency copper loss

## 12.4. Eddy currents in winding conductors

12.4.1. The skin effect

12.4.4. Power loss in a layer

12.4.2. The proximity effect

12.4.5. Example: power loss in a transformer winding


12.4.3. MMF diagrams

12.4.6. PWM waveform harmonics

## 12.1. Review of basic magnetics



### 12.1.1. Basic relations

---


 


# Basic quantities

## *Magnetic quantities*

  

## *Electrical quantities*

  


# Magnetic field $\mathbf{H}$ and magnetomotive force $\mathcal{F}$


Magnetomotive force (MMF)  $\mathcal{F}$  between points  $x_1$  and  $x_2$  is related to the magnetic field  $\mathbf{H}$  according to

$$\mathcal{F} = \int_{x_1}^{x_2} \mathbf{H} \cdot d\mathbf{l}$$

 *Example: uniform magnetic field of magnitude  $H$*



 *Analogous to electric field of strength  $E$ , which induces voltage (EMF)  $V$ :*




# Flux density $\mathbf{B}$ and total flux $\Phi$

The total magnetic flux  $\Phi$  passing through a surface of area  $A_c$  is related to the flux density  $\mathbf{B}$  according to


$$\Phi = \int_{\text{surface } S} \mathbf{B} \cdot d\mathbf{A}$$

*Example: uniform flux density of magnitude  $B$*

$$\Phi = B A_c$$

 

 *Analogous to electrical conductor current density of magnitude  $J$ , which leads to total conductor current  $I$ :*




# Faraday's law

Voltage  $v(t)$  is induced in a loop of wire by change in the total flux  $\Phi(t)$  passing through the interior of the loop, according to

$$v(t) = \frac{d\Phi(t)}{dt}$$

For uniform flux distribution,  $\Phi(t) = B(t)A_c$  and hence

$$v(t) = A_c \frac{dB(t)}{dt}$$

 


# Lenz's law

The voltage  $v(t)$  induced by the changing flux  $\Phi(t)$  is of the polarity that tends to drive a current through the loop to counteract the flux change.

 *Example: a shorted loop of wire*

- Changing flux  $\Phi(t)$  induces a voltage  $v(t)$  around the loop
- This voltage, divided by the impedance of the loop conductor, leads to current  $i(t)$
- This current induces a flux  $\Phi'(t)$ , which tends to oppose changes in  $\Phi(t)$



# Ampere's law


The net MMF around a closed path is equal to the total current passing through the interior of the path:

$$\oint_{\text{closed path}} \mathbf{H} \cdot d\mathbf{l} = \text{total current passing through interior of path}$$

*Example: magnetic core. Wire carrying current  $i(t)$  passes through core window.*

- Illustrated path follows magnetic flux lines around interior of core
- For uniform magnetic field strength  $H(t)$ , the integral (MMF) is  $H(t)l_m$ . So

$$F(t) = H(t) l_m = i(t)$$

 




# Ampere's law: discussion

---

- Relates magnetic field strength  $H(t)$  to winding current  $i(t)$
- We can view winding currents as sources of MMF
- Previous example: total MMF around core,  $\oint H(t)dl_m$ , is equal to the winding current MMF  $i(t)$
- The total MMF around a closed loop, accounting for winding current MMF's, is zero


# Core material characteristics: the relation between $B$ and $H$

*Free space*

 

$\mu_0$  = permeability of free space  
 $= 4\pi \cdot 10^{-7}$  Henries per meter


*A magnetic core material*

 

Highly nonlinear, with hysteresis  
and saturation


# Piecewise-linear modeling of core material characteristics

*No hysteresis or saturation*

 

Typical  $\mu_r = 10^3 - 10^5$

*Saturation, no hysteresis*

 

Typical  $B_{sat} = 0.3-0.5\text{T}$ , ferrite  
0.5-1T, powdered iron  
1-2T, iron laminations

# Units

*Table 12.1. Units for magnetic quantities*

<i>quantity</i>	<i>MKS</i>	<i>unrationalized cgs</i>	<i>conversions</i>
core material equation	$B = \mu_0 \mu_r H$	$B = \mu_r H$	
$B$	Tesla	Gauss	$1\text{T} = 10^4\text{G}$
$H$	Ampere / meter	Oersted	$1\text{A/m} = 4\pi \cdot 10^{-3} \text{ Oe}$
$\Phi$	Weber	Maxwell	$1\text{Wb} = 10^8 \text{ Mx}$ $1\text{T} = 1\text{Wb} / \text{m}^2$

## Example: a simple inductor

*Faraday's law:*

For each turn of wire, we can write


$$v_{turn}(t) = \frac{d\Phi(t)}{dt}$$

Total winding voltage is

$$v(t) = n v_{turn}(t) = n \frac{d\Phi(t)}{dt}$$

Express in terms of the average flux density  $B(t) = \Phi(t)/A_c$

$$v(t) = n A_c \frac{dB(t)}{dt}$$

 

# Inductor example: Ampere's law


Choose a closed path which follows the average magnetic field line around the interior of the core. Length of this path is called the *mean magnetic path length*  $l_m$ .

For uniform field strength  $H(t)$ , the core MMF around the path is  $H l_m$ .

Winding contains  $n$  turns of wire, each carrying current  $i(t)$ . The net current passing through the path interior (i.e., through the core window) is  $ni(t)$ .

From Ampere's law, we have

$$H(t) l_m = n i(t)$$

 


# Inductor example: core material model

$$B = \begin{cases} B_{sat} & \text{for } H \geq B_{sat} / \mu \\ \mu H & \text{for } |H| < B_{sat} / \mu \\ -B_{sat} & \text{for } H \leq -B_{sat} / \mu \end{cases}$$

Find winding current at onset of saturation:  
substitute  $i = I_{sat}$  and  $H = B_{sat}/\mu$  into  
equation previously derived via Ampere's  
law. Result is

$$I_{sat} = \frac{B_{sat} l_m}{\mu n}$$

 

# Electrical terminal characteristics

We have:

$$v(t) = n A_c \frac{dB(t)}{dt} \quad H(t) l_m = n i(t) \quad B = \begin{cases} B_{sat} & \text{for } H \geq B_{sat} / \mu \\ \mu H & \text{for } |H| < B_{sat} / \mu \\ -B_{sat} & \text{for } H \leq -B_{sat} / \mu \end{cases}$$

Eliminate  $B$  and  $H$ , and solve for relation between  $v$  and  $i$ . For  $|i| < I_{sat}$ ,

$$v(t) = \mu n A_c \frac{dH(t)}{dt} \quad \longrightarrow \quad v(t) = \frac{\mu n^2 A_c}{l_m} \frac{di(t)}{dt}$$

which is of the form

$$v(t) = L \frac{di(t)}{dt} \quad \text{with} \quad L = \frac{\mu n^2 A_c}{l_m}$$

—an inductor

For  $|i| > I_{sat}$  the flux density is constant and equal to  $B_{sat}$ . Faraday's law then predicts

$$v(t) = n A_c \frac{dB_{sat}}{dt} = 0 \quad \text{—saturation leads to short circuit}$$



## 12.1.2. Magnetic circuits

Uniform flux and magnetic field inside a rectangular element:


MMF between ends of element is

$$F = H l$$

Since  $H = B / \mu$  and  $B = \Phi / A_c$ , we can express  $F$  as

$$F = \frac{l}{\mu A_c} \Phi \quad \text{with} \quad R = \frac{l}{\mu A_c}$$

A corresponding model:

 

$$R = \frac{l}{\mu A_c}$$

$R$  = reluctance of element

# Magnetic circuits: magnetic structures composed of multiple windings and heterogeneous elements

---



- Represent each element with reluctance
- Windings are sources of MMF
- MMF  $\rightarrow$  voltage, flux  $\rightarrow$  current
- Solve magnetic circuit using Kirchoff's laws, etc.

# Magnetic analog of Kirchhoff's current law

Divergence of  $\mathbf{B} = 0$

Flux lines are continuous and cannot end

Total flux entering a node must be zero

  

# Magnetic analog of Kirchoff's voltage law

---

Follows from Ampere's law:


$$\oint_{\text{closed path}} \mathbf{H} \cdot d\mathbf{l} = \text{total current passing through interior of path}$$

Left-hand side: sum of MMF's across the reluctances around the closed path

Right-hand side: currents in windings are sources of MMF's. An  $n$ -turn winding carrying current  $i(t)$  is modeled as an MMF (voltage) source, of value  $ni(t)$ .

Total MMF's around the closed path add up to zero.



## Example: inductor with air gap

 

Ampere's law:

$$F_c + F_g = n i$$

# Magnetic circuit model

  


$$F_c + F_g = n i$$

$$n i = \Phi (R_c + R_g)$$

$$R_c = \frac{l_c}{\mu A_c}$$

$$R_g = \frac{l_g}{\mu_0 A_c}$$

# Solution of model

 


Faraday's law:  $v(t) = n \frac{d\Phi(t)}{dt}$

Substitute for  $\Phi$ :  $v(t) = \frac{n^2}{R_c + R_g} \frac{di(t)}{dt}$

Hence inductance is

$$L = \frac{n^2}{R_c + R_g}$$

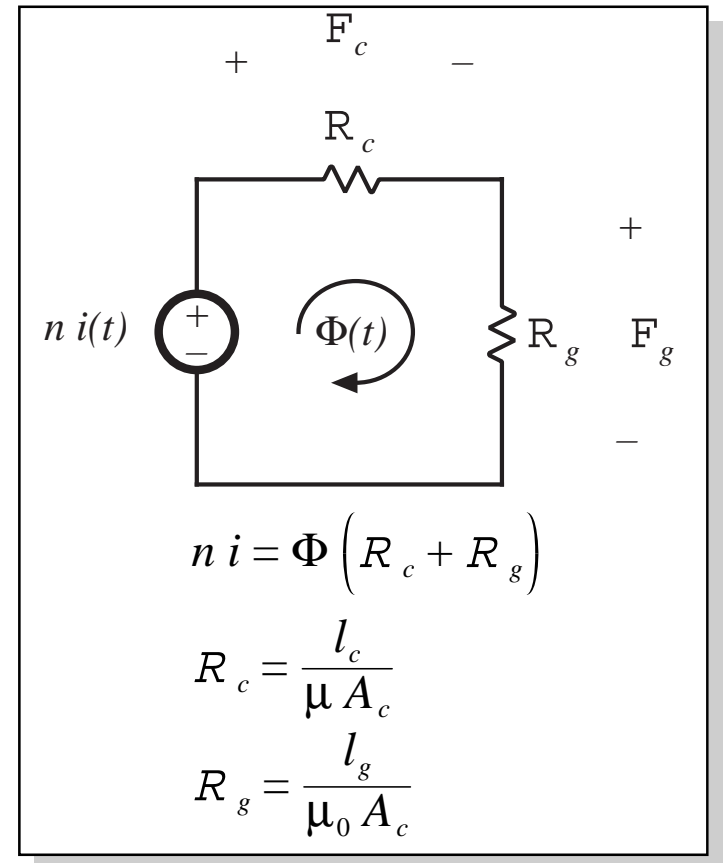

# Effect of air gap

$$n i = \Phi (R_c + R_g)$$


$$L = \frac{n^2}{R_c + R_g}$$

$$\Phi_{sat} = B_{sat} A_c$$

$$I_{sat} = \frac{B_{sat} A_c}{n} (R_c + R_g)$$

Effect of air gap:

 - decrease inductance
- increase saturation current
- inductance is less dependent on core permeability






## 12.2. Transformer modeling

Two windings, no air gap:


$$R = \frac{l_m}{\mu A_c}$$

$$F_c = n_1 i_1 + n_2 i_2$$

$$\Phi R = n_1 i_1 + n_2 i_2$$

 

Magnetic circuit model:

 

## 12.2.1. The ideal transformer

In the ideal transformer, the core reluctance  $R$  approaches zero.

MMF  $F_c = \Phi R$  also approaches zero. We then obtain

$$0 = n_1 i_1 + n_2 i_2$$

Also, by Faraday's law,

$$v_1 = n_1 \frac{d\Phi}{dt}$$



$$v_2 = n_2 \frac{d\Phi}{dt}$$

Eliminate  $\Phi$  :

$$\frac{d\Phi}{dt} = \frac{v_1}{n_1} = \frac{v_2}{n_2}$$

Ideal transformer equations:
  
$$\frac{v_1}{n_1} = \frac{v_2}{n_2} \quad \text{and} \quad n_1 i_1 + n_2 i_2 = 0$$



## 12.2.2. The magnetizing inductance

For nonzero core reluctance, we obtain

$$\Phi R = n_1 i_1 + n_2 i_2 \quad \text{with} \quad v_1 = n_1 \frac{d\Phi}{dt}$$

Eliminate  $\Phi$ :

$$v_1 = \frac{n_1^2}{R} \frac{d}{dt} \left[ i_1 + \frac{n_2}{n_1} i_2 \right]$$



This equation is of the form

$$v_1 = L_{mp} \frac{d i_{mp}}{dt}$$

with

$$L_{mp} = \frac{n_1^2}{R}$$

$$i_{mp} = i_1 + \frac{n_2}{n_1} i_2$$

  

# Magnetizing inductance: discussion

---

- Models magnetization of core material
- A real, physical inductor, that exhibits saturation and hysteresis
- If the secondary winding is disconnected:
  - we are left with the primary winding on the core
  - primary winding then behaves as an inductor
  - the resulting inductor is the magnetizing inductance, referred to the primary winding
- Magnetizing current causes the ratio of winding currents to differ from the turns ratio

# Transformer saturation

---

- Saturation occurs when core flux density  $B(t)$  exceeds saturation flux density  $B_{sat}$ .
- When core saturates, the magnetizing current becomes large, the impedance of the magnetizing inductance becomes small, and the windings are effectively shorted out.
- Large winding currents  $i_1(t)$  and  $i_2(t)$  **do not** necessarily lead to saturation. If

$$0 = n_1 i_1 + n_2 i_2$$

then the magnetizing current is zero, and there is no net magnetization of the core.

- Saturation is caused by excessive applied volt-seconds


# Saturation vs. applied volt-seconds

Magnetizing current depends on the integral of the applied winding voltage:

$$i_{mp}(t) = \frac{1}{L_{mp}} \int v_1(t) dt$$

Flux density is proportional:
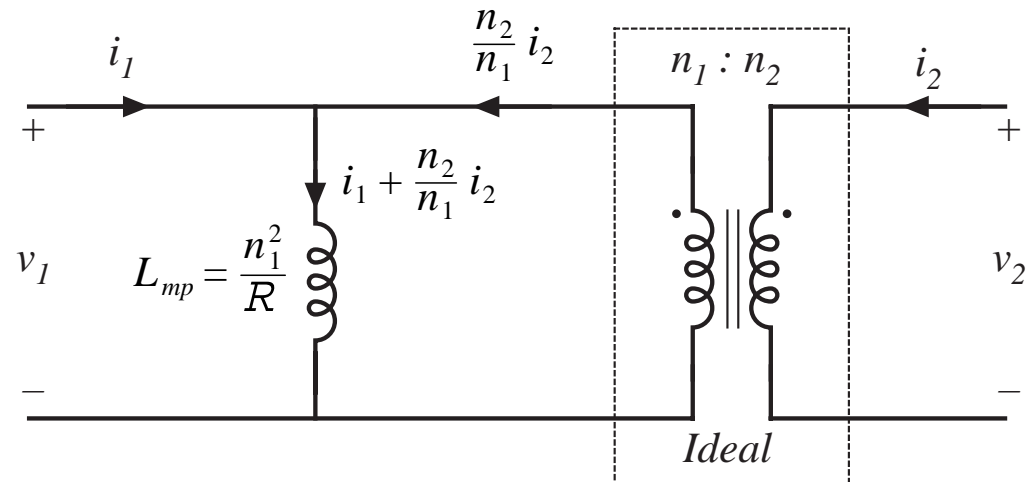
$$B(t) = \frac{1}{n_1 A_c} \int v_1(t) dt$$




Flux density becomes large, and core saturates, when the applied volt-seconds  $\lambda_1$  are too large, where

$$\lambda_1 = \int_{t_1}^{t_2} v_1(t) dt$$

limits of integration chosen to coincide with positive portion of applied voltage waveform

### 12.2.3. Leakage inductances

 

# Transformer model, including leakage inductance

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \begin{bmatrix} L_{11} & L_{12} \\ L_{12} & L_{22} \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$


mutual inductance

$$L_{12} = \frac{n_1 n_2}{R} = \frac{n_2}{n_1} L_{mp}$$

primary and secondary  
self-inductances

$$L_{11} = L_{l1} + \frac{n_1}{n_2} L_{12}$$
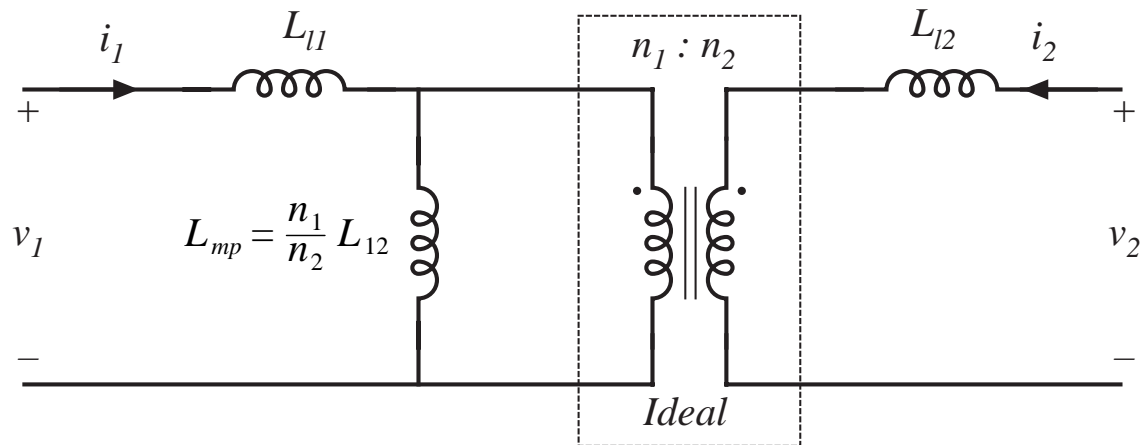
$$L_{22} = L_{l2} + \frac{n_2}{n_1} L_{12}$$



effective turns ratio

$$n_e = \sqrt{\frac{L_{22}}{L_{11}}}$$

coupling coefficient

$$k = \frac{L_{12}}{\sqrt{L_{11} L_{22}}}$$



## 12.3. Loss mechanisms in magnetic devices

---

Low-frequency losses:

- Dc copper loss

- Core loss: hysteresis loss

High-frequency losses: the skin effect

- Core loss: classical eddy current losses

- Eddy current losses in ferrite cores

High frequency copper loss: the proximity effect

- Proximity effect: high frequency limit

- MMF diagrams, losses in a layer, and losses in basic multilayer windings

- Effect of PWM waveform harmonics

## 12.3.1. Core loss

Energy per cycle  $W$  flowing into  $n$ -turn winding of an inductor, excited by periodic waveforms of frequency  $f$ :

$$W = \int_{\text{one cycle}} v(t)i(t)dt$$


Relate winding voltage and current to core  $B$  and  $H$  via Faraday's law and Ampere's law:

$$v(t) = n A_c \frac{dB(t)}{dt}$$

$$H(t) l_m = n i(t)$$

Substitute into integral:

 
$$\begin{aligned} W &= \int_{\text{one cycle}} \left( n A_c \frac{dB(t)}{dt} \right) \left( \frac{H(t) l_m}{n} \right) dt \\ &= (A_c l_m) \int_{\text{one cycle}} H dB \end{aligned}$$


 
# Core loss: Hysteresis loss

$$W = (A_c l_m) \int_{\text{one cycle}} H dB$$

The term  $A_c l_m$  is the volume of the core, while the integral is the area of the  $B$ - $H$  loop.



(energy lost per cycle) = (core volume) (area of  $B$ - $H$  loop)

$$P_H = (f)(A_c l_m) \int_{\text{one cycle}} H dB$$

Hysteresis loss is directly proportional to applied frequency

# Modeling hysteresis loss

---

- Hysteresis loss varies directly with applied frequency
- Dependence on maximum flux density: how does area of  $B$ - $H$  loop depend on maximum flux density (and on applied waveforms)?  
Emperical equation (Steinmetz equation):

$$P_H = K_H f B_{\max}^{\alpha} (\text{core volume})$$


The parameters  $K_H$  and  $\alpha$  are determined experimentally.

Dependence of  $P_H$  on  $B_{\max}$  is predicted by the theory of magnetic domains.
 
# Core loss: eddy current loss

---

Magnetic core materials are reasonably good conductors of electric current. Hence, according to Lenz's law, magnetic fields within the core induce currents ("eddy currents") to flow within the core. The eddy currents flow such that they tend to generate a flux which opposes changes in the core flux  $\Phi(t)$ . The eddy currents tend to prevent flux from penetrating the core.




# Modeling eddy current loss

---

- Ac flux  $\Phi(t)$  induces voltage  $v(t)$  in core, according to Faraday's law. Induced voltage is proportional to derivative of  $\Phi(t)$ . In consequence, magnitude of induced voltage is directly proportional to excitation frequency  $f$ .
- If core material impedance  $Z$  is purely resistive and independent of frequency,  $Z = R$ , then eddy current magnitude is proportional to voltage:  $i(t) = v(t)/R$ . Hence magnitude of  $i(t)$  is directly proportional to excitation frequency  $f$ .
- Eddy current power loss  $i^2(t)R$  then varies with square of excitation frequency  $f$ .
- Classical Steinmetz equation for eddy current loss:
$$P_E = K_E f^2 B_{\max}^2 (\text{core volume})$$
- Ferrite core material impedance is capacitive. This causes eddy current power loss to increase as  $f^4$ .

# Total core loss: manufacturer's data

Ferrite core material

 

Empirical equation, at a fixed frequency:

$$P_{fe} = K_{fe} B_{max}^b A_c l_m$$

# Core materials

---

Core type	$B_{sat}$	Relative core loss	Applications
Laminations iron, silicon steel	1.5 - 2.0 T	high	50-60 Hz transformers, inductors
Powdered cores powdered iron, molypermalloy	0.6 - 0.8 T	medium	1 kHz transformers, 100 kHz filter inductors
Ferrite Manganese-zinc, Nickel-zinc	0.25 - 0.5 T	low	20 kHz - 1 MHz transformers, ac inductors



## 12.3.2. Low-frequency copper loss

---


DC resistance of wire

$$R = \rho \frac{l_b}{A_w}$$

where  $A_w$  is the wire bare cross-sectional area, and  $l_b$  is the length of the wire. The resistivity  $\rho$  is equal to  $1.724 \cdot 10^{-6} \Omega \text{ cm}$  for soft-annealed copper at room temperature. This resistivity increases to  $2.3 \cdot 10^{-6} \Omega \text{ cm}$  at  $100^\circ\text{C}$ .


The wire resistance leads to a power loss of

$$P_{cu} = I_{rms}^2 R$$

 

## 12.4. Eddy currents in winding conductors

### 12.4.1. The skin effect

 


# Penetration depth $\delta$

For sinusoidal currents: current density is an exponentially decaying function of distance into the conductor, with characteristic length  $\delta$  known as the *penetration depth* or *skin depth*.

$$\delta = \sqrt{\frac{\rho}{\pi \mu f}}$$

For copper at room temperature:

 
$$\delta = \frac{7.5}{\sqrt{f}} \text{ cm}$$


 
## 12.4.2. The proximity effect

Ac current in a conductor induces eddy currents in adjacent conductors by a process called the *proximity effect*. This causes significant power loss in the windings of high-frequency transformers and ac inductors.

A multi-layer foil winding, with  $d \gg \delta$ . Each layer carries net current  $i(t)$ .



# Estimating proximity loss: high-frequency limit

Let  $P_1$  be power loss in layer 1:

$$P_1 = I_{rms}^2 \left( R_{dc} \frac{d}{\delta} \right)$$

Power loss  $P_2$  in layer 2 is:


$$\begin{aligned} P_2 &= I_{rms}^2 \left( R_{dc} \frac{d}{\delta} \right) + (2I_{rms})^2 \left( R_{dc} \frac{d}{\delta} \right) \\ &= 5P_1 \end{aligned}$$

Power loss  $P_3$  in layer 3 is:

$$\begin{aligned} P_3 &= (2I_{rms})^2 \left( R_{dc} \frac{d}{\delta} \right) + (3I_{rms})^2 \left( R_{dc} \frac{d}{\delta} \right) \\ &= 13P_1 \end{aligned}$$

Power loss  $P_m$  in layer m is:

$$P_m = ((m-1)^2 + m^2) P_1$$

 

# Total loss in $M$ -layer winding: high-frequency limit

---

Add up losses in each layer:

$$P_w \big|_{d \gg \delta} = \sum_{j=1}^M P_j = \frac{M}{3} (2M^2 + 1) P_1$$

## ***Compare with dc copper loss:***

If foil thickness were  $d = \delta$ , then at dc each layer would produce copper loss  $P_1$ . The copper loss of the  $M$ -layer winding would be

$$P_{w,dc} \big|_{d=\delta} = M P_1$$


For foil thicknesses other than  $d = \delta$ , the dc resistance and power loss are changed by a factor of  $d/\delta$ . The total winding dc copper loss is

$$P_{w,dc} = M P_1 \frac{\delta}{d}$$

So the proximity effect increases the copper loss by a factor of

$$F_R \big|_{d \gg \delta} = \frac{P_w \big|_{d \gg \delta}}{P_{w,dc}} = \frac{1}{3} \frac{d}{\delta} (2M^2 + 1)$$
 
# Approximating a layer of round conductors as an effective foil conductor



Conductor spacing factor:


$$\eta = \sqrt{\frac{\pi}{4}} d \frac{n_l}{l_w}$$

Effective ratio of conductor thickness to skin depth:

$$\phi = \sqrt{\eta} \frac{d}{\delta}$$

### 12.4.3. Magnetic fields in the vicinity of winding conductors: MMF diagrams

*Two-winding transformer example*

 





# Transformer example: magnetic field lines

$$(m_p - m_s) i = F(x)$$

$$H(x) = \frac{F(x)}{l_w}$$

 


# Ampere's law and MMF diagram

 


$$(m_p - m_s) i = F(x)$$

$$H(x) = \frac{F(x)}{l_w}$$


# MMF diagram for $d \gg \delta$

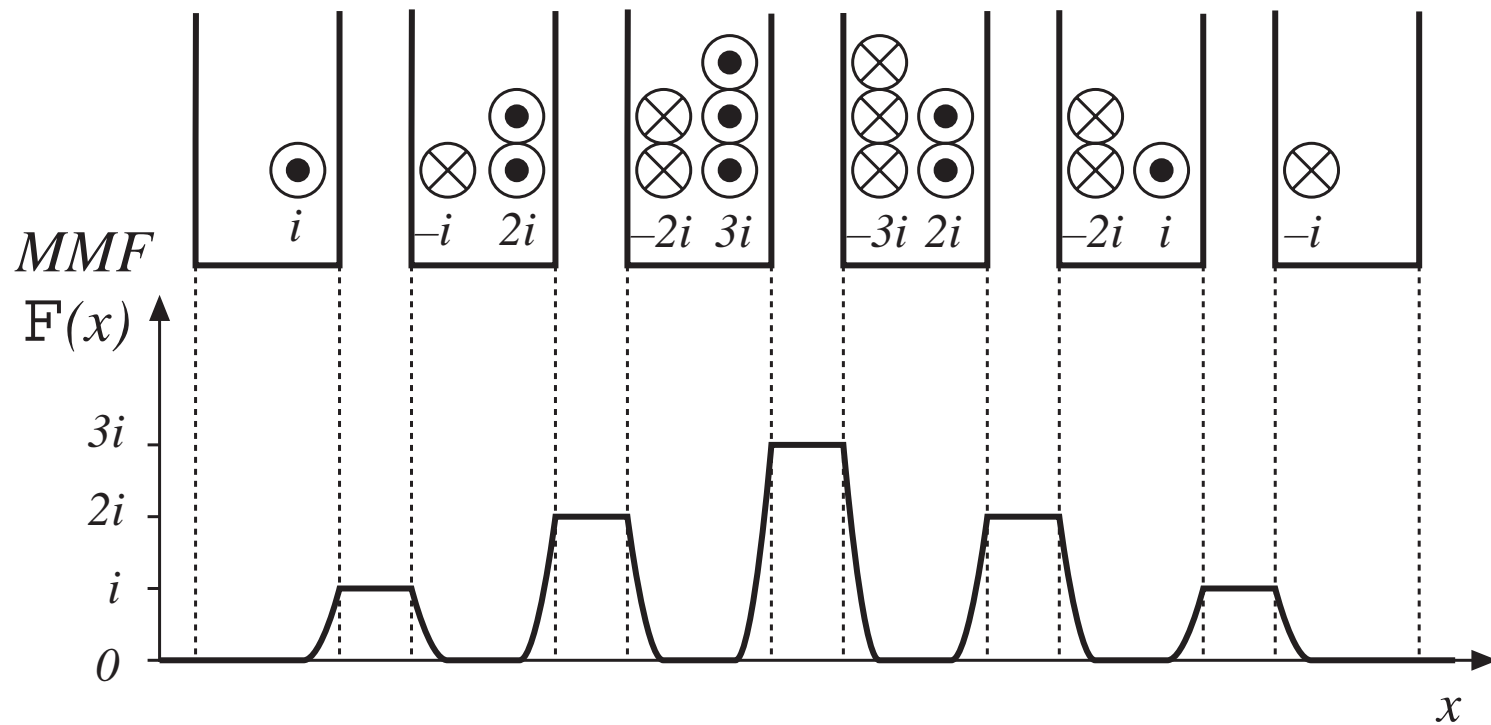

# Interleaved windings

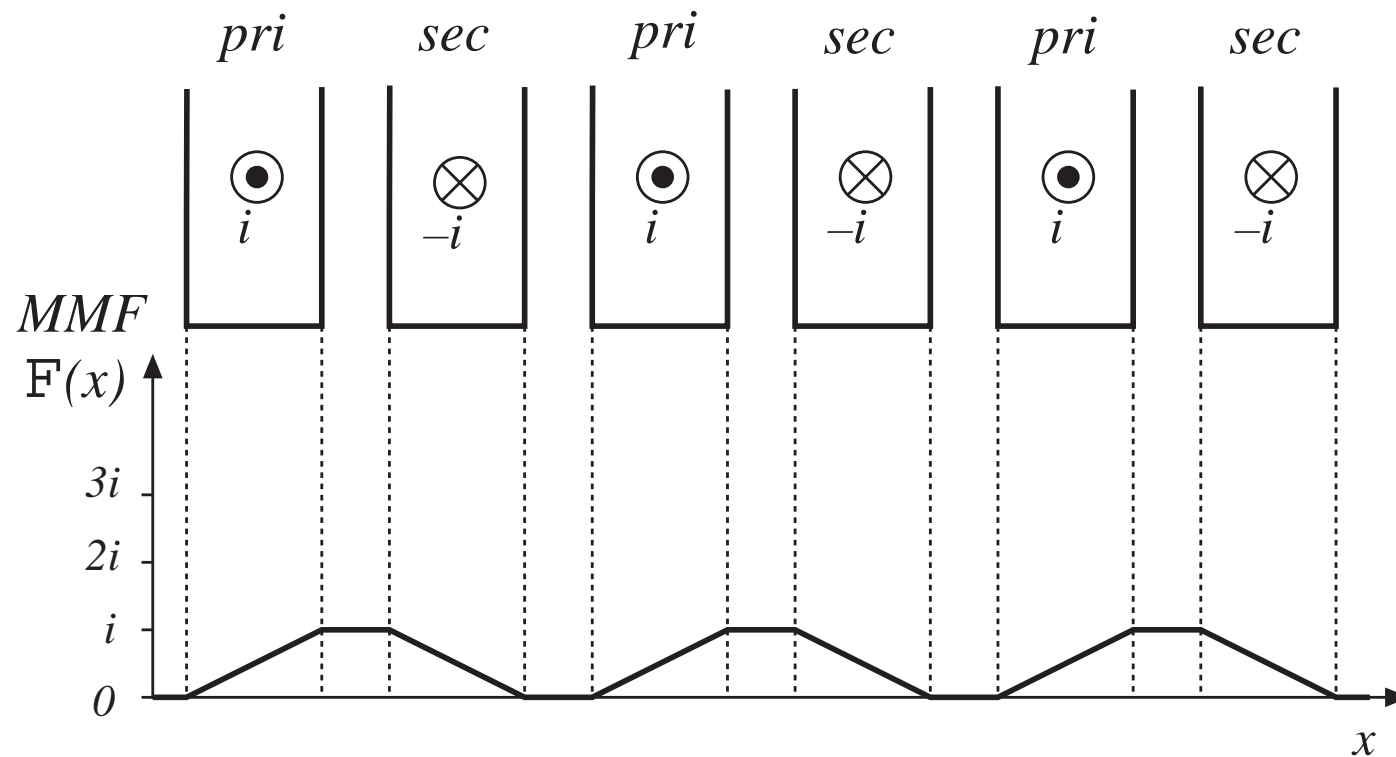
 
# Partially-interleaved windings: fractional layers




## 12.4.4. Power loss in a layer

Approximate computation of copper loss in one layer

Assume uniform magnetic fields at surfaces of layer, of strengths  $H(0)$  and  $H(d)$ . Assume that these fields are parallel to layer surface (i.e., neglect fringing and assume field normal component is zero).

 The magnetic fields  $H(0)$  and  $H(d)$  are driven by the MMFs  $F(0)$  and  $F(d)$ . Sinusoidal waveforms are assumed, and rms values are used. It is assumed that  $H(0)$  and  $H(d)$  are in phase.



## Solution for layer copper loss $P$

Solve Maxwell's equations to find current density distribution within layer. Then integrate to find total copper loss  $P$  in layer. Result is

$$P = R_{dc} \frac{\Phi}{n_l^2} \left[ \left( F^2(d) + F^2(0) \right) G_1(\varphi) - 4 F(d)F(0) G_2(\varphi) \right]$$

where

$$R_{dc} = \rho \frac{(MLT) n_l^2}{l_w \eta d}$$

$$G_1(\varphi) = \frac{\sinh(2\varphi) + \sin(2\varphi)}{\cosh(2\varphi) - \cos(2\varphi)}$$

$$G_2(\varphi) = \frac{\sinh(\varphi) \cos(\varphi) + \cosh(\varphi) \sin(\varphi)}{\cosh(2\varphi) - \cos(2\varphi)}$$

$$\varphi = \sqrt{\eta} \frac{d}{\delta} \quad \eta = \sqrt{\frac{\pi}{4}} d \frac{n_l}{l_w}$$

$n_l$  = number of turns in layer,  
 $R_{dc}$  = dc resistance of layer,

$(MLT)$  = mean-length-per-turn,  
 or circumference, of layer.

# Winding carrying current $I$ , with $n_l$ turns per layer

If winding carries current of rms magnitude  $I$ , then

$$F(d) - F(0) = n_l I$$

Express  $F(d)$  in terms of the winding current  $I$ , as

$$F(d) = m n_l I$$


The quantity  $m$  is the ratio of the MMF  $F(d)$  to the layer ampere-turns  $n_l I$ . Then,

$$\frac{F(0)}{F(d)} = \frac{m-1}{m}$$

Power dissipated in the layer can now be written

$$P = I^2 R_{dc} \varphi Q'(\varphi, m)$$
 
$$Q'(\varphi, m) = (2m^2 - 2m + 1) G_1(\varphi) - 4m(m-1) G_2(\varphi)$$






# Increased copper loss in layer

$$\frac{P}{I^2 R_{dc}} = \phi Q'(\phi, m)$$

$$\frac{P}{I^2 R_{dc}}$$

 


# Layer copper loss vs. layer thickness

$$\frac{P}{P_{dc}|_{d=\delta}} = Q'(\phi, m)$$

$$\frac{P}{P_{dc}|_{\phi=1}}$$

 Relative to copper  
loss when  $d = \delta$



## 12.4.5. Example: Power loss in a transformer winding

Two winding transformer


Each winding consists of  $M$  layers

Proximity effect increases copper loss in layer  $m$  by the factor

$$\frac{P}{I^2 R_{dc}} = \varphi Q'(\varphi, m)$$

Sum losses over all primary layers:

 
$$F_R = \frac{P_{pri}}{P_{pri,dc}} = \frac{1}{M} \sum_{m=1}^M \varphi Q'(\varphi, m)$$



 
# Increased total winding loss

Express summation in closed form:

$$F_R = \varphi \left[ G_1(\varphi) + \frac{2}{3} (M^2 - 1) (G_1(\varphi) - 2G_2(\varphi)) \right]$$



# Total winding loss

 

## 12.4.6. PWM waveform harmonics

*Fourier series:*

$$i(t) = I_0 + \sum_{j=1}^{\infty} \sqrt{2} I_j \cos(j\omega t)$$

with

$$I_j = \frac{\sqrt{2} I_{pk}}{j \pi} \sin(j\pi D) \quad I_0 = DI_{pk}$$


*Copper loss:*

Dc  $P_{dc} = I_0^2 R_{dc}$

Ac 
$$P_j = I_j^2 R_{dc} \sqrt{j} \varphi_1 \left[ G_1(\sqrt{j} \varphi_1) + \frac{2}{3} (M^2 - 1) \left( G_1(\sqrt{j} \varphi_1) - 2G_2(\sqrt{j} \varphi_1) \right) \right]$$

Total, relative to value predicted by low-frequency analysis:
 
$$\frac{P_{cu}}{D I_{pk}^2 R_{dc}} = D + \frac{2\varphi_1}{D\pi^2} \sum_{j=1}^{\infty} \frac{\sin^2(j\pi D)}{j \sqrt{j}} \left[ G_1(\sqrt{j} \varphi_1) + \frac{2}{3} (M^2 - 1) \left( G_1(\sqrt{j} \varphi_1) - 2G_2(\sqrt{j} \varphi_1) \right) \right]$$



# Harmonic loss factor $F_H$

---


Effect of harmonics:  $F_H$  = ratio of total ac copper loss to fundamental copper loss

$$F_H = \frac{\sum_{j=1}^{\infty} P_j}{P_1}$$

The total winding copper loss can then be written


$$P_{cu} = I_0^2 R_{dc} + F_H F_R I_1^2 R_{dc}$$
 
# Increased proximity losses induced by PWM waveform harmonics: $D = 0.5$





 
# Increased proximity losses induced by PWM waveform harmonics: $D = 0.3$


 
# Increased proximity losses induced by PWM waveform harmonics: $D = 0.1$



# Summary of Key Points

---

1. Magnetic devices can be modeled using lumped-element magnetic circuits, in a manner similar to that commonly used to model electrical circuits. The magnetic analogs of electrical voltage  $V$ , current  $I$ , and resistance  $R$ , are magnetomotive force (MMF)  $\mathcal{F}$ , flux  $\Phi$ , and reluctance  $\mathcal{R}$  respectively.
2. Faraday's law relates the voltage induced in a loop of wire to the derivative of flux passing through the interior of the loop.
3. Ampere's law relates the total MMF around a loop to the total current passing through the center of the loop. Ampere's law implies that winding currents are sources of MMF, and that when these sources are included, then the net MMF around a closed path is equal to zero.
4. Magnetic core materials exhibit hysteresis and saturation. A core material saturates when the flux density  $B$  reaches the saturation flux density  $B_{sat}$ .

## Summary of key points

---

5. Air gaps are employed in inductors to prevent saturation when a given maximum current flows in the winding, and to stabilize the value of inductance. The inductor with air gap can be analyzed using a simple magnetic equivalent circuit, containing core and air gap reluctances and a source representing the winding MMF.
6. Conventional transformers can be modeled using sources representing the MMFs of each winding, and the core MMF. The core reluctance approaches zero in an ideal transformer. Nonzero core reluctance leads to an electrical transformer model containing a magnetizing inductance, effectively in parallel with the ideal transformer. Flux that does not link both windings, or “leakage flux,” can be modeled using series inductors.
7. The conventional transformer saturates when the applied winding volt-seconds are too large. Addition of an air gap has no effect on saturation. Saturation can be prevented by increasing the core cross-sectional area, or by increasing the number of primary turns.

## Summary of key points

---

8. Magnetic materials exhibit core loss, due to hysteresis of the  $B$ - $H$  loop and to induced eddy currents flowing in the core material. In available core materials, there is a tradeoff between high saturation flux density  $B_{sat}$  and high core loss  $P_{fe}$ . Laminated iron alloy cores exhibit the highest  $B_{sat}$  but also the highest  $P_{fe}$ , while ferrite cores exhibit the lowest  $P_{fe}$  but also the lowest  $B_{sat}$ . Between these two extremes are powdered iron alloy and amorphous alloy materials.
9. The skin and proximity effects lead to eddy currents in winding conductors, which increase the copper loss  $P_{cu}$  in high-current high-frequency magnetic devices. When a conductor has thickness approaching or larger than the penetration depth  $\delta$ , magnetic fields in the vicinity of the conductor induce eddy currents in the conductor. According to Lenz's law, these eddy currents flow in paths that tend to oppose the applied magnetic fields.

## Summary of key points

---

10. The magnetic field strengths in the vicinity of the winding conductors can be determined by use of MMF diagrams. These diagrams are constructed by application of Ampere's law, following the closed paths of the magnetic field lines which pass near the winding conductors. Multiple-layer noninterleaved windings can exhibit high maximum MMFs, with resulting high eddy currents and high copper loss.
11. An expression for the copper loss in a layer, as a function of the magnetic field strengths or MMFs surrounding the layer, is given in Section 12.4.4. This expression can be used in conjunction with the MMF diagram, to compute the copper loss in each layer of a winding. The results can then be summed, yielding the total winding copper loss. When the effective layer thickness is near to or greater than one skin depth, the copper losses of multiple-layer noninterleaved windings are greatly increased.

## Summary of key points

---

12. Pulse-width-modulated winding currents of contain significant total harmonic distortion, which can lead to a further increase of copper loss. The increase in proximity loss caused by current harmonics is most pronounced in multiple-layer non-interleaved windings, with an effective layer thickness near one skin depth.

# Chapter 13. Filter Inductor Design

---

- 13.1. Several types of magnetic devices, their  $B$ - $H$  loops, and core vs. copper loss
- 13.2. Filter inductor design constraints
- 13.3. The core geometrical constant  $K_g$
- 13.4. A step-by-step design procedure
- 13.5. Summary of key points



## 13.1. Several types of magnetic devices, their $B$ - $H$ loops, and core vs. copper loss

---

A key design decision: the choice of maximum operating flux density  $B_{max}$

- Choose  $B_{max}$  to avoid saturation of core, or
- Further reduce  $B_{max}$ , to reduce core losses

Different design procedures are employed in the two cases.

Types of magnetic devices:

Filter inductor

Ac inductor

Conventional transformer

Coupled inductor

Flyback transformer




SEPIC transformer

Magnetic amplifier

Saturable reactor


# Filter inductor

*CCM buck example*

  
 

 
## Filter inductor, cont.

- Negligible core loss, negligible proximity loss
- Loss dominated by dc copper loss
- Flux density chosen simply to avoid saturation
- Air gap is employed
- Could use core materials having high saturation flux density (and relatively high core loss), even though converter switching frequency is high



# Ac inductor

 
 


## Ac inductor, cont.

---

- Core loss, copper loss, proximity loss are all significant
- An air gap is employed
- Flux density is chosen to reduce core loss
- A high-frequency material (ferrite) must be employed

# Conventional transformer

  

$$H(t) = \frac{n i_{mp}(t)}{l_m}$$




## Conventional transformer, cont.

---

- Core loss, copper loss, and proximity loss are usually significant
- No air gap is employed
- Flux density is chosen to reduce core loss
- A high frequency material (ferrite) must be employed
   
# Coupled inductor

*Two-output  
forward converter  
example*








## Coupled inductor, cont.

---

- A filter inductor having multiple windings
- Air gap is employed
- Core loss and proximity loss usually not significant
- Flux density chosen to avoid saturation
- Low-frequency core material can be employed

# DCM Flyback transformer

   


## DCM flyback transformer, cont.

---

- Core loss, copper loss, proximity loss are significant
- Flux density is chosen to reduce core loss
- Air gap is employed
- A high-frequency core material (ferrite) must be used

## 13.2. Filter inductor design constraints

---


 


Objective:

Design inductor having a given inductance  $L$ ,  
which carries worst-case current  $I_{max}$  without saturating,  
and which has a given winding resistance  $R$ , or,  
equivalently, exhibits a worst-case copper loss of

$$P_{cu} = I_{rms}^2 R$$

# Assumed filter inductor geometry

  

$$R_c = \frac{l_c}{\mu_c A_c}$$

$$R_g = \frac{l_g}{\mu_0 A_c}$$

Solve magnetic circuit:

$$ni = \Phi (R_c + R_g)$$

For  $R_c \gg R_g$ :  $ni \approx \Phi R_g$

## 13.2.1. Constraint: maximum flux density

---

Given a peak winding current  $I_{max}$ , it is desired to operate the core flux density at a peak value  $B_{max}$ . The value of  $B_{max}$  is chosen to be less than the worst-case saturation flux density of the core material.

From solution of magnetic circuit:

$$ni = BA_c R_g$$

Let  $I = I_{max}$  and  $B = B_{max}$  :

$$nI_{max} = B_{max}A_c R_g = B_{max} \frac{l_g}{\mu_0}$$

This is constraint #1. The turns ratio  $n$  and air gap length  $l_g$  are unknown.

## 13.3.2. Constraint: Inductance

---

Must obtain specified inductance  $L$ . We know that the inductance is

$$L = \frac{n^2}{R_g} = \frac{\mu_0 A_c n^2}{l_g}$$

This is constraint #2. The turns ratio  $n$ , core area  $A_c$ , and air gap length  $l_g$  are unknown.

### 13.3.3. Constraint: Winding area

---

Wire must fit through core window (i.e., hole in center of core)

Total area of copper in window:


$$nA_W$$

Area available for winding conductors:

$$K_u W_A$$

Third design constraint:

$$K_u W_A \geq nA_W$$

 



# The window utilization factor $K_u$ also called the “fill factor”

---

$K_u$  is the fraction of the core window area that is filled by copper

Mechanisms that cause  $K_u$  to be less than 1:

- Round wire does not pack perfectly, which reduces  $K_u$  by a factor of 0.7 to 0.55 depending on winding technique
- Insulation reduces  $K_u$  by a factor of 0.95 to 0.65, depending on wire size and type of insulation
- Bobbin uses some window area
- Additional insulation may be required between windings

Typical values of  $K_u$ :

0.5 for simple low-voltage inductor

0.25 to 0.3 for off-line transformer

0.05 to 0.2 for high-voltage transformer (multiple kV)

0.65 for low-voltage foil-winding inductor

## 13.2.4 Winding resistance

---

The resistance of the winding is

$$R = \rho \frac{l_b}{A_w}$$

where  $\rho$  is the resistivity of the conductor material,  $l_b$  is the length of the wire, and  $A_w$  is the wire bare area. The resistivity of copper at room temperature is  $1.724 \cdot 10^{-6} \Omega\text{-cm}$ . The length of the wire comprising an  $n$ -turn winding can be expressed as

$$l_b = n (MLT)$$

where  $(MLT)$  is the mean-length-per-turn of the winding. The mean-length-per-turn is a function of the core geometry. The above equations can be combined to obtain the fourth constraint:

$$R = \rho \frac{n (MLT)}{A_w}$$

## 13.3 The core geometrical constant $K_g$

---

The four constraints:

$$nI_{max} = B_{max} \frac{l_g}{\mu_0}$$

$$K_u W_A \geq nA_w$$

$$L = \frac{\mu_0 A_c n^2}{l_g}$$

$$R = \rho \frac{n (MLT)}{A_w}$$

These equations involve the quantities

$A_c$ ,  $W_A$ , and  $MLT$ , which are functions of the core geometry,

$I_{max}$ ,  $B_{max}$ ,  $\mu_0$ ,  $L$ ,  $K_u$ ,  $R$ , and  $\rho$ , which are given specifications or other known quantities, and

$n$ ,  $l_g$ , and  $A_w$ , which are unknowns.

Eliminate the three unknowns, leading to a single equation involving the remaining quantities.

# Core geometrical constant $K_g$

---

Elimination of  $n$ ,  $l_g$ , and  $A_w$  leads to

$$\frac{A_c^2 W_A}{(MLT)} \geq \frac{\rho L^2 I_{max}^2}{B_{max}^2 R K_u}$$

- Right-hand side: specifications or other known quantities
- Left-hand side: function of only core geometry

So we must choose a core whose geometry satisfies the above equation.

The core geometrical constant  $K_g$  is defined as

$$K_g = \frac{A_c^2 W_A}{(MLT)}$$

# Discussion

---

$$K_g = \frac{A_c^2 W_A}{(MLT)} \geq \frac{\rho L^2 I_{max}^2}{B_{max}^2 R K_u}$$

$K_g$  is a figure-of-merit that describes the effective electrical size of magnetic cores, in applications where the following quantities are specified:

- Copper loss
- Maximum flux density

How specifications affect the core size:

A smaller core can be used by increasing

$B_{max} \Rightarrow$  use core material having higher  $B_{sat}$

$R \Rightarrow$  allow more copper loss

How the core geometry affects electrical capabilities:

A larger  $K_g$  can be obtained by increase of

$A_c \Rightarrow$  more iron core material, or

$W_A \Rightarrow$  larger window and more copper

## 13.4 A step-by-step procedure

---

The following quantities are specified, using the units noted:

Wire resistivity	$\rho$	( $\Omega$ -cm)
Peak winding current	$I_{max}$	(A)
Inductance	$L$	(H)
Winding resistance	$R$	( $\Omega$ )
Winding fill factor	$K_u$	
Core maximum flux density	$B_{max}$	(T)

The core dimensions are expressed in cm:

Core cross-sectional area	$A_c$	(cm <sup>2</sup> )
Core window area	$W_A$	(cm <sup>2</sup> )
Mean length per turn	$MLT$	(cm)

The use of centimeters rather than meters requires that appropriate factors be added to the design equations.

# Determine core size

---

$$K_g \geq \frac{\rho L^2 I_{max}^2}{B_{max}^2 R K_u} 10^8 \quad (\text{cm}^5)$$

Choose a core which is large enough to satisfy this inequality  
(see *Appendix 2 for magnetics design tables*).

Note the values of  $A_c$ ,  $W_A$ , and  $MLT$  for this core.

## Determine air gap length

---

$$l_g = \frac{\mu_0 L I_{max}^2}{B_{max}^2 A_c} 10^4 \quad (\text{m})$$

with  $A_c$  expressed in  $\text{cm}^2$ .  $\mu_0 = 4\pi 10^{-7} \text{ H/m}$ .

The air gap length is given in meters.

The value expressed above is approximate, and neglects fringing flux and other nonidealities.



$$A_L$$

Core manufacturers sell gapped cores. Rather than specifying the air gap length, the equivalent quantity  $A_L$  is used.

$A_L$  is equal to the inductance, in mH, obtained with a winding of 1000 turns.

When  $A_L$  is specified, it is the core manufacturer's responsibility to obtain the correct gap length.

The required  $A_L$  is given by:

$$A_L = \frac{10B_{max}^2 A_c^2}{LI_{max}^2} \quad (\text{mH/1000 turns})$$

*Units:*

$A_c$	cm <sup>2</sup> ,
$L$	Henries,
$B_{max}$	Tesla.

$$L = A_L n^2 10^{-9} \quad (\text{Henries})$$

# Determine number of turns $n$

---

$$n = \frac{LI_{max}}{B_{max}A_c} 10^4$$

## Evaluate wire size

---

$$A_w \leq \frac{K_u W_A}{n} \quad (\text{cm}^2)$$

Select wire with bare copper area  $A_w$  less than or equal to this value.  
An American Wire Gauge table is included in Appendix 2.

As a check, the winding resistance can be computed:

$$R = \frac{\rho n (MLT)}{A_w} \quad (\Omega)$$

## 13.5 Summary of key points


---

1. A variety of magnetic devices are commonly used in switching converters. These devices differ in their core flux density variations, as well as in the magnitudes of the ac winding currents. When the flux density variations are small, core loss can be neglected. Alternatively, a low-frequency material can be used, having higher saturation flux density.
2. The core geometrical constant  $K_g$  is a measure of the magnetic size of a core, for applications in which copper loss is dominant. In the  $K_g$  design method, flux density and total copper loss are specified.
 
# Chapter 14. Transformer Design

Some more advanced design issues, not considered in previous chapter:

- Inclusion of core loss
- Selection of operating flux density to optimize total loss
- Multiple winding design: how to allocate the available window area among several windings
- A transformer design procedure
- How switching frequency affects transformer size



# Chapter 14. Transformer Design



---

- 14.1. Winding area optimization
- 14.2. Transformer design: Basic constraints
- 14.3. A step-by-step transformer design procedure
- 14.4. Examples
- 14.5. Ac inductor design
- 14.6. Summary
  
## 14.1. Winding area optimization

**Given:** application with  $k$  windings having known rms currents and desired turns ratios


$$\frac{v_1(t)}{n_1} = \frac{v_2(t)}{n_2} = \dots = \frac{v_k(t)}{n_k}$$



**Q:** how should the window area  $W_A$  be allocated among the windings?

# Allocation of winding area

---

 

$$0 < \alpha_j < 1$$

$$\alpha_1 + \alpha_2 + \dots + \alpha_k = 1$$



# Copper loss in winding $j$

---

Copper loss (not accounting for proximity loss) is

$$P_{cu,j} = I_j^2 R_j$$

Resistance of winding  $j$  is

$$R_j = \rho \frac{l_j}{A_{w,j}}$$

with

$$l_j = n_j (MLT)$$

length of wire, winding  $j$

$$A_{w,j} = \frac{W_A K_u \alpha_j}{n_j}$$

wire area, winding  $j$

Hence

$$P_{cu,j} = \frac{n_j^2 i_j^2 \rho (MLT)}{W_A K_u \alpha_j}$$

# Total copper loss of transformer


---

Sum previous expression over all windings:

$$P_{cu,tot} = P_{cu,1} + P_{cu,2} + \dots + P_{cu,k} = \frac{\rho (MLT)}{W_A K_u} \sum_{j=1}^k \left( \frac{n_j^2 I_j^2}{\alpha_j} \right)$$

Need to select values for  $\alpha_1, \alpha_2, \dots, \alpha_k$  such that the total copper loss is minimized
 
# Variation of copper losses with $\alpha_1$



**For  $\alpha_1 = 0$ :** wire of winding 1 has zero area.  $P_{cu,1}$  tends to infinity

**For  $\alpha_1 = 1$ :** wires of remaining windings have zero area. Their copper losses tend to infinity

There is a choice of  $\alpha_1$  that minimizes the total copper loss

# Method of Lagrange multipliers to minimize total copper loss

---

Minimize the function

$$P_{cu,tot} = P_{cu,1} + P_{cu,2} + \dots + P_{cu,k} = \frac{\rho (MLT)}{W_A K_u} \sum_{j=1}^k \left( \frac{n_j^2 I_j^2}{\alpha_j} \right)$$

subject to the constraint

$$\alpha_1 + \alpha_2 + \dots + \alpha_k = 1$$

Define the function

$$f(\alpha_1, \alpha_2, \dots, \alpha_k, \xi) = P_{cu,tot}(\alpha_1, \alpha_2, \dots, \alpha_k) + \xi g(\alpha_1, \alpha_2, \dots, \alpha_k)$$

where

$$g(\alpha_1, \alpha_2, \dots, \alpha_k) = 1 - \sum_{j=1}^k \alpha_j$$

is the constraint that must equal zero

and  $\xi$  is the Lagrange multiplier

# Lagrange multipliers

## continued

---

Optimum point is solution of the system of equations

$$\frac{\partial f(\alpha_1, \alpha_2, \dots, \alpha_k, \xi)}{\partial \alpha_1} = 0$$

$$\frac{\partial f(\alpha_1, \alpha_2, \dots, \alpha_k, \xi)}{\partial \alpha_2} = 0$$

$\vdots$

$$\frac{\partial f(\alpha_1, \alpha_2, \dots, \alpha_k, \xi)}{\partial \alpha_k} = 0$$

$$\frac{\partial f(\alpha_1, \alpha_2, \dots, \alpha_k, \xi)}{\partial \xi} = 0$$

Result:

$$\xi = \frac{\rho (MLT)}{W_A K_u} \left( \sum_{j=1}^k n_j I_j \right)^2 = P_{cu,tot}$$

$$\alpha_m = \frac{n_m I_m}{\sum_{n=1}^{\infty} n_j I_j}$$

An alternate form:

$$\alpha_m = \frac{V_m I_m}{\sum_{n=1}^{\infty} V_j I_j}$$

# Interpretation of result

---

$$\alpha_m = \frac{V_m I_m}{\sum_{n=1}^{\infty} V_n I_n}$$

Apparent power in winding  $j$  is

$$V_j I_j$$


where  $V_j$  is the rms or peak applied voltage

$I_j$  is the rms current

Window area should be allocated according to the apparent powers of the windings

# Example

## PWM full-bridge transformer

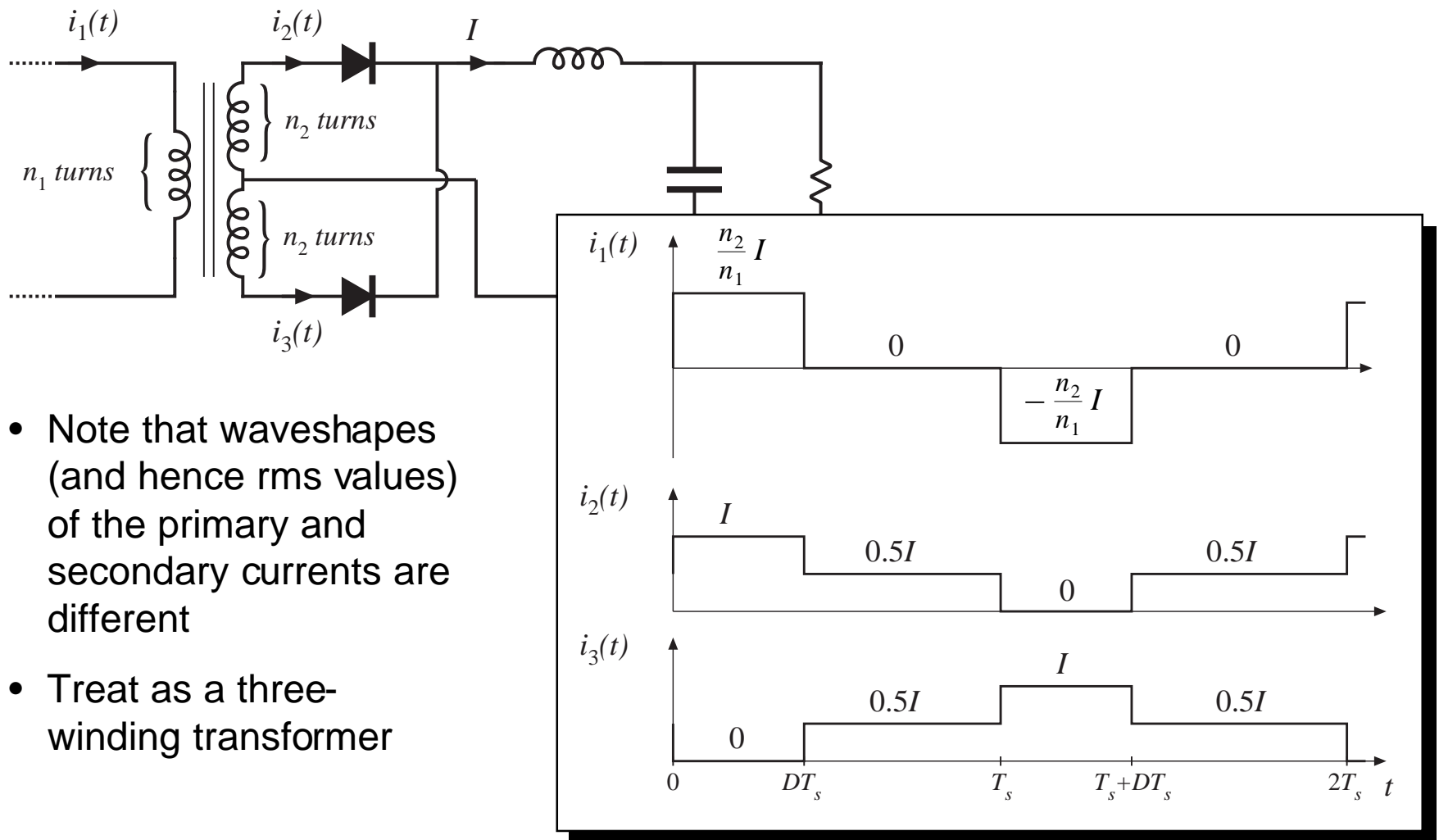


- Note that waveshapes (and hence rms values) of the primary and secondary currents are different
- Treat as a three-winding transformer

# Expressions for RMS winding currents

$$I_1 = \sqrt{\frac{1}{2T_s} \int_0^{2T_s} i_1^2(t) dt} = \frac{n_2}{n_1} I \sqrt{D}$$

$$I_2 = I_3 = \sqrt{\frac{1}{2T_s} \int_0^{2T_s} i_2^2(t) dt} = \frac{1}{2} I \sqrt{1 + D}$$

see Appendix 1

 



# Allocation of window area:

$$\alpha_m = \frac{V_m I_m}{\sum_{n=1}^{\infty} V_n I_n}$$


---

Plug in rms current expressions. Result:

$$\alpha_1 = \frac{1}{\left(1 + \sqrt{\frac{1+D}{D}}\right)}$$

Fraction of window area allocated to primary winding

$$\alpha_2 = \alpha_3 = \frac{1}{2} \frac{1}{\left(1 + \sqrt{\frac{D}{1+D}}\right)}$$

Fraction of window area allocated to each secondary winding

# Numerical example

---

Suppose that we decide to optimize the transformer design at the worst-case operating point  $D = 0.75$ . Then we obtain

$$\alpha_1 = 0.396$$

$$\alpha_2 = 0.302$$

$$\alpha_3 = 0.302$$

The total copper loss is then given by

$$\begin{aligned} P_{cu,tot} &= \frac{\rho(MLT)}{W_A K_u} \left( \sum_{j=1}^3 n_j I_j \right)^2 \\ &= \frac{\rho(MLT) n_2^2 I^2}{W_A K_u} \left( 1 + 2D + 2\sqrt{D(1+D)} \right) \end{aligned}$$

## 14.2 Transformer design:

### Basic constraints

---

*Core loss*

$$P_{fe} = K_{fe} B_{max}^{\beta} A_c l_m$$

Typical value of  $\beta$  for ferrite materials: 2.6 or 2.7

$B_{max}$  is the peak value of the ac component of  $B(t)$

So increasing  $B_{max}$  causes core loss to increase rapidly

This is the first constraint

# Flux density


## Constraint #2

Flux density  $B(t)$  is related to the applied winding voltage according to Faraday's Law. Denote the volt-seconds applied to the primary winding during the positive portion of  $v_1(t)$  as  $\lambda_1$ :

$$\lambda_1 = \int_{t_1}^{t_2} v_1(t) dt$$

This causes the flux to change from its negative peak to its positive peak. From Faraday's law, the peak value of the ac component of flux density is

$$B_{max} = \frac{\lambda_1}{2n_1A_c}$$

 

To attain a given flux density, the primary turns should be chosen according to

$$n_1 = \frac{\lambda_1}{2B_{max}A_c}$$

# Copper loss

## Constraint #3

---

- Allocate window area between windings in optimum manner, as described in previous section
- Total copper loss is then equal to

$$P_{cu} = \frac{\rho(MLT)n_1^2 I_{tot}^2}{W_A K_u}$$

with

$$I_{tot} = \sum_{j=1}^k \frac{n_j}{n_1} I_j$$

Eliminate  $n_1$ , using result of previous slide:

$$P_{cu} = \left( \frac{\rho \lambda_1^2 I_{tot}^2}{K_u} \right) \left( \frac{(MLT)}{W_A A_c^2} \right) \left( \frac{1}{B_{max}^2} \right)$$

Note that copper loss decreases rapidly as  $B_{max}$  is increased

# Total power loss


$$4. P_{tot} = P_{cu} + P_{fe}$$

There is a value of  $B_{max}$  that minimizes the total power loss

$$P_{tot} = P_{fe} + P_{cu}$$

$$P_{fe} = K_{fe} B_{max}^{\beta} A_c l_m$$
 
$$P_{cu} = \left( \frac{\rho \lambda_1^2 I_{tot}^2}{K_u} \right) \left( \frac{(MLT)}{W_A A_c^2} \right) \left( \frac{1}{B_{max}^2} \right)$$



## 5. Find optimum flux density $B_{max}$

---

Given that

$$P_{tot} = P_{fe} + P_{cu}$$

Then, at the  $B_{max}$  that minimizes  $P_{tot}$ , we can write

$$\frac{dP_{tot}}{dB_{max}} = \frac{dP_{fe}}{dB_{max}} + \frac{dP_{cu}}{dB_{max}} = 0$$

Note: optimum does not necessarily occur where  $P_{fe} = P_{cu}$ . Rather, it occurs where

$$\frac{dP_{fe}}{dB_{max}} = - \frac{dP_{cu}}{dB_{max}}$$

# Take derivatives of core and copper loss

---

$$P_{fe} = K_{fe} B_{max}^{\beta} A_c l_m$$

$$P_{cu} = \left( \frac{\rho \lambda_1^2 I_{tot}^2}{K_u} \right) \left( \frac{(MLT)}{W_A A_c^2} \right) \left( \frac{1}{B_{max}^2} \right)$$

$$\frac{dP_{fe}}{dB_{max}} = \beta K_{fe} B_{max}^{(\beta-1)} A_c l_m$$

$$\frac{dP_{cu}}{dB_{max}} = -2 \left( \frac{\rho \lambda_1^2 I_{tot}^2}{4K_u} \right) \left( \frac{(MLT)}{W_A A_c^2} \right) B_{max}^{-3}$$

Now, substitute into  $\frac{dP_{fe}}{dB_{max}} = -\frac{dP_{cu}}{dB_{max}}$  and solve for  $B_{max}$ :

$$B_{max} = \left[ \frac{\rho \lambda_1^2 I_{tot}^2}{2K_u} \frac{(MLT)}{W_A A_c^3 l_m} \frac{1}{\beta K_{fe}} \right]^{\left( \frac{1}{\beta+2} \right)}$$

Optimum  $B_{max}$  for a given core and application



# Total loss

Substitute optimum  $B_{max}$  into expressions for  $P_{cu}$  and  $P_{fe}$ . The total loss is:

$$P_{tot} = \left[ A_c l_m K_{fe} \right]^{\left( \frac{2}{\beta+2} \right)} \left[ \frac{\rho \lambda_1^2 I_{tot}^2}{4K_u} \frac{(MLT)}{W_A A_c^2} \right]^{\left( \frac{\beta}{\beta+2} \right)} \left[ \left( \frac{\beta}{2} \right)^{-\left( \frac{\beta}{\beta+2} \right)} + \left( \frac{\beta}{2} \right)^{\left( \frac{2}{\beta+2} \right)} \right]$$

Rearrange as follows:

$$\frac{W_A (A_c)^{(2(\beta-1)/\beta)}}{(MLT) l_m^{(2/\beta)}} \left[ \left( \frac{\beta}{2} \right)^{-\left( \frac{\beta}{\beta+2} \right)} + \left( \frac{\beta}{2} \right)^{\left( \frac{2}{\beta+2} \right)} \right]^{-\left( \frac{\beta+2}{\beta} \right)} = \frac{\rho \lambda_1^2 I_{tot}^2 K_{fe}^{(2/\beta)}}{4K_u (P_{tot})^{((\beta+2)/\beta)}}$$

Left side: terms depend on core geometry

Right side: terms depend on specifications of the application

# The core geometrical constant $K_{gfe}$

Define 
$$K_{gfe} = \frac{W_A (A_c)^{(2(\beta-1)/\beta)}}{(MLT) l_m^{(2/\beta)}} \left[ \left( \frac{\beta}{2} \right)^{-\left( \frac{\beta}{\beta+2} \right)} + \left( \frac{\beta}{2} \right)^{\left( \frac{2}{\beta+2} \right)} \right]^{-\left( \frac{\beta+2}{\beta} \right)}$$

Design procedure: select a core that satisfies

$$K_{gfe} \geq \frac{\rho \lambda_1^2 I_{tot}^2 K_{fe}^{(2/\beta)}}{4K_u (P_{tot})^{((\beta+2)/\beta)}}$$

Appendix 2 lists the values of  $K_{gfe}$  for common ferrite cores

$K_{gfe}$  is similar to the  $K_g$  geometrical constant used in Chapter 13:

- $K_g$  is used when  $B_{max}$  is specified
- $K_{gfe}$  is used when  $B_{max}$  is to be chosen to minimize total loss

## 14.3 Step-by-step transformer design procedure

---

The following quantities are specified, using the units noted:

Wire effective resistivity	$\rho$	( $\Omega$ -cm)
Total rms winding current, ref to pri	$I_{tot}$	(A)
Desired turns ratios	$n_2/n_1, n_3/n_1, \text{etc.}$	
Applied pri volt-sec	$\lambda_1$	(V-sec)
Allowed total power dissipation	$P_{tot}$	(W)
Winding fill factor	$K_u$	
Core loss exponent	$\beta$	
Core loss coefficient	$K_{fe}$	(W/cm <sup>3</sup> T <sup><math>\beta</math></sup> )

Other quantities and their dimensions:

Core cross-sectional area	$A_c$	(cm <sup>2</sup> )
Core window area	$W_A$	(cm <sup>2</sup> )
Mean length per turn	$MLT$	(cm)
Magnetic path length	$l_e$	(cm)
Wire areas	$A_{w1}, \dots$	(cm <sup>2</sup> )
Peak ac flux density	$B_{max}$	(T)

# Procedure

## 1. Determine core size

---

$$K_{gfe} \geq \frac{\rho \lambda_1^2 I_{tot}^2 K_{fe}^{(2/\beta)}}{4K_u (P_{tot})^{((\beta+2)/\beta)}} 10^8$$

Select a core from Appendix 2 that satisfies this inequality.

It may be possible to reduce the core size by choosing a core material that has lower loss, i.e., lower  $K_{fe}$ .

## 2. Evaluate peak ac flux density

---

$$B_{max} = \left[ 10^8 \frac{\rho \lambda_1^2 I_{tot}^2}{2K_u} \frac{(MLT)}{W_A A_c^3 l_m} \frac{1}{\beta K_{fe}} \right]^{\left(\frac{1}{\beta + 2}\right)}$$

At this point, one should check whether the saturation flux density is exceeded. If the core operates with a flux dc bias  $B_{dc}$ , then  $B_{max} + B_{dc}$  should be less than the saturation flux density.

If the core will saturate, then there are two choices:

- Specify  $B_{max}$  using the  $K_g$  method of Chapter 13, or
- Choose a core material having greater core loss, then repeat steps 1 and 2

## 3. and 4. Evaluate turns

---

Primary turns:

$$n_1 = \frac{\lambda_1}{2B_{max}A_c} 10^4$$

Choose secondary turns according to desired turns ratios:

$$\begin{aligned} n_2 &= n_1 \left( \frac{n_2}{n_1} \right) \\ n_3 &= n_1 \left( \frac{n_3}{n_1} \right) \\ &\vdots \end{aligned}$$

## 5. and 6. Choose wire sizes

---

Fraction of window area  
assigned to each winding:

$$\alpha_1 = \frac{n_1 I_1}{n_1 I_{tot}}$$

$$\alpha_2 = \frac{n_2 I_2}{n_1 I_{tot}}$$

$\vdots$

$$\alpha_k = \frac{n_k I_k}{n_1 I_{tot}}$$

Choose wire sizes according  
to:

$$A_{w1} \leq \frac{\alpha_1 K_u W_A}{n_1}$$

$$A_{w2} \leq \frac{\alpha_2 K_u W_A}{n_2}$$

$\vdots$

# Check: computed transformer model

Predicted magnetizing inductance, referred to primary:

$$L_M = \frac{\mu n_1^2 A_c}{l_m}$$

Peak magnetizing current:


$$i_{M, pk} = \frac{\lambda_1}{2L_M}$$

Predicted winding resistances:

$$R_1 = \frac{\rho n_1 (MLT)}{A_{w1}}$$


$$R_2 = \frac{\rho n_2 (MLT)}{A_{w2}}$$

⋮

 


 
## 14.4.1 Example 1: Single-output isolated Cuk converter



$$100 \text{ W}$$

$$f_s = 200 \text{ kHz}$$

$$D = 0.5$$

$$n = 5$$

$$K_u = 0.5$$


$$\text{Allow } P_{tot} = 0.25 \text{ W}$$

Use a ferrite pot core, with Magnetics Inc. P material. Loss parameters at 200 kHz are

$$K_{fe} = 24.7$$

$$\beta = 2.6$$

# Waveforms

 

Applied primary volt-seconds:

$$\lambda_1 = DT_s V_{c1} = (0.5) (5 \mu\text{sec}) (25 \text{ V}) = 62.5 \text{ V-}\mu\text{sec}$$

Applied primary rms current:

$$I_1 = \sqrt{D \left( \frac{I}{n} \right)^2 + D' (I_g)^2} = 4 \text{ A}$$

Applied secondary rms current:

$$I_2 = nI_1 = 20 \text{ A}$$

Total rms winding current:

$$I_{\text{tot}} = I_1 + \frac{1}{n} I_2 = 8 \text{ A}$$

# Choose core size

---

$$K_{gfe} \geq \frac{(1.724 \cdot 10^{-6})(62.5 \cdot 10^{-6})^2(8)^2(24.7)^{(2/2.6)}}{4(0.5)(0.25)^{(4.6/2.6)}} 10^8$$
$$= 0.00295$$

Pot core data of Appendix 2 lists 2213 pot core with

$$K_{gfe} = 0.0049$$

Next smaller pot core is not large enough.

# Evaluate peak ac flux density

---

$$B_{max} = \left[ 10^8 \frac{(1.724 \cdot 10^{-6})(62.5 \cdot 10^{-6})^2(8)^2}{2 (0.5)} \frac{(4.42)}{(0.297)(0.635)^3(3.15)} \frac{1}{(2.6)(24.7)} \right]^{(1/4.6)}$$
$$= 0.0858 \text{ Tesla}$$

This is much less than the saturation flux density of approximately 0.35 T. Values of Bmax in the vicinity of 0.1 T are typical for ferrite designs that operate at frequencies in the vicinity of 100 kHz.

# Evaluate turns

---

$$n_1 = 10^4 \frac{(62.5 \cdot 10^{-6})}{2(0.0858)(0.635)}$$
$$= 5.74 \text{ turns}$$

$$n_2 = \frac{n_1}{n} = 1.15 \text{ turns}$$

In practice, we might select

$$n_1 = 5 \quad \text{and} \quad n_2 = 1$$

This would lead to a slightly higher flux density and slightly higher loss.

# Determine wire sizes

---

Fraction of window area allocated to each winding:

$$\alpha_1 = \frac{(4 \text{ A})}{(8 \text{ A})} = 0.5$$

$$\alpha_2 = \frac{\left(\frac{1}{5}\right)(20 \text{ A})}{(8 \text{ A})} = 0.5$$

(Since, in this example, the ratio of winding rms currents is equal to the turns ratio, equal areas are allocated to each winding)

Wire areas:

$$A_{w1} = \frac{(0.5)(0.5)(0.297)}{(5)} = 14.8 \cdot 10^{-3} \text{ cm}^2$$

$$A_{w2} = \frac{(0.5)(0.5)(0.297)}{(1)} = 74.2 \cdot 10^{-3} \text{ cm}^2$$

From wire table,  
Appendix 2:

AWG #16

AWG #9

# Wire sizes: discussion

---

## *Primary*

5 turns #16 AWG

## *Secondary*


1 turn #9 AWG

- Very large conductors!
- One turn of #9 AWG is not a practical solution

## *Some alternatives*

- Use foil windings
- Use Litz wire or parallel strands of wire
 
# Effect of switching frequency on transformer size for this P-material Cuk converter example




- As switching frequency is increased from 25 kHz to 250 kHz, core size is dramatically reduced
- As switching frequency is increased from 400 kHz to 1 MHz, core size increases



## 14.4.2 Example 2
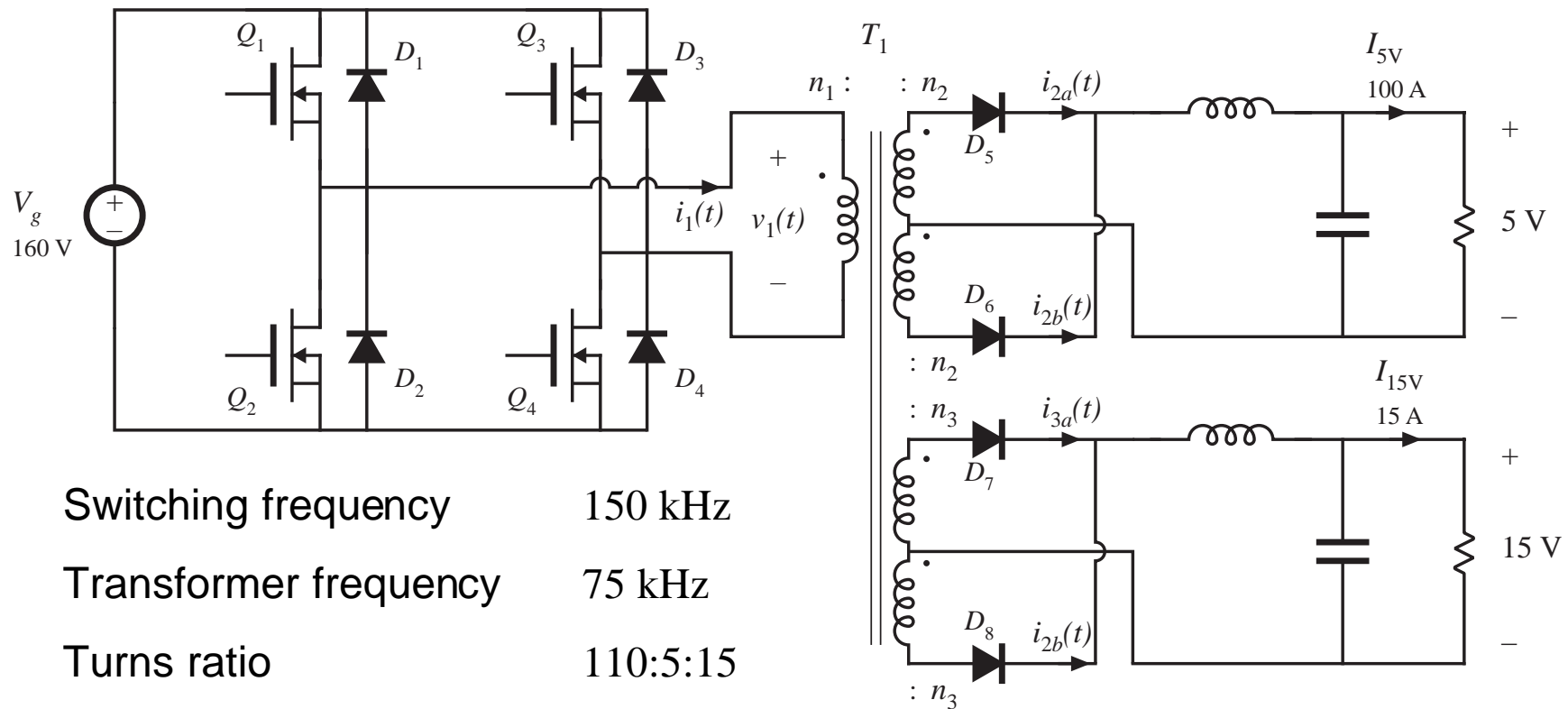
### Multiple-Output Full-Bridge Buck Converter



Switching frequency      150 kHz

Transformer frequency      75 kHz

Turns ratio      110:5:15

Optimize transformer at       $D = 0.75$

# Other transformer design details

---

Use Magnetics, Inc. ferrite P material. Loss parameters at 75 kHz:

$$K_{fe} = 7.6 \text{ W/T}^\beta\text{cm}^3$$

$$\beta = 2.6$$

Use E-E core shape

Assume fill factor of

$$K_u = 0.25 \quad (\text{reduced fill factor accounts for added insulation required in multiple-output off-line application})$$



Allow transformer total power loss of

$$P_{tot} = 4 \text{ W} \quad (\text{approximately 0.5\% of total output power})$$

Use copper wire, with


$$\rho = 1.724 \cdot 10^{-6} \text{ } \Omega\text{-cm}$$

# Applied transformer waveforms

 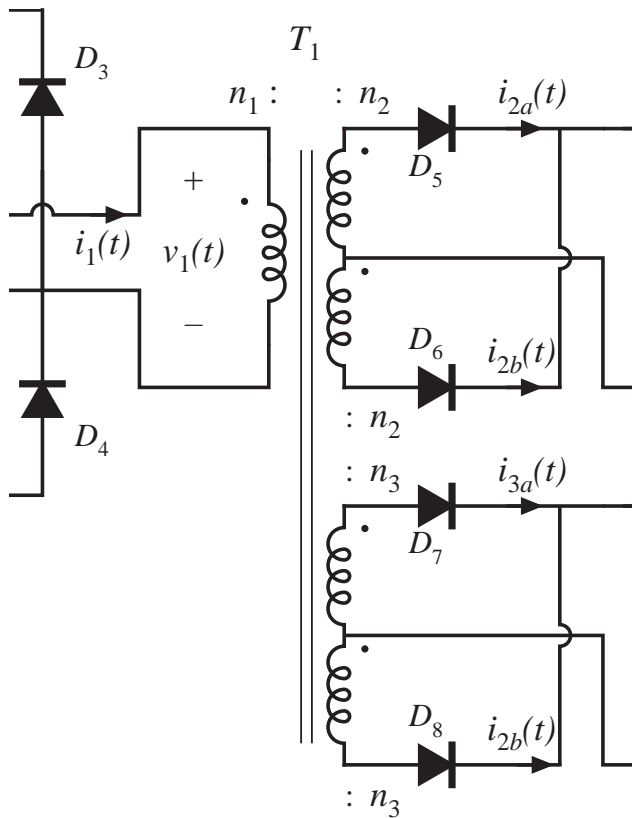


# Applied primary volt-seconds

---

 


$$\lambda_1 = DT_s V_g = (0.75) (6.67 \mu\text{sec}) (160 \text{ V}) = 800 \text{ V-}\mu\text{sec}$$

# Applied primary rms current

 

$$I_1 = \left( \frac{n_2}{n_1} I_{5V} + \frac{n_3}{n_1} I_{15V} \right) \sqrt{D} = 5.7 \text{ A}$$
 
## Applied rms current, secondary windings



$$I_2 = \frac{1}{2} I_{5V} \sqrt{1 + D} = 66.1 \text{ A}$$

$$I_3 = \frac{1}{2} I_{15V} \sqrt{1 + D} = 9.9 \text{ A}$$

$$I_{tot}$$

---

RMS currents, summed over all windings and referred to primary

$$\begin{aligned} I_{tot} &= \sum_{\substack{\text{all 5} \\ \text{windings}}} \frac{n_j}{n_1} I_j = I_1 + 2 \frac{n_2}{n_1} I_2 + 2 \frac{n_3}{n_1} I_3 \\ &= (5.7 \text{ A}) + \frac{5}{110} (66.1 \text{ A}) + \frac{15}{110} (9.9 \text{ A}) \\ &= 14.4 \text{ A} \end{aligned}$$


# Select core size

$$K_{gfe} \geq \frac{(1.724 \cdot 10^{-6})(800 \cdot 10^{-6})^2(14.4)^2(7.6)^{(2/2.6)}}{4(0.25)(4)^{(4.6/2.6)}} 10^8$$

$$= 0.00937$$

## A2.2 EE core data

From Appendix 2

 

Core type	Geometrical constant	Geometrical constant	Cross-sectional area	Bobbin winding area	Mean length per turn	Magnetic path length	Core weight
(A) (mm)	$K_{gs}$ $\text{cm}^5$	$K_{gfe}$ $\text{cm}^x$	$A_c$ $(\text{cm}^2)$	$W_A$ $(\text{cm}^2)$	$MLT$ (cm)	$l_m$ (cm)	(g)
EE22	$8.26 \cdot 10^{-3}$	$1.8 \cdot 10^{-3}$	0.41	0.196	3.99	3.96	8.81
EE30	$85.7 \cdot 10^{-3}$	$6.7 \cdot 10^{-3}$	1.09	0.476	6.60	5.77	32.4
→ EE40	0.209	$11.8 \cdot 10^{-3}$	1.27	1.10	8.50	7.70	50.3
EE50	0.909	$28.4 \cdot 10^{-3}$	2.26	1.78	10.0	9.58	116



## Evaluate ac flux density $B_{max}$

---

Eq. (14.41):

$$B_{max} = \left[ 10^8 \frac{\rho \lambda_1^2 I_{tot}^2}{2K_u} \frac{(MLT)}{W_A A_c^3 l_m} \frac{1}{\beta K_{fe}} \right]^{\left(\frac{1}{\beta + 2}\right)}$$

Plug in values:

$$B_{max} = \left[ 10^8 \frac{(1.724 \cdot 10^{-6})(800 \cdot 10^{-6})^2 (14.4)^2}{2 (0.25)} \frac{(8.5)}{(1.1)(1.27)^3 (7.7)} \frac{1}{(2.6)(7.6)} \right]^{(1/4.6)}$$

= 0.23 Tesla

This is less than the saturation flux density of approximately 0.35 T

# Evaluate turns

Choose  $n_1$  according to Eq. (14.42):

$$n_1 = \frac{\lambda_1}{2B_{max}A_c} 10^4$$
$$n_1 = 10^4 \frac{(800 \cdot 10^{-6})}{2(0.23)(1.27)}$$
$$= 13.7 \text{ turns}$$

Choose secondary turns  
according to desired turns ratios:

$$n_2 = \frac{5}{110} n_1 = 0.62 \text{ turns}$$

$$n_3 = \frac{15}{110} n_1 = 1.87 \text{ turns}$$

## *Rounding the number of turns*

To obtain desired turns ratio  
of

110:5:15

we might round the actual  
turns to

22:1:3

Increased  $n_1$  would lead to

- Less core loss
- More copper loss
- Increased total loss

# Loss calculation

## with rounded turns

---

With  $n_1 = 22$ , the flux density will be reduced to

$$B_{max} = \frac{(800 \cdot 10^{-6})}{2 (22) (1.27)} 10^4 = 0.143 \text{ Tesla}$$

The resulting losses will be

$$P_{fe} = (7.6)(0.143)^{2.6}(1.27)(7.7) = 0.47 \text{ W}$$

$$P_{cu} = \frac{(1.724 \cdot 10^{-6})(800 \cdot 10^{-6})^2(14.4)^2}{4 (0.25)} \frac{(8.5)}{(1.1)(1.27)^2} \frac{1}{(0.143)^2} 10^8$$
$$= 5.4 \text{ W}$$

$$P_{tot} = P_{fe} + P_{cu} = 5.9 \text{ W}$$

Which exceeds design goal of 4 W by 50%. So use next larger core size: EE50.

# Calculations with EE50

---

Repeat previous calculations for EE50 core size. Results:

$$B_{max} = 0.14 \text{ T}, n_1 = 12, P_{tot} = 2.3 \text{ W}$$

Again round  $n_1$  to 22. Then

$$B_{max} = 0.08 \text{ T}, P_{cu} = 3.89 \text{ W}, P_{fe} = 0.23 \text{ W}, P_{tot} = 4.12 \text{ W}$$

Which is close enough to 4 W.

# Wire sizes for EE50 design

---

## Window allocations

$$\alpha_1 = \frac{I_1}{I_{tot}} = \frac{5.7}{14.4} = 0.396$$

$$\alpha_2 = \frac{n_2 I_2}{n_1 I_{tot}} = \frac{5}{110} \frac{66.1}{14.4} = 0.209$$

$$\alpha_3 = \frac{n_3 I_3}{n_1 I_{tot}} = \frac{15}{110} \frac{9.9}{14.4} = 0.094$$

## Wire gauges

$$A_{w1} = \frac{\alpha_1 K_u W_A}{n_1} = \frac{(0.396)(0.25)(1.78)}{(22)} = 8.0 \cdot 10^{-3} \text{ cm}^2$$

$\Rightarrow$  AWG #19

$$A_{w2} = \frac{\alpha_2 K_u W_A}{n_2} = \frac{(0.209)(0.25)(1.78)}{(1)} = 93.0 \cdot 10^{-3} \text{ cm}^2$$

$\Rightarrow$  AWG #8

$$A_{w3} = \frac{\alpha_3 K_u W_A}{n_3} = \frac{(0.094)(0.25)(1.78)}{(3)} = 13.9 \cdot 10^{-3} \text{ cm}^2$$

$\Rightarrow$  AWG #16

Might actually use foil or Litz wire for secondary windings

# Part IV

## Modern Rectifiers and Power System Harmonics

---

- Chapter 15      Power and Harmonics in Nonsinusoidal Systems
- Chapter 16      Line-Commutated Rectifiers
- Chapter 17      The Ideal Rectifier
- Chapter 18      Low Harmonic Rectifier Modeling and Control

# Chapter 15


## Power And Harmonics in Nonsinusoidal Systems

---

- 15.1. Average power  
in terms of Fourier series
- 15.2. RMS value of a waveform
- 15.3. Power factor  
THD  
Distortion and Displacement factors
- 15.4. Power phasors in sinusoidal systems
- 15.5. Harmonic currents in three-phase systems
- 15.6. AC line current harmonic standards
 
## 15.1. Average power

*Observe transmission of energy through surface  $S$*



Express voltage  
and current as  
Fourier series:

$$v(t) = V_0 + \sum_{n=1}^{\infty} V_n \cos(n\omega t - \phi_n)$$
$$i(t) = I_0 + \sum_{n=1}^{\infty} I_n \cos(n\omega t - \theta_n)$$

relate energy  
transmission to  
harmonics



# Energy transmitted to load, per cycle

---

$$W_{cycle} = \int_0^T v(t)i(t)dt$$

This is related to average power as follows:

$$P_{av} = \frac{W_{cycle}}{T} = \frac{1}{T} \int_0^T v(t)i(t)dt$$

Investigate influence of harmonics on average power: substitute Fourier series

$$P_{av} = \frac{1}{T} \int_0^T \left( V_0 + \sum_{n=1}^{\infty} V_n \cos(n\omega t - \phi_n) \right) \left( I_0 + \sum_{n=1}^{\infty} I_n \cos(n\omega t - \theta_n) \right) dt$$

# Evaluation of integral

---

Orthogonality of harmonics: Integrals of cross-product terms are zero

$$\int_0^T \left( V_n \cos(n\omega t - \phi_n) \right) \left( I_m \cos(m\omega t - \theta_m) \right) dt = \begin{cases} 0 & \text{if } n \neq m \\ \frac{V_n I_n}{2} \cos(\phi_n - \theta_n) & \text{if } n = m \end{cases}$$

Expression for average power becomes

$$P_{av} = V_0 I_0 + \sum_{n=1}^{\infty} \frac{V_n I_n}{2} \cos(\phi_n - \theta_n)$$

So net energy is transmitted to the load only when the Fourier series of  $v(t)$  and  $i(t)$  contain terms at the same frequency. For example, if the voltage and current both contain third harmonic, then they lead to the average power


$$\frac{V_3 I_3}{2} \cos(\phi_3 - \theta_3)$$

# Example 1

**Voltage:** fundamental only

**Current:** third harmonic only

**Power:** zero average

 


## Example 2

**Voltage:** third harmonic only

**Current:** third harmonic only, in phase with voltage

**Power:** nonzero average

 

## Example 3

---

Fourier series:

$$v(t) = 1.2 \cos(\omega t) + 0.33 \cos(3\omega t) + 0.2 \cos(5\omega t)$$

$$i(t) = 0.6 \cos(\omega t + 30^\circ) + 0.1 \cos(5\omega t + 45^\circ) + 0.1 \cos(7\omega t + 60^\circ)$$

Average power calculation:


$$P_{av} = \frac{(1.2)(0.6)}{2} \cos(30^\circ) + \frac{(0.2)(0.1)}{2} \cos(45^\circ) = 0.32$$

## Example 3

**Voltage:** 1st, 3rd, 5th

**Current:** 1st, 5th, 7th

 **Power:** net energy is transmitted at fundamental and fifth harmonic frequencies



## 15.2. Root-mean-square (RMS) value of a waveform, in terms of Fourier series

---

$$(\text{rms value}) = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

Insert Fourier series. Again, cross-multiplication terms have zero average. Result is

$$(\text{rms value}) = \sqrt{V_0^2 + \sum_{n=1}^{\infty} \frac{V_n^2}{2}}$$

- Similar expression for current
- Harmonics always increase rms value
- Harmonics do not necessarily increase average power
- Increased rms values mean increased losses

## 15.3. Power factor

---

For efficient transmission of energy from a source to a load, it is desired to maximize average power, while minimizing rms current and voltage (and hence minimizing losses).

Power factor is a figure of merit that measures how efficiently energy is transmitted. It is defined as

$$\text{power factor} = \frac{(\text{average power})}{(\text{rms voltage}) (\text{rms current})}$$

Power factor always lies between zero and one.



### 15.3.1. Linear resistive load, nonsinusoidal voltage

---

Then current harmonics are in phase with, and proportional to, voltage harmonics. All harmonics result in transmission of energy to load, and unity power factor occurs.

$$I_n = \frac{V_n}{R} \qquad \theta_n = \varphi_n \qquad \text{so} \quad \cos(\theta_n - \varphi_n) = 1$$

$$(\text{rms voltage}) = \sqrt{V_0^2 + \sum_{n=1}^{\infty} \frac{V_n^2}{2}}$$

$$\begin{aligned} (\text{rms current}) &= \sqrt{I_0^2 + \sum_{n=1}^{\infty} \frac{I_n^2}{2}} = \sqrt{\frac{V_0^2}{R^2} + \sum_{n=1}^{\infty} \frac{V_n^2}{2R^2}} \\ &= \frac{1}{R} (\text{rms voltage}) \end{aligned}$$

$$P_{av} = V_0 I_0 + \sum_{n=1}^{\infty} \frac{V_n I_n}{2} \cos(\varphi_n - \theta_n)$$

### 15.3.2. Nonlinear dynamical load, sinusoidal voltage

---

With a sinusoidal voltage, current harmonics do not lead to average power. However, current harmonics do increase the rms current, and hence they decrease the power factor.

$$P_{av} = \frac{V_1 I_1}{2} \cos (\varphi_1 - \theta_1)$$

$$(\text{rms current}) = \sqrt{I_0^2 + \sum_{n=1}^{\infty} \frac{I_n^2}{2}}$$

$$(\text{power factor}) = \left( \frac{\frac{I_1}{\sqrt{2}}}{\sqrt{I_0^2 + \sum_{n=1}^{\infty} \frac{I_n^2}{2}}} \right) (\cos (\varphi_1 - \theta_1))$$

$$= (\text{distortion factor}) (\text{displacement factor})$$

# Distortion factor

---

Defined only for sinusoidal voltage.


$$(\text{distortion factor}) = \left( \frac{\frac{I_1}{\sqrt{2}}}{\sqrt{I_0^2 + \sum_{n=1}^{\infty} \frac{I_n^2}{2}}} \right) = \frac{(\text{rms fundamental current})}{(\text{rms current})}$$

Related to Total Harmonic Distortion (THD):

$$(\text{THD}) = \frac{\sqrt{\sum_{n=2}^{\infty} I_n^2}}{I_1}$$


$$(\text{distortion factor}) = \frac{1}{\sqrt{1 + (\text{THD})^2}}$$

# Distortion factor vs. THD

 

 
# Peak detection rectifier example

*Conventional single-phase peak detection rectifier*



*Typical ac line current spectrum*

 

## Maximum power obtainable from 120V 15A wall outlet

---

*with peak detection rectifier*

$$\begin{aligned} & (\text{ac voltage}) (\text{derated breaker current}) (\text{power factor}) (\text{rectifier efficiency}) \\ &= (120 \text{ V}) \quad (80\% \text{ of } 15 \text{ A}) \quad (0.55) \quad (0.98) \\ &= 776 \text{ W} \end{aligned}$$

*at unity power factor*

$$\begin{aligned} & (\text{ac voltage}) (\text{derated breaker current}) (\text{power factor}) (\text{rectifier efficiency}) \\ &= (120 \text{ V}) \quad (80\% \text{ of } 15 \text{ A}) \quad (0.99) \quad (0.93) \\ &= 1325 \text{ W} \end{aligned}$$

## 15.4. Power phasors in sinusoidal systems

---

*Apparent power* is the product of the rms voltage and rms current

It is easily measured —simply the product of voltmeter and ammeter readings

Unit of apparent power is the volt-ampere, or VA

Many elements, such as transformers, are rated according to the VA that they can supply

So power factor is the ratio of average power to apparent power

With sinusoidal waveforms (no harmonics), we can also define the

*real power  $P$*

*reactive power  $Q$*

*complex power  $S$*

If the voltage and current are represented by phasors  $V$  and  $I$ , then

$$S = VI^* = P + jQ$$


with  $I^*$  = complex conjugate of  $I$ ,  $j$  = square root of  $-1$ . The magnitude of  $S$  is the apparent power (VA). The real part of  $S$  is the average power  $P$  (watts). The imaginary part of  $S$  is the reactive power  $Q$  (reactive volt-amperes, or VARs).

## Example: power phasor diagram

The phase angle between the voltage and current, or  $(\varphi_1 - \theta_1)$ , coincides with the angle of  $S$ . The power factor is

$$\text{power factor} = \frac{P}{\|S\|} = \cos(\varphi_1 - \theta_1)$$

 In this purely sinusoidal case, the distortion factor is unity, and the power factor coincides with the displacement factor.





# Reactive power $Q$

---

The reactive power  $Q$  does not lead to net transmission of energy between the source and load. When  $Q \neq 0$ , the rms current and apparent power are greater than the minimum amount necessary to transmit the average power  $P$ .

*Inductor:* current lags voltage by  $90^\circ$ , hence displacement factor is zero.

The alternate storing and releasing of energy in an inductor leads to current flow and nonzero apparent power, but  $P = 0$ .

Just as resistors consume real (average) power  $P$ , inductors can be viewed as consumers of reactive power  $Q$ .

*Capacitor:* current leads voltage by  $90^\circ$ , hence displacement factor is zero.

Capacitors supply reactive power  $Q$ .

They are often placed in the utility power distribution system near inductive loads. If  $Q$  supplied by capacitor is equal to  $Q$  consumed by inductor, then the net current (flowing from the source into the capacitor-inductive-load combination) is in phase with the voltage, leading to unity power factor and minimum rms current magnitude.

# Lagging fundamental current of phase-controlled rectifiers

---

It will be seen in the next chapter that phase-controlled rectifiers produce a nonsinusoidal current waveform whose fundamental component lags the voltage.

This lagging current does not arise from energy storage, but it does nonetheless lead to a reduced displacement factor, and to rms current and apparent power that are greater than the minimum amount necessary to transmit the average power.

At the fundamental frequency, phase-controlled rectifiers can be viewed as consumers of reactive power  $Q$ , similar to inductive loads.

## 15.5. Harmonic currents in three phase systems

---


The presence of harmonic currents can also lead to some special problems in three-phase systems:

- In a four-wire three-phase system, harmonic currents can lead to large currents in the neutral conductors, which may easily exceed the conductor rms current rating
- Power factor correction capacitors may experience significantly increased rms currents, causing them to fail

In this section, these problems are examined, and the properties of harmonic current flow in three-phase systems are derived:

- Harmonic neutral currents in 3 $\phi$  four-wire networks
- Harmonic neutral voltages in 3 $\phi$  three-wire wye-connected loads
 
## 15.5.1. Harmonic currents in three-phase four-wire networks



*Fourier series of  
line currents and  
voltages:*

$$i_a(t) = I_{a0} + \sum_{k=1}^{\infty} I_{ak} \cos(k\omega t - \theta_{ak})$$

$$i_b(t) = I_{b0} + \sum_{k=1}^{\infty} I_{bk} \cos(k(\omega t - 120^\circ) - \theta_{bk})$$

$$i_c(t) = I_{c0} + \sum_{k=1}^{\infty} I_{ck} \cos(k(\omega t + 120^\circ) - \theta_{ck})$$

$$v_{an}(t) = V_m \cos(\omega t)$$

$$v_{bn}(t) = V_m \cos(\omega t - 120^\circ)$$

$$v_{cn}(t) = V_m \cos(\omega t + 120^\circ)$$

# Neutral current

---

$$i_n(t) = I_{a0} + I_{b0} + I_{c0} + \sum_{k=1}^{\infty} \left[ I_{ak} \cos(k\omega t - \theta_{ak}) + I_{bk} \cos(k(\omega t - 120^\circ) - \theta_{bk}) + I_{ck} \cos(k(\omega t + 120^\circ) - \theta_{ck}) \right]$$

If the load is unbalanced, then there is nothing more to say. The neutral connection may contain currents having spectrum similar to the line currents.

In the balanced case,  $I_{ak} = I_{bk} = I_{ck} = I_k$  and  $\theta_{ak} = \theta_{bk} = \theta_{ck} = \theta_k$ , for all  $k$ ; i.e., the harmonics of the three phases all have equal amplitudes and phase shifts. The neutral current is then

$$i_n(t) = 3I_0 + \sum_{k=3,6,9,\dots}^{\infty} 3I_k \cos(k\omega t - \theta_k)$$

# Neutral currents

---

$$i_n(t) = 3I_0 + \sum_{k=3,6,9,\dots}^{\infty} 3I_k \cos(k\omega t - \theta_k)$$

- Fundamental and most harmonics cancel out
- Triplen (triple-n, or 0, 3, 6, 9, ...) harmonics do not cancel out, but add. Dc components also add.
- Rms neutral current is

$$i_{n, rms} = 3 \sqrt{I_0^2 + \sum_{k=3,6,9,\dots}^{\infty} \frac{I_k^2}{2}}$$

# Example

A balanced nonlinear load produces line currents containing fundamental and 20% third harmonic:  $i_{an}(t) = I_1 \cos(\omega t - \theta_1) + 0.2 I_1 \cos(3\omega t - \theta_3)$ . Find the rms neutral current, and compare its amplitude to the rms line current amplitude.


**Solution**

$$i_{n, rms} = 3 \sqrt{\frac{(0.2I_1)^2}{2}} = \frac{0.6 I_1}{\sqrt{2}}$$
$$i_{1, rms} = \sqrt{\frac{I_1^2 + (0.2I_1)^2}{2}} = \frac{I_1}{\sqrt{2}} \sqrt{1 + 0.04} \approx \frac{I_1}{\sqrt{2}}$$

- The neutral current magnitude is 60% of the line current magnitude!
- The triplen harmonics in the three phases add, such that 20% third harmonic leads to 60% third harmonic neutral current.
- Yet the presence of the third harmonic has very little effect on the rms value of the line current. Significant unexpected neutral current flows.
 
## 15.5.2. Harmonic currents in three-phase three-wire networks

Wye-connected nonlinear load, no neutral connection:





# No neutral connection

---

If the load is balanced, then it is still true that

$$i_n(t) = 3I_0 + \sum_{k=3,6,9,\dots}^{\infty} 3I_k \cos(k\omega t - \theta_k)$$

But  $i_n(t) = 0$ , since there is no neutral connection.

So the ac line currents cannot contain dc or triplen harmonics.


What happens:

A voltage is induced at the load neutral point, that causes the line current dc and triplen harmonics to become zero.

The load neutral point voltage contains dc and triplen harmonics.

With an unbalanced load, the line currents can still contain dc and triplen harmonics.

# Delta-connected load

 

- There is again no neutral connection, so the ac line currents contain no dc or triplen harmonics
- The load currents may contain dc and triplen harmonics: with a balanced nonlinear load, these circulate around the delta.

# Harmonic currents in power factor correction capacitors


---

PFC capacitors are usually not intended to conduct significant harmonic currents.

Heating in capacitors is a function of capacitor equivalent series resistance (esr) and rms current. The maximum allowable rms current then leads to the capacitor rating:

$$\text{rated rms voltage } V_{rms} = \frac{I_{rms}}{2\pi fC}$$
 
$$\text{rated reactive power} = \frac{I_{rms}^2}{2\pi fC}$$



## 15.6. AC line current harmonic standards

---

15.6.1. US MIL-STD-461B

15.6.2. International Electrotechnical Commission Standard 555

15.6.3. IEEE/ANSI Standard 519

## 15.6.1. US MIL-STD-461B

---

- For loads of 1kW or greater, no current harmonic magnitude may be greater than 3% of the fundamental magnitude.
- For the  $n$ th harmonic with  $n > 33$ , the harmonic magnitude may not exceed  $(1/n)$  times the fundamental magnitude.
- Harmonic limits are now employed by all of the US armed forces. The specific limits are often tailored to the specific application.
- The shipboard application is a good example of the problems faced in a relatively small stand-alone power system having a large fraction of electronic loads.

## 15.6.2. International Electrotechnical Commission Standard 555

---

- First draft of their IEC-555 standard:1982. It has since undergone a number of revisions.
- Enforcement of IEC-555 is the prerogative of each individual country, and hence it has been sometimes difficult to predict whether and where this standard will actually be given the force of law.
- Nonetheless, IEC-555 is now enforced in Europe, making it a de facto standard for commercial equipment intended to be sold worldwide.
- IEC-555 covers a number of different types of low power equipment, with differing harmonic limits. Harmonics for equipment having an input current of up to 16A, connected to 50 or 60 Hz, 220V to 240V single phase circuits (two or three wire), as well as 380V to 415V three phase (three or four wire) circuits, are limited.

# Low-power harmonic limits

---

- In a city environment such as a large building, a large fraction of the total power system load can be nonlinear
- Example: a major portion of the electrical load in a building is comprised of fluorescent lights, which present a very nonlinear characteristic to the utility system.
- A modern office may also contain a large number of personal computers, printers, copiers, etc., each of which may employ peak detection rectifiers.
- Although each individual load is a negligible fraction of the total local load, these loads can collectively become significant.

# IEC-555: Class A and B

---

**Class A:** Balanced three-phase equipment, and any equipment which does not fit into the other categories. This class includes low harmonic rectifiers for computer and other office equipment. These limits are given in Table 15.1, and are absolute ampere limits.

**Class B:** Portable tools, and similar devices. The limits are equal to the Table 15.1 limits, multiplied by 1.5.



# Class A limits

*Table 15.1. IEC-555 Harmonic current limits, Class A and certain Class C*

<i>Odd harmonics</i>		<i>Even harmonics</i>	
<i>Harmonic number</i>	<i>Maximum current</i>	<i>Harmonic number</i>	<i>Maximum current</i>
3	2.30A	2	1.08A
5	1.14A	4	0.43A
7	0.77A	6	0.30A
9	0.40A	$8 \leq n \leq 40$	$0.23A \cdot (8/n)$
11	0.33A		
13	0.21A		
$15 \leq n \leq 39$	$0.15A \cdot (15/n)$		

## IEC-555: Class C

---

**Class C:** Lighting equipment, including dimmers and gas discharge lamps. The input current harmonics of ballasted lamps with an input power of more than 25W must meet the limits of Table 15.2, expressed as a percent of the fundamental current. If the input power is less than 25W, then Table 15.3 applies. Incandescent lamp fixtures containing phase-control dimmers, rated at greater than 600W, must meet the limits of Table 15.1. When testing for compliance, the dimmer must drive a rated-power lamp, with the phase control set to a firing angle of  $90^\circ \pm 5^\circ$ . Incandescent lamp dimmers rated at less than 600W are not covered by the standard. Discharge lamps containing dimmers must meet the limits of both Tables 15.2 and 15.3 at maximum load. Harmonic currents at any dimming position may not exceed the maximum load harmonic currents.


# Class C limits

*Table 15.2. IEC-555 Harmonic current limits, certain Class C*

<i>Harmonic number</i>	<i>Maximum current, percent of fundamental</i>
2	2%
3	(30%) · (power factor)
5	10%
7	7%
9	5%
$11 \leq n \leq 39$	3%
 
# IEC-555: Class D

**Class D:** Equipment not covered by Class B or C, which has a special waveshape as defined below. This class is directed at diode-capacitor peak-detection rectifiers. Equipment is placed in class D if the ac input current waveshape lies within the shaded area for at least 95% of the duration of each half-cycle. The center line of the shaded area is set to coincide with the peak of the current waveform. A sinusoid, and a typical peak detection rectifier waveform, are shown for reference; the sinusoid is not Class D but the peak detection rectifier waveform is. The limits for Class D equipment are given in Table 15.3.



# Class D limits

*Table 15.3. IEC-555 Harmonic current limits, Class D and certain Class C*

<i>Odd harmonics</i>			<i>Even harmonics</i>		
<i>Harmonic number</i>	<i>Relative limit (mA/W)</i>	<i>Absolute limit (A)</i>	<i>Harmonic number</i>	<i>Relative limit (mA/W)</i>	<i>Absolute limit (A)</i>
3	3.6	2.30A	2	1.0	0.3A
5	2.0	1.14A	4	0.5	0.15A
7	1.5	0.77A			
9	1.0	0.40A			
$11 \leq n \leq 39$	$0.6 \cdot (11/n)$	0.33A			

### 15.6.3. IEEE/ANSI Standard 519

---

- In 1993, the IEEE published a revised draft standard limiting the amplitudes of current harmonics, *IEEE Guide for Harmonic Control and Reactive Compensation of Static Power Converters*.
- Harmonic limits are based on the ratio of the fundamental component of the load current  $I_L$  to the short circuit current at the point of common (PCC) coupling at the utility  $I_{sc}$ .
- Stricter limits are imposed on large loads than on small loads. The limits are similar in magnitude to IEC-555, and cover high voltage loads (of much higher power) not addressed by IEC-555. Enforcement of this standard is presently up to the local utility company.
- The odd harmonic limits are listed in Tables 15.4 and 15.5. The limits for even harmonics are 25% of the odd harmonic limits. Dc current components and half-wave rectifiers are not allowed.

# IEEE-519 current limits, low voltage systems

*Table 15.4. IEEE-519 Maximum odd harmonic current limits for general distribution systems, 120V through 69kV*

$I_{sc}/I_L$	$n < 11$	$11 \leq n < 17$	$17 \leq n < 23$	$23 \leq n < 35$	$35 \leq n$	$THD$
<20	4.0%	2.0%	1.5%	0.6%	0.3%	5.0%
20–50	7.0%	3.5%	2.5%	1.0%	0.5%	8.0%
50–100	10.0%	4.5%	4.0%	1.5%	0.7%	12.0%
100–1000	12.0%	5.5%	5.0%	2.0%	1.0%	15.0%
>1000	15.0%	7.0%	6.0%	2.5%	1.4%	20.0%

# IEEE-519 current limits, high voltage systems

*Table 15.5. IEEE-519 Maximum odd harmonic current limits for general distribution systems, 69.001kV through 161kV*

$I_{sc}/I_L$	$n < 11$	$11 \leq n < 17$	$17 \leq n < 23$	$23 \leq n < 35$	$35 \leq n$	<i>THD</i>
<20	2.0%	1.0%	0.75%	0.3%	0.15%	2.5%
20–50	3.5%	1.75%	1.25%	0.5%	0.25%	4.0%
50–100	5.0%	2.25%	2.0%	0.75%	0.35%	6.0%
100–1000	6.0%	2.75%	2.5%	1.0%	0.5%	7.5%
>1000	7.5%	3.5%	3.0%	1.25%	0.7%	10.0%



# IEEE-519 voltage limits

---

*Table 15.6. IEEE-519 voltage distortion limits*

<i>Bus voltage at PCC</i>	<i>Individual harmonics</i>	<i>THD</i>
69kV and below	3.0%	5.0%
69.001kV–161kV	1.5%	2.5%
above 161kV	1.0%	1.5%

It is the responsibility of the utility to meet these limits.

# Chapter 16

## Line-Commutated Rectifiers

---

### 16.1 The single-phase full-wave rectifier

16.1.1 Continuous conduction mode

16.1.2 Discontinuous conduction mode

16.1.3 Behavior when  $C$  is large

16.1.4 Minimizing  $THD$  when  $C$  is small

### 16.2 The three-phase bridge rectifier

16.2.1 Continuous conduction mode

16.2.2 Discontinuous conduction mode

### 16.3 Phase control

16.3.1 Inverter mode

16.3.2 Harmonics and power factor


16.3.3 Commutation

16.4 Harmonic trap filters

16.5 Transformer connections

16.6 Summary
 
## 16.1 The single-phase full-wave rectifier



Full-wave rectifier with dc-side  $L$ - $C$  filter

Two common reasons for including the dc-side  $L$ - $C$  filter:


- Obtain good dc output voltage (large  $C$ ) and acceptable ac line current waveform (large  $L$ )
- Filter conducted EMI generated by dc load (small  $L$  and  $C$ )

## 16.1.1 Continuous conduction mode

Large  $L$

Typical ac line waveforms for CCM :

 As  $L \rightarrow \infty$ , ac line current approaches a square wave



CCM results, for  $L \rightarrow \infty$  :

$$\text{distortion factor} = \frac{I_{1, rms}}{I_{rms}} = \frac{4}{\pi \sqrt{2}} = 90.0\%$$


$$\text{THD} = \sqrt{\left(\frac{1}{\text{distortion factor}}\right)^2 - 1} = 48.3\%$$

## 16.1.2 Discontinuous conduction mode

Small  $L$

Typical ac line waveforms for DCM :

 As  $L \rightarrow 0$ , ac line current approaches impulse functions (peak detection)



As the inductance is reduced, the THD rapidly increases, and the distortion factor decreases.

Typical distortion factor of a full-wave rectifier with no inductor is in the range 55% to 65%, and is governed by ac system inductance.


## 16.1.3 Behavior when C is large

Solution of the full-wave rectifier circuit for infinite C:

Define

$$K_L = \frac{2L}{RT_L}$$


$$M = \frac{V}{V_m}$$

 
 
## 16.1.4 Minimizing $THD$ when $C$ is small

Sometimes the  $L$ - $C$  filter is present only to remove high-frequency conducted EMI generated by the dc load, and is not intended to modify the ac line current waveform. If  $L$  and  $C$  are both zero, then the load resistor is connected directly to the output of the diode bridge, and the ac line current waveform is purely sinusoidal.

An approximate argument: the  $L$ - $C$  filter has negligible effect on the ac line current waveform provided that the filter input impedance  $Z_i$  has zero phase shift at the second harmonic of the ac line frequency,  $2f_L$ .




# Approximate THD

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$R_0 = \sqrt{\frac{L}{C}}$$


$$Q = \frac{R}{R_0}$$
 
$$f_p = \frac{1}{2\pi RC} = \frac{f_0}{Q}$$







# Example

 

Typical ac line current and voltage waveforms, near the boundary between continuous and discontinuous modes and with small dc filter capacitor.  $f_0/f_L = 10$ ,  $Q = 1$

## 16.2 The Three-Phase Bridge Rectifier

  


## 16.2.1 Continuous conduction mode

*Fourier series:*


$$i_a(t) = \sum_{n=1,5,7,11,\dots}^{\infty} \frac{4}{n\pi} I_L \sin\left(\frac{n\pi}{2}\right) \sin\left(\frac{n\pi}{3}\right) \sin(n\omega t)$$

- Similar to square wave, but missing triplen harmonics
- THD = 31%
- Distortion factor =  $3/\pi = 95.5\%$
- In comparison with single phase case:

 the missing  $60^\circ$  of current improves the distortion factor from 90% to 95%, because the triplen harmonics are removed




## A typical CCM waveform

 

Inductor current contains sixth harmonic ripple (360 Hz for a 60 Hz ac system). This ripple is superimposed on the ac line current waveform, and influences the fifth and seventh harmonic content of  $i_a(t)$ .

## 16.2.2 Discontinuous conduction mode

 


Phase  $a$  current contains pulses at the positive and negative peaks of the line-to-line voltages  $v_{ab}(t)$  and  $v_{ac}(t)$ . Distortion factor and THD are increased. Distortion factor of the typical waveform illustrated above is 71%.

## 16.3 Phase control

Replace diodes with SCRs:


Phase control waveforms:

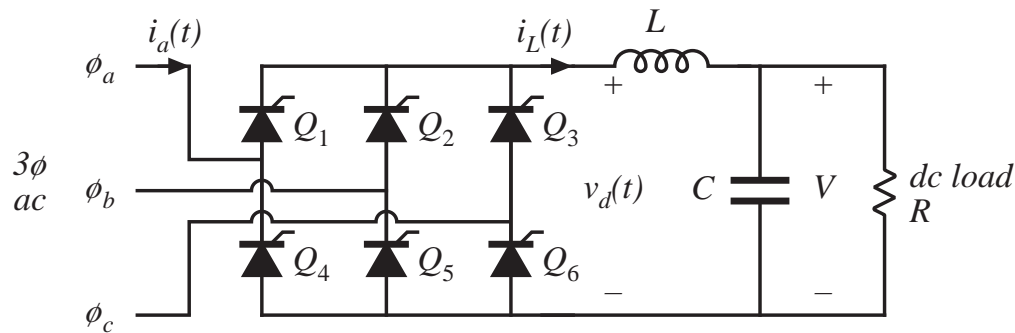

Average (dc) output voltage:

$$V = \frac{3}{\pi} \int_{30^\circ + \alpha}^{90^\circ + \alpha} \sqrt{3} V_m \sin(\theta + 30^\circ) d\theta$$
 
$$= \frac{3\sqrt{2}}{\pi} V_{L-L, rms} \cos \alpha$$




Upper thyristor:

$Q_3$     $Q_1$     $Q_1$     $Q_2$     $Q_2$     $Q_3$

Lower thyristor:


$Q_5$     $Q_5$     $Q_6$     $Q_6$     $Q_4$     $Q_4$
 
# Dc output voltage vs. delay angle $\alpha$



$$\begin{aligned} V &= \frac{3}{\pi} \int_{30^\circ+\alpha}^{90^\circ+\alpha} \sqrt{3} V_m \sin(\theta + 30^\circ) d\theta \\ &= \frac{3\sqrt{2}}{\pi} V_{L-L, rms} \cos \alpha \end{aligned}$$

## 16.3.1 Inverter mode

 

If the load is capable of supplying power, then the direction of power flow can be reversed by reversal of the dc output voltage  $V$ . The delay angle  $\alpha$  must be greater than  $90^\circ$ . The current direction is unchanged.



## 16.3.2 Harmonics and power factor

---

Fourier series of ac line current waveform, for large dc-side inductance:

$$i_a(t) = \sum_{n=1,5,7,11,\dots}^{\infty} \frac{4}{n\pi} I_L \sin\left(\frac{n\pi}{2}\right) \sin\left(\frac{n\pi}{3}\right) \sin(n\omega t - n\alpha)$$


Same as uncontrolled rectifier case, except that waveform is delayed by the angle  $\alpha$ . This causes the current to lag, and decreases the displacement factor. The power factor becomes:

$$\text{power factor} = 0.955 \left| \cos(\alpha) \right|$$

When the dc output voltage is small, then the delay angle  $\alpha$  is close to  $90^\circ$  and the power factor becomes quite small. The rectifier apparently consumes reactive power, as follows:

$$Q = \sqrt{3} I_{a, rms} V_{L-L, rms} \sin \alpha = I_L \frac{3\sqrt{2}}{\pi} V_{L-L, rms} \sin \alpha$$
 
# Real and reactive power in controlled rectifier at fundamental frequency




$$P = I_L \frac{3\sqrt{2}}{\pi} V_{L-L, rms} \cos \alpha$$

$$Q = \sqrt{3} I_{a, rms} V_{L-L, rms} \sin \alpha = I_L \frac{3\sqrt{2}}{\pi} V_{L-L, rms} \sin \alpha$$
 
## 16.4 Harmonic trap filters


A passive filter, having resonant zeroes tuned to the harmonic frequencies



# Harmonic trap


Ac source:  
model with  
Thevenin-equiv  
voltage source  
and impedance  
 $Z_s'(s)$ . Filter often  
contains series  
inductor  $sL_s'$ .  
Lump into  
effective  
impedance  $Z_s(s)$ :

$$Z_s(s) = Z_s'(s) + sL_s'$$


 

 
# Filter transfer function


$$H(s) = \frac{i_s(s)}{i_R(s)} = \frac{Z_1 \parallel Z_2 \parallel \dots}{Z_s + Z_1 \parallel Z_2 \parallel \dots} \quad \text{or} \quad H(s) = \frac{i_s(s)}{i_R(s)} = \frac{Z_s \parallel Z_1 \parallel Z_2 \parallel \dots}{Z_s}$$



# Simple example

  


# Simple example: transfer function

 


- Series resonance: fifth harmonic trap
- Parallel resonance:  $C_1$  and  $L_s$
- Parallel resonance tends to increase amplitude of third harmonic
- $Q$  of parallel resonance is larger than  $Q$  of series resonance

## Example 2

 




# Approximate impedance asymptotes



 


# Transfer function asymptotes


---

 

# Bypass resistor

   
 
# Harmonic trap filter with high-frequency roll-off




## 16.5 Transformer connections


Three-phase transformer connections can be used to shift the phase of the voltages and currents

This shifted phase can be used to cancel out the low-order harmonics

 
Three-phase delta-wye transformer connection shifts phase by  $30^\circ$ :



# Twelve-pulse rectifier

 

# Waveforms of 12 pulse rectifier

 

- Ac line current contains 1st, 11th, 13th, 23rd, 25th, etc. These harmonic amplitudes vary as  $1/n$
- 5th, 7th, 17th, 19th, etc. harmonics are eliminated

# Rectifiers with high pulse number

---

Eighteen-pulse rectifier:

- Use three six-pulse rectifiers
- Transformer connections shift phase by  $0^\circ$ ,  $+20^\circ$ , and  $-20^\circ$
- No 5th, 7th, 11th, 13th harmonics

Twenty-four-pulse rectifier

- Use four six-pulse rectifiers
- Transformer connections shift phase by  $0^\circ$ ,  $15^\circ$ ,  $-15^\circ$ , and  $30^\circ$
- No 5th, 7th, 11th, 13th, 17th, or 19th harmonics

If  $p$  is pulse number, then rectifier produces line current harmonics of number  $n = pk \pm 1$ , with  $k = 0, 1, 2, \dots$



# Chapter 17

## The Ideal Rectifier

---

- 17.1 Properties of the ideal rectifier
- 17.2 Realization of a near-ideal rectifier
- 17.3 Single-phase converter systems employing ideal rectifiers
- 17.4 RMS values of rectifier waveforms
- 17.5 Ideal three-phase rectifiers

## 17.1 Properties of the ideal rectifier


---

It is desired that the rectifier present a resistive load to the ac power system. This leads to

- unity power factor
- ac line current has same waveshape as voltage

$$i_{ac}(t) = \frac{v_{ac}(t)}{R_e}$$

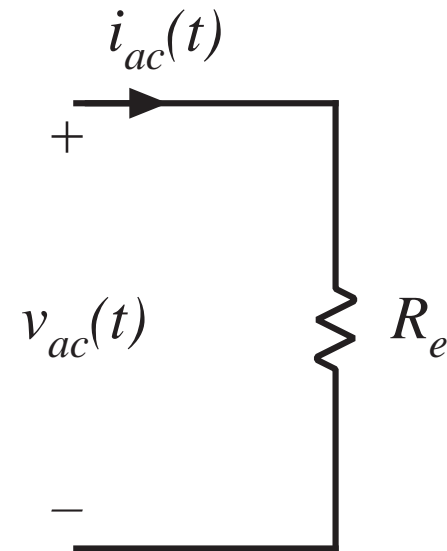$R_e$  is called the *emulated resistance*




# Control of power throughput

---


$$P_{av} = \frac{V_{ac,rms}^2}{R_e(v_{control})}$$

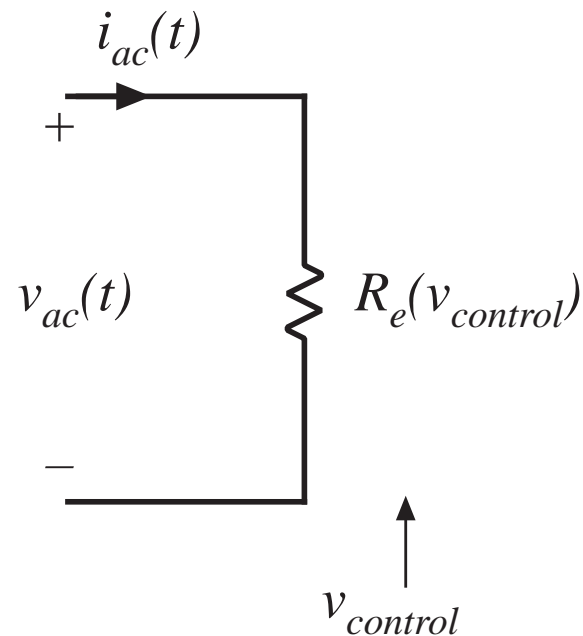Power apparently “consumed” by  $R_e$  is actually transferred to rectifier dc output port. To control the amount of output power, it must be possible to adjust the value of  $R_e$ .



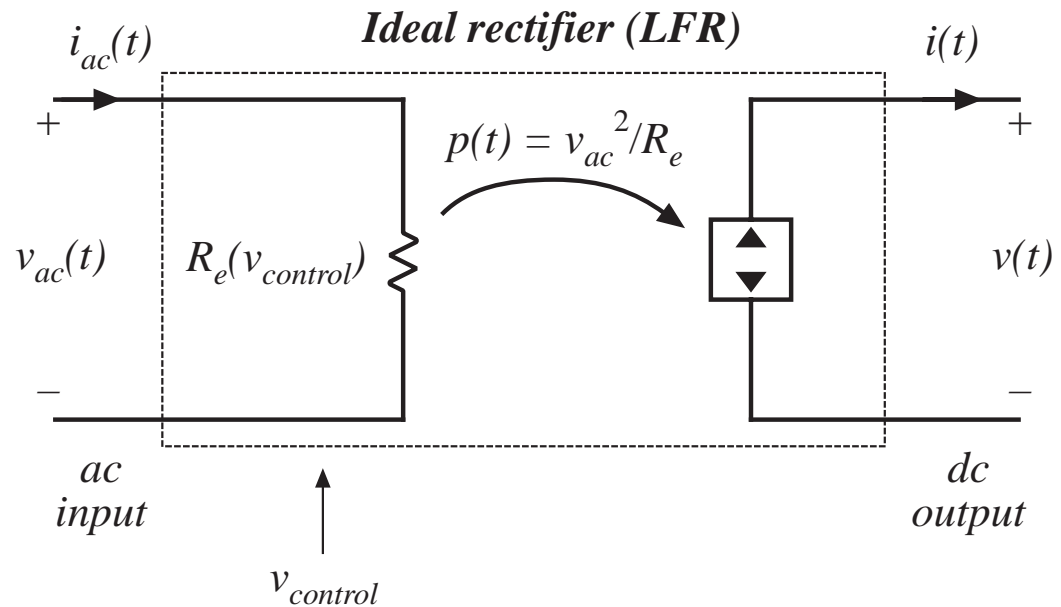
# Output port model

The ideal rectifier is lossless and contains no internal energy storage. Hence, the instantaneous input power equals the instantaneous output power. Since the instantaneous power is independent of the dc load characteristics, the output port obeys a power source characteristic.




$$p(t) = \frac{v_{ac}^2(t)}{R_e(v_{control}(t))} \quad v(t)i(t) = p(t) = \frac{v_{ac}^2(t)}{R_e}$$


# The dependent power source

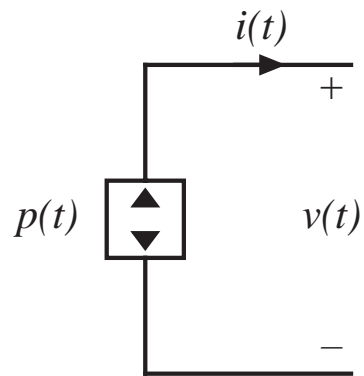

power  
source

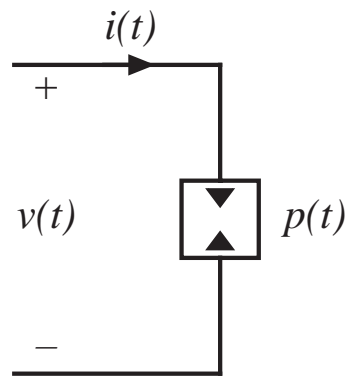

power  
sink

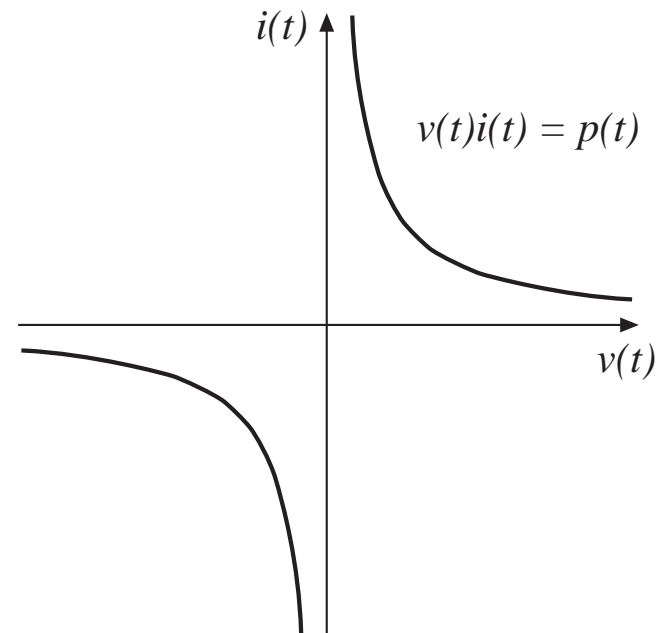

$i$ - $v$  characteristic

# Equations of the ideal rectifier / LFR

---

Defining equations of the ideal rectifier:

$$i_{ac}(t) = \frac{v_{ac}(t)}{R_e(v_{control})}$$

$$v(t)i(t) = p(t)$$

$$p(t) = \frac{v_{ac}^2(t)}{R_e(v_{control}(t))}$$


When connected to a resistive load of value  $R$ , the input and output rms voltages and currents are related as follows:

$$\frac{V_{rms}}{V_{ac,rms}} = \sqrt{\frac{R}{R_e}}$$



$$\frac{I_{ac,rms}}{I_{rms}} = \sqrt{\frac{R}{R_e}}$$
 
## 17.2 Realization of a near-ideal rectifier

Control the duty cycle of a dc-dc converter, such that the input current is proportional to the input voltage:



# Waveforms

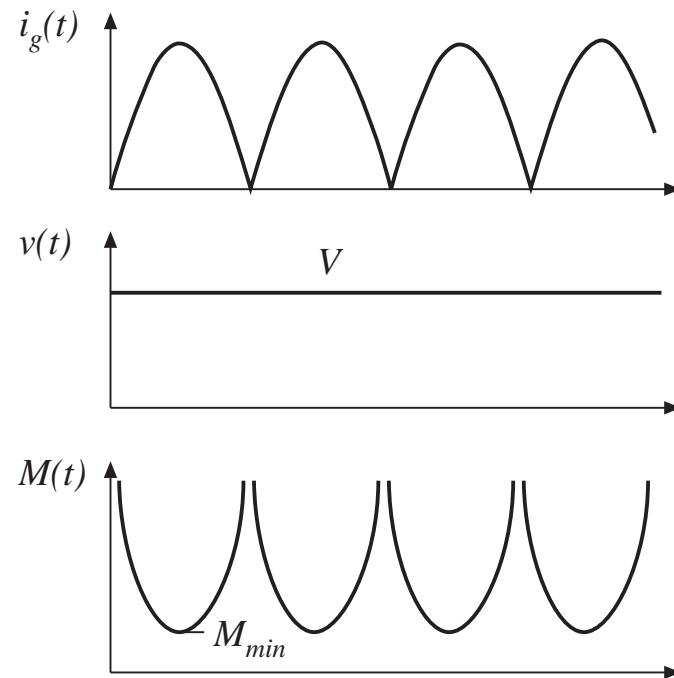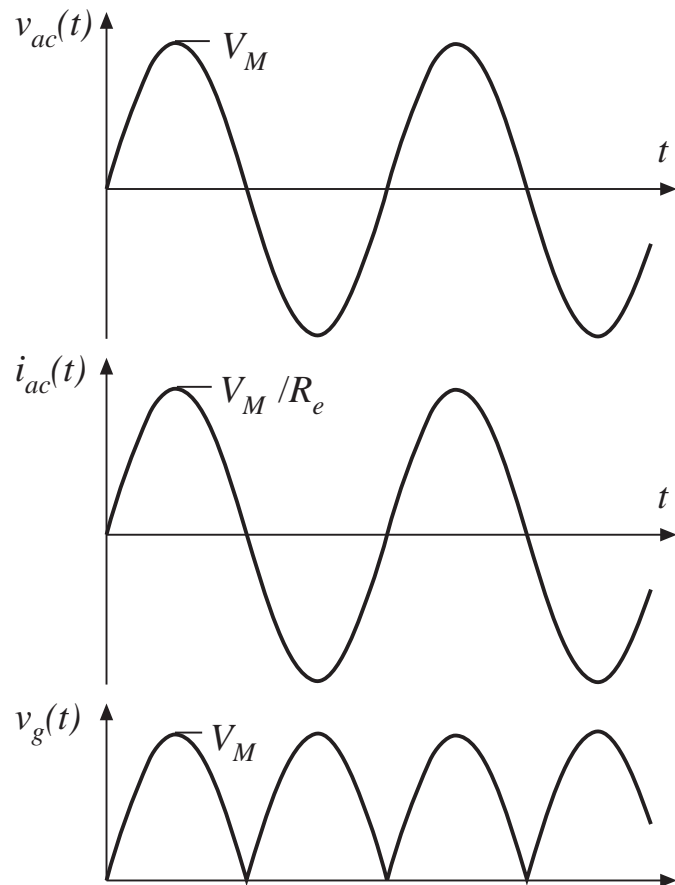

$$v_{ac}(t) = V_M \sin(\omega t)$$

$$v_g(t) = V_M |\sin(\omega t)|$$

$$M(d(t)) = \frac{v(t)}{v_g(t)} = \frac{V}{V_M |\sin(\omega t)|}$$


$$M_{min} = \frac{V}{V_M}$$



# Choice of converter

---


$$M(d(t)) = \frac{v(t)}{v_g(t)} = \frac{V}{V_M |\sin(\omega t)|}$$

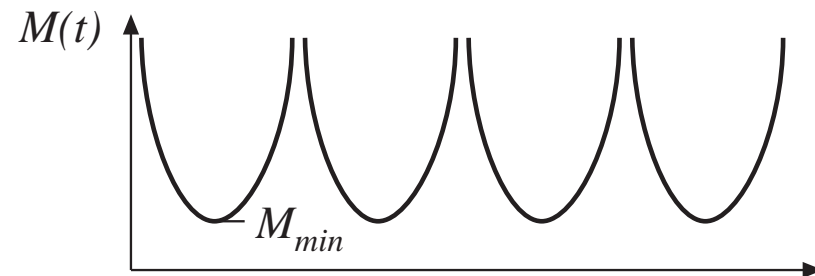

- To avoid distortion near line voltage zero crossings, converter should be capable of producing  $M(d(t))$  approaching infinity
- Above expression neglects converter dynamics
- Boost, buck-boost, Cuk, SEPIC, and other converters with similar conversion ratios are suitable
- We will see that the boost converter exhibits lowest transistor stresses. For this reason, it is most often chosen
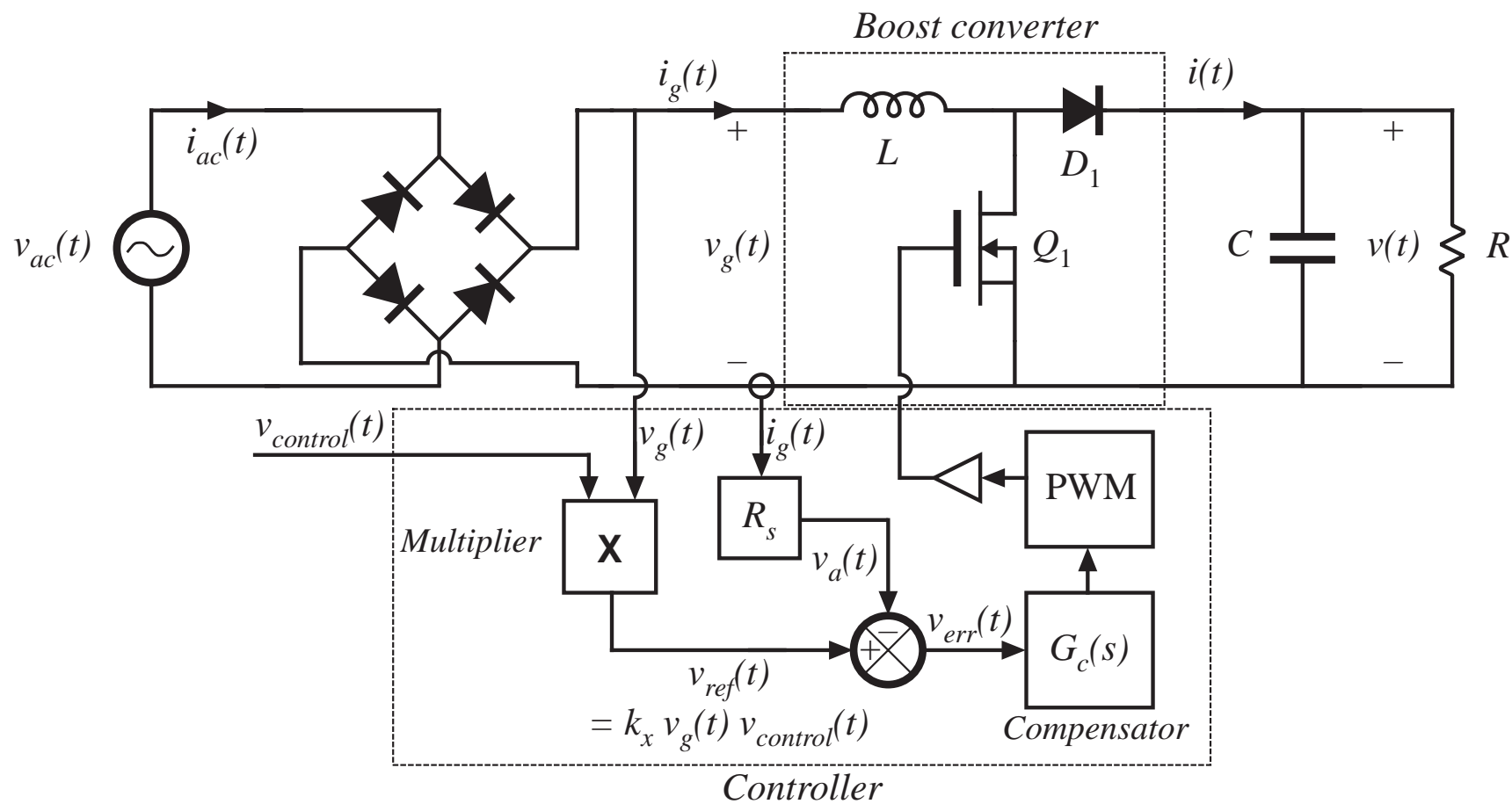
# Boost converter

with controller to cause input current to follow input voltage



# Variation of duty cycle in boost rectifier

---

$$M(d(t)) = \frac{v(t)}{v_g(t)} = \frac{V}{V_M |\sin(\omega t)|}$$

Since  $M \geq 1$  in the boost converter, it is required that  $V \geq V_M$

If the converter operates in CCM, then

$$M(d(t)) = \frac{1}{1 - d(t)}$$

The duty ratio should therefore follow

$$d(t) = 1 - \frac{v_g(t)}{V} \quad \text{in CCM}$$

## CCM/DCM boundary, boost rectifier

---

Inductor current ripple is

$$\Delta i_g(t) = \frac{v_g(t)d(t)T_s}{2L}$$

Low-frequency (average) component of inductor current waveform is

$$\langle i_g(t) \rangle_{T_s} = \frac{v_g(t)}{R_e}$$

The converter operates in CCM when

$$\langle i_g(t) \rangle_{T_s} > \Delta i_g(t) \Rightarrow d(t) < \frac{2L}{R_e T_s}$$

Substitute CCM expression for  $d(t)$ :

$$R_e < \frac{2L}{T_s \left(1 - \frac{v_g(t)}{V}\right)} \quad \text{for CCM}$$

## CCM / DCM boundary

---

$$R_e < \frac{2L}{T_s \left(1 - \frac{v_g(t)}{V}\right)} \quad \text{for CCM}$$

Note that  $v_g(t)$  varies with time, between 0 and  $V_M$ . Hence, this equation may be satisfied at some points on the ac line cycle, and not at others. The converter always operates in CCM provided that

$$R_e < \frac{2L}{T_s}$$

The converter always operates in DCM provided that

$$R_e > \frac{2L}{T_s \left(1 - \frac{V_M}{V}\right)}$$


For  $R_e$  between these limits, the converter operates in DCM when  $v_g(t)$  is near zero, and in CCM when  $v_g(t)$  approaches  $V_M$ .

# Static input characteristics of the boost converter

A plot of input current  $i_g(t)$  vs input voltage  $v_g(t)$ , for various duty cycles  $d(t)$ . In CCM, the boost converter equilibrium equation is

$$\frac{v_g(t)}{V} = 1 - d(t)$$

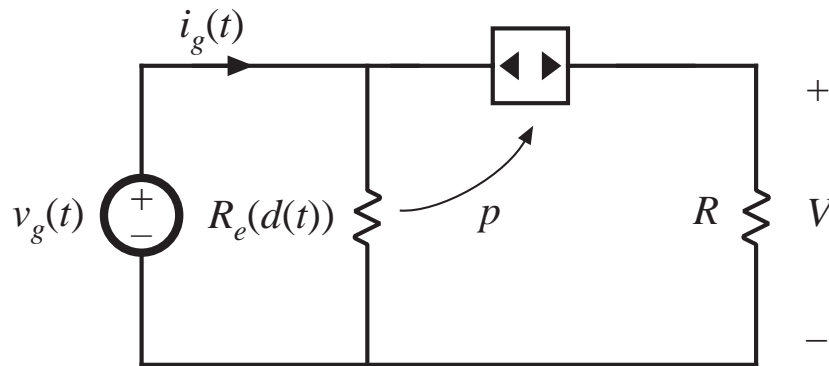The input characteristic in DCM is found by solution of the averaged DCM model (Fig. 10.12(b)):



**Beware!** This DCM  $R_e(d)$  from Chapter 10 is not the same as the rectifier emulated resistance  $R_e = v_g/i_g$

Solve for input current:

$$i_g(t) = \frac{v_g(t)}{R_e(d(t))} + \frac{p(t)}{V - v_g(t)}$$

$$\text{with } p(t) = \frac{v_g^2(t)}{R_e(d(t))}$$

$$R_e(d(t)) = \frac{2L}{d^2(t)T_s}$$

# Static input characteristics of the boost converter

---


Now simplify DCM current expression, to obtain

$$\frac{2L}{VT_s} i_g(t) \left( 1 - \frac{v_g(t)}{V} \right) = d^2(t) \frac{v_g(t)}{V}$$

CCM/DCM mode boundary, in terms of  $v_g(t)$  and  $i_g(t)$ :

$$\frac{2L}{VT_s} i_g(t) > \left( \frac{v_g(t)}{V} \right) \left( 1 - \frac{v_g(t)}{V} \right)$$
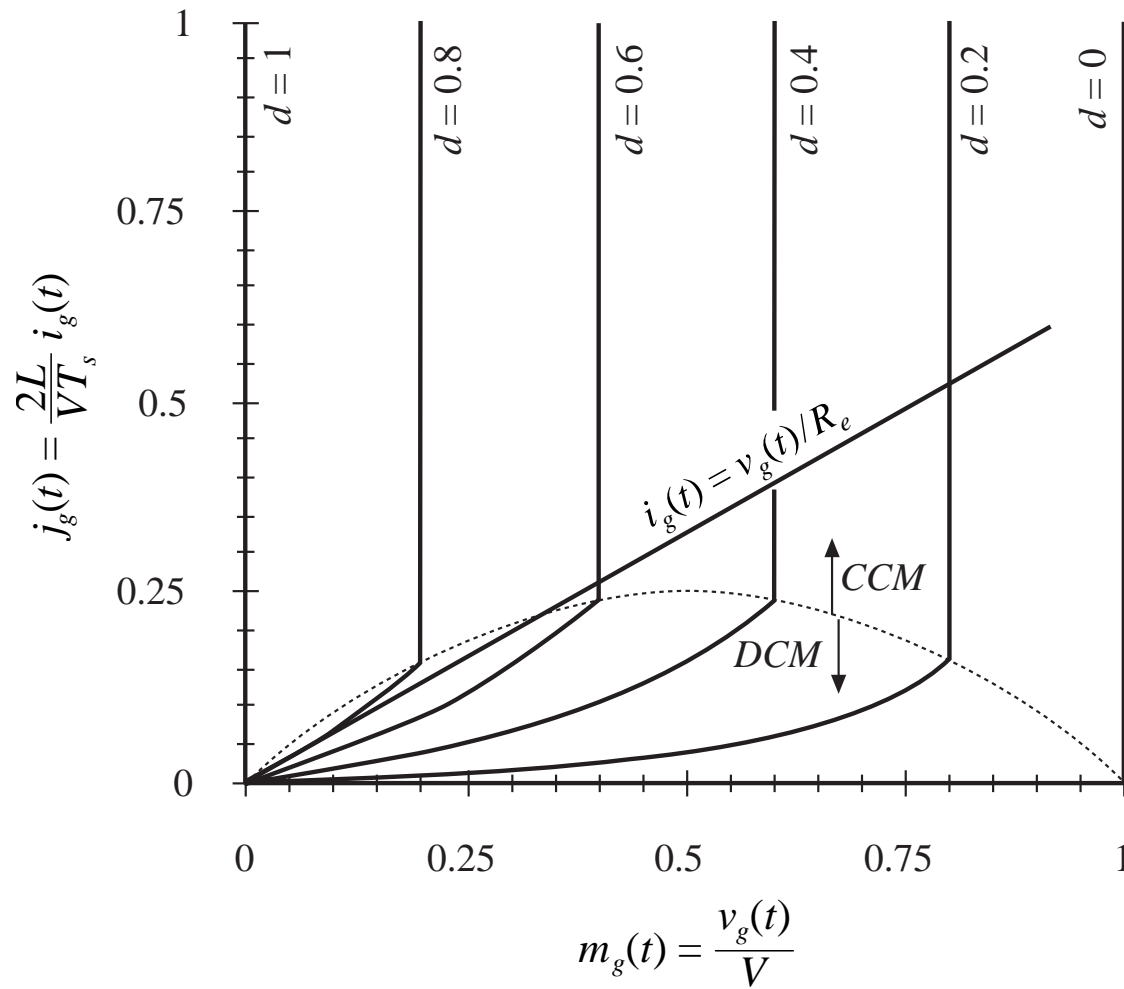
# Boost input characteristics with superimposed resistive characteristic



CCM:

$$\frac{v_g(t)}{V} = 1 - d(t)$$

DCM:

$$\frac{2L}{VT_s} i_g(t) \left( 1 - \frac{v_g(t)}{V} \right) = d^2(t) \frac{v_g(t)}{V}$$


CCM when

$$\frac{2L}{VT_s} i_g(t) > \left( \frac{v_g(t)}{V} \right) \left( 1 - \frac{v_g(t)}{V} \right)$$



# $R_e$ of the multiplying (average current) controller

Solve circuit to find  $R_e$ :

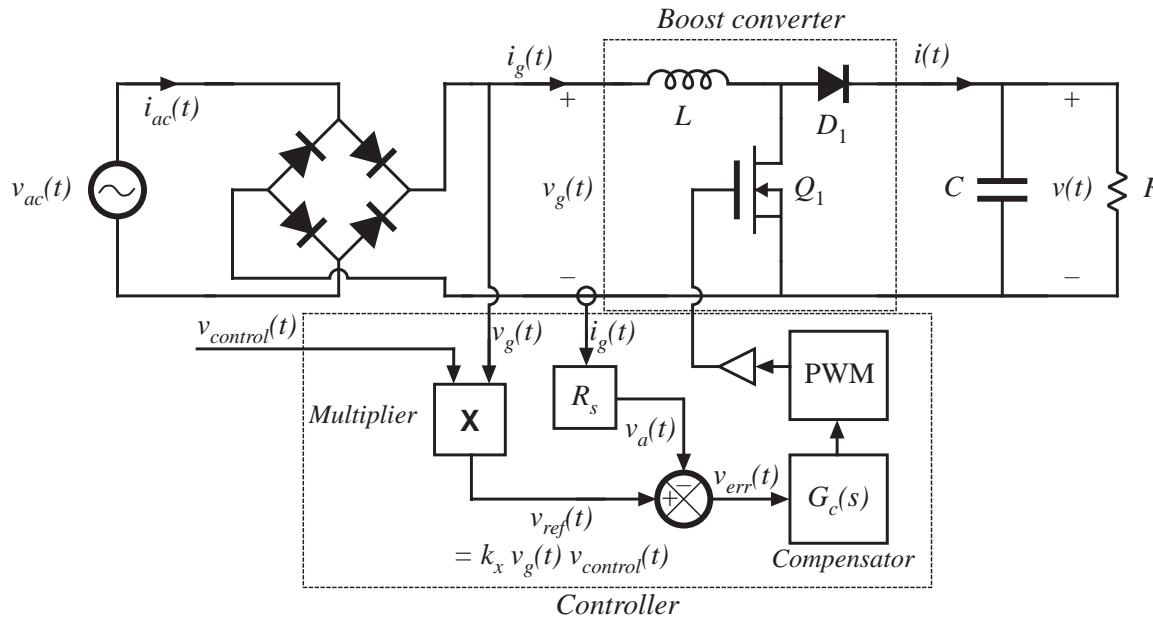

Current sensor gain

$$v_a(t) = i_g(t)R_s$$

when the error signal is small,

$$v_a(t) \approx v_{ref}(t)$$

multiplier equation

$$v_{ref}(t) = k_x v_g(t) v_{control}(t)$$


then  $R_e$  is

$$R_e = \frac{v_g(t)}{i_g(t)} = \frac{\left( \frac{v_{ref}(t)}{k_x v_{control}(t)} \right)}{\left( \frac{v_a(t)}{R_s} \right)}$$

simplify:

$$R_e(v_{control}(t)) = \frac{R_s}{k_x v_{control}(t)}$$

# Low frequency system model

 

$$R_e(v_{control}(t)) = \frac{R_s}{k_x v_{control}(t)}$$

This model also applies to other converters that are controlled in the same manner, including buck-boost, Cuk, and SEPIC.

# Open-loop DCM approach

---

We found in Chapter 10 that the buck-boost, SEPIC, and Cuk converters, when operated open-loop in DCM, inherently behave as loss-free resistors. This suggests that they could also be used as near-ideal rectifiers, without need for a multiplying controller.

Advantage: simple control

Disadvantages: higher peak currents, larger input current EMI

Like other DCM applications, this approach is usually restricted to low power (< 200W).

The boost converter can also be operated in DCM as a low harmonic rectifier. Input characteristic is

$$\langle i_g(t) \rangle_{T_s} = \frac{v_g(t)}{R_e} + \frac{v_g^2(t)}{R_e (v(t) - v_g(t))}$$

Input current contains harmonics. If  $v$  is sufficiently greater than  $v_g$ , then harmonics are small.

## 17.3 Single-phase converter systems containing ideal rectifiers

---

- It is usually desired that the output voltage  $v(t)$  be regulated with high accuracy, using a wide-bandwidth feedback loop
- For a given constant load characteristic, the instantaneous load current and power are then also constant:

$$p_{load}(t) = v(t)i(t) = VI$$

- The instantaneous input power of a single-phase ideal rectifier is not constant:

$$p_{ac}(t) = v_g(t)i_g(t)$$

with

$$v_g(t) = V_M \left| \sin(\omega t) \right| \qquad i_g(t) = \frac{v_g(t)}{R_e}$$

so

$$p_{ac}(t) = \frac{V_M^2}{R_e} \sin^2(\omega t) = \frac{V_M^2}{2R_e} \left( 1 - \cos(2\omega t) \right)$$

## Power flow in single-phase ideal rectifier system


---

- Ideal rectifier is lossless, and contains no internal energy storage.
- Hence instantaneous input and output powers must be equal
- An energy storage element must be added
- Capacitor energy storage: instantaneous power flowing into capacitor is equal to difference between input and output powers:

$$p_C(t) = \frac{dE_C(t)}{dt} = \frac{d\left(\frac{1}{2} C v_C^2(t)\right)}{dt} = p_{ac}(t) - p_{load}(t)$$


Energy storage capacitor voltage must be allowed to vary, in accordance with this equation

# Capacitor energy storage in 1ø system

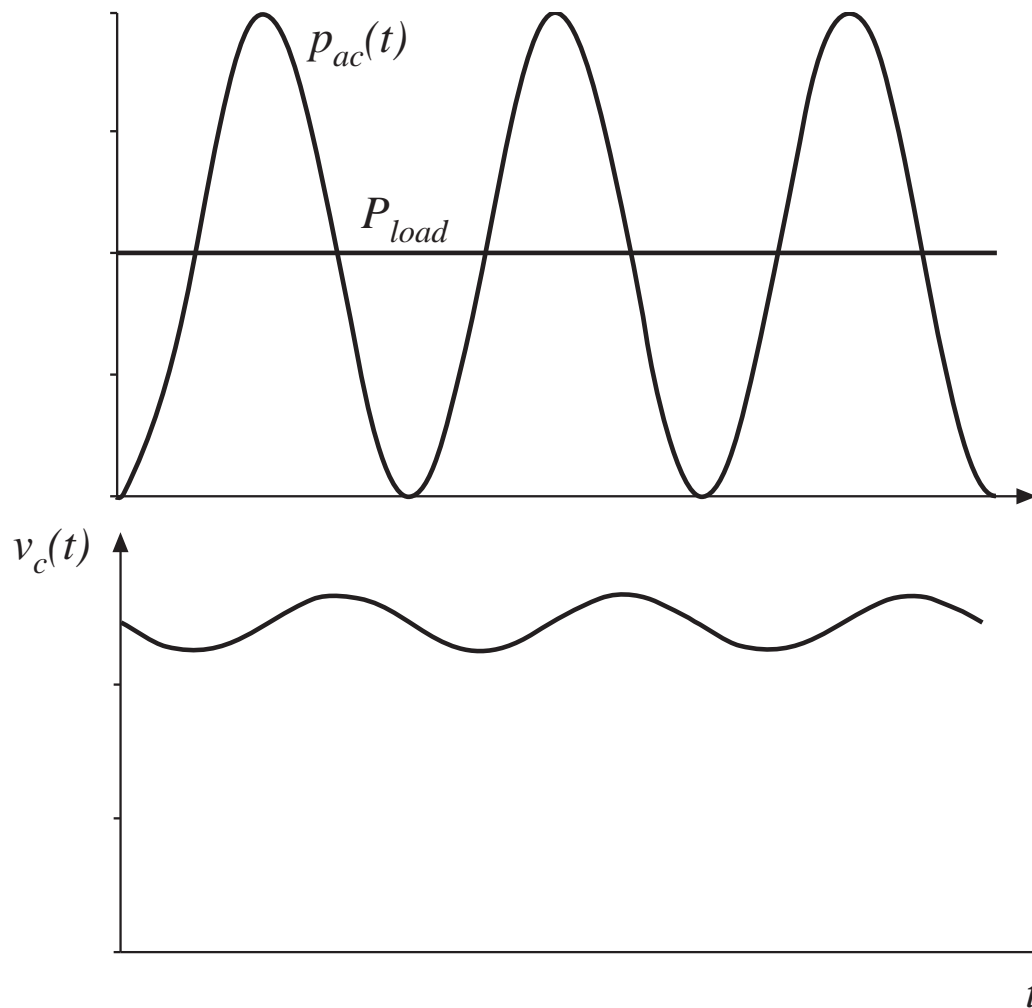

$$\frac{d\left(\frac{1}{2} C v_c^2(t)\right)}{dt} = p_{ac}(t) - p_{load}(t)$$
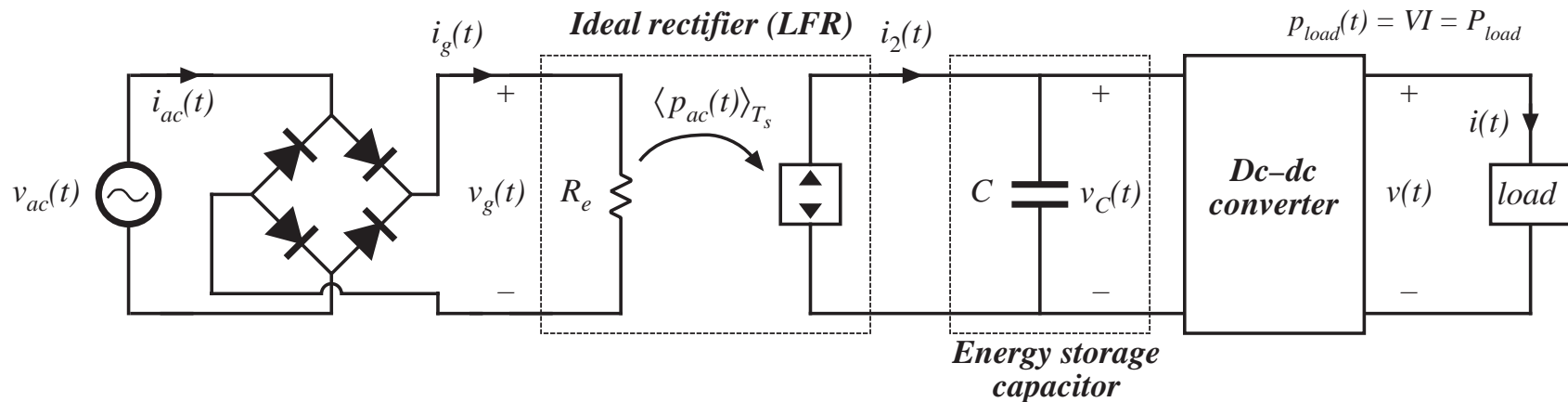
# Single-phase system with internal energy storage



Energy storage capacitor voltage  $v_C(t)$  must be independent of input and output voltage waveforms, so that it can vary according to

$$\frac{d\left(\frac{1}{2} C v_C^2(t)\right)}{dt} = p_{ac}(t) - p_{load}(t)$$

This system is capable of

- Wide-bandwidth control of output voltage
- Wide-bandwidth control of input current waveform
- Internal independent energy storage

# Hold up time

---

Internal energy storage allows the system to function in other situations where the instantaneous input and output powers differ.

*A common example:* continue to supply load power in spite of failure of ac line for short periods of time.

*Hold up time:* the duration which the dc output voltage  $v(t)$  remains regulated after  $v_{ac}(t)$  has become zero

A typical hold-up time requirement: supply load for one complete missing ac line cycle, or 20msec in a 50Hz system

During the hold-up time, the load power is supplied entirely by the energy storage capacitor



# Energy storage element

---

Instead of a capacitor, an inductor or higher-order LC network could store the necessary energy.

*But*, inductors are not good energy-storage elements

## Example

100V 100 $\mu$ F capacitor

100A 100 $\mu$ H inductor

each store 1 Joule of energy

But the capacitor is considerably smaller, lighter, and less expensive

So a single big capacitor is the best solution

# Inrush current

---

A problem caused by the large energy storage capacitor: the large inrush current observed during system startup, necessary to charge the capacitor to its equilibrium value.

Boost converter is not capable of controlling this inrush current.

Even with  $d = 0$ , a large current flows through the boost converter diode to the capacitor, as long as  $v(t) < v_g(t)$ .

Additional circuitry is needed to limit the magnitude of this inrush current.

Converters having buck-boost characteristics are capable of controlling the inrush current. Unfortunately, these converters exhibit higher transistor stresses.

# Universal input

---

The capability to operate from the ac line voltages and frequencies found everywhere in the world:

50Hz and 60Hz

Nominal rms line voltages of 100V to 260V:

100V, 110V, 115V, 120V, 132V, 200V, 220V, 230V, 240V, 260V

Regardless of the input voltage and frequency, the near-ideal rectifier produces a constant nominal dc output voltage. With a boost converter, this voltage is 380 or 400V.

# Low-frequency model of dc-dc converter


Dc-dc converter produces well-regulated dc load voltage  $V$ .

Load therefore draws constant current  $I$ .

Load power is therefore the constant value  $P_{load} = VI$ .


To the extent that dc-dc converter losses can be neglected, then dc-dc converter input power is  $P_{load}$ , regardless of capacitor voltage  $v_c(t)$ .

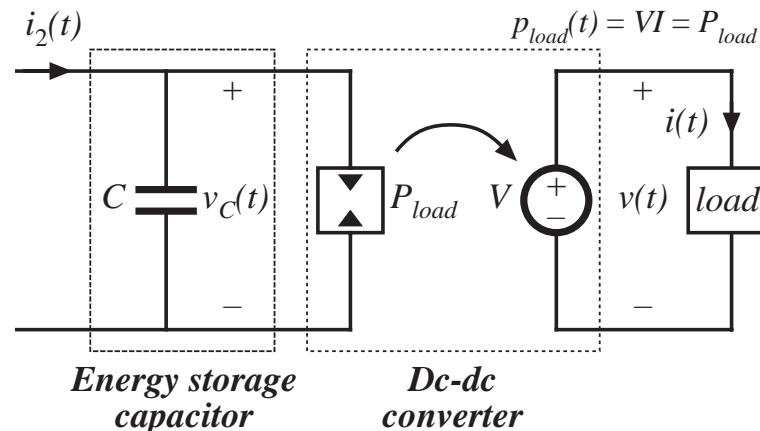Dc-dc converter input port behaves as a power sink. A low frequency converter model is




# Low-frequency energy storage process, 1 $\phi$ system

A complete low-frequency system model:

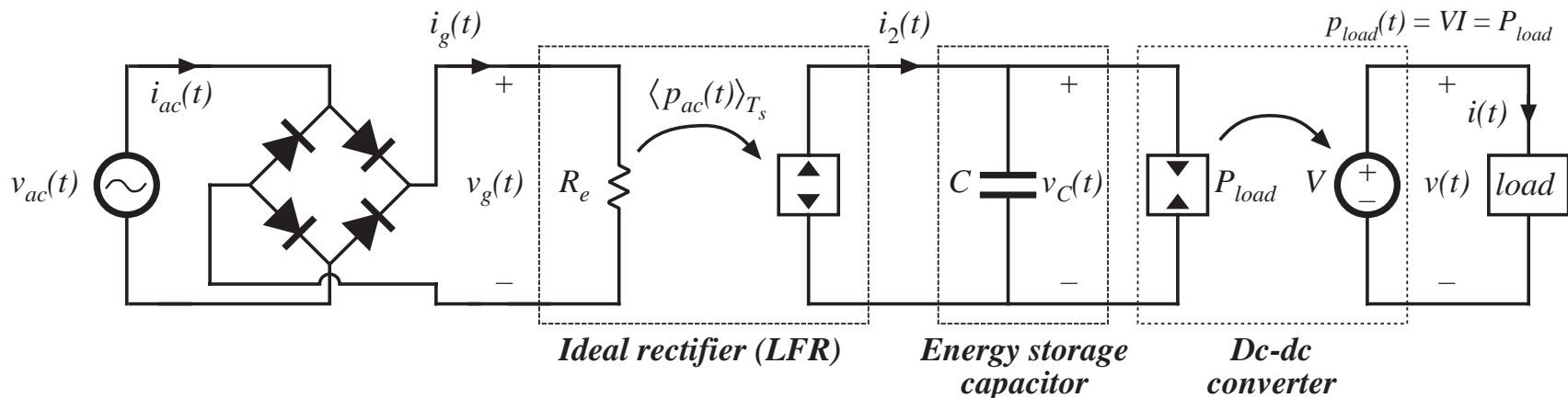

- Difference between rectifier output power and dc-dc converter input power flows into capacitor
- In equilibrium, average rectifier and load powers must be equal
- But the system contains no mechanism to accomplish this
- An additional feedback loop is necessary, to adjust  $R_e$  such that the rectifier average power is equal to the load power

# Obtaining average power balance

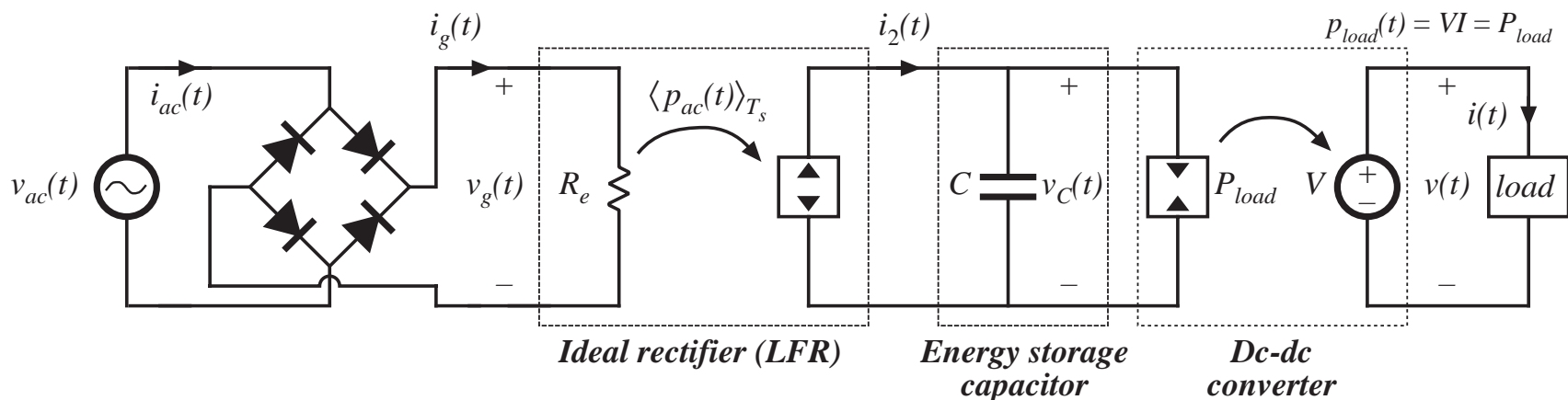


If the load power exceeds the average rectifier power, then there is a net discharge in capacitor energy and voltage over one ac line cycle.

There is a net increase in capacitor charge when the reverse is true.

This suggests that rectifier and load powers can be balanced by regulating the energy storage capacitor voltage.
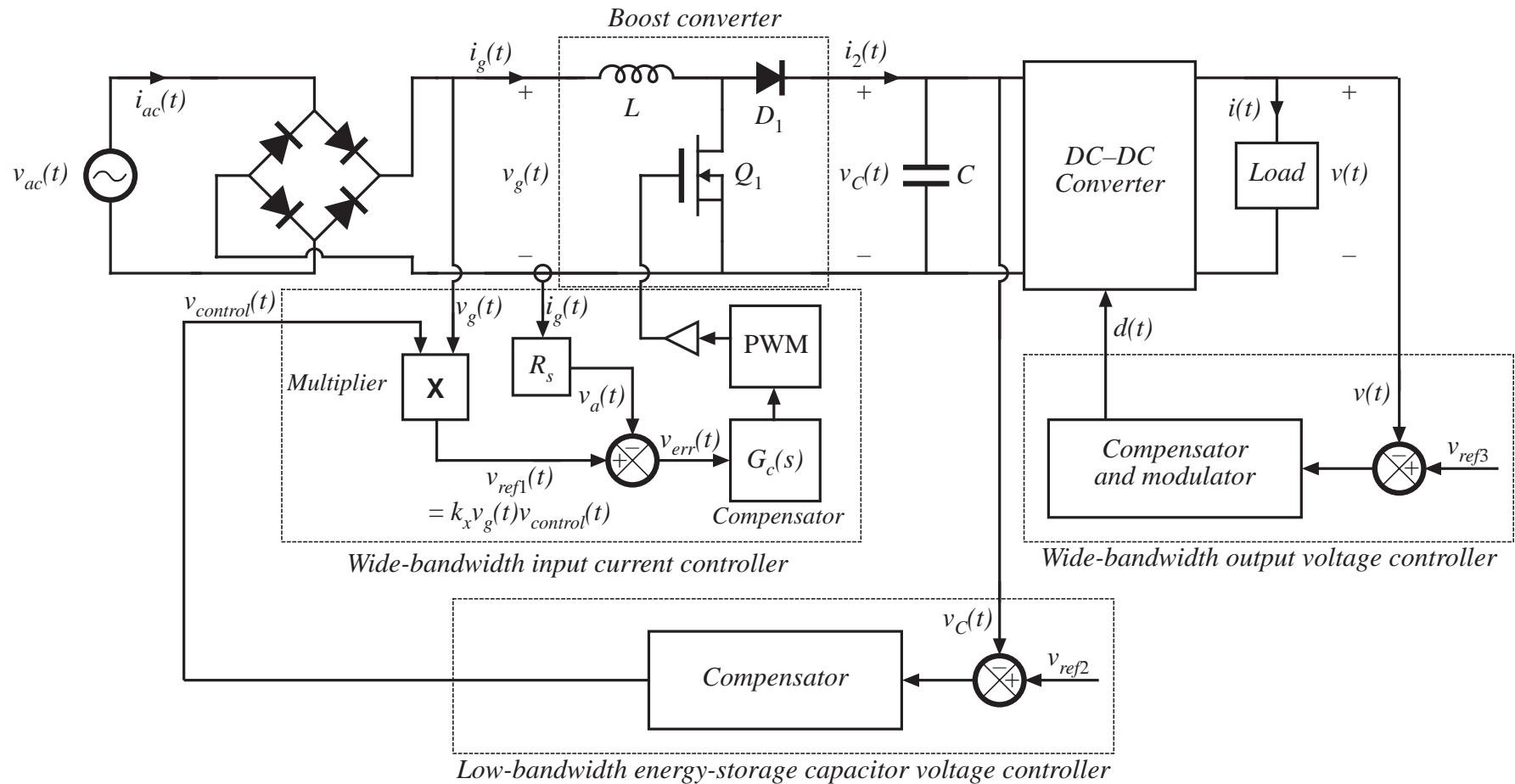
# A complete 1 $\phi$ system containing three feedback loops



# Bandwidth of capacitor voltage loop

---

- The energy-storage-capacitor voltage feedback loop causes the dc component of  $v_c(t)$  to be equal to some reference value
- Average rectifier power is controlled by variation of  $R_e$ .
- $R_e$  must not vary too quickly; otherwise, ac line current harmonics are generated
- Extreme limit: loop has infinite bandwidth, and  $v_c(t)$  is perfectly regulated to be equal to a constant reference value
  - Energy storage capacitor voltage then does not change, and this capacitor does not store or release energy
  - Instantaneous load and ac line powers are then equal
  - Input current becomes

$$i_{ac}(t) = \frac{p_{ac}(t)}{v_{ac}(t)} = \frac{p_{load}(t)}{v_{ac}(t)} = \frac{P_{load}}{V_M \sin(\omega t)}$$




# Input current waveform, extreme limit

$$i_{ac}(t) = \frac{p_{ac}(t)}{v_{ac}(t)} = \frac{p_{load}(t)}{v_{ac}(t)} = \frac{P_{load}}{V_M \sin(\omega t)}$$

THD  $\rightarrow \infty$

Power factor  $\rightarrow 0$

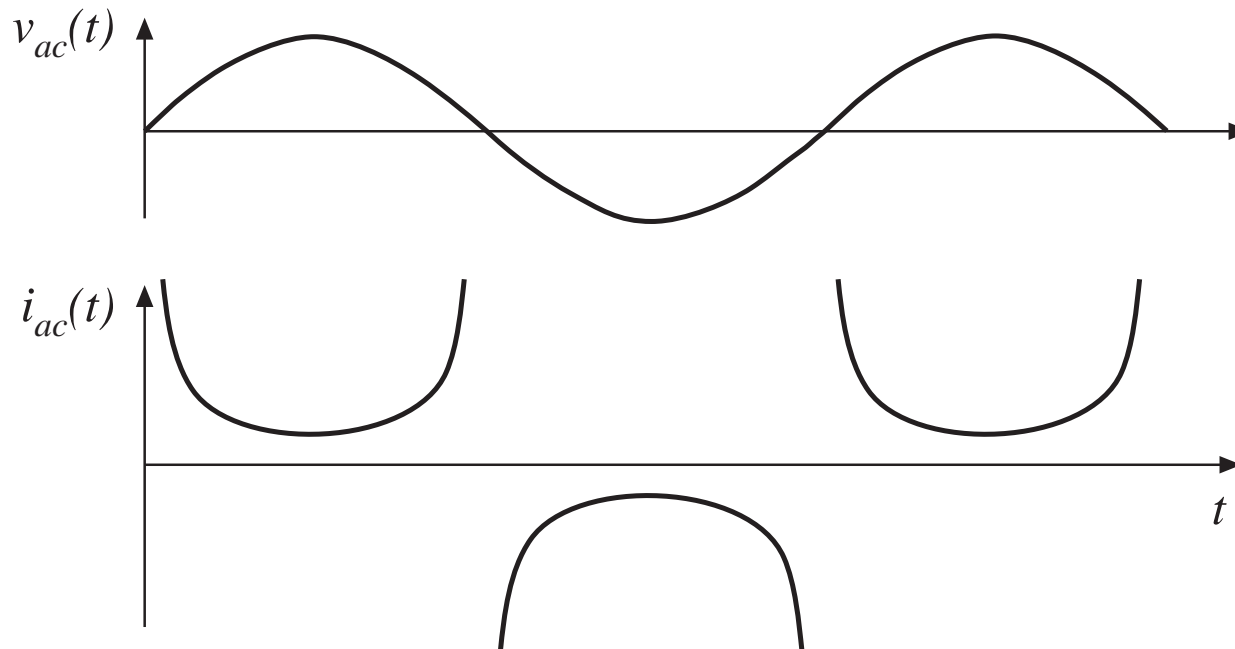


So bandwidth of capacitor voltage loop must be limited, and THD increases rapidly with increasing bandwidth
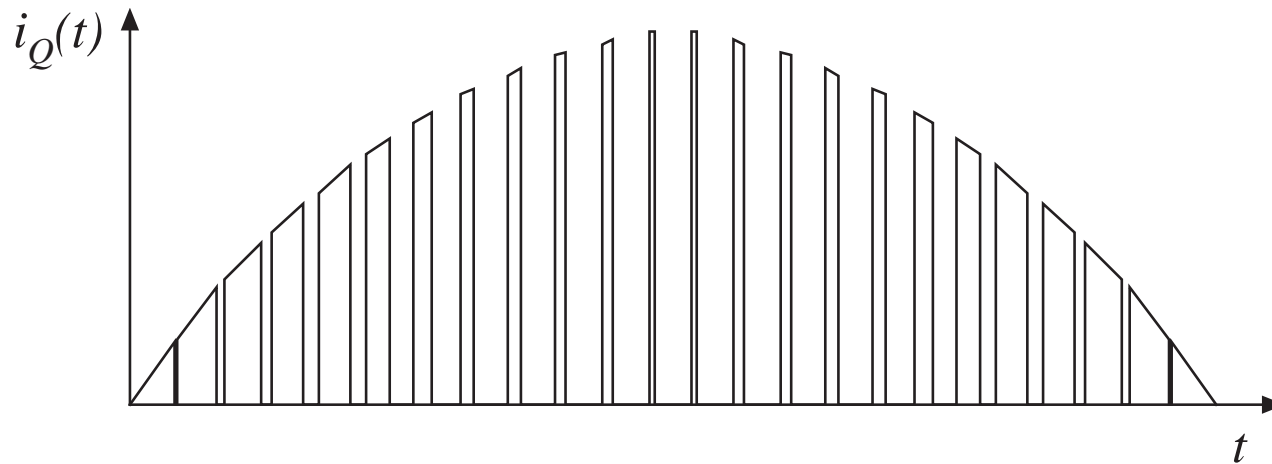
## 17.4 RMS values of rectifier waveforms

---

Doubly-modulated transistor current waveform, boost rectifier:



Computation of rms value of this waveform is complex and tedious

Approximate here using double integral

Generate tables of component rms and average currents for various rectifier converter topologies, and compare

# RMS transistor current


RMS transistor current is

$$I_{Qrms} = \sqrt{\frac{1}{T_{ac}} \int_0^{T_{ac}} i_Q^2(t) dt}$$

Express as sum of integrals over all switching periods contained in one ac line period:

$$I_{Qrms} = \sqrt{\frac{1}{T_{ac}} T_s \sum_{n=1}^{T_{ac}/T_s} \left( \frac{1}{T_s} \int_{(n-1)T_s}^{nT_s} i_Q^2(t) dt \right)}$$

 Quantity in parentheses is the value of  $i_Q^2$ , averaged over the  $n^{\text{th}}$  switching period.



# Approximation of RMS expression

$$I_{Qrms} = \sqrt{\frac{1}{T_{ac}} T_s \sum_{n=1}^{T_{ac}/T_s} \left( \frac{1}{T_s} \int_{(n-1)T_s}^{nT_s} i_Q^2(t) dt \right)}$$

When  $T_s \ll T_{ac}$ , then the summation can be approximated by an integral, which leads to the double-average:

$$\begin{aligned} I_{Qrms} &\approx \sqrt{\frac{1}{T_{ac}} \lim_{T_s \rightarrow 0} \left[ T_s \sum_{n=1}^{T_{ac}/T_s} \left( \frac{1}{T_s} \int_{(n-1)T_s}^{nT_s} i_Q^2(\tau) d\tau \right) \right]} \\ &= \sqrt{\frac{1}{T_{ac}} \int_0^{T_{ac}} \frac{1}{T_s} \int_t^{t+T_s} i_Q^2(\tau) d\tau dt} \\ &= \sqrt{\left\langle \left\langle i_Q^2(t) \right\rangle_{T_s} \right\rangle_{T_{ac}}} \end{aligned}$$

## 17.4.1 Boost rectifier example

---

For the boost converter, the transistor current  $i_Q(t)$  is equal to the input current when the transistor conducts, and is zero when the transistor is off. The average over one switching period of  $i_Q^2(t)$  is therefore

$$\begin{aligned}\langle i_Q^2 \rangle_{T_s} &= \frac{1}{T_s} \int_t^{t+T_s} i_Q^2(t) dt \\ &= d(t) i_{ac}^2(t)\end{aligned}$$

If the input voltage is

$$v_{ac}(t) = V_M |\sin \omega t|$$

then the input current will be given by

$$i_{ac}(t) = \frac{V_M}{R_e} |\sin \omega t|$$

and the duty cycle will ideally be

$$\frac{V}{v_{ac}(t)} = \frac{1}{1 - d(t)}$$

(this neglects  
converter dynamics)

# Boost rectifier example

---

Duty cycle is therefore

$$d(t) = 1 - \frac{V_M}{V} |\sin \omega t|$$

Evaluate the first integral:

$$\langle i_Q^2 \rangle_{T_s} = \frac{V_M^2}{R_e^2} \left( 1 - \frac{V_M}{V} |\sin \omega t| \right) \sin^2(\omega t)$$

Now plug this into the RMS formula:

$$\begin{aligned} I_{Qrms} &= \sqrt{\frac{1}{T_{ac}} \int_0^{T_{ac}} \langle i_Q^2 \rangle_{T_s} dt} \\ &= \sqrt{\frac{1}{T_{ac}} \int_0^{T_{ac}} \frac{V_M^2}{R_e^2} \left( 1 - \frac{V_M}{V} |\sin \omega t| \right) \sin^2(\omega t) dt} \\ I_{Qrms} &= \sqrt{\frac{2}{T_{ac}} \frac{V_M^2}{R_e^2} \int_0^{T_{ac}/2} \left( \sin^2(\omega t) - \frac{V_M}{V} \sin^3(\omega t) \right) dt} \end{aligned}$$

## Integration of powers of $\sin \theta$ over complete half-cycle

$$\frac{1}{\pi} \int_0^\pi \sin^n(\theta) d\theta = \begin{cases} \frac{2}{\pi} \frac{2 \cdot 4 \cdot 6 \cdots (n-1)}{1 \cdot 3 \cdot 5 \cdots n} & \text{if } n \text{ is odd} \\ \frac{1 \cdot 3 \cdot 5 \cdots (n-1)}{2 \cdot 4 \cdot 6 \cdots n} & \text{if } n \text{ is even} \end{cases}$$

$n$	$\frac{1}{\pi} \int_0^\pi \sin^n(\theta) d\theta$
1	$\frac{2}{\pi}$
2	$\frac{1}{2}$
3	$\frac{4}{3\pi}$
4	$\frac{3}{8}$
5	$\frac{16}{15\pi}$
6	$\frac{15}{48}$

## Boost example: Transistor RMS current

---

$$I_{Qrms} = \frac{V_M}{\sqrt{2}R_e} \sqrt{1 - \frac{8}{3\pi} \frac{V_M}{V}} = I_{ac\ rms} \sqrt{1 - \frac{8}{3\pi} \frac{V_M}{V}}$$

Transistor RMS current is minimized by choosing  $V$  as small as possible:  $V = V_M$ . This leads to

$$I_{Qrms} = 0.39I_{ac\ rms}$$

When the dc output voltage is not too much greater than the peak ac input voltage, the boost rectifier exhibits very low transistor current. Efficiency of the boost rectifier is then quite high, and 95% is typical in a 1kW application.



# Table of rectifier current stresses for various topologies

**Table 17.2** Summary of rectifier current stresses for several converter topologies

	<i>rms</i>	<i>Average</i>	<i>Peak</i>
CCM boost			
Transistor	$I_{ac\ rms} \sqrt{1 - \frac{8}{3\pi} \frac{V_M}{V}}$	$I_{ac\ rms} \frac{2\sqrt{2}}{\pi} \left(1 - \frac{\pi}{8} \frac{V_M}{V}\right)$	$I_{ac\ rms} \sqrt{2}$
Diode	$I_{dc} \sqrt{\frac{16}{3\pi} \frac{V}{V_M}}$	$I_{dc}$	$2 I_{dc} \frac{V}{V_M}$
Inductor	$I_{ac\ rms}$	$I_{ac\ rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac\ rms} \sqrt{2}$
CCM flyback, with $n$ :1 isolation transformer and input filter			
Transistor, xfmr primary	$I_{ac\ rms} \sqrt{1 + \frac{8}{3\pi} \frac{V_M}{nV}}$	$I_{ac\ rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac\ rms} \sqrt{2} \left(1 + \frac{V}{n}\right)$
$L_1$	$I_{ac\ rms}$	$I_{ac\ rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac\ rms} \sqrt{2}$
$C_1$	$I_{ac\ rms} \sqrt{\frac{8}{3\pi} \frac{V_M}{nV}}$	0	$I_{ac\ rms} \sqrt{2} \max\left(1, \frac{V_M}{nV}\right)$
Diode, xfmr secondary	$I_{dc} \sqrt{\frac{3}{2} + \frac{16}{3\pi} \frac{nV}{V_M}}$	$I_{dc}$	$2I_{dc} \left(1 + \frac{nV}{V_M}\right)$

# Table of rectifier current stresses

## continued

CCM SEPIC, nonisolated

Transistor	$I_{ac\ rms} \sqrt{1 + \frac{8}{3\pi} \frac{V_M}{V}}$	$I_{ac\ rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac\ rms} \sqrt{2} \left(1 + \frac{V_l}{V}\right)$
$L_1$	$I_{ac\ rms}$	$I_{ac\ rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac\ rms} \sqrt{2}$
$C_1$	$I_{ac\ rms} \sqrt{\frac{8}{3\pi} \frac{V_M}{V}}$	0	$I_{ac\ rms} \max \left(1, \frac{V_l}{V}\right)$
$L_2$	$I_{ac\ rms} \frac{V_M}{V} \frac{\sqrt{3}}{2}$	$\frac{I_{ac\ rms}}{\sqrt{2}} \frac{V_M}{V}$	$I_{ac\ rms} \frac{V_M}{V} \sqrt{2}$
Diode	$I_{dc} \sqrt{\frac{3}{2} + \frac{16}{3\pi} \frac{V}{V_M}}$	$I_{dc}$	$2I_{dc} \left(1 + \frac{V}{V_M}\right)$

CCM SEPIC, with  $n:1$  isolation transformer

transistor	$I_{ac\ rms} \sqrt{1 + \frac{8}{3\pi} \frac{V_M}{nV}}$	$I_{ac\ rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac\ rms} \sqrt{2} \left(1 + \frac{V_l}{n}\right)$
$L_1$	$I_{ac\ rms}$	$I_{ac\ rms} \frac{2\sqrt{2}}{\pi}$	$I_{ac\ rms} \sqrt{2}$
$C_1$ , xfmr primary	$I_{ac\ rms} \sqrt{\frac{8}{3\pi} \frac{V_M}{nV}}$	0	$I_{ac\ rms} \sqrt{2} \max \left(1, \frac{V_l}{n}\right)$
Diode, xfmr secondary	$I_{dc} \sqrt{\frac{3}{2} + \frac{16}{3\pi} \frac{nV}{V_M}}$	$I_{dc}$	$2I_{dc} \left(1 + \frac{nV}{V_M}\right)$

with, in all cases,  $\frac{I_{ac\ rms}}{I_{dc}} = \sqrt{2} \frac{V}{V_M}$  , ac input voltage =  $V_M \sin(\omega t)$

dc output voltage =  $V$

# Comparison of rectifier topologies

---

## **Boost converter**

- Lowest transistor rms current, highest efficiency
- Isolated topologies are possible, with higher transistor stress
- No limiting of inrush current
- Output voltage must be greater than peak input voltage

## **Buck-boost, SEPIC, and Cuk converters**

- Higher transistor rms current, lower efficiency
- Isolated topologies are possible, without increased transistor stress
- Inrush current limiting is possible
- Output voltage can be greater than or less than peak input voltage

# Comparison of rectifier topologies


1kW, 240Vrms example. Output voltage: 380Vdc. Input current: 4.2Arms

Converter	Transistor rms current	Transistor voltage	Diode rms current	Transistor rms current, 120V	Diode rms current, 120V
Boost	2 A	380 V	3.6 A	6.6 A	5.1 A
Nonisolated SEPIC	5.5 A	719 V	4.85 A	9.8 A	6.1 A
Isolated SEPIC	5.5 A	719 V	36.4 A	11.4 A	42.5 A

Isolated SEPIC example has 4:1 turns ratio, with 42V 23.8A dc load

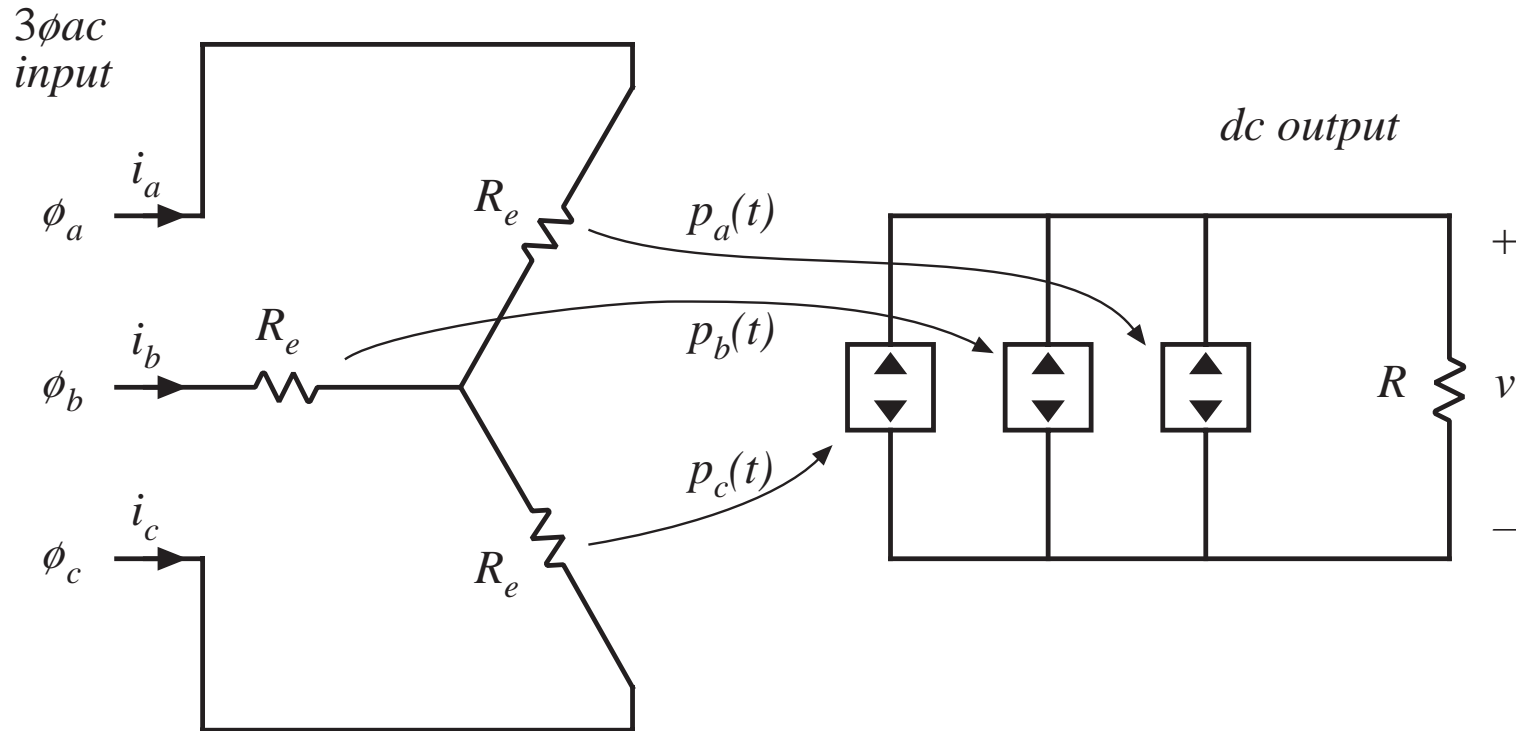
## 17.5 Ideal three-phase rectifiers

Ideal 3 $\phi$  rectifier, modeled as three 1 $\phi$  ideal rectifiers:


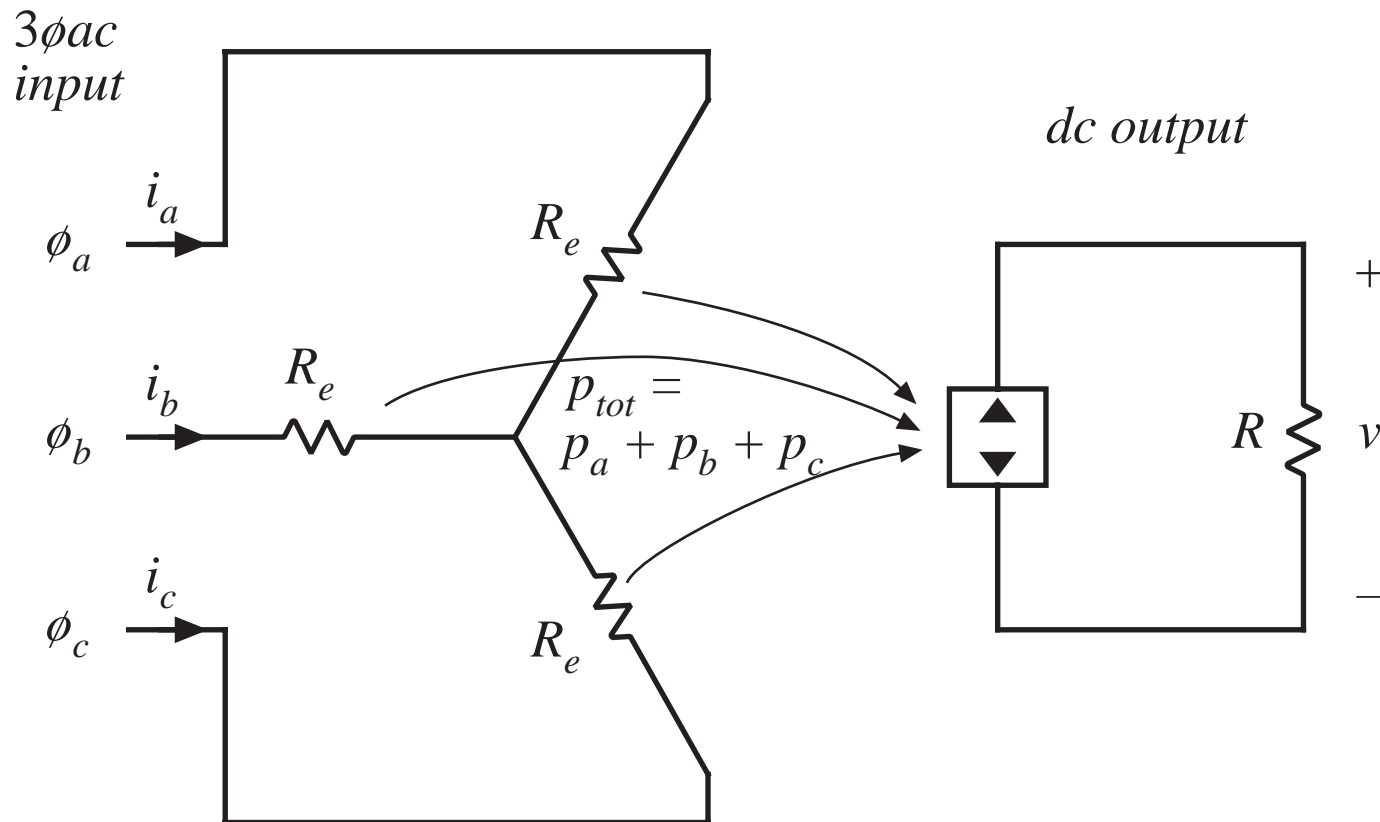
# Ideal 3 $\phi$ rectifier model

Combine parallel-connected power sources into a single source  $p_{tot}(t)$ :



## Value of $p_{tot}(t)$

Ac input voltages:

$$v_{an}(t) = V_M \sin(\omega t)$$

$$v_{bn}(t) = V_M \sin(\omega t - 120^\circ)$$


$$v_{cn}(t) = V_M \sin(\omega t - 240^\circ)$$

Instantaneous phase powers:

$$p_a(t) = \frac{v_{an}^2(t)}{R_e} = \frac{V_M^2}{2R_e} (1 - \cos(2\omega t))$$

$$p_b(t) = \frac{v_{bn}^2(t)}{R_e} = \frac{V_M^2}{2R_e} (1 - \cos(2\omega t - 240^\circ))$$
 
$$p_c(t) = \frac{v_{cn}^2(t)}{R_e} = \frac{V_M^2}{2R_e} (1 - \cos(2\omega t - 120^\circ))$$



Total 3φ instantaneous power:


$$p_{tot}(t) = p_a(t) + p_b(t) + p_c(t) = \frac{3}{2} \frac{V_M^2}{R_e}$$

- 2<sup>nd</sup> harmonic terms add to zero
- total 3φ power  $p_{tot}(t)$  is constant
 
# Instantaneous power in ideal 3 $\phi$ rectifier

$$p_{tot}(t) = p_a(t) + p_b(t) + p_c(t) = \frac{3}{2} \frac{V_M^2}{R_e}$$


- In a balanced system, the ideal 3 $\phi$  rectifier supplies constant power to its dc output
- a constant power load can be supplied, without need for low-frequency internal energy storage





## 17.5.1 Three-phase rectifiers operating in CCM

### *3 $\phi$ ac–dc boost rectifier*

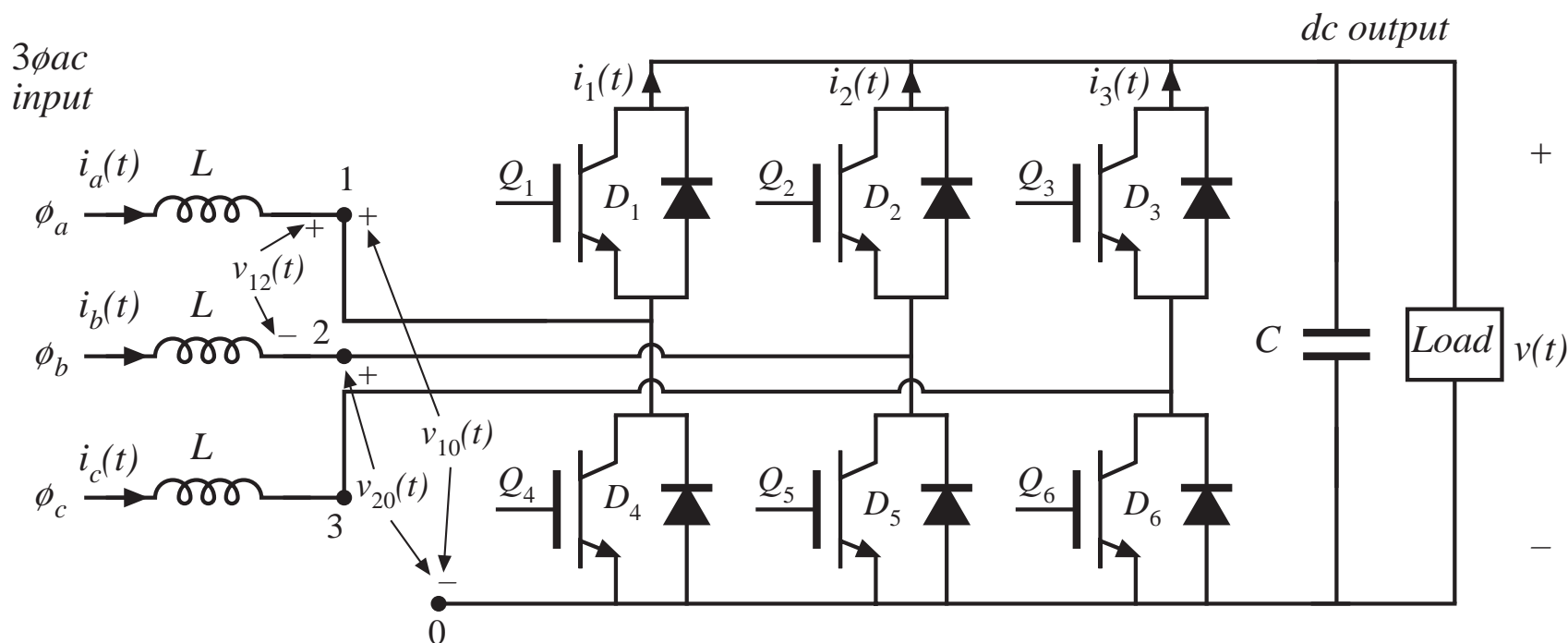

- Uses six current-bidirectional switches
- Operation of each individual phase is similar to the 1 $\phi$  boost rectifier

# The 3 $\phi$ ac–dc boost rectifier



---

- Voltage-source inverter, operated backwards as a rectifier
- Converter is capable of bidirectional power flow
- Dc output voltage  $V$  must be greater than peak ac line-line voltage  $V_{L,pk}$ .
- Ac input currents are nonpulsating. In CCM, input EMI filtering is relatively easy
- Very low RMS transistor currents and conduction loss
- The leading candidate to replace uncontrolled 3 $\phi$  rectifiers
- Requires six active devices
- Cannot regulate output voltage down to zero:
  - no current limiting
  - cannot replace traditional buck-type controlled rectifiers

# Control of switches in CCM 3øac-dc boost rectifier
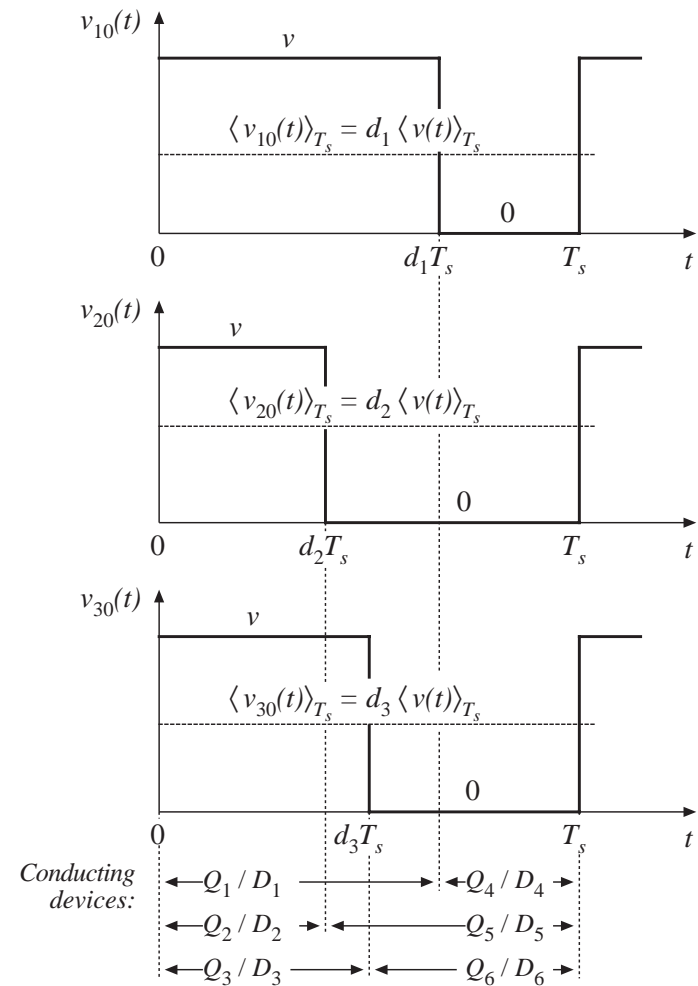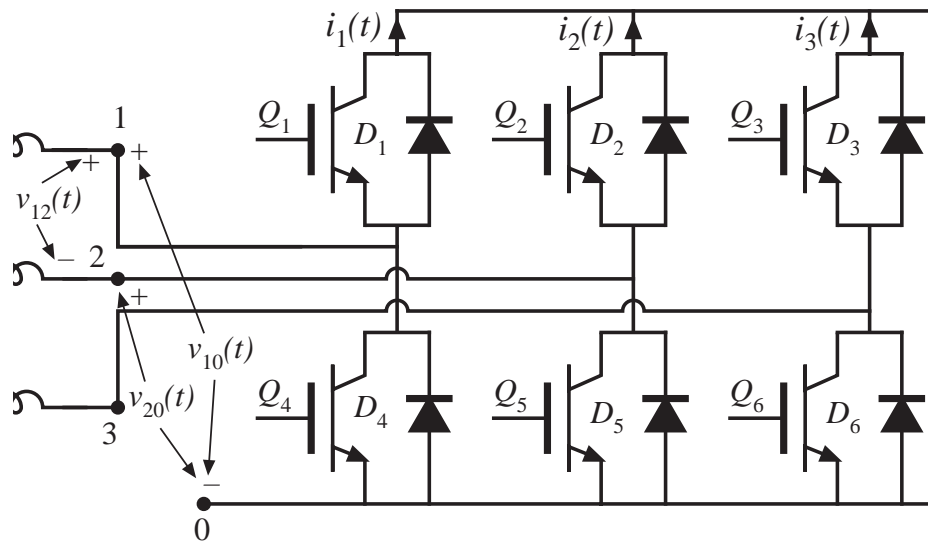
## Pulse-width modulation:

Drive lower transistors ( $Q_4 - Q_6$ ) with complements of duty cycles of respective upper transistors ( $Q_1 - Q_3$ ). Each phase operates independently, with its own duty cycle.



# Average switch waveforms

Average the switch voltages:

$$\langle v_{10}(t) \rangle_{T_s} = d_1(t) \langle v(t) \rangle_{T_s}$$

$$\langle v_{20}(t) \rangle_{T_s} = d_2(t) \langle v(t) \rangle_{T_s}$$

$$\langle v_{30}(t) \rangle_{T_s} = d_3(t) \langle v(t) \rangle_{T_s}$$

Average line-line voltages:

$$\langle v_{12}(t) \rangle_{T_s} = \langle v_{10}(t) \rangle_{T_s} - \langle v_{20}(t) \rangle_{T_s} = (d_1(t) - d_2(t)) \langle v(t) \rangle_{T_s}$$

$$\langle v_{23}(t) \rangle_{T_s} = \langle v_{20}(t) \rangle_{T_s} - \langle v_{30}(t) \rangle_{T_s} = (d_2(t) - d_3(t)) \langle v(t) \rangle_{T_s}$$


$$\langle v_{31}(t) \rangle_{T_s} = \langle v_{30}(t) \rangle_{T_s} - \langle v_{10}(t) \rangle_{T_s} = (d_3(t) - d_1(t)) \langle v(t) \rangle_{T_s}$$

Average switch output-side currents:


$$\langle i_1(t) \rangle_{T_s} = d_1(t) \langle i_a(t) \rangle_{T_s}$$

$$\langle i_2(t) \rangle_{T_s} = d_2(t) \langle i_b(t) \rangle_{T_s}$$
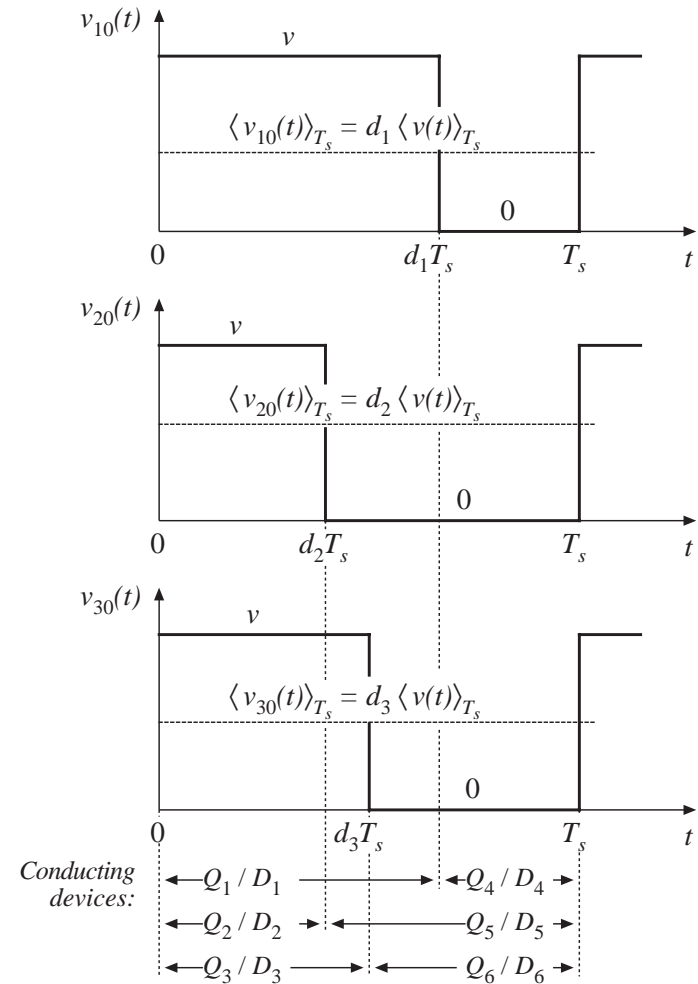
$$\langle i_3(t) \rangle_{T_s} = d_3(t) \langle i_c(t) \rangle_{T_s}$$



# Averaged circuit model

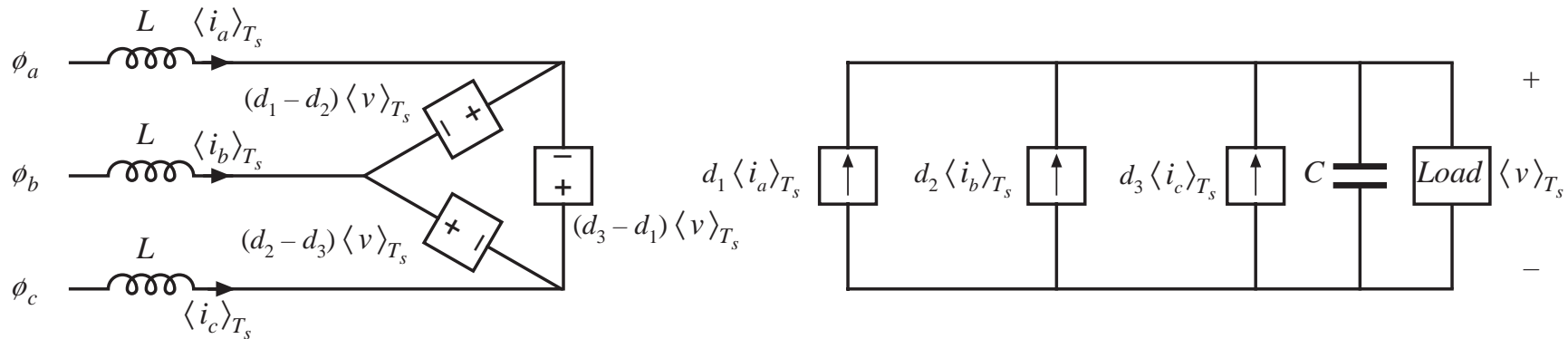

$$\begin{aligned}\langle v_{12}(t) \rangle_{T_s} &= \langle v_{10}(t) \rangle_{T_s} - \langle v_{20}(t) \rangle_{T_s} = (d_1(t) - d_2(t)) \langle v(t) \rangle_{T_s} \\ \langle v_{23}(t) \rangle_{T_s} &= \langle v_{20}(t) \rangle_{T_s} - \langle v_{30}(t) \rangle_{T_s} = (d_2(t) - d_3(t)) \langle v(t) \rangle_{T_s} \\ \langle v_{31}(t) \rangle_{T_s} &= \langle v_{30}(t) \rangle_{T_s} - \langle v_{10}(t) \rangle_{T_s} = (d_3(t) - d_1(t)) \langle v(t) \rangle_{T_s}\end{aligned}$$

$$\begin{aligned}\langle i_1(t) \rangle_{T_s} &= d_1(t) \langle i_a(t) \rangle_{T_s} \\ \langle i_2(t) \rangle_{T_s} &= d_2(t) \langle i_b(t) \rangle_{T_s} \\ \langle i_3(t) \rangle_{T_s} &= d_3(t) \langle i_c(t) \rangle_{T_s}\end{aligned}$$

**Q:** How to vary  $d(t)$  such that the desired ac and dc waveforms are obtained?

Solution is not unique.

# Sinusoidal PWM

---

A simple modulation scheme: Sinusoidal PWM

Vary duty cycles sinusoidally, in synchronism with ac line

$$d_1(t) = D_0 + \frac{1}{2} D_m \sin(\omega t - \phi)$$

$$d_2(t) = D_0 + \frac{1}{2} D_m \sin(\omega t - \phi - 120^\circ)$$

$$d_3(t) = D_0 + \frac{1}{2} D_m \sin(\omega t - \phi - 240^\circ)$$

where

$\omega$  is the ac line frequency

$D_0$  is a dc bias

$D_m$  is the *modulation index*

For  $D_0 = 0.5$ ,  $D_m$  in the above equations must be less than 1.

The modulation index is defined as one-half of the peak amplitude of the fundamental component of the duty cycle modulation. In some other modulation schemes, it is possible that  $D_m > 1$ .

## Solution, linear sinusoidal PWM

---

If the switching frequency is high, then the inductors can be small and have negligible effect at the ac line frequency. The averaged switch voltage and ac line voltage are then equal:

$$\langle v_{12}(t) \rangle_{T_s} = (d_1(t) - d_2(t)) \langle v(t) \rangle_{T_s} \approx v_{ab}(t)$$

Substitute expressions for duty cycle and ac line voltage variations:

$$\frac{1}{2} D_m \left[ \sin(\omega t - \phi) - \sin(\omega t - \phi - 120^\circ) \right] \langle v(t) \rangle_{T_s} = V_M \left[ \sin(\omega t) - \sin(\omega t - 120^\circ) \right]$$

For small  $L$ ,  $\phi$  tends to zero. The expression then becomes

$$\frac{1}{2} D_m V = V_M$$

Solve for the output voltage:

$$V = \frac{2V_M}{D_m} \qquad V = \frac{2}{\sqrt{3}} \frac{V_{L,pk}}{D_m} = 1.15 \frac{V_{L,pk}}{D_m}$$

# Boost rectifier with sinusoidal PWM

---


$$V = \frac{2}{\sqrt{3}} \frac{V_{L,pk}}{D_m} = 1.15 \frac{V_{L,pk}}{D_m}$$

With sinusoidal PWM, the dc output voltage must be greater than 1.15 times the peak line-line input voltage. Hence, the boost rectifier increases the voltage magnitude.



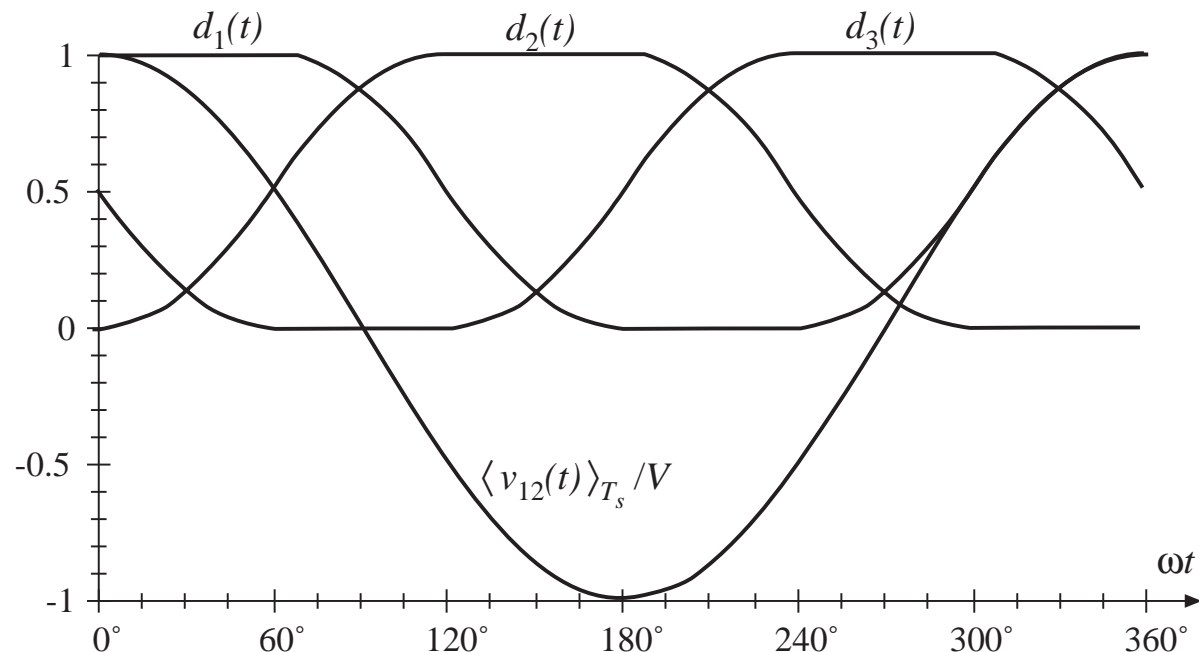
# Nonlinear modulation

- Triplen harmonics can be added to the duty ratio modulation, without appearing in the line-line voltages.
- *Overmodulation*, in which the modulation index  $D_m$  is increased beyond 1, also




leads to undistorted line-line voltages provided that  $D_m \leq 1.15$ . The pulse width modulator saturates, but the duty ratio variations contain only triplen harmonics.  $V = V_{L,pk}$  is obtained at  $D_m = 1.15$ . Further increases in  $D_m$  cause distorted ac line waveforms.

# Buck-type 3 $\phi$ ac–dc rectifier

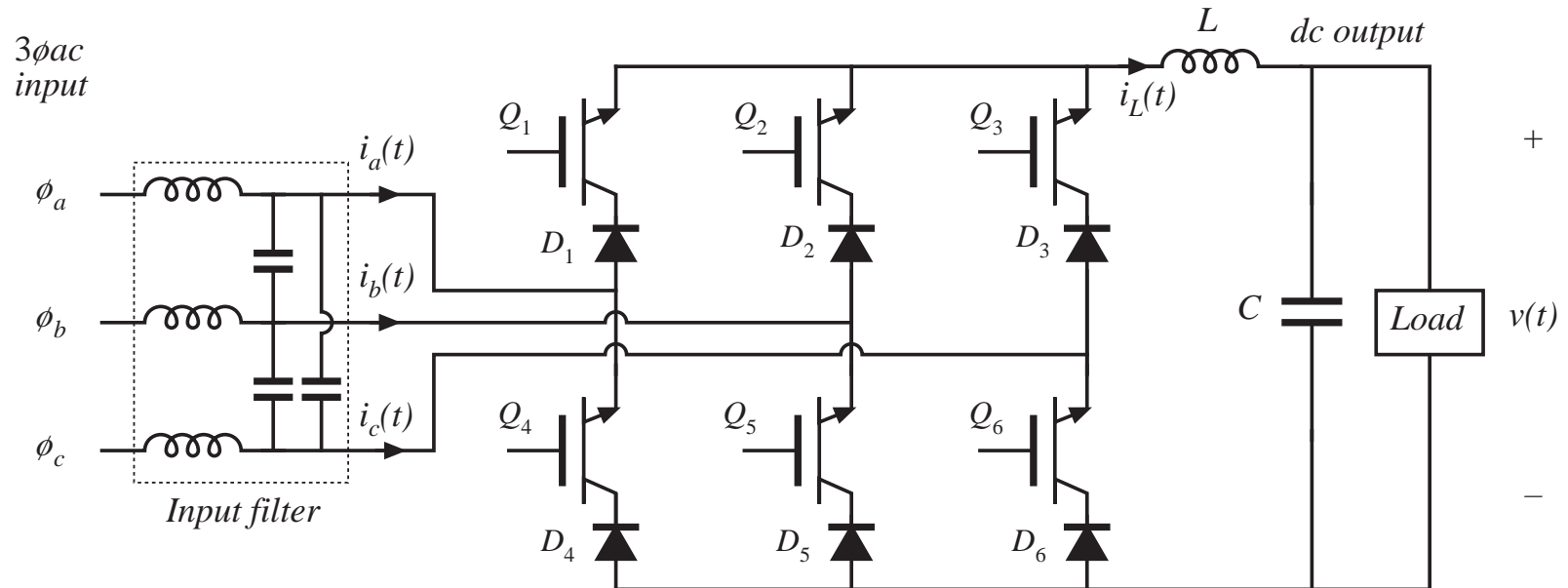


- Can produce controlled dc output voltages in the range  $0 \leq V \leq V_{L,pk}$
- Requires two-quadrant voltage-bidirectional switches
- Exhibits greater active semiconductor stress than boost topology
- Can operate in inverter mode by reversal of output voltage polarity


# Buck–boost topology

 

# Cuk topology

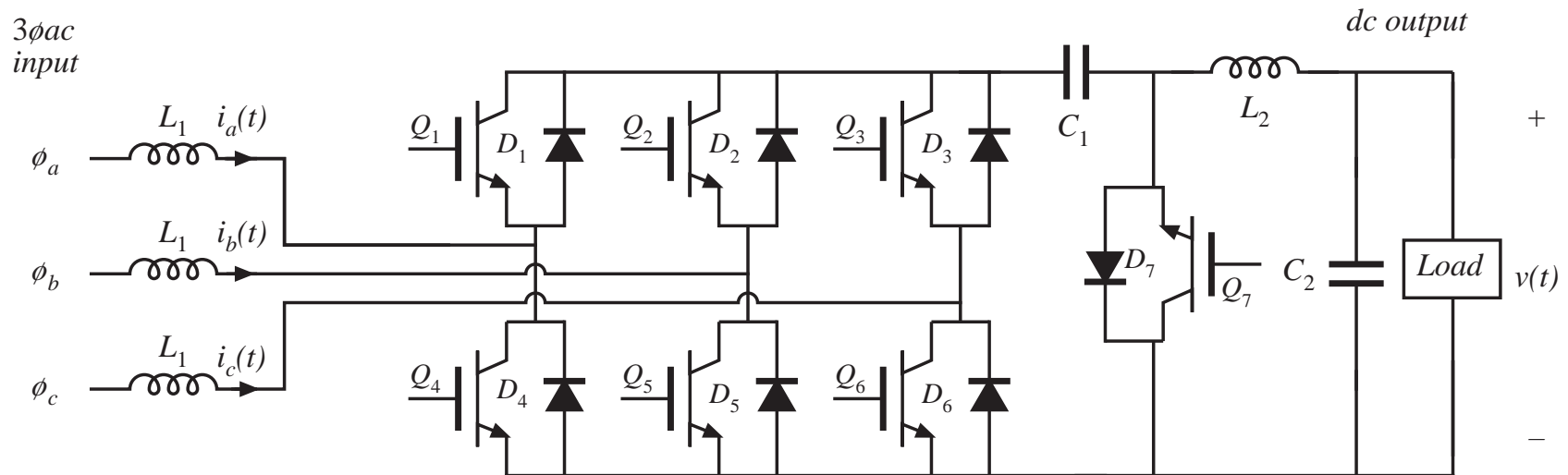

# Use of three single-phase rectifiers

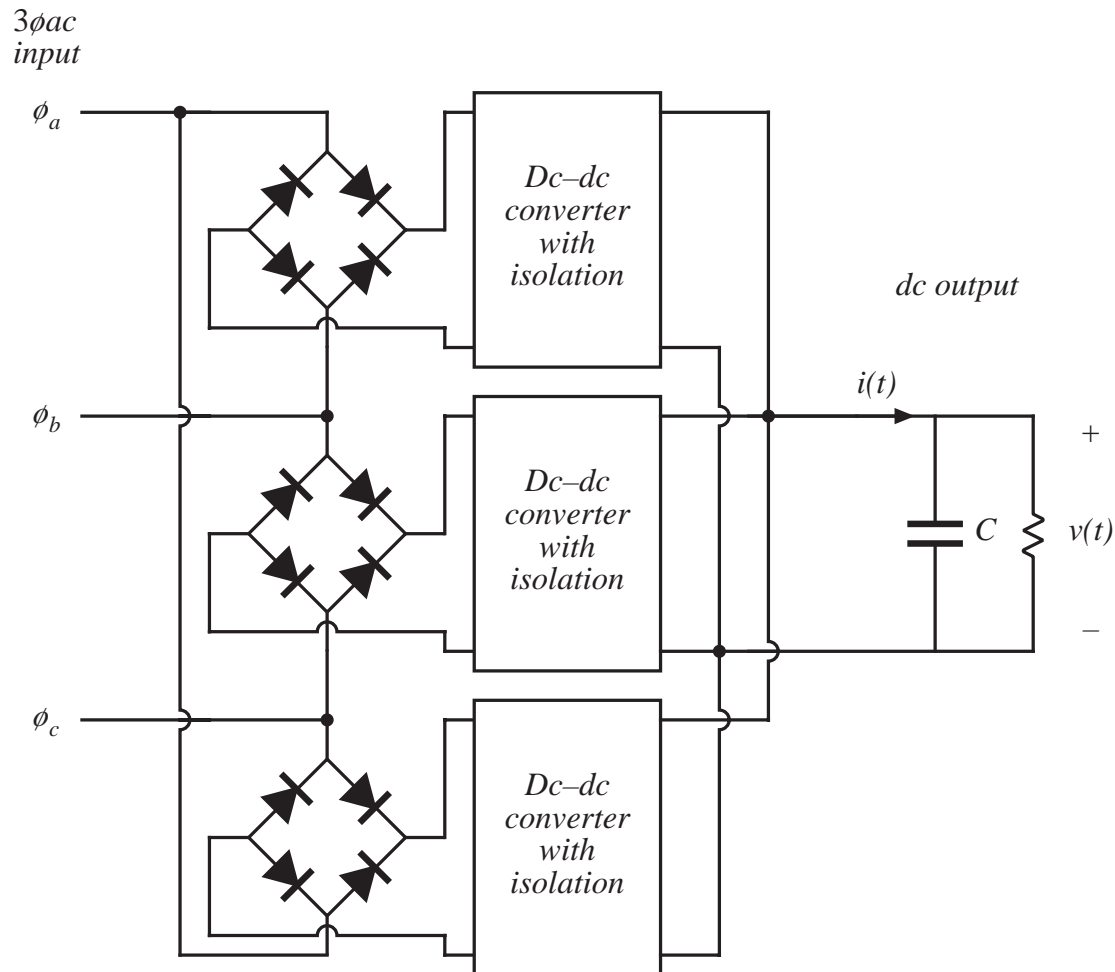

- Each rectifier must include isolation between input and output
- Isolation transformers must be rated to carry the pulsating single-phase ac power  $p_{ac}(t)$
- Outputs can be connected in series or parallel
- Because of the isolation requirement, semiconductor stresses are greater than in 3 $\phi$  boost rectifier

## 17.5.2 Some other approaches to three-phase rectification

---


Low-harmonic rectification requires active semiconductor devices that are much more expensive than simple peak-detection diode rectifiers.

What is the minimum active silicon required to perform the function of 3 $\phi$  low-harmonic rectification?

- No active devices are needed: diodes and harmonic traps will do the job, but these require low-frequency reactive elements
- When control of the output voltage is needed, then there must be at least one active device
- To avoid low-frequency reactive elements, at least one high-frequency switch is needed




So let's search for approaches that use just one active switch, and only high-frequency reactive elements
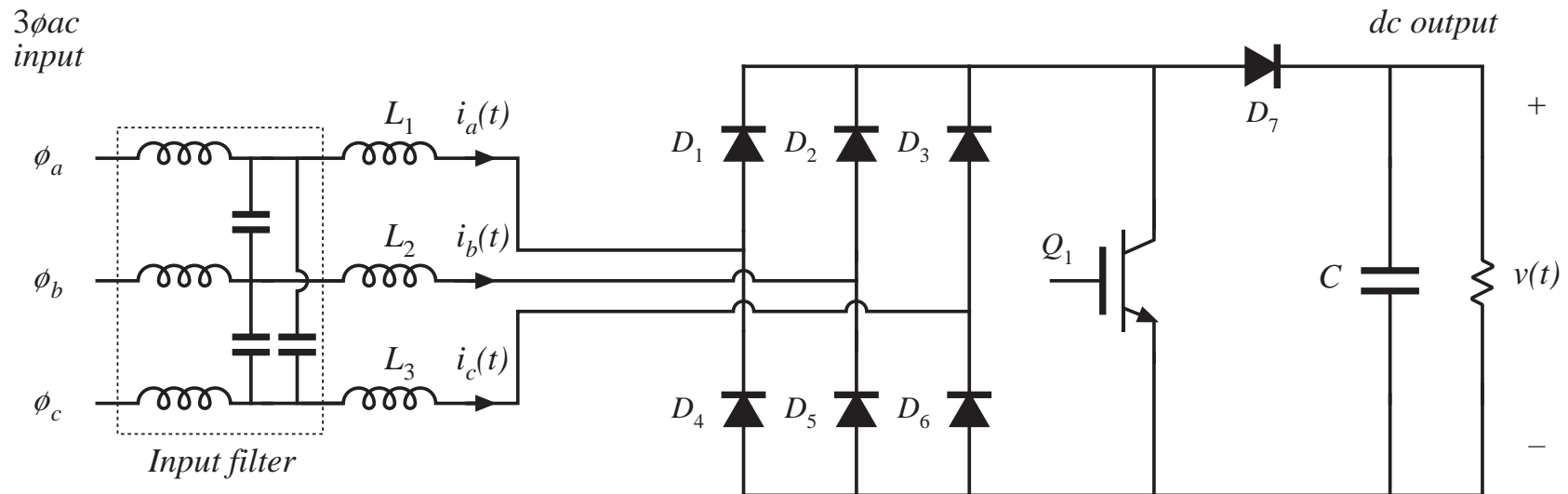
# The single-switch DCM boost 3 $\phi$ rectifier




Inductors  $L_1$  to  $L_3$  operate in discontinuous conduction mode, in conjunction with diodes  $D_1$  to  $D_6$ . Average input currents  $\langle i_a(t) \rangle_{T_s}$ ,  $\langle i_b(t) \rangle_{T_s}$ , and  $\langle i_c(t) \rangle_{T_s}$  are approximately proportional to the instantaneous input line-neutral voltages. Transistor is operated with constant duty cycle; slow variation of the duty cycle allows control of output power.
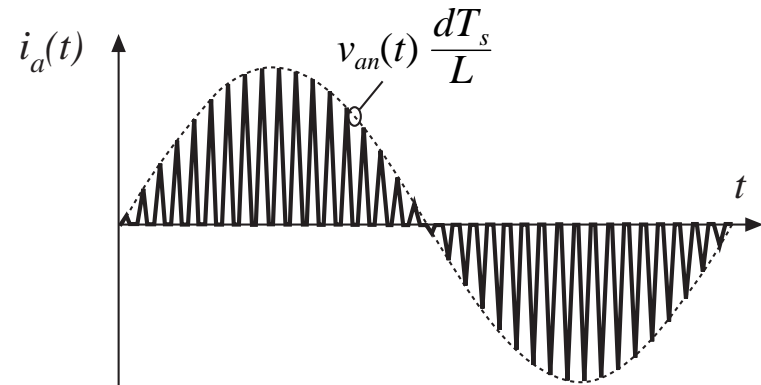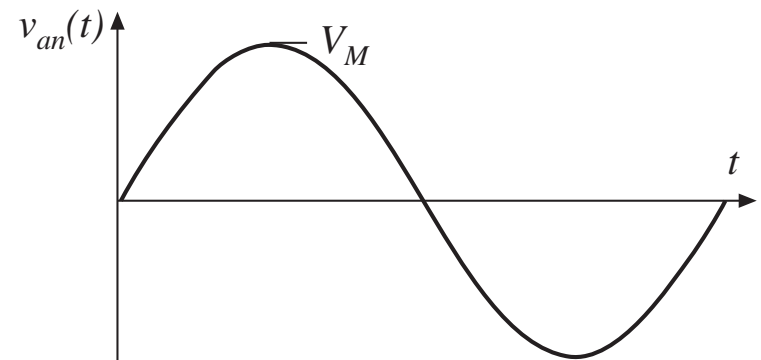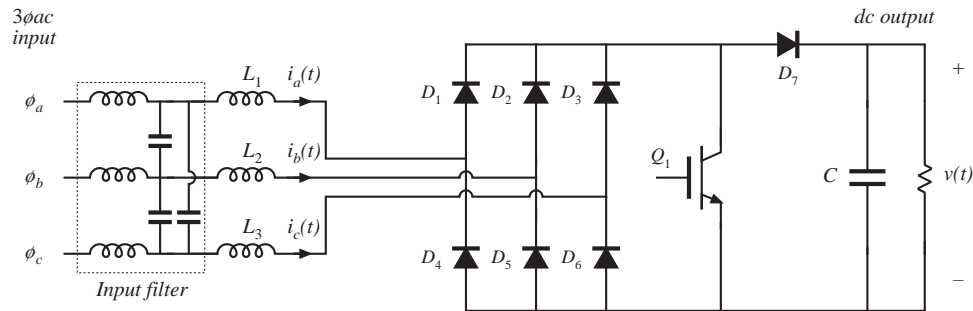
# The single-switch DCM boost 3 $\phi$ rectifier




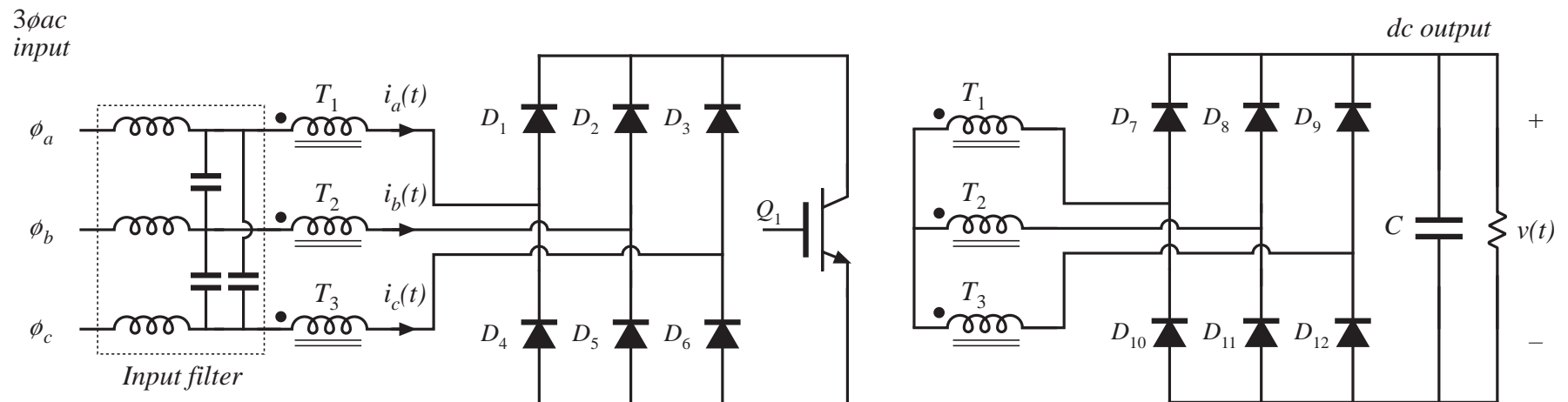
# The single-switch 3 $\phi$ DCM flyback rectifier



# The single-switch 3 $\phi$ DCM flyback rectifier


This converter is effectively three independent single-phase DCM flyback converters that share a common switch.

Since the open-loop DCM flyback converter can be modeled as a Loss-Free Resistor, three-phase low-harmonic rectification is obtained naturally.


Basic converter has a boost characteristic, but buck-boost characteristic is possible (next slide).

Inrush current limiting and isolation are obtained easily.

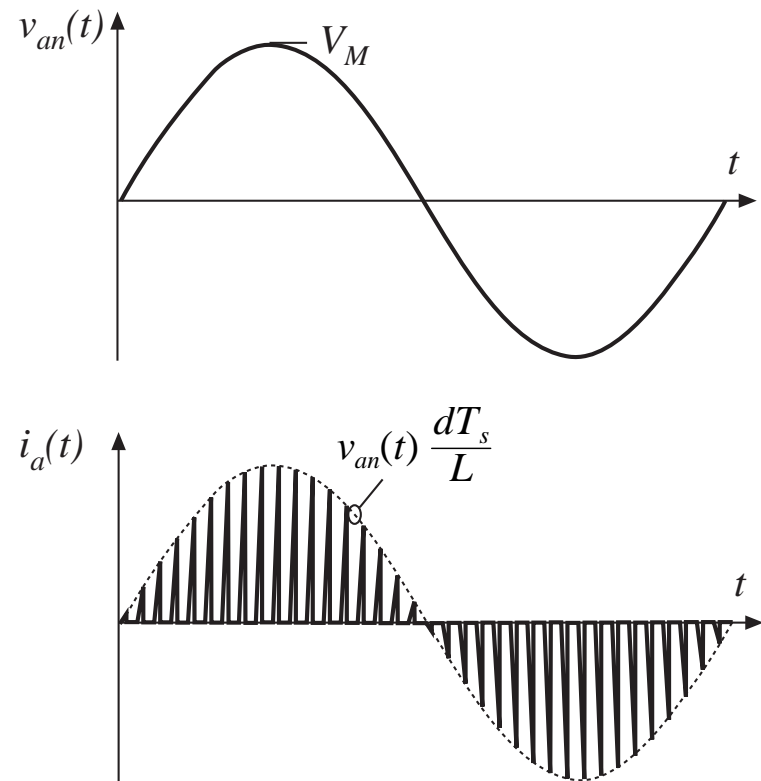
High peak currents, needs an input EMI filter


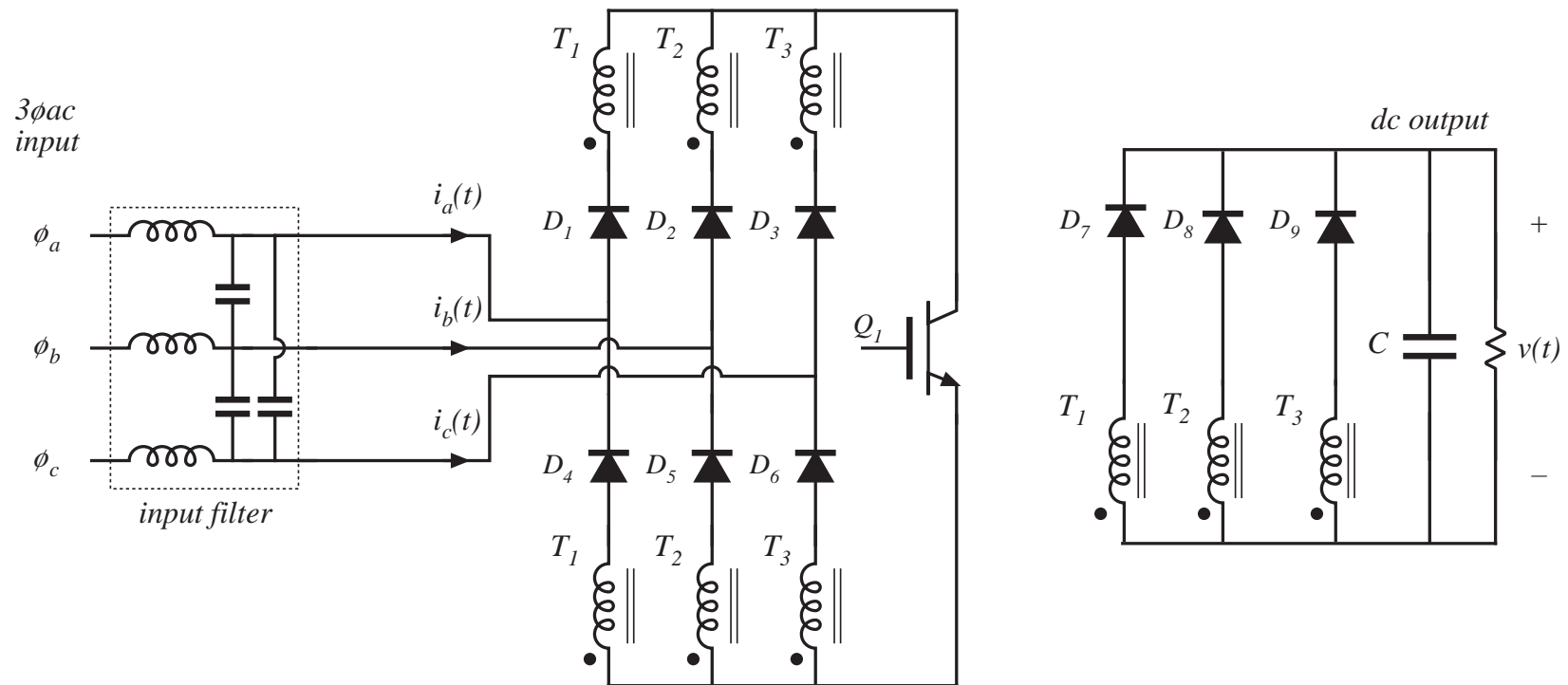
# 3 $\phi$ Flyback rectifier with buck-boost conversion ratio


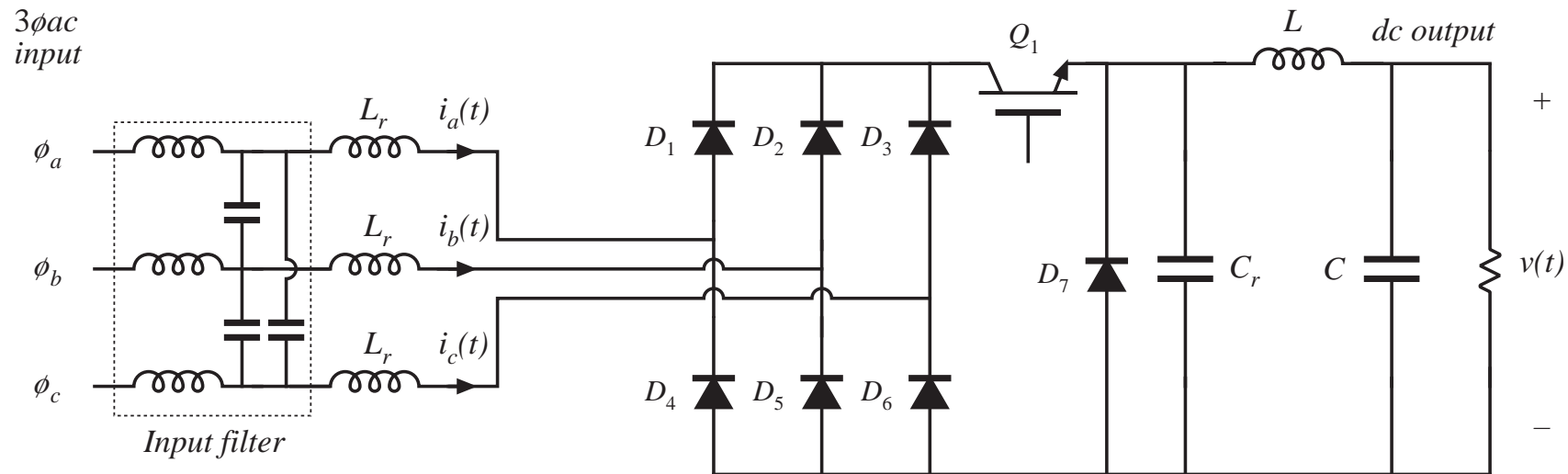
# Single-switch three-phase zero-current-switching quasi-resonant buck rectifier




Inductors  $L_r$  and capacitor  $C_r$  form resonant tank circuits, having resonant frequency slightly greater than the switching frequency.

Turning on  $Q_1$  initiates resonant current pulses, whose amplitudes depend on the instantaneous input line-neutral voltages.

When the resonant current pulses return to zero, diodes  $D_1$  to  $D_6$  are reverse-biased. Transistor  $Q_1$  can then be turned off at zero current.

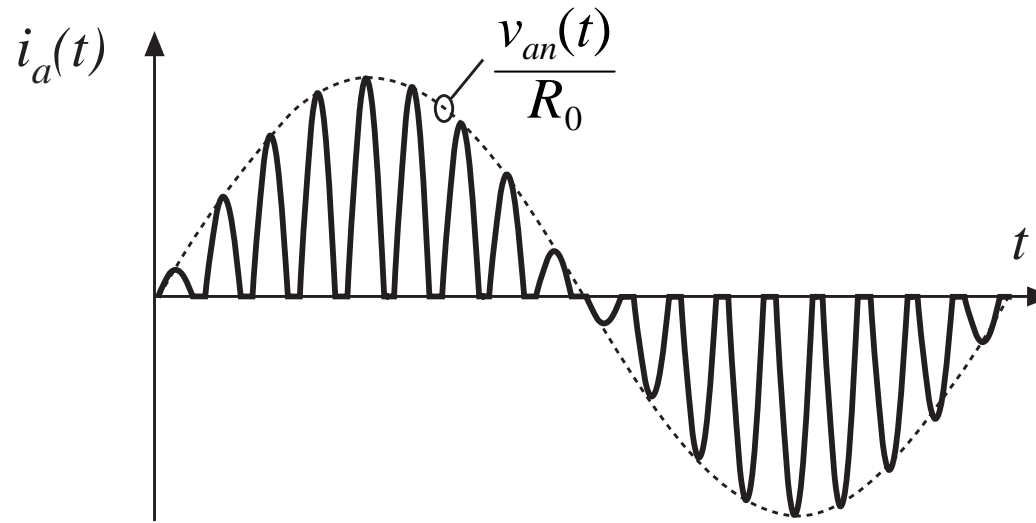
# Single-switch three-phase zero-current-switching quasi-resonant buck rectifier



Input line currents are approximately sinusoidal pulses, whose amplitudes follow the input line-neutral voltages.

Lowest total active semiconductor stress of all buck-type 3 $\phi$  low harmonic rectifiers
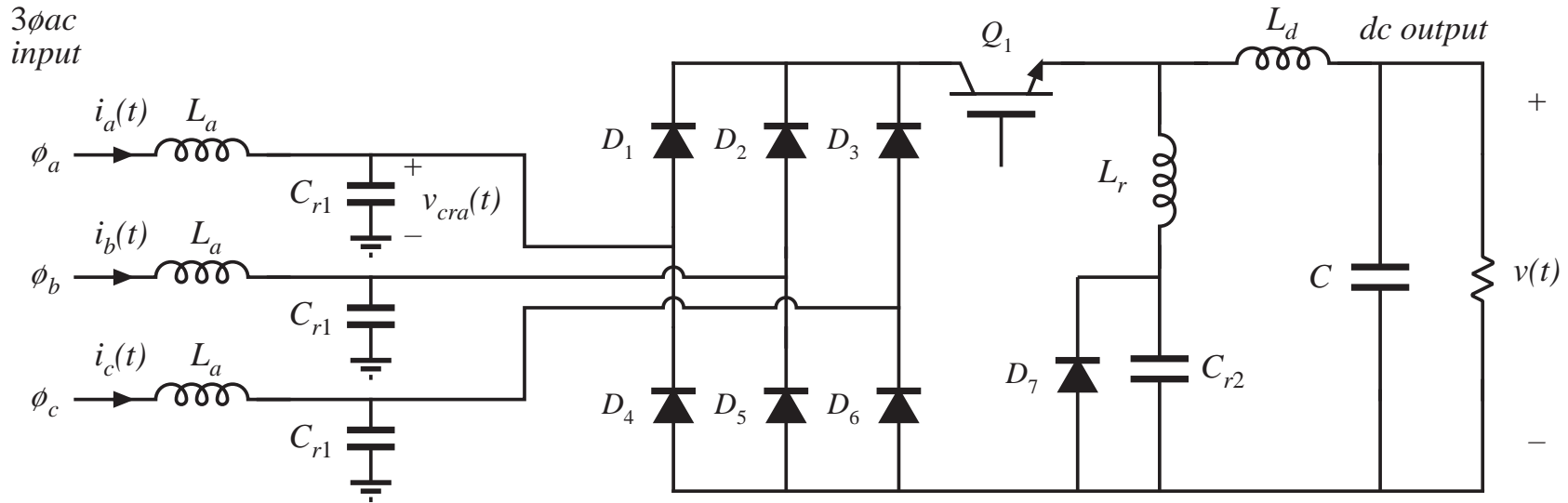
# Multiresonant single-switch zero-current switching 3 $\phi$ buck rectifier




Inductors  $L_r$  and capacitors  $C_{r1}$  and  $C_{r2}$  form resonant tank circuits, having resonant frequency slightly greater than the switching frequency.

Turning on  $Q_1$  initiates resonant voltage pulses in  $v_{cra}(t)$ , whose amplitudes depend on the instantaneous input line-neutral currents  $i_a(t)$  to  $i_c(t)$ .

All diodes switch off when their respective tank voltages reach zero. Transistor  $Q_1$  is turned off at zero current.

 
# Multiresonant single-switch zero-current switching 3 $\phi$ buck rectifier



Input-side resonant voltages are approximately sinusoidal pulses, whose amplitudes follow the input currents. Input filter inductors operate in CCM.

Higher total active semiconductor stress than previous approach, but less EMI filtering is needed. Low THD: < 4% THD can be obtained.

# Harmonic correction

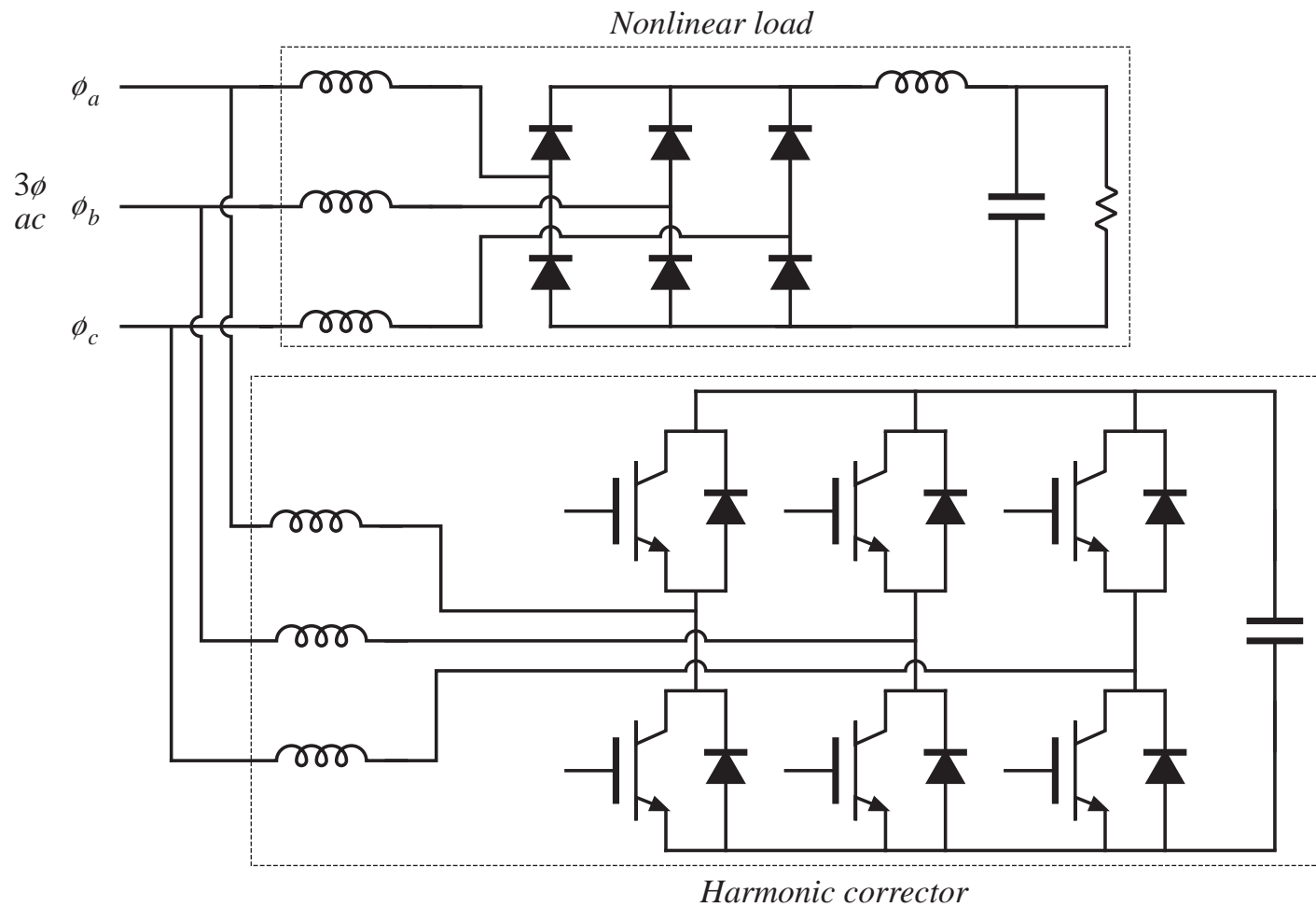



# Harmonic correction

---

- An active filter that is controlled to cancel the harmonic currents created by a nonlinear load.
- Does not need to conduct the average load power.
- Total active semiconductor stress is high when the nonlinear load generates large harmonic currents having high THD.
- In the majority of applications, this approach exhibits greater total active semiconductor stress than the simple  $3\phi$  CCM boost rectifier.

## 17.6 Summary of key points

---

1. The ideal rectifier presents an effective resistive load, the emulated resistance  $R_e$ , to the ac power system. The power apparently “consumed” by  $R_e$  is transferred to the dc output port. In a three-phase ideal rectifier, input resistor emulation is obtained in each phase. In both the single-phase and three-phase cases, the output port follows a power source characteristic, dependent on the instantaneous ac input power. Ideal rectifiers can perform the function of low-harmonic rectification, without need for low-frequency reactive elements.
2. The dc-dc boost converter, as well as other converters capable of increasing the voltage, can be adapted to the ideal rectifier application. A control system causes the input current to be proportional to the input voltage. The converter may operate in CCM, DCM, or in both modes. The mode boundary is expressed as a function of  $R_e$ ,  $2L/T_s$ , and the instantaneous voltage ratio  $v_g(t)/V$ . A well-designed average current controller leads to resistor emulation regardless of the operating mode; however, other schemes discussed in the next chapter may lead to distorted current waveforms when the mode boundary is crossed.

## Summary of key points

---

3. In a single-phase system, the instantaneous ac input power is pulsating, while the dc load power is constant. Whenever the instantaneous input and output powers are not equal, the ideal rectifier system must contain energy storage. A large capacitor is commonly employed; the voltage of this capacitor must be allowed to vary independently, as necessary to store and release energy. A slow feedback loop regulates the dc component of the capacitor voltage, to ensure that the average ac input power and dc load power are balanced.
4. RMS values of rectifiers waveforms can be computed by double integration. In the case of the boost converter, the rms transistor current can be as low as 39% of the rms ac input current, when  $V$  is close in value to  $V_M$ . Other converter topologies such as the buck-boost, SEPIC, and Cuk converters exhibit significantly higher rms transistor currents but are capable of limiting the converter inrush current.

## Summary of key points

---

5. In the three-phase case, a boost-type rectifier based on the PWM voltage-source inverter also exhibits low rms transistor currents. This approach requires six active switching elements, and its dc output voltage must be greater than the peak input line-to-line voltage. Average current control can be used to obtain input resistor emulation. An equivalent circuit can be derived by averaging the switch waveforms. The converter operation can be understood by assuming that the switch duty cycles vary sinusoidally; expressions for the average converter waveforms can then be derived.
6. Other three-phase rectifier topologies are known, including six-switch rectifiers having buck and buck-boost characteristics. In addition, three-phase low-harmonic rectifiers having a reduced number of active switches, as few as one, are discussed here.

# Chapter 18

## Low Harmonic Rectifier Modeling and Control

---

### **18.1 Modeling losses and efficiency in CCM high-quality rectifiers**

Expression for controller duty cycle  $d(t)$

Expression for the dc load current

Solution for converter efficiency  $\eta$

Design example

### **18.2 Controller schemes**

Average current control

Feedforward

Current programmed control

Hysteretic control

Nonlinear carrier control

### **18.3 Control system modeling**

Modeling the outer low-bandwidth control system


Modeling the inner wide-bandwidth average current controller

# 18.1 Modeling losses and efficiency in CCM high-quality rectifiers


**Objective:** extend procedure of Chapter 3, to predict the output voltage, duty cycle variations, and efficiency, of PWM CCM low harmonic rectifiers.

**Approach:** Use the models developed in Chapter 3. Integrate over one ac line cycle to determine steady-state waveforms and average power.

## Boost example


 


*Dc-dc boost converter circuit*

 


*Averaged dc model*

# Modeling the ac-dc boost rectifier

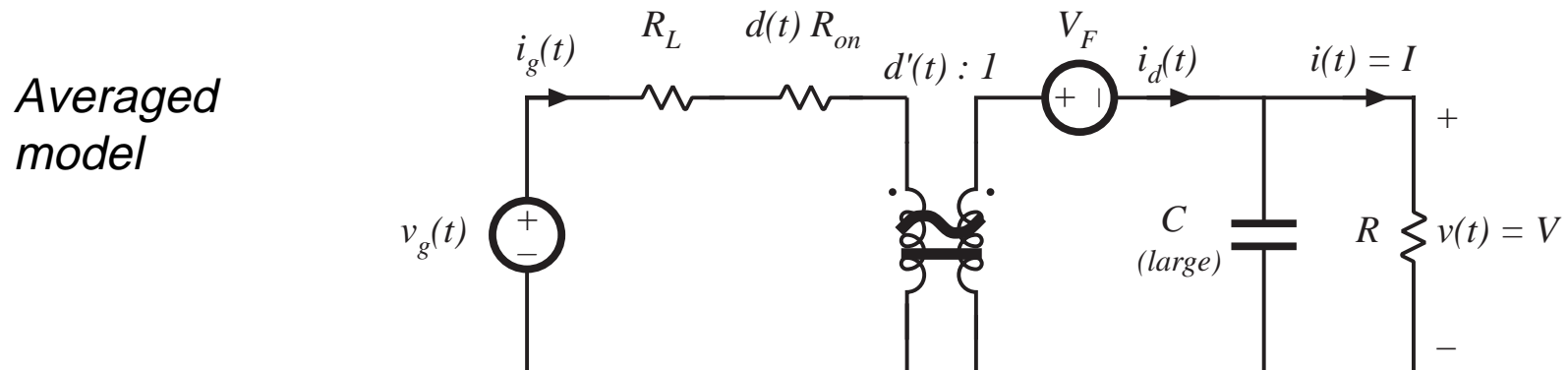
 


# Boost rectifier waveforms

 


*Typical waveforms  
(low frequency components)*

$$i_g(t) = \frac{v_g(t)}{R_e}$$

  


 
## Example: boost rectifier with MOSFET on-resistance



Averaged model

Inductor dynamics are neglected, a good approximation when the ac line variations are slow compared to the converter natural frequencies


## 18.1.1 Expression for controller duty cycle $d(t)$

Solve input side of model:

$$i_g(t)d(t)R_{on} = v_g(t) - d'(t)v$$

with  $i_g(t) = \frac{v_g(t)}{R_e}$

$$v_g(t) = V_M |\sin \omega t|$$

 

eliminate  $i_g(t)$ :

$$\frac{v_g(t)}{R_e} d(t)R_{on} = v_g(t) - d'(t)v$$

solve for  $d(t)$ :

$$d(t) = \frac{v - v_g(t)}{v - v_g(t) \frac{R_{on}}{R_e}}$$

Again, these expressions neglect converter dynamics, and assume that the converter always operates in CCM.

## 18.1.2 Expression for the dc load current


Solve output side of model, using charge balance on capacitor  $C$ :

$$I = \langle i_d \rangle_{T_{ac}}$$

$$i_d(t) = d'(t)i_g(t) = d'(t) \frac{v_g(t)}{R_e}$$

But  $d'(t)$  is:
 
$$d'(t) = \frac{v_g(t) \left( 1 - \frac{R_{on}}{R_e} \right)}{v - v_g(t) \frac{R_{on}}{R_e}}$$



hence  $i_d(t)$  can be expressed as

$$i_d(t) = \frac{v_g^2(t)}{R_e} \frac{\left( 1 - \frac{R_{on}}{R_e} \right)}{v - v_g(t) \frac{R_{on}}{R_e}}$$

Next, average  $i_d(t)$  over an ac line period, to find the dc load current  $I$ .

## Dc load current $I$

Now substitute  $v_g(t) = V_M \sin \omega t$ , and integrate to find  $\langle i_d(t) \rangle_{T_{ac}}$ :

$$I = \langle i_d \rangle_{T_{ac}} = \frac{2}{T_{ac}} \int_0^{T_{ac}/2} \left( \frac{V_M^2}{R_e} \right) \frac{\left( 1 - \frac{R_{on}}{R_e} \right) \sin^2(\omega t)}{\left( v - \frac{V_M R_{on}}{R_e} \sin(\omega t) \right)} dt$$

This can be written in the normalized form

$$I = \frac{2}{T_{ac}} \frac{V_M^2}{V R_e} \left( 1 - \frac{R_{on}}{R_e} \right) \int_0^{T_{ac}/2} \frac{\sin^2(\omega t)}{1 - a \sin(\omega t)} dt$$

with 
$$a = \left( \frac{V_M}{V} \right) \left( \frac{R_{on}}{R_e} \right)$$

# Integration

---

By waveform symmetry, we need only integrate from 0 to  $T_{ac}/4$ . Also, make the substitution  $\theta = \omega t$ :

$$I = \frac{V_M^2}{VR_e} \left( 1 - \frac{R_{on}}{R_e} \right) \frac{2}{\pi} \int_0^{\pi/2} \frac{\sin^2(\theta)}{1 - a \sin(\theta)} d\theta$$

This integral is obtained not only in the boost rectifier, but also in the buck-boost and other rectifier topologies. The solution is

$$\frac{4}{\pi} \int_0^{\pi/2} \frac{\sin^2(\theta)}{1 - a \sin(\theta)} d\theta = F(a) = \frac{2}{a^2\pi} \left( -2a - \pi + \frac{4 \sin^{-1}(a) + 2 \cos^{-1}(a)}{\sqrt{1 - a^2}} \right)$$

- Result is in closed form
- $a$  is a measure of the loss resistance relative to  $R_e$
- $a$  is typically much smaller than unity


# The integral $F(a)$

$$\frac{4}{\pi} \int_0^{\pi/2} \frac{\sin^2(\theta)}{1 - a \sin(\theta)} d\theta = F(a) = \frac{2}{a^2 \pi} \left( -2a - \pi + \frac{4 \sin^{-1}(a) + 2 \cos^{-1}(a)}{\sqrt{1 - a^2}} \right)$$

Approximation via  
polynomial:

$$F(a) \approx 1 + 0.862a + 0.78a^2$$

For  $|a| \leq 0.15$ , this approximate expression is within 0.1% of the exact value. If the  $a^2$  term is omitted, then the accuracy drops to  $\pm 2\%$  for  $|a| \leq 0.15$ . The accuracy of  $F(a)$  coincides with the accuracy of the rectifier efficiency  $\eta$ .

 

## 18.1.4 Solution for converter efficiency $\eta$

---

Converter average input power is

$$P_{in} = \langle p_{in}(t) \rangle_{T_{ac}} = \frac{V_M^2}{2R_e}$$

Average load power is

$$P_{out} = VI = (V) \left( \frac{V_M^2}{VR_e} \left( 1 - \frac{R_{on}}{R_e} \right) \frac{F(a)}{2} \right) \quad \text{with} \quad a = \left( \frac{V_M}{V} \right) \left( \frac{R_{on}}{R_e} \right)$$


So the efficiency is

$$\eta = \frac{P_{out}}{P_{in}} = \left( 1 - \frac{R_{on}}{R_e} \right) F(a)$$

Polynomial approximation:

$$\eta \approx \left( 1 - \frac{R_{on}}{R_e} \right) \left( 1 + 0.862 \frac{V_M}{V} \frac{R_{on}}{R_e} + 0.78 \left( \frac{V_M}{V} \frac{R_{on}}{R_e} \right)^2 \right)$$

# Boost rectifier efficiency

 

$$\eta = \frac{P_{out}}{P_{in}} = \left(1 - \frac{R_{on}}{R_e}\right) F(a)$$

- To obtain high efficiency, choose  $V$  slightly larger than  $V_M$
- Efficiencies in the range 90% to 95% can then be obtained, even with  $R_{on}$  as high as  $0.2R_e$
- Losses other than MOSFET on-resistance are not included here



## 18.1.5 Design example

---

Let us design for a given efficiency. Consider the following specifications:

Output voltage	390 V
Output power	500 W
rms input voltage	120 V
Efficiency	95%

Assume that losses other than the MOSFET conduction loss are negligible.

Average input power is


$$P_{in} = \frac{P_{out}}{\eta} = \frac{500 \text{ W}}{0.95} = 526 \text{ W}$$

Then the emulated resistance is

$$R_e = \frac{V_{g, rms}^2}{P_{in}} = \frac{(120 \text{ V})^2}{526 \text{ W}} = 27.4 \Omega$$
 
# Design example

Also,  $\frac{V_M}{V} = \frac{120\sqrt{2} \text{ V}}{390 \text{ V}} = 0.435$



95% efficiency with  $V_M/V = 0.435$  occurs with  $R_{on}/R_e \approx 0.075$ .

So we require a MOSFET with on resistance of

$$R_{on} \leq (0.075) R_e$$

$$= (0.075) (27.4 \Omega) = 2 \Omega$$

## 18.2 Controller schemes

---

Average current control

Feedforward

Current programmed control


Hysteretic control

Nonlinear carrier control

## 18.2.1 Average current control
 
### *Boost example*

Low frequency  
(average) component  
of input current is  
controlled to follow  
input voltage




# Use of multiplier to control average power

As discussed in Chapter 17, an output voltage feedback loop adjusts the emulated resistance  $R_e$  such that the rectifier power equals the dc load power:

$$P_{av} = \frac{V_{g,rms}^2}{R_e} = P_{load}$$

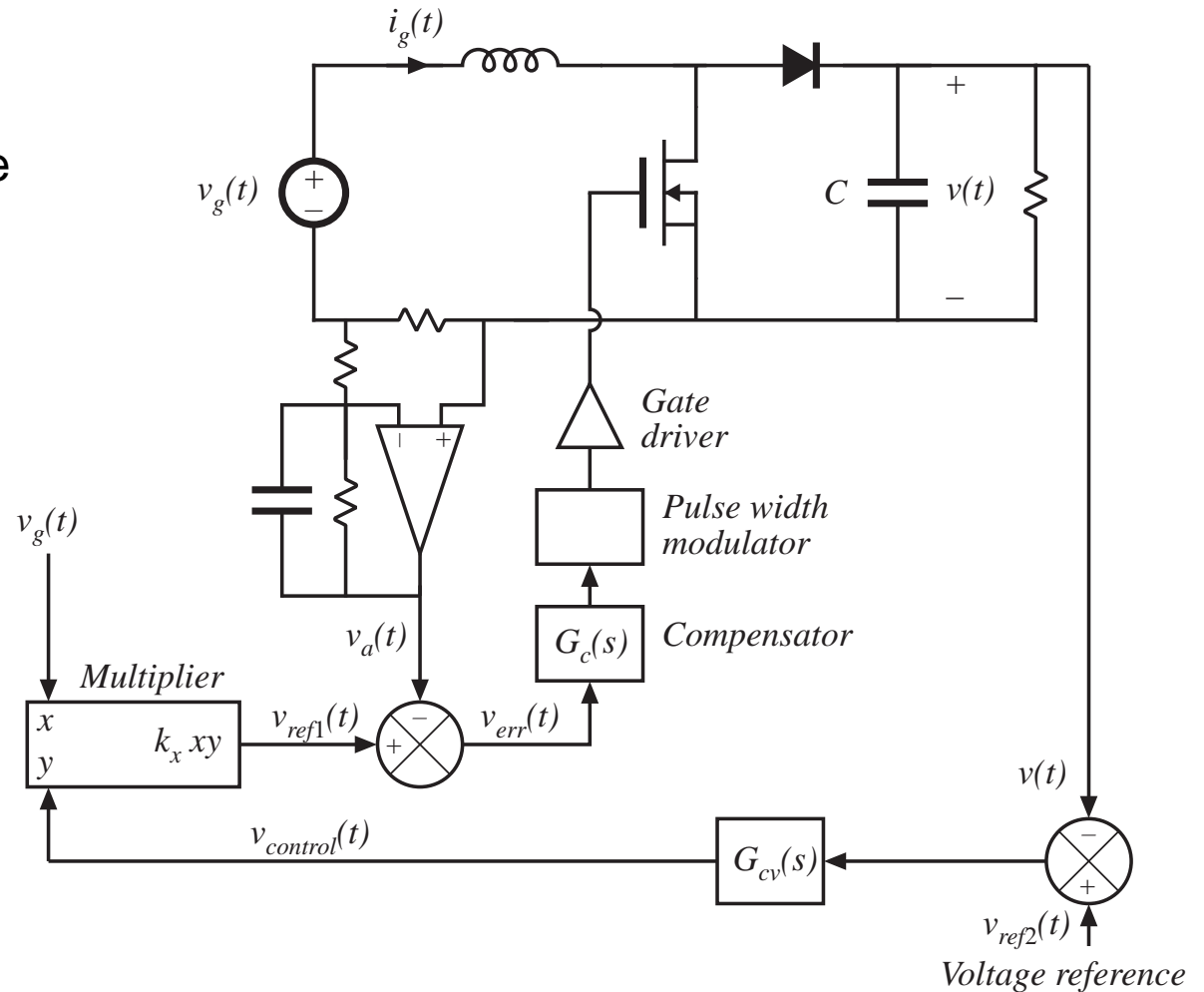An analog multiplier introduces the dependence of  $R_e$  on  $v(t)$ .




## 18.2.2 Feedforward

Feedforward is sometimes used to cancel out disturbances in the input voltage  $v_g(t)$ .

To maintain a given power throughput  $P_{av}$ , the reference voltage  $v_{ref1}(t)$  should be
 
$$v_{ref1}(t) = \frac{P_{av} v_g(t) R_s}{V_{g,rms}^2}$$




# Feedforward, continued

Controller with feedforward produces the following reference:

$$v_{ref1}(t) = \frac{k_v v_{control}(t) v_g(t)}{V_M^2}$$

The average power is then given by
 
$$P_{av} = \frac{k_v v_{control}(t)}{2R_s}$$




## 18.2.3 Current programmed control

Current programmed control is a natural approach to obtain input resistor emulation:

Peak transistor current is programmed to follow input voltage.

 Peak transistor current differs from average inductor current, because of inductor current ripple and artificial ramp. This leads to significant input current waveform distortion.





# CPM boost converter: Static input characteristics

$$\langle i_g(t) \rangle_{T_s} = \begin{cases} v_g(t) \frac{Li_c^2(t)f_s}{(V - v_g(t)) \left( \frac{v_g(t)}{V} + \frac{m_a L}{V} \right)} & \text{in DCM} \\ i_c(t) + m_a T_s \left( \frac{v_g(t)}{V} - 1 \right) + \frac{v_g^2(t) T_s}{2LV} & \text{in CCM} \end{cases}$$

Mode boundary: CCM occurs when

$$\langle i_g(t) \rangle_{T_s} > \frac{T_s V}{2L} \frac{v_g(t)}{V} \left( 1 - \frac{v_g(t)}{V} \right)$$


or, 
$$i_c(t) > \frac{T_s V}{L} \left( \frac{m_a L}{V} + \frac{v_g(t)}{V} \right) \left( 1 - \frac{v_g(t)}{V} \right)$$

It is desired that 
$$i_c(t) = \frac{v_g(t)}{R_e}$$


Minimum slope compensation:

$$m_a = \frac{V}{2L}$$

 *Static input characteristics of CPM boost, with minimum slope compensation:*


 
## 18.3 Control system modeling of high quality rectifiers



Two loops:

Outer low-bandwidth controller

Inner wide-bandwidth controller

## 18.3.1 Modeling the outer low-bandwidth control system

---


This loop maintains power balance, stabilizing the rectifier output voltage against variations in load power, ac line voltage, and component values

The loop must be slow, to avoid introducing variations in  $R_e$  at the harmonics of the ac line frequency

Objective of our modeling efforts: low-frequency small-signal model that predicts transfer functions at frequencies below the ac line frequency

# Large signal model

averaged over switching period  $T_s$

 

Ideal rectifier model, assuming that inner wide-bandwidth loop operates ideally

High-frequency switching harmonics are removed via averaging

Ac line-frequency harmonics are included in model

Nonlinear and time-varying

# Predictions of large-signal model


If the input voltage is

$$v_g(t) = \sqrt{2} v_{g,rms} |\sin(\omega t)|$$


Then the instantaneous power is:

$$\langle p(t) \rangle_{T_s} = \frac{\langle v_g(t) \rangle_{T_s}^2}{R_e(v_{control}(t))} = \frac{v_{g,rms}^2}{R_e(v_{control}(t))} (1 - \cos(2\omega t))$$

 which contains a constant term plus a second-harmonic term



 
# Separation of power source into its constant and time-varying components



The second-harmonic variation in power leads to second-harmonic variations in the output voltage and current


# Removal of even harmonics via averaging

---

 

$$T_{2L} = \frac{1}{2} \frac{2\pi}{\omega} = \frac{\pi}{\omega}$$

# Resulting averaged model

 

Time invariant model

Power source is nonlinear



# Perturbation and linearization

The averaged model predicts that the rectifier output current is

$$\begin{aligned}\langle i_2(t) \rangle_{T_{2L}} &= \frac{\langle p(t) \rangle_{T_{2L}}}{\langle v(t) \rangle_{T_{2L}}} = \frac{v_{g,rms}^2(t)}{R_e(v_{control}(t)) \langle v(t) \rangle_{T_{2L}}} \\ &= f\left(v_{g,rms}(t), \langle v(t) \rangle_{T_{2L}}, v_{control}(t)\right)\end{aligned}$$

Let

$$\begin{aligned}\langle v(t) \rangle_{T_{2L}} &= V + \hat{v}(t) \\ \langle i_2(t) \rangle_{T_{2L}} &= I_2 + \hat{i}_2(t) \\ v_{g,rms} &= V_{g,rms} + \hat{v}_{g,rms}(t) \\ v_{control}(t) &= V_{control} + \hat{v}_{control}(t)\end{aligned}$$

with

$$\begin{aligned}V &\gg |\hat{v}(t)| \\ I_2 &\gg |\hat{i}_2(t)| \\ V_{g,rms} &\gg |\hat{v}_{g,rms}(t)| \\ V_{control} &\gg |\hat{v}_{control}(t)|\end{aligned}$$

# Linearized result

$$I_2 + \hat{i}_2(t) = g_2 \hat{v}_{g,rms}(t) + j_2 \hat{v}(t) - \frac{\hat{v}_{control}(t)}{r_2}$$


where

$$g_2 = \left. \frac{df(v_{g,rms}, V, V_{control})}{dv_{g,rms}} \right|_{v_{g,rms} = V_{g,rms}} = \frac{2}{R_e(V_{control})} \frac{V_{g,rms}}{V}$$

$$\left( -\frac{1}{r_2} \right) = \left. \frac{df(V_{g,rms}, \langle v \rangle_{T_{2L}}, V_{control})}{d\langle v \rangle_{T_{2L}}} \right|_{\langle v \rangle_{T_{2L}} = V} = -\frac{I_2}{V}$$

$$j_2 = \left. \frac{df(V_{g,rms}, V, v_{control})}{dv_{control}} \right|_{v_{control} = V_{control}} = -\frac{V_{g,rms}^2}{VR_e^2(V_{control})} \left. \frac{dR_e(v_{control})}{dv_{control}} \right|_{v_{control} = V_{control}}$$

# Small-signal equivalent circuit

 

Predicted transfer functions

*Control-to-output* 
$$\frac{\hat{v}(s)}{\hat{v}_{control}(s)} = j_2 R || r_2 \frac{1}{1 + sC R || r_2}$$


*Line-to-output* 
$$\frac{\hat{v}(s)}{\hat{v}_{g,rms}(s)} = g_2 R || r_2 \frac{1}{1 + sC R || r_2}$$

# Model parameters

**Table 18.1** Small-signal model parameters for several types of rectifier control schemes

<i>Controller type</i>	$g_2$	$j_2$	$r_2$
Average current control with feedforward, Fig. 18.9	0	$\frac{P_{av}}{VV_{control}}$	$\frac{V^2}{P_{av}}$
Current-programmed control, Fig. 18.10	$\frac{2P_{av}}{VV_{g,rms}}$	$\frac{P_{av}}{VV_{control}}$	$\frac{V^2}{P_{av}}$
Nonlinear-carrier charge control of boost rectifier, Fig. 18.14	$\frac{2P_{av}}{VV_{g,rms}}$	$\frac{P_{av}}{VV_{control}}$	$\frac{V^2}{2P_{av}}$
Boost with hysteretic control, Fig. 18.13(b)	$\frac{2P_{av}}{VV_{g,rms}}$	$\frac{P_{av}}{VT_{on}}$	$\frac{V^2}{P_{av}}$
DCM buck–boost, flyback, SEPIC, or Cuk converters	$\frac{2P_{av}}{VV_{g,rms}}$	$\frac{2P_{av}}{VD}$	$\frac{V^2}{P_{av}}$

# Constant power load

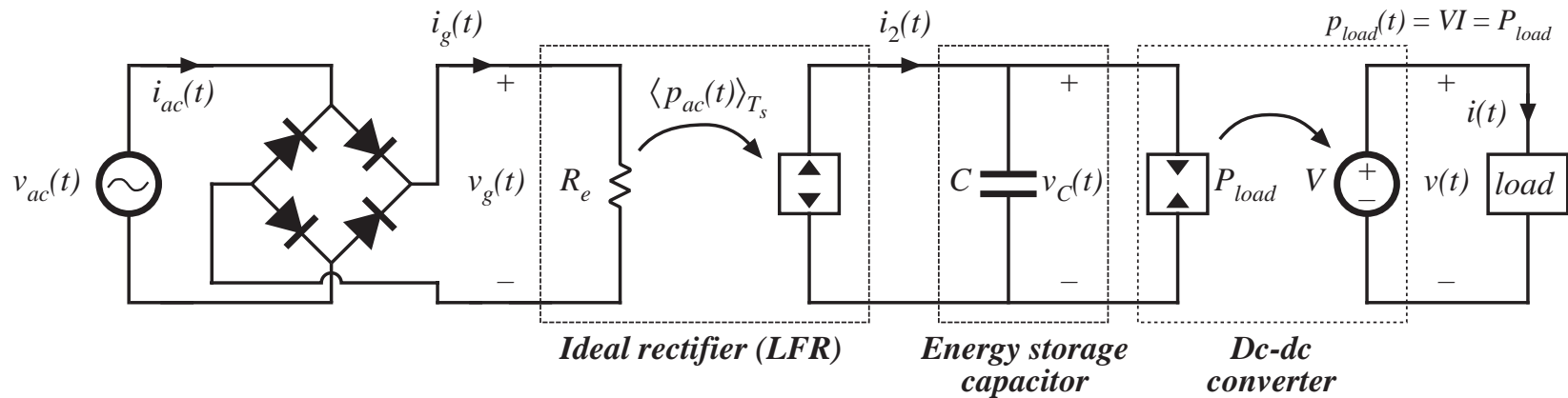

Rectifier and dc-dc converter operate with same average power

Incremental resistance  $R$  of constant power load is negative, and is

$$R = -\frac{V^2}{P_{av}}$$

which is equal in magnitude and opposite in polarity to rectifier incremental output resistance  $r_2$  for all controllers except NLC

# Transfer functions with constant power load

---


When  $r_2 = -R$ , the parallel combination  $r_2 \parallel R$  becomes equal to zero. The small-signal transfer functions then reduce to

$$\frac{\hat{v}(s)}{\hat{v}_{control}(s)} = \frac{j_2}{sC}$$

$$\frac{\hat{v}(s)}{\hat{v}_{g,rms}(s)} = \frac{g_2}{sC}$$
 
## 18.3.2 Modeling the inner wide-bandwidth average current controller

Averaged (but not linearized) boost converter model, Fig. 7.42:



In Chapter 7,  
we perturbed  
and linearized  
using the  
assumptions

$$\begin{aligned}\langle v_g(t) \rangle_{T_s} &= V_g + \hat{v}_g(t) \\ d(t) &= D + \hat{d}(t) \Rightarrow d'(t) = D' - \hat{d}(t) \\ \langle i(t) \rangle_{T_s} &= \langle i_1(t) \rangle_{T_s} = I + \hat{i}(t) \\ \langle v(t) \rangle_{T_s} &= \langle v_2(t) \rangle_{T_s} = V + \hat{v}(t) \\ \langle v_1(t) \rangle_{T_s} &= V_1 + \hat{v}_1(t) \\ \langle i_2(t) \rangle_{T_s} &= I_2 + \hat{i}_2(t)\end{aligned}$$

Problem: variations in  $v_g$ ,  
 $i_1$ , and  $d$  are not small.

So we are faced with the  
design of a control  
system that exhibits  
significant nonlinear  
time-varying behavior.

# Linearizing the equations of the boost rectifier

---

When the rectifier operates near steady-state, it is true that

$$\langle v(t) \rangle_{T_s} = V + \hat{v}(t)$$

with

$$|\hat{v}(t)| \ll |V|$$

In the special case of the boost rectifier, this is sufficient to linearize the equations of the average current controller.

The boost converter average inductor voltage is

$$L \frac{d\langle i_g(t) \rangle_{T_s}}{dt} = \langle v_g(t) \rangle_{T_s} - d'(t)V - d'(t)\hat{v}(t)$$

substitute:

$$L \frac{d\langle i_g(t) \rangle_{T_s}}{dt} = \langle v_g(t) \rangle_{T_s} - d'(t)V - d'(t)\hat{v}(t)$$



# Linearized boost rectifier model


$$L \frac{d\langle i_g(t) \rangle_{T_s}}{dt} = \langle v_g(t) \rangle_{T_s} - d'(t)V - d'(t)\hat{v}(t)$$

The nonlinear term is much smaller than the linear ac term. Hence, it can be discarded to obtain

$$L \frac{d\langle i_g(t) \rangle_{T_s}}{dt} = \langle v_g(t) \rangle_{T_s} - d'(t)V$$

Equivalent circuit:

$$\frac{i_g(s)}{d(s)} = \frac{V}{sL}$$

 

# The quasi-static approximation

---

The above approach is not sufficient to linearize the equations needed to design the rectifier averaged current controllers of buck-boost, Cuk, SEPIC, and other converter topologies. These are truly nonlinear time-varying systems.

An approximate approach that is sometimes used in these cases: the *quasi-static approximation*

Assume that the ac line variations are much slower than the converter dynamics, so that the rectifier always operates near equilibrium. The quiescent operating point changes slowly along the input sinusoid, and we can find the slowly-varying “equilibrium” duty ratio as in Section 18.1.

The converter small-signal transfer functions derived in Chapters 7 and 8 are evaluated, using the time-varying operating point. The poles, zeroes, and gains vary slowly as the operating point varies. An average current controller is designed, that has a positive phase margin at each operating point.

# Quasi-static approximation: discussion

---

In the literature, several authors have reported success using this method

Should be valid provided that the converter dynamics are sufficiently fast, such that the converter always operates near the assumed operating points

No good condition on system parameters, which can justify the approximation, is presently known for the basic converter topologies

It is well-understood in the field of control systems that, when the converter dynamics are not sufficiently fast, then the quasi-static approximation yields neither necessary nor sufficient conditions for stability. Such behavior can be observed in rectifier systems. Worst-case analysis to prove stability should employ simulations.

# Chapter 19

## Resonant Conversion

---

### **Introduction**

#### **19.1 Sinusoidal analysis of resonant converters**

#### **19.2 Examples**

Series resonant converter

Parallel resonant converter

#### **19.3 Exact characteristics of the series and parallel resonant converters**

#### **19.4 Soft switching**

Zero current switching

Zero voltage switching

The zero voltage transition converter

#### **19.5 Load-dependent properties of resonant converters**

# Introduction to Resonant Conversion

---


Resonant power converters contain resonant L-C networks whose voltage and current waveforms vary sinusoidally during one or more subintervals of each switching period. These sinusoidal variations are large in magnitude, and the small ripple approximation does not apply.

Some types of resonant converters:




- Dc-to-high-frequency-ac inverters
- Resonant dc-dc converters
- Resonant inverters or rectifiers producing line-frequency ac

# A basic class of resonant inverters


*Basic circuit*

 

*Several resonant tank networks*

   
 
# Tank network responds only to fundamental component of switched waveforms




Tank current and output voltage are essentially sinusoids at the switching frequency  $f_s$ .

Output can be controlled by variation of switching frequency, closer to or away from the tank resonant frequency
 
# Derivation of a resonant dc-dc converter

Rectify and filter the output of a dc-high-frequency-ac inverter




The series resonant dc-dc converter


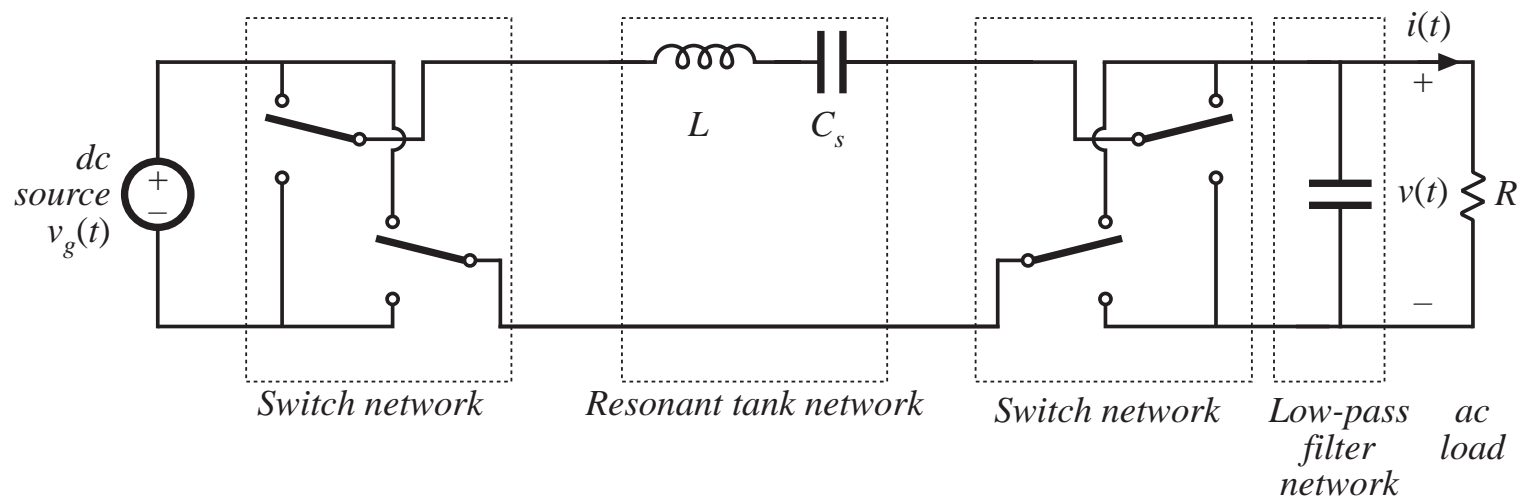
# A series resonant link inverter


Same as dc-dc series resonant converter, except output rectifiers are replaced with four-quadrant switches:





# Quasi-resonant converters

In a conventional PWM converter, replace the PWM switch network with a switch network containing resonant elements.

## Buck converter example

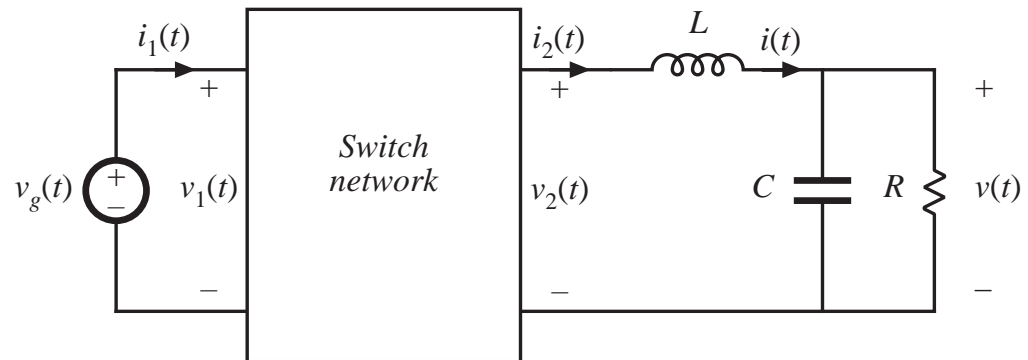

Two  
switch  
networks:

 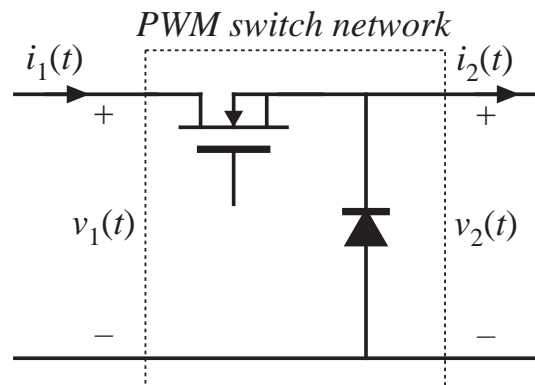

# Resonant conversion: advantages

---

The chief advantage of resonant converters: reduced switching loss

*Zero-current switching*

*Zero-voltage switching*

Turn-on or turn-off transitions of semiconductor devices can occur at zero crossings of tank voltage or current waveforms, thereby reducing or eliminating some of the switching loss mechanisms. Hence resonant converters can operate at higher switching frequencies than comparable PWM converters

Zero-voltage switching also reduces converter-generated EMI

Zero-current switching can be used to commutate SCRs

In specialized applications, resonant networks may be unavoidable

High voltage converters: significant transformer leakage inductance and winding capacitance leads to resonant network

# Resonant conversion: disadvantages

---

Can optimize performance at one operating point, but not with wide range of input voltage and load power variations

Significant currents may circulate through the tank elements, even when the load is disconnected, leading to poor efficiency at light load

Quasi-sinusoidal waveforms exhibit higher peak values than equivalent rectangular waveforms

These considerations lead to increased conduction losses, which can offset the reduction in switching loss

Resonant converters are usually controlled by variation of switching frequency. In some schemes, the range of switching frequencies can be very large

Complexity of analysis


# Resonant conversion: Outline of discussion

---

- Simple steady-state analysis via sinusoidal approximation
- Simple and exact results for the series and parallel resonant converters
- Mechanisms of soft switching
- Circulating currents, and the dependence (or lack thereof) of conduction loss on load power
- Quasi-resonant converter topologies
- Steady-state analysis of quasi-resonant converters
- Ac modeling of quasi-resonant converters via averaged switch modeling

## 19.1 Sinusoidal analysis of resonant converters


A resonant dc-dc converter:

 

If tank responds primarily to fundamental component of switch network output voltage waveform, then harmonics can be neglected.

Let us model all ac waveforms by their fundamental components.

# The sinusoidal approximation

 


Tank current and output voltage are essentially sinusoids at the switching frequency  $f_s$ .

Neglect harmonics of switch output voltage waveform, and model only the fundamental component.


Remaining ac waveforms can be found via phasor analysis.
 
## 19.1.1 Controlled switch network model



If the switch network produces a square wave, then its output voltage has the following Fourier series:
 
$$v_s(t) = \frac{4V_g}{\pi} \sum_{n=1, 3, 5, \dots} \frac{1}{n} \sin(n\omega_s t)$$




The fundamental component is

$$v_{s1}(t) = \frac{4V_g}{\pi} \sin(\omega_s t) = V_{s1} \sin(\omega_s t)$$

So model switch network output port with voltage source of value  $v_{s1}(t)$




# Model of switch network input port

 

Assume that switch network output current is


$$i_s(t) \approx I_{s1} \sin(\omega_s t - \varphi_s)$$

 It is desired to model the dc component (average value) of the switch network input current.





$$\begin{aligned} \langle i_g(t) \rangle_{T_s} &= \frac{2}{T_s} \int_0^{T_s/2} i_g(\tau) d\tau \\ &\approx \frac{2}{T_s} \int_0^{T_s/2} I_{s1} \sin(\omega_s \tau - \varphi_s) d\tau \\ &= \frac{2}{\pi} I_{s1} \cos(\varphi_s) \end{aligned}$$

# Switch network: equivalent circuit

 

- Switch network converts dc to ac
- Dc components of input port waveforms are modeled
- Fundamental ac components of output port waveforms are modeled
- Model is power conservative: predicted average input and output powers are equal
  
## 19.1.2 Modeling the rectifier and capacitive filter networks



Assume large output filter capacitor, having small ripple.

$v_R(t)$  is a square wave, having zero crossings in phase with tank output current  $i_R(t)$ .

If  $i_R(t)$  is a sinusoid:

$$i_R(t) = I_{R1} \sin(\omega_s t - \phi_R)$$

Then  $v_R(t)$  has the following Fourier series:


$$v_R(t) = \frac{4V}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{n} \sin(n\omega_s t - \phi_R)$$

# Sinusoidal approximation: rectifier


Again, since tank responds only to fundamental components of applied waveforms, harmonics in  $v_R(t)$  can be neglected.  $v_R(t)$  becomes

$$v_{R1}(t) = \frac{4V}{\pi} \sin(\omega_s t - \phi_R) = V_{R1} \sin(\omega_s t - \phi_R)$$


*Actual waveforms*

 

*with harmonics ignored*

 

# Rectifier dc output port model

 


Output capacitor charge balance: dc load current is equal to average rectified tank output current

$$\left\langle |i_R(t)| \right\rangle_{T_s} = I$$

Hence

$$\begin{aligned} I &= \frac{2}{T_s} \int_0^{T_s/2} I_{R1} \left| \sin(\omega_s t - \phi_R) \right| dt \\ &= \frac{2}{\pi} I_{R1} \end{aligned}$$

 

# Equivalent circuit of rectifier


Rectifier input port:

Fundamental components of current and voltage are sinusoids that are in phase

Hence rectifier presents a resistive load to tank network

Effective resistance  $R_e$  is

 
$$R_e = \frac{v_{R1}(t)}{i_{R1}(t)} = \frac{8}{\pi^2} \frac{V}{I}$$



With a resistive load  $R$ , this becomes

$$R_e = \frac{8}{\pi^2} R = 0.8106R$$

## 19.1.3 Resonant tank network

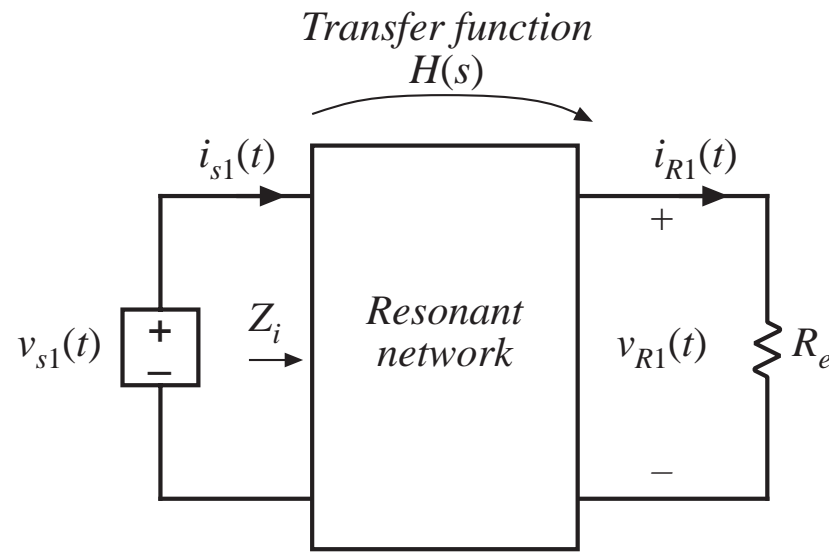

Model of ac waveforms is now reduced to a linear circuit. Tank network is excited by effective sinusoidal voltage (switch network output port), and is load by effective resistive load (rectifier input port).

Can solve for transfer function via conventional linear circuit analysis.

# Solution of tank network waveforms

Transfer function:

$$\frac{v_{R1}(s)}{v_{s1}(s)} = H(s)$$

Ratio of peak values of input and output voltages:


$$\frac{V_{R1}}{V_{s1}} = \| H(s) \|_{s=j\omega_s}$$

Solution for tank output current:

$$i_R(s) = \frac{v_{R1}(s)}{R_e} = \frac{H(s)}{R_e} v_{s1}(s)$$


which has peak magnitude

$$I_{R1} = \frac{\| H(s) \|_{s=j\omega_s}}{R_e} V_{s1}$$

 


 
## 19.1.4 Solution of converter voltage conversion ratio $M = V / V_g$



$$M = \frac{V}{V_g} = \underbrace{\left(R\right)}_{\left(\frac{V}{I}\right)} \underbrace{\left(\frac{2}{\pi}\right)}_{\left(\frac{I}{I_{R1}}\right)} \underbrace{\left(\frac{1}{R_e}\right)}_{\left(\frac{I_{R1}}{V_{R1}}\right)} \underbrace{\left(\|H(s)\|_{s=j\omega_s}\right)}_{\left(\frac{V_{R1}}{V_{s1}}\right)} \underbrace{\left(\frac{4}{\pi}\right)}_{\left(\frac{V_{s1}}{V_g}\right)}$$

Eliminate  $R_e$ :

$$\frac{V}{V_g} = \|H(s)\|_{s=j\omega_s}$$

# Conversion ratio $M$


---

$$\frac{V}{V_g} = \| H(s) \|_{s = j\omega_s}$$


So we have shown that the conversion ratio of a resonant converter, having switch and rectifier networks as in previous slides, is equal to the magnitude of the tank network transfer function. This transfer function is evaluated with the tank loaded by the effective rectifier input resistance  $R_e$ .

## 19.2 Examples

### 19.2.1 Series resonant converter

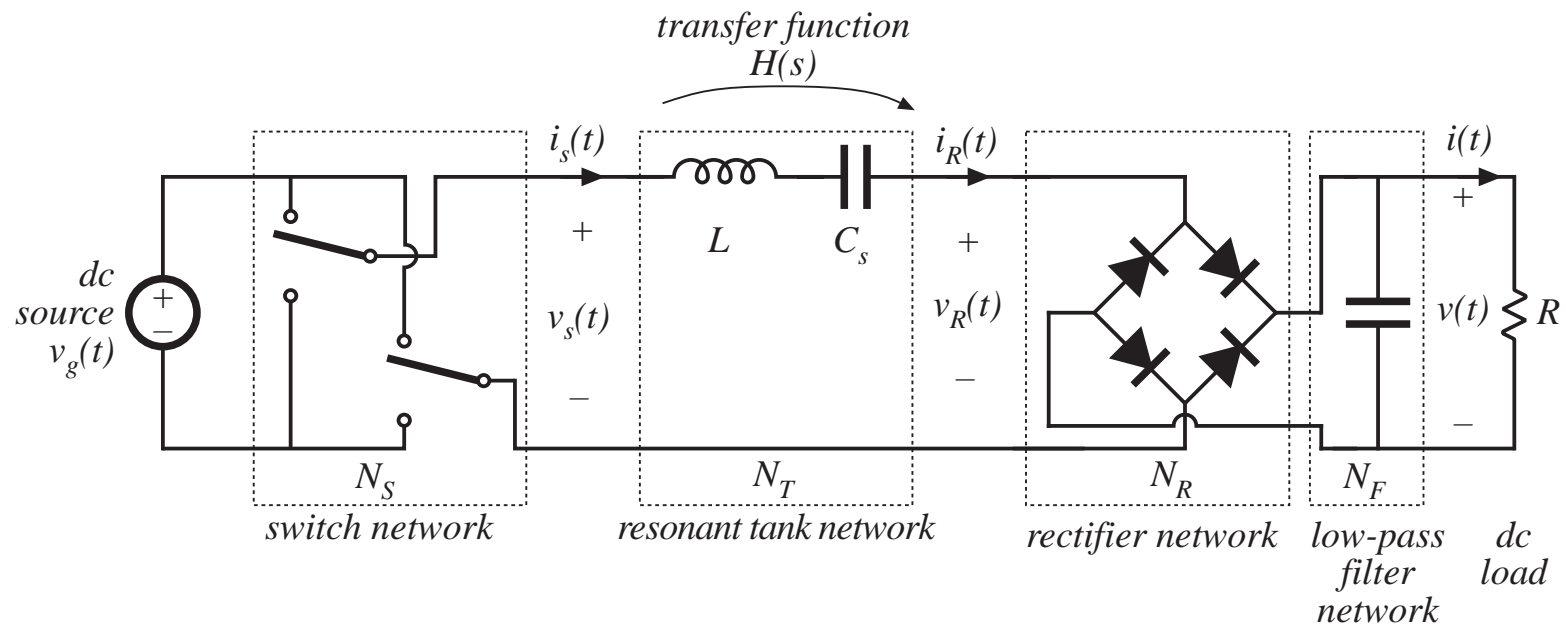

# Model: series resonant converter

 

$$H(s) = \frac{R_e}{Z_i(s)} = \frac{R_e}{R_e + sL + \frac{1}{sC}}$$

$$= \frac{\left(\frac{s}{Q_e \omega_0}\right)}{1 + \left(\frac{s}{Q_e \omega_0}\right) + \left(\frac{s}{\omega_0}\right)^2}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = 2\pi f_0$$

$$R_0 = \sqrt{\frac{L}{C}}$$


$$Q_e = \frac{R_0}{R_e}$$

$$M = \|H(j\omega_s)\| = \frac{1}{\sqrt{1 + Q_e^2 \left(\frac{1}{F} - F\right)^2}}$$


## Construction of $Z_i$

 

# Construction of $H$

 

## 19.2.2 Subharmonic modes of the SRC

 

*Example:* excitation of tank by third harmonic of switching frequency


Can now approximate  $v_s(t)$  by its third harmonic:

$$v_s(t) \approx v_{sn}(t) = \frac{4V_g}{n\pi} \sin(n\omega_s t)$$

Result of analysis:


$$M = \frac{V}{V_g} = \frac{\|H(jn\omega_s)\|}{n}$$

# Subharmonic modes of SRC

 


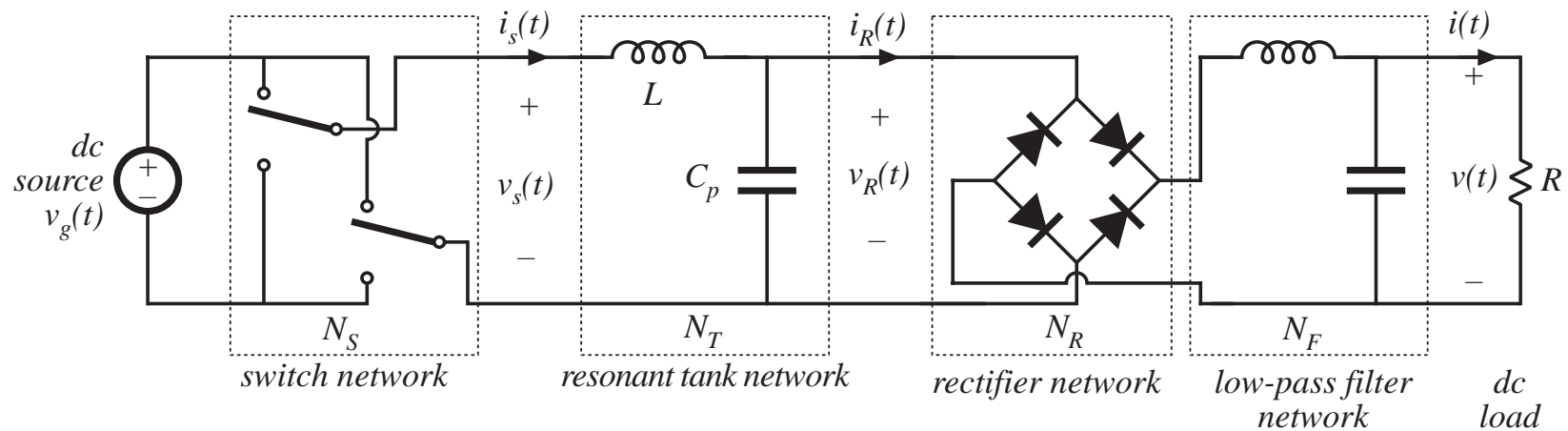
## 19.2.3 Parallel resonant dc-dc converter






Differs from series resonant converter as follows:

- Different tank network

- Rectifier is driven by sinusoidal voltage, and is connected to inductive-input low-pass filter

- Need a new model for rectifier and filter networks
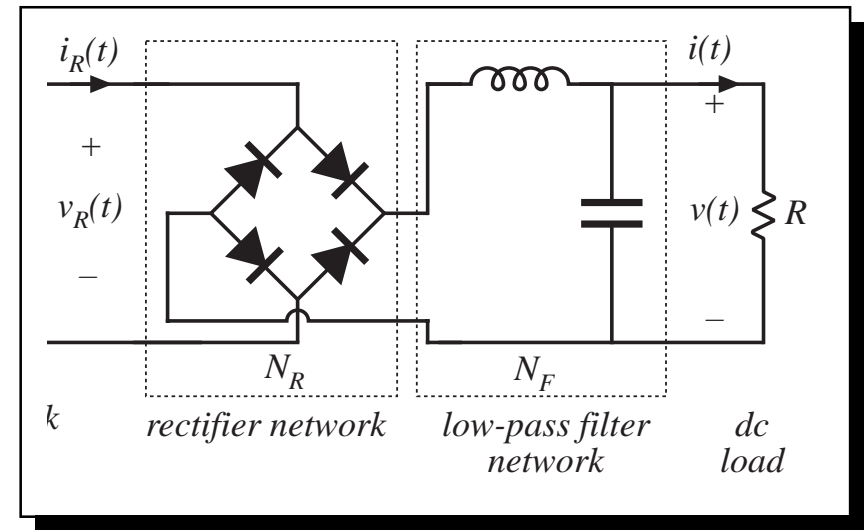  
# Model of uncontrolled rectifier with inductive filter network



Fundamental component of  $i_R(t)$ :

$$i_{R1}(t) = \frac{4I}{\pi} \sin (\omega_s t - \phi_R)$$

## Effective resistance $R_e$

---

Again define

$$R_e = \frac{v_{R1}(t)}{i_{R1}(t)} = \frac{\pi V_{R1}}{4I}$$

In steady state, the dc output voltage  $V$  is equal to the average value of  $|v_R|$ :


$$V = \frac{2}{T_s} \int_0^{T_s/2} V_{R1} \left| \sin(\omega_s t - \phi_R) \right| dt = \frac{2}{\pi} V_{R1}$$

For a resistive load,  $V = IR$ . The effective resistance  $R_e$  can then be expressed

$$R_e = \frac{\pi^2}{8} R = 1.2337R$$


## Equivalent circuit model of uncontrolled rectifier with inductive filter network

---

 

# Equivalent circuit model

## Parallel resonant dc-dc converter

 


$$M = \frac{V}{V_g} = \frac{8}{\pi^2} \| H(s) \|_{s=j\omega_s}$$


$$H(s) = \frac{Z_o(s)}{sL}$$

$$Z_o(s) = sL \parallel \frac{1}{sC} \parallel R_e$$

# Construction of $Z_o$

 

# Construction of $H$

 

## Dc conversion ratio of the PRC

---

$$\begin{aligned} M &= \frac{8}{\pi^2} \left\| \frac{Z_o(s)}{sL} \right\|_{s=j\omega_s} = \frac{8}{\pi^2} \left\| \frac{1}{1 + \frac{s}{Q_e \omega_0} + \left(\frac{s}{\omega_0}\right)^2} \right\|_{s=j\omega_s} \\ &= \frac{8}{\pi^2} \frac{1}{\sqrt{(1 - F^2)^2 + \left(\frac{F}{Q_e}\right)^2}} \end{aligned}$$

At resonance, this becomes

$$M = \frac{8}{\pi^2} \frac{R_e}{R_0} = \frac{R}{R_0}$$

- PRC can step up the voltage, provided  $R > R_0$
- PRC can produce  $M$  approaching infinity, provided output current is limited to value less than  $V_g / R_0$




## 19.3 Exact characteristics of the series and parallel resonant dc-dc converters


Define

$$\frac{f_0}{k+1} < f_s < \frac{f_0}{k} \quad \text{or} \quad \frac{1}{k+1} < F < \frac{1}{k} \quad \text{mode index } k$$
 
$$\xi = k + \frac{1 + (-1)^k}{2} \quad \text{subharmonic index } \xi$$


 
## 19.3.1 Exact characteristics of the series resonant converter



Normalized load voltage and current:

$$M = \frac{V}{nV_g} \qquad J = \frac{InR_0}{V_g}$$


---

### Waveforms for type $k$ CCM, odd $k$ :


 
# Series resonant converter

Waveforms for type  $k$  CCM, even  $k$  :



# Exact steady-state solution, CCM

## Series resonant converter

---

$$M^2 \xi^2 \sin^2 \left( \frac{\gamma}{2} \right) + \frac{1}{\xi^2} \left( \frac{J\gamma}{2} + (-1)^k \right)^2 \cos^2 \left( \frac{\gamma}{2} \right) = 1$$

where

$$M = \frac{V}{nV_g} \quad J = \frac{InR_0}{V_g}$$

$$\gamma = \frac{\omega_0 T_s}{2} = \frac{\pi}{F}$$

- Output characteristic, i.e., the relation between  $M$  and  $J$ , is elliptical
- $M$  is restricted to the range

$$0 \leq M \leq \frac{1}{\xi}$$

# Control-plane characteristics

---


For a resistive load, eliminate  $J$  and solve for  $M$  vs.  $\gamma$

$$M = \frac{\left(\frac{Q\gamma}{2}\right)}{\xi^4 \tan^2\left(\frac{\gamma}{2}\right) + \left(\frac{Q\gamma}{2}\right)^2} \left[ (-1)^{k+1} + \sqrt{1 + \frac{\left[\xi^2 - \cos^2\left(\frac{\gamma}{2}\right)\right] \left[\xi^4 \tan^2\left(\frac{\gamma}{2}\right) + \left(\frac{Q\gamma}{2}\right)^2\right]}{\left(\frac{Q\gamma}{2}\right)^2 \cos^2\left(\frac{\gamma}{2}\right)}} \right]$$

Exact, closed-form, valid for any CCM
 
# Discontinuous conduction mode

Type  $k$  DCM: during each half-switching-period, the tank rings for  $k$  complete half-cycles. The output diodes then become reverse-biased for the remainder of the half-switching-period.



## Steady-state solution: type $k$ DCM, odd $k$

---

$$M = \frac{1}{k}$$

Conditions for operation in type  $k$  DCM, odd  $k$  :

$$f_s < \frac{f_0}{k}$$

$$\frac{2(k+1)}{\gamma} > J > \frac{2(k-1)}{\gamma}$$



## Steady-state solution: type $k$ DCM, even $k$


$$J = \frac{2k}{\gamma}$$

Conditions for operation in type  $k$  DCM, even  $k$  :


$$f_s < \frac{f_0}{k}$$

$$\frac{1}{k-1} > M > \frac{1}{k+1}$$

 
*gyrator model, SRC  
operating in an even  
DCM:*




# Control plane characteristics, SRC

 


# Mode boundaries, SRC

 

 
# Output characteristics, SRC above resonance


 
# Output characteristics, SRC below resonance


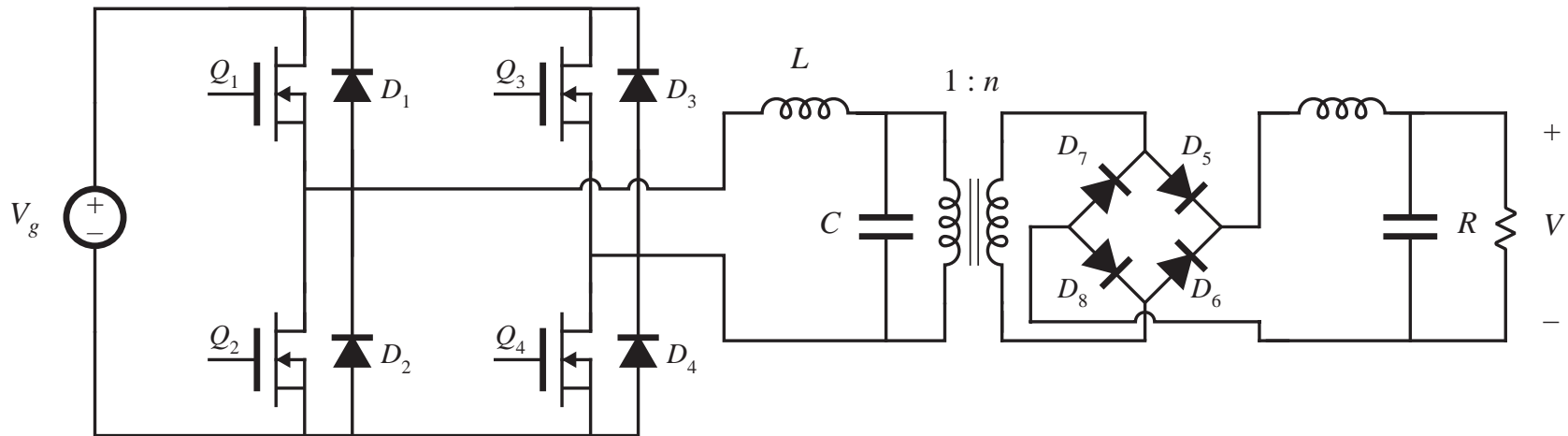
## 19.3.2 Exact characteristics of the parallel resonant converter



Normalized load voltage and current:

$$M = \frac{V}{nV_g}$$


$$J = \frac{InR_0}{V_g}$$

# Parallel resonant converter in CCM

*CCM closed-form solution*

$$M = \left(\frac{2}{\gamma}\right) \left( \phi - \frac{\sin(\phi)}{\cos\left(\frac{\gamma}{2}\right)} \right)$$
 
$$\phi = \begin{cases} -\cos^{-1} \left( \cos\left(\frac{\gamma}{2}\right) + J \sin\left(\frac{\gamma}{2}\right) \right) & \text{for } 0 < \gamma < \pi \\ +\cos^{-1} \left( \cos\left(\frac{\gamma}{2}\right) + J \sin\left(\frac{\gamma}{2}\right) \right) & \text{for } \pi < \gamma < 2\pi \end{cases}$$



# Parallel resonant converter in DCM

## Mode boundary

$$J > J_{crit}(\gamma) \quad \text{for DCM}$$

$$J < J_{crit}(\gamma) \quad \text{for CCM}$$

$$J_{crit}(\gamma) = -\frac{1}{2} \sin(\gamma) + \sqrt{\sin^2\left(\frac{\gamma}{2}\right) + \frac{1}{4} \sin^2(\gamma)}$$

## DCM equations

$$M_{C0} = 1 - \cos(\beta)$$

$$J_{L0} = J + \sin(\beta)$$


$$\cos(\alpha + \beta) - 2 \cos(\alpha) = -1$$

$$-\sin(\alpha + \beta) + 2 \sin(\alpha) + (\delta - \alpha) = 2J$$

$$\beta + \delta = \gamma$$


$$M = 1 + \left(\frac{2}{\gamma}\right)(J - \delta)$$

(require iteration)

 




# Output characteristics of the PRC

 

Solid curves: CCM

Shaded curves: DCM
 
# Control characteristics of the PRC with resistive load



## 19.4 Soft switching

---

Soft switching can mitigate some of the mechanisms of switching loss and possibly reduce the generation of EMI

Semiconductor devices are switched on or off at the zero crossing of their voltage or current waveforms:

*Zero-current switching:* transistor turn-off transition occurs at zero current. Zero-current switching eliminates the switching loss caused by IGBT current tailing and by stray inductances. It can also be used to commutate SCR's.


*Zero-voltage switching:* transistor turn-on transition occurs at zero voltage. Diodes may also operate with zero-voltage switching. Zero-voltage switching eliminates the switching loss induced by diode stored charge and device output capacitances.

Zero-voltage switching is usually preferred in modern converters.

*Zero-voltage transition converters* are modified PWM converters, in which an inductor charges and discharges the device capacitances. Zero-voltage switching is then obtained.

## 19.4.1 Operation of the full bridge below resonance: Zero-current switching

*Series resonant converter example*

 

Operation below resonance: input tank current leads voltage


Zero-current switching (ZCS) occurs

# Tank input impedance

*Operation below resonance:* tank input impedance  $Z_i$  is dominated by tank capacitor.



$\angle Z_i$  is positive, and tank input current leads tank input voltage.

 Zero crossing of the tank input current waveform  $i_s(t)$  occurs before the zero crossing of the voltage  $v_s(t)$ .



# Switch network waveforms, below resonance



## Zero-current switching

  

Conduction sequence:  $Q_1-D_1-Q_2-D_2$

$Q_1$  is turned off during  $D_1$  conduction interval, without loss


# ZCS turn-on transition: hard switching

  

$Q_1$  turns on while  $D_2$  is conducting. Stored charge of  $D_2$  and of semiconductor output capacitances must be removed. Transistor turn-on transition is identical to hard-switched PWM, and switching loss occurs.

## 19.4.2 Operation of the full bridge below resonance: Zero-voltage switching

*Series resonant converter example*

 

Operation above resonance: input tank current lags voltage

Zero-voltage switching (ZVS) occurs




# Tank input impedance

*Operation above resonance:* tank input impedance  $Z_i$  is dominated by tank inductor.



$\angle Z_i$  is negative, and tank input current lags tank input voltage.

 Zero crossing of the tank input current waveform  $i_s(t)$  occurs after the zero crossing of the voltage  $v_s(t)$ .



# Switch network waveforms, above resonance



## Zero-voltage switching

  

Conduction sequence:  $D_1$ – $Q_1$ – $D_2$ – $Q_2$


$Q_1$  is turned on during  $D_1$  conduction interval, without loss
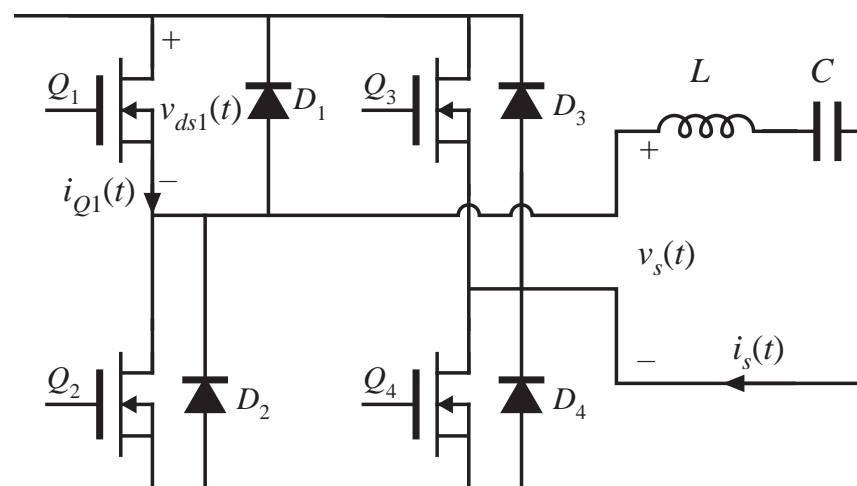 
# ZVS turn-off transition: hard switching?




When  $Q_1$  turns off,  $D_2$  must begin conducting. Voltage across  $Q_1$  must increase to  $V_g$ . Transistor turn-off transition is identical to hard-switched PWM. Switching loss may occur (but see next slide).
 
# Soft switching at the ZVS turn-off transition



 - Introduce small capacitors  $C_{leg}$  across each device (or use device output capacitances).
- Introduce delay between turn-off of  $Q_1$  and turn-on of  $Q_2$ .




Tank current  $i_s(t)$  charges and discharges  $C_{leg}$ . Turn-off transition becomes lossless. During commutation interval, no devices conduct.


So zero-voltage switching exhibits low switching loss: losses due to diode stored charge and device output capacitances are eliminated.
 
## 19.4.3 The zero-voltage transition converter

*Basic version based on full-bridge PWM buck converter*



 - Can obtain ZVS of all primary-side MOSFETs and diodes
- Secondary-side diodes switch at zero-current, with loss
- Phase-shift control



## 19.5 Load-dependent properties of resonant converters

---

### **Resonant inverter design objectives:**

1. Operate with a specified load characteristic and range of operating points
  - With a nonlinear load, must properly match inverter output characteristic to load characteristic
2. Obtain zero-voltage switching or zero-current switching
  - Preferably, obtain these properties at all loads
  - Could allow ZVS property to be lost at light load, if necessary
3. Minimize transistor currents and conduction losses
  - To obtain good efficiency at light load, the transistor current should scale proportionally to load current (in resonant converters, it often doesn't!)

# Topics of Discussion

## Section 19.5

---

Inverter output  $i$ - $v$  characteristics

Two theorems

- Dependence of transistor current on load current
- Dependence of zero-voltage/zero-current switching on load resistance
- Simple, intuitive frequency-domain approach to design of resonant converter

Examples and interpretation

- Series
- Parallel
- LCC

# Inverter output characteristics

Let  $H_\infty$  be the open-circuit ( $R \rightarrow \infty$ ) transfer function:

$$\left. \frac{v_o(j\omega)}{v_i(j\omega)} \right|_{R \rightarrow \infty} = H_\infty(j\omega)$$


and let  $Z_{o0}$  be the output impedance (with  $v_i \rightarrow$  short-circuit). Then,

$$v_o(j\omega) = H_\infty(j\omega) v_i(j\omega) \frac{R}{R + Z_{o0}(j\omega)}$$

The output voltage magnitude is:

$$\|v_o\|^2 = v_o v_o^* = \frac{\|H_\infty\|^2 \|v_i\|^2}{\left(1 + \|Z_{o0}\|^2 / R^2\right)}$$

with  $R = \|v_o\| / \|i_o\|$

 

This result can be rearranged to obtain

$$\|v_o\|^2 + \|i_o\|^2 \|Z_{o0}\|^2 = \|H_\infty\|^2 \|v_i\|^2$$

Hence, at a given frequency, the output characteristic (i.e., the relation between  $\|v_o\|$  and  $\|i_o\|$ ) of any resonant inverter of this class is elliptical.




# Inverter output characteristics

General resonant inverter output characteristics are elliptical, of the form

$$\frac{\|v_o\|^2}{V_{oc}^2} + \frac{\|i_o\|^2}{I_{sc}^2} = 1$$

with  $V_{oc} = \|H_\infty\| \|v_i\|$


$$I_{sc} = \frac{\|H_\infty\| \|v_i\|}{\|Z_{o0}\|}$$

 


This result is valid provided that (i) the resonant network is purely reactive, and (ii) the load is purely resistive.

# Matching ellipse to application requirements

*Electronic ballast*

 


*Electrosurgical generator*

 
 
# Input impedance of the resonant tank network

$$Z_i(s) = Z_{i0}(s) \frac{1 + \frac{R}{Z_{o0}(s)}}{1 + \frac{R}{Z_{o\infty}(s)}} = Z_{i\infty}(s) \frac{1 + \frac{Z_{o0}(s)}{R}}{1 + \frac{Z_{o\infty}(s)}{R}}$$



where

$$Z_{i0} = \left. \frac{v_i}{i_i} \right|_{R \rightarrow 0}$$

$$Z_{i\infty} = \left. \frac{v_i}{i_i} \right|_{R \rightarrow \infty}$$

$$Z_{o0} = \left. \frac{v_o}{-i_o} \right|_{v_i \rightarrow \text{short circuit}}$$

$$Z_{o\infty} = \left. \frac{v_o}{-i_o} \right|_{v_i \rightarrow \text{open circuit}}$$

# Other relations

Reciprocity

$$\frac{Z_{i0}}{Z_{i\infty}} = \frac{Z_{o0}}{Z_{o\infty}}$$

Tank transfer function

$$H(s) = \frac{H_{\infty}(s)}{1 + \frac{R}{Z_{o0}}}$$

where  $H_{\infty} = \left. \frac{v_o(s)}{v_i(s)} \right|_{R \rightarrow \infty}$

$$\|H_{\infty}\|^2 = Z_{o0} \left( \frac{1}{Z_{i0}} - \frac{1}{Z_{i\infty}} \right)$$

If the tank network is purely reactive, then each of its impedances and transfer functions have zero real parts:

$$Z_{i0} = -Z_{i0}^*$$

$$Z_{i\infty} = -Z_{i\infty}^*$$

$$Z_{o0} = -Z_{o0}^*$$



$$Z_{o\infty} = -Z_{o\infty}^*$$

$$H_{\infty} = -H_{\infty}^*$$

Hence, the input impedance magnitude is



$$\|Z_i\|^2 = Z_i Z_i^* = \|Z_{i0}\|^2 \frac{\left(1 + \frac{R^2}{\|Z_{o0}\|^2}\right)}{\left(1 + \frac{R^2}{\|Z_{o\infty}\|^2}\right)}$$
  
# $Z_{i0}$ and $Z_{i\infty}$ for 3 common inverters





$$Z_{i0}(s) = sL + \frac{1}{sC_s}$$

$$Z_{i\infty}(s) = \infty$$

  

$$Z_{i0}(s) = sL$$

$$Z_{i\infty}(s) = sL + \frac{1}{sC_p}$$

  

$$Z_{i0}(s) = sL + \frac{1}{sC_s}$$

$$Z_{i\infty}(s) = sL + \frac{1}{sC_p} + \frac{1}{sC_s}$$

# A Theorem relating transistor current variations to load resistance $R$

---

**Theorem 1:** If the tank network is purely reactive, then its input impedance  $\|Z_i\|$  is a monotonic function of the load resistance  $R$ .

- So as the load resistance  $R$  varies from 0 to  $\infty$ , the resonant network input impedance  $\|Z_i\|$  varies monotonically from the short-circuit value  $\|Z_{i0}\|$  to the open-circuit value  $\|Z_{i\infty}\|$ .
- The impedances  $\|Z_{i\infty}\|$  and  $\|Z_{i0}\|$  are easy to construct.
- If you want to minimize the circulating tank currents at light load, maximize  $\|Z_{i\infty}\|$ .
- Note: for many inverters,  $\|Z_{i\infty}\| < \|Z_{i0}\|$  ! The no-load transistor current is therefore greater than the short-circuit transistor current.

# Proof of Theorem 1

Previously shown:

$$\|Z_i\|^2 = \|Z_{i0}\|^2 \frac{\left(1 + \frac{R}{\|Z_{o0}\|^2}\right)}{\left(1 + \frac{R}{\|Z_{o\infty}\|^2}\right)}$$

➔ Differentiate:

$$\frac{d\|Z_i\|^2}{dR} = 2\|Z_{i0}\|^2 \frac{\left(\frac{1}{\|Z_{o0}\|^2} - \frac{1}{\|Z_{o\infty}\|^2}\right)R}{\left(1 + \frac{R^2}{\|Z_{o\infty}\|^2}\right)^2}$$

➔ Derivative has roots at:


- (i)  $R = 0$
- (ii)  $R = \infty$
- (iii)  $\|Z_{o0}\| = \|Z_{o\infty}\|$ , or  $\|Z_{i0}\| = \|Z_{i\infty}\|$

*So the resonant network input impedance is a monotonic function of  $R$ , over the range  $0 < R < \infty$ .*

*In the special case  $\|Z_{i0}\| = \|Z_{i\infty}\|$ ,  $\|Z_i\|$  is independent of  $R$ .*

## Example: $\|Z_i\|$ of LCC

- for  $f < f_m$ ,  $\|Z_i\|$  increases with increasing  $R$ .
- for  $f > f_m$ ,  $\|Z_i\|$  decreases with increasing  $R$ .
- at a given frequency  $f$ ,  $\|Z_i\|$  is a monotonic function of  $R$ .
- It's not necessary to draw the entire plot: just construct  $\|Z_{i0}\|$  and  $\|Z_{i\infty}\|$ .

 



# Discussion: LCC

$\parallel Z_{i0} \parallel$  and  $\parallel Z_{i\infty} \parallel$  both represent series resonant impedances, whose Bode diagrams are easily constructed.


$\parallel Z_{i0} \parallel$  and  $\parallel Z_{i\infty} \parallel$  intersect at frequency  $f_m$ .

**For  $f < f_m$**







then  $\parallel Z_{i0} \parallel < \parallel Z_{i\infty} \parallel$ ; hence transistor current decreases as load current decreases

 **For  $f > f_m$**

then  $\parallel Z_{i0} \parallel > \parallel Z_{i\infty} \parallel$ ; hence transistor current increases as load current decreases, and transistor current is greater than or equal to short-circuit current for all  $R$



# Discussion -series and parallel

      

- No-load transistor current = 0, both above and below resonance.
- ZCS below resonance, ZVS above resonance
- Above resonance: no-load transistor current is *greater* than short-circuit transistor current. ZVS.
- Below resonance: no-load transistor current is less than short-circuit current (for  $f < f_m$ ), but determined by  $\|Z_{i\infty}\|$ . ZCS.

# A Theorem relating the ZVS / ZCS boundary to load resistance $R$

---

**Theorem 2:** If the tank network is purely reactive, then the boundary between zero-current switching and zero-voltage switching occurs when the load resistance  $R$  is equal to the critical value  $R_{crit}$ , given by

$$R_{crit} = \| Z_{o0} \| \sqrt{\frac{-Z_{i\infty}}{Z_{i0}}}$$

It is assumed that zero-current switching (ZCS) occurs when the tank input impedance is capacitive in nature, while zero-voltage switching (ZVS) occurs when the tank is inductive in nature. This assumption gives a necessary but not sufficient condition for ZVS when significant semiconductor output capacitance is present.

## Proof of Theorem 2

Previously shown:

$$Z_i = Z_{i\infty} \frac{1 + \frac{Z_{o0}}{R}}{1 + \frac{Z_{o\infty}}{R}}$$

If ZCS occurs when  $Z_i$  is capacitive, while ZVS occurs when  $Z_i$  is inductive, then the boundary is determined by  $\angle Z_i = 0$ . Hence, the critical load  $R_{crit}$  is the resistance which causes the imaginary part of  $Z_i$  to be zero:

$$\text{Im}(Z_i(R_{crit})) = 0$$

Note that  $Z_{i\infty}$ ,  $Z_{o0}$ , and  $Z_{o\infty}$  have zero real parts. Hence,

$$\begin{aligned} \text{Im}(Z_i(R_{crit})) &= \text{Im}(Z_{i\infty}) \text{Re} \left( \frac{1 + \frac{Z_{o0}}{R_{crit}}}{1 + \frac{Z_{o\infty}}{R_{crit}}} \right) \\ &= \text{Im}(Z_{i\infty}) \text{Re} \left( \frac{1 - \frac{Z_{o0}Z_{o\infty}}{R_{crit}^2}}{1 + \frac{\|Z_{o\infty}\|^2}{R_{crit}^2}} \right) \end{aligned}$$

Solution for  $R_{crit}$  yields

$$R_{crit} = \|Z_{o0}\| \sqrt{\frac{-Z_{i\infty}}{Z_{i0}}}$$

## Discussion — Theorem 2


---

$$R_{crit} = \|Z_{o0}\| \sqrt{\frac{-Z_{i\infty}}{Z_{i0}}}$$

- Again,  $Z_{i\infty}$ ,  $Z_{i0}$ , and  $Z_{o0}$  are pure imaginary quantities.
- If  $Z_{i\infty}$  and  $Z_{i0}$  have the same phase (both inductive or both capacitive), then there is no real solution for  $R_{crit}$ .
- Hence, if at a given frequency  $Z_{i\infty}$  and  $Z_{i0}$  are both capacitive, then ZCS occurs for all loads. If  $Z_{i\infty}$  and  $Z_{i0}$  are both inductive, then ZVS occurs for all loads.
- If  $Z_{i\infty}$  and  $Z_{i0}$  have opposite phase (one is capacitive and the other is inductive), then there is a real solution for  $R_{crit}$ . The boundary between ZVS and ZCS operation is then given by  $R = R_{crit}$ .
- Note that  $R = \|Z_{o0}\|$  corresponds to operation at matched load with maximum output power. The boundary is expressed in terms of this matched load impedance, and the ratio  $Z_{i\infty} / Z_{i0}$ .


# LCC example

- For  $f > f_\infty$ , ZVS occurs for all  $R$ .
- For  $f < f_0$ , ZCS occurs for all  $R$ .
- For  $f_0 < f < f_\infty$ , ZVS occurs for  $R < R_{crit}$ , and ZCS occurs for  $R > R_{crit}$ .
- Note that  $R = \|Z_{o0}\|$  corresponds to operation at matched load with maximum output power. The boundary is expressed in terms of this matched load impedance, and the ratio  $Z_{i\infty} / Z_{i0}$ .

 


$$R_{crit} = \|Z_{o0}\| \sqrt{\frac{-Z_{i\infty}}{Z_{i0}}}$$

# LCC example, continued

 

Typical dependence of  $R_{crit}$  and matched-load impedance  $\|Z_{00}\|$  on frequency  $f$ , LCC example.

 

Typical dependence of tank input impedance phase vs. load  $R$  and frequency, LCC example.

## 19.6 Summary of Key Points

---

1. The sinusoidal approximation allows a great deal of insight to be gained into the operation of resonant inverters and dc–dc converters. The voltage conversion ratio of dc–dc resonant converters can be directly related to the tank network transfer function. Other important converter properties, such as the output characteristics, dependence (or lack thereof) of transistor current on load current, and zero-voltage- and zero-current-switching transitions, can also be understood using this approximation. The approximation is accurate provided that the effective  $Q$ -factor is sufficiently large, and provided that the switching frequency is sufficiently close to resonance.
2. Simple equivalent circuits are derived, which represent the fundamental components of the tank network waveforms, and the dc components of the dc terminal waveforms.



## Summary of key points

---

3. Exact solutions of the ideal dc–dc series and parallel resonant converters are listed here as well. These solutions correctly predict the conversion ratios, for operation not only in the fundamental continuous conduction mode, but in discontinuous and subharmonic modes as well.
4. Zero-voltage switching mitigates the switching loss caused by diode recovered charge and semiconductor device output capacitances. When the objective is to minimize switching loss and EMI, it is preferable to operate each MOSFET and diode with zero-voltage switching.
5. Zero-current switching leads to natural commutation of SCRs, and can also mitigate the switching loss due to current tailing in IGBTs.

## Summary of key points

---

6. The input impedance magnitude  $\|Z_i\|$ , and hence also the transistor current magnitude, are monotonic functions of the load resistance  $R$ . The dependence of the transistor conduction loss on the load current can be easily understood by simply plotting  $\|Z_i\|$  in the limiting cases as  $R \rightarrow \infty$  and as  $R \rightarrow 0$ , or  $\|Z_{i\infty}\|$  and  $\|Z_{i0}\|$ .
7. The ZVS/ZCS boundary is also a simple function of  $Z_{i\infty}$  and  $Z_{i0}$ . If ZVS occurs at open-circuit and at short-circuit, then ZVS occurs for all loads. If ZVS occurs at short-circuit, and ZCS occurs at open-circuit, then ZVS is obtained at matched load provided that  $\|Z_{i\infty}\| > \|Z_{i0}\|$ .
8. The output characteristics of all resonant inverters considered here are elliptical, and are described completely by the open-circuit transfer function magnitude  $\|H_\infty\|$ , and the output impedance  $\|Z_{o0}\|$ . These quantities can be chosen to match the output characteristics to the application requirements.

# Chapter 20

## Quasi-Resonant Converters

---

### Introduction

#### 20.1 The zero-current-switching quasi-resonant switch cell

20.1.1 Waveforms of the half-wave ZCS quasi-resonant switch cell

20.1.2 The average terminal waveforms

20.1.3 The full-wave ZCS quasi-resonant switch cell

#### 20.2 Resonant switch topologies

20.2.1 The zero-voltage-switching quasi-resonant switch

20.2.2 The zero-voltage-switching multiresonant switch

20.2.3 Quasi-square-wave resonant switches

#### 20.3 Ac modeling of quasi-resonant converters



#### 20.4 Summary of key points

# The resonant switch concept



A quite general idea:

1. PWM switch network is replaced by a resonant switch network
2. This leads to a quasi-resonant version of the original PWM converter

  *Example:* realization of the switch cell in the buck converter




# Two quasi-resonant switch cells

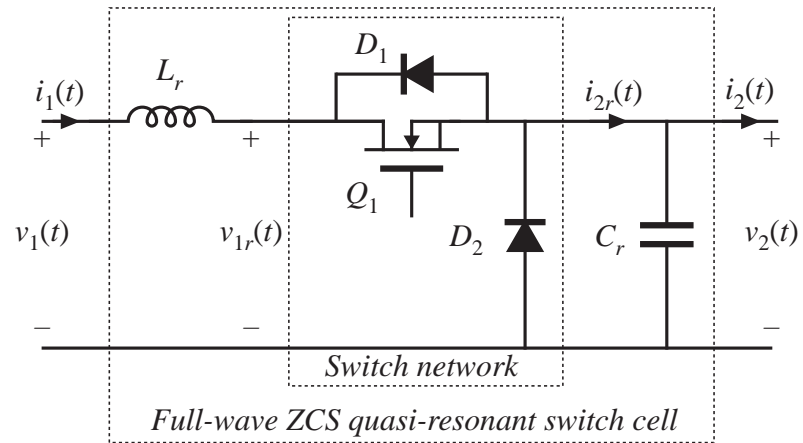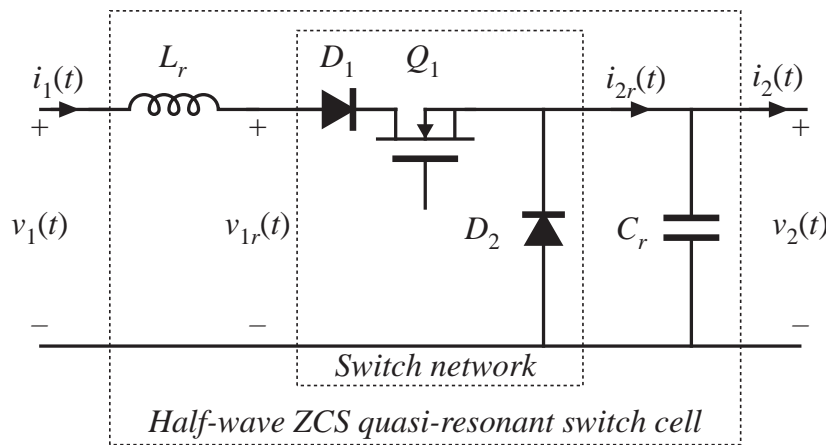

Insert either of the above switch cells into the buck converter, to obtain a ZCS quasi-resonant version of the buck converter.  $L_r$  and  $C_r$  are small in value, and their resonant frequency  $f_0$  is greater than the switching frequency  $f_s$ .
 
$$f_0 = \frac{1}{2\pi \sqrt{L_r C_r}} = \frac{\omega_0}{2\pi}$$



## 20.1 The zero-current-switching quasi-resonant switch cell

Tank inductor  $L_r$  in series with transistor:  
transistor switches at zero crossings of inductor  
current waveform



Tank capacitor  $C_r$  in parallel with diode  $D_2$  : diode  
switches at zero crossings of capacitor voltage  
waveform

Two-quadrant switch is required:

*Half-wave:*  $Q_1$  and  $D_1$  in series, transistor  
turns off at first zero crossing of current  
waveform

*Full-wave:*  $Q_1$  and  $D_1$  in parallel, transistor  
turns off at second zero crossing of current  
waveform

  Performances of half-wave and full-wave cells  
differ significantly.



# Averaged switch modeling of ZCS cells

---

It is assumed that the converter filter elements are large, such that their switching ripples are small. Hence, we can make the small ripple approximation as usual, for these elements:

$$i_2(t) \approx \langle i_2(t) \rangle_{T_s}$$
$$v_1(t) \approx \langle v_1(t) \rangle_{T_s}$$

In steady state, we can further approximate these quantities by their dc values:

$$i_2(t) \approx I_2$$
$$v_1(t) \approx V_1$$

Modeling objective: find the average values of the terminal waveforms

$$\langle v_2(t) \rangle_{T_s} \text{ and } \langle i_1(t) \rangle_{T_s}$$


# The switch conversion ratio $\mu$

A generalization of the duty cycle  $d(t)$

The switch conversion ratio  $\mu$  is the ratio of the average terminal voltages of the switch network. It can be applied to non-PWM switch networks. For the CCM PWM case,  $\mu = d$ .

If  $V/V_g = M(d)$  for a PWM CCM converter, then  $V/V_g = M(\mu)$  for the same converter with a switch network having conversion ratio  $\mu$ .

 Generalized switch averaging, and  $\mu$ , are defined and discussed in Section 10.3.



$$\begin{aligned} i_2(t) &\approx \langle i_2(t) \rangle_{T_s} \\ v_1(t) &\approx \langle v_1(t) \rangle_{T_s} \end{aligned} \quad \mu = \frac{\langle v_2(t) \rangle_{T_s}}{\langle v_{1r}(t) \rangle_{T_s}} = \frac{\langle i_1(t) \rangle_{T_s}}{\langle i_2(t) \rangle_{T_s}}$$


In steady state:

$$\begin{aligned} i_2(t) &\approx I_2 \\ v_1(t) &\approx V_1 \end{aligned} \quad \mu = \frac{V_2}{V_1} = \frac{I_1}{I_2}$$



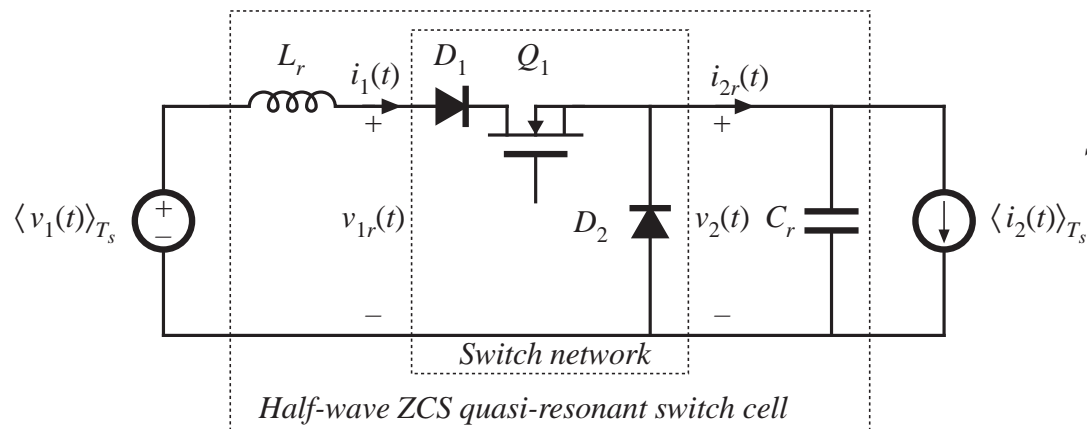
## 20.1.1 Waveforms of the half-wave ZCS quasi-resonant switch cell

The half-wave ZCS quasi-resonant switch cell, driven by the terminal quantities  $\langle v_1(t) \rangle_{T_s}$  and  $\langle i_2(t) \rangle_{T_s}$ .




Each switching period contains four subintervals

Waveforms:

 
 
# Subinterval 1

Diode  $D_2$  is initially conducting the filter inductor current  $I_2$ . Transistor  $Q_1$  turns on, and the tank inductor current  $i_1$  starts to increase. So all semiconductor devices conduct during this subinterval, and the circuit reduces to:



Circuit equations:

$$\frac{di_1(t)}{dt} = \frac{V_1}{L_r} \quad \text{with } i_1(0) = 0$$

Solution:  $i_1(t) = \frac{V_1}{L_r} t = \omega_0 t \frac{V_1}{R_0}$


where  $R_0 = \sqrt{\frac{L_r}{C_r}}$

This subinterval ends when diode  $D_2$  becomes reverse-biased. This occurs at time  $\omega_0 t = \alpha$ , when  $i_1(t) = I_2$ .

$$i_1(\alpha) = \alpha \frac{V_1}{R_0} = I_2 \quad \alpha = \frac{I_2 R_0}{V_1}$$
 
## Subinterval 2

Diode  $D_2$  is off. Transistor  $Q_1$  conducts, and the tank inductor and tank capacitor ring sinusoidally. The circuit reduces to:



The circuit equations are

$$L_r \frac{di_1(\omega_0 t)}{dt} = V_1 - v_2(\omega_0 t) \quad v_2(\alpha) = 0$$

$$C_r \frac{dv_2(\omega_0 t)}{dt} = i_1(\omega_0 t) - I_2 \quad i_1(\alpha) = I_2$$

The solution is

$$i_1(\omega_0 t) = I_2 + \frac{V_1}{R_0} \sin(\omega_0 t - \alpha)$$

$$v_2(\omega_0 t) = V_1 \left( 1 - \cos(\omega_0 t - \alpha) \right)$$

The dc components of these waveforms are the dc solution of the circuit, while the sinusoidal components have magnitudes that depend on the initial conditions and on the characteristic impedance  $R_0$ .

## Subinterval 2 continued

Peak inductor current:

$$I_{1pk} = I_2 + \frac{V_1}{R_0}$$

$$i_1(\omega_0 t) = I_2 + \frac{V_1}{R_0} \sin(\omega_0 t - \alpha)$$


$$v_2(\omega_0 t) = V_1 \left( 1 - \cos(\omega_0 t - \alpha) \right)$$

This subinterval ends at the first zero crossing of  $i_1(t)$ . Define  $\beta$  = angular length of subinterval 2. Then

$$i_1(\alpha + \beta) = I_2 + \frac{V_1}{R_0} \sin(\beta) = 0$$

$$\sin(\beta) = -\frac{I_2 R_0}{V_1}$$

 Must use care to select the correct branch of the arcsine function. Note (from the  $i_1(t)$  waveform) that  $\beta > \pi$ .



Hence

$$\beta = \pi + \sin^{-1} \left( \frac{I_2 R_0}{V_1} \right)$$

$$-\frac{\pi}{2} < \sin^{-1}(x) \leq \frac{\pi}{2}$$

$$I_2 < \frac{V_1}{R_0}$$

# Boundary of zero current switching

---

If the requirement

$$I_2 < \frac{V_1}{R_0}$$

is violated, then the inductor current never reaches zero. In consequence, the transistor cannot switch off at zero current.


The resonant switch operates with zero current switching only for load currents less than the above value. The characteristic impedance must be sufficiently small, so that the ringing component of the current is greater than the dc load current.

Capacitor voltage at the end of subinterval 2 is

$$v_2(\alpha + \beta) = V_{c1} = V_1 \left( 1 + \sqrt{1 - \left( \frac{I_2 R_0}{V_1} \right)^2} \right)$$
 
## Subinterval 3

All semiconductor devices are off. The circuit reduces to:



The circuit equations are

$$C_r \frac{dv_2(\omega_0 t)}{dt} = -I_2$$

$$v_2(\alpha + \beta) = V_{c1}$$

The solution is

$$v_2(\omega_0 t) = V_{c1} - I_2 R_0 (\omega_0 t - \alpha - \beta)$$

Subinterval 3 ends when the tank capacitor voltage reaches zero, and diode  $D_2$  becomes forward-biased. Define  $\delta$  = angular length of subinterval 3. Then

$$v_2(\alpha + \beta + \delta) = V_{c1} - I_2 R_0 \delta = 0$$

$$\delta = \frac{V_{c1}}{I_2 R_0} = \frac{V_1}{I_2 R_0} \left( 1 - \sqrt{1 - \left( \frac{I_2 R_0}{V_1} \right)^2} \right)$$

## Subinterval 4

---

Subinterval 4, of angular length  $\xi$ , is identical to the diode conduction interval of the conventional PWM switch network.

Diode  $D_2$  conducts the filter inductor current  $I_2$

The tank capacitor voltage  $v_2(t)$  is equal to zero.

Transistor  $Q_1$  is off, and the input current  $i_1(t)$  is equal to zero.

The length of subinterval 4 can be used as a control variable. Increasing the length of this interval reduces the average output voltage.

# Maximum switching frequency

---

The length of the fourth subinterval cannot be negative, and the switching period must be at least long enough for the tank current and voltage to return to zero by the end of the switching period.

The angular length of the switching period is

$$\omega_0 T_s = \alpha + \beta + \delta + \xi = \frac{2\pi f_0}{f_s} = \frac{2\pi}{F}$$

where the normalized switching frequency  $F$  is defined as

$$F = \frac{f_s}{f_0}$$

So the minimum switching period is

$$\omega_0 T_s \geq \alpha + \beta + \delta$$

Substitute previous solutions for subinterval lengths:

$$\frac{2\pi}{F} \geq \frac{I_2 R_0}{V_1} + \pi + \sin^{-1} \left( \frac{I_2 R_0}{V_1} \right) + \frac{V_1}{I_2 R_0} \left( 1 - \sqrt{1 - \left( \frac{I_2 R_0}{V_1} \right)^2} \right)$$





## 20.1.2 The average terminal waveforms

Averaged switch modeling: we need to determine the average values of  $i_1(t)$  and  $v_2(t)$ . The average switch input current is given by

$$\langle i_1(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} i_1(t) dt = \frac{q_1 + q_2}{T_s}$$

$q_1$  and  $q_2$  are the areas under the current waveform during subintervals 1 and 2.  $q_1$  is given by the triangle area formula:
  
$$q_1 = \int_0^{\frac{\alpha}{\omega_0}} i_1(t) dt = \frac{1}{2} \left( \frac{\alpha}{\omega_0} \right) (I_2)$$



# Charge arguments: computation of $q_2$

$$q_2 = \int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} i_1(t) dt$$

Node equation for subinterval 2:



$$i_1(t) = i_c(t) + I_2$$

Substitute:

$$q_2 = \int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} i_c(t) dt + \int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} I_2 dt$$

Second term is integral of constant  $I_2$ :
  
$$\int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} I_2 dt = I_2 \frac{\beta}{\omega_0}$$



*Circuit during subinterval 2*

# Charge arguments


## continued

$$q_2 = \int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} i_c(t) dt + \int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} I_2 dt$$

First term: integral of the capacitor current over subinterval 2. This can be related to the change in capacitor voltage :

$$\int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} i_c(t) dt = C \left( v_2 \left( \frac{\alpha+\beta}{\omega_0} \right) - v_2 \left( \frac{\alpha}{\omega_0} \right) \right)$$
 
$$\int_{\frac{\alpha}{\omega_0}}^{\frac{\alpha+\beta}{\omega_0}} i_c(t) dt = C (V_{c1} - 0) = CV_{c1}$$



Substitute results for the two integrals:

$$q_2 = CV_{c1} + I_2 \frac{\beta}{\omega_0}$$

Substitute into expression for average switch input current:

$$\langle i_1(t) \rangle_{T_s} = \frac{\alpha I_2}{2\omega_0 T_s} + \frac{CV_{c1}}{T_s} + \frac{\beta I_2}{\omega_0 T_s}$$

## Switch conversion ratio $\mu$

---

$$\mu = \frac{\langle i_1(t) \rangle_{T_s}}{I_2} = \frac{\alpha}{2\omega_0 T_s} + \frac{CV_{c1}}{I_2 T_s} + \frac{\beta}{\omega_0 T_s}$$

Eliminate  $\alpha$ ,  $\beta$ ,  $V_{c1}$  using previous results:

$$\mu = F \frac{1}{2\pi} \left[ \frac{1}{2} J_s + \pi + \sin^{-1}(J_s) + \frac{1}{J_s} \left( 1 + \sqrt{1 - J_s^2} \right) \right]$$

where

$$J_s = \frac{I_2 R_0}{V_1}$$

## Analysis result: switch conversion ratio $\mu$


Switch conversion ratio: 
$$\mu = F \frac{1}{2\pi} \left[ \frac{1}{2} J_s + \pi + \sin^{-1}(J_s) + \frac{1}{J_s} \left( 1 + \sqrt{1 - J_s^2} \right) \right]$$

with  $J_s = \frac{I_2 R_0}{V_1}$


This is of the form

$$\mu = F P_{\frac{1}{2}}(J_s)$$
 
$$P_{\frac{1}{2}}(J_s) = \frac{1}{2\pi} \left[ \frac{1}{2} J_s + \pi + \sin^{-1}(J_s) + \frac{1}{J_s} \left( 1 + \sqrt{1 - J_s^2} \right) \right]$$


 
# Characteristics of the half-wave ZCS resonant switch



Switch  
characteristics:

$$\mu = FP_{\frac{1}{2}}(J_s)$$

Mode boundary:

$$J_s \leq 1$$

$$\mu \leq 1 - \frac{J_s F}{4\pi}$$

## Buck converter containing half-wave ZCS quasi-resonant switch

Conversion ratio of the buck converter is (from inductor volt-second balance):

$$M = \frac{V}{V_g} = \mu$$

For the buck converter,


$$J_s = \frac{IR_0}{V_g}$$

ZCS occurs when

$$I \leq \frac{V_g}{R_0}$$

Output voltage varies over the range
 
$$0 \leq V \leq V_g - \frac{FIR_0}{4\pi}$$



# Boost converter example

For the boost converter,

$$M = \frac{V}{V_g} = \frac{1}{1 - \mu}$$


$$J_s = \frac{I_2 R_0}{V_1} = \frac{I_g R_0}{V}$$

$$I_g = \frac{I}{1 - \mu}$$

Half-wave ZCS equations:

$$\mu = FP_{\frac{1}{2}}(J_s)$$


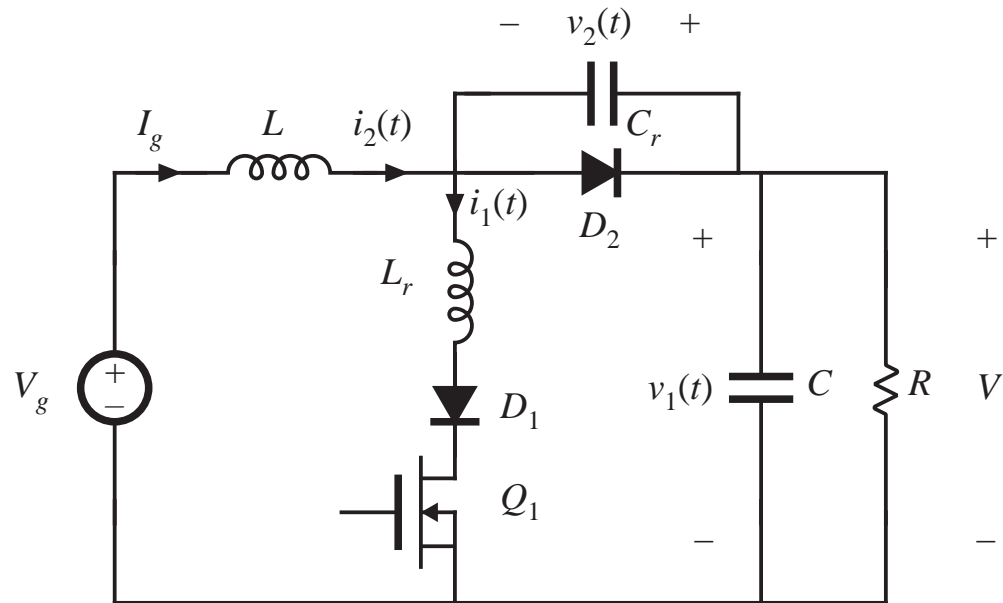
$$P_{\frac{1}{2}}(J_s) = \frac{1}{2\pi} \left[ \frac{1}{2} J_s + \pi + \sin^{-1}(J_s) + \frac{1}{J_s} \left( 1 + \sqrt{1 - J_s^2} \right) \right]$$







## 20.1.3 The full-wave ZCS quasi-resonant switch cell

*Half wave*

  

*Full wave*

 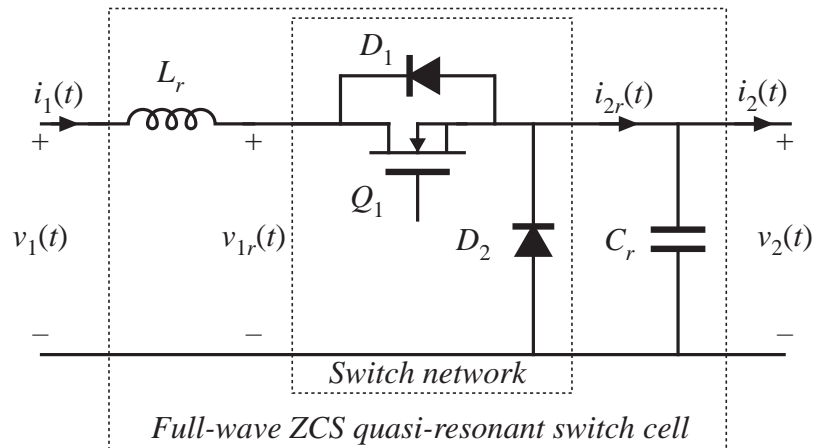

## Analysis: full-wave ZCS

---

Analysis in the full-wave case is nearly the same as in the half-wave case. The second subinterval ends at the second zero crossing of the tank inductor current waveform. The following quantities differ:

$$\beta = \begin{cases} \pi + \sin^{-1}(J_s) & \text{(half wave)} \\ 2\pi - \sin^{-1}(J_s) & \text{(full wave)} \end{cases}$$
$$V_{c1} = \begin{cases} V_1 \left(1 + \sqrt{1 - J_s^2}\right) & \text{(half wave)} \\ V_1 \left(1 - \sqrt{1 - J_s^2}\right) & \text{(full wave)} \end{cases}$$

In either case,  $\mu$  is given by

$$\mu = \frac{\langle i_1(t) \rangle_{T_s}}{I_2} = \frac{\alpha}{2\omega_0 T_s} + \frac{CV_{c1}}{I_2 T_s} + \frac{\beta}{\omega_0 T_s}$$

# Full-wave cell: switch conversion ratio $\mu$

$$P_1(J_s) = \frac{1}{2\pi} \left[ \frac{1}{2} J_s + 2\pi - \sin^{-1}(J_s) + \frac{1}{J_s} \left( 1 - \sqrt{1 - J_s^2} \right) \right]$$


$$\mu = F P_1(J_s)$$

Full-wave case:  $P_1$  can be approximated as

$$P_1(J_s) \approx 1$$


so

$$\mu \approx F = \frac{f_s}{f_0}$$

 

## 20.2 Resonant switch topologies

Basic ZCS switch cell:

 

SPST switch  $SW$ :

- Voltage-bidirectional two-quadrant switch for half-wave cell
- Current-bidirectional two-quadrant switch for full-wave cell

Connection of resonant elements:


Can be connected in other ways that preserve high-frequency components of tank waveforms

# Connection of tank capacitor

Connection of tank capacitor to two other points at ac ground.

This simply changes the dc component of tank capacitor voltage.

 The ac high-frequency components of the tank waveforms are unchanged.




# A test to determine the topology of a resonant switch network

Replace converter elements by their high-frequency equivalents:

- Independent voltage source  $V_g$ : short circuit
- Filter capacitors: short circuits
- Filter inductors: open circuits

The resonant switch network remains.

 
If the converter contains a ZCS quasi-resonant switch, then the result of these operations is



# Zero-current and zero-voltage switching
 
## ZCS quasi-resonant switch:

- Tank inductor is in series with switch; hence  $SW$  switches at zero current
- Tank capacitor is in parallel with diode  $D_2$ ; hence  $D_2$  switches at zero voltage




## Discussion


- Zero voltage switching of  $D_2$  eliminates switching loss arising from  $D_2$  stored charge.
- Zero current switching of  $SW$ : device  $Q_1$  and  $D_1$  output capacitances lead to switching loss. In full-wave case, stored charge of diode  $D_1$  leads to switching loss.
- Peak transistor current is  $(1 + J_s) V_g/R_0$ , or more than twice the PWM value.
 
## 20.2.1 The zero-voltage-switching quasi-resonant switch cell

When the previously-described operations are followed, then the converter reduces to



 A full-wave version based on the PWM buck converter:





# ZVS quasi-resonant switch cell

Switch conversion ratio

$$\mu = 1 - FP_1 \left( \frac{1}{J_s} \right) \quad \text{half-wave}$$

$$\mu = 1 - FP_1 \left( \frac{1}{J_s} \right) \quad \text{full-wave}$$


ZVS boundary

$$J_s \geq 1$$

peak transistor voltage  $V_{cr,pk} = (1 + J_s) V_1$


A problem with the quasi-resonant ZVS switch cell: peak transistor voltage becomes very large when zero voltage switching is required for a large range of load currents.

Tank waveforms

 

 
## 20.2.2 The ZVS multiresonant switch

When the previously-described operations are followed, then the converter reduces to



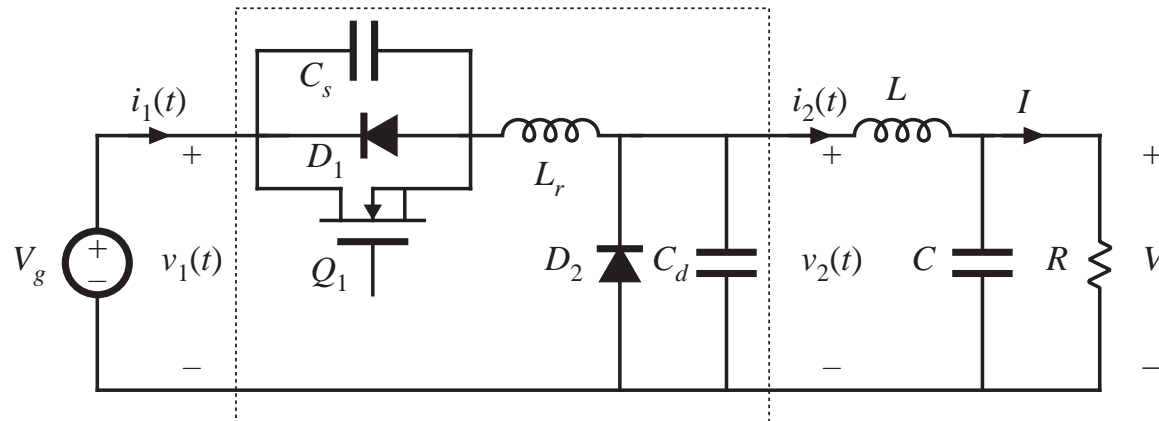
A half-wave version based on the PWM buck converter:




## 20.2.3 Quasi-square-wave resonant switches

When the previously-described operations are followed, then the converter reduces to


ZCS

 

ZVS


 

 
# A quasi-square-wave ZCS buck with input filter



- The basic ZCS QSW switch cell is restricted to  $0 \leq \mu \leq 0.5$
- Peak transistor current is equal to peak transistor current of PWM cell
- Peak transistor voltage is increased
- Zero-current switching in all semiconductor devices

# A quasi-square-wave ZVS buck

  


- The basic ZVS QSW switch cell is restricted to  $0.5 \leq \mu \leq 1$
- Peak transistor voltage is equal to peak transistor voltage of PWM cell
- Peak transistor current is increased
- Zero-voltage switching in all semiconductor devices
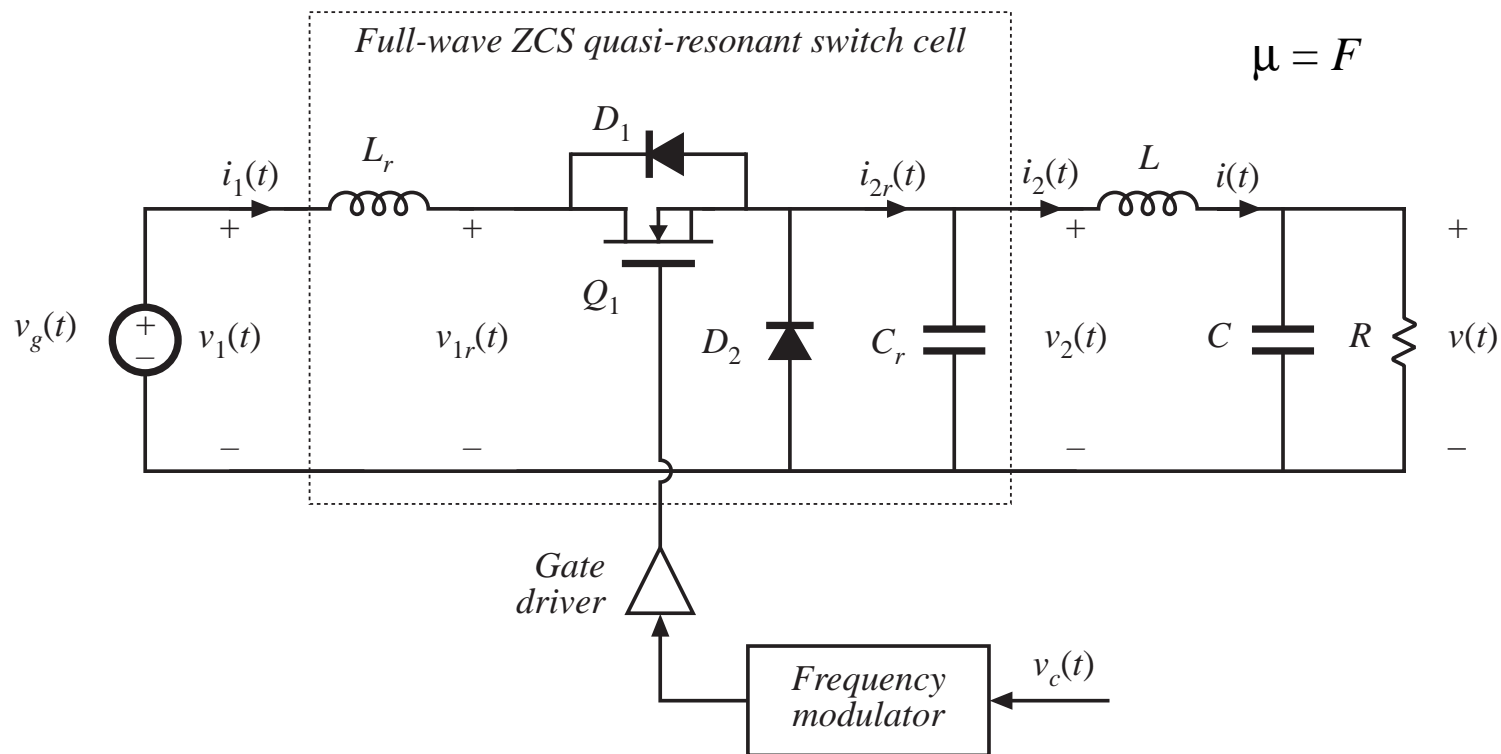
## 20.3 Ac modeling of quasi-resonant converters

Use averaged switch modeling technique: apply averaged PWM model, with  $d$  replaced by  $\mu$

Buck example with full-wave ZCS quasi-resonant cell:



# Small-signal ac model

Averaged switch equations:

$$\langle v_2(t) \rangle_{T_s} = \mu \langle v_{1r}(t) \rangle_{T_s}$$


$$\langle i_1(t) \rangle_{T_s} = \mu \langle i_{2r}(t) \rangle_{T_s}$$

Linearize:

$$\hat{i}_1(t) = \hat{f}_s(t) \frac{I_2}{f_0}$$


$$\hat{v}_2(t) = \frac{F_s}{f_0} \hat{v}_{1r}(t) + \hat{f}_s(t) \frac{V_1}{f_0}$$

Resulting ac model:

 
 
# Low-frequency model

Tank dynamics occur only at frequency near or greater than switching frequency —discard tank elements



—same as PWM buck, with  $d$  replaced by  $F$




## Example 2: Half-wave ZCS quasi-resonant buck

Now,  $\mu$  depends on  $j_s$ :

$$\mu(t) = \frac{f_s(t)}{f_0} P_{\frac{1}{2}}(j_s(t))$$
 
$$j_s(t) = R_0 \frac{\langle i_{2r}(t) \rangle_{T_s}}{\langle v_{1r}(t) \rangle_{T_s}}$$



# Small-signal modeling

Perturbation and linearization of  $\mu(v_{1r}, i_{2r}, f_s)$ :

$$\hat{\mu}(t) = K_v \hat{v}_{1r}(t) + K_i \hat{i}_{2r}(t) + K_c \hat{f}_s(t)$$


with

$$\begin{aligned} K_v &= -\frac{\partial \mu}{\partial j_s} \frac{R_0 I_2}{V_1^2} \\ K_i &= -\frac{\partial \mu}{\partial j_s} \frac{R_0}{V_1} \\ K_c &= \frac{\mu_0}{F_s} \end{aligned} \quad \frac{\partial \mu}{\partial j_s} = \frac{F_s}{2\pi f_0} \left( \frac{1}{2} - \frac{1 + \sqrt{1 - J_s^2}}{J_s^2} \right)$$


Linearized terminal equations of switch network:

$$\begin{aligned} \hat{i}_1(t) &= \hat{\mu}(t) I_2 + \hat{i}_{2r}(t) \mu_0 \\ \hat{v}_2(t) &= \mu_0 \hat{v}_{1r}(t) + \hat{\mu}(t) V_1 \end{aligned}$$

# Equivalent circuit model

 
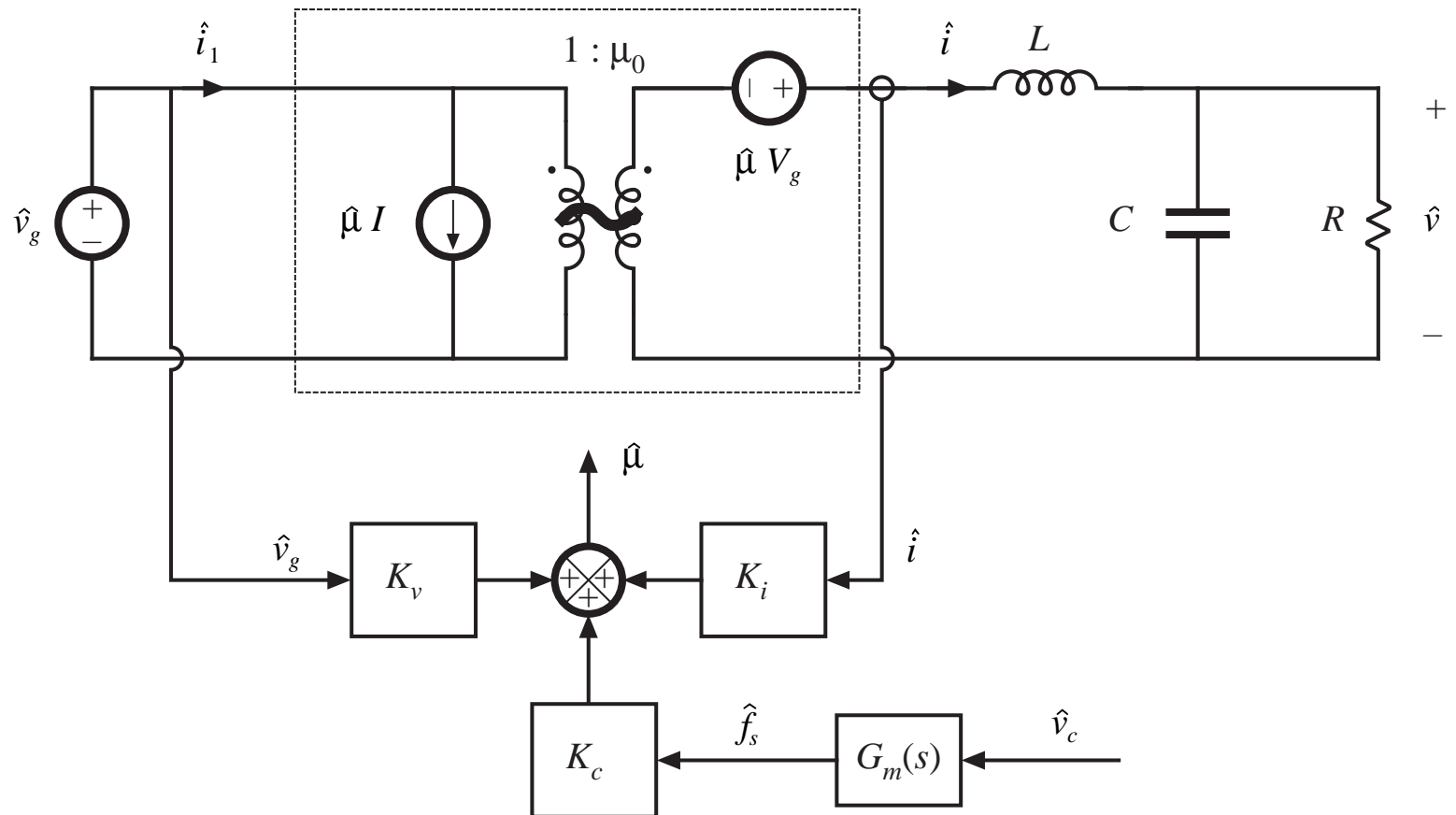
# Low frequency model: set tank elements to zero



# Predicted small-signal transfer functions

## Half-wave ZCS buck

---

$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{1}{Q} \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

$$G_{vc}(s) = G_{c0} \frac{1}{1 + \frac{1}{Q} \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Full-wave: poles and zeroes are same as PWM

Half-wave: effective feedback reduces Q-factor and dc gains

$$G_{g0} = \frac{\mu_0 + K_v V_g}{1 + \frac{K_i V_g}{R}}$$

$$G_{c0} = \frac{K_c V_g}{1 + \frac{K_i V_g}{R}}$$

$$\omega_0 = \sqrt{\frac{1 + \frac{K_i V_g}{R}}{L_r C_r}}$$

$$Q = \frac{\sqrt{1 + \frac{K_i V_g}{R}}}{\frac{R_0}{R} + K_i V_g \frac{R}{R_0}}$$

$$R_0 = \sqrt{\frac{L_r}{C_r}}$$

## 20.4 Summary of key points

---

1. In a resonant switch converter, the switch network of a PWM converter is replaced by a switch network containing resonant elements. The resulting hybrid converter combines the properties of the resonant switch network and the parent PWM converter.
2. Analysis of a resonant switch cell involves determination of the switch conversion ratio  $\mu$ . The resonant switch waveforms are determined, and are then averaged. The switch conversion ratio  $\mu$  is a generalization of the PWM CCM duty cycle  $d$ . The results of the averaged analysis of PWM converters operating in CCM can be directly adapted to the related resonant switch converter, simply by replacing  $d$  with  $\mu$ .
3. In the zero-current-switching quasi-resonant switch, diode  $D_2$  operates with zero-voltage switching, while transistor  $Q_1$  and diode  $D_1$  operate with zero-current switching.

## Summary of key points

---

4. In the zero-voltage-switching quasi-resonant switch, the transistor  $Q_1$  and diode  $D_1$  operate with zero-voltage switching, while diode  $D_2$  operates with zero-current switching.
5. Full-wave versions of the quasi-resonant switches exhibit very simple control characteristics: the conversion ratio  $\mu$  is essentially independent of load current. However, these converters exhibit reduced efficiency at light load, due to the large circulating currents. In addition, significant switching loss is incurred due to the recovered charge of diode  $D_1$ .
6. Half-wave versions of the quasi-resonant switch exhibit conversion ratios that are strongly dependent on the load current. These converters typically operate with wide variations of switching frequency.
7. In the zero-voltage-switching multiresonant switch, all semiconductor devices operate with zero-voltage switching. In consequence, very low switching loss is observed.

## Summary of key points

---

8. In the quasi-square-wave zero-voltage-switching resonant switches, all semiconductor devices operate with zero-voltage switching, and with peak voltages equal to those of the parent PWM converter. The switch conversion ratio is restricted to the range  $0.5 \leq \mu \leq 1$ .
9. The small-signal ac models of converters containing resonant switches are similar to the small-signal models of their parent PWM converters. The averaged switch modeling approach can be employed to show that the quantity  $d(t)$  is simply replaced by  $\mu(t)$ .
10. In the case of full-wave quasi-resonant switches,  $\mu$  depends only on the switching frequency, and therefore the transfer function poles and zeroes are identical to those of the parent PWM converter.
11. In the case of half-wave quasi-resonant switches, as well as other types of resonant switches, the conversion ratio  $\mu$  is a strong function of the switch terminal quantities  $v_1$  and  $i_2$ . This leads to effective feedback, which modifies the poles, zeroes, and gains of the transfer functions.



## Appendix 2

### Magnetics Design Tables

Geometrical data for several standard ferrite core shapes are listed here. The geometrical constant  $K_g$  is a measure of core size, useful for designing inductors and transformers which attain a given copper loss [1]. The  $K_g$  method for inductor design is described in Chapter 13.  $K_g$  is defined as

$$K_g = \frac{A_c^2 W_A}{MLT} \quad (\text{A2.1})$$

where  $A_c$  is the core cross-sectional area,  $W_A$  is the window area, and  $MLT$  is the winding mean-length-per-turn. The geometrical constant  $K_{gfe}$  is a similar measure of core size, which is useful for designing ac inductors and transformers when the total copper plus core loss is constrained. The  $K_{gfe}$  method for magnetics design is described in Chapter 14.  $K_{gfe}$  is defined as

$$K_{gfe} = \frac{W_A A_c^{2(1-1/\beta)}}{MLT l_e^{2/\beta}} u(\beta) \quad (\text{A2.2})$$


where  $l_e$  is the core mean magnetic path length, and  $\beta$  is the core loss exponent:

$$P_{fe} = K_{fe} B_{\max}^\beta \quad (\text{A2.3})$$

For modern ferrite materials,  $\beta$  typically lies in the range 2.6 to 2.8. The quantity  $u(\beta)$  is defined as


$$u(\beta) = \left[ \left( \frac{\beta}{2} \right)^{-\left( \frac{\beta}{\beta+2} \right)} + \left( \frac{\beta}{2} \right)^{\left( \frac{2}{\beta+2} \right)} \right]^{-\left( \frac{\beta+2}{\beta} \right)} \quad (\text{A2.4})$$

$u(\beta)$  is equal to 0.305 for  $\beta = 2.7$ . This quantity varies by roughly 5% over the range  $2.6 \leq \beta \leq 2.8$ . Values of  $K_{gfe}$  are tabulated for  $\beta = 2.7$ ; variation of  $K_{gfe}$  over the range  $2.6 \leq \beta \leq 2.8$  is typically quite small.

 **A2.1 Pot core data**


Core type	Geometrical constant	Geometrical constant	Cross-sectional area	Bobbin winding area	Mean length per turn	Magnetic path length	Thermal resistance	Core weight
(AH) (mm)	$K_{g_5}$ cm <sup>5</sup>	$K_{gfe}$ cm <sup>x</sup>	$A_c$ (cm <sup>2</sup> )	$W_A$ (cm <sup>2</sup> )	MLT (cm)	$l_m$ (cm)	$R_{th}$ (°C/W)	(g)
704	$0.738 \cdot 10^{-6}$	$1.61 \cdot 10^{-6}$	0.070	$0.22 \cdot 10^{-3}$	1.46	1.0		0.5
905	$0.183 \cdot 10^{-3}$	$256 \cdot 10^{-6}$	0.101	0.034	1.90	1.26		1.0
1107	$0.667 \cdot 10^{-3}$	$554 \cdot 10^{-6}$	0.167	0.055	2.30	1.55		1.8
1408	$2.107 \cdot 10^{-3}$	$1.1 \cdot 10^{-3}$	0.251	0.097	2.90	2.00	100	3.2
1811	$9.45 \cdot 10^{-3}$	$2.6 \cdot 10^{-3}$	0.433	0.187	3.71	2.60	60	7.3
2213	$27.1 \cdot 10^{-3}$	$4.9 \cdot 10^{-3}$	0.635	0.297	4.42	3.15	38	13
2616	$69.1 \cdot 10^{-3}$	$8.2 \cdot 10^{-3}$	0.948	0.406	5.28	3.75	30	20
3019	0.180	$14.2 \cdot 10^{-3}$	1.38	0.587	6.20	4.50	23	34
3622	0.411	$21.7 \cdot 10^{-3}$	2.02	0.748	7.42	5.30	19	57
4229	1.15	$41.1 \cdot 10^{-3}$	2.66	1.40	8.60	6.81	13.5	104

### A2.2 EE core data

 


Core type	Geometrical constant	Geometrical constant	Cross-sectional area	Bobbin winding area	Mean length per turn	Magnetic path length	Core weight
(A) (mm)	$K_{g_5}$ $\text{cm}^5$	$K_{gfe}$ $\text{cm}^x$	$A_c$ $(\text{cm}^2)$	$W_A$ $(\text{cm}^2)$	$MLT$ (cm)	$l_m$ (cm)	(g)
EE12	$0.731 \cdot 10^{-3}$	$0.458 \cdot 10^{-3}$	0.14	0.085	2.28	2.7	2.34
EE16	$2.02 \cdot 10^{-3}$	$0.842 \cdot 10^{-3}$	0.19	0.190	3.40	3.45	3.29
EE19	$4.07 \cdot 10^{-3}$	$1.3 \cdot 10^{-3}$	0.23	0.284	3.69	3.94	4.83
EE22	$8.26 \cdot 10^{-3}$	$1.8 \cdot 10^{-3}$	0.41	0.196	3.99	3.96	8.81
EE30	$85.7 \cdot 10^{-3}$	$6.7 \cdot 10^{-3}$	1.09	0.476	6.60	5.77	32.4
EE40	0.209	$11.8 \cdot 10^{-3}$	1.27	1.10	8.50	7.70	50.3
EE50	0.909	$28.4 \cdot 10^{-3}$	2.26	1.78	10.0	9.58	116
EE60	1.38	$36.4 \cdot 10^{-3}$	2.47	2.89	12.8	11.0	135
EE70/68/19	5.06	$127 \cdot 10^{-3}$	3.24	6.75	14.0	9.0	280


### A2.3 EC core data

 

Core type	Geometrical constant	Geometrical constant	Cross-sectional area	Bobbin winding area	Mean length per turn	Magnetic path length	Thermal resistance	Core weight
(A) (mm)	$K_{g_5}$ $\text{cm}^5$	$K_{gfe}$ $\text{cm}^x$	$A_c$ $(\text{cm}^2)$	$W_A$ $(\text{cm}^2)$	$MLT$ (cm)	$l_m$ (cm)	$R_{th}$ (°C/W)	(g)
EC35	0.131	$9.9 \cdot 10^{-3}$	0.843	0.975	5.30	7.74	18.5	35.5
EC41	0.374	$19.5 \cdot 10^{-3}$	1.21	1.35	5.30	8.93	16.5	57.0
EC52	0.914	$31.7 \cdot 10^{-3}$	1.80	2.12	7.50	10.5	11.0	111
EC70	2.84	$56.2 \cdot 10^{-3}$	2.79	4.71	12.9	14.4	7.5	256

 **A2.4 ETD core data**

Core type	Geometrical constant	Geometrical constant	Cross-sectional area	Bobbin winding area	Mean length per turn	Magnetic path length	Thermal resistance	Core weight
(A) (mm)	$K_{g_5}$ $\text{cm}^5$	$K_{gfe}$ $\text{cm}^x$	$A_c$ $(\text{cm}^2)$	$W_A$ $(\text{cm}^2)$	$MLT$ (cm)	$l_m$ (cm)	$R_{th}$ (°C/W)	(g)
ETD29	0.0978	$8.5 \cdot 10^{-3}$	0.76	0.903	5.33	7.20		30
ETD34	0.193	$13.1 \cdot 10^{-3}$	0.97	1.23	6.00	7.86	19	40
ETD39	0.397	$19.8 \cdot 10^{-3}$	1.25	1.74	6.86	9.21	15	60
ETD44	0.846	$30.4 \cdot 10^{-3}$	1.74	2.13	7.62	10.3	12	94
ETD49	1.42	$41.0 \cdot 10^{-3}$	2.11	2.71	8.51	11.4	11	124

 **A2.5 PQ core data**


Core type	Geometrical constant	Geometrical constant	Cross-sectional area	Bobbin winding area	Mean length per turn	Magnetic path length	Core weight
$(A_l/2D)$ (mm)	$K_{g_5}$ $\text{cm}^5$	$K_{gfe}$ $\text{cm}^x$	$A_c$ $(\text{cm}^2)$	$W_A$ $(\text{cm}^2)$	$MLT$ (cm)	$l_m$ (cm)	(g)
PQ 20/16	$22.4 \cdot 10^{-3}$	$3.7 \cdot 10^{-3}$	0.62	0.256	4.4	3.74	13
PQ 20/20	$33.6 \cdot 10^{-3}$	$4.8 \cdot 10^{-3}$	0.62	0.384	4.4	4.54	15
PQ 26/20	$83.9 \cdot 10^{-3}$	$7.2 \cdot 10^{-3}$	1.19	0.333	5.62	4.63	31
PQ 26/25	0.125	$9.4 \cdot 10^{-3}$	1.18	0.503	5.62	5.55	36
PQ 32/20	0.203	$11.7 \cdot 10^{-3}$	1.70	0.471	6.71	5.55	42
PQ 32/30	0.384	$18.6 \cdot 10^{-3}$	1.61	0.995	6.71	7.46	55
PQ 35/35	0.820	$30.4 \cdot 10^{-3}$	1.96	1.61	7.52	8.79	73
PQ 40/40	1.20	$39.1 \cdot 10^{-3}$	2.01	2.50	8.39	10.2	95

**A2.6 American wire gauge data**

AWG#	Bare area, $10^{-3} \text{ cm}^2$	Resistance, $10^{-6} \Omega/\text{cm}$	Diameter, cm
0000	1072.3	1.608	1.168
000	850.3	2.027	1.040
00	674.2	2.557	0.927
0	534.8	3.224	0.825
1	424.1	4.065	0.735
2	336.3	5.128	0.654
3	266.7	6.463	0.583
4	211.5	8.153	0.519
5	167.7	10.28	0.462
6	133.0	13.0	0.411
7	105.5	16.3	0.366
8	83.67	20.6	0.326
9	66.32	26.0	0.291
10	52.41	32.9	0.267
11	41.60	41.37	0.238
12	33.08	52.09	0.213
13	26.26	69.64	0.190
14	20.02	82.80	0.171
15	16.51	104.3	0.153
16	13.07	131.8	0.137
17	10.39	165.8	0.122
18	8.228	209.5	0.109
19	6.531	263.9	0.0948
20	5.188	332.3	0.0874
21	4.116	418.9	0.0785
22	3.243	531.4	0.0701
23	2.508	666.0	0.0632
24	2.047	842.1	0.0566
25	1.623	1062.0	0.0505
26	1.280	1345.0	0.0452
27	1.021	1687.6	0.0409
28	0.8046	2142.7	0.0366
29	0.6470	2664.3	0.0330
30	0.5067	3402.2	0.0294
31	0.4013	4294.6	0.0267
32	0.3242	5314.9	0.0241
33	0.2554	6748.6	0.0236
34	0.2011	8572.8	0.0191
35	0.1589	10849	0.0170
36	0.1266	13608	0.0152
37	0.1026	16801	0.0140
38	0.08107	21266	0.0124
39	0.06207	27775	0.0109
40	0.04869	35400	0.0096
41	0.03972	43405	0.00863
42	0.03166	54429	0.00762
43	0.02452	70308	0.00685

# Appendix 3: Averaged switch modeling of a CCM SEPIC

*SEPIC example: write circuit with switch network explicitly identified*

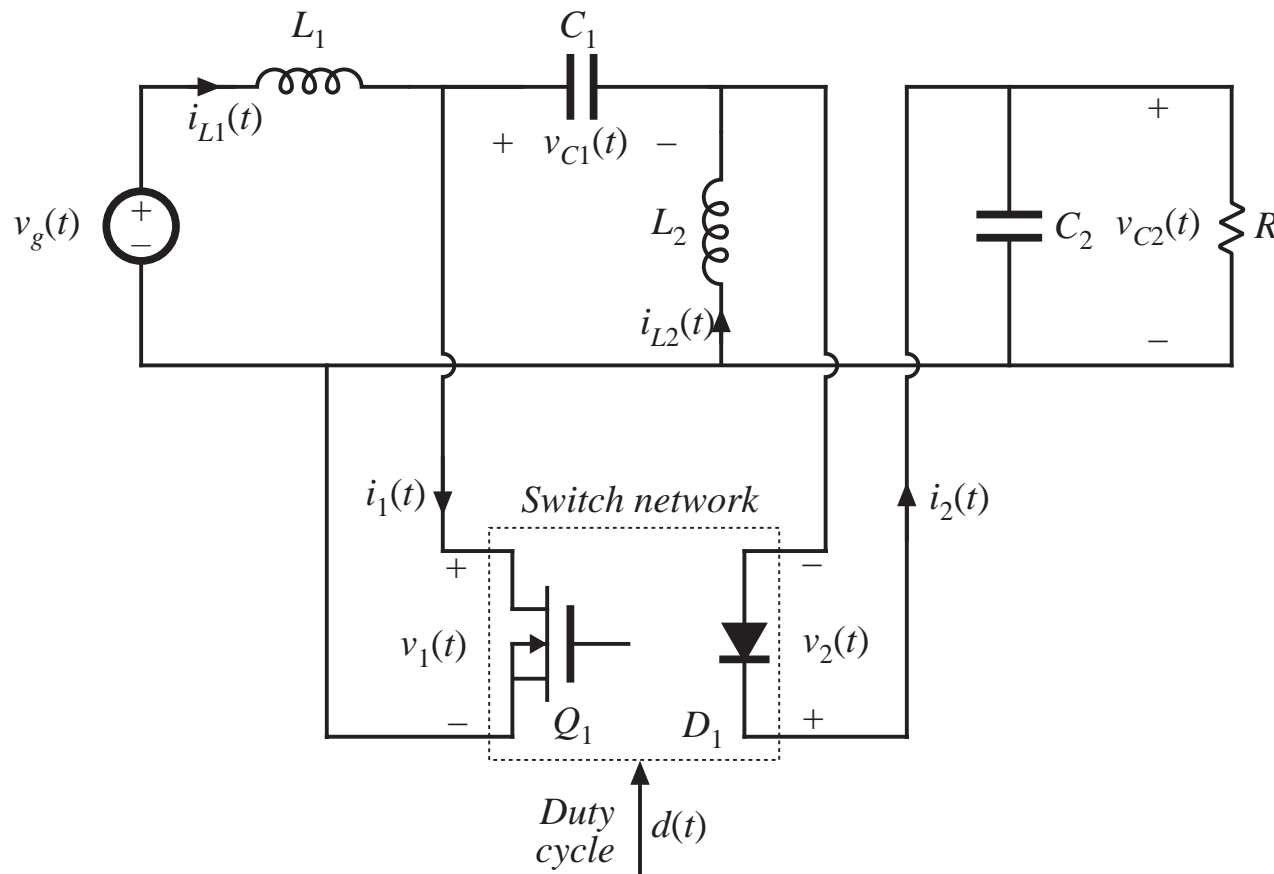

*Appendix 3: Averaged switch modeling  
of a CCM SEPIC*



# A few points regarding averaged switch modeling

---

- The switch network can be defined arbitrarily, as long as its terminal voltages and currents are independent, and the switch network contains no reactive elements.
- It is **not** necessary that some of the switch network terminal quantities coincide with inductor currents or capacitor voltages of the converter, or be nonpulsating.
- The object is simply to write the averaged equations of the switch network; i.e., to express the average values of half of the switch network terminal waveforms as functions of  
the average values of the remaining switch network terminal waveforms,  
and  
the control input.

# SEPIC CCM waveforms

*Sketch terminal waveforms of switch network*

  

*Appendix 3: Averaged switch modeling  
of a CCM SEPIC*



# Expressions for average values of switch network terminal waveforms

---

*Use small ripple approximation*

$$\langle v_1(t) \rangle_{T_s} = d'(t) \left( \langle v_{C1}(t) \rangle_{T_s} + \langle v_{C2}(t) \rangle_{T_s} \right)$$

$$\langle i_1(t) \rangle_{T_s} = d(t) \left( \langle i_{L1}(t) \rangle_{T_s} + \langle i_{L2}(t) \rangle_{T_s} \right)$$

$$\langle v_2(t) \rangle_{T_s} = d(t) \left( \langle v_{C1}(t) \rangle_{T_s} + \langle v_{C2}(t) \rangle_{T_s} \right)$$

$$\langle i_2(t) \rangle_{T_s} = d'(t) \left( \langle i_{L1}(t) \rangle_{T_s} + \langle i_{L2}(t) \rangle_{T_s} \right)$$

*Need next to eliminate the capacitor voltages and inductor currents from these expressions, to write the equations of the switch network.*

# Derivation of switch network equations (Algebra steps)

We can write


$$\langle i_{L1}(t) \rangle_{T_s} + \langle i_{L2}(t) \rangle_{T_s} = \frac{\langle i_1(t) \rangle_{T_s}}{d(t)}$$

$$\langle v_{C1}(t) \rangle_{T_s} + \langle v_{C2}(t) \rangle_{T_s} = \frac{\langle v_2(t) \rangle_{T_s}}{d(t)}$$

Hence


$$\langle v_1(t) \rangle_{T_s} = \frac{d'(t)}{d(t)} \langle v_2(t) \rangle_{T_s}$$
 
$$\langle i_2(t) \rangle_{T_s} = \frac{d'(t)}{d(t)} \langle i_1(t) \rangle_{T_s}$$




# Steady-state switch model: Dc transformer model

---

 
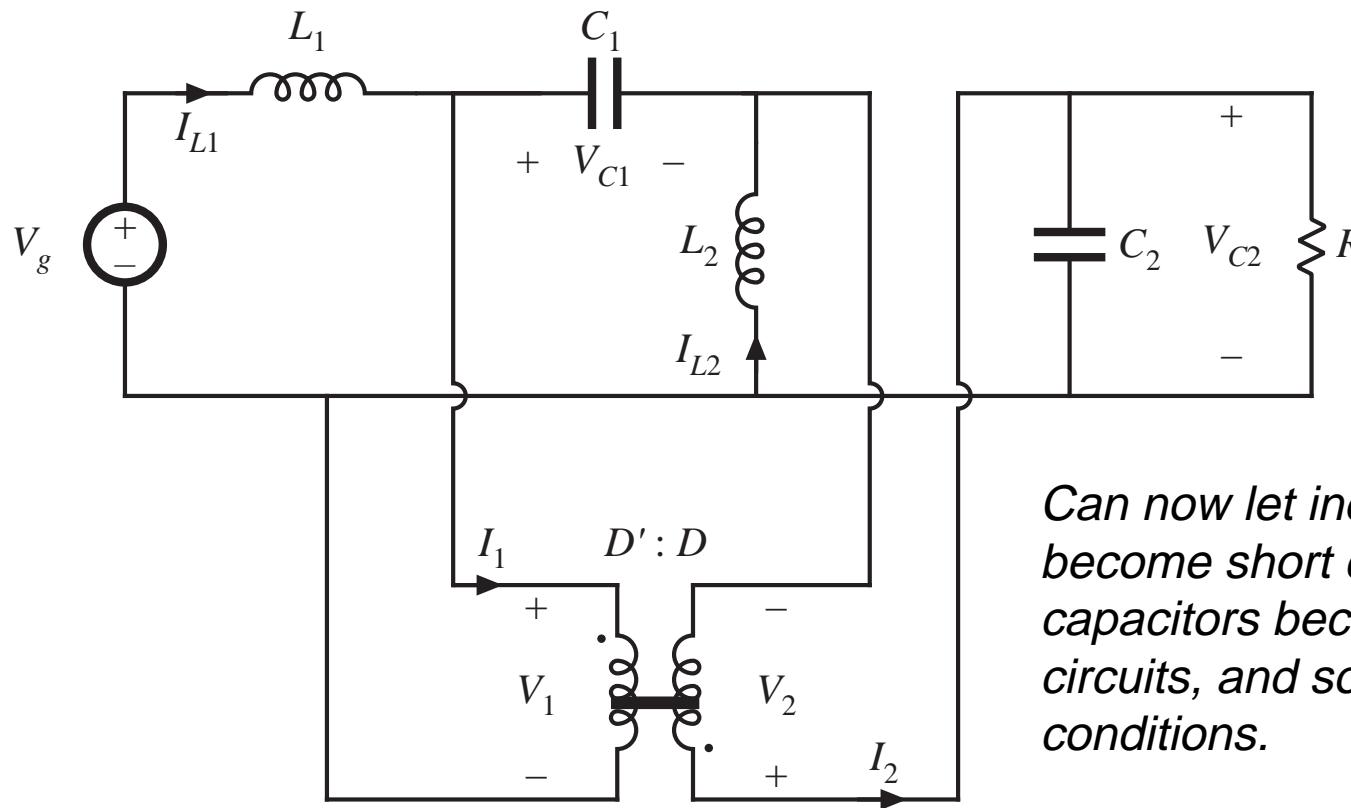
# Steady-state CCM SEPIC model

*Replace switch network with dc transformer model*



*Can now let inductors become short circuits, capacitors become open circuits, and solve for dc conditions.*

# Small-signal model

Perturb and linearize the switch network averaged waveforms, as usual:

$$\begin{aligned}d(t) &= D + \hat{d}(t) \\ \langle v_1(t) \rangle_{T_s} &= V_1 + \hat{v}_1(t) \\ \langle i_1(t) \rangle_{T_s} &= I_1 + \hat{i}_1(t) \\ \langle v_2(t) \rangle_{T_s} &= V_2 + \hat{v}_2(t) \\ \langle i_2(t) \rangle_{T_s} &= I_2 + \hat{i}_2(t)\end{aligned}$$

Voltage equation becomes

$$(D + \hat{d})(V_1 + \hat{v}_1) = (D' - \hat{d})(V_2 + \hat{v}_2)$$

Eliminate nonlinear terms and solve for  $v_1$  terms:

$$\begin{aligned}(V_1 + \hat{v}_1) &= \frac{D'}{D} (V_2 + \hat{v}_2) - \hat{d} \left( \frac{V_1 + V_2}{D} \right) \\ &= \frac{D'}{D} (V_2 + \hat{v}_2) - \hat{d} \left( \frac{V_1}{DD'} \right)\end{aligned}$$

*Appendix 3: Averaged switch modeling  
of a CCM SEPIC*

# Linearization, continued

---

Current equation becomes


$$(D + \hat{d})(I_2 + \hat{i}_2) = (D' - \hat{d})(I_1 + \hat{i}_1)$$

Eliminate nonlinear terms  
and solve for  $i_2$  terms:

$$\begin{aligned}(I_2 + \hat{i}_2) &= \frac{D'}{D} (I_1 + \hat{i}_1) - \hat{d} \left( \frac{I_1 + I_2}{D} \right) \\ &= \frac{D'}{D} (I_1 + \hat{i}_1) - \hat{d} \left( \frac{I_2}{DD'} \right)\end{aligned}$$

 
# Switch network: Small-signal ac model

*Reconstruct equivalent circuit in the usual manner:*


 
# Small-signal ac model of the CCM SEPIC

*Replace switch network with small-signal ac model:*



*Can now solve this  
model to determine  
ac transfer functions*