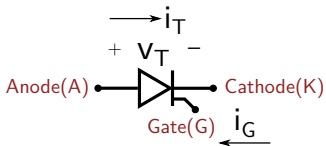


Thyristors: Silicon Controlled Rectifier (SCR)

- ▶ Switches of “Thyristor” family: p-n-p-n structure
- ▶ Silicon controlled rectifier (SCR) is the most popular [Other members of thyristor family are: Asymmetrical SCR, Reverse conducting thyristor, Light-fired thyristor, Gate turn-off thyristor (GTO), Integrated gate commutated thyristor (IGCT), Triode AC switch (TRIAC), Static induction thyristor, MOS controlled thyristor (MCT)]
- ▶ SCR:- First solid state power semiconductor device developed to function as a controlled switch (1957), supporting large voltages and currents
- ▶ SCR is still ‘the’ controlled switch with the highest power handling capability - Large voltage and current ratings: 12kV/1.5kA, 8.5kV/4.2kA, 6kV/6kA
- ▶ High power (MW) applications: Synchronous motor drives, HVDC transmission, Flexible AC transmission, Locomotives for transportation
- ▶ Low and medium power applications: Battery chargers, Uninterruptible power supply (UPS), Welding
- ▶ Popular manufactures: Mitsubishi, ABB, Fuji Electric, Toshiba, Vishay




Silicon Controlled Rectifier (SCR)




Disc/Hockey puck



Silicon Controlled Rectifier (SCR)

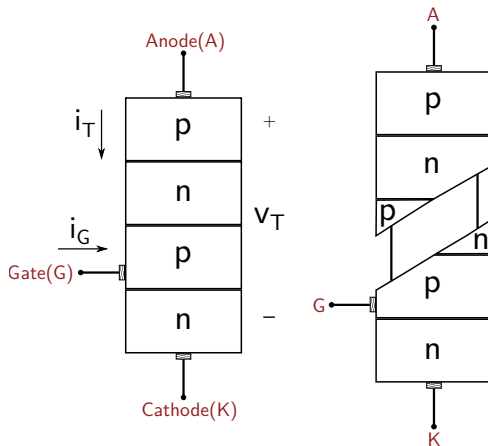



Basic structure of SCR

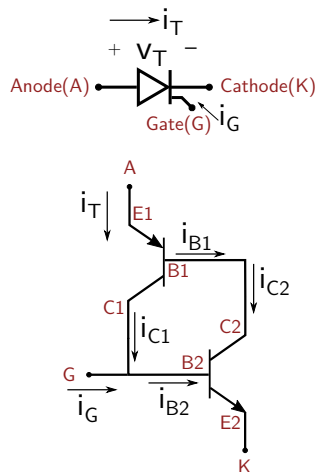

Two transistor model of SCR
to explain the regenerative turn-ON process



V-I characteristics of an SCR

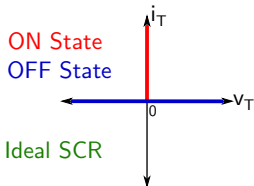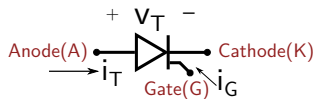


Ideal SCR



Practical SCR:

Finite ON-state loss (conduction loss)
Negligible OFF-state loss (blocking loss)
OFF to ON: turn-ON loss
ON to OFF: turn-OFF loss
(due to reverse recovery)


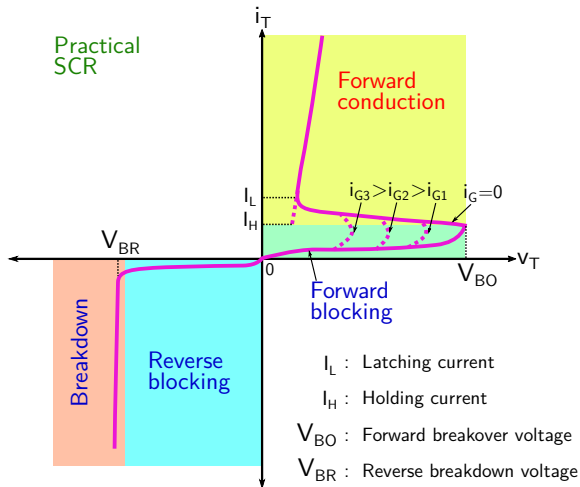
Additional time required to regain
forward blocking capability
after reverse recovery



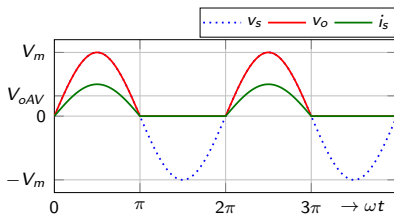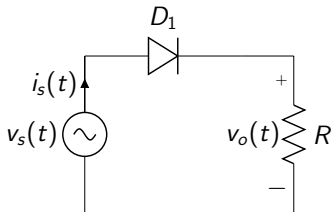1-phase half-wave rectifiers: Uncontrolled vs controlled



$$V_{oAV} = \frac{V_m}{\pi}$$

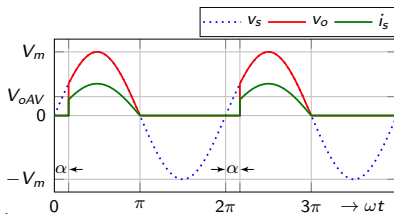
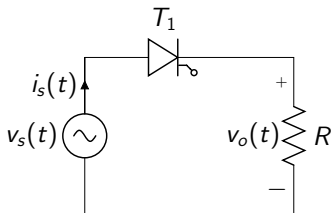


$$V_{oAV} = \frac{V_m}{\pi} \left(\frac{1 + \cos \alpha}{2} \right)$$



Firing angle α - Represents the switching delay with respect to a "natural" firing instant that would be valid for a circuit consisting of diodes.



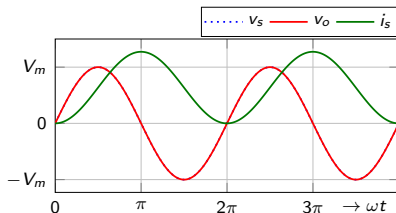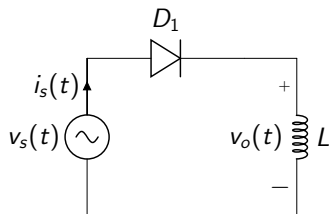1-phase half-wave rectifiers: Uncontrolled vs controlled



$$V_{oAV} = 0$$

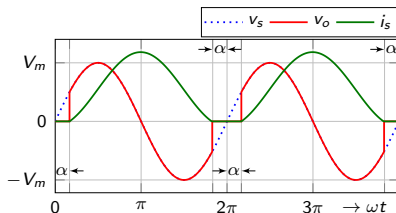
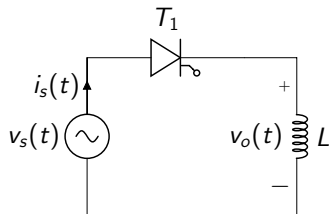


$$V_{oAV} = 0$$




The diagram shows a series circuit. On the left is an AC voltage source $v_s(t)$ with a tilde symbol inside a circle. Above the source is the current $i_s(t)$ with an upward arrow. To the right of the source is a diode D_1 pointing to the right. Further right is a node with a '+' sign. A horizontal wire connects this node to an inductor L (represented by a coil). After the inductor, the wire goes down to a resistor R (represented by a zigzag line). The other end of the resistor is connected back to the bottom wire of the AC source. The output voltage $v_o(t)$ is indicated between the node after the diode (marked '+') and the bottom wire (marked '-').
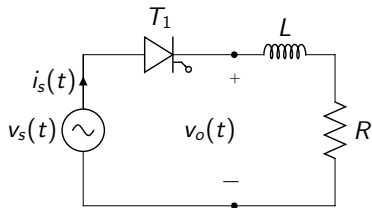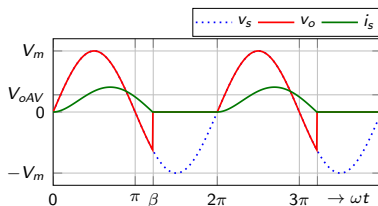
$$V_{oAV} = \frac{V_m}{\pi} \left(\frac{1 - \cos \beta}{2} \right)$$





$$\text{Average of } i_s = \frac{V_{oAV}}{R}$$
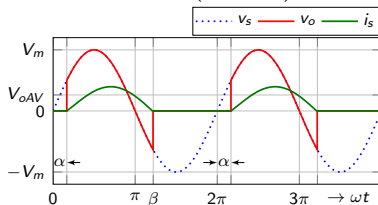
$$V_{oAV} = \frac{V_m}{\pi} \left(\frac{\cos \alpha - \cos \beta}{2} \right)$$





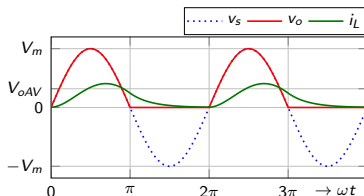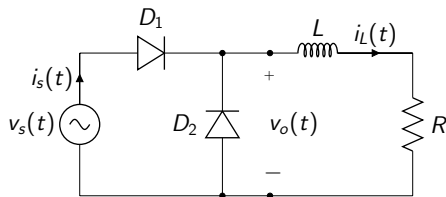1-phase half-wave rectifiers: Uncontrolled vs controlled



$$\text{Average of } i_L = \frac{V_{oAV}}{R}$$

$$V_{oAV} = \frac{V_m}{\pi}$$

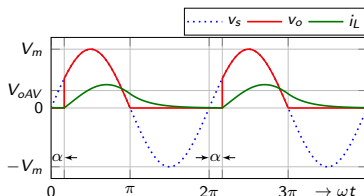
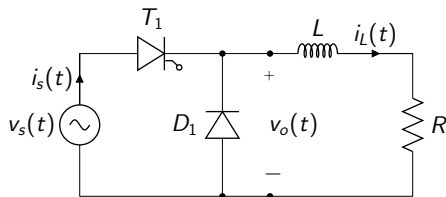


$$\text{Average of } i_L = \frac{V_{oAV}}{R}$$



$$V_{oAV} = \frac{V_m}{\pi} \left(\frac{1 + \cos \alpha}{2} \right)$$



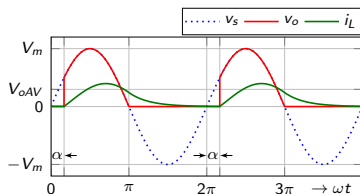
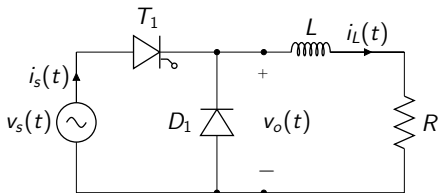
1-phase half-wave controlled rectifier with free-wheeling diode



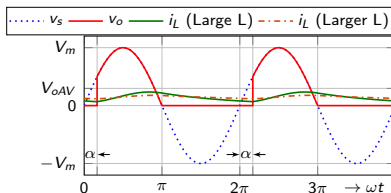
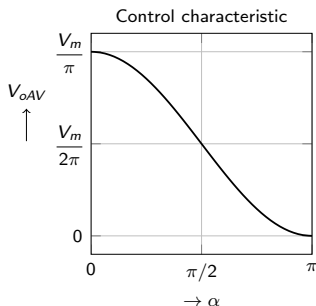
$$V_{oAV} = \frac{V_m}{\pi} \left(\frac{1 + \cos \alpha}{2} \right)$$





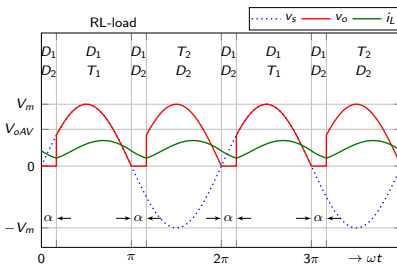
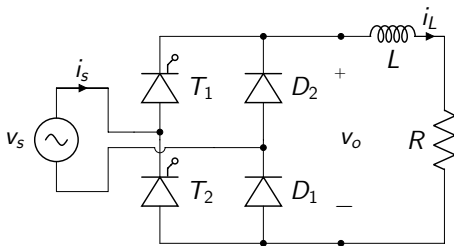
1-phase semi-controlled bridge rectifier: Circuit 1


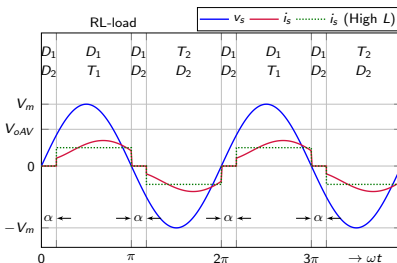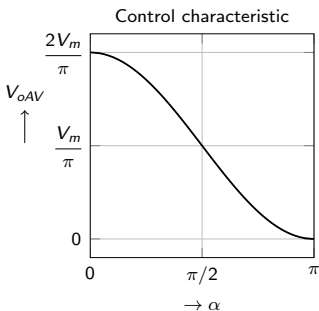
$$V_{oAV} = \frac{V_m}{\pi} (1 + \cos \alpha)$$




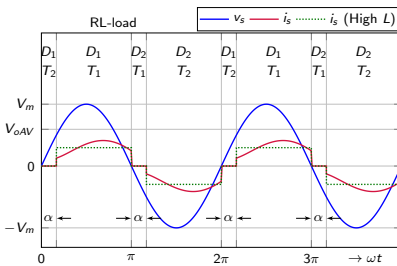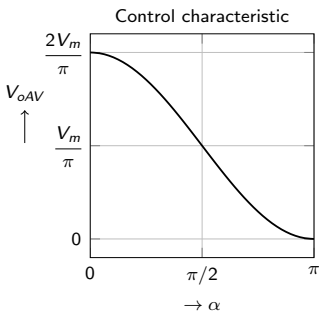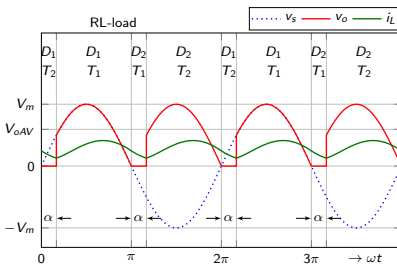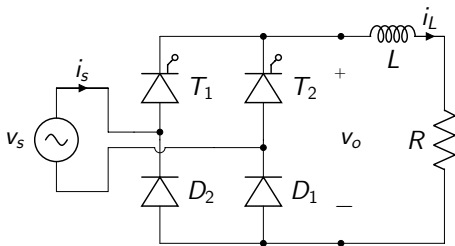1-phase semi-controlled bridge rectifier: Circuit 2



1-phase semi-controlled bridge rectifier: Quality of source current i_s

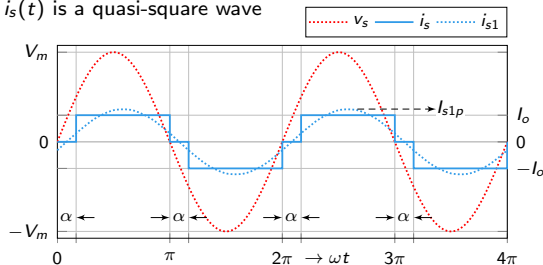Highly inductive (Constant I_o) load $\Rightarrow i_s(t)$ is a quasi-square wave



- ▶ Displacement power factor

$$DPF = \cos \frac{\alpha}{2}$$

- ▶ RMS value of the source current

$$I_{sRMS} = I_o \sqrt{1 - \frac{\alpha}{\pi}}$$

- ▶ RMS value of the fundamental component $I_{s1RMS} = \frac{2\sqrt{2}}{\pi} I_o \cos \frac{\alpha}{2}$



- ▶ Distortion factor $DF_1 = 2 \cos \frac{\alpha}{2} \sqrt{\frac{2}{\pi(\pi - \alpha)}}$

- ▶ Total power factor $PF = (1 + \cos \alpha) \sqrt{\frac{2}{\pi(\pi - \alpha)}}$



- ▶ $i_s(t)$ doesn't contain even harmonics



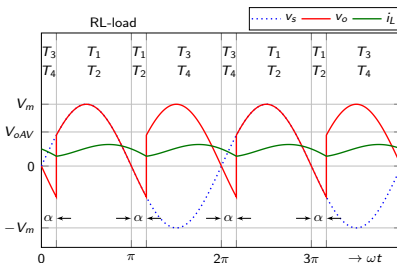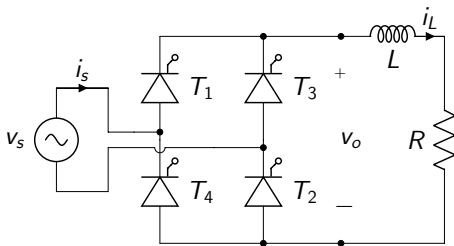1-phase fully-controlled bridge rectifier: Continuous load current



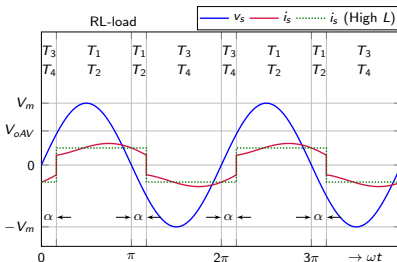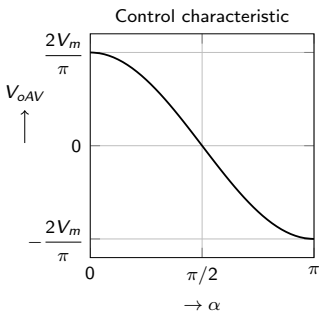
$$V_{oAV} = \frac{2V_m}{\pi} \cos \alpha$$



1-phase fully-controlled bridge rectifier: Quality of source current i_s

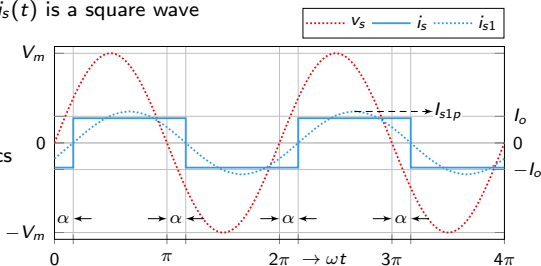Highly inductive (Constant I_o) load $\Rightarrow i_s(t)$ is a square wave



- ▶ $i_s(t)$ doesn't contain even harmonics
- ▶ Displacement power factor
 $DPF = \cos \alpha$
- ▶ RMS value of the source current
 $I_{sRMS} = I_o$
- ▶ RMS value of the fundamental component


$$I_{s1RMS} = \frac{4I_o}{\pi} \frac{1}{\sqrt{2}} = 0.9I_o$$

- ▶ RMS value of the n^{th} harmonic component $I_{snRMS} = \frac{I_{s1RMS}}{n}$
- ▶ $DF_1 = 0.9 \Rightarrow$ power factor $PF = 0.9 \cos \alpha$
- ▶ Total harmonic distortion $I_{sTHD} = 48.43\%$



1-phase fully-controlled bridge: Output characteristic

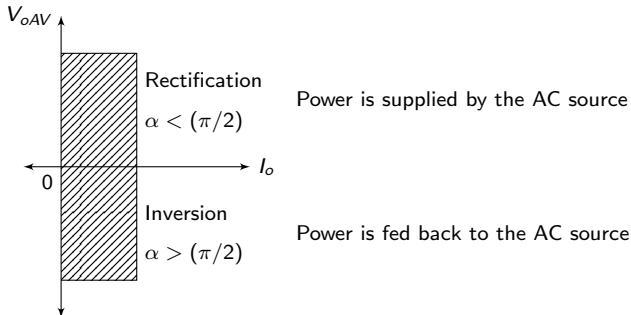A fully-controlled bridge can operate in two quadrants of the ($V_{oAV} - I_o$) plane





The circuit is commonly referred to as '1-phase fully-controlled converter' since it can be operated either as a rectifier or as an inverter. The term 'inverter' is used in the context of power flow from the DC-side to the AC-side; not referring to DC-AC conversion.


Inversion mode requires a source of energy to be present on the DC side, for example a battery or a DC motor (back e.m.f.).



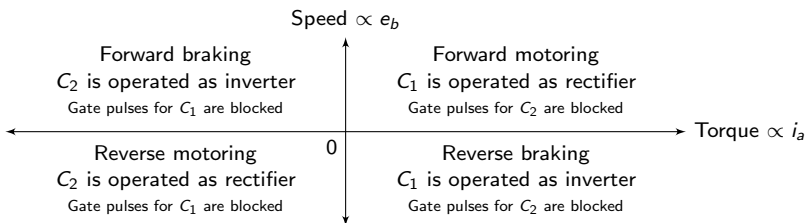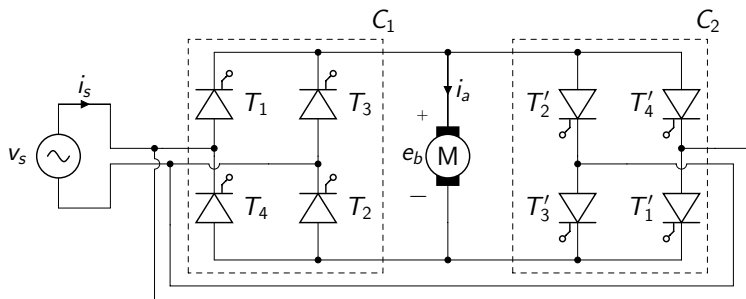1-phase dual converter: 4-quadrant DC-motor drive



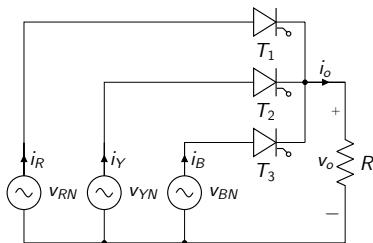3-ph half-wave (3-pulse) controlled rectifier: R-Load




Average output voltage V_{oAV}


$$= \frac{1}{(2\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin(\omega t) d(\omega t)$$

$$= \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha$$

$$0 \leq \alpha \leq \frac{\pi}{6}$$

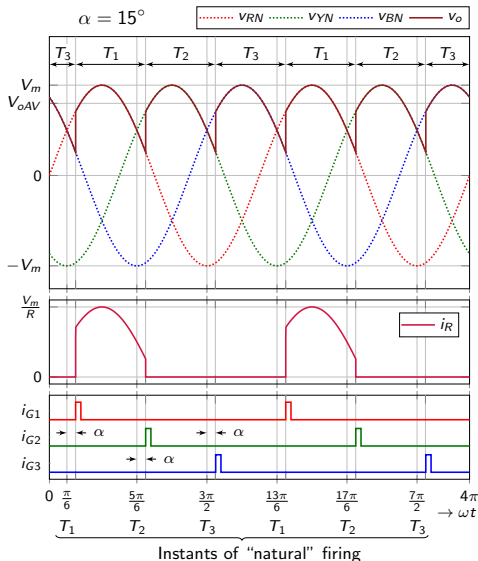

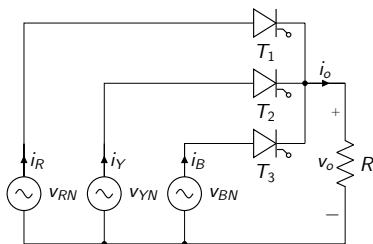3-ph half-wave (3-pulse) controlled rectifier: R-Load




Average output voltage V_{oAV}


$$= \frac{1}{(2\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin(\omega t) d(\omega t)$$

$$= \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha$$

$$0 \leq \alpha \leq \frac{\pi}{6}$$

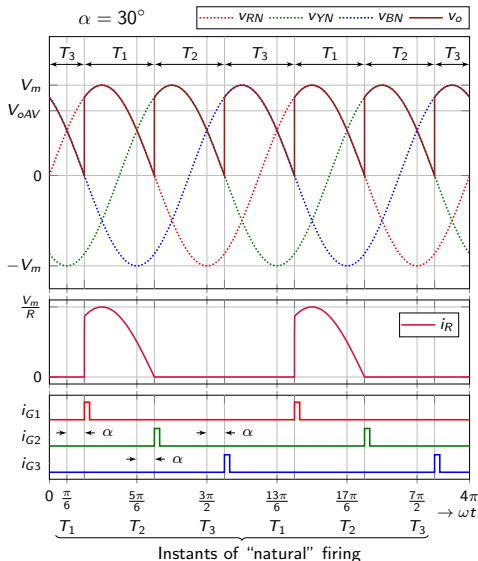

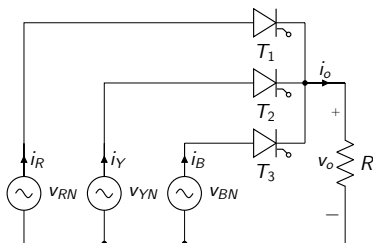3-ph half-wave (3-pulse) controlled rectifier: R-Load




Average output voltage V_{oAV}


$$= \frac{1}{(2\pi/3)} \int_{\pi/6 + \alpha}^{\pi} V_m \sin(\omega t) d(\omega t)$$

$$= \frac{3V_m}{2\pi} \left[1 + \cos\left(\alpha + \frac{\pi}{6}\right) \right]$$
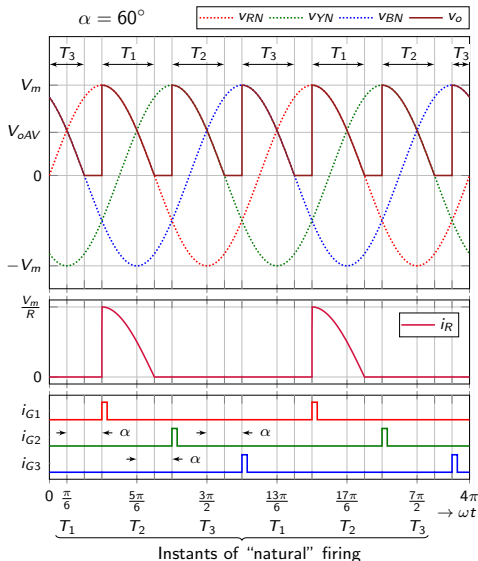
$$\frac{\pi}{6} \leq \alpha \leq \frac{5\pi}{6}$$



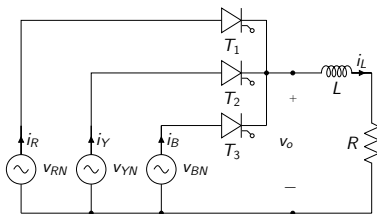3-ph half-wave (3-pulse) controlled rectifier: RL-Load




Average output voltage V_{oAV}


$$= \frac{1}{(2\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin(\omega t) d(\omega t)$$

$$= \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha$$

Valid if i_L is continuous, for any α

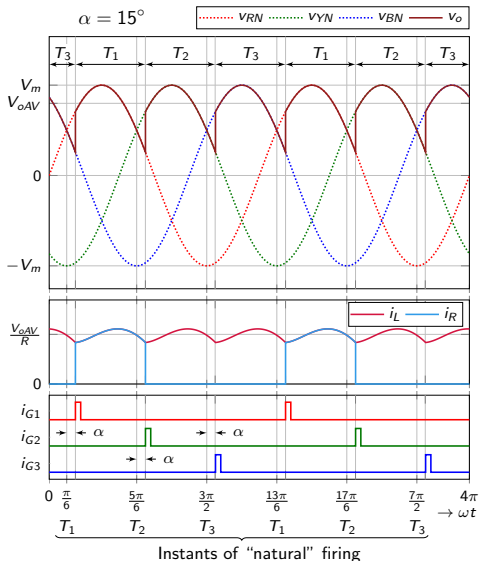

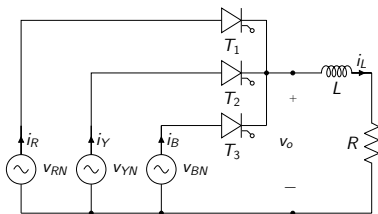3-ph half-wave (3-pulse) controlled rectifier: RL-Load




Average output voltage V_{oAV}


$$= \frac{1}{(2\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin(\omega t) d(\omega t)$$

$$= \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha$$

Valid if i_L is continuous, for any α

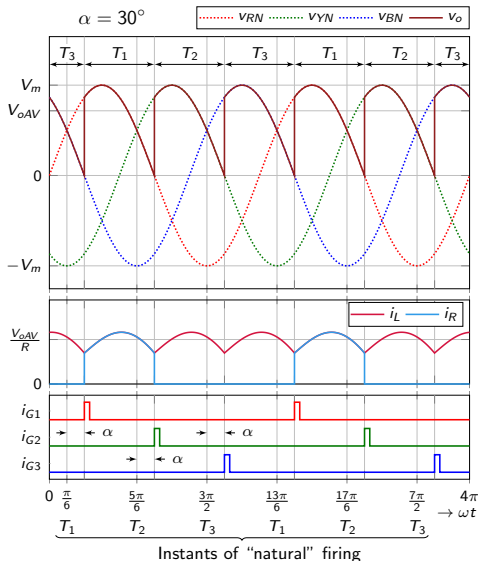

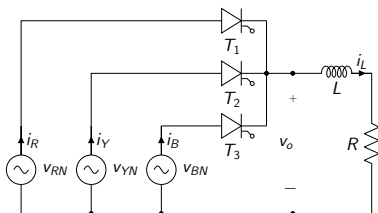3-ph half-wave (3-pulse) controlled rectifier: RL-Load




Average output voltage V_{oAV}


$$= \frac{1}{(2\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_m \sin(\omega t) d(\omega t)$$

$$= \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha$$

Valid if i_L is continuous, for any α

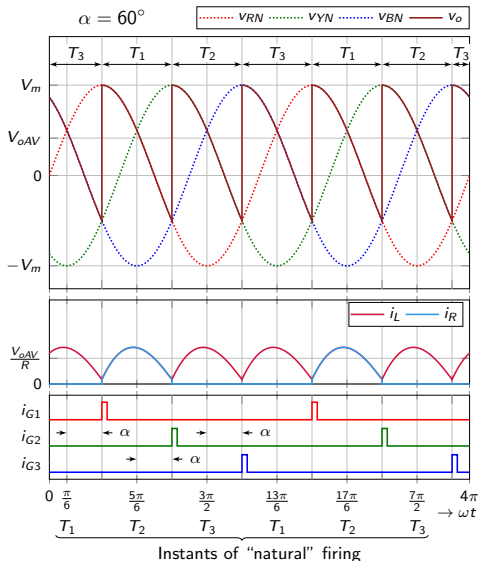

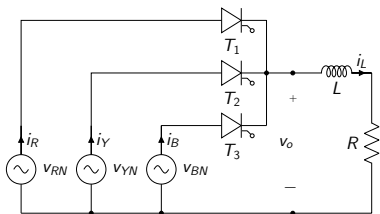3-ph half-wave (3-pulse) controlled rectifier: RL-Load




Average output voltage V_{oAV}

$$= \frac{1}{(2\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\pi + \beta} V_m \sin(\omega t) d(\omega t)$$

$$= \frac{3V_m}{2\pi} \left[\cos \beta + \cos \left(\frac{\pi}{6} + \alpha \right) \right]$$


If i_L is discontinuous,

V_{oAV} depends on β

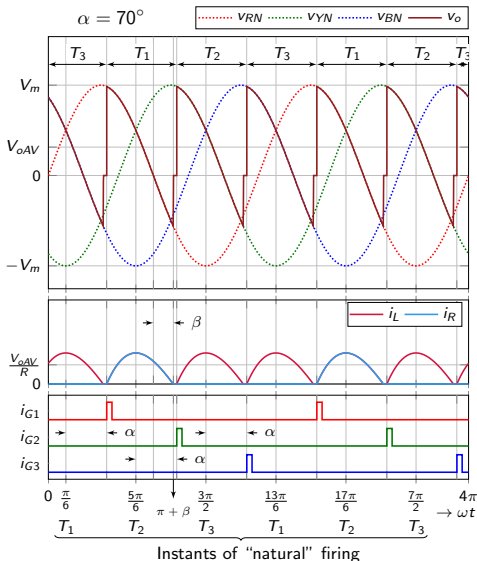

3-ph half-wave (3-pulse) controlled rectifier: RL-Load

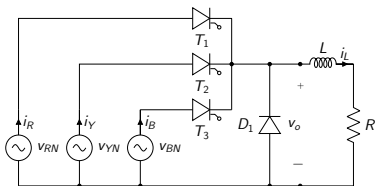Free-wheeling diode avoids negative excursions of v_o




Average output voltage V_{oAV}

$$= \frac{1}{(2\pi/3)} \int_{\pi/6 + \alpha}^{\pi} V_m \sin(\omega t) d(\omega t)$$

$$= \frac{3V_m}{2\pi} \left[1 + \cos\left(\alpha + \frac{\pi}{6}\right) \right]$$

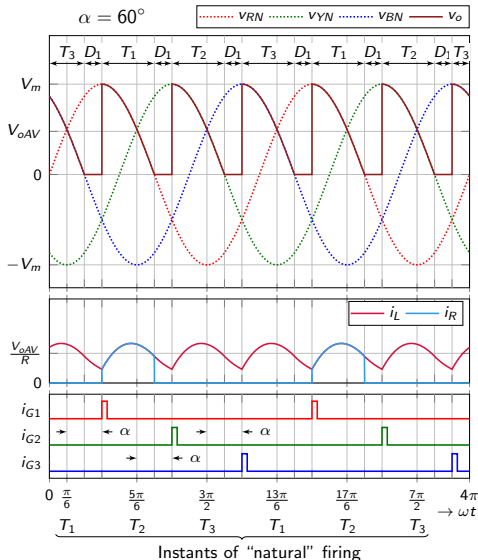
$$\frac{\pi}{6} \leq \alpha \leq \frac{5\pi}{6}$$




3-ph half-wave (3-pulse) controlled rectifier: Control characteristic

Average output voltage

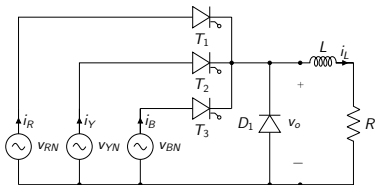
$$V_{oAV} = \begin{cases} \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha, & 0 \leq \alpha \leq \frac{\pi}{6} \\ \frac{3V_m}{2\pi} \left[1 + \cos \left(\alpha + \frac{\pi}{6} \right) \right], & \frac{\pi}{6} \leq \alpha \leq \frac{5\pi}{6} \end{cases}$$



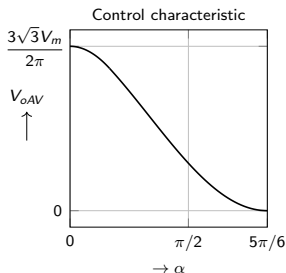Source current i_R contains DC component (finite average value)




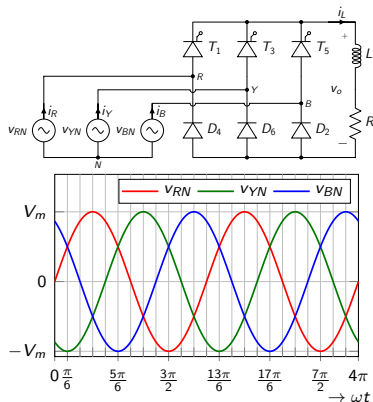3-ph semi-controlled bridge rectifier: RL-Load and $0 \leq \alpha \leq \frac{\pi}{3}$




Average output voltage V_{oAV}
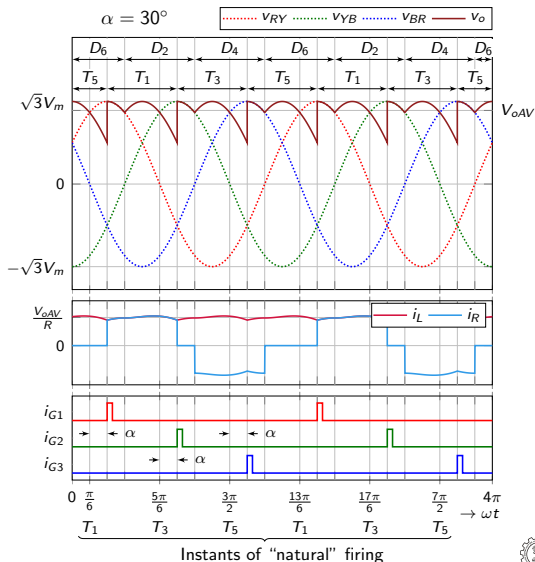
$$\begin{aligned}
 &= \frac{1}{(2\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} v_o(t) d(\omega t) \\
 &= \frac{3\sqrt{3}V_m}{2\pi} (1 + \cos \alpha)
 \end{aligned}$$




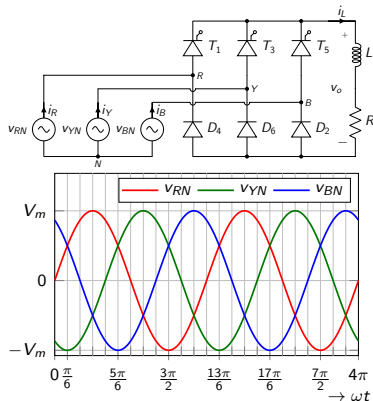3-ph semi-controlled bridge rectifier: RL-Load and $0 \leq \alpha \leq \frac{\pi}{3}$





Average output voltage V_{oAV}
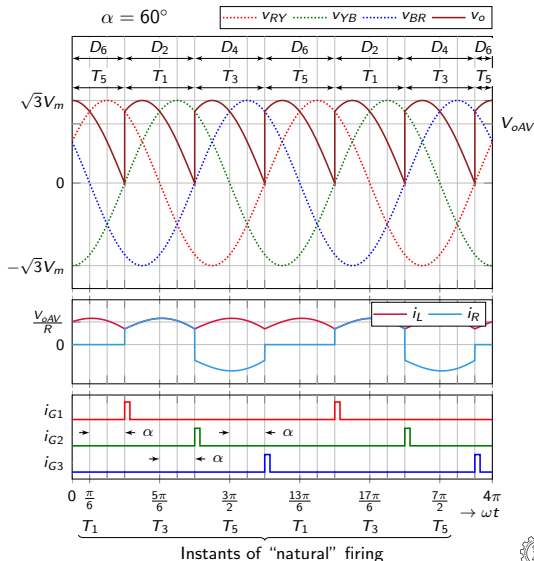
$$\begin{aligned}
 &= \frac{1}{(2\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} v_o(t) d(\omega t) \\
 &= \frac{3\sqrt{3}V_m}{2\pi} (1 + \cos \alpha)
 \end{aligned}$$




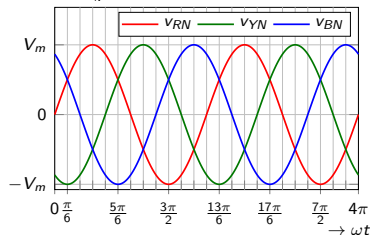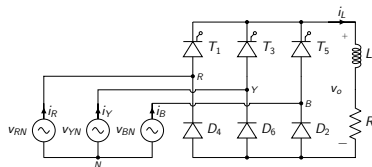3-ph semi-controlled bridge rectifier: RL-Load and $\frac{\pi}{3} \leq \alpha \leq \pi$




Average output voltage V_{oAV}
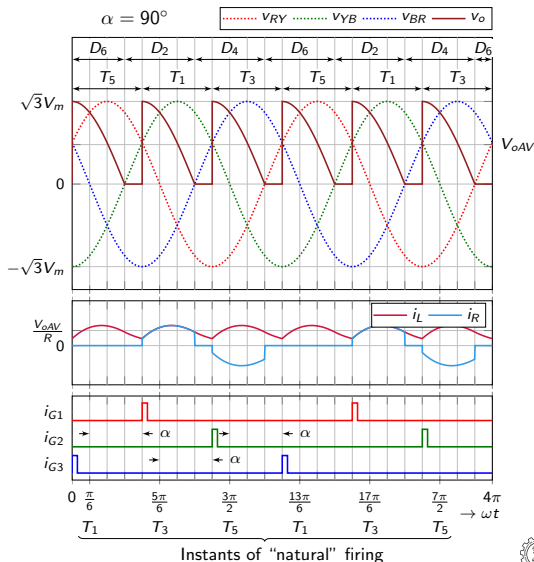
$$\begin{aligned}
 &= \frac{1}{(2\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{7\pi}{6}} v_o(t) d(\omega t) \\
 &= \frac{3\sqrt{3}V_m}{2\pi} (1 + \cos \alpha)
 \end{aligned}$$



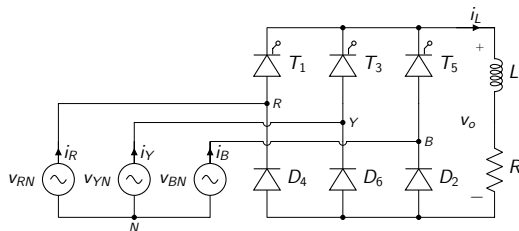
3-ph semi-controlled bridge rectifier: Control characteristic



Average output voltage

$$V_{oAV} = \frac{3\sqrt{3}V_m}{2\pi} (1 + \cos \alpha)$$

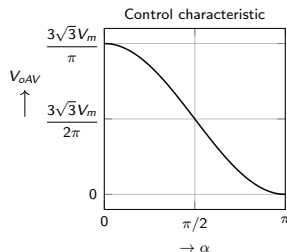
- ▶ Each switch (diode/thyristor) conducts for 120°
- ▶ Only 2 switches conduct at any given instant
- ▶ T_1 and D_2 conduct together for any α
- ▶ T_1 and D_6 conduct together only if $\alpha < 60^\circ$
- ▶ T_1 and D_4 conduct together only if $\alpha > 60^\circ$
- ▶ Similar observations can be made for other thyristors



3-ph semi-controlled bridge rectifier: Quality of source current

Highly inductive load (constant I_o)

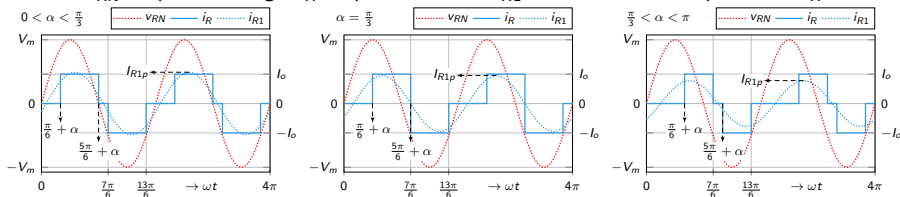v_{RN} : R-phase voltage; i_R : R-phase current; i_{R1} : Fundamental component of i_R



$$I_{RRMS} = I_o \sqrt{\frac{2}{3}} \quad \alpha \leq \frac{\pi}{3}$$

$$a_1 = \frac{2}{2\pi} \left[\int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} I_o \cos(\omega t) d(\omega t) + \int_{\frac{7\pi}{6}}^{\frac{13\pi}{6}} (-I_o) \cos(\omega t) d(\omega t) \right]$$

$$I_{RRMS} = I_o \sqrt{1 - \frac{\alpha}{\pi}} \quad \alpha > \frac{\pi}{3}$$

$$a_1 = \frac{2}{2\pi} \left[\int_{\frac{\pi}{6} + \alpha}^{\frac{7\pi}{6}} I_o \cos(\omega t) d(\omega t) + \int_{\frac{5\pi}{6} + \alpha}^{\frac{13\pi}{6}} (-I_o) \cos(\omega t) d(\omega t) \right]$$

a_1 has the same value in both the cases


Similar is the case with b_1



3-ph semi-controlled bridge rectifier: Quality of source current

Highly inductive load (constant I_o)

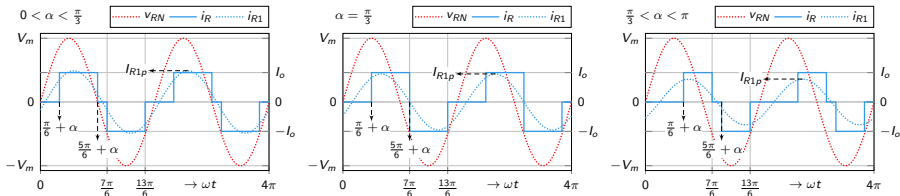v_{RN} : R-phase voltage; i_R : R-phase current; i_{R1} : Fundamental component of i_R



$$I_{RRMS} = I_o \sqrt{\frac{2}{3}} \quad \alpha \leq \frac{\pi}{3}$$

$$I_{RRMS} = I_o \sqrt{1 - \frac{\alpha}{\pi}} \quad \alpha > \frac{\pi}{3}$$

$$a_1 = -\frac{I_o \sqrt{3}}{\pi} \sin \alpha \quad \text{and} \quad b_1 = \frac{I_o \sqrt{3}}{\pi} (1 + \cos \alpha) \Rightarrow \tan^{-1} \left(\frac{a_1}{b_1} \right) = -\frac{\alpha}{2}$$

$$i_{R1} \text{ lags } v_{RN} \text{ by } \frac{\alpha}{2} \Rightarrow \text{Displacement power factor } DPF = \cos \frac{\alpha}{2}$$

$$I_{R1p} = \frac{2\sqrt{3}I_o}{\pi} \cos \frac{\alpha}{2} \quad \text{and} \quad I_{R1RMS} = \frac{I_o \sqrt{6}}{\pi} \cos \frac{\alpha}{2}$$

$$\text{Distortion factor } DF_1 = \frac{3}{\pi} \cos \frac{\alpha}{2} \quad \alpha \leq \frac{\pi}{3}$$




$$\text{Power factor } PF = \frac{3}{\pi} \cos^2 \frac{\alpha}{2} \quad \alpha \leq \frac{\pi}{3}$$

$$DF_1 = \sqrt{\frac{6}{\pi(\pi-\alpha)}} \cos \frac{\alpha}{2} \quad \alpha > \frac{\pi}{3}$$

$$PF = \sqrt{\frac{6}{\pi(\pi-\alpha)}} \cos^2 \frac{\alpha}{2} \quad \alpha > \frac{\pi}{3}$$



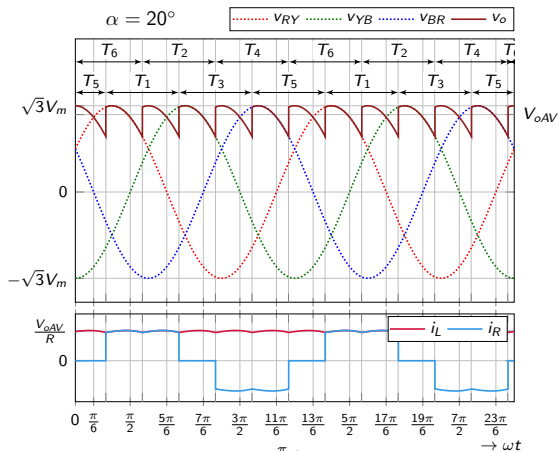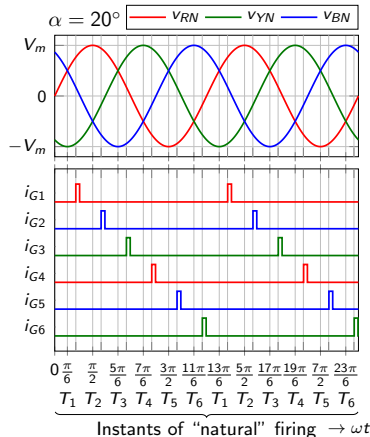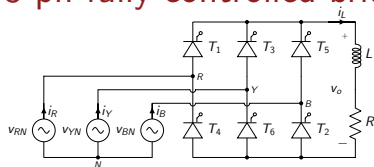3-ph fully-controlled bridge rectifier: RL-Load






$$V_{oAV} = \frac{1}{(\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} v_o(t) d(\omega t)$$

$$= \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$$



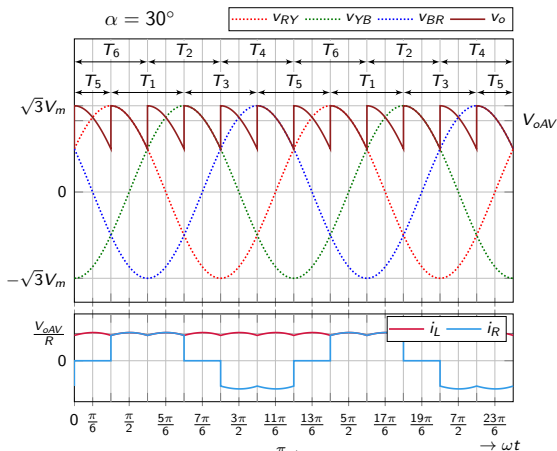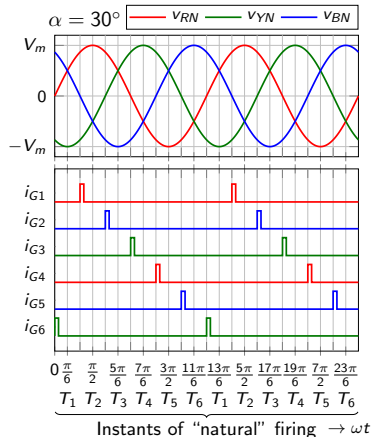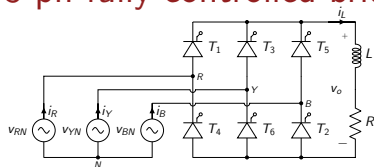3-ph fully-controlled bridge rectifier: RL-Load






$$V_{oAV} = \frac{1}{(\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} v_o(t) d(\omega t)$$

$$= \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$$



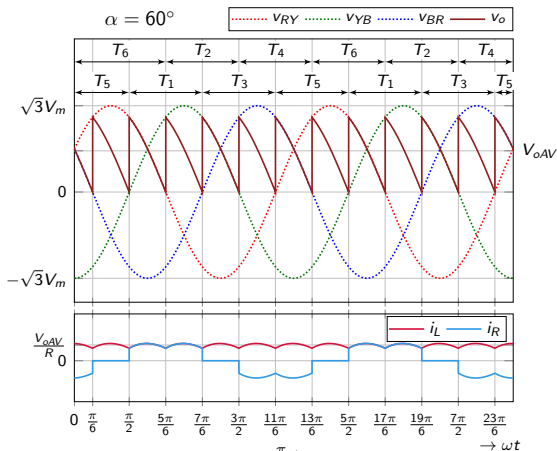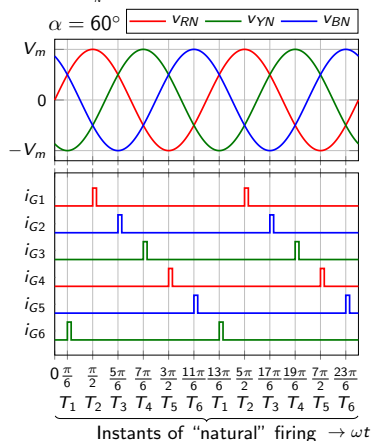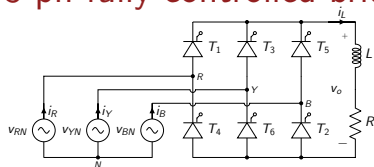3-ph fully-controlled bridge rectifier: RL-Load






$$V_{oAV} = \frac{1}{(\pi/3)} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} v_o(t) d(\omega t)$$

$$= \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$$



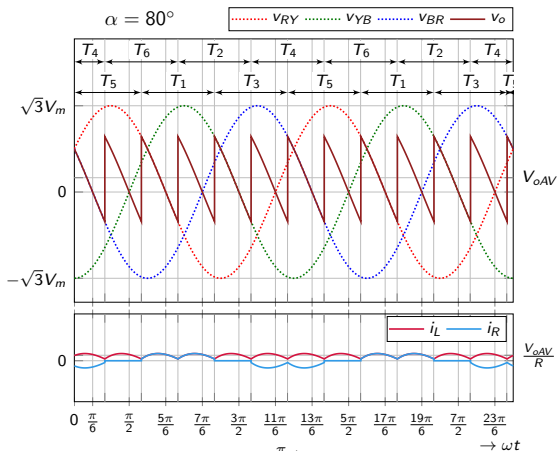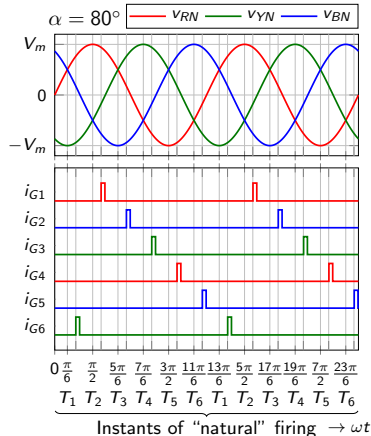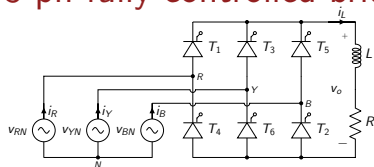3-ph fully-controlled bridge rectifier: RL-Load




$$V_{oAV} = \frac{1}{(\pi/3)} \int_{\pi/6+\alpha}^{\pi/2+\alpha} v_o(t) d(\omega t)$$

$$= \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$$



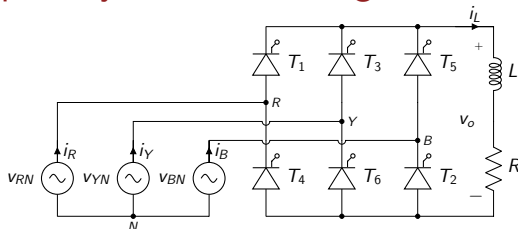
3-ph fully-controlled bridge rectifier: Continuous load current



Average output voltage


$$V_{oAV} = \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$$

- ▶ Each thyristor conducts for 120°
- ▶ Only 2 thyristors conduct at any given instant
- ▶ Operates as rectifier ($\alpha < 90^\circ$) and inverter ($\alpha > 90^\circ$)
- ▶ Average output voltage is negative when $\alpha > 90^\circ$
- ▶ Power transfer is from DC-side to AC-side when $\alpha > 90^\circ \rightarrow$ Inversion
- ▶ Energy source should be present on the DC-side to operate in inversion mode
- ▶ 3-ph dual converter can be used for 4-quadrant motor-drive applications (similar to 1-phase)

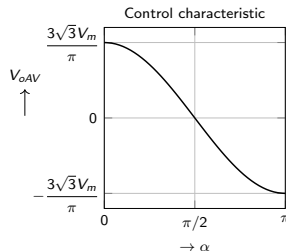

3-ph fully-controlled bridge rectifier: Quality of source current

Highly inductive (constant I_o) load

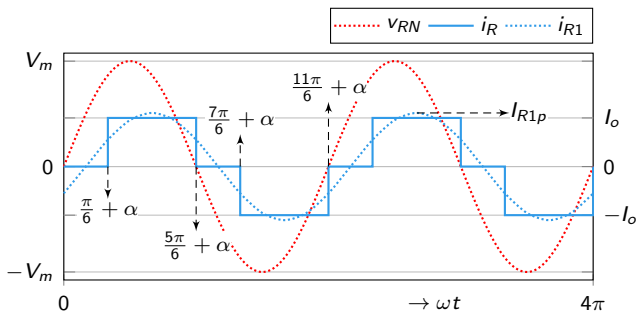

- ▶ i_{R1} lags v_{RN} by $\alpha \Rightarrow$ Displacement power factor $DPF = \cos \alpha$
- ▶ $I_{RRMS} = I_o \sqrt{\frac{2}{3}}$ and $I_{R1RMS} = I_o \frac{\sqrt{6}}{\pi} \Rightarrow DF_1 = \frac{3}{\pi}$ and $I_{RTHD} = 31.08\%$
- ▶ Total power factor $PF = \frac{3}{\pi} \cos \alpha$
- ▶ Order of harmonics in i_R is $5, 7, 11, 13, 17, 19, \dots$ or $6m \pm 1, m = 1, 2, 3, \dots$



Module 2: Summary

- ▶ Silicon Controlled Rectifier (SCR): operation and characteristics
- ▶ Half-wave and full-wave controlled rectifiers, 1-phase and 3-phase, semi-controlled and fully-controlled
- ▶ Controllable DC output voltage from a fixed AC input voltage
- ▶ Fully-controlled converters: operation as inverter (Power flow from DC-side to AC-side)
- ▶ Dual-converter: four-quadrant motor drive
- ▶ Displacement power factor is not unity; the converters draw reactive power from input
- ▶ Output DC voltage waveforms are not smooth; input current contains harmonics - distorts the voltage at point of common coupling

