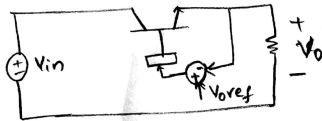



Linear regulator vs switched-mode DC-DC converter

Linear regulator



- $V_{in} > V_o$
- Excellent regulation of V_o
- Very low ripple in V_o
- Poor efficiency

Switched-mode DC-DC converter

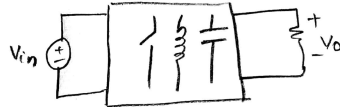

- $V_{in} > V_o$ or $V_{in} < V_o$
- Regulated V_o
- ^{low} Ripple in $V_o \Rightarrow$ large capacitor
- 100% efficiency ideally



DC-DC converters: Analysis in periodic steady-state

Analysis of DC-DC converters in periodic steady-state:

① Assumptions

- (i) switches have no ON-state voltage drops \Rightarrow No conduction loss
- (ii) switches change their states instantaneously \Rightarrow No switching loss
- (iii) Winding resistance of inductor = 0
- (iv) Equivalent series resistance (ESR) of capacitor = 0

② Approximations: Small-ripple approximation

Output voltage is constant: $v_o \approx V_o$

current through inductor is constant: $i_L \approx I_L$ (continuous conduction mode)

③ Principles

- (i) Volt-sec balance across inductor
- (ii) Amp-sec (charge) balance across capacitor
- (iii) Power balance $P_{in} = P_{out}$
- (iv) KCL, KVL

(v) flux continuity
 (vi) Volt-sec bal across each winding
 (v) & (vi) for isolated DC-DC converters




DC-DC converters: Design of circuit components

Design & choice of circuit components


component	Design/choice based on
MOSFET	Blocking voltage, Peak current, RMS current, ON-state resistance $R_{DS(on)}$, Transition times t_{on} & t_{off}
Diode	Blocking voltage, Average current, Forward voltage drop, Reverse recovery charge
Inductor	Peak-to-peak ripple current, average current, switching frequency, worst-case duty cycle, power loss
Capacitor	Voltage rating, peak-to-peak voltage ripple, RMS ripple current, ESR

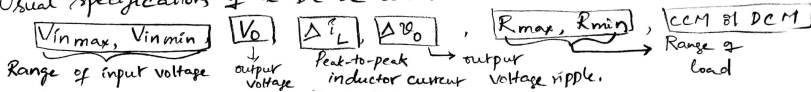Usual Specifications of a DC-DC converter



Buck (step-down) converter

Buck Converter

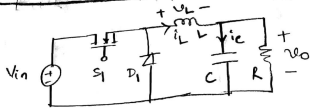

$0 < t < DT_s : S_1 \text{ ON } D_1 \text{ OFF}$
 $DT_s < t < T_s : S_1 \text{ OFF } D_1 \text{ ON}$

$$V_o = D V_{in}$$

$$\Delta i_L = \frac{V_o(1-D)T_s}{L}$$

$$\Delta v_o = \frac{\Delta i_L T_s}{8C}$$

$$T_o = 2\pi\sqrt{LC} \quad f_o = \frac{1}{T_o}$$


$$\Delta v_o \approx V_o$$

$$\Rightarrow T_s \ll T_o$$

$$f_{sw} \gg f_o$$

$$T_s = \frac{1}{f_{sw}}$$
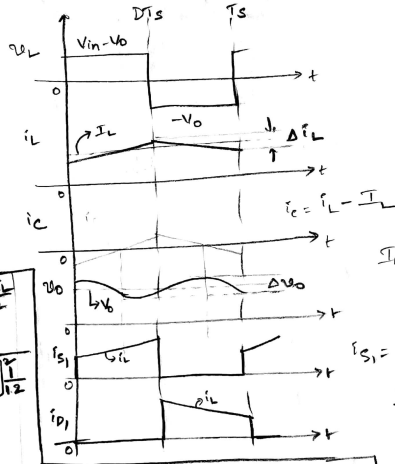
$$\begin{aligned}
 i_{S1 \text{ pk}} &= I_L + \frac{\Delta i_L}{2} \\
 i_{S1 \text{ RMS}} &= I_L \sqrt{D + \left(1 + \frac{\Delta i_L}{I_L}\right)^2 \frac{1}{12}} \\
 &\approx I_L \sqrt{D} \\
 i_{D1 \text{ av}} &= (1-D)I_L
 \end{aligned}$$



$$I_L = \frac{V_o}{R}$$

$i_{S1} = i_{in}$
 ↓
 Input current
 is
 pulsating!

$$i_{in \text{ av}} = D I_L = i_{S1 \text{ av}}$$




Buck (step-down) converter


Buck Converter:

$$\Delta i_L = \frac{V_o (1-D) T_s}{L}$$


for given V_o , T_s & L

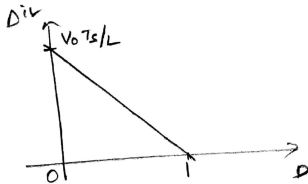

Effect of one non-ideality

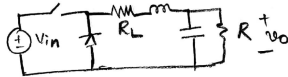
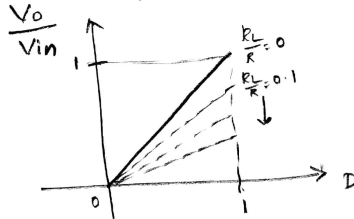
$$V_o = \frac{D V_{in}}{1 + \frac{R_L}{R}}$$




Date



Boost (step-up) converter

Boost Converter

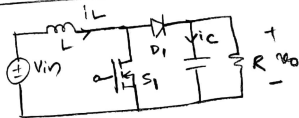


$0 < t < DT_s$: S_1 ON D_1 OFF
 $DT_s < t < T_s$: S_1 OFF D_1 ON

$$V_0 = \frac{V_{in}}{1-D}, \quad 0 < D < 1$$

$$I_L = \frac{V_0}{(1-D)R}$$

$$\Delta I_L = \frac{V_0 D (1-D) T_s}{L}$$

$$\Delta V_0 = V_0 \frac{DT_s}{RC}$$

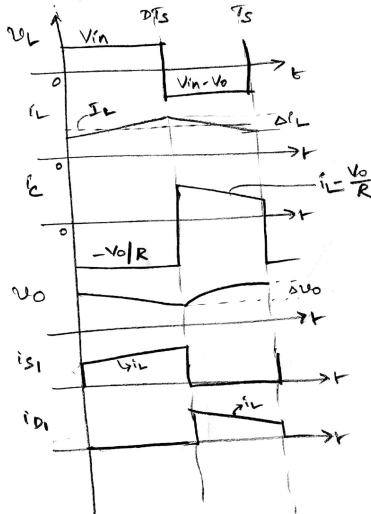

$i_{in} = I_L$
 ↓
 Input current
 i_S
 smooth.

Conte




Boost (step-up) converter


Boost converter

$$\Delta I_L = \frac{V_o D (1-D) T_s}{L}$$


for given V_o , T_s & L

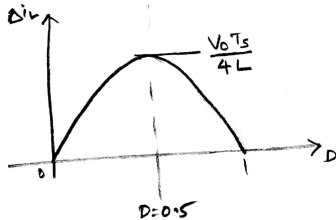

Effect of one non-ideality:

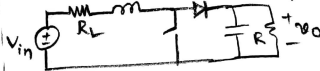
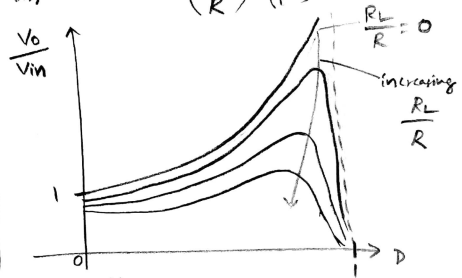
$$\frac{V_o}{V_{in}} = \frac{1}{1-D} \cdot \frac{1}{1 + \left(\frac{R_L}{R}\right) \frac{1}{(1-D)^2}}$$




Practically $D_{max} = \frac{1}{2} \pm \frac{2}{3}$.



Buck-boost converter

Buck-boost converter

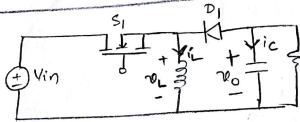

$0 < t < DT_S$: S_1 ON D_1 OFF


$DT_S < t < T_S$: S_1 OFF D_1 ON

$$V_O = \frac{-D}{1-D} V_{in} \quad 0 < D < 1$$

$$\Delta I_L = \frac{-V_O (1-D) T_S}{L}$$

$$\Delta V_O = \frac{-V_O D T_S}{RC}$$

$$I_L = \frac{-V_O}{R(1-D)}$$

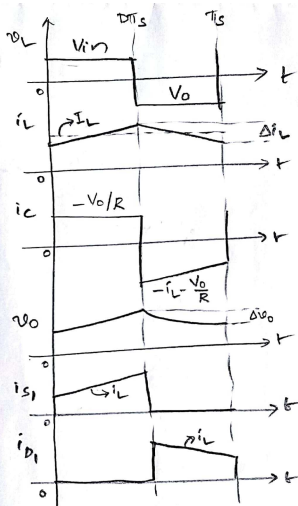

$i_{S1} = i_{in}$
↓
Input current is pulsating




Buck-boost converter


Buck-boost converter

$$\Delta i_L = \frac{-V_O (1-D) T_s}{L}$$


for given V_O, T_s, L

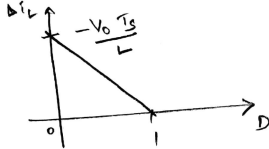

Effect of one non-ideality

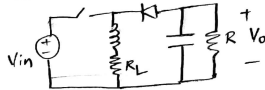

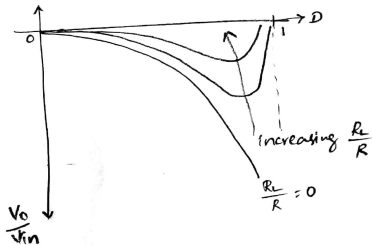
$$\frac{V_O}{V_{in}} = \frac{-D}{(1-D) \left[1 + \frac{1}{(1-D)^2} \frac{R_L}{R} \right]}$$



Ćuk converter

Ćuk Converter

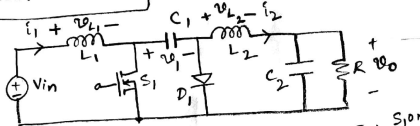

$$v_1 \approx V_1 = \frac{V_{in}}{1-D}$$

$$v_o \approx V_o = \frac{-D}{1-D} V_{in}$$

$$I_1 = \left[\frac{D}{1-D} \right]^2 \frac{V_{in}}{R} = \frac{-D}{1-D} I_2$$

$$I_2 = \frac{-D}{1-D} \frac{V_{in}}{R} = \frac{V_o}{R}$$

$\frac{V_o}{V_{in}}$ same as buck-boost

$0 < t < DT_s: S_{1ON}, D_{1OFF}$

$DT_s < t < T_s: S_{1OFF}, D_{1ON}$

Advantages of Ćuk converter compared to buck-boost

→ Non-pulsating input current

→ Isolated gate drive not needed

$$\Delta i_1 = \frac{V_{in} D T_s}{L_1} \quad \Delta v_o = \frac{\Delta i_2 T_s}{8C}$$

$$\Delta i_2 = \frac{V_{in} D T_s}{L_2}$$

$$\Delta v_o = \frac{V_{in} D^2 T_s}{2(1-D) R C_1}$$




Module 4: Summary

- ▶ Linear regulator vs switched-mode DC-DC converter
- ▶ Principles of steady-state analysis of DC-DC converters (non-isolated and isolated)
- ▶ Non-isolated DC-DC converters: Buck, Boost, Buck-Boost and Ćuk
- ▶ Switch-realization and design of the various circuit components with typical specifications
- ▶ Examples of the effect of non-idealities




1-ph 2-level voltage source inverter (VSI)

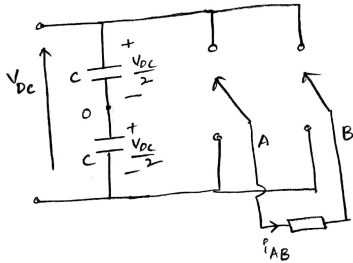Single-phase two-level voltage source inverter (VSI):



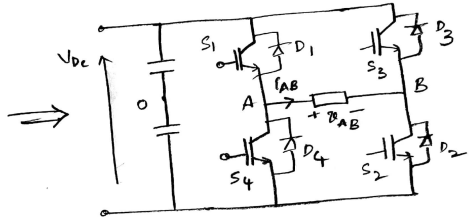Pole voltages v_{AO} , v_{BO}
 can have two levels $+\frac{V_{DC}}{2}$ or $-\frac{V_{DC}}{2}$
 \Rightarrow 2-level VSI



Switches should have
 Unidirectional voltage blocking
 Bidirectional current carrying
 capabilities


$i_{AB} > 0 \Rightarrow S_1$ or D_4 conduct

$i_{AB} < 0 \Rightarrow S_4$ or D_1 conduct



1-ph 2-level VSI: Square-wave operation

1-ph 2-level VSI:

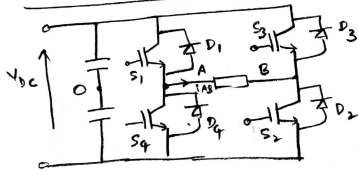

Peak value of the fundamental component of v_{AB} , denoted by

$$V_{AB,1} = \frac{4V_{dc}}{\pi}$$

Square-wave operation gives the maximum possible output voltage

But v_{AB} contains all odd harmonics!
For fixed V_{dc} , amplitude of $v_{AB,1}$ is constant


Square wave operation

Desired frequency of fundamental component or output v_{AB}

$$= f_1 ; T_1 = \frac{1}{f_1}$$

S_1 & S_2 are ON for $0 < t < \frac{T_1}{2} \Rightarrow v_{AB} = V_{dc}$

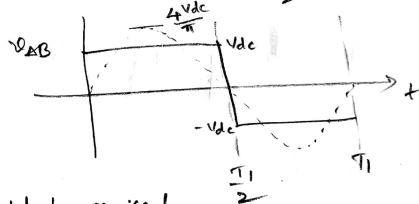S_3 , S_4 are ON for $\frac{T_1}{2} < t < T_1 \Rightarrow v_{AB} = -V_{dc}$




1-ph 2-level VSI: Pulse width modulation (PWM)

Pulse Width Modulation (PWM):

Required

- To control the output voltage with fixed DC input \rightarrow ①
- To reduce the harmonic content in the output voltage \rightarrow ②

Example:

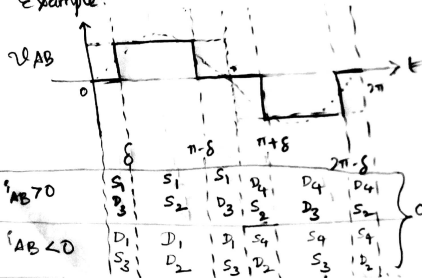

$$V_{AB,1} = \frac{4V_{DC}}{\pi} \cos \delta$$

vary $\delta \Rightarrow$ ① achieved

$$V_{AB,3n} = \frac{4V_{DC}}{\pi} \cos 3n\delta$$

No triplen

$\delta = 30^\circ \Rightarrow V_{AB,3n} = 0 \Rightarrow$ ② achieved

To achieve both ① & ②
create multiple transitions,
 $\delta_1, \delta_2, \dots$ Maintaining HWS
QWS.



1-ph 2-level VSI: Selective harmonic elimination PWM


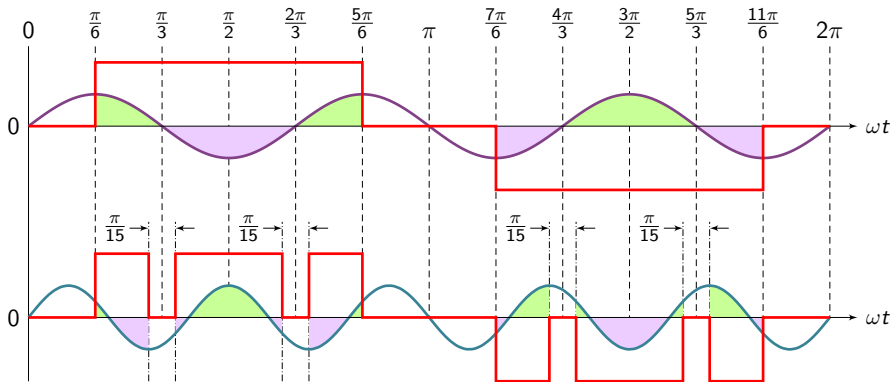


Illustration of harmonic elimination

1-ph 2-level VSI: Selective harmonic elimination PWM

Selective Harmonic elimination PWM (SHEPWM):

Example

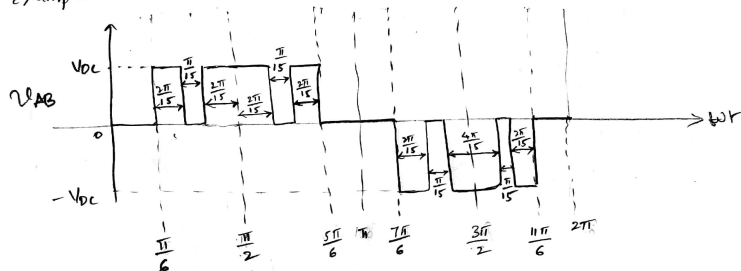

v_{AB} is free from 3^{rd} and 5^{th} harmonics.

SHEPWM is OFF-LINE PWM \Rightarrow switching instants need to be calculated separately before implementation.




1-ph 2-level VSI: Sine-triangle PWM

Real-time PWM : Sine-triangle PWM (STPWM)

1 ph-VSI : Two types of STPWM

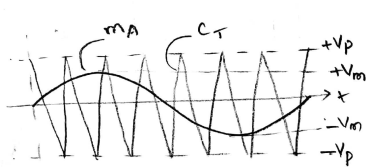- Bipolar voltage switching
- Unipolar voltage switching




$m_A = V_m \sin \omega t \rightarrow$ Modulating wave

$C_T \rightarrow$ Triangular carrier

$m_A > C_T \Rightarrow S_1 \text{ and } S_2 \text{ ON}$ $\begin{cases} i_{AB} > 0 \Rightarrow S_1 S_2 \text{ Conductor} \\ i_{AB} < 0 \Rightarrow D_1 D_2 \text{ Conductor} \end{cases}$

otherwise $S_3 \text{ and } S_4 \text{ ON}$

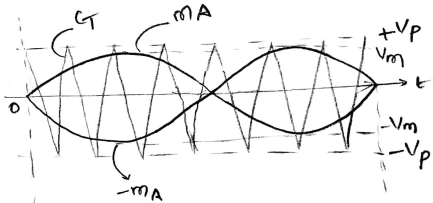$\begin{cases} i_{AB} > 0 \Rightarrow D_4 D_3 \text{ Conductor} \\ i_{AB} < 0 \Rightarrow S_4 S_3 \text{ Conductor} \end{cases}$



Both legs are switched independently

$m_A > C_T \Rightarrow S_1 \text{ ON otherwise } S_4 \text{ ON}$


$-m_A > C_T \Rightarrow S_3 \text{ ON otherwise } S_2 \text{ ON}$

→ Switch/diode conduction polarity of i_{AB} determined by the polarity of i_{AB}



1-ph 2-level VSI: Sine-triangle PWM


1-ph VSI: Bipolar Voltage Switching

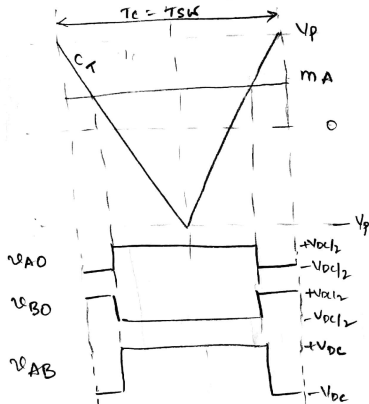

$$v_{AO(av)} = \frac{V_{dc}}{2} \frac{m_a}{V_p} \quad v_{BO(av)} = -\frac{V_{dc}}{2} \frac{m_a}{V_p}$$

$$v_{AB(av)} = v_{AO(av)} - v_{BO(av)} = V_{dc} \frac{m_a}{V_p}$$

Unipolar Voltage Switching

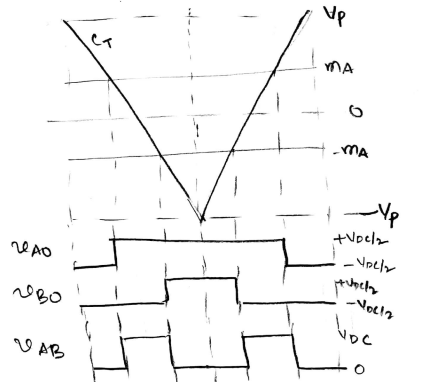

$$v_{AO(av)} = \frac{V_{dc}}{2} \frac{m_a}{V_p} \quad v_{BO(av)} = -\frac{V_{dc}}{2} \frac{m_a}{V_p}$$

$$v_{AB(av)} = V_{dc} \frac{m_a}{V_p}$$



1-ph 2-level VSI: Sine-triangle PWM



1 ph VSI : ST PWM

Bipolar Voltage Switching

Unipolar Voltage Switching

Same fundamental component $\Delta V_{AB} \Rightarrow V_{AB,1} = m_A \cdot \frac{V_{DC}}{V_p}$
 $\omega_1 = 2\pi f_1$
 $= V_{DC} \cdot \frac{V_m}{V_p} \sin \omega_1 t$

Harmonics are different

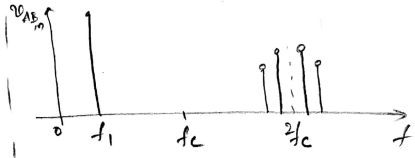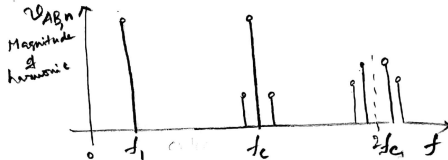

Dominant harmonic in V_{AB} is around $2f_c$ for unipolar volt. switching
 Same value of load inductance offers more impedance at $2f_c$
 \Rightarrow current wave form i_{AB} is smoother in case of unipolar volt. switching



1-ph 2-level VSI: Sine-triangle PWM vs square-wave operation

1-ph STPWM:

Fundamental voltage at output $v_{AB,1} = V_{DC} \frac{V_m}{V_p} \sin \omega t$

$\frac{V_m}{V_p}$: Modulation index \rightarrow Ratio of the peak value of modulating signal to that of carrier signal

$\frac{V_m}{V_p} \leq 1.0 \Rightarrow$ linear modulation

Maximum possible amplitude of the fundamental component of output voltage, in linear modulation = V_{DC}
Harmonics are at frequencies far from f_1



Square wave operation yields a fundamental component $\left\{ \frac{4V_{DC}}{\pi} = 1.27 V_{DC} \right.$

But v_{AB} has all odd harmonics



3-phase 2-level VSI

3-ph 2-level VSI:

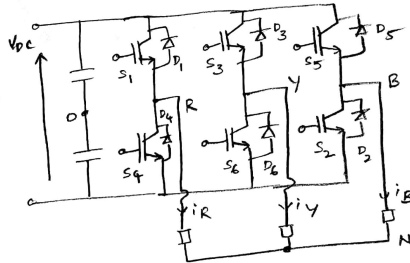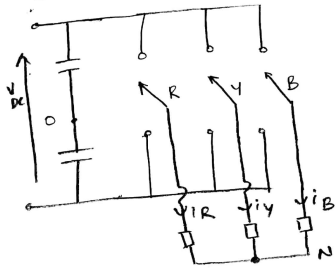


$$\left. \begin{matrix} v_{RO} \\ v_{YO} \\ v_{BO} \end{matrix} \right\} \pm \frac{V_{DC}}{2} ; \quad \begin{matrix} v_{RY} = v_{RO} - v_{YO} \\ v_{YB} = v_{YO} - v_{BO} \\ v_{BR} = v_{BO} - v_{RO} \end{matrix}$$

$$\begin{aligned} v_{RN} &= \frac{v_{RY} - v_{BR}}{3} = \frac{2v_{RO} - v_{YO} - v_{BO}}{3} \\ v_{YN} &= \frac{v_{YB} - v_{RY}}{3} = \frac{2v_{YO} - v_{BO} - v_{RO}}{3} \\ v_{BN} &= \frac{v_{BR} - v_{YB}}{3} = \frac{2v_{BO} - v_{RO} - v_{YO}}{3} \end{aligned}$$

Load is balanced; $v_{RN} + v_{YN} + v_{BN} = 0$.
 $i_R + i_Y + i_B = 0$



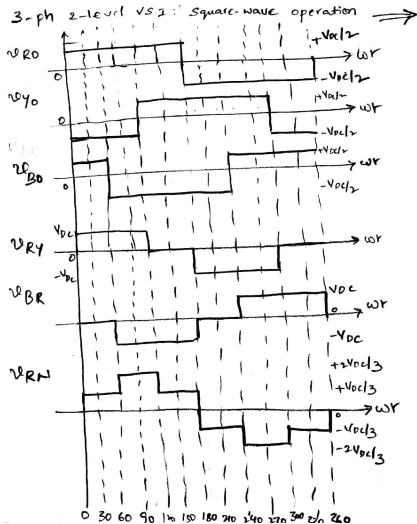3-phase 2-level VSI: Square-wave or six-step operation



⇒ Also known as Six-step operation

Fundamental component of v_{RO}

$$v_{RO,1} = \frac{4 V_{dc}}{\pi} \cdot \frac{1}{2} = \frac{2 V_{dc}}{\pi}$$

$$v_{RY,1} = \frac{4 V_{dc}}{\pi} \cos 30^\circ = \sqrt{3} \cdot \frac{2 V_{dc}}{\pi}$$

$$v_{RN,1} = \frac{2 V_{dc}}{\pi} \left\{ \begin{array}{l} \text{Max. possible amplitude} \\ \text{of phase voltage} \\ \text{or output} \end{array} \right.$$

$$v_{RO,1} = v_{RN,1}$$

v_{RO} , v_{YO} , v_{BO} } Contain all odd harmonics

v_{RY} , v_{RN} , v_{YB} , v_{YN} , v_{BR} , v_{BN} } Contain only non-triplen odd harmonics.

3rd harmonics of v_{RO} , v_{YO} , v_{BO} are in phase & get cancelled in v_{RY} , v_{YB} , v_{BR} .



3-phase 2-level VSI: Sine-triangle PWM


Sine-triangle PWM : 3ph- 2 level VSI

$$v_{RO}^{Tc} = v_{RO,1} = \frac{V_{DC}}{2} \frac{m_R}{V_p} = \frac{V_{DC}}{2} \frac{V_m}{V_p} \sin \omega_1 t$$

$$v_{YO}^{Tc} = v_{YO,1} = \frac{V_{DC}}{2} \frac{m_Y}{V_p} = \frac{V_{DC}}{2} \frac{V_m}{V_p} \sin(\omega_1 t - 120^\circ)$$

$$v_{BO}^{Tc} = v_{BO,1} = \frac{V_{DC}}{2} \frac{m_B}{V_p} = \frac{V_{DC}}{2} \frac{V_m}{V_p} \sin(\omega_1 t + 120^\circ)$$

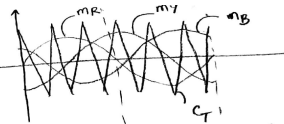Maximum amplitude of fundamental phase voltage at output $= \frac{V_{DC}}{2} = 0.5 V_{DC}$
 (VRN) in linear modulation
 Harmonics are at frequencies far from f_1



All legs are controlled independently

$$m_R > C_T \Rightarrow v_{RO} = +\frac{V_{DC}}{2} \text{ else } -\frac{V_{DC}}{2}$$

$$m_Y > C_T \Rightarrow v_{YO} = +\frac{V_{DC}}{2} \text{ else } -\frac{V_{DC}}{2}$$

$$m_B > C_T \Rightarrow v_{BO} = +\frac{V_{DC}}{2} \text{ else } -\frac{V_{DC}}{2}$$

Square wave operation gives } $\frac{2V_{DC}}{\pi} = 0.637 V_{DC}$
 fundamental component
 2 ph- voltage

But VRN has all odd non-triplen harmonics



Module 5: Summary

- ▶ Switch realization in DC-AC inverters
- ▶ Single-phase two-level voltage source inverter (VSI)
 - ▶ Square-wave operation
 - ▶ Concept of pulse width modulation (PWM)
 - ▶ Selective harmonic elimination PWM (off-line PWM)
 - ▶ Real-time PWM: sine-triangle PWM
 - ▶ Simulation examples
- ▶ Three-phase two-level VSI
 - ▶ Square-wave or six-step operation
 - ▶ Sine-triangle PWM

